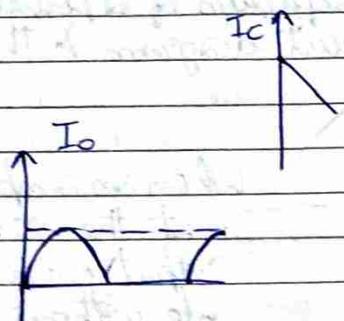


13-1-20



* Class
Amp

Sem - 4

I Analog



* Class
Amp

Electronics

II

(iv) Class C Power Amplifier:

Below the cut off point then
only collector current flows.

Unit - I


Analog Electronics - II

Shail B Jain
Linear Integrated Circuits

Books

D. Roy Choudhury

Operational Amplifier (Op-amp):

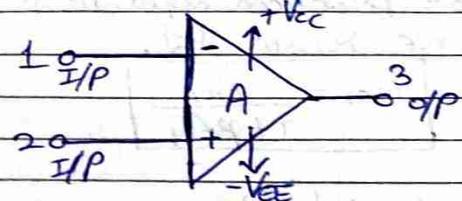

- Terminal 1 & 2 are called input terminals where terminal 1 is called inverting input terminal & terminal 2 is called non-inverting input terminal.
- Terminal 3 is the output terminal.

Characteristics of Ideal Op-Amp: (2.5 marks)

1. Open loop gain should be infinite ($A_{OL} \rightarrow \infty$).
2. Input impedance should be infinite ($Z_i \rightarrow \infty$).
3. Output impedance should be zero ($Z_o \rightarrow 0$).
4. Bandwidth should be infinite.
5. CMRR (Common Mode Rejection Ratio) should be infinite.

Explanations of all above points are on the next page.

Explanation of point ①:

For an ideal op-amp A_{OL} is infinite. It means for practical applications we must have to reduce this gain. Now we will use negative feedback for practical applications except oscillator. We know that,

$$A_{OL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

Explanation of point ②:

There is no any current flowing through terminal 1 & terminal 2 because for an ideal op-amp Z_i is infinite which means the voltage at terminal 1 & terminal 2 are always same & this is called virtual ground or virtual short.

Virtual Short/Virtual Ground:

For an open loop configuration the output voltage can be written as,

$$V_o = A_{OL} (V_+ - V_-)$$

$$\Rightarrow V_o = V_+ - V_-$$

A_{OL}

Since $A_{OL} \rightarrow \infty$

$$\Rightarrow V_o = V_+ - V_-$$

∞


$$\Rightarrow V_+ = V_-$$

i.e. Voltage at the 2nd input terminal are same

same which means they are short which is known as virtual short or virtual ground.

14.1.20 Configuration of a Op-Amp:

1. Inverting Configuration:

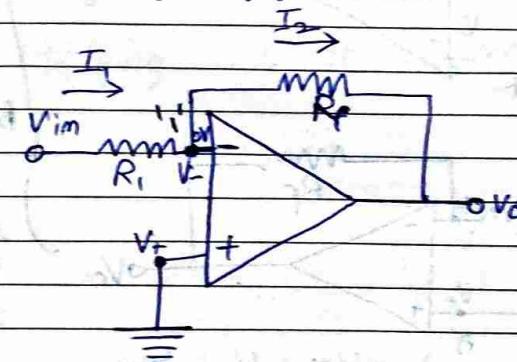

Applying KCL at node '1' we get,

$$I_1 = I_2$$

$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_o}{R_f}$$


$$\Rightarrow \frac{V_{in}}{R_1} = -\frac{V_o}{R_f} \rightarrow V_o = -\frac{R_f}{R_1} V_{in}$$

$$\text{or } \frac{V_o}{V_{in}} = -\frac{R_f}{R_1} \rightarrow \text{gain}$$

→ The -ve sign in output expression represents 180° phase shift b/w input & output.

→ $\frac{R_f}{R_1}$ is called feedback gain.

2. Non-Inverting Configuration:

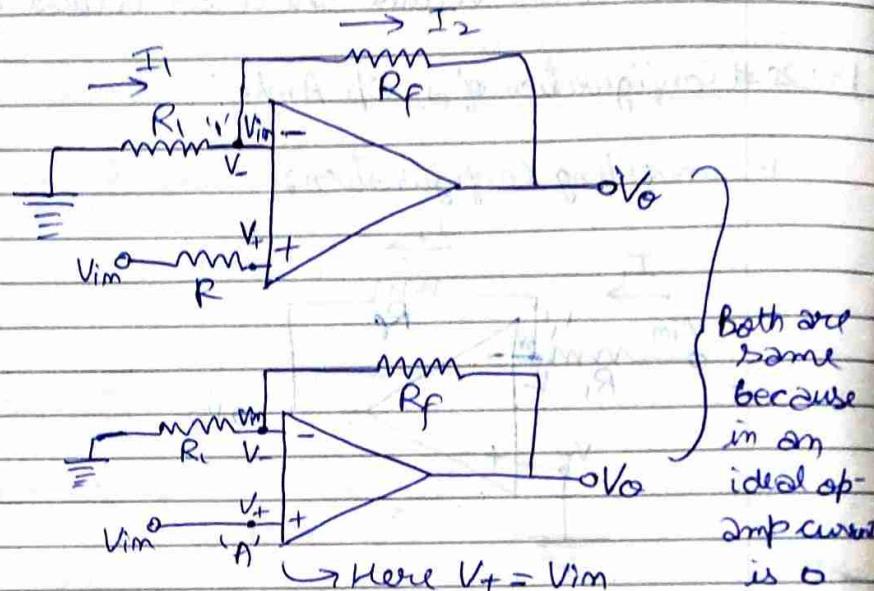

KCL at node 1 we get,

$$I_1 = I_2 \\ \rightarrow \frac{0 - V_{in}}{R_i} = \frac{V_{in} - V_o}{R_f}$$

$$\Rightarrow -V_{in}R_f = (V_{in} - V_o)R_i$$


$$\Rightarrow V_o R_i = V_{in}(R_i + R_f)$$

$$\Rightarrow V_o = \frac{V_{in}(R_i + R_f)}{R_i}$$

$$\text{or } V_o = V_{in} \left[1 + \frac{R_f}{R_i} \right]$$

$$\Rightarrow \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i} \rightarrow \text{gain}$$

Q1.

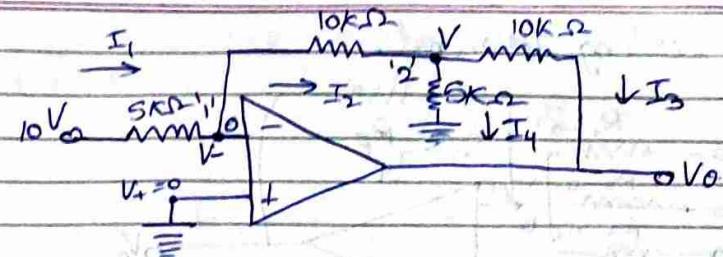

Ans: Applying KVL at mode '1',

$$I_1 = I_2$$

$$\frac{10 - 0}{5k\Omega} = \frac{0 - V}{10k\Omega}$$

$$V = -\frac{10 \times 10k\Omega}{5k\Omega}$$

$$V = -20V$$

Applying KVL at mode '2',

$$I_2 = I_3 + I_4$$

$$\frac{0 - 20}{10k\Omega} = \frac{V - V_o}{10k\Omega} + \frac{V - 0}{5k\Omega}$$

$$\frac{20}{10k\Omega} = -20 - V_o + (-20) \\ \frac{20}{10k\Omega} = -20 - V_o - 40$$

$$\Rightarrow 20 = -20 - V_o - 40$$

$$\Rightarrow V_o = -60 - 20$$


$$\boxed{V_o = -80V}$$

Adder:

1. Inverting Adder:

In inverting adder we apply input at the

inverting terminal.

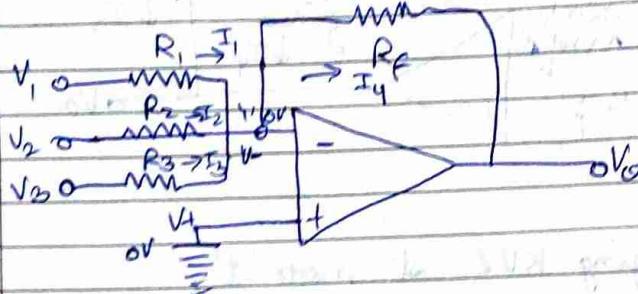

Applying KCL at node '1' we get,

$$I_1 + I_2 + I_3 = I_4$$

$$\frac{V_1 - 0}{R_1} + \frac{V_2 - 0}{R_2} + \frac{V_3 - 0}{R_3} = \frac{0 - V_0}{R_f}$$

$$\Rightarrow V_0 = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

If $R_f = R_1 = R_2 = R_3 = R$
then, $V_0 = -[V_1 + V_2 + V_3]$

Q2. Design an inverting adder circuit with output $-10V_1 + 5V_2 + 20V_3$.

Ans 2. We know $V_0 = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$ (Inverting Adder)

Given $V_0 = -10V_1 + 5V_2 + 20V_3$


On comparing above 2 eqn we get,

$$-\frac{R_f}{R_1} = -10, -\frac{R_f}{R_2} = 5, -\frac{R_f}{R_3} = 20$$

If we take $R_f = 20\Omega$

then, $R_1 = 2\Omega, R_2 = 4\Omega, R_3 = 1\Omega$

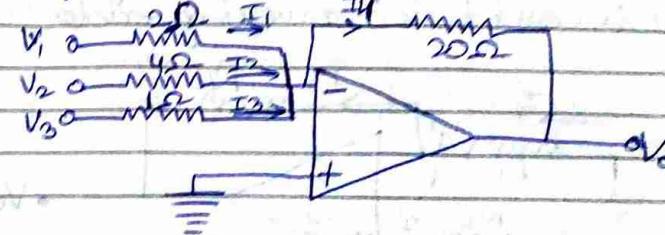or $V_0 = -10V_1 + 5V_2 + 20V_3$
therefore, circuit will be,



16/120

Q3: Design an op-amp inverting adder circuit having $V_0 = -5V_1 - 4V_2 - 10V_3$.

Ans 3: We know, $V_0 = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$

& Given $V_0 = -5V_1 - 4V_2 - 10V_3$


On comparing above 2 eqn we get,

$$-\frac{R_f}{R_1} = -5, -\frac{R_f}{R_2} = -4, -\frac{R_f}{R_3} = -10$$

If we take $R_f = 20\Omega$

then, $R_1 = 4\Omega, R_2 = 5\Omega, R_3 = 2\Omega$


therefore, circuit will be,

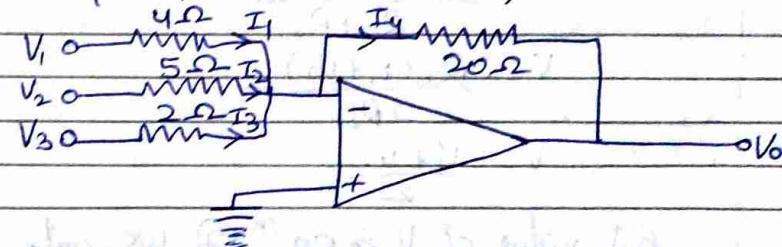

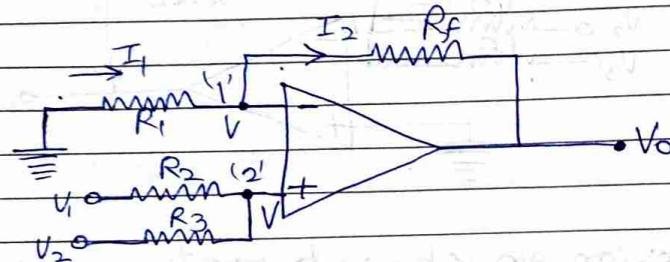2. Non-Inverting Adder:

When more than one input is applied at non-

inverting terminal & the non-inverting terminal is grounded w.r.t. non-inverting terminal then it is called non-inverting adder.



$$V = \frac{V_1 R_2 + V_2 R_2}{R_2 + R_3} \rightarrow ①$$

Applying KCL at node 1 we get,

$$I_1 = I_2$$

$$\frac{0 - V}{R_1} = \frac{V - V_0}{R_f}$$

$$V_0 = \left(1 + \frac{R_f}{R_1}\right)V \rightarrow ②$$

~~or~~ ~~N.B.~~ Let $R_2 = R_3$ then we have,

$$V = \frac{V_1 R_2 + V_2 R_2}{R_2 + R_2}$$

$$V = \frac{R_2(V_1 + V_2)}{2R_2}$$

$$V = \frac{V_1 + V_2}{2}$$

Put value of V in eq. ② we get,


$$V_0 = \left(1 + \frac{R_f}{R_1}\right) \frac{V_1 + V_2}{2}$$

Let $R_f/R_1 = 1$ then we have,

$$V_0 = V_1 + V_2$$

Voltage Follower:

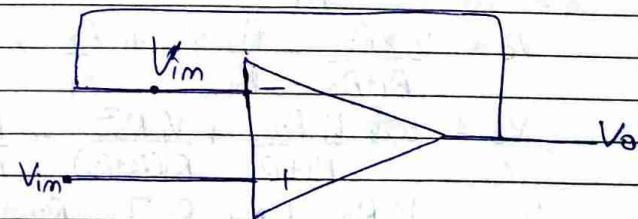Voltage Follower circuit is used to match impedance between two different circuits or amplifiers.




Here, $V_0 = V_{in}$

$$\text{therefore, } A_{CL} = \frac{V_0}{V_{in}} = 1$$

17-1-2020

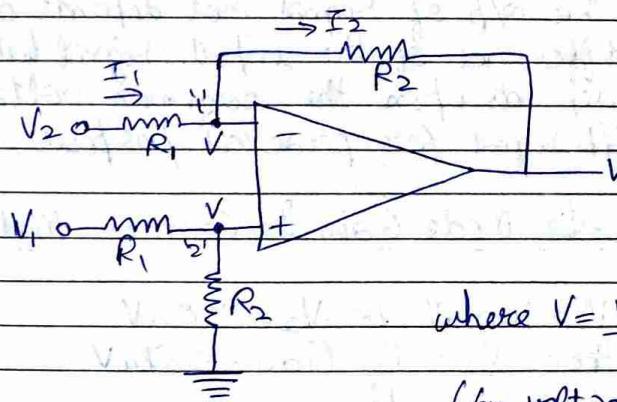Difference Amplifier/Subtractor Circuit/Differential Amp:



$$\text{where } V = \frac{V_1 \times R_2}{R_1 + R_2}$$

(by voltage divider)

Applying KCL at node 1

$$\frac{V_2 - V}{R_1} = \frac{V - V_0}{R_2}$$

$$\frac{V_0}{R_F} = \frac{(V_1 - V_2)}{R_1}$$

$$V - V_0 = \frac{R_2}{R_1} (V_2 - V)$$

$$V_0 = V - \frac{R_2}{R_1} (V_2 - V)$$

$$V_0 = \frac{V_1 \times R_2}{R_1 + R_2} - \frac{R_2}{R_1} V_2 + \frac{R_2}{R_1} \times \frac{V_1 \times R_2}{R_1 + R_2}$$

$$V_0 = \frac{V_1 R_2}{R_1 + R_2} + \frac{V_1 R_2^2}{R_1 (R_1 + R_2)} - \frac{R_2}{R_1} V_2$$

$$V_0 = \frac{V_1 R_2}{R_1 + R_2} \left[1 + \frac{R_2}{R_1} \right] - \frac{R_2}{R_1} V_2$$

$$\Rightarrow V_0 = \frac{R_2}{R_1} (V_1 - V_2)$$

$$\text{Let } R_2 = R_1 \text{ then } V_0 = V_1 - V_2$$

Note: The o/p of signal not depends only on the difference of the input signal but it also depends upon the common voltage of the i/b signal for practical purposes.

Differential Mode Gain & Common Mode Gain:

$$\text{Let } V_1 = 100 \mu\text{V} \& V_2 = 50 \mu\text{V}$$

$$\text{then } V_0 = \frac{R_2}{R_1} (100 - 50) \mu\text{V}$$

$$\text{Let } R_2 = R_1 \text{ then } V_0 = 50 \mu\text{V}$$

$$\text{Now consider } V_1 = 1000 \mu\text{V} \& V_2 = 950 \mu\text{V}$$

$$\text{then } V_0 = 50 \mu\text{V} [R_2 = R_1]$$

This is true only for an ideal op-amp. However, in practical applications, there is small response to the common mode component of the input voltage signals.

The common mode signal is defined as the average of the input signals i.e. $V_{cm} = \frac{V_1 + V_2}{2} \rightarrow ①$

$$\& V_d = V_1 - V_2 \rightarrow ②$$

From eqⁿ ① & ②

$$\boxed{V_1 = \frac{2V_{cm} + V_d}{2} \text{ or } V_{cm} + \frac{V_d}{2}} \rightarrow ③$$

$$\& \boxed{V_2 = \frac{2V_{cm} - V_d}{2} \text{ or } V_{cm} - \frac{V_d}{2}} \rightarrow ④$$

For the difference amplifier the circuit is symmetric but due to mismatch the gain of the amplifier w.r.t +ve terminal is slightly different in magnitude to that of -ve terminal. So, even with the same voltage applied to both the inputs the output is not 0 & it can be expressed as $\boxed{V_{out} = A_1 V_1 + A_2 V_2} \rightarrow ⑤$

where $A_1 = \text{Gain when input 1 is applied (+ve)}$
 $\& A_2 = \text{Gain when input 2 is applied (-ve)}$

Now putting the value of V_1 & V_2 from eqⁿ ③ & ④ into ⑤ we get,

$$V_o = A_1 \left[V_{cm} + \frac{V_d}{2} \right] + A_2 \left[V_{cm} - \frac{V_d}{2} \right]$$

$$\boxed{V_o = V_{cm} [A_1 + A_2] + \frac{V_d}{2} [A_1 - A_2]}$$

$$\Rightarrow V_o = V_{cm} A_{cm} + V_d A_{dm} \quad \rightarrow ⑥$$

$$A_{cm} = A_1 + A_2, \quad A_{dm} = \frac{A_1 - A_2}{2}$$


Common Mode Rejection Ratio (CMRR):

It is the ratio of differential mode to common mode gain. It is represented by ρ .

$$\text{i.e. } \rho = \frac{|A_{cm}|}{|A_{dm}|} = \frac{|A_{cm}|}{|A_{cm}| - |A_{dm}|}$$

$$\rho = \frac{(A_1 + A_2)}{2(A_1 - A_2)} \quad (\text{from above eqn})$$

Ques: IPU [Edt, 2017] 1st Term]

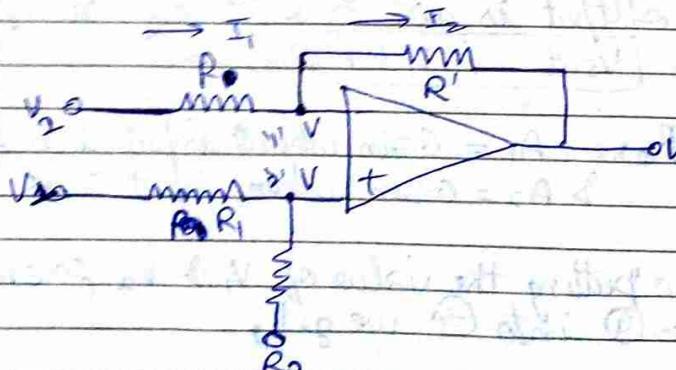

(i) Find the o/p voltage V_o .

(ii) Show that the o/p corresponding to CM voltage $V_{cm} = \frac{V_1 + V_2}{2}$ is 0 if $\frac{R'}{R} = \frac{R_2}{R_1}$. Find V_o in this case.

(iii) Find CMRR of the amplifier if $\frac{R'}{R} + \frac{R_2}{R_1}$

Ans: (i) Here $V = \frac{V_o R_2}{R_1 + R_2}$

Applying KCL at node 1,

$$I_1 = I_2$$

$$\frac{V_2 - V}{R} = \frac{V - V_o}{R'}$$


$$V - \frac{R'}{R} [V_2 - V] = V_o$$

$$V_o = V \left[1 + \frac{R'}{R} \right] - \frac{R'}{R} V_2$$

$$V_o =$$


Note: Always the o/p saturates b/w $\pm V_{EE} \leq V_o \leq V_{cc} + V_{ee}$

2011/2012 Subtractor:

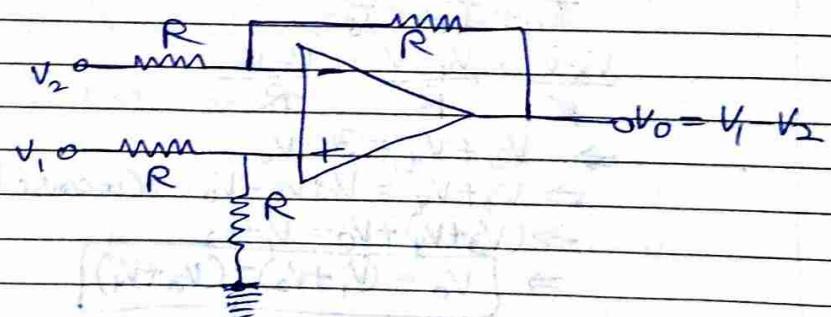

Adder/Subtractor Circuit:

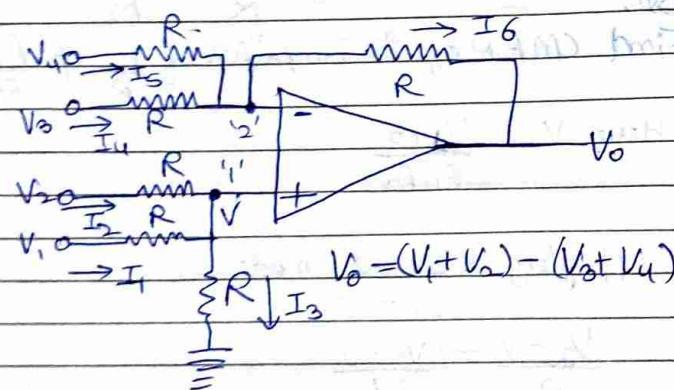This circuit provides addition & subtraction operation simultaneously.



KCL at node '1':

$$I_1 + I_2 = I_3$$

$$\frac{V_1 - V}{R} + \frac{V_2 - V}{R} = \frac{V}{R}$$

$$\Rightarrow V_1 + V_2 = 3V$$

$$\therefore V = \frac{V_1 + V_2}{3}$$

KCL at node '2':

$$I_4 + I_5 = I_6$$

$$\frac{V_3 - V}{R} + \frac{V_4 - V}{R} = \frac{V - V_0}{R}$$


$$\Rightarrow V_3 + V_4 = 3V - V_0$$

$$\Rightarrow V_3 + V_4 = V_1 + V_2 - V_0 \quad (\text{because } V = \frac{V_1 + V_2}{3})$$

$$\Rightarrow (V_3 + V_4) + V_0 = V_1 + V_2$$

$$\Rightarrow V_0 = (V_1 + V_2) - (V_3 + V_4)$$

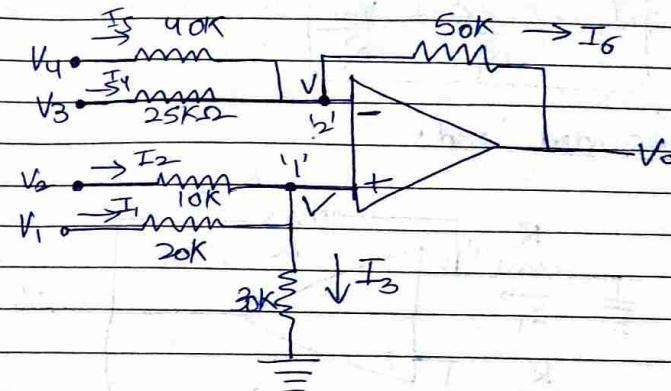- Q1. For the given figure 1, $V_4 = 2V$, $V_3 = 3V$, $V_6 = 4V$, $V_1 = 5V$. $\boxed{V_0 = 6.58V}$



Apply KCL at node '1':

$$I_1 + I_2 = I_3$$

$$\frac{V_1 - V}{20k\Omega} + \frac{V_2 - V}{10k\Omega} = \frac{V}{30k\Omega}$$

$$\rightarrow 3V_1 - 3V + 6V_2 - 6V = 2V$$

$$\rightarrow 3V_1 + 6V_2 = 11V \quad \Rightarrow V = 3 \times 5 + 6 \times 4$$

$$\boxed{V = 3.54V}$$


Apply KCL at node '2':

$$\frac{V_4 - V}{40k\Omega} + \frac{V_3 - V}{25k\Omega} = \frac{V - V_0}{50k\Omega}$$

$$\Rightarrow \boxed{V_0 = 6.58V}$$

Voltage to Current Converter:


Floating Load:

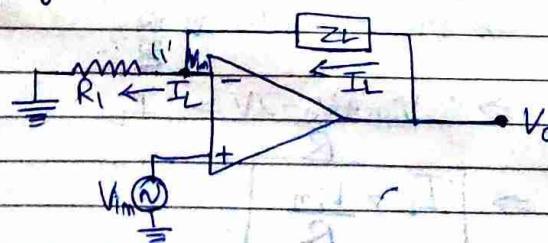

Applying KCL at node 1:

$$I_L = \frac{V_{im} - V}{R_1} = \frac{V_{im}}{R_1}$$

*** Grounded Load:

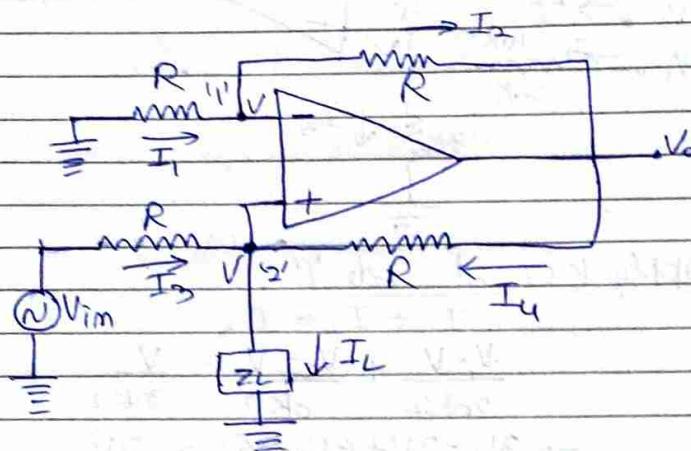

KCL at node 1:

$$I_1 = I_2$$

$$\frac{0 - V}{R} = \frac{V - V_o}{R} \Rightarrow V_o = 2V$$

$$\text{or } V = \frac{V_o}{2}$$

KCL at node 2:

$$I_3 + I_4 = I_L$$


$$\frac{V_{im} - V}{R} + \frac{V_o - V}{R} = I_L$$

$$\Rightarrow V_{im} + V_o - 2V = I_L$$

$$\Rightarrow I_L = \frac{V_{im} + V_o - 2V}{R}$$

Current to Voltage Converter: (Gross Resistance Amplifier)

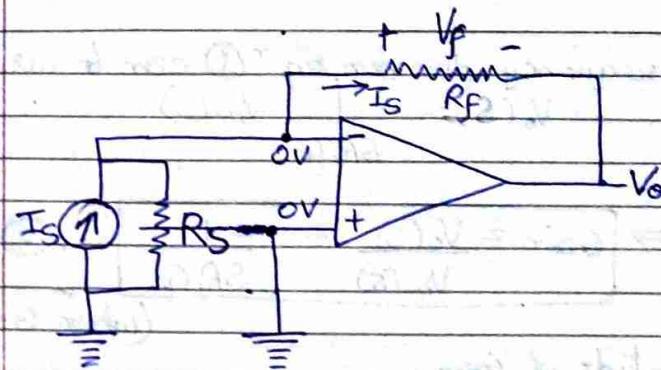Photocell, Photodiode and Photo voltaic cell gives an op/b current which is proportional to an incident radiant energy or light. The current through these devices can be converted to voltage by using current to voltage converter & hence the amount of light incident on these devices can be measured.




We know from above circuit $V_f = I_s R_F$

$$\text{Also } V_f = -V_o \Rightarrow V_o = -I_s R_F$$

Integrator:

- (i) Basic (2.5 marks)
- (ii) Practical (Derivation + Numericals) (6.5 marks) [Lossy Integrator]

Basic Integrator circuit:

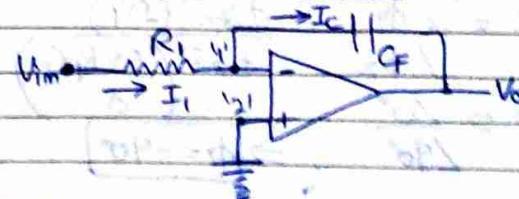

Apply KCL at node Y:

$$I_1 = I_C$$

$$\frac{V_{im}}{R_i} = -C_F \frac{dV_o}{dt}$$

Integrating both sides we get,

$$\int dV_o = - \int R_i C_F V_{im} dt$$

$$V_o(t) = \frac{1}{R_i C_F} \int V_{im} dt + V_c(t) \rightarrow ①$$

In frequency domain eq. ① can be written as

$$V_o(s) = -\frac{1}{SR_i C_F} V_{im}(s)$$

$$\Rightarrow \boxed{\text{Gain} = \frac{V_o(s)}{V_{im}(s)} = -\frac{1}{SR_i C_F}} \rightarrow ②$$

(where $S \rightarrow j\omega$)

Magnitude of Gain,

$$|\text{Gain}| = \left| \frac{V_o(s)}{V_{im}(s)} \right|$$

$$|\text{Gain}| = \left| \frac{-1}{j\omega R_i C_F} \right|$$

$$|\text{Gain}| = \sqrt{(-1)^2 + (\omega)^2} = \sqrt{\omega^2 + (1/R_i C_F)^2}$$


$$|\text{Gain}| = \frac{1}{\omega R_i C_F} = \frac{1}{2\pi f R_i C_F}$$

$$\begin{aligned} \text{Angle } \phi &= \angle \phi_1 = \tan^{-1}(\omega R_i C_F) \\ \angle \phi_2 &= \tan^{-1}(\omega R_i C_F) \\ \phi &= \frac{90^\circ}{180^\circ} \Rightarrow \phi = -90^\circ \end{aligned}$$

→ This circuit provides an output voltage which is proportional to the time integral of the input and $R_i C_F$.

→ This circuit also works as an integrator, when time constant is very large, that is $R_i C_F$ should be large.

Differentiator:

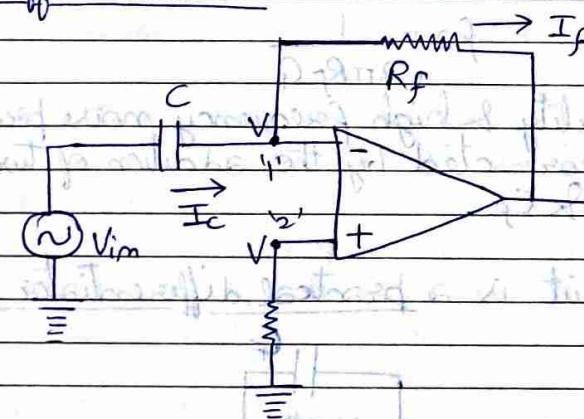

This circuit performs the mathematical operation of differentiation. The output waveform is the derivative of the input waveform.

Applying KCL at node Y we get,

$$\begin{aligned} I_C &= I_f \\ C_i \frac{d(V_{im} - V)}{dt} &= \frac{V - V_o}{R_f} \end{aligned}$$

As $V=0$, because gain (A) is very large,

$$C_i \frac{dV_{im}}{dt} = -\frac{V_o}{R_f}$$

$$V_o = -R_f C_i \frac{dV_{im}}{dt}$$


→ Since the differentiator performs the reverse of the integrator's function, a cosine wave input will produce a sine wave output or a triangular input will produce a square wave output.

→ The gain of circuit (R_f/X_C) increases with increase in frequency at a rate of 20dB/decade. This makes the circuit unstable.

$$f_a = \frac{1}{2\pi R_f C}$$

→ Both stability & high frequency noise problems can be corrected by the addition of two components: R_i & C_f .

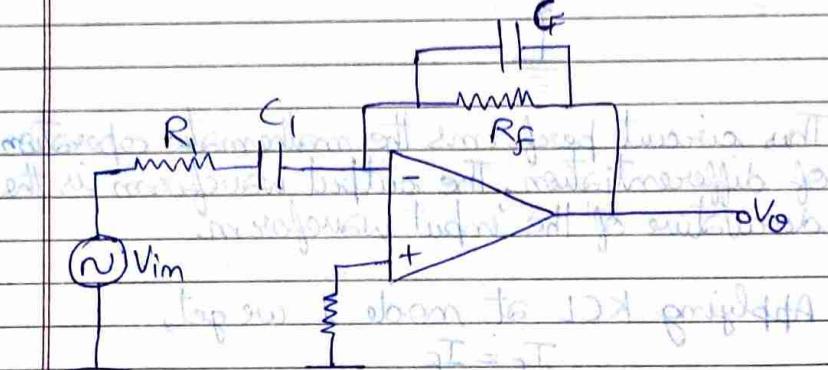This circuit is a practical differentiator.



$$\text{then, } f_b = \frac{1}{2\pi R_f C}$$

Thus $R_i C_f$ & $R_f C_f$ helps to reduce significantly the effect of high frequency input, amplifier noise, and offsets.

→ The differentiator is most commonly used in wav-

shaping circuits to detect high frequency components in an input signal and also as a rate of change of detector in FM modulation.

- (i) Design an op-amp differentiator that will differentiate input signal $f_{max} = 100\text{Hz}$.
- (ii) Draw the output waveform for sine wave of 1V peak of 100 Hz applied to the differentiator.
- (iii) Repeat part (ii) for square wave input.

Ans: (i) To design a good differentiator take the value of f_a , which is equal to highest frequency of the input signal.

Consider a value of C (less than $1\mu\text{F}$) & find the value of R_f . Let $C = 0.1\mu\text{F}$ (Always)

$$\text{Let } f_b = 10 f_a$$

Now calculate the value of R_i & C_f from the relation $R_f (f_a = R_i C_f)$

We have from the basic differentiator circuit,

$$f_a = \frac{1}{2\pi R_f C} = 100 \text{ rad/s}$$

$$\Rightarrow R_f = \frac{1}{2\pi f_a C}$$

$$2 \times 3.14 \times 100 \times 0.1 \times 10^{-6}$$

$$R_f = 15.9 \text{ k}\Omega$$

Also we have $f_6 = 10 f_2$

$$f_6 = 10 \times 100 \text{ Hz}$$

$$\boxed{f_6 = 1000 \text{ Hz or } 1 \text{ kHz}}$$

We know that, $f_6 = \frac{1}{2\pi R_1 C_6}$

$$\Rightarrow R_1 = \frac{1}{2\pi f_6 C_6}$$

$$\Rightarrow R_1 = \frac{1}{2 \times 3.14 \times 1000 \times 0.1 \times 10^{-6}}$$

$$\Rightarrow \boxed{R_1 = 1.59 \text{ k}\Omega}$$

From the condition of practical differentiator i.e.

$R_f C_f = R_1 C_6$, we have,

$$C_f = \frac{R_1 C_6}{R_f}$$

$$C_f = \frac{1.59 \text{ k}\Omega \times 0.1 \times 10^{-6}}{15.9 \text{ k}\Omega}$$

$$\boxed{C_f = 0.01 \mu\text{F}}$$

(ii) Also we have, $V_o = -R_f C_f \frac{dV_m}{dt}$

$$\text{Where } V_m = V_0' \sin \omega t$$

$$= I \sin \omega t \quad (\text{because } IV \text{ peak})$$

$$= \sin 2\pi f t$$


$$= \sin 200\pi t$$

$$V_0 = -R_f C_f \frac{d(\sin 200\pi t)}{dt}$$

$$\Rightarrow V_0 = -R_f C_f (\cos 200\pi t) (200\pi)$$

$$\Rightarrow \boxed{V_0 = -200\pi R_f C_f \cos(200\pi t)}$$

Output waveform:

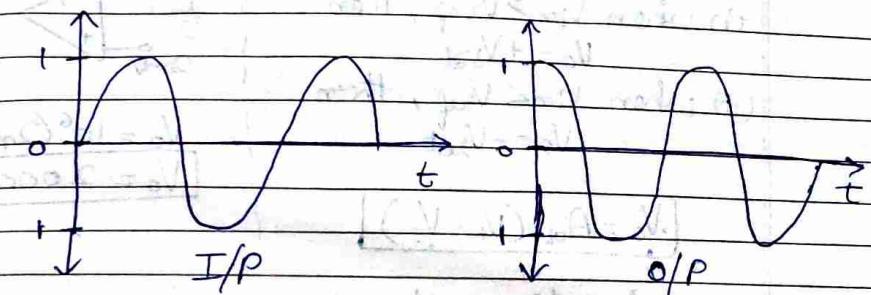


Comparator:

1. In an open loop configuration, op-amp behaves as analog comparator.
2. It compares one time varying signal with the fixed reference voltage.
3. The output of comparator saturates at $+V_{sat}$ or $-V_{sat}$.
 $+V_{cc} \rightarrow +V_{sat}$
 $-V_{ee} \rightarrow -V_{sat}$

Types of Comparator:

1. Non-Inverting Comparator
2. Inverting Comparator

Non-Inverting Comparator:

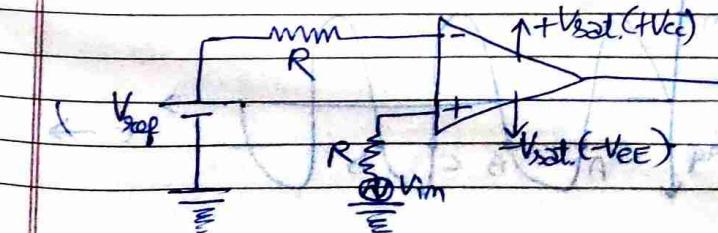


Rules:(i) when $V_m > V_{ref}$, then

$$V_o = +V_{sat}$$

(ii) when $V_m < V_{ref}$, then






$$V_o = -V_{sat}$$

$$[V_o = A_{ol} (V_+ - V_-)]$$

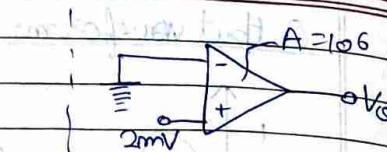



$$V_o = 10^6 (2M\Omega - V_b)$$


$$V_o = 2000V$$
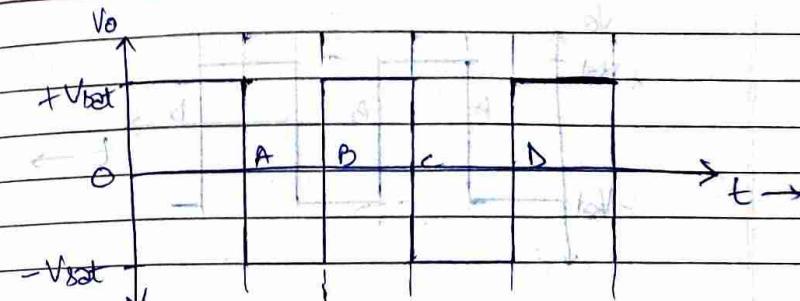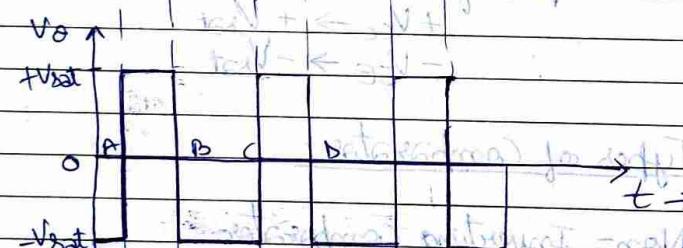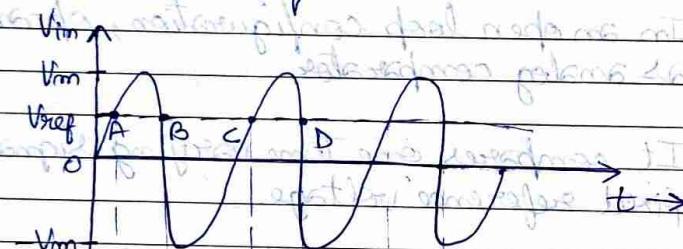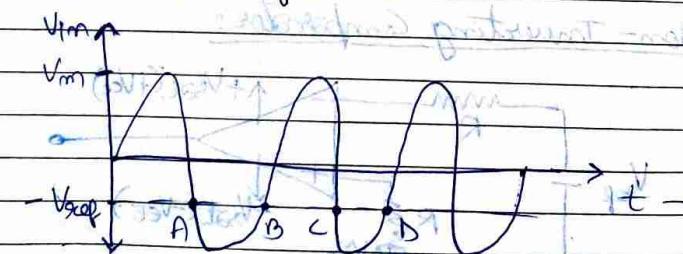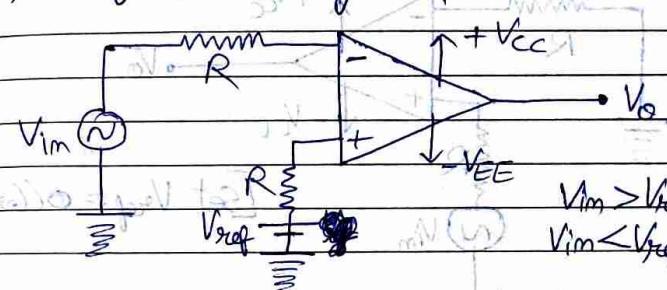
# I/P & O/P Waveforms:Case 1: When V_{ref} is +veCase-2: When V_{ref} is -ve# No. of Edge Inverting Comparator:


$$V_m > V_{ref}; V_o = +V_{sat}$$

$$V_m < V_{ref}; V_o = -V_{sat}$$

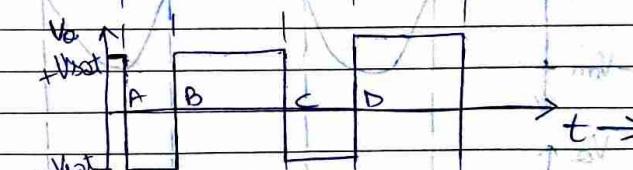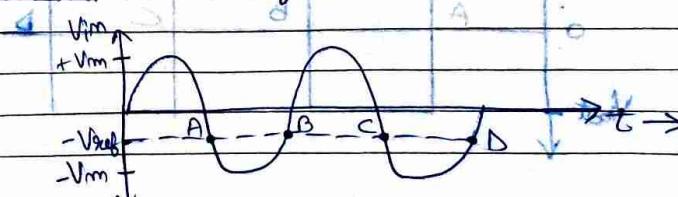
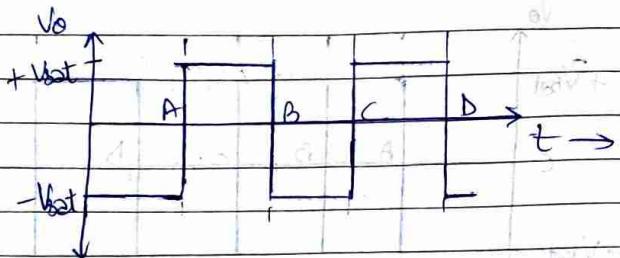
Case-1: When V_{ref} is +veCase-2: When V_{ref} is -ve



Zero-cross Detector:

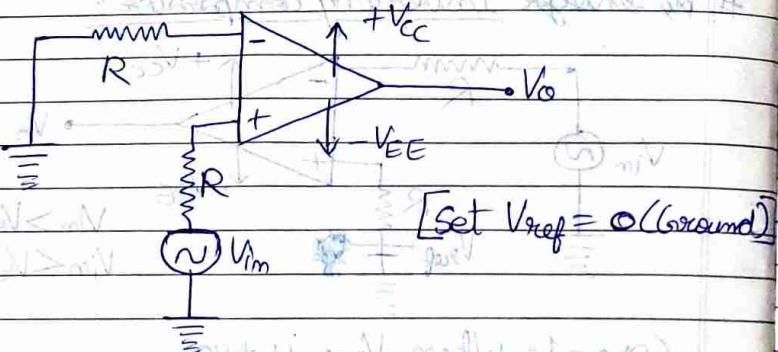


I/P & O/P Waveform:

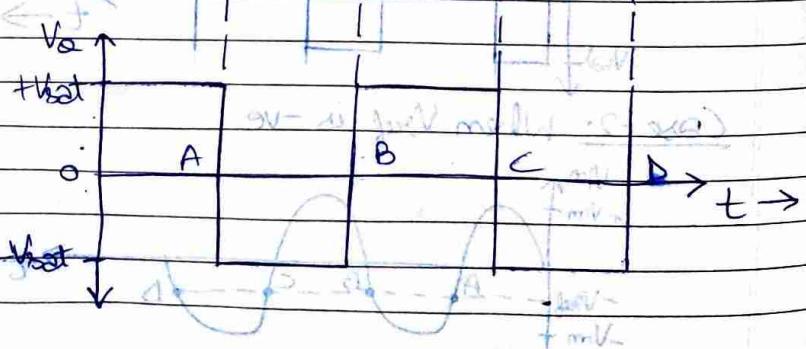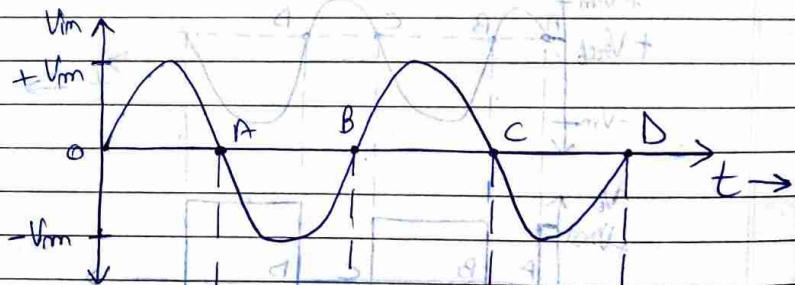

3/0/20 Log & Antilog Amplifier:

1. To perform the funcⁿ's such as $\ln(x)$, $\log(x)$ or $\sinh(x)$.
2. Log Amplifier can perform direct dB (decibel) display on digital voltmeter & spectrum analyser.
3. Log amplifier can also be used to compress the dynamic range of a signal.

(I) Log Amplifier:

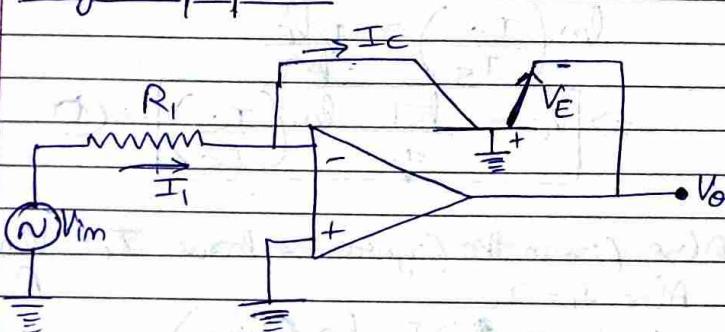

Since collector terminal is held at virtual ground & base of transistor is also grounded then, the voltage-current relationship becomes that of a diode & it is written as,

$$I_E = I_S (e^{qV_E/RT} - 1)$$

We know that $I_E = I_B + I_C$

Also $I_B = 0$ (grounded) $\Rightarrow I_C = I_E$

$$I_C = I_S (e^{qV_E/RT} - 1) \quad \text{where } I_S = \text{saturation current}$$

$k = \text{Boltzmann's constant} = 1.38 \times 10^{-23} \text{ J/K}$
 $T = \text{temp. (in K)}$

$$\rightarrow \frac{I_c}{I_s} = e^{\frac{qV_E}{RT}} - 1$$

$$\rightarrow \frac{I_c + I_s}{I_s} = e^{\frac{qV_E}{RT}}$$

$$\rightarrow \frac{I_c + I_s}{I_s} = e^{\frac{qV_E}{RT}}$$

$$\approx \frac{I_c}{I_s} = e^{\frac{qV_E}{RT}} \quad (\text{because } I_s \text{ is very small})$$

Taking natural log on both sides we get,

$$\ln\left(\frac{I_c}{I_s}\right) = \frac{qV_E}{kT}$$

$$\Rightarrow V_E = \frac{kT}{q} \cdot \ln\left(\frac{I_c}{I_s}\right) \rightarrow ①$$

Also from the figure we have, $I_i = \frac{V_{im}}{R_i}$

$$\text{Also } I_i = I_c$$

$$\therefore V_E = \frac{kT}{q} \cdot \ln\left(\frac{V_{im}}{R_i I_s}\right)$$

$$\text{Also } V_o = -V_E \Rightarrow V_o = -\frac{kT}{q} \cdot \ln\left(\frac{V_{im}}{R_i I_s}\right)$$


Let $R_i I_s = V_{ref}$. (V_{reference})

$$\Rightarrow V_o = -\frac{kT}{q} \cdot \ln\left(\frac{V_{im}}{V_{ref}}\right)$$

\rightarrow From the above expression we have $V_{ref} = R_i I_s$
~~it depends upon the value of I_s . We know~~

that I_s depends on temp.

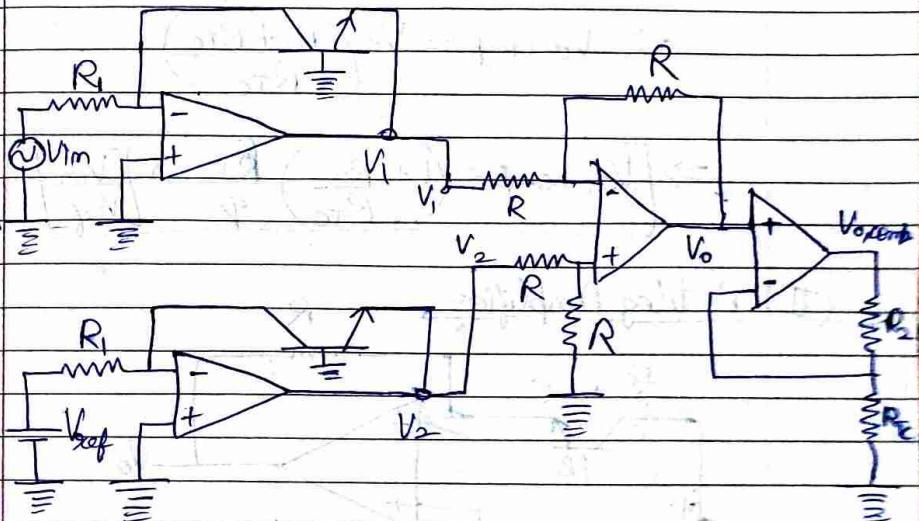Log Amplifier with Saturation Current & Temperature Compensation:



$$\text{Since } V_1 = -\frac{kT}{q} \cdot \ln\left(\frac{V_{im}}{R_i I_s}\right) \rightarrow ①$$

$$V_2 = -\frac{kT}{q} \cdot \ln\left(\frac{V_{ref}}{R_i I_s}\right) \rightarrow ②$$

Also Second circuit is a subtractor & hence
 $V_o = V_2 - V_1$.

$$V_o = -\frac{kT}{q} \cdot \ln\left(\frac{V_{ref}}{R_i I_s}\right) + \frac{kT}{q} \cdot \ln\left(\frac{V_{im}}{R_i I_s}\right)$$

$$V_o = \frac{kT}{q} \left[\ln\left(\frac{V_{im}}{R_i I_s}\right) - \ln\left(\frac{V_{ref}}{I_s R_i}\right) \right]$$

$$V_o = \frac{kT}{q} \left[\ln\left(\frac{V_{im}}{V_{ref}}\right) \right] \text{ or } -\frac{kT}{q} \ln\left(\frac{V_{ref}}{V_{im}}\right) \rightarrow ③$$


$\Rightarrow V_{o,comp}$ Also from the above figure

$$V_o = \frac{V_{o,comp} \times R_{TC}}{R_2 + R_{TC}}$$


$$\Rightarrow V_{o,comp} = V_o \left(\frac{R_2 + R_{TC}}{R_{TC}} \right)$$

$$\Rightarrow V_{o,comp} = \left(1 + \frac{R_2}{R_{TC}} \right) \frac{kT}{q} \ln \left[\frac{V_{in}}{V_{ref}} \right]$$

(II) Antilog Amplifier:

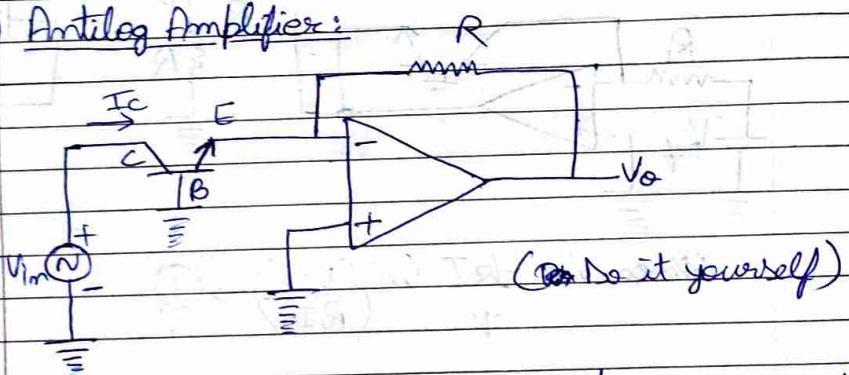

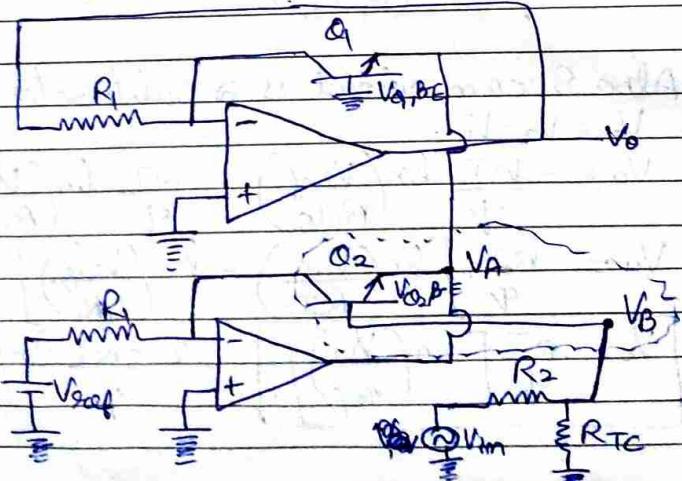Antilog Amplifier with Temperature Compensation:



$$V_{o, BE} = \frac{kT}{q} \ln \left(\frac{V_o}{R_1 I_S} \right) \rightarrow ①$$

$$V_{o_2, BE} = \frac{kT}{q} \ln \left(\frac{V_{o_2}}{R_1 I_S} \right) \rightarrow ②$$

Since Emitter terminal of transistor Q1 is connected to V_A . Hence V_A can be written as,

$$V_A = -V_{o, BE} = -\frac{kT}{q} \ln \left(\frac{V_o}{R_1 I_S} \right) \rightarrow ③$$

(highlighted part)

$$\begin{array}{c} V_{o, BE} \\ \downarrow \\ V_B \xrightarrow{+} V_A \xrightarrow{-} V_B - V_A = V_{o_2, BE} \\ \downarrow \\ V_B \end{array} \Rightarrow V_B - V_A = V_{o_2, BE}$$

$$\Rightarrow V_B - V_A = -\frac{kT}{q} \ln \left(\frac{V_{ref}}{R_1 I_S} \right) \rightarrow ④$$

Now putting the value of V_B , V_A & $V_{o_2, BE}$, we get,
From figure $V_B = \frac{V_{in} R_{TC}}{R_2 + R_{TC}}$

$$\Rightarrow \frac{V_{in} R_{TC}}{R_2 + R_{TC}} + \frac{kT}{q} \ln \left(\frac{V_o}{R_1 I_S} \right) = \frac{kT}{q} \ln \left(\frac{V_{ref}}{R_1 I_S} \right)$$

$$\Rightarrow \frac{V_{in} R_{TC}}{R_2 + R_{TC}} = \frac{kT}{q} \ln \left(\frac{V_{ref}}{R_1 I_S} \right) - \frac{kT}{q} \ln \left(\frac{V_o}{R_1 I_S} \right)$$

To convert natural log into \log_{10} , multiply 0.4343 both sides we get,

$$\begin{aligned} \Rightarrow -\frac{q}{kT} (0.4343) \left(\frac{V_{in} R_{TC}}{R_2 + R_{TC}} \right) &= 0.4343 \log_{10} \left(\frac{V_o}{V_{ref}} \right) \\ &= \log_{10} \left(\frac{V_o}{V_{ref}} \right) \end{aligned}$$

$$\text{Let } K' = \frac{g}{RT} (0.4343) \left(\frac{R_{TC}}{R_2 + R_{TC}} \right)$$

$$\Rightarrow -K' V_{im} = \log_{10} \left(\frac{V_o}{V_{ref}} \right)$$

$$\Rightarrow \frac{V_o}{V_{ref}} = 10^{-K' V_{im}}$$

$$\Rightarrow V_o = V_{ref} 10^{-K' V_{im}}$$

Precision Rectifier Using Op-amp:

→ Precision Rectifier using op-amp circuit also known as a super diode.

→ The basic circuit of precision rectifier is

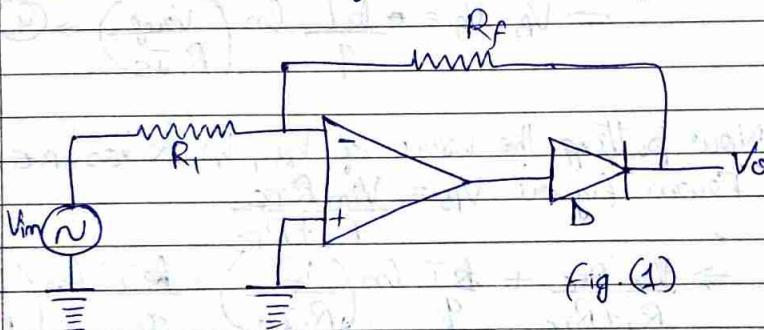


Fig. (1)


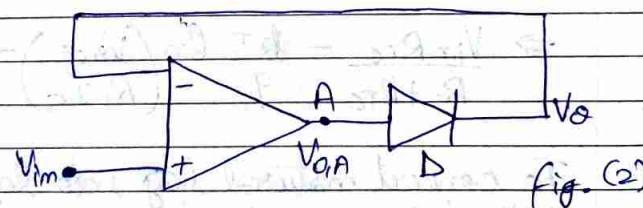


Fig. (2)

Rule / Note: When $V_{im} > V_f$ (voltage drop across diode) then the voltage at point A is +ve & when $V_{im} < V_f$ ($V_f(Ge)=0.3, V_f(S)=0.7$) then voltage at point A is -ve.

→ If sinusoidal input is applied to figure 2 then for +ve half cycle diode D₁ conducts and its output follows the input when diode is ideal.

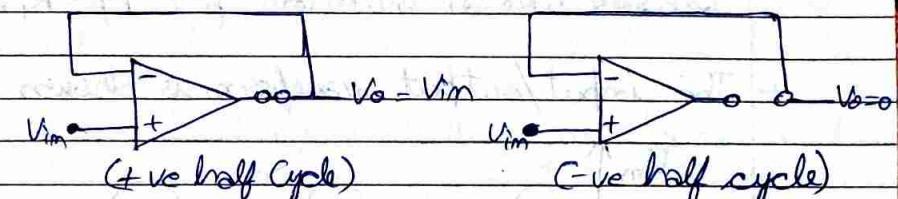
→ For -ve half cycle of input diode D₂ is reverse biased and output is zero.



Types of Rectifiers:

- (I) Half wave Rectifier
- (II) Full wave Rectifier

Half Wave Rectifier:

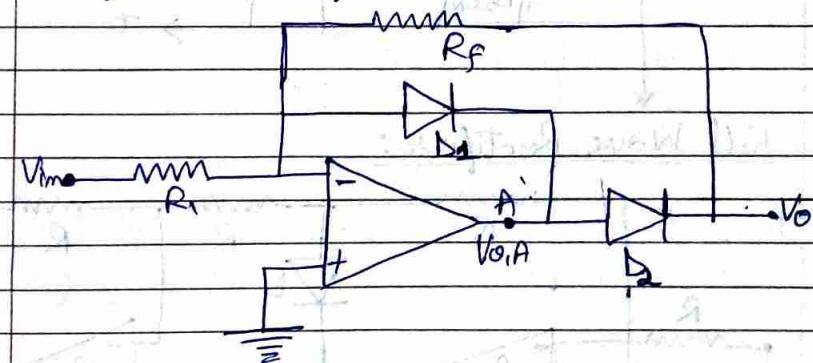


Operation ①:


→ For +ve half cycle diode D₁ conducts causing V_o,A to go to -ve by one diode drop (0.6V). Hence, diode D₂ is reverse biased, then the

output will be 0.

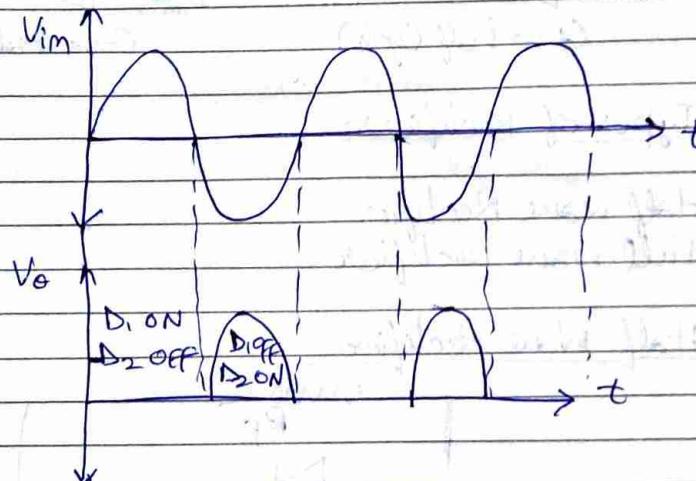- For -ve half cycle of the input diode D_2 conducts and D_1 will be off. The -ve input V_{im} forces the op-amp output $V_{o,A}$ to go to +ve & causes D_2 to conduct, then the circuit behaves like an inverter for $R_f = R_i$.
- The input/output waveform is shown below;




Full Wave Rectifier:

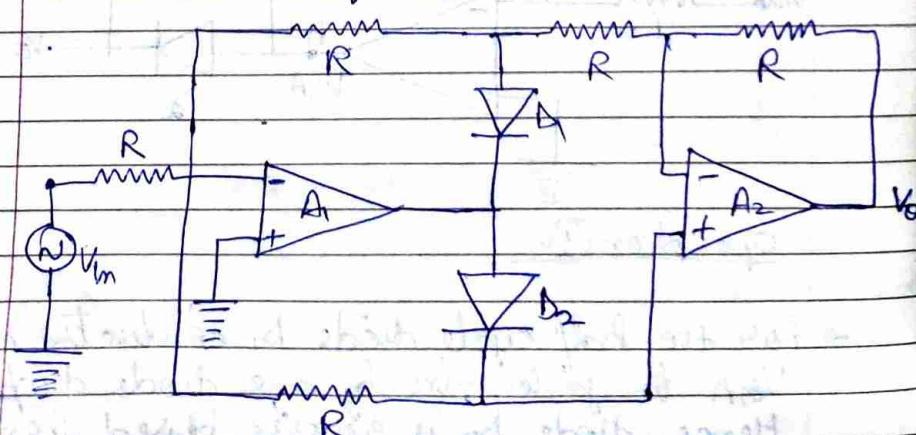


Operation:

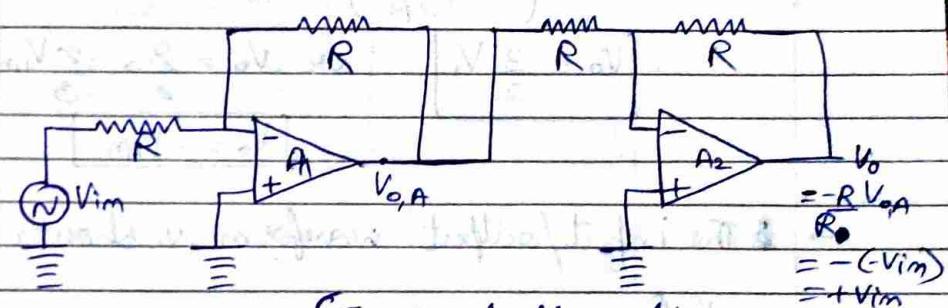- For the half cycle of the input diode D_1 conducts and D_2 will be off. Hence, both op-amps A_1 & A_2 works as an inverter.
- For the half cycle of the input diode D_2 conducts and D_1 will be off. The -ve input V_{im} forces the
- For -ve half cycle of the input D_2 conducts & D_1 will be off. The equivalent circuit can be drawn as,




(For the half cycle)

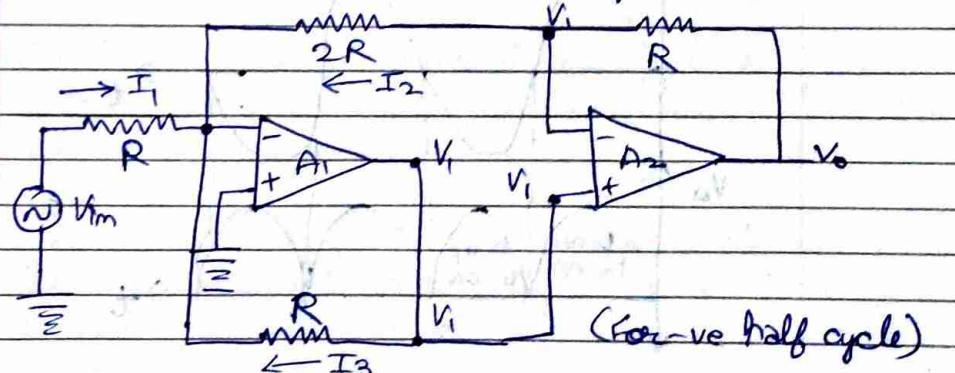

Consider the output of op-amp A_1 is V_1 . Applying KVL we get,
 $I_1 + I_2 + I_3 = 0$

$$\Rightarrow \frac{V_{im}}{R} + \frac{V_1}{2R} + \frac{V_1}{R} = 0$$

$$V_1 = -\frac{2}{3} V_{im}$$

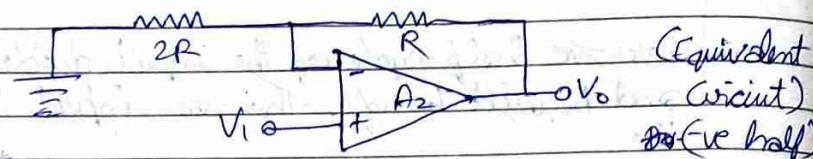

$$\Rightarrow V_o = \left(1 + \frac{R_f}{R_i}\right) V_{im}$$


$$V_o = \left(1 + \frac{R}{2R}\right) V_{im}$$

$$V_o = \frac{3}{2} V_1$$

$$\text{or } V_o = \frac{3}{2} \times \frac{-2}{3} V_{im}$$

$$V_o = -V_{im}$$

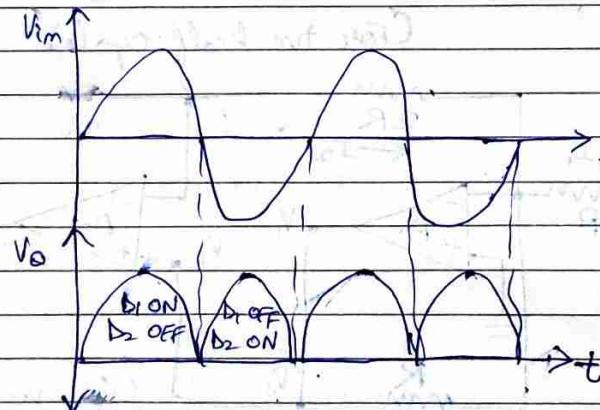The input/output waveform is shown below.




Clipper:

Clipper circuit is used to clip off ~~negative~~ portions

portion of the sinusoidal input.

→ The clipping level is obtained by the reference voltage, V_{ref} and could be obtained from the +ve supply voltage.


Positive Clipper:

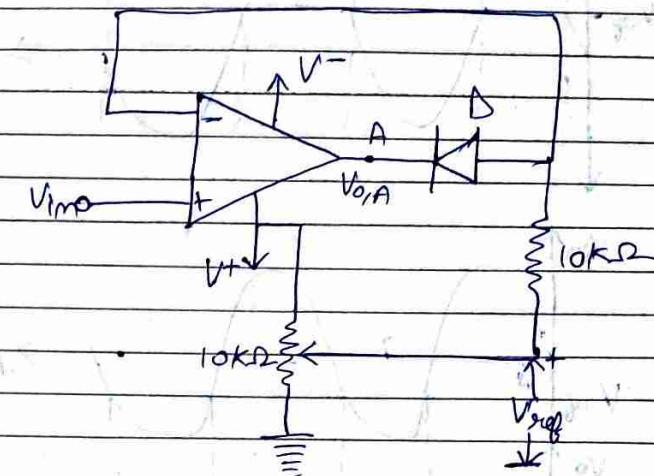

Operation:

→ For $V_{im} < V_{ref}$, the diode D conducts & op-amp works as a voltage follower & V_{out} follows V_{im} till $V_{im} \leq V_{ref}$.

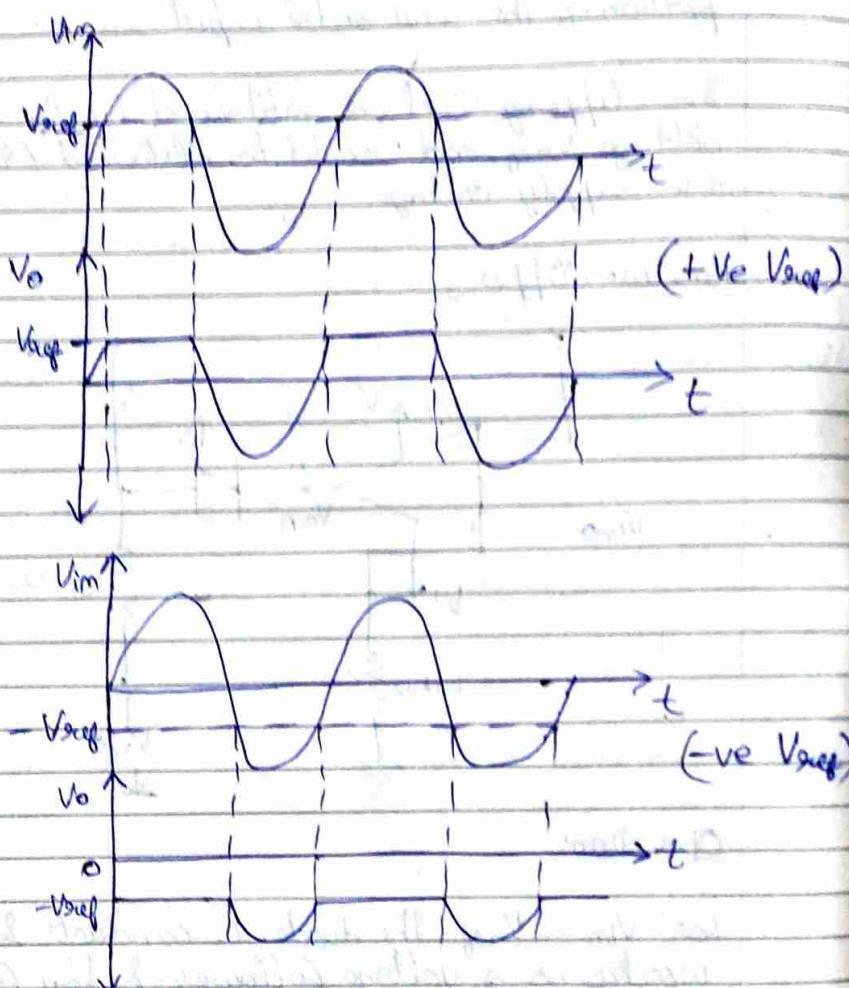→ When $V_{im} > V_{ref}$, the output $V_{o,A}$ of op-amp is large enough to drive the diode into cutoff region. The op-amp operates in open loop & hence $V_o = V_{ref}$. However if, V_{ref} is -ve then the entire output waveform above V_{ref} will get clipped off.



Note:

Negative clipper can be obtained by just reversing the diode & provide supply through V^- for V_{ref} .


Clamper:

~~want~~

- Clammer is called dc inserter or restorer.
- The circuit is used to add a ~~to~~ desired dc

level to the o/p voltage i.e. the output is clamped to a desired dc level.

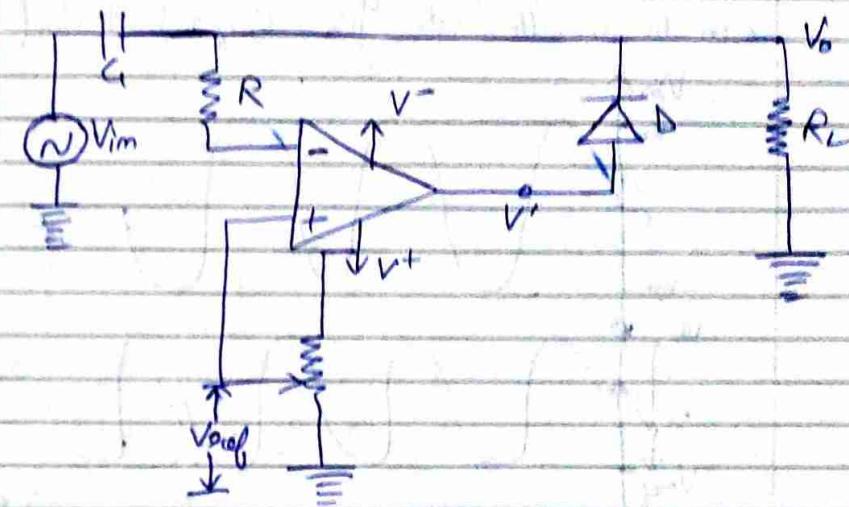
→ If the clamped dc level is +ve, then it is called +ve clamper & if clamped dc level is -ve, then it is called -ve clamper.



Operation:

- The output voltage in the circuit is the net result of ac & dc input voltages applied at inverting & non-inverting terminals respectively.
- For the V_{ref} , the voltage at V' is also +ve and hence, the diode D will be forward biased. Then the output $V_o = V_{ref}$.
- Now consider the ac input signal applied at inverting terminal, $V_{im} = V_m \sin \omega t$. During the -ve half cycle ~~for~~ of input, the diode D conducts


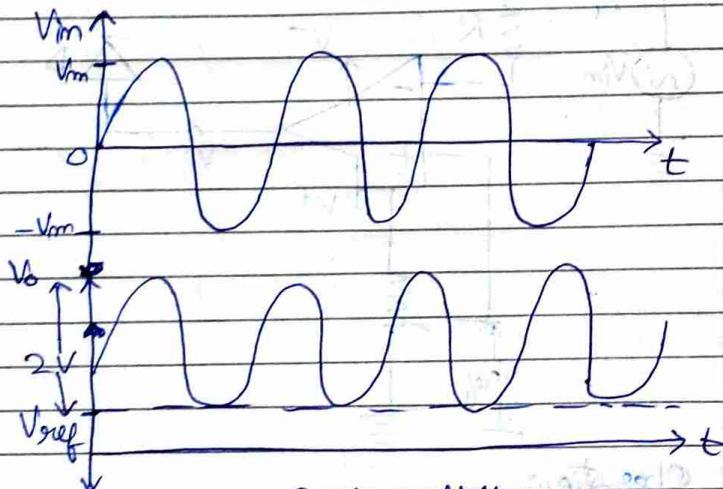
and capacitor C_1 charges to diode D upto -ve peak of input. However, during +ve half cycle of input diode D is reversed biased & the capacitor retains its previous voltage V_m . Since, the voltage V_m is in series with dc input signal, then the voltage can be written as $V_m + V_m$. Therefore total output voltage can be written as, $[V_o = V_{ref} + V_m + V_m]$



Oscillator:

- RC phase shift
- Wein Bridge
- Hartley
- ~~Colpitt~~

Basic Principle of oscillator:

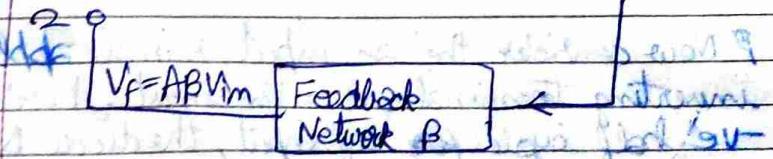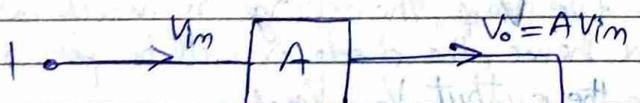


Baerhauzen Criteria of Oscillation:

$$A\beta = 1$$

$$|A\beta| = 1$$

$\angle A\beta = 0^\circ$ or multiples of 2π .

RC Phase Shift Oscillation:

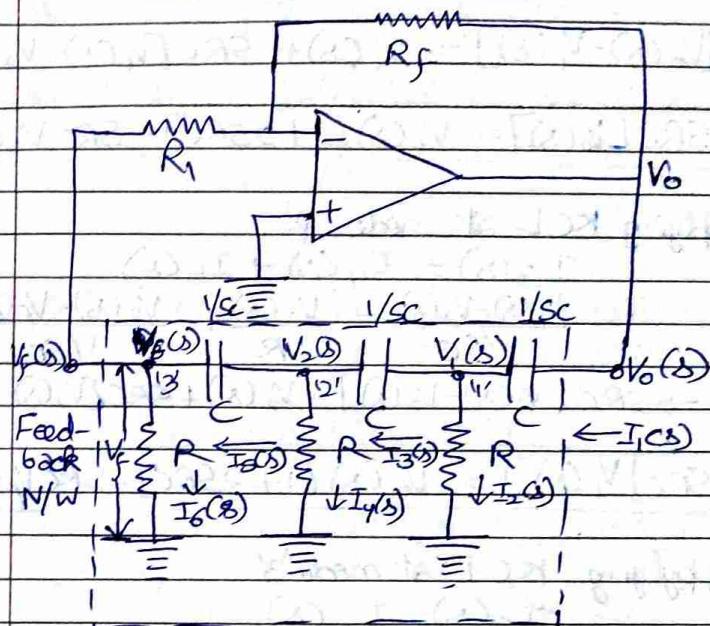

We know, that $A\beta = 1$ where $\beta = \frac{V_f}{V_o}$ & $A = \text{gain}$

→ Since, feedback network is applied at inverting terminal hence, phase shift provided due to inverting configurations is 180° .

→ One RC section will provide 60° phase shift. Hence, all the 3 ~~RC~~ sections will provide 180° phase shift. Therefore total phase shift is equal

$$to \ 180^\circ + 180^\circ = 360^\circ.$$

∴ Applying KCL at node '1',

$$I_1(s) = I_2(s) + I_3(s)$$

$$\frac{V_o(s) - V_1(s)}{1/SC} = \frac{V_1(s)}{R} + \frac{V_1(s) - V_2(s)}{1/SC}$$

$$SRC[V_o(s) - V_1(s)] = V_1(s) + SRC[V_1(s) - V_2(s)]$$

$$SRC[V_o(s)] = V_1(s)[1 + 2SRC] - SRCV_2(s) \rightarrow ①$$

Applying KCL at node '2'.

$$I_3(s) = I_4(s) + I_5(s)$$

$$\Rightarrow \frac{V_1(s) - V_2(s)}{1/SC} = \frac{V_2(s)}{R} + \frac{V_2(s) - V_f(s)}{1/SC}$$

$$\Rightarrow SRC[V_1(s) - V_2(s)] = V_2(s) + SRC[V_2(s) - V_f(s)]$$

$$\Rightarrow SRC[V_1(s)] = V_2(s)[1 + 2SRC] - SRCV_f(s) \rightarrow ②$$

Applying KCL at node '3'.

$$I_5(s) = I_6(s)$$

$$\Rightarrow \frac{V_2(s) - V_f(s)}{1/SC} = \frac{V_f(s)}{R}$$

$$\Rightarrow SRC[V_2(s)] = V_f(s)[1 + SRC]$$

$$\Rightarrow V_2(s) = V_f(s) \frac{(1 + SRC)}{SRC} \rightarrow ③$$

Putting value of $V_2(s)$ in eqⁿ ② we get,

$$SRC[V_1(s)] = V_f(s)[1 + SRC](1 + 2SRC) - SRCV_f(s)$$

$$\Rightarrow S^2 R^2 C^2 V_1(s) = V_f(s)(1 + SRC)(1 + 2SRC) - SRC^2 V_f(s)$$

$$\Rightarrow S^2 R^2 C^2 V_1(s) = V_f(s) [1 + 3SRC + 2S^2 R^2 C^2 - S^2 R^2 C^2]$$

$$\Rightarrow V_1(s) = \frac{V_f(s) [S^2 R^2 C^2 + 3SRC + 1]}{S^2 R^2 C^2} \rightarrow ④$$

Now putting the values of $V_1(s)$ & $V_2(s)$ in eqⁿ ①

$$\Rightarrow SRCV_0(s) = \frac{V_f(s)(S^2 R^2 C^2 + 3SRC + 1)(1 + 2SRC)}{S^2 R^2 C^2} - SRC \left[\frac{V_f(s)(1 + SRC)}{SRC} \right]$$

$$\Rightarrow SRCV_0(s) = \frac{V_f(s)[S^2 R^2 C^2 + 3SRC + 1 + 2S^3 R^3 C^3 + 6S^2 R^2 C^2 + 2SRC]}{S^2 R^2 C^2} - V_f(s)[1 + SRC]$$

$$\Rightarrow SRCV_0(s) = V_f(s)[S^3 R^3 C^3 + 6S^2 R^2 C^2 + 5SRC + 1] \rightarrow ⑤$$

$$\Rightarrow \frac{V_f(s) = B}{V_0(s)} = \frac{S^3 R^3 C^3}{S^3 R^3 C^3 + 6S^2 R^2 C^2 + 5SRC + 1} \rightarrow ⑥$$

Now from imaginary part since $V_f(s) = B$
 $V_0(s)$

⇒ From Barkhausen criteria we have,
 $AB = 1$ & from fig. $A = -\frac{R_F}{R_1}$

$$\Rightarrow \left(\frac{-R_F}{R_1} \right) \left(\frac{S^3 R^3 C^3}{S^3 R^3 C^3 + 6S^2 R^2 C^2 + 5SRC + 1} \right) = 1$$

put $S = j\omega$

$$\Rightarrow \left(\frac{-R_F}{R_1} \right) \frac{(j\omega)^3 R^3 C^3}{(j\omega)^3 R^3 C^3 + 6(j\omega)^2 R^2 C^2 + 5(j\omega) R C + 1} = 1 \quad ⑦$$

$$\left(\frac{-R_f}{R_1}\right) \frac{-j\omega^3 R^3 C^3}{-j\omega^3 R^3 C^3 - 6\omega^2 R^2 C^2 + 5j\omega R C + 1} = 1$$

$$\left(\frac{R_f}{R_1}\right) j\omega^3 R^3 C^3 = -j\omega^3 R^3 C^3 - 6\omega^2 R^2 C^2 + 5j\omega R C + 1$$

$$\left(\frac{R_f}{R_1}\right) j\omega^3 R^3 C^3 = 1 - 6\omega^2 R^2 C^2 + j[5\omega R C - \omega^3 R^3 C^3]$$

Equating real & img. part on both sides we get,
For Real part, $0 = 1 - 6\omega^2 R^2 C^2$

$$\Rightarrow 6\omega^2 R^2 C^2 = 1 \Rightarrow \omega^2 = \frac{1}{6R^2 C^2}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{6} RC}$$

$$\text{Also } \omega = 2\pi f = \frac{1}{\sqrt{6} RC}$$

$$\Rightarrow f_o = \frac{1}{2\pi\sqrt{6} RC}$$

For Img. part, $\frac{R_f}{R_1} j\omega^3 R^3 C^3 = 5\omega R C - \omega^3 R^3 C^3$

$$\frac{R_f}{R_1} = \frac{5}{\omega^2 R^2 C^2} - 1$$

Putting value of ω^2 in above eqⁿ we have,

$$\frac{R_f}{R_1} = \frac{5}{\frac{R^2 C^2}{6R^2 C^2}} - 1 = 30 - 1$$

$$\Rightarrow \frac{R_f}{R_1} = 29$$

Ans. In RC phase shift oscillator we have 3 different RC sections so we have to find the value of R for all the 3 sections by taking the value of capacitor, $C = 0.1 \mu F$

We know, $f_o = \frac{1}{2\pi\sqrt{6} RC}$

$$\Rightarrow R = \frac{1}{2 \times 3.14 \times \sqrt{6} \times 100 \times 0.1 \times 10^{-6}}$$

$$\Rightarrow R = 6.5 K\Omega$$

To prevent loading effect of amplifier because of RC network, it is necessary to take $R_1 \geq 10R$

$$\Rightarrow R_1 = 10R = 10 \times 6.5 K\Omega$$


$$\Rightarrow R_1 = 65 K\Omega$$

$$\text{Also, } \frac{R_f}{R_1} = 29 \Rightarrow R_f = 29 R_1$$

$$R_f = 29 \times 65 K\Omega$$


$$\Rightarrow R_f = 1885 K\Omega$$

$$R_f = 1885 K\Omega$$

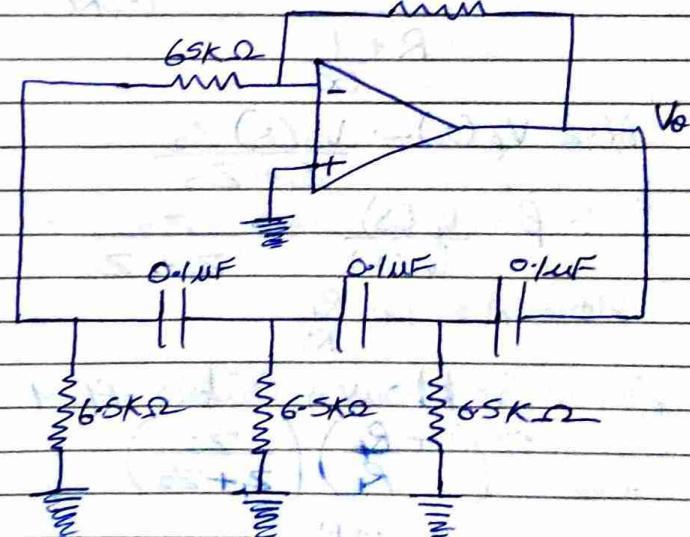

Q1. Design the RC phase shift oscillator for $f_o = 100 Hz$

Wein Bridge Oscillator:

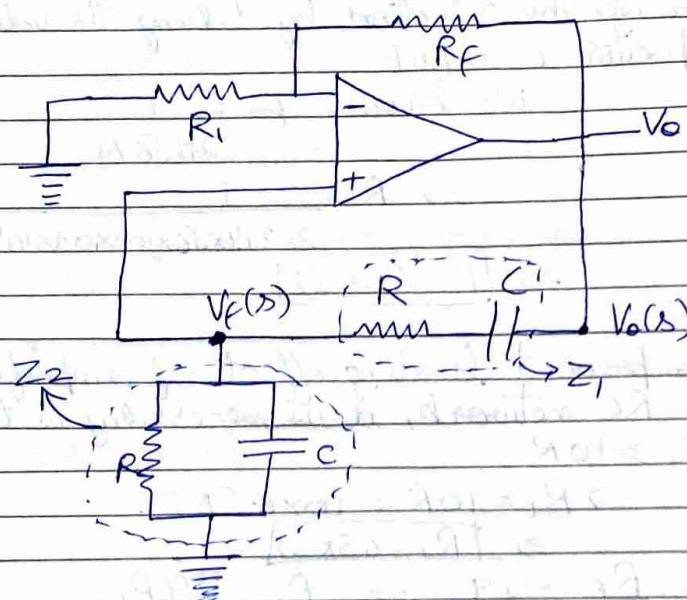

$$\text{From above fig. } Z_1 = R + \frac{1}{SC} = \frac{1+SRC}{SC}$$

$$\& Z_2 = R \times \frac{1}{SC} = \frac{R}{1+SRC}$$

$$\frac{R+1}{SC}$$

$$\text{Also } V_f(s) = \frac{V_0(s)Z_2}{Z_1 + Z_2}$$

$$\& \beta = \frac{V_f(s)}{V_0(s)} = \frac{Z_2}{Z_1 + Z_2}$$

$$\text{Here } A = 1 + \frac{RF}{R_1}$$

From Barkhausen Criteria $AB=1$

$$\Rightarrow \left(1 + \frac{RF}{R_1}\right) \left(\frac{Z_2}{Z_1 + Z_2} \right) = 1$$

$$\left(1 + \frac{RF}{R_1}\right) \left[\frac{R}{1+SRC} \right] = 1$$

$$\frac{1+RF}{R_1} \cdot \frac{R}{1+SRC + \frac{R}{SC}} = 1$$

put $S=j\omega$

$$\left(1 + \frac{RF}{R_1}\right) \left[\frac{RSC}{1+S^2R^2C^2+2SRC+SRC} \right] = 1$$

$$\Rightarrow \left(1 + \frac{RF}{R_1}\right) \left[\frac{j\omega RC}{1+j\omega^2RC^2+3j\omega RC} \right] = 1$$

$$\Rightarrow \left(1 + \frac{RF}{R_1}\right) \left[\frac{j\omega RC}{1-\omega^2R^2C^2+3j\omega RC} \right] = 1$$

$$\Rightarrow \left(1 + \frac{RF}{R_1}\right) j\omega RC = 1 - \omega^2 R^2 C^2 + 3j\omega RC$$

Equating Real & img. part we get,

$$1 - \omega^2 R^2 C^2 = 0$$

$$\omega^2 R^2 C^2 = 1$$

$$\omega = \frac{1}{RC}$$


$$\therefore f = \frac{1}{2\pi RC}$$

$$\& \left(1 + \frac{RF}{R_1}\right) \omega RC = 3\omega RC$$

$$\boxed{\frac{RF}{R_1} = 2}$$

So, in Wein bridge oscillator we have frequency, $f = \frac{1}{2\pi RC}$ & ratio of $\frac{RF}{R_1} = 2$

Hartley Oscillator:

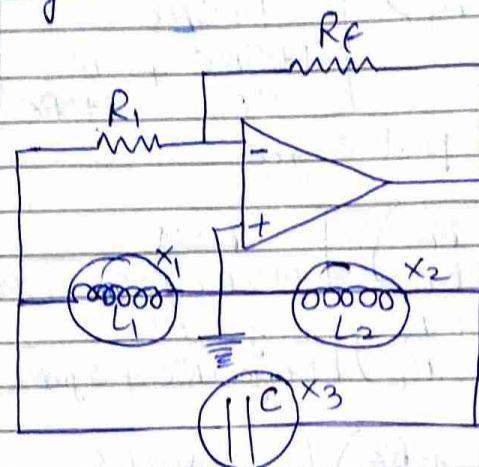

To find the freq. of oscillation in hartley oscillator, the sum of total reactance of tank circuit must be zero.

$$\text{i.e. } X_1 + X_2 + X_3 = 0$$

$$\Rightarrow SL_1 + SL_2 + \frac{1}{j\omega C} = 0$$

$$\Rightarrow j\omega L_1 + j\omega L_2 + \frac{1}{j\omega C} = 0$$


$$\Rightarrow j\omega(L_1 + L_2) = -\frac{1}{j\omega C}$$

$$\Rightarrow (L_1 + L_2) = \frac{1}{\omega^2 C}$$

$$\Rightarrow \omega^2 = \frac{1}{C(L_1 + L_2)} \Rightarrow \omega = \frac{1}{\sqrt{C(L_1 + L_2)}}$$

$$\Rightarrow f = \frac{1}{2\pi\sqrt{C(L_1 + L_2)}} \quad & |A| \geq L_2 \\ \Rightarrow |A| \geq \frac{L_2}{L_1}$$

Colpitt Oscillator:

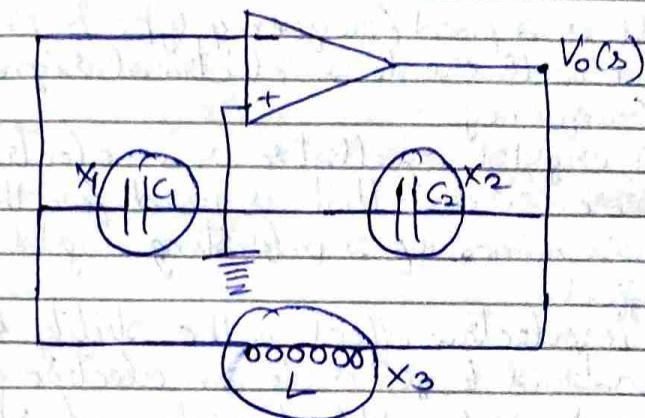

To find freq. of oscillation, the sum of total reactance of the tank circuit must be zero.

$$\text{i.e. } X_1 + X_2 + X_3 = 0$$

$$\Rightarrow \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + SL = 0$$

$$\Rightarrow \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j\omega L = 0$$

$$\Rightarrow \frac{1}{j\omega} \left[\frac{1}{C_1} + \frac{1}{C_2} \right] = -j\omega L$$

$$\Rightarrow \left[\frac{1}{C_1} + \frac{1}{C_2} \right] = \omega^2 L$$

$$\Rightarrow \omega^2 = \frac{1}{L} \left[\frac{C_1 + C_2}{C_1 C_2} \right]$$


$$\Rightarrow \omega = \sqrt{\frac{1}{L} \left(\frac{C_1 + C_2}{C_1 C_2} \right)}$$

$$\Rightarrow f = \frac{1}{2\pi} \sqrt{\frac{1}{L} \left(\frac{C_1 + C_2}{C_1 C_2} \right)}$$


$$|A| \geq \frac{C_1}{C_2}$$

Crystal Oscillator :

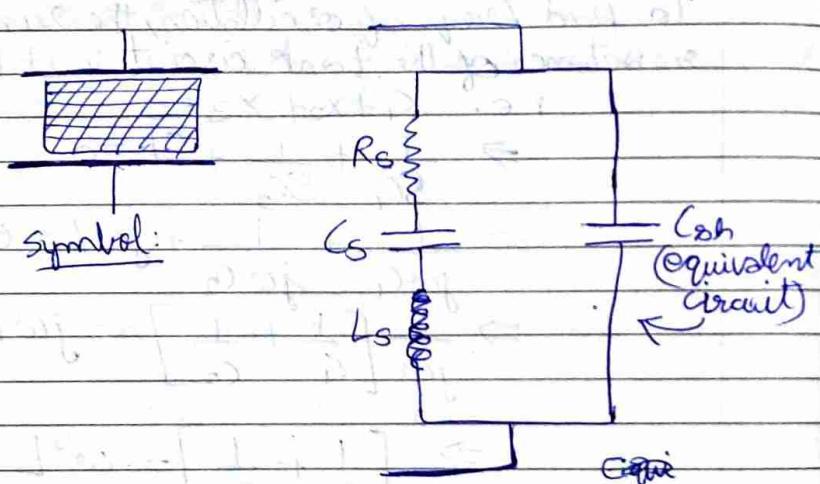- It is a fixed frequency type & RF oscillator.
- It will create an electrical signal with even frequency.
- A crystal oscillator is an electrical oscillator circuit that is used for the mechanical resonance of a vibrating crystal of piezoelectric effect.
- Piezoelectric effect is the ability of certain material to generate an electric charge in response to applied mechanical stress.



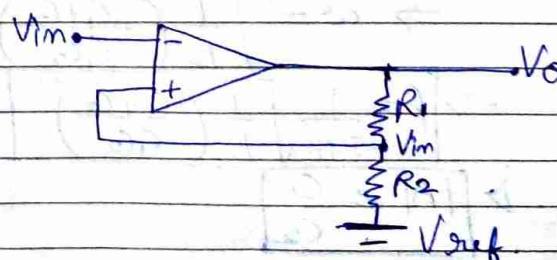Schmitt Trigger circuit / regeneration Comparator:



- A Schmitt trigger circuit can be obtained by providing positive feedback in basic comparator circuit.
- In comparator circuit output saturates b/w positive & negative max. supply of voltage.
- Consider $[V_o = +V_{sat}]$ then, voltage at positive terminal is called upper threshold voltage & it can be obtained by,

$$V_{UT} = \frac{V_o R_2 + V_{ref} R_1}{R_1 + R_2}$$

$$V_{UT} = \frac{+V_{sat} R_2 + V_{ref} R_1}{R_1 + R_2} \rightarrow ①$$

- Now consider $[V_o = -V_{sat}]$, then voltage at positive terminal is called lower threshold voltage & it can be obtained as,

$$V_{LT} = \frac{-V_{sat} R_2 + V_{ref} R_1}{R_1 + R_2} \rightarrow ②$$

- The difference b/w upper threshold & lower threshold voltage is called Hysteresis Voltage.

$$V_H = V_{UT} - V_{LT}$$


$$V_H = \frac{2V_{sat} R_2}{R_1 + R_2}$$

Instrumentation Amplifier:

- In a number of industrial and common

applications, it is required to measure & control physical quantities.

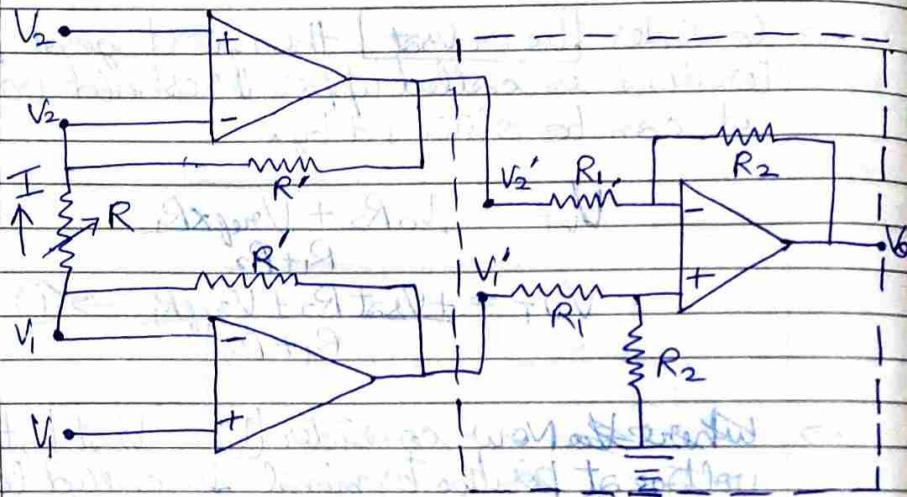→ Some examples are measurement control of temperature, humidity, light intensity, water flow etc.



In above fig. we have,

$$V_0 = \frac{R_2}{R_1} (V_1' - V_2') \rightarrow ①$$

$$\text{Also } I = \frac{V_1 - V_2}{R} \rightarrow ②$$

$$\text{Also } I = \frac{V_1' - V_1}{R'}$$

$$\Rightarrow IR' = V_1' - V_1 \Rightarrow V_1' = V_1 + IR'$$

$$V_1' = V_1 + (V_1 - V_2) \frac{R'}{R} \rightarrow ③$$

$$\text{Also } I = \frac{V_2 - V_2'}{R'}$$

$$V_2' = V_2 - IR'$$

$$\Rightarrow V_2' = V_2 - (V_1 - V_2) \frac{R'}{R} \rightarrow ④$$

Now putting the value of V_1' & V_2' in eqn ① we get,


$$V_0 = \frac{R_2}{R_1} \left[V_1 + (V_1 - V_2) \frac{R'}{R} - V_2 + (V_1 - V_2) \frac{R'}{R} \right]$$

$$\Rightarrow V_0 = (V_1 - V_2) \frac{R_2}{R_1} \left(1 + 2 \frac{R'}{R} \right)$$

Features of Instrumentation Amplifier:

- 1.) High gain accuracy.
- 2.) High CMRR.
- 3.) High gain stability with temperature coefficient.
- 4.) Low dc offset.

Block Schematic of Op-Amp:

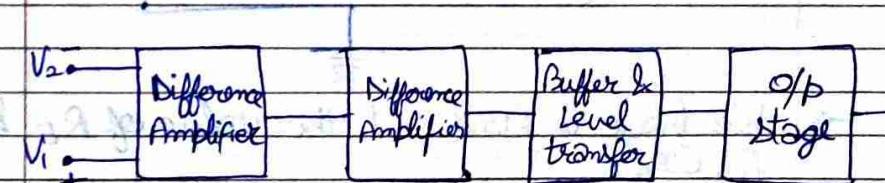


- 1.) 2 stage difference amplifier provides high gain and high input resistance.
- 2.) Buffer circuit is an emitter follower circuit, whose input impedance is very high, so that it prevents from loading of the high stage gain.
- 3.) The level translator adjust the dc voltages, so that output is zero for zero input voltage.

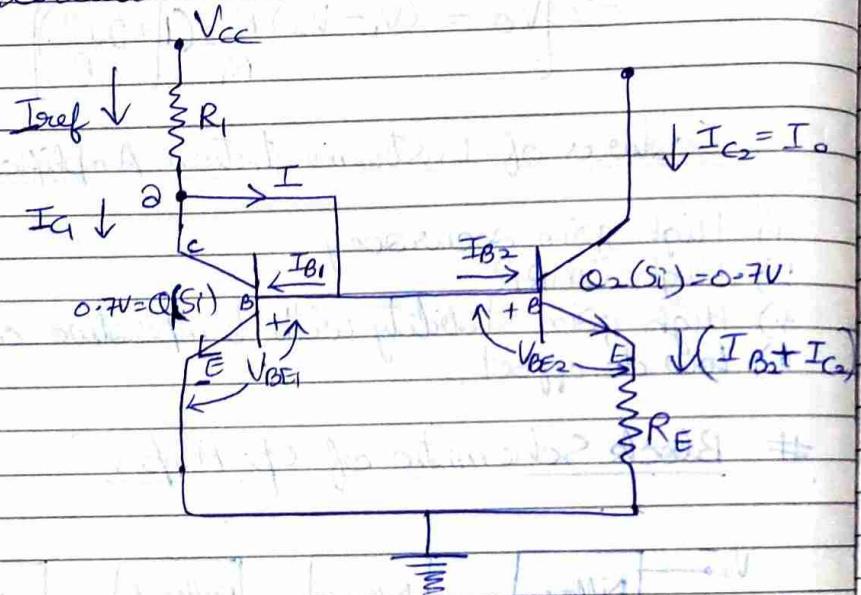i) The output stage provides low output impedance

Widlar Current Source:

→ It can be obtained by providing emitter resistance in basic constant current source circuit.



→ We have to find out the value of R_E & I_{C_2} (I_0).

→ The collector current for transistor Q1 & Q2 in forward active mode can be written as,

$$I_{C_1} = \alpha_F I_{ESE} e^{\frac{V_{BE1}}{V_T}} \rightarrow ①$$

$$I_{C_2} = \alpha_F I_{ESE} e^{\frac{V_{BE2}}{V_T}} \rightarrow ②$$

where I_{ESE} → Reverse saturation current of emitter-base

Dividing eqn ① by ② we get,

$$\frac{I_{C_1}}{I_{C_2}} = e^{\frac{V_{BE1} - V_{BE2}}{V_T}} \rightarrow ③$$

Now apply KVL, which contains emitter-base junctⁿ of both transistors,

$$V_{BE1} - V_{BE2} = (I_{B_2} + I_{C_2}) R_E \rightarrow ④$$

Now taking natural log on both sides of eqⁿ ③ we get,

$$\ln\left(\frac{I_{C_1}}{I_{C_2}}\right) = \frac{V_{BE_1} - V_{BE_2}}{V_T}$$

$$\Rightarrow V_{BE_1} - V_{BE_2} = V_T \ln\left(\frac{I_{C_1}}{I_{C_2}}\right) \rightarrow ⑤$$

From eqⁿ ④ & ⑤ we have

$$(I_{B_2} + I_{C_2}) R_E = V_T \ln\left(\frac{I_{C_1}}{I_{C_2}}\right)$$

$$\left(\frac{1}{B} + 1\right) I_{C_2} R_E = V_T \ln\left(\frac{I_{C_1}}{I_{C_2}}\right)$$

$$R_E = V_T \ln\left(\frac{I_{C_1}}{I_{C_2}}\right) \rightarrow ⑥$$

$$\left(\frac{1}{B} + 1\right) I_{C_2}$$

Now apply KCL at node '2',

$$I_{ref} = I_{C_1} + I_{B_1} + I_{B_2}$$

$$\Rightarrow I_{ref} = I_{C_1} + \frac{I_{C_1}}{B} + \frac{I_{C_2}}{B}$$

$$I_{ref} = I_{C_1} \left(1 + \frac{1}{B}\right) + \frac{I_{C_2}}{B}$$

Consider transistor Q₁ & Q₂ are identical
i.e. $\beta_1 = \beta_2 = \beta$

In wider current source,


$I_{C_2} \ll I_{C_1}$, $\frac{I_{C_2}}{\beta}$ can be neglected

$$\Rightarrow I_{\text{ref}} = I_{C_1} \left(1 + \frac{1}{\beta}\right)$$

$$\Rightarrow I_{C_1} = \frac{I_{\text{ref}}}{1 + \frac{1}{\beta}}$$

$$\text{where } I_{\text{ref}} = \frac{V_{CC} - V_{BE_1}}{R_1}$$

Wilson's Current Source:

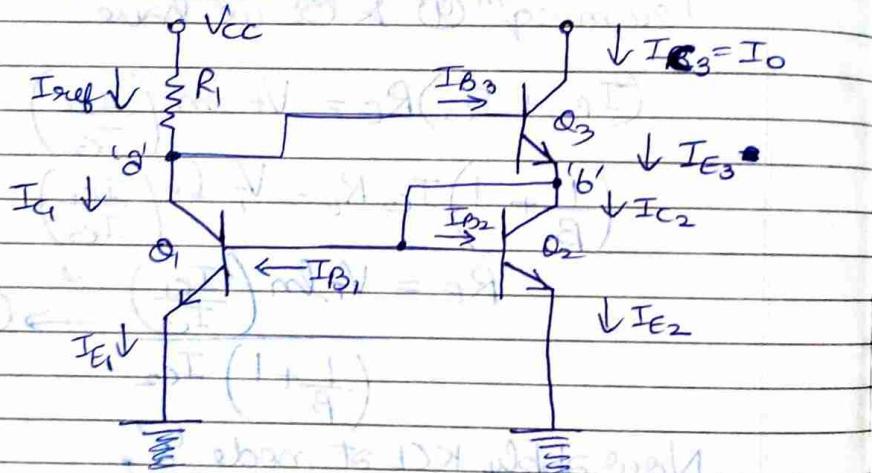

Consider transistor Q_1 & Q_2 are identical
i.e. $V_{BE_1} = V_{BE_2}$, $I_C = I_{C_2}$, $I_B = I_{B_2} = I_B$

Applying KCL at node 'b',

$$\Rightarrow I_{E_3} = I_{C_2} + I_{B_1} + I_{B_2}$$

$$I_{E_3} = I_{C_2} + \frac{I_{C_1}}{\beta} + \frac{I_{C_2}}{\beta}$$

$$I_{E_3} = \frac{I_{C_1} + I_{C_2}}{\beta} \left(1 + \frac{1}{\beta}\right)$$

$$\text{Since } I_{C_1} = I_{C_2}, \text{ so } I_{E_3} = \left(1 + \frac{2}{\beta}\right) I_{C_2} \rightarrow ①$$

I_{E_3} can also be written as,

$$I_{E_3} = I_{B_3} + I_{C_3}$$

$$I_{E_3} = \frac{I_{C_3} + I_{E_3}}{\beta} = \left(1 + \frac{1}{\beta}\right) I_{C_3} \rightarrow ②$$

Equating eqⁿ ① & ② we get,

$$\left(1 + \frac{2}{\beta}\right) I_{C_2} = \left(1 + \frac{1}{\beta}\right) I_{C_3}$$

$$I_{C_2} = \frac{(1+1/\beta)}{(1+2/\beta)} I_{C_3}$$

$$I_{C_3} = \frac{(1+2/\beta)}{(1+1/\beta)} I_{C_2}$$

$$\Rightarrow I_{C_3} = \frac{\beta+2}{\beta+1} I_{C_2}$$

Since $I_{C_1} = I_{C_2}$, $\therefore I_{C_1}$ or collector current of transistor Q_3 will be,

$$I_0 = \frac{(\beta+2)}{(\beta+1)} I_{C_1}$$

Now apply KCL at node 'a',

$$\Rightarrow I_{\text{ref}} = I_{C_1} + I_{B_3}$$

$$I_{\text{ref}} = I_{C_1} + \frac{I_{C_3}}{\beta}$$

$$I_{\text{ref}} = \frac{(\beta+1)}{(\beta+2)} I_0 + \frac{I_0}{\beta}$$

$$\Rightarrow I_{ref} = \left(\frac{\beta+1}{\beta+2} + \frac{1}{\beta} \right) I_0$$

$$\Rightarrow I_{ref} = \left(\frac{\beta^2 + \beta + \beta + 2}{\beta(\beta+2)} \right) I_0$$

$$\Rightarrow I_{ref} = \boxed{\left(\frac{\beta^2 + 2\beta + 2}{\beta(\beta+2)} \right) I_0}$$

where, $I_{ref} = \frac{V_{cc} - V_a}{R_1}$

where $V_a = V_{BE3} - V_{BE2} = 0$

$$V_a = V_{BE3} + V_{BE2}$$

Also $V_{BE3} = V_{BE2} = V_{BE}$

$$\Rightarrow \boxed{V_a = 2V_{BE}}$$

$$\Rightarrow \boxed{I_{ref} = \frac{V_{cc} - 2V_{BE}}{R_1}}$$

Thermal Drift of an Op-amp:

The dependence of op-amp parameters with temp which affects its performance is specified as op-amp thermal drift.

There can be changes in op-amp bias currents, input offset voltage and input offset current with temp. as given in the manufacturer's data sheet of specific op-amps.

$$\frac{\partial I}{\partial T} + \alpha T (\text{mV}) = \text{particular value}$$

$$\frac{I_C}{I_S} = e^{V_{BE1} - V_{BE2}/V_T} \rightarrow ③$$

Now apply