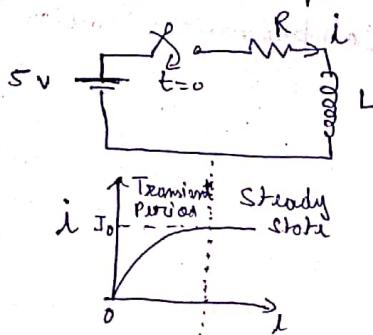


Difference between Transient & Steady State

- (ii) Transient :- Transient period is defined as that very short time period between two steady states.




- Before closing switch, current in circuit was zero, $I=0$ (Steady state)
- After closing switch at $t=0$, current will grow exponentially to steady value I_s . (New steady state)
- Time period between $i=0$ to $i=I_s$ is called transient period.

- Any disturbance (disturbance or change in steady state) causes transients in electric circuit.
 - Transients are entirely associated with the changes in stored energy in inductor and capacitors.
 - Since there is no stored energy in resistors, there are no transients in pure resistive circuits.
- (iii) Steady state - when transients die out, a new steady state is achieved.


Modelling of electrical System

- Any electrical system (electrical circuit / network) can be modelled in terms of differential equation.
- System response = Solution of differential equation.
- Solution of differential equation contains Complementary function (C.F.) and Particular Integral (P.I.).
- Complementary function gives transient response.
Note :- Transient response is also called natural or free response of a system.
- Particular Integral gives steady state response of a system. Steady state response is also called forced response of a system.

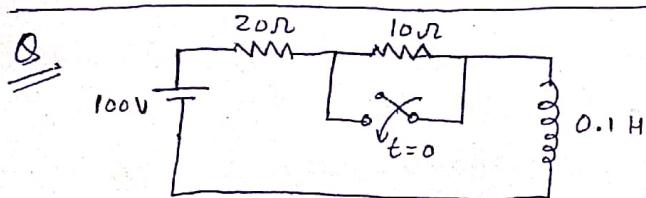

Initially circuit was in steady state before closing switch.
switch is closed at $t=0$
Find $i(t)$ supplied by 100V battery.

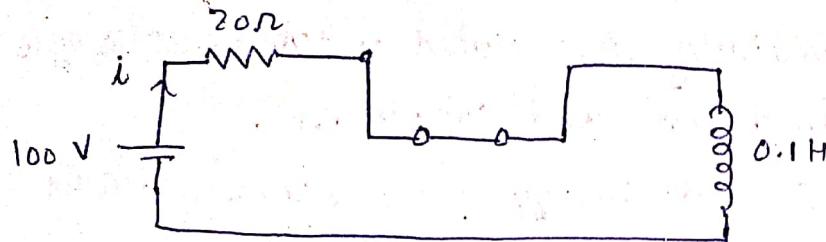Sol. When switch is closed at $t=0$, Resistor (10Ω) is bypassed from the circuit



Apply KVL

$$100 = i(t) 20 + 0.1 \frac{di(t)}{dt} \rightarrow \text{Differential equation}$$

$$i(t) = C.F + P.I.$$

~~C.F~~ $1000 = 200 i(t) + \frac{di(t)}{dt}$

$$(D + 200) i(t) = 1000$$

$$C.F \Rightarrow C.F \quad D + 200 = 0 \Rightarrow D = -200$$

$$C.F = C_1 e^{-200t}$$

$$P.I \Rightarrow i(t) = \int e^{-200t} \cdot 1000 dt$$

$$\Rightarrow \frac{1000 \times e^{-200t}}{-200} + C_2$$

(No need for constant of integration)


$$= 5$$

$$i(t) = C_1 e^{-200t} + 5$$

Due to presence of inductor

$$i(0^-) = i(0^+)$$

$$\text{For } i(0^-) \Rightarrow$$

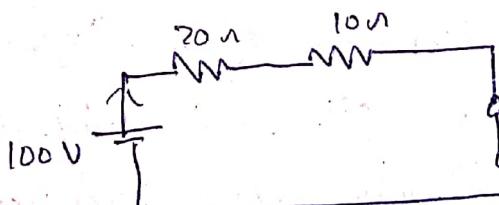

L short circuit
(under study state)

$$i(0^-) = \frac{100}{30} A$$

$$\therefore i(0^+) = \frac{10}{3} A$$


~~i(0)~~ $i(0) = C_1 e^{-200(0)} + 5$

$$\frac{10}{3} = C_1 + 5$$

$$C_1 = -\frac{5}{3}$$

$$i(t) = \left(-\frac{5}{3} e^{-200t} + 5 \right) A$$

Solution

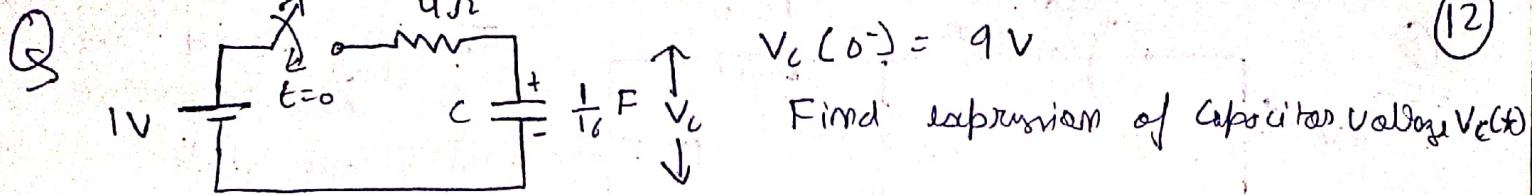

Sol.

$$i(t) = C \frac{dV_c}{dt}$$

$$\frac{1}{C} \int_0^t i(t) dt = dV_c$$

$$\frac{1}{C} \int_0^t i(t) dt = \int_9^{V_c} dV_c$$

$$V_c - 9 = \frac{1}{C} \int_0^t i(t) dt$$

$$V_c = \frac{1}{C} \int_0^t i(t) dt + 9$$

Apply KVL

$$I = i(t) 4 + V_c$$

$$I = 4i(t) + 16 \int_0^t i(t) dt + 9$$

Differentiate both sides

$$0 = 4 \frac{d i(t)}{dt} + 16 i(t)$$

$$i(t) = C.F + P.I.$$

$$P.I = 0$$

$$C.F \Rightarrow (4D + 16) i(t) = 0 \Rightarrow D = -4$$

$$i(t) = C_1 e^{-4t}$$

Circuit at $t = 0^+$

$$i(0^+) = \frac{1-9}{4} = -2$$

$$i(0) = C_1 e^{-4(0)}$$


$$-2 = C_1$$


$$\therefore i(t) = -2 e^{-4t}$$

$$V_c = 16 \int_0^t i(t) dt + 9 = 16 \int_0^t -2 e^{-4t} dt + 9$$

$$V_c = \frac{-32}{-4} [e^{-4t}]_0^t + 9 = 8[e^{-4t} - 1] + 9$$

$$V_c = 1 + 8e^{-4t}$$

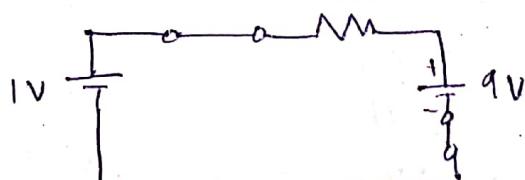


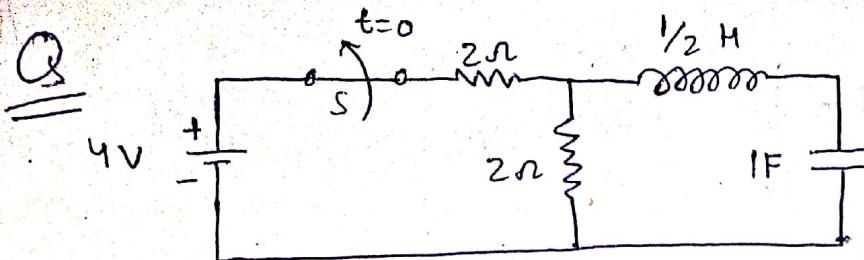

Initially switch S was closed and circuit was in steady state.

At $t=0$, switch S was opened. Find the expression for inductor current.


Sol. Circuit before opening switch S.

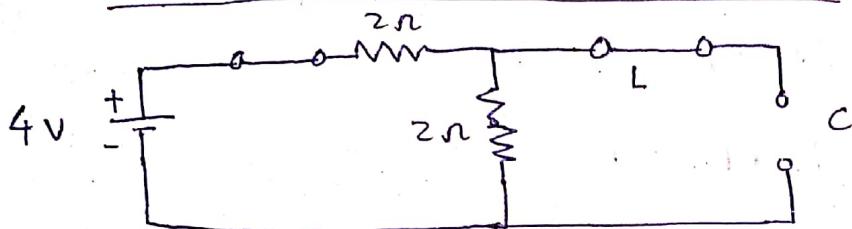

$$\text{Voltage across Capacitor (under steady state, } S \text{ closed)} = \left(\frac{4}{2+2} \right) \times 2 = 2 \text{ V}$$

$$\text{Inductor current (under steady state, } S \text{ closed)} = 0$$

Circuit After opening Switch S:

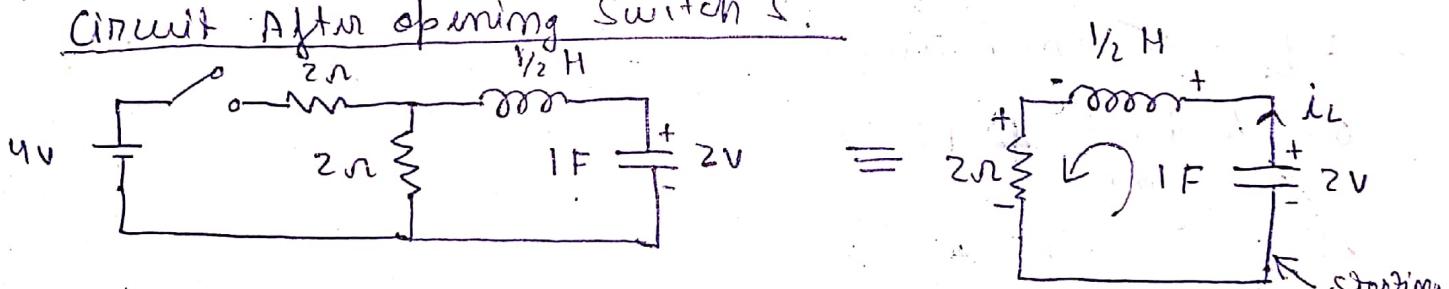

KVL in above circuit

$$V_C - \frac{d i_L(t)}{dt} - i_L(t) 2 = 0$$

$$\text{Also } i_L(t) = C \frac{d V_C}{dt}$$

$$\frac{1}{C} \int_0^t i_L(t) dt = \int_0^t \frac{d V_C}{dt} dt$$

$$\frac{1}{C} \int_0^t i_L(t) dt = V_C - 2$$

Put V_C in KVL eq.

$$\frac{1}{C} \int_0^t i_L(t) dt + 2 = \frac{1}{2} \frac{d i_L(t)}{dt} + 2 i_L(t)$$

Differentiate both sides

$$i_L(t) = \frac{1}{2} \frac{d^2 i_L(t)}{dt^2} + 2 \frac{d i_L(t)}{dt}$$

(13)

$$\frac{d^2 i_L(t)}{dt^2} + 4 \frac{di_L(t)}{dt} - 2 i_L(t) = 0$$

$$i_L(t) = C.F.$$

$$C.F. \Rightarrow D^2 + 4D - 2 = 0$$

$$D = \frac{-4 \pm \sqrt{16 - 4(-2)}}{2} = -4.449, 0.449,$$

$$i_L(t) = C_1 e^{-4.449t} + C_2 e^{0.449t}$$

Initial condition after opening switch at $t=0$

$$(i) i_L(0^+) = 0$$

(ii) Since voltage across capacitor cannot change instantaneously & inductor current is zero, therefore, voltage across inductor should be 2V (It should follow KVL)

$$V_L = L \frac{di_L}{dt} \Rightarrow 2 = \frac{1}{2} \frac{di_L}{dt} \quad @ t=0^+$$

$$\therefore \frac{di_L}{dt} = 4 \text{ at } t=0^+ \Rightarrow \frac{di_L(0^+)}{dt} = 4$$

$$i_L(0) = C_1 + C_2 \rightarrow \text{from initial condition I}$$

$$0 = C_1 + C_2$$

$$C_1 = -C_2$$


$$\frac{di_L(0^+)}{dt} = C_1 \times (-4.449) e^{-4.449t} + C_2 \times (0.449) e^{0.449t}$$

$$4 = -4.449 C_1 + 0.449 C_2$$

$$C_2 = 0.816, C_1 = -0.816$$

$$\therefore i_L(t) = -0.816 e^{-4.449t} + 0.816 e^{0.449t}$$

Solution.

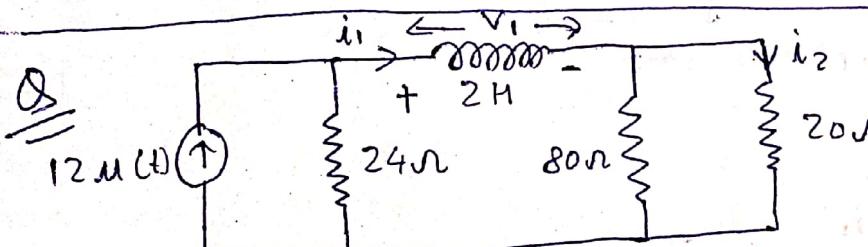

Find i_1, i_2, V_1 at

(i) $t=0^+$

(ii) $t=0^-$

(iii) $t=\infty$


(iv) $t=50\text{ms}$

Sol. (ii) Since excitation source is Step signal, it has zero value for $t < 0$.

$$\therefore i_1(0^-) = 0; i_2(0^-) = 0; V_1(0^-) = 0.$$

(i) $t = 0^+$ (initial stage)

Eq. circuit at $t = 0^+$

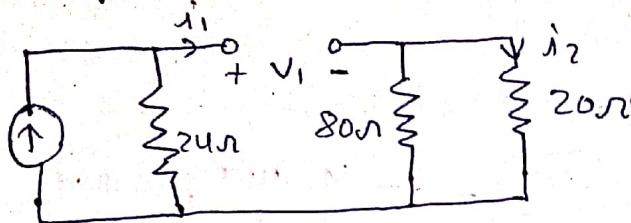


$$i_1(0^+) = 0$$

$$i_2(0^+) = 0$$

$$\begin{aligned} V_1(0^+) &= \text{Voltage across } 24\Omega \\ &= 24 \times 12 = 288 \text{ V} \end{aligned}$$

(ii) $t = \infty$ (Final or steady state)

Eq. circuit at $t = \infty$

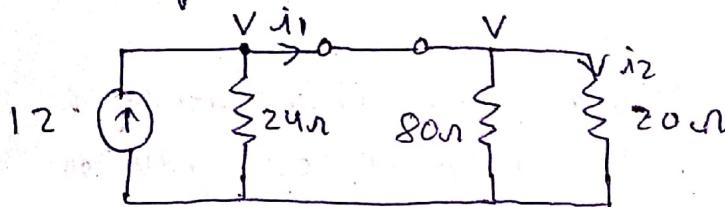

Applying KCL at the node

$$12 = \frac{V}{24} + \frac{V}{80} + \frac{V}{20} = 0.0416V + 0.0125V + 0.05V = 0.1041V$$

$$V = 115.2 \text{ V}$$


$$i_1 = 12 - \frac{115.2}{24} = 7.2 \text{ A}$$

$$i_2 = \frac{115.2}{20} = 5.76$$

$$V_1 = 0$$

$$\therefore i_1(\infty) = 7.2 \text{ A}; i_2(\infty) = 5.76 \text{ A} \quad V_1(\infty) = 0$$

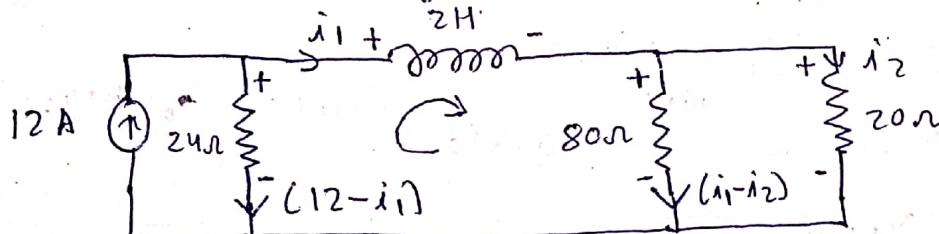(iv) General expression for $i_1(t)$, $i_2(t)$, $V_1(t)$



KVL in ~~left side~~ right side loop

$$80(i_1 - i_2) = 20i_2$$

$$80i_1 = 100i_2$$

$$i_2 = \frac{80}{100}i_1$$

KVL in left side loop

$$(12 - i_1)24 - 2 \frac{di_1}{dt} - 80(i_1 - i_2) = 0$$

$$288 - 24i_1 - 2 \frac{di_1}{dt} - 80\left(i_1 - \frac{80}{100}i_1\right) = 0$$

$$288 = 40i_1 + 2 \frac{di_1}{dt} \Rightarrow \frac{di_1}{dt} + 20i_1 = 144$$

$$i_1(t) = C_1 e^{-20t} + e^{-20t} \int 144 e^{20t} dt$$

$$i_1(t) = C_1 e^{-20t} + 7.2$$

$$i_1(0) = C_1 + 7.2 \rightarrow \text{initial condition}$$

$$\therefore C_1 = -7.2$$

$$i_1(t) = -7.2 e^{-20t} + 7.2 = 7.2 (1 - e^{-20t})$$

$$i_2(t) = 0.8 i_1(t) = 5.76 (1 - e^{-20t})$$


$$V_1(t) = L \frac{di_1}{dt}$$

$$= 2 \left[\frac{d}{dt} [7.2(1 - e^{-20t})] \right] = 2(-7.2)(-20) e^{-20t}$$

$$V_1(t) = 288 e^{-20t}$$

$$i_1(0.05) = 4.55 \text{ A} ; i_2(0.05) = 3.64 \text{ A} ; V_1(0.05) = 105.4 \text{ V}$$

Q

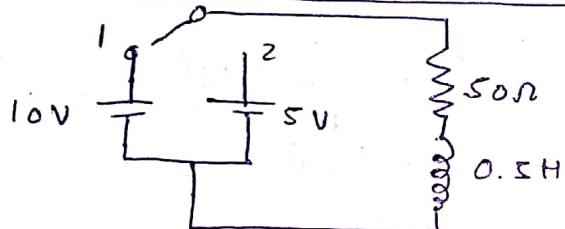


At $t=0$ switch is closed at position 1

After $t=0.5\text{ms}$ switch is moved to position 2.

Find $i(t)$ in both cases.

Sol:

Switch at position 1

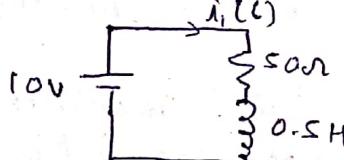

$$10 = i_1 50 + 0.5 \frac{di_1}{dt}$$

$$20 = 100i_1 + \frac{di_1}{dt}$$

$$i_1(t) = C_1 e^{-\frac{Rt}{L}} + \text{steady state current}$$

$$i_1(t) = C_1 e^{-100t} + 0.2$$

$$i_1(0) = C_1 + 0.2$$

$$0 = C_1 + 0.2$$


$$C_1 = -0.2$$

$$i_1(t) = -0.2 e^{-100t} + 0.2$$

$$i_1(0.0005) = -0.2 e^{-100(0.0005)} + 0.2$$

$$i_1(0.0005) = 0.00975$$

Switch at position 2

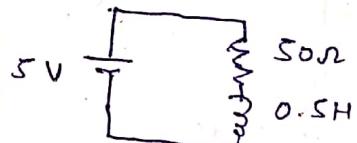

$$5 = i_2 50 + 0.5 \frac{di_2}{dt}$$

$$10 = 100i_2 + \frac{di_2}{dt}$$

$$i_2(t) = C_2 e^{-\frac{R(t-t')}{L}} + \text{steady state current}$$


$$i_2(t) = C_2 e^{-100(t-0.0005)} + 0.1$$

$$i_2(0.0005) = C_2 + 0.1$$


$$0.00975 = C_2 + 0.1$$

$$C_2 = -0.001 - 0.0902$$
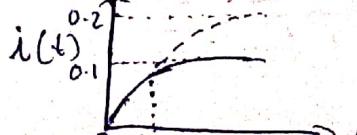
$$i_2(t) = -0.0902 e^{-100(t-0.0005)} + 0.1$$



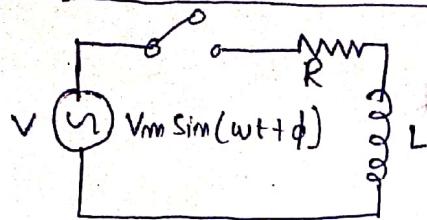Transient response with sinusoidal excitation



$V = V_m \sin(wt + \phi)$ where ϕ varies from 0 to 2π depending on the switching instant.

Switch is closed at $t=0^+$



$$Ri + L \frac{di}{dt} = V_m \sin(wt + \phi)$$

$$i(t) = C.F. + P.I.$$

$$C.F. = C_1 e^{-\frac{Rt}{L}} \xrightarrow{\substack{\text{Dies out after} \\ \text{some time}}} \text{Transient}$$


P.I. = Steady state current
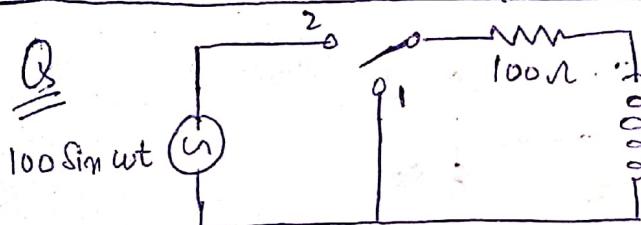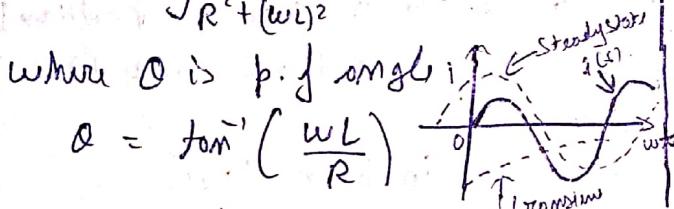
$$P.I. = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(wt + \phi - \theta)$$



System frequency is 50 Hz

Sol. Switch in position 2

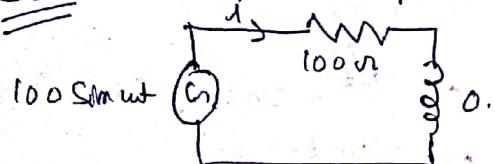

KVL in the loop.


$$100i + 0.1 \frac{di}{dt} = 100 \sin wt$$

$$1000i + \frac{di}{dt} = 1000 \sin wt$$

$$i(t) = C.F. + P.I.$$

$$C.F. = C_1 e^{-\frac{100t}{0.1}}$$
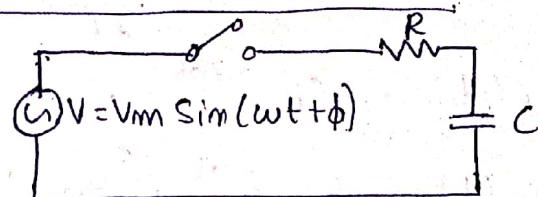
$$P.I. = \frac{100}{\sqrt{(100)^2 + (2\pi(50)0.1)^2}} \sin \left(wt - \tan^{-1} \frac{2\pi(50)(0.1)}{100} \right)$$



Switch is closed at $t=0^+$ ($t=0$)

$$iR + \frac{1}{C} \int i dt + V_c(0^+) = V_m \sin(wt + \phi)$$

Differentiate both the sides

$$R \frac{di}{dt} + \frac{1}{C} i = w V_m \cos(wt + \phi)$$

$$i(t) = C.F. + P.I.$$

$$C.F. = C_1 e^{-\frac{t}{RC}} \xrightarrow{\substack{\text{Dies out after} \\ \text{some time}}} \text{Transient}$$

P.I. = Steady state current

$$P.I. = \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin(wt + \phi + \theta)$$

where θ is p.f. angle

$$\theta = \tan^{-1} \frac{1}{\omega CR}$$

Initially switch was in position 1 and steady state in inductor was 1 A.

At $t=0$ switch is moved to 2.

Final expression for $i(t)$

$$P.I. = \frac{100}{104.8} \sin(\omega t - 17.43^\circ)$$

$$= 0.954 \sin(\omega t - 17.43^\circ)$$

$$i(t) = C_1 e^{-1000t} + 0.954 \sin(\omega t - 17.43^\circ)$$

$$i(0) = 1 \text{ A} \quad (\text{Initial Condition})$$

$$1 = C_1 + 0.954 \sin(-17.43^\circ)$$

$$1 = C_1 + (-0.285)$$


$$C_1 = \cancel{0.285} \quad 1.285$$

$$i(t) = 1.285 e^{-1000t} + 0.954 \sin(\omega t - 17.43^\circ)$$

$$i(t) = 1.285 e^{-1000t} + 0.954 \sin(\omega t - 17.43^\circ)$$

Solution.

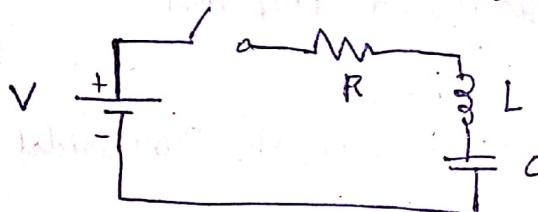Transient response in RLC circuit with DC excitation



Switch is closed at $t=0$

Apply KVL.

$$V = i(R) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i dt + V_c(0)$$

Differentiate both sides

$$0 = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$


$$i(t) = C_1 e^{P_1 t} + C_2 e^{P_2 t}$$

$$P_1, P_2 = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}} = \omega \pm \beta$$

$$\omega = -\frac{R}{2L}, \beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$


Case I : If ρ_1 & ρ_2 are real & unequal. $\left[\left(\frac{R}{2L} \right)^2 > \frac{1}{LC} \right]$
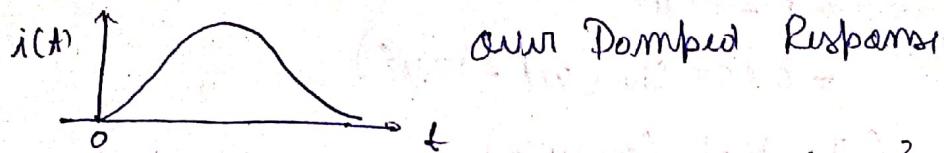
$$i(t) = e^{\rho_1 t} (C_1 e^{\rho_2 t} + C_2 e^{-\rho_2 t})$$




Case II If $\rho_1 = \rho_2$ ($R = 0$) $\left[\left(\frac{R}{2L} \right)^2 = \frac{1}{LC} \right]$
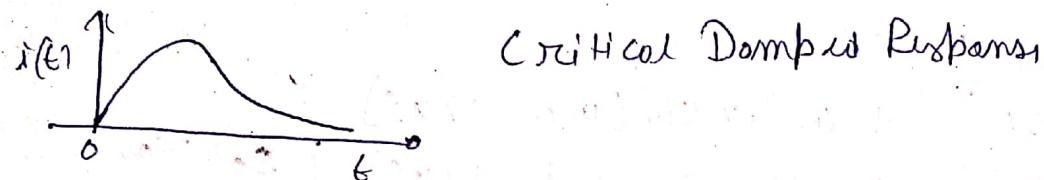
$$\therefore i(t) = e^{\rho t} (C_1 + C_2 t)$$




Case III If ρ_1 & ρ_2 are complex conjugates $\left[\left(\frac{R}{2L} \right)^2 < \frac{1}{LC} \right]$
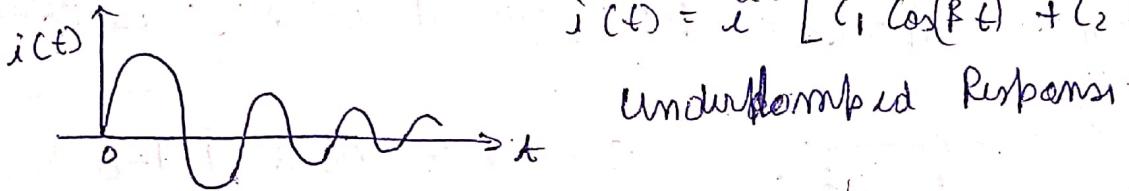
$$i(t) = e^{\rho t} [C_1 \cos(\beta t) + C_2 \sin(\beta t)]$$



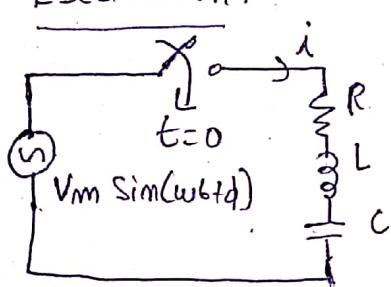Transient Response in Series RLC Circuit with Sinusoidal Excitation.



$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i dt + V_c \cos(\omega t + \phi) = V_m \sin(\omega t + \phi)$$

Differentiate both sides

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = \omega V_m \cos(\omega t + \phi)$$


$$i(t) = C.F. + P.I$$

C.F. gives transient response and it is same as in Case I of RLC with DC excitation (Above Case).

P.I. gives steady state response

$$P.I. = \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L \right)^2}}$$

$$\sin \left[\omega t + \phi + \tan^{-1} \left(\frac{\frac{1}{\omega C} - \omega L}{R} \right) \right]$$

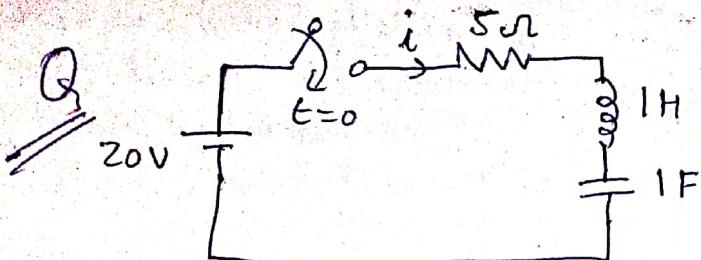Find $i(t)$

Initially there is no energy stored in the system.

Sol. Apply KVL

$$20 = 5i + 1 \frac{di}{dt} + \frac{1}{t} \int_0^t i dt$$

Differentiate both sides

$$0 = 5 \frac{di}{dt} + \frac{d^2 i}{dt^2} + i \Rightarrow \frac{d^2 i}{dt^2} + 5 \frac{di}{dt} + i = 0$$

$$i = C.F. + P.I.$$

$$P.I. = 0$$

$$C.F. \Rightarrow D^2 + 5D + 1 = 0$$

$$D = \frac{-5 \pm \sqrt{25-4}}{2} = -0.21, -4.79$$

$$\therefore i(t) = C_1 e^{-0.21t} + C_2 e^{-4.79t}$$

$$\text{Initial condition: } i(0^+) = 0$$

$$V_C(0^+) = 0 \quad (\text{Behaviour of capacitor})$$

$$V_R(0^+) = 0 \quad (\text{No current out } t=0^+)$$

$$\therefore V_L(0^+) = 20V \quad (\text{To satisfy KVL})$$

$$V_L(0^+) = L \frac{di(0^+)}{dt} = 20V$$

$$\therefore i(0^+) = C_1 + C_2$$

$$0 = C_1 + C_2$$

$$C_1 = -C_2$$

$$\frac{di(0^+)}{dt} = -0.21C_1 - 4.79C_2$$


$$20 = -0.21(-C_2) - 4.79C_2$$

$$20 = 0.21C_2 - 4.79C_2$$

$$C_2 = -4.36$$


$$C_1 = 4.36$$
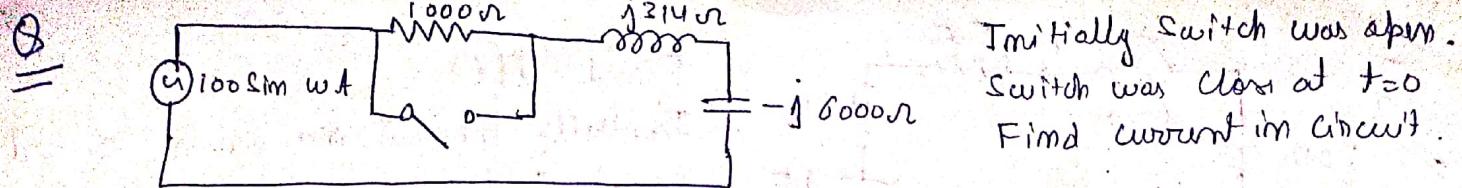
$$\therefore i(t) = 4.36 e^{-0.21t} - 4.36 e^{-4.79t}$$



Initially switch was open.
Switch was closed at $t=0$.
Find current in circuit.

Sol Switch in open position

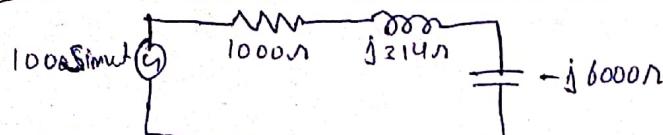


$$\text{Steady state current} = \frac{100 \sin(wt + \tan^{-1}(\frac{j214}{R}))}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$i(\infty) = \frac{100}{\sqrt{(1000)^2 + (5686)^2}} \sin(wt + \tan^{-1}(\frac{5686}{1000}))$$

$$i(\infty) = 0.0173 \sin(wt + 80^\circ)$$

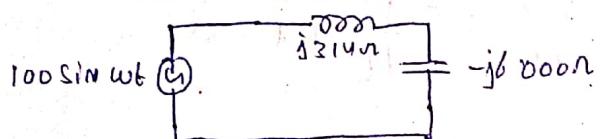Switch in close position (Resistor is bypassed)



$$\text{KVL in loop: } 100 \sin wt = i \frac{di}{dt} + \frac{1}{5.2 \times 10^{-7}} \int i dt + V_C(0^+)$$

$$w 100 \cos wt = \frac{d^2 i}{dt^2} + \frac{1}{5.2 \times 10^{-7}} i$$

$$i(t) = C.F + P.I$$

$$C.F \Rightarrow \left(D^2 + \frac{1}{5.2 \times 10^{-7}} \right) = 0 \quad , \quad D = \pm j1373.6$$

$$C.F = C_1 \cos(1373.6 t) + C_2 \sin(1373.6 t)$$

$$P.I = \text{Steady state current} = \frac{100}{5686} \sin(wt + 90^\circ)$$

$$P.I = 0.0176 \sin(wt + 90^\circ) = 0.0176 \cos wt$$

$$i(0^+) = 0.0173 [\sin(w(0) + 80^\circ)] = 0.0173 \times \sin 80^\circ = 0.0170$$

$$V_C = 0.0173 \angle 80^\circ \times 6000 \angle -90^\circ \rightarrow \text{switch in open condition}$$

$$= 103.8 \angle -10^\circ = 103.8 \sin(wt - 10^\circ)$$

$$V_C(0^+) = 103.8 \sin(w(0) - 10^\circ) = -18.02$$

Voltage across inductor at $t=0^+$ = - (Voltage across capacitor at $t=0^+$)

$$i \frac{di}{dt}(0^+) = 18.02$$

$$18.02 = -C_1 (1373.5) \sin(1373.5(0)) + C_2 (1373.5) \cos(1373.5(0))$$

$$18.02 = C_2 (1373.5)$$

$$C_2 = 0.0131$$

$$i(0^+) = C_1 + 0.0176$$

$$0.0170 = C_1 + 0.0176$$

$$C_1 = -0.0006$$

$$i(t) = -0.0006 \cos(1373.5t) + 0.0131 \sin(1373.5t) + 0.0176 \sin(wt + 90^\circ)$$