

## Experiment - 7

\* Aim :- to study the operation of a Full Subtractor.

\* Apparatus :- Breadboard, connecting wires, power supply, IC 7408, IC 7432, IC 7480, IC 7404, LED Display board.

\* Theory :- A full subtractor is a combinational circuit that performs the subtraction involving three bits. It has three inputs A, B and Bin and two outputs D (Difference) and Bout (Borrow out). It can be implemented by using two half subtractors.


\* Procedure :-

1. Connect the IC on breadboard.
2. Give +5V to pin 14 and ground pin 7
3. Connect the input pins in A, B and Bin of IC from binary switches.
4. Connect output pins D and Bout of IC from LED.
5. Switch on the power supply and change the input combinations at every instant.
6. Verify the truth table.

\* Result :- the truth table for Full Subtractor is verified.

\* Precautions :-

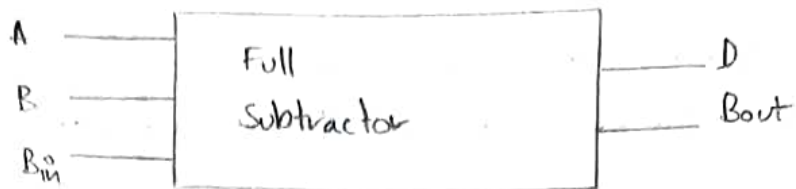1. Insert the IC carefully on the breadboard.
2. Take care while supplying voltage to the IC.
3. Connections should be made according to the diagrams.



★ Truth table

A	B	$B_{in}$	D	$B_{out}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

★ K-Map for D (Difference)

		$B_{in}$			
		00	01	11	10
A	0		(1)		(1)
	1	(1)		(1)	

$$D = \bar{A}\bar{B}B_{in} + \bar{A}B\bar{B}_{in} + AB\bar{B}_{in} + \bar{A}BB_{in} = A \oplus B \oplus B_{in}$$

★ K-Map for B<sub>out</sub> (Borrow out)

		00	01	11	10
A \ B <sub>in</sub>	0	0	1	1	0
	1	0	1	0	1

$$B_{out} = \bar{A}B_{in} + BB_{in} + \bar{A}B$$

$$= \bar{A}B + B_{in}(\bar{A} + B)$$

★ Circuit Diagram of Full Subtractor

