

Unit - 1

DC

O BASIC ELEMENTS



Active Elements

→ These Elements which supply / deliver Electrical Energy

For ex: Battery, Generator, Operational Amplifier, Transistor, current source, voltage source, etc.



Passive Elements

→ These elements can only store / receive energy, which it can either dissipate or absorb.

For ex: Resistor, Inductor, Capacitor, Transformer, Switch, etc.

- Bilateral Elements: The elements in which magnitude of current remains same regardless of the direction.

For ex : Resistor

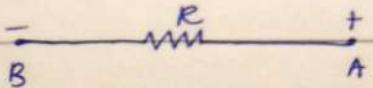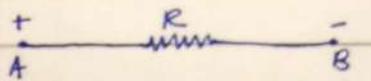


- Unilateral Elements: The elements in which there is a change in functioning when direction of current changes.

For ex : Diode



(Forward Bias)

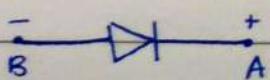

(Reverse Bias)

○ Electric Current (I): Rate of flow of Electrical charge

$$I = \frac{dq}{dt}$$

(Unit → Ampere (A))

1 Coulomb = 6.25×10^{18} e⁻s
(A)

Electric Charge (q⁻) = 1.602×10^{-19} C


○ Ohm's law

The voltage across a conductor is directly proportional to the current flowing through it, provided all physical conditions & temperature remains constant.

$$\begin{aligned} V &\propto I \\ \Rightarrow V &= IR \end{aligned}$$

○ Laws of Resistance
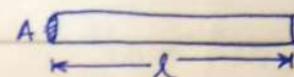
$$\left. \begin{array}{l} 1^{\text{st}} : R \propto l \\ 2^{\text{nd}} : R \propto \frac{1}{A} \end{array} \right\} \Rightarrow R = \frac{\rho l}{A}$$



$\rho \rightarrow$ resistivity
(unit: $\Omega \text{ m}$ (ohm))

• Conductance: Reciprocal of Resistance.
It offers the flow of current.

$$G = \frac{1}{R}$$

(unit → mho)

• Conductivity (σ): Reciprocal of Resistivity.

$$\sigma = \frac{1}{\rho}$$

(unit → mho/m
or
siemens/m)

- Potential Energy Difference: The potential diff. b/w two points is the amount of Electrical Energy required to move a unit charge b/w two points.


$$\frac{V_B - V_A \text{ OR}}{A \leftarrow V_A - V_B \rightarrow B} \quad [\text{unit} \rightarrow \text{volt (V)}]$$

- Electromotive force (emf): emf is equal to the terminal voltage when no current flows. It is the force that causes an electric current to flow in an electric circuit.

[unit → volt (V)]

- Terminal Voltage: The potential difference across the terminals of a load when current flows through the circuit.

$$V_{AB} = \epsilon - Ir$$

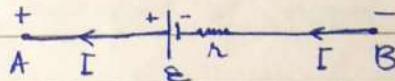

Sources

Independent Sources

→ value does not depend upon any other voltage & current.

(i) Voltage Source (constant voltage across two terminals)



(ii) Current Source (maintains constant current).



Dependent Sources

→ Value depends upon some voltage or current.


(i) VDVS (Voltage depended Voltage Source)

(ii) CDCS (current depended current source)

(iii) VDGS (Voltage depended current source)

(iv) CDVS (current depended voltage source)

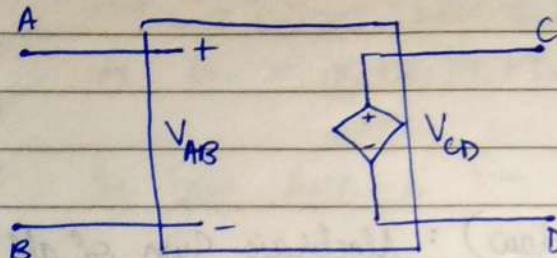
(i) Voltage depended Voltage Source (VDVS)



$$V_{CD} \propto V_{AB}$$


$$\Rightarrow V_{CD} = M V_{AB}$$

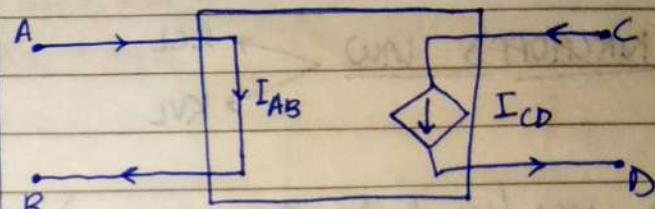(ii) Current depended Current Source (CDCS)




$$I_{CD} \propto I_{AB}$$

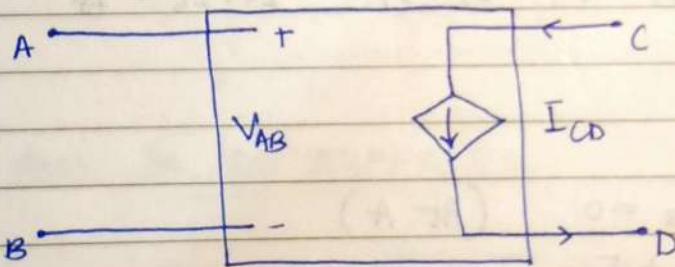(iii) Voltage depended current Source (VDCS)



$$I_{CD} \propto V_{AB}$$

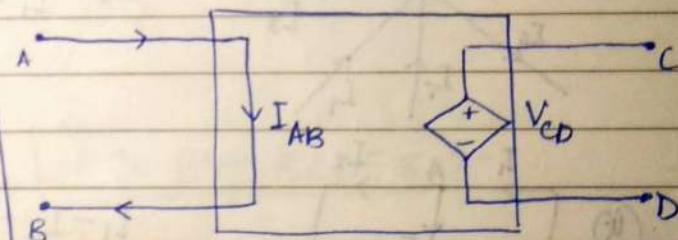(iv) Current depended voltage Source (CDVS)




$$V_{CD} \propto I_{AB}$$


Unit - 1 DC

□ KIRCHHOFF'S LAW \longleftrightarrow KCL \longleftrightarrow KVL


i) KCL (Kirchoff's Current Law) (Junction law) : Algebraic sum of all currents meeting at a junction / point is zero.
OR

Sum of incoming current on a junction is equal to sum of outgoing current.

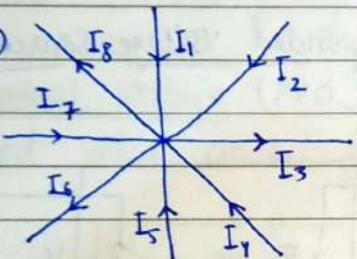(i)  $I_1 + I_2 - I_3 + I_4 + I_5 - I_6 + I_7 - I_8 = 0$
 $\Rightarrow I_1 + I_2 + I_4 + I_5 + I_7 = I_3 + I_6 + I_8$.

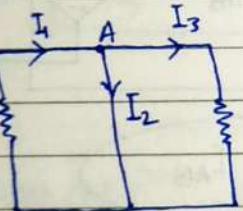(ii)  $I_1 - I_2 - I_3 = 0 \quad (\text{At A})$
 $\Rightarrow I_1 = I_2 + I_3$

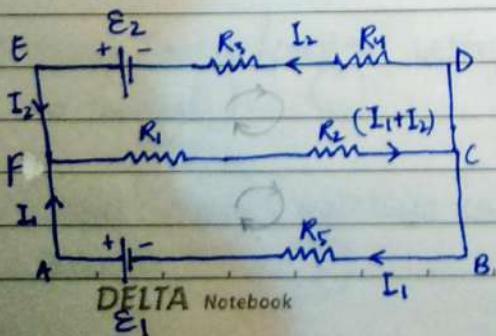2) KVL (Kirchoff's Voltage Law) (Loop law) : The algebraic sum of emfs acting in a circuit is equal to the algebraic sum of products of current & resistance



In loop ABCFA :

$$E_1 - R_1(I_1 + I_2) - R_2(I_1 + I_2) - I_1 R_5 = 0$$
 $\Rightarrow E_1 = (R_1 + R_2)(I_1 + I_2) + I_1 R_5$

In loop EDCFE :-


$$-\varepsilon_2 + I_2 R_3 + I_2 R_4 + R_3(I_2 + I_1) + R_2(I_1 + I_2) = 0$$

$$\Rightarrow \varepsilon_2 = (R_1 + R_2)(I_1 + I_2) + I_2(R_3 + R_4)$$

In loop ABDEA :-

$$\varepsilon_1 - \varepsilon_2 + I_2 R_3 + I_2 R_4 - I_1 R_5 = 0$$
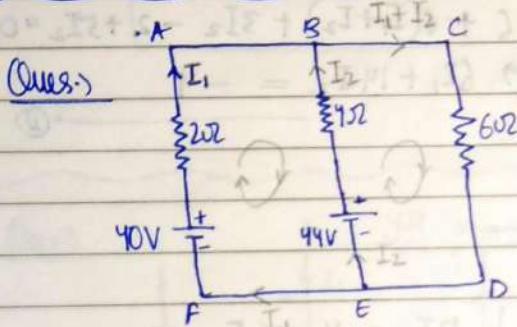
$$\Rightarrow \varepsilon_1 - \varepsilon_2 = I_1 R_5 - I_2(R_3 + R_4)$$



(Ques.) Calculate current through each battery & the load.

Ans.) In loop ABFEDA :-

$$40 - 2I_1 + 4I_2 - 44 = 0$$

$$\Rightarrow 4I_2 - 2I_1 = 4$$

$$\Rightarrow 2I_2 - I_1 = 2 \quad \text{--- (I)}$$

In loop BCDEB :-

$$44 - 4I_2 - 6(I_1 + I_2) = 0$$

$$\Rightarrow 6I_1 + 10I_2 = 44$$

$$\Rightarrow 3I_1 + 5I_2 = 22 \quad \text{--- (II)}$$

Solving eqn. (I) × 3 & eqn. (II) :-

$$-3I_1 + 6I_2 = 6$$

$$3I_1 + 5I_2 = 22$$

$$11I_2 = 28$$


$$\Rightarrow I_2 = \frac{28}{11} A$$

$$\Rightarrow I_1 = 2I_2 - 2$$

$$\Rightarrow I_1 = \frac{2 \times 28}{11} - 2$$

$$\Rightarrow I_1 = \frac{34}{11} A$$

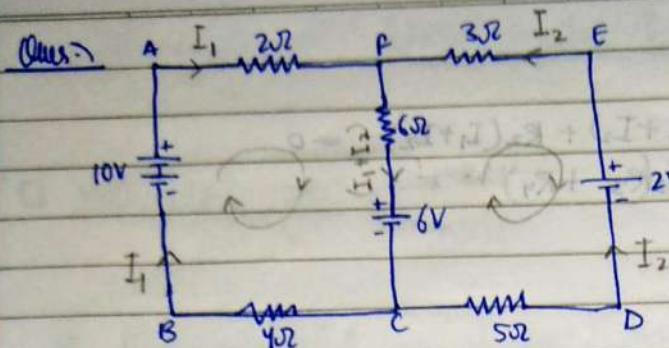DELTA Notebook
load current = $I_1 + I_2 = \frac{62}{11} A$



find current through each battery.

Ans:- In loop AFCBA :-

$$10 - 2I_1 - 6(I_1 + I_2) - 6 - 4I_1 = 0 \\ \Rightarrow 12I_1 + 6I_2 = 4 \quad \text{--- (1)}$$

In loop FEDCF :-

$$6 + 6(I_1 + I_2) + 3I_2 - 2 + 5I_2 = 0 \\ \Rightarrow 6I_1 + 14I_2 = -4 \quad \text{--- (2)}$$


Solving eqn (1) & (2) $\times 2$:-

$$\begin{aligned} 12I_1 + 28I_2 &= -8 \\ 12I_1 + 6I_2 &= 4 \\ 22I_2 &= -12 \\ I_2 &= -\frac{6}{11} \text{ A} \end{aligned}$$

$$\begin{aligned} 12I_1 &= 4 - 6I_2 \\ 12I_1 &= 4 + \frac{36}{11} \\ I_1 &= \frac{20}{33} \text{ A} \end{aligned}$$

and,
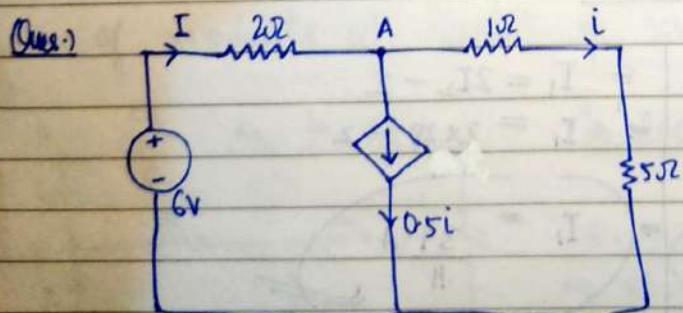
$$(I_1 + I_2) = \frac{20}{33} - \frac{6}{11} = \frac{2}{33} \text{ A}$$




Determine current (i) in 5Ω resistor.

Ans.) KCL at A node : —

$$I = 0.5i + i \\ = 1.5i$$

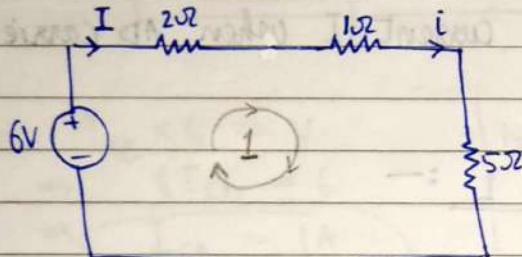
(Now, let's neglect \downarrow dependent source)



In loop 1 :

$$6 - 2I - i - 5i = 0 \\ \Rightarrow 2I + (i) = 6 \\ \Rightarrow 2(1.5i) + 6i = 6 \\ \Rightarrow i = \frac{6}{9} = \frac{2}{3} A$$

Ques.)

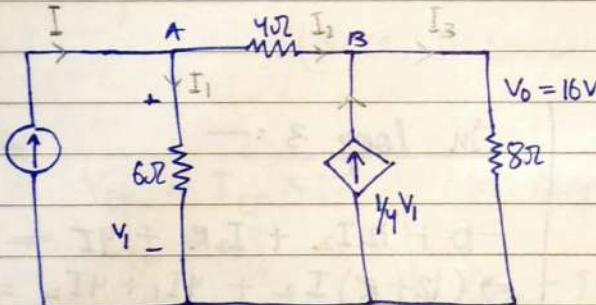

Calculate the value of
 V_1, I_1, I_2, I_3 .

$$\text{Ans.) } I_3 = \frac{V_0}{R} = \frac{16}{8} = 2A$$

Now,

KCL at point B : —

$$\frac{1}{4}V_1 = I_2 + I_3$$


$$V_{AB} = I_2 \times 4 \\ \Rightarrow V_B - V_A = 4I_2 \\ \Rightarrow 16 - V_1 = 4I_2 \\ \Rightarrow 16 - 4I_2 - 4I_3 = 4I_2 \\ \Rightarrow 8I_2 + 8 = 16 \\ \Rightarrow I_2 = 1A$$

$$\text{So, } V_1 = 4I_2 + 4I_3 \\ \Rightarrow V_1 = 4(1+2) \\ \Rightarrow V_1 = 12V$$

so, $V_1 = I_1 \times 6$
 $\Rightarrow I_2 = 6I_1$
 $\Rightarrow I_1 = 2A$

and, $I + I_2 - I_1 = 0$ (KCL at A)
 $\Rightarrow I = I_1 - I_2$
 $\Rightarrow I = 2 - 1$
 $\Rightarrow I = 1A$

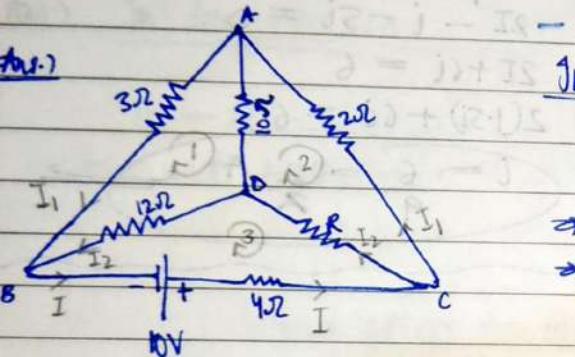Ques: Find value of resistance R & current I when AD carries no current.



In loop 1 :-

$$3I_1 - 12I_2 + 0(10\Omega) = 0$$
 $\Rightarrow 12I_2 = 3I_1$
 $\Rightarrow I_1 = 4I_2$

In loop 2 :-


$$2I_1 - RI_2 + 0(10) = 0$$
 $\Rightarrow RI_2 = 2I_1$
 $\Rightarrow R = \frac{2I_1}{I_2}$
 $\Rightarrow R = \frac{2(4I_2)}{I_2}$
 $\Rightarrow R = 8\Omega$

In loop 3 :-

$$-10 + 12I_2 + I_2R + 4I = 0$$
 $\Rightarrow (12+R)I_2 + 4I_1 + 4I_2 = 10$
 $\Rightarrow 4I_1 + (16+R)I_2 = 10$
 $\Rightarrow 16I_2 + 16I_2 + 8I_2 = 10$
 $\Rightarrow I_2 = \frac{1}{4}A$

so, $I_1 = 4I_2$
 $= 1A$

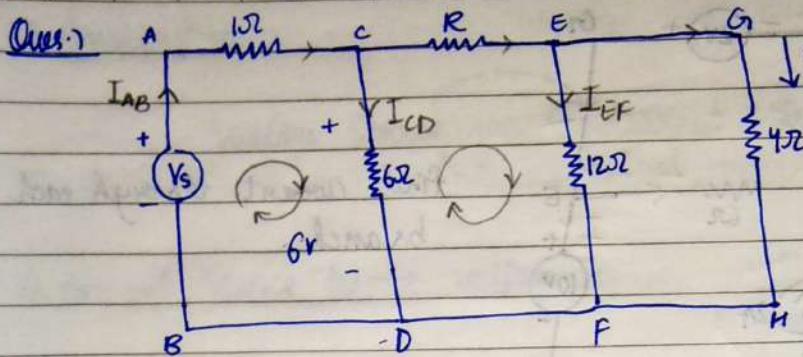so, $I = I_1 + I_2$
 $\Rightarrow I = \frac{5}{4}A$



Calculate value of R and V_s?

$$\begin{aligned} \text{Ans.) } & I_{CD} \times 6 = V \\ & \Rightarrow 6I_{CD} = 6 \\ & \Rightarrow I_{CD} = 1 \text{ A} \end{aligned}$$

Now, Voltage across GH :-

$$\begin{aligned} V_{GH} &= \frac{3}{4} \times 4 \\ &= 3 \text{ V} \end{aligned}$$

Now, Voltage across EF will be = voltage across GH
(since, || connection)

$$\begin{aligned} \text{So, } & V_{EF} = I_{EF} \times 12 \\ & \Rightarrow I_{EF} = \frac{3}{12} \\ & \Rightarrow I_{EF} = \frac{1}{4} \text{ A} \end{aligned}$$


In loop CEFDC :-

$$\begin{aligned} & 6I_{CD} - I_{CE}R - 12I_{EF} = 0 \\ & \Rightarrow 6 \times 1 - 1 \times R - 12 \times \frac{1}{4} = 0 \quad \left(I_{CE} = I_{EF} + I_{GH} \right) \\ & \Rightarrow R = 3\Omega \end{aligned}$$

Now,

In loop ACDRA :-
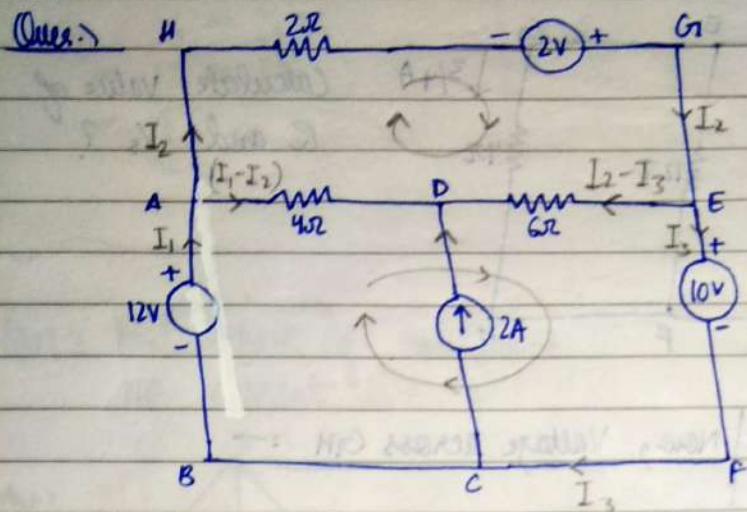
$$\begin{aligned} & V_s - I_{AB} \times 1 - 6I_{CD} = 0 \quad (\because I_{AB} = I_{CD} + I_{CE}) \\ & \Rightarrow V_s - 2 \times 1 - 6 \times 1 = 0 \\ & \Rightarrow V_s = 8 \text{ V} \end{aligned}$$



find current through each branch.

Ans.) KCL at point D :-

$$I_4 - I_2 + I_2 - I_3 + 2 = 0 \\ \Rightarrow I_3 - I_1 = 2 \quad \text{--- (1)}$$

KVL in loop AEFAE :-

$$I_2 - 4(I_1 - I_2) + 6(I_2 - I_3) - 10 = 0 \\ \Rightarrow I_2 - 4I_1 + 4I_2 + 6I_2 - 6I_3 - 10 = 0 \\ \Rightarrow 4I_1 - 10I_2 + 6I_3 = 2 \quad \text{--- (II)}$$

KVL in loop HGEAH :-

$$2 - 6(I_2 - I_3) + 4(I_1 - I_2) - 2I_2 = 0 \\ \Rightarrow 6I_2 - 6I_3 - 4I_1 + 4I_2 + 2I_2 = 2 \\ \Rightarrow -4I_1 + 12I_2 - 6I_3 = 2 \quad \text{--- (III)}$$

Adding eqn. (II) & (III) :-

$$4I_1 - 10I_2 + 6I_3 = 2 \\ \cancel{-4I_1 + 12I_2 - 6I_3 = 2}$$

$$2I_2 = 4 \\ \Rightarrow I_2 = 2A$$

eqn. (II) :

$$4I_1 - 10I_2 + 6I_3 = 2$$

$$4I_1 - 20 + 6I_3 = 2$$

$$2I_1 + 3I_3 = 11 \quad \text{--- (IV)}$$

Solving eqn (I) × 2 & (IV)

$$2I_1 + 3I_3 = 11$$


$$-2I_1 + 2I_3 = 4$$

$$I_3 = 15/5$$

$$\Rightarrow I_3 = 3A$$


So, $I_1 = 1A$

Conversions

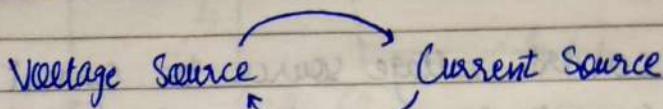


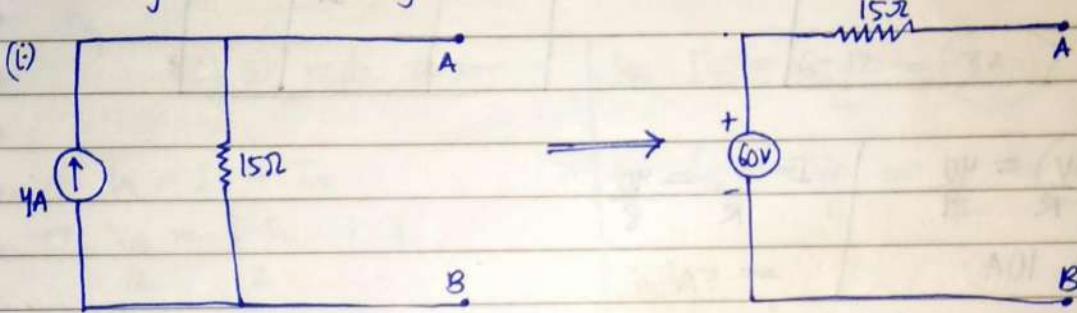1) Current Source to → Voltage Source.

→ If current source is to be converted to voltage source, then join the voltage source with resistor in series.


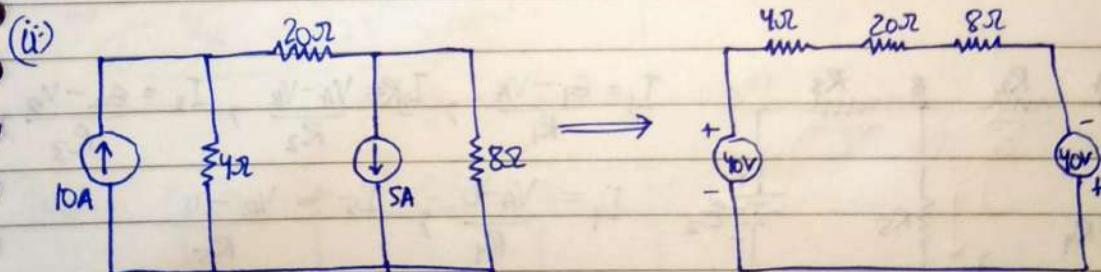
$$\begin{aligned} V &= IR \\ &= 4 \times 15 \\ &= 60 \text{ V} \end{aligned}$$




$$\begin{aligned} V &= IR \\ &= 10 \times 4 \\ &= 40 \text{ V} \end{aligned}$$

$$\begin{aligned} V &= IR \\ &= 5 \times 8 \\ &= 40 \text{ V} \end{aligned}$$

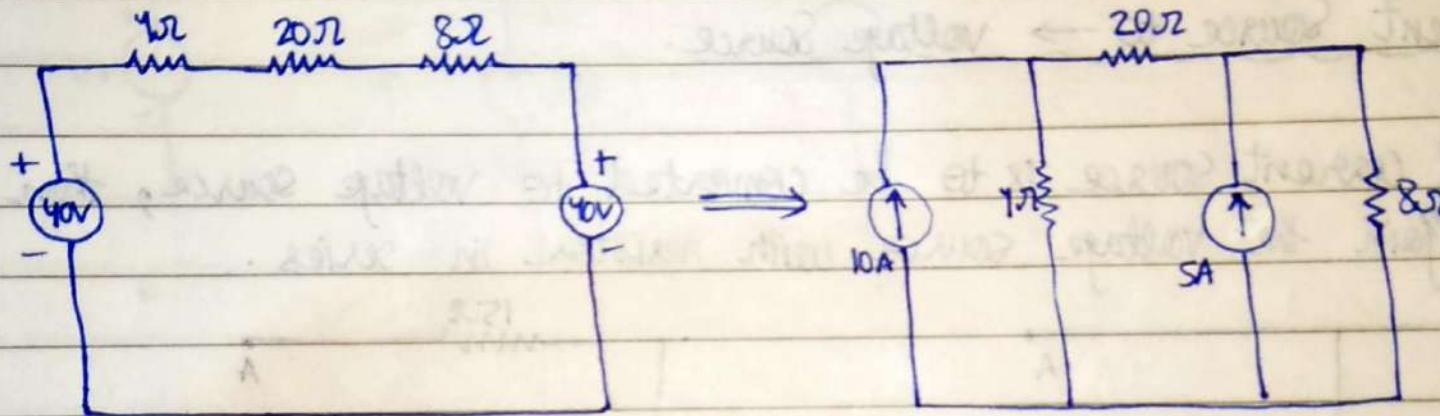2) Voltage Source \rightarrow Current Source

\rightarrow If we have to convert voltage source to current source, then join the current source with resistor/lead in parallel.




$$I = \frac{V}{R} = \frac{40}{4}$$

$$= 10A$$

$$I = \frac{V}{R} = \frac{40}{8}$$

$$= 5A$$

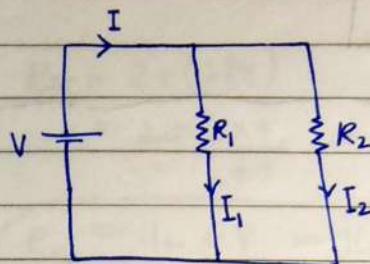Unit - 1◎ Current Division Rule

We know: In Parallel combination:—

Voltage remains same in all resistor
and current is different.

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} \xrightarrow{\text{So,}} V = I R_{\text{eq}}$$

$$= I \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$


So,

$$I_1 = \frac{V}{R_1}$$

$$\Rightarrow I_1 = I \left(\frac{R_1 R_2}{R_1 + R_2} \right) \frac{1}{R_1} \quad \text{Similarly,}$$

$$\Rightarrow I_1 = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \frac{R_1}{R_1 + R_2}$$

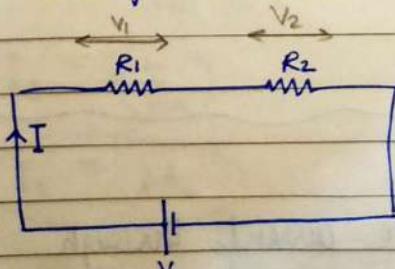◎ Voltage Distribution Rule

We know: In Series combination :-

current remains same and voltage is
different in all resistor

$$R_{\text{eq}} = R_1 + R_2 \xrightarrow{\text{So,}}$$

$$V = I R_{\text{eq}}$$

$$\Rightarrow I = \frac{V}{R_1 + R_2}$$

So,

1 - (in)

$$V_1 = IR_1$$

$$\Rightarrow V_1 = \left(\frac{V}{R_1 + R_2} \right) R_1$$


similarly,

$$\Rightarrow V_1 = \frac{VR_1}{R_1 + R_2}$$

$$V_2 = \frac{VR_2}{R_1 + R_2}$$

Unit - 1 DC Circuits

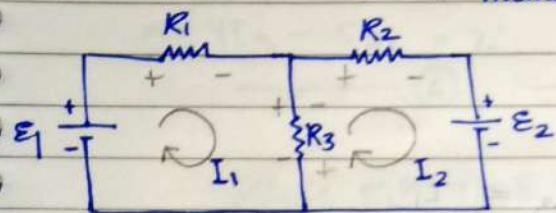□ MESH ANALYSIS → In this method we use KVL in a different method and develop a technique which makes analysing circuits easier than KVL.



Step 1 : To consider mesh currents in either clockwise or anti-clockwise.

→ Step 2 : Write the mesh equations to all meshes using KVL and then use Ohm's law.

In mesh 1 :-

$$\epsilon_1 - I_1 R_1 - I_1 R_3 + I_2 R_3 = 0$$

$$\Rightarrow I_1 (R_1 + R_3) - I_2 R_3 = \epsilon_1 \quad \text{--- (1)}$$


In mesh 2 :-

$$-I_2 R_3 + I_1 R_3 - I_2 R_2 - \epsilon_2 = 0$$

$$\Rightarrow I_1 R_3 - I_2 (R_2 + R_3) = \epsilon_2 \quad \text{--- (2)}$$

and get :-

$I_1 \neq I_2$ value.

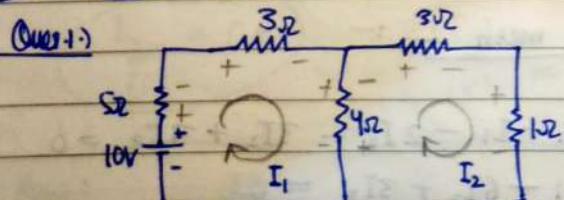

find current across 1Ω resistor.

Ans:- $10 - 5I_1 - 3I_1 - 4I_1 + 4I_2 = 0$

$$\Rightarrow 12I_1 - 4I_2 = 10$$

$$\Rightarrow 6I_1 - 2I_2 = 5 \quad \text{--- (1)}$$

andy in mesh 2 :-

$$-4I_2 + 4I_1 - 3I_2 - I_2 = 0$$

$$\Rightarrow 4I_1 - 8I_2 = 0$$

$$\rightarrow I_1 - 2I_2 = 0$$

11

Subtracting ① - ⑪ : -

$$\begin{array}{rcl} 6I_1 - 2I_2 & = & 5 \\ \hookrightarrow I_1 + 2I_2 & = & 0 \end{array}$$

$$\Rightarrow \underline{I_1 = 1A}$$


$$I_2 = \frac{I_1}{2}$$

$$\rightarrow I_2 = 0.5 \text{ A}$$

80

$$\text{Current across } 1\Omega \text{ resistor} = 0.5 \text{ A}$$

Ques 2:-

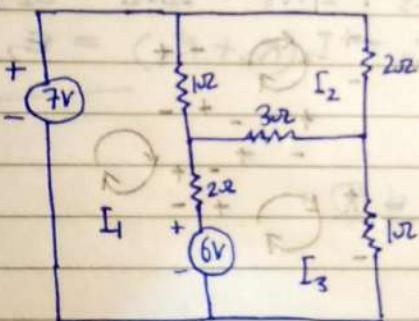

Calculate current in each branch.

Ans.) In mesh 1 :-

$$-6 + 7 - I_1 + I_2 - 2I_4 + 2I_3 = 0$$

$$\Rightarrow 3I_1 - I_2 - 2I_3 = 1$$

— ①

In mesh 2 :-

$$-I_2 + I_1 - 2I_3 - 3I_4 + 3I_5 = 0$$

$$I_1 - 6I_2 + 3I_3 = 0$$

— ⑪

In mesh is :-

$$6 - 2I_3 + 2I_1 - 3I_3 + 3I_2 - I_3 = 0$$

$$\text{DELTANotebook } -2I_1 - 3I_2 + 6I_3 = 6$$

三

Solving eqⁿ. (II) $\times 2$ & (III) :-

$$\begin{aligned} 2I_1 - 12I_2 + 6I_3 &= 0 \\ -2I_1 - 3I_2 + 6I_3 &= 6 \\ 12I_3 - 15I_2 &= 6 \\ \Rightarrow 4I_3 - 5I_2 &= 2 \end{aligned}$$

(a)

Solving eqⁿ. (II) $\times 3$ & (I) :-

$$\begin{aligned} 3I_1 - 18I_2 + 9I_3 &= 0 \\ 6I_1 + 3I_2 - 2I_3 &= 1 \\ 11I_3 - 17I_2 &= -1 \end{aligned}$$

(b)

Solving eqⁿ. (a) $\times 11$ & (b) $\times 4$:-

$$\begin{aligned} 44I_3 - 55I_2 &= 22 \\ 44I_3 + 68I_2 &= -4 \\ 13I_2 &= 26 \\ I_2 &= 2A \end{aligned}$$

$$\begin{aligned} I_3 &= \frac{5(2) + 2}{4} \\ I_3 &= 3A \end{aligned}$$

So,

$$\begin{aligned} I_1 &= 6I_2 - 3I_3 \\ \Rightarrow I_1 &= 6 \times 2 - 3 \times 3 \\ \Rightarrow I_1 &= 3A \end{aligned}$$

So,

$$I_{12} = I_1 - I_2 = 3 - 2$$

(ii) $= 1A$

$$I_{12} = I_3$$

(ii) $= 3A$

$$I_{32} = I_3 - I_2$$


(ii) $= 1A$

$$I_{2R} = 0A$$

(ii)

$$I_{2R} = I_2$$

(ii) $= 2A$

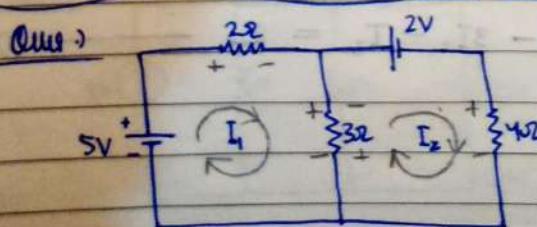

Calculate current across 3Ω resistor.

Ans.) In mesh 1:

$$5 - 2I_1 - 3I_2 + 3I_2 = 0 \\ \Rightarrow 5I_1 - 3I_2 = 5 \quad \text{--- (1)}$$

In mesh 2:

$$-2 - 4I_2 - 3I_2 + 3I_1 = 0 \\ \Rightarrow 3I_1 - 7I_2 = 2 \quad \text{--- (2)}$$

Solving eqn. (1) $\times 3$ & (2) $\times 5$:-

$$\begin{aligned} \Rightarrow 15I_1 - 35I_2 &= 10 \\ 15I_1 + 9I_2 &= 15 \\ -26I_2 &= -5 \\ \Rightarrow I_2 &= \frac{5}{26} \text{ A} \end{aligned}$$

$$\begin{aligned} I_1 &= \frac{5 + 3 \times \frac{5}{26}}{5} \\ &= \frac{145}{5 \times 26} = \frac{29}{26} \text{ A} \end{aligned}$$

So,


$$\text{Current across } 3\Omega \text{ resistor} = I_1 - I_2$$

$$= \frac{29}{26} - \frac{5}{26}$$

$$= \frac{24}{26} \text{ A}$$

$$= \frac{12}{13} \text{ A}$$

Ques.)

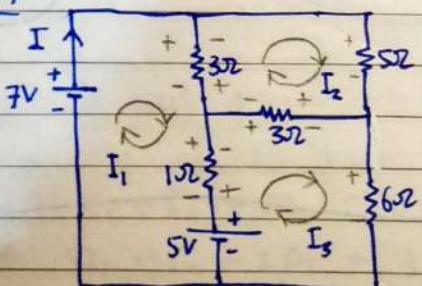

find current I :

Ans.) In mesh 1 :

$$7 - 3I_1 + 3I_2 - I_1 + I_3 - 5 = 0 \\ \Rightarrow 4I_1 - 3I_2 - I_3 = 2 \quad \text{--- (1)}$$

In mesh 2 :

$$-3I_2 + 3I_1 - 5I_2 - 3I_2 + 3I_3 = 0$$

$$\Rightarrow 3I_1 - 11I_2 + 3I_3 = 0 \quad \text{--- (2)}$$

In mesh 3 :

$$5 - I_3 + I_1 - 3I_3 + 3I_2 - 6I_3 = 0 \\ \Rightarrow -I_1 - 3I_2 + 10I_3 = 5 \quad \text{--- (III)}$$

Solving eqn. (III) $\times 3$ & eqn. (II) :-

$$\begin{aligned} -3I_1 - 9I_2 + 30I_3 &= 15 \\ 3I_1 - 11I_2 + 3I_3 &= 0 \\ \hline 23I_3 - 20I_2 &= 15 \end{aligned} \quad \text{--- (a)}$$

Solving eqn. (III) $\times 4$ & eqn. (I) :-

$$\begin{aligned} -4I_1 - 12I_2 + 40I_3 &= 20 \\ 4I_1 - 3I_2 - I_3 &= 2 \\ \hline 39I_3 - 15I_2 &= 22 \end{aligned} \quad \text{--- (b)}$$

Solving eqn. (b) $\times 4$ & eqn. (a) $\times 3$:-

$$\begin{aligned} 156I_3 - 60I_2 &= 88 \\ (-) 99I_3 + 60I_2 &= 95 \\ \hline 57I_3 &= 143 \\ \Rightarrow I_3 &= 0.754 \text{ A} \end{aligned}$$

$$I_2 = \frac{39 \times 0.754 - 22}{15}$$

$$\Rightarrow I_2 = 0.493 \text{ A}$$


So,

$$I_1 = -5 - 3 \times 0.493 + 10 \times 0.754 \\ \Rightarrow I_1 = 1.061 \text{ A}$$

So, $I = I_1 = 1.061 \text{ A}$



(Question related to Source Conversion)

(Ans.)

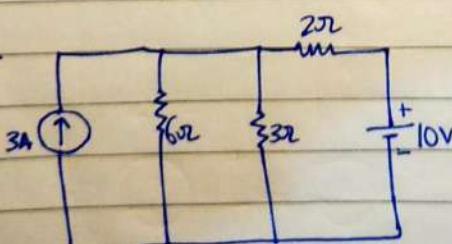

Calculate current across 3Ω resistor.

thus can be redrawn as :-

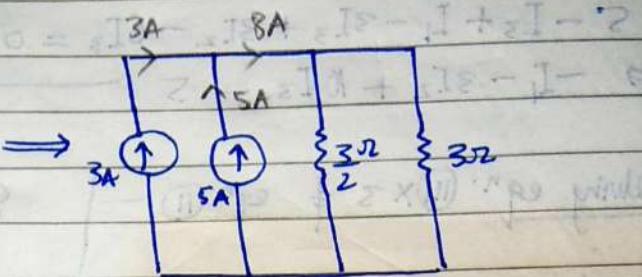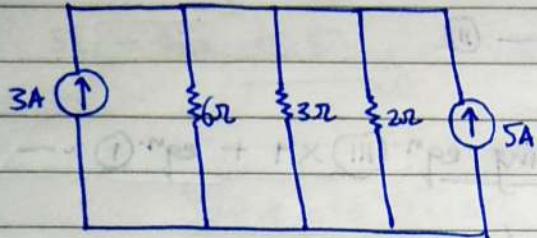

Using current division Rule :-


$$I_{3\Omega} = 8 \times \frac{3/2}{3 + 3/2}$$

$$\Rightarrow I_{3\Omega} = 8 \times \frac{3}{9}$$


$$\Rightarrow I_{3\Omega} = \frac{8}{3} A$$

(This question can be done using KVL/mesh or any other method.)


TRANSFORMATIONS (Star & Delta).

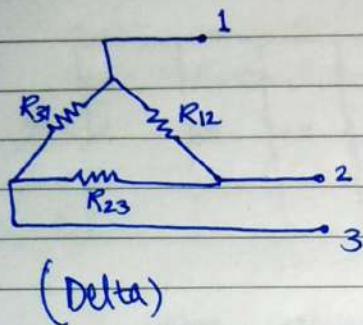

\approx
(equivalent)

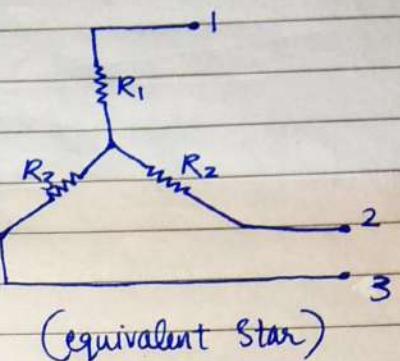


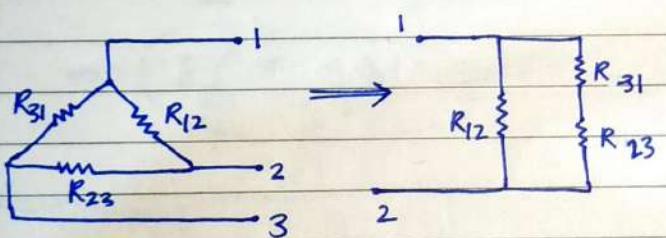1. Delta $\xrightarrow{\text{to}}$ Star Transformation



$$\text{So, } \frac{1}{R_{\text{eq}}(12)} = \frac{1}{R_{12}} + \frac{1}{R_{23} + R_{31}} \\ \Rightarrow R_{\text{eq}}(12) = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

but, In star :

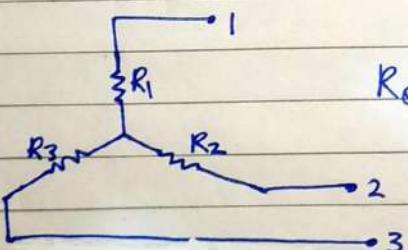

$$R_{\text{eq}}(12) = R_1 + R_2$$

$$\Rightarrow R_1 + R_2 = R_{12}(R_{23} + R_{31}) \quad \text{--- (a)}$$

$$R_{12} + R_{23} + R_{31}$$

Similarly,

In case of terminal 2 \neq 3 :

$$R_2 + R_3 = \frac{R_{23}(R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (b)}$$

In case of terminal 3 ≠ 1 :-

$$R_3 + R_1 = \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (1)}$$

Now,

Subtracting (1) - (6) :

$$R_1 + R_3 - R_2 - R_3 = \frac{R_{12}R_{31} - R_{12}R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 - R_2 = \frac{R_{12}R_{31} - R_{12}R_{23}}{R_{12} + R_{23} + R_{31}}$$

similarly,

we can find values of R_2 & R_3 .

Now, adding this eqn. ≠ (1) :

$$2R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\Rightarrow R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (e)}$$

$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (f)}$$

$$R_3 = \frac{R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (g)}$$

2] Star-to \rightarrow Delta Transformation

eqn. (2) \times (f) :-

$$R_1 R_2 = \frac{R_{12}^2 R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- (1)}$$

eqn. (f) \times (g) :-

$$R_2 R_3 = \frac{R_{12} R_{23}^2 R_{31}}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- (2)}$$

eqn. (2) \times (g) :-

$$R_3 R_1 = \frac{R_{12} R_{23} R_{31}^2}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- (3)}$$

Now, Adding eqn. ①, ② & ③ :-

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})^2} (R_{12} + R_{23} + R_{31})$$

$$\Rightarrow R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} \cdot R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (4)}$$

Now, putting eqn. (9) in eqn. (4) :-

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = R_{12} \left(\frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} \right)$$

$$\Rightarrow R_{12} \cdot R_3 = R_1 R_2 + R_2 R_3 + R_3 R_1$$

$$\Rightarrow R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


Similarly, we can find R_{23} & R_{31} :-

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

(Ans.)

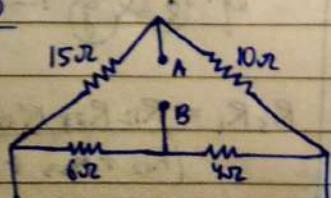

find the equivalent resistance between points A - B.

Ans.) $R_{eq}(\text{AB}) = (15+6) \parallel (10+4)$


$\Rightarrow " = 21 \parallel 14$

$\Rightarrow " = \frac{21 \times 14}{21 + 14}$



$\Rightarrow " = \frac{3 \times 21 \times 14}{355}$

$\Rightarrow " = \frac{42}{5}$

$R_{eq}(\text{AB}) = 8.4 \Omega$

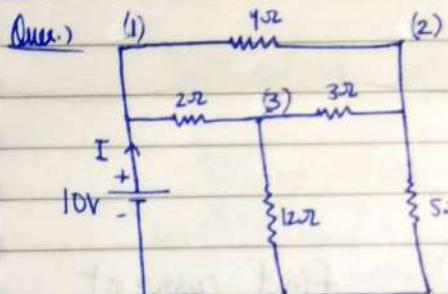

find current I.

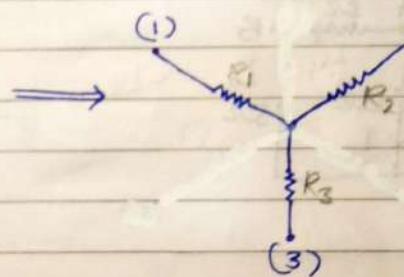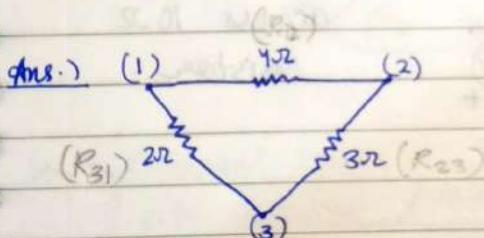

$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$



$$= \frac{4 \times 2}{2 + 3 + 4} = \frac{8}{9} \Omega$$


$$R_2 = \frac{4 \times 3}{2 + 3 + 4}$$

$$= \frac{12}{9} \Omega$$

$$R_3 = \frac{3 \times 2}{2 + 3 + 4}$$

$$= \frac{6}{9} \Omega$$

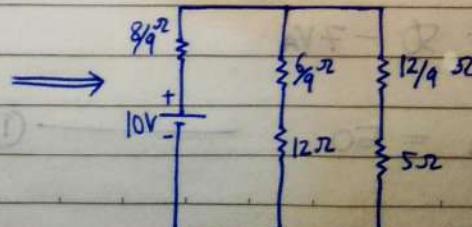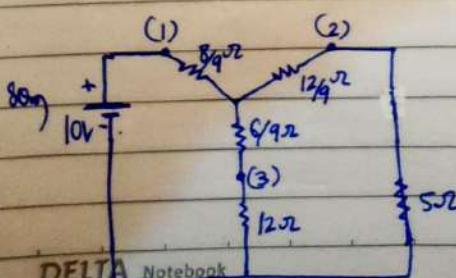

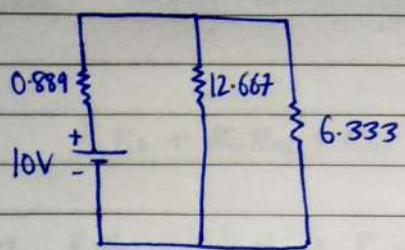


$$\begin{aligned}
 R_{eq} &= 0.889 + (12.667 \parallel 6.333) \\
 &= 0.889 + \frac{12.667 \times 6.333}{12.667 + 6.333} \\
 &= 0.889 + \frac{80.220}{19} \\
 &= 5.111 \Omega
 \end{aligned}$$

Soln

$$I = \frac{V}{R_{eq}} = \frac{10}{5.111}$$

$$\Rightarrow I = 1.956 \text{ A}$$

(Question of Nodal Analysis)

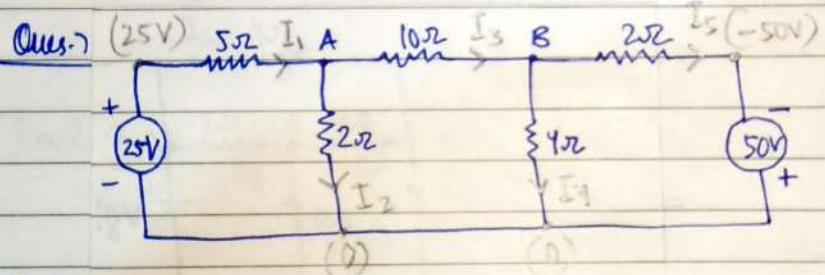

find current across 10 ohm resistor

Ans.)

KCL at node A :-

$$I_1 = I_2 + I_3$$

$$\Rightarrow \frac{25 - V_A}{5} = \frac{V_A - 0}{2} + \frac{V_A - V_B}{10}$$

$$\Rightarrow \frac{V_A - V_B}{10} = \frac{2(25 - V_A) - 5V_A}{10}$$

$$\Rightarrow V_A - V_B = 50 - 7V_A$$

$$\Rightarrow 8V_A - V_B = 50 \quad \text{--- (1)}$$

Now, KCL at Node B :-

$$I_3 = I_4 + I_5$$

$$\Rightarrow \frac{V_A - V_B}{10} = \frac{V_B - 0}{4} + \frac{V_B - (-50)}{2}$$

$$\Rightarrow \frac{V_A - V_B}{5} = \frac{V_B + 2V_B + 100}{4}$$

$$\Rightarrow 2V_A - 2V_B = 5V_B + 10V_B + 500$$

$$\Rightarrow 2V_A - 17V_B = 500 \quad \text{--- (i)}$$

Subtracting eqn. (i) from eqn. (ii) × 4 :

$$\begin{aligned} 8V_A - 68V_B &= 2000 \\ \cancel{8V_A} \cancel{+ V_B} &= \cancel{-50} \\ -67V_B &= 1950 \\ \Rightarrow V_B &= -29.10 \text{ V} \end{aligned}$$


$$\begin{aligned} V_A &= \frac{50 + V_B}{8} \\ \Rightarrow V_A &= \frac{50 - 29.10}{8} \\ \Rightarrow V_A &= 2.61 \text{ V} \end{aligned}$$

So, (Current across
10Ω resistor) $I_s = \frac{V_A - V_B}{10}$
 $\Rightarrow I_3 = \frac{2.61 - (-29.10)}{10}$

$$\Rightarrow I_3 = 3.17165 \text{ A}$$

Unit - 1

◎ Current Division Rule

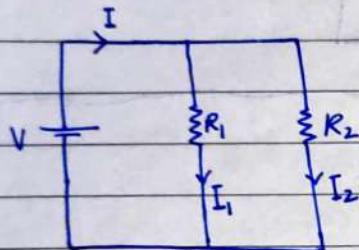

we know: In Parallel combination: —

voltage remains same in all resistor
and current is different.

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} \quad \xrightarrow{\text{so,}}$$

$$\begin{aligned} V &= I R_{\text{eq}} \\ &= I \left(\frac{R_1 R_2}{R_1 + R_2} \right) \end{aligned}$$

∴

$$I_1 = \frac{V}{R_1}$$


$$\Rightarrow I_1 = I \left(\frac{R_1 R_2}{R_1 + R_2} \right) \frac{1}{R_1}$$

Similarly,

$$\Rightarrow I_1 = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \frac{R_1}{R_1 + R_2}$$

◎ Voltage Distribution Rule

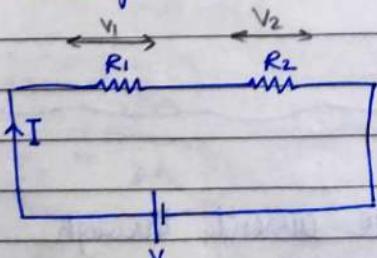

we know: In Series combination :-

current remains same and voltage is different in all resistor

∴

$$R_{\text{eq}} = R_1 + R_2 \quad \xrightarrow{\text{so,}}$$

$$\begin{aligned} V &= I R_{\text{eq}} \\ \Rightarrow I &= \frac{V}{R_1 + R_2} \end{aligned}$$

So,

$$V_1 = IR_1$$




$$\rightarrow V_1 = \left(\frac{V}{R_1 + R_2} \right) R_1 \quad \text{similarly,}$$

$$\rightarrow \boxed{V_1 = \frac{VR_1}{R_1 + R_2}}$$

$$\boxed{V_2 = \frac{VR_2}{R_1 + R_2}}$$


SUPERPOSITION THEOREM

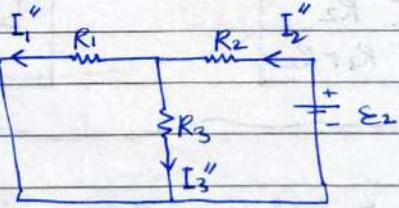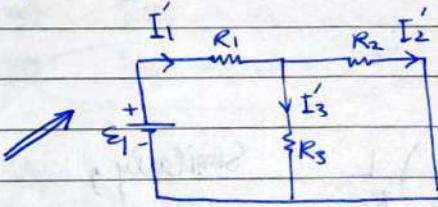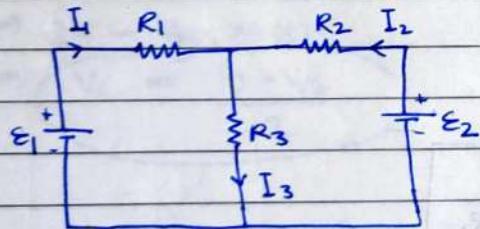
→ If more than one source acts simultaneously in an Electric Circuit, then the current through any one of the branches of the circuit is the summation of currents which would flow through the branch of each source, keeping all the other sources short circuited / dead.



$$\begin{aligned} I_1 &= I_1' - I_1'' \\ I_2 &= -I_2' + I_2'' \\ I_3 &= I_3' + I_3'' \end{aligned}$$

Calculate current through each resistor.

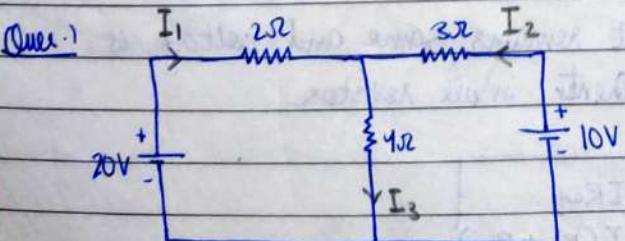

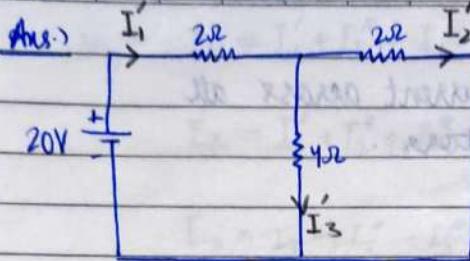

$$R_{eq} = 2 + (2 \parallel 4)$$

$$\therefore R_{eq} = 2 + \frac{2 \times 4}{2+4}$$

$$R_{eq} = \frac{12+8}{6} = \frac{10}{3} \Omega$$

$$\text{So, } I_1' = \frac{V}{R_{eq}} = \frac{20}{10/3} = 6A$$

$$\Rightarrow I_1' = 6A$$

$$\text{So, } I_2' = I_1' \left(\frac{R_3}{R_2+R_3} \right)$$

$$\Rightarrow I_2' = 6 \left(\frac{4}{2+4} \right)$$

$$\Rightarrow I_2' = 4A$$

and,

$$I_3' = I_1' \left(\frac{R_2}{R_2+R_3} \right)$$

$$\Rightarrow I_3' = 6 \left(\frac{2}{2+4} \right)$$


$$\Rightarrow I_3' = 2A$$

So,

$$I_1 = I_1' - I_1'' = 4A$$

$$I_2 = -I_2' + I_2'' = -1A$$

$$I_3 = I_3' + I_3'' = 3A$$

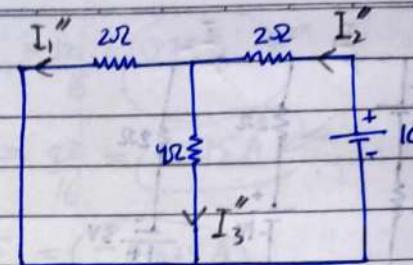

$$\frac{R_{eq}}{R_{eq}} = 2 + (2 \parallel 4)$$

$$\Rightarrow \frac{R_{eq}}{R_{eq}} = \frac{10}{3} \Omega$$

$$\text{So, } I_1'' = \frac{V}{R_{eq}} = \frac{10}{10/3} = 3A$$

$$\Rightarrow I_1'' = 3A$$

$$I_2'' = I_2'' \left(\frac{R_3}{R_1+R_3} \right)$$

$$\Rightarrow I_2'' = 3 \left(\frac{4}{2+4} \right)$$


$$\Rightarrow I_2'' = 2A$$

and,


$$I_3'' = I_2'' \left(\frac{R_1}{R_1+R_3} \right)$$

$$\Rightarrow I_3'' = 3 \left(\frac{2}{2+4} \right)$$

$$\Rightarrow I_3'' = 1A$$

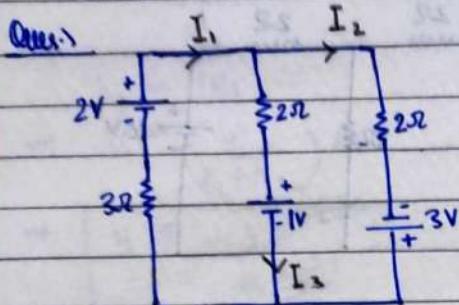

Calculate current across all resistors.

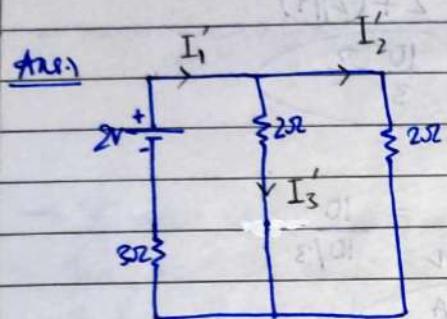


$$R_{eq} = 3 + (2 \parallel 2) \\ = 3 + 1 \\ = 4\Omega$$

$$\text{so, } I_1' = \frac{V}{R_{eq}} = \frac{2}{4} = \frac{1}{2} \text{ A}$$

$$I_2' = I_1' \left(\frac{2}{4} \right) \\ \Rightarrow I_2' = \frac{1}{2} \times \frac{2}{4} \\ \Rightarrow I_2' = \frac{1}{4} \text{ A}$$
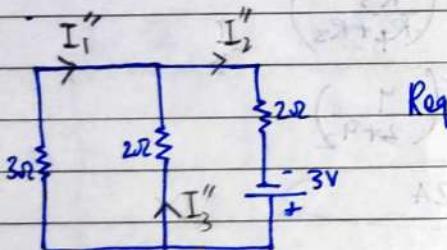
$$I_3' = I_1' \left(\frac{2}{4} \right) \\ \Rightarrow I_3' = \frac{1}{2} \times \frac{2}{4} \\ \Rightarrow I_3' = \frac{1}{4} \text{ A}$$




$$R_{eq} = 2 + (2 \parallel 3) \\ = 2 + \frac{6}{5} \\ = \frac{16}{5} \Omega$$

$$\text{so, } I_2'' = \frac{V}{R_{eq}} = \frac{3}{16/5} = \frac{15}{16} \text{ A}$$

$$\text{and, } I_1'' = I_2'' \left(\frac{2}{5} \right) \\ \Rightarrow I_1'' = \frac{15}{16} \times \frac{2}{5} \\ \Rightarrow I_1'' = \frac{6}{16} \text{ A}$$
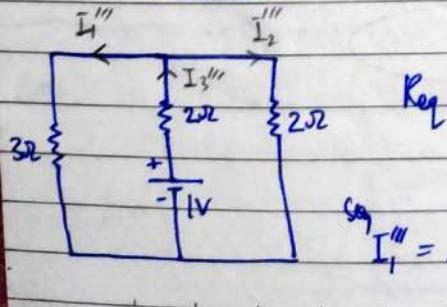
$$I_3'' = I_2'' \left(\frac{3}{5} \right) \\ \Rightarrow I_3'' = \frac{15}{16} \times \frac{3}{5} \\ \Rightarrow I_3'' = \frac{9}{16} \text{ A}$$



$$R_{eq} = 2 + (2 \parallel 3) \\ = \frac{16}{5} \Omega$$

$$I_3''' = \frac{V}{R_{eq}} = \frac{1}{16/5} = \frac{5}{16} \text{ A}$$


$$I_1''' = \frac{5}{16} \times \frac{2}{5} = \frac{2}{16} \text{ A}$$

$$I_2''' = \frac{5}{16} \times \frac{3}{5} = \frac{3}{16} \text{ A}$$


So, $I_1 = I_1' + I_1'' - I_1''' = \frac{8}{16} + \frac{6}{16} - \frac{2}{16} = \frac{12}{16} = 0.75A$

$I_2 = I_2' + I_2'' + I_2''' = \frac{4}{16} + \frac{15}{16} + \frac{3}{16} = \frac{22}{16} = 1.375A$

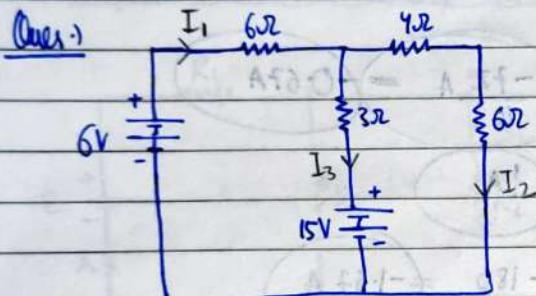$I_3 = I_3' - I_3'' - I_3''' = \frac{4}{16} - \frac{9}{16} - \frac{5}{16} = -\frac{10}{16} = -0.625A$



Calculate current across 3Ω?

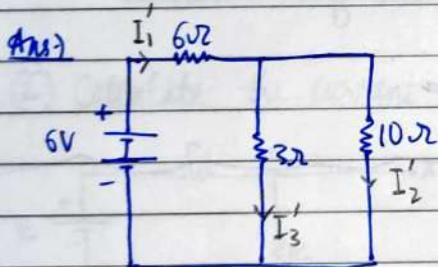


$$\begin{aligned} R_{eq} &= 6 + (3 || 10) \\ &= 6 + \frac{30}{13} \\ &= \frac{108}{13} \Omega \end{aligned}$$

$$\begin{aligned} \text{So, } I_1' &= \frac{V}{R_{eq}} \\ &= \frac{6}{108/13} \\ &= \frac{78}{108} A \end{aligned}$$

and, $I_2' = I_1' \left(\frac{3}{13} \right)$

$$\begin{aligned} &= \frac{6}{108} \times \frac{3}{13} \\ &= \frac{18}{108} A \end{aligned}$$
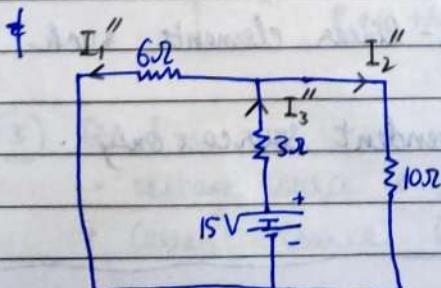
$$\begin{aligned} I_3' &= I_1' \left(\frac{10}{13} \right) \\ &= \frac{6}{108} \times \frac{10}{13} \\ &= \frac{60}{108} \end{aligned}$$



$$\begin{aligned} R_{eq} &= 3 + (6 || 10) \\ &= 3 + \frac{60}{16} \\ &= \frac{108}{16} \Omega \end{aligned}$$

$$\begin{aligned} \text{So, } I_3'' &= \frac{V}{R_{eq}} \\ &= \frac{15}{108/16} \\ &= \frac{240}{108} A \end{aligned}$$

$$I_1' = I_2'' \left(\frac{10}{16} \right)$$

$$= \frac{15}{108} \times \frac{10}{16}$$

$$= \frac{150}{108}$$

$$I_2' = I_3'' \left(\frac{6}{16} \right)$$

$$= \frac{15}{108} \times \frac{6}{16}$$

$$= \frac{90}{108}$$

□ THEVENIN'S

→ This the
two-term
 R_{TH} can

Steps to


$$I_1 = I_1' - I_1'' = \frac{78}{108} - \frac{150}{108} = \frac{-72}{108} A = -0.67 A$$

$$I_2 = I_2' + I_2'' = \frac{18}{108} + \frac{90}{108} = 1 A$$

$$I_3 = I_3' - I_3'' = \frac{60}{108} - \frac{240}{108} = \frac{-180}{108} = -1.67 A$$

Answer → $-1.67 A$

② Calculate

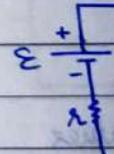

then

→

○ Applications of Superposition Theorem

→ Useful in circuit analysis, when the circuit has a large no. of independent sources.

→ Used in AC as well as DC network.

○ Drawbacks :

→ Not applicable to circuit consisting of non-linear elements such as diode.

→ Cannot be applied to circuit having dependent sources only.

→ Used for calculating power.


③ for

·

THEVENIN'S THEOREM


→ This theorem provides a mathematical technique for replacing a two-terminal network by a voltage source V_{TH} & resistance R_{TH} connected in series.

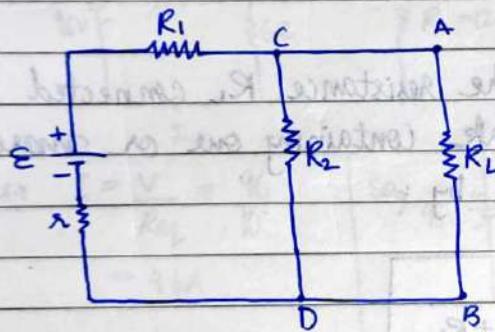Steps to calculate I_L , V_{TH} & R_{TH} :-



(1) Remove or disconnect the load resistance to get an open circuit (R_L).

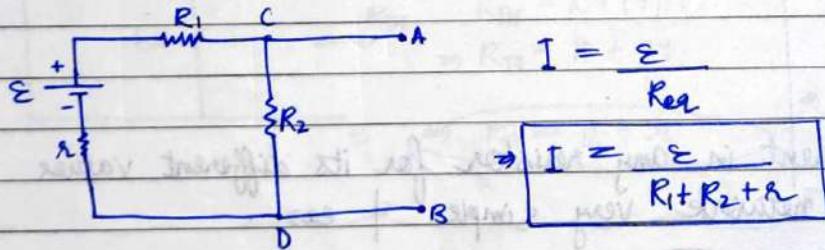(2) Calculate the current flowing through the circuit



then, Open Circuit Voltage or Thvenin's Voltage is given by : (V_{TH})

$$\boxed{V_{TH} = IR_2}$$


$$\Rightarrow \boxed{V_{TH} = \frac{\epsilon}{R_1 + R_2 + r} \cdot R_2}$$

V_{TH} is the voltage across AB terminal which is same as voltage drop across R_2 resistor

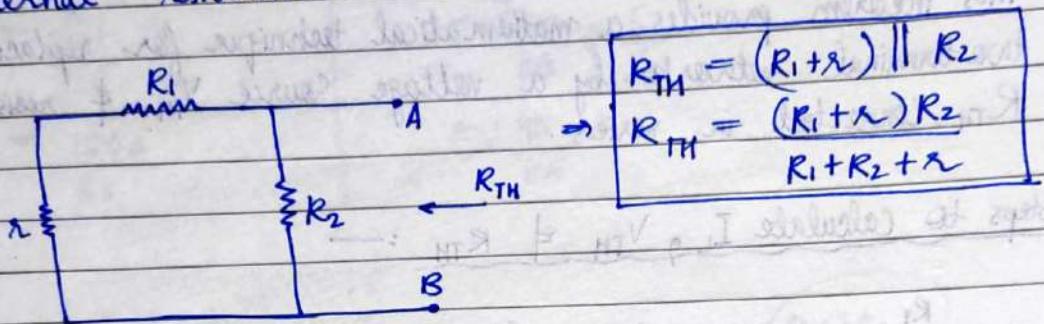
(3) for R_{TH} :-

- voltage source is short circuited.
- current source is open circuited.

Sol. Remove the voltage source from circuit leaving behind the internal resistance.




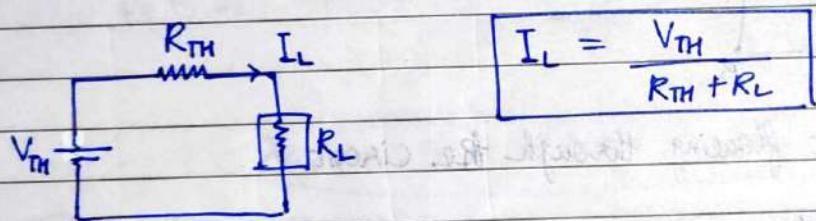(4) The current (I_L) flowing through the resistance R_L connected across any two terminals of network containing one or more sources of current/voltage is given by :



Advantages :-

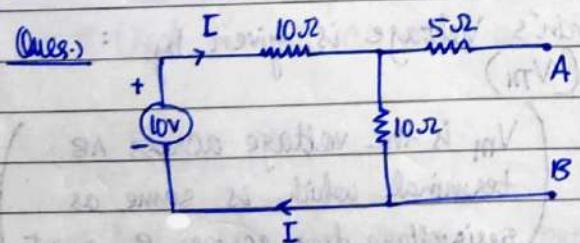- We can find current in any resistor for its different values
- Makes electronic network very simple & easy.



Determine the Thévenin's Voltage & Thévenin's Resistance (AB) ?



Ans. $I = \frac{V}{R_{eq}} = \frac{10}{10+10} = 0.5 \text{ A.}$

so, $V_{TH} = 0.5 \times 10$
 $\Rightarrow V_{TH} = 5 \text{ V}$

Delta


Dt.:
Pg.: Delta

and the

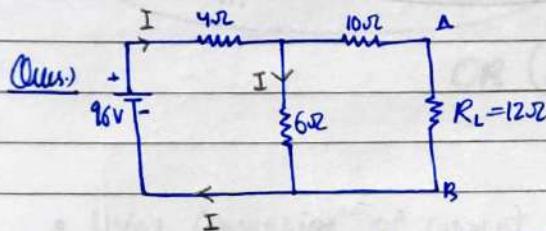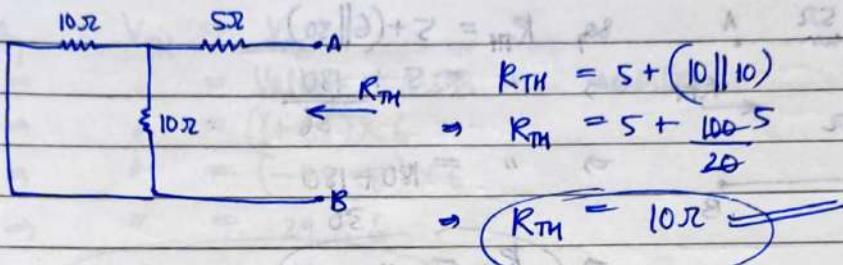


Find the current in 12Ω resistance
using Thevenin's Theorem.

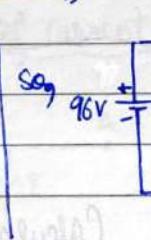
$$\text{Ans. } I = \frac{V}{R_{eq}} = \frac{96}{10}$$
$$= 9.6A$$



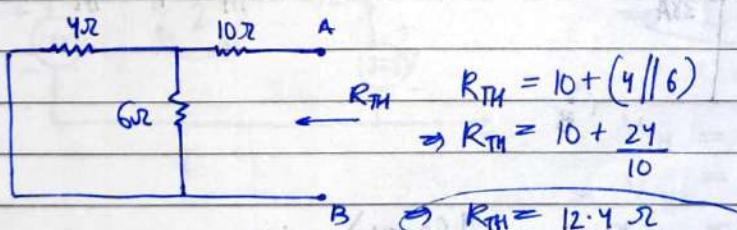
$$V_{TH} = I \times 6$$
$$\Rightarrow V_{TH} = 9.6 \times 6$$
$$\Rightarrow V_{TH} = 57.6V$$


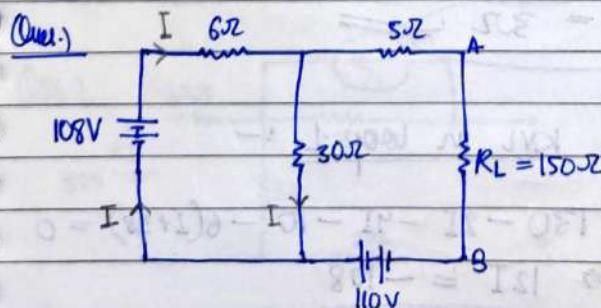
$$\text{S.Q. } I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{57.6}{12.4 + 12}$$
$$\Rightarrow I_L = \frac{57.6}{24.4} = 2.36A$$



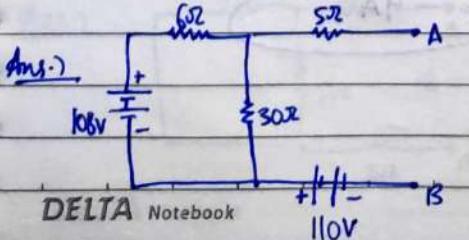
By Thevenin's Theorem calculate the
load current in load resistance.



$$\text{Ans. } I = \frac{V}{R_{eq}} = \frac{108}{36}$$




$$\Rightarrow I = 3A$$
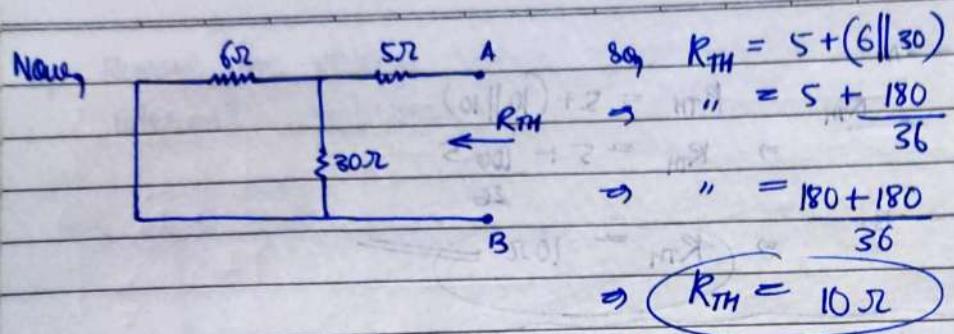
$$V_{TH} = 3 \times 30 + 110V$$
$$\Rightarrow V_{TH} = 200V$$



$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{200}{10 + 150}$

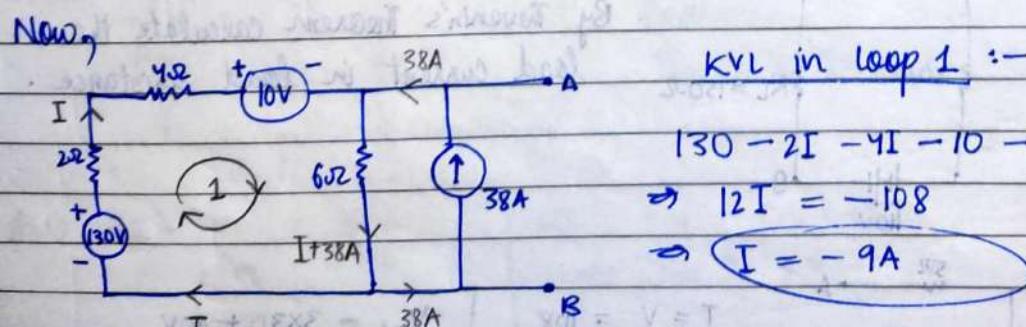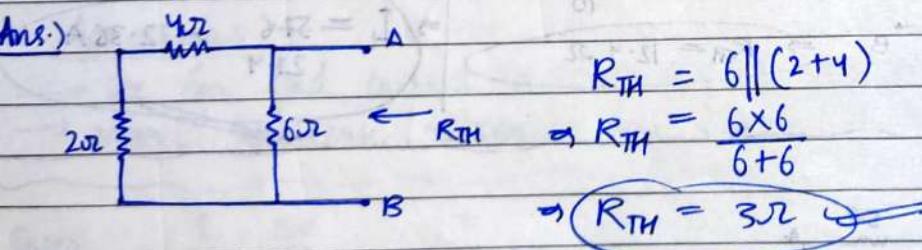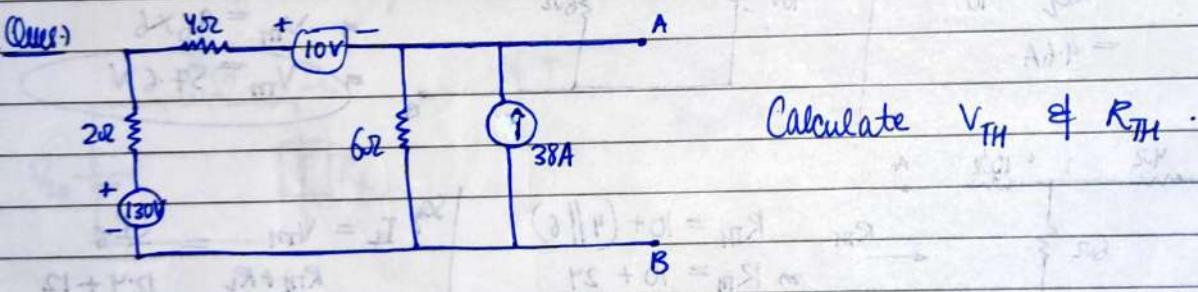
 $\Rightarrow I_L = \frac{200}{160} = 1.25A$



So, $V_{TH} = V_{AB}$
 " = Voltage across 6Ω resistor
 " = $(I + 38) \times 6$
 " = $(-9 + 58) \times 6$
 " = 29×6
 $\Rightarrow V_{TH} = 174 \text{ V}$

OR (Alternate method to find V_{TH})

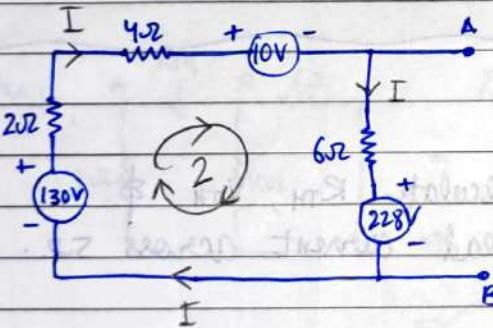- Using Conversion of current Source to voltage Source :-




KVL :-


$$130 - 2I - 4I - 10 - 6I - 228 = 0$$

$$\Rightarrow I = -9 \text{ A}$$

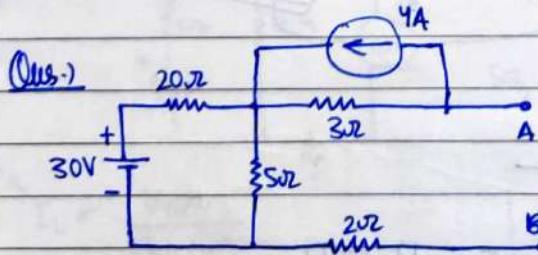So, $V_{TH} = V_{AB}$
 $\Rightarrow V_{TH} = 228 + 6I$
 $\Rightarrow V_{TH} = 228 + 6 \times -9$
 $\Rightarrow V_{TH} = 174 \text{ V}$



Calculate V_{TH} & R_{TH} .

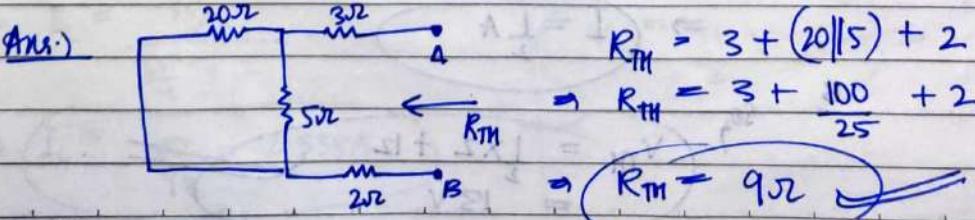


$$R_{TH} = 3 + (20||5) + 2$$

$$\Rightarrow R_{TH} = 3 + \frac{100}{25} + 2$$

$$\Rightarrow R_{TH} = 9\Omega$$

For V_{TH} :-

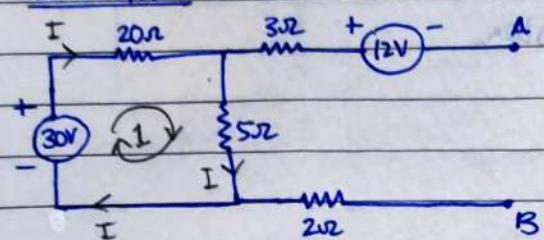

KVL in loop 1 :-

$$30 - 20I - 5I = 0$$

$$\Rightarrow I = \frac{30}{25} = \frac{6}{5} A$$

So,


$$V_{TH} = V_{AB}$$

$$\Rightarrow V_{TH} = 5I - 12$$

$$\Rightarrow V_{TH} = 5 \times \frac{6}{5} - 12$$


$$\Rightarrow V_{TH} = -6 V$$

Ques.)

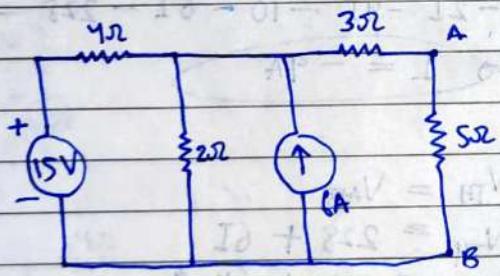


Calculate R_{TH} , V_{TH} & Load current across 5Ω .

Ans.)

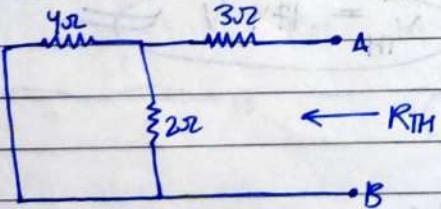

$$R_{TH} = 3 + (2||4)$$
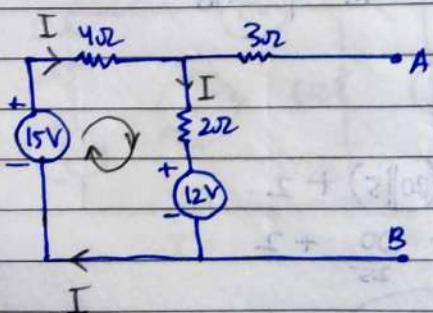
$$\Rightarrow R_{TH} = \frac{13}{3} \Omega$$



KVL :-

$$(15 - 4I - 2I - 12) = 0$$

$$\Rightarrow I = \frac{1}{2} A$$

So,

$$V_{TH} = \frac{1}{2} \times 2 + 12$$

=


13 V

$$\text{So, } I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$\rightarrow I_L = \frac{13}{\frac{13}{3} + 5}$$


$$\rightarrow I_L = \frac{39}{28} \text{ A}$$

Ques.:

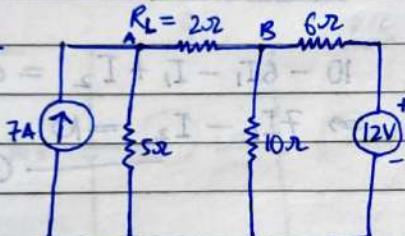

Calculate V_{TH} , R_{TH} & load current (I_L) .

Ans.:

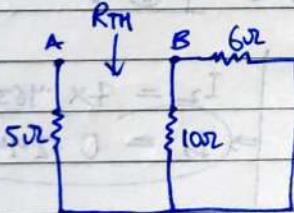


$$R_{TH} = (6||10) + 5$$

$$\therefore = \frac{60}{16} + 5$$

$$\therefore = \frac{15}{4} + 5$$

$$\therefore R_{TH} = \frac{35}{4} \Omega$$

Now,

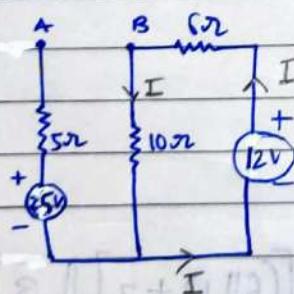

$$I = \frac{12}{6+10} = \frac{3}{4} \text{ A}$$

$$\text{So, } V_{TH} = -\frac{3}{4} \times 10 + 35 \quad (V_{TH} = V_A - V_B)$$

$$\text{So, } I_L = \frac{V_{TH}}{R_{TH} + R_L}$$


$$\rightarrow I_L = \frac{35/2}{\frac{35}{4} + 2}$$

$$\rightarrow I_L = \frac{110}{43} = 2.558 \text{ A}$$

$$V_{TH} = 35 - \frac{15}{2}$$


$$V_{TH} = \frac{55}{2} \text{ V}$$

(Ans.)

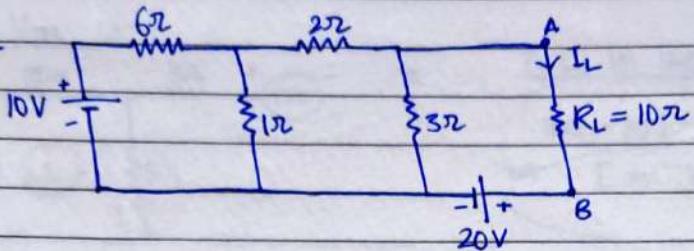

Find current I_L .

(Ans.)

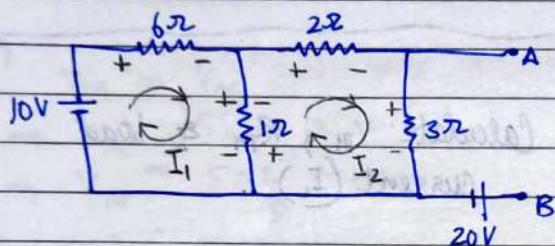

In mesh 1 :-

$$10 - 6I_1 - I_1 + I_2 = 0$$

$$\Rightarrow 7I_1 - I_2 = 10 \quad \text{--- (1)}$$

In mesh 2 :-

$$-I_2 + I_1 - 2I_2 - 3I_2 = 0$$

$$\Rightarrow I_1 - 6I_2 = 0$$

$$\text{--- (2)}$$

Subtracting eqn. (1) $\times 6$ & (2) :-

$$42I_1 - 6I_2 = 60$$

$$\Rightarrow I_1 - 6I_2 = 0$$

$$4I_1 = 60$$

$$\Rightarrow I_1 = 1.463 \text{ A}$$

$$I_2 = 7 \times 1.463 - 10$$

$$\Rightarrow I_2 = 0.244 \text{ A}$$


So,

$$V_{TH} = V_{AB}$$

$$\Rightarrow " = 3I_2 - 20$$

$$\Rightarrow " = 3 \times 0.244 - 20$$
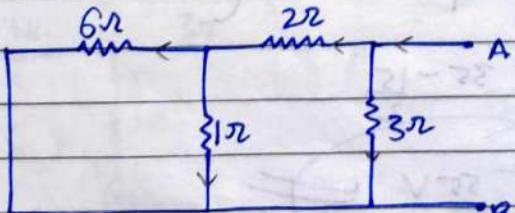
$$\Rightarrow V_{TH} = -19.268 \text{ V}$$



$$R_{TH} = [(6 \parallel 1) + 2] \parallel 3$$

$$\Rightarrow " = \left(\frac{6 \times 1}{6+1} + 2 \right) \parallel 3$$


$$\Rightarrow " = 2.857 \parallel 3$$

$$\Rightarrow " = \frac{2.857 \times 3}{5.857}$$

$$\Rightarrow R_{TH} = 1.4634 \Omega$$

Dt.:
Pg.:

Delta

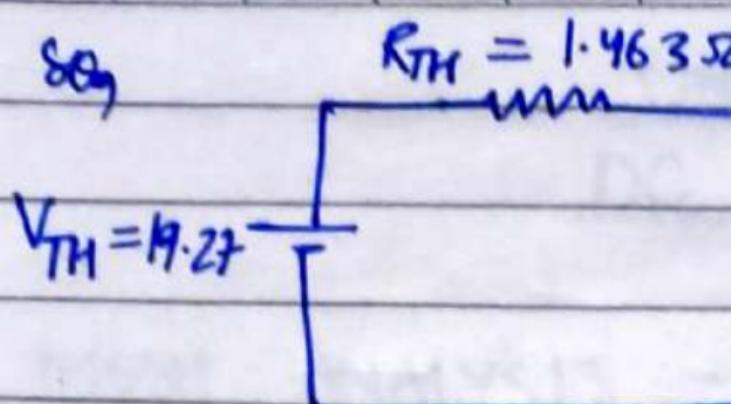


so,

$$\frac{V_{TH}}{R_{TH} + R_L} = I_L$$
$$R_L = 10 \Omega \Rightarrow I_L = \frac{-19.27}{1.4634 + 10}$$

$$\Rightarrow I_L = -1.681 \text{ A}$$


Question of Superposition Theorem .)

Ques. 1.)

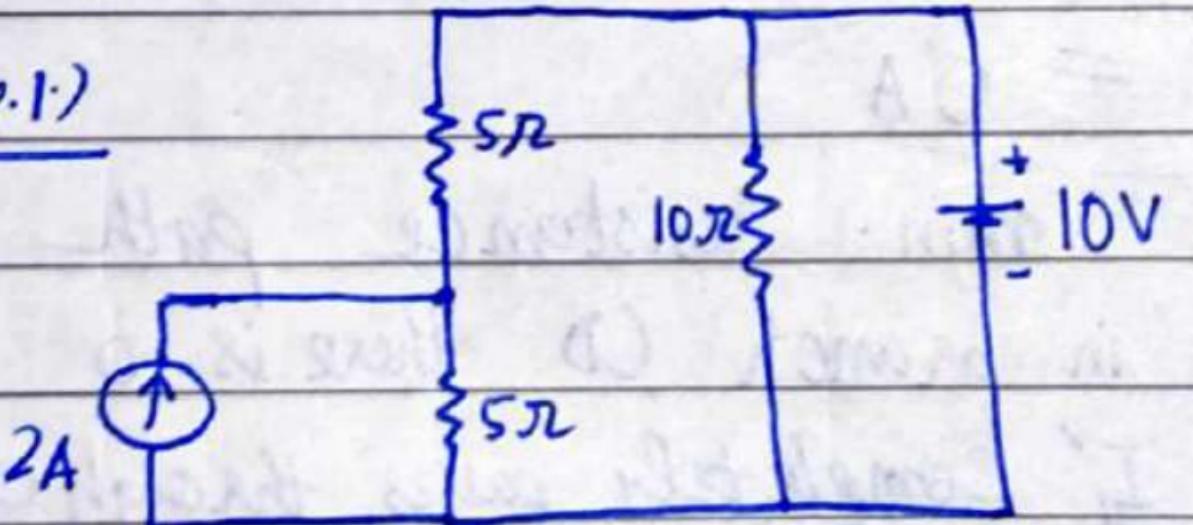

find current across 10Ω resistor .

Ans.) • Considering 10V battery :

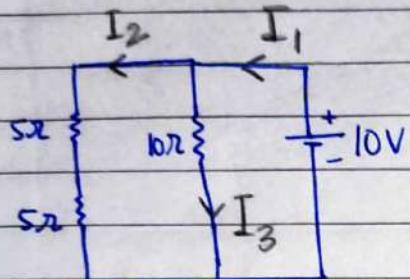

$$\begin{aligned}
 \text{Req} &= (5+5) \parallel 10 & \text{so, } I_1 &= V/\text{Req} \\
 &\Rightarrow " = 10 \parallel 10 & \Rightarrow I_1 &= 10/5 \\
 &\Rightarrow " = \frac{10 \times 10}{10+10} & \Rightarrow I_1 &= 2 \text{ A} \\
 \Rightarrow \text{Req} &= 5\Omega
 \end{aligned}$$


Using current divider rule :-

$$I_3 = \frac{(5+5)}{(5+5)+10} \times I_1$$

$$\Rightarrow I_3 = 2 \times \frac{10}{20}$$

$$\Rightarrow I_3 = 1 \text{ A}$$

• Considering 2A current source :

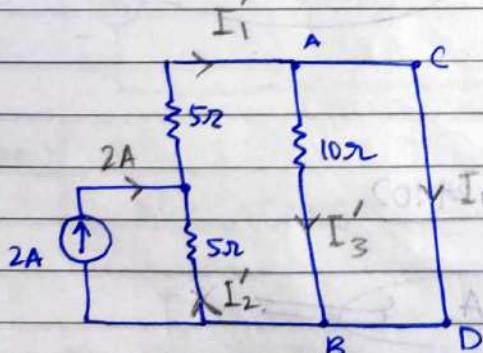

In ideal conditions : we know :-

Resistance of a
branch / connecting wire = 0
(CD in this case)


So, Using current divider rule :

$$I_3' = I_1' \times \frac{0}{10+0}$$

$$I_3' = 0 \text{ A}$$


Note :- Current always follows the min. resistance path.
(And here in this case since, in branch CD there is 0 resistance, so, the current I_1' completely passes through CD & not in AB. So, $I_1' = I_1$ & $I_3' = 0$)

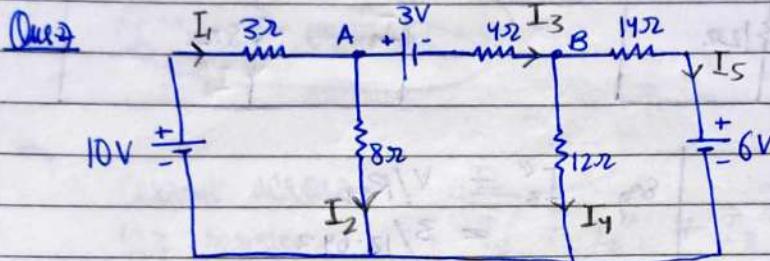so, current through $10\ \Omega$ resistor = $1A$



find current across $8\ \Omega$ resistor.

Ans. 2.) • Considering 10V battery :

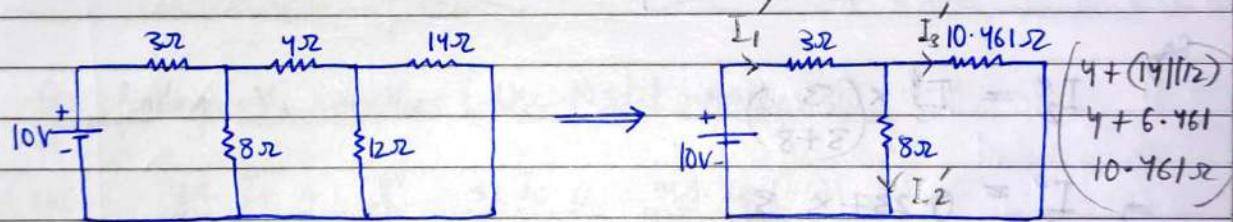

$$\begin{aligned} R_{eq} &= 3 + (8 \parallel 10.461) \\ &= 3 + \frac{8 \times 10.461}{8 + 10.461} \\ &= 3 + 4.533 \\ &= 7.533\ \Omega \end{aligned}$$

$$\begin{aligned} \text{so, } I_1' &= V/R_{eq} \\ \Rightarrow I_1' &= 10/7.533 \\ \Rightarrow I_1' &= 1.327\ A \end{aligned}$$


so, $I_2' = I_1' \left(\frac{10.461}{8 + 10.461} \right)$

$$\Rightarrow I_2' = \frac{1.327 \times 10.461}{18.461}$$

$$\Rightarrow I_2' = 0.751\ A$$

Now,

- Considering 3V battery :-

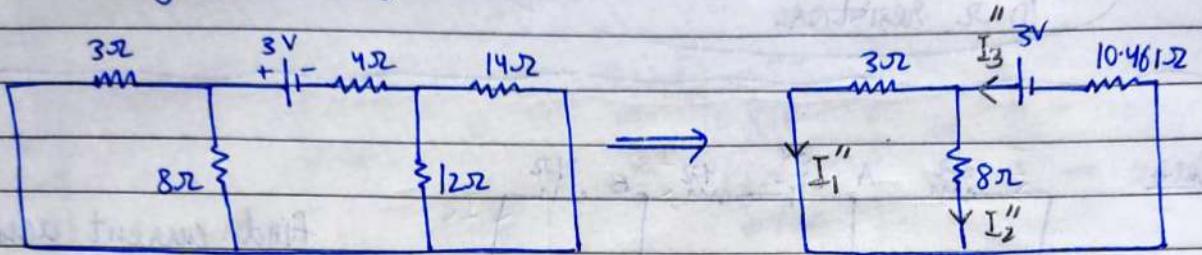


$$\begin{aligned} R_{eq} &= (3 \parallel 8) + 10.46 \\ &= \frac{3 \times 8}{3+8} + 10.46 \\ &= 12.643 \Omega \end{aligned}$$

$$\begin{aligned} \text{So, } I_3'' &= V/R_{eq} \\ &= 3/12.643 \\ &= 0.237 A \end{aligned}$$

$$\begin{aligned} \text{So, } I_2'' &= I_3'' \times \left(\frac{3}{3+8} \right) \\ \Rightarrow I_2'' &= 0.237 \times \frac{3}{11} \\ \Rightarrow I_2'' &= 0.064 A \end{aligned}$$

- Considering 6V battery :-

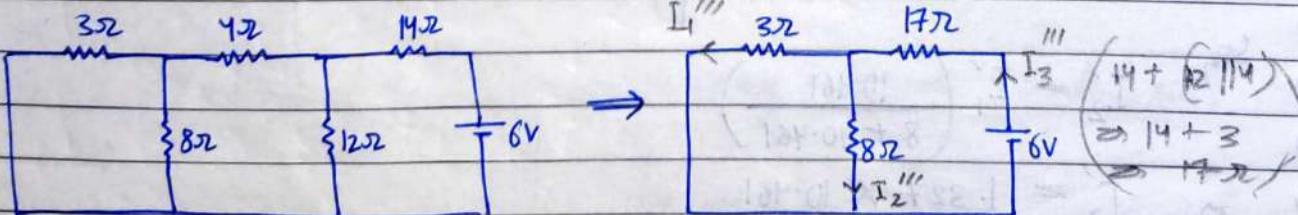

$$\begin{aligned} R_{eq} &= 17 + (3 \parallel 8) \\ &= 17 + \frac{3 \times 8}{3+8} \\ &= 19.182 \Omega \end{aligned}$$

$$\begin{aligned} \text{So, } I_3''' &= V/R_{eq} \\ &= 6/19.182 \\ &= 0.312 A \end{aligned}$$


$$\text{So, } I_2''' = I_3''' \times \left(\frac{3}{3+8} \right)$$

$$\Rightarrow I_2''' = 0.312 \times \frac{3}{11}$$

$$\Rightarrow I_2''' = 0.085 \text{ A}$$

$$\begin{aligned} \text{Current across } 1\Omega \text{ resistor} &= I_2 \\ &= I_2' + I_2'' + I_2''' \\ &= 0.751 + 0.064 + 0.085 \\ &= 0.900 \text{ A} \end{aligned}$$

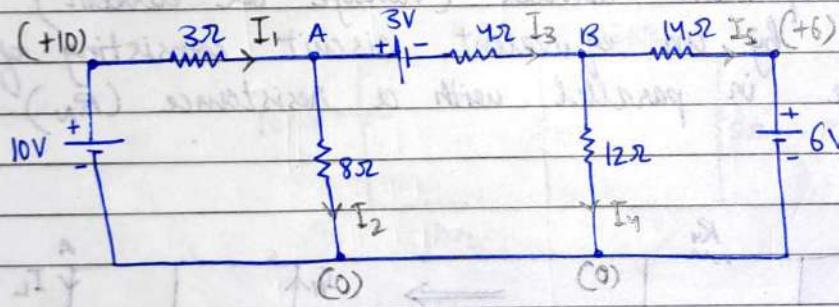for finding $V_A \neq V_B$ (Use Nodal Analysis) :-



KCL at node A :

$$I_1 = I_2 + I_3$$

$$\Rightarrow \frac{10-V_A}{3} = \frac{V_A}{8} + \frac{V_A - 3 - V_B}{4}$$

$$\Rightarrow \frac{10-V_A}{3} = \frac{V_A}{8} + \frac{2V_A - 6 - 2V_B}{8}$$

$$\Rightarrow 80 - 8V_A = 3V_A + 6V_A - 18 - 6V_B$$

$$\Rightarrow 17V_A - 6V_B = 98$$

KCL at node B :

$$I_3 = I_4 + I_5$$

$$\Rightarrow \frac{V_A - 3 - V_B}{4} = \frac{V_B}{12} + \frac{V_B - 6}{14}$$

$$\Rightarrow \frac{V_B - 6}{14} = \frac{3V_A - 9 - 3V_B - V_B}{12 - 6}$$

$$\Rightarrow 6V_B - 36 = 21V_A - 63 - 28V_B$$

$$\Rightarrow 21V_A - 34V_B = 27$$

Solving eqn. ① & ⑪ :-

Subtracting eqn. ① × 34 & eqn. ⑪ × 6 :-

$$578V_A - 204V_B = 3332$$

$$\rightarrow 126V_A + 204V_B = 162$$

$$452V_A = 3170$$


$$\Rightarrow V_A = 7.013V$$

$$V_B = \frac{17 \times 7.013 - 98}{6}$$

$$\Rightarrow V_B = 3.536V$$

NORTON'S THEOREM

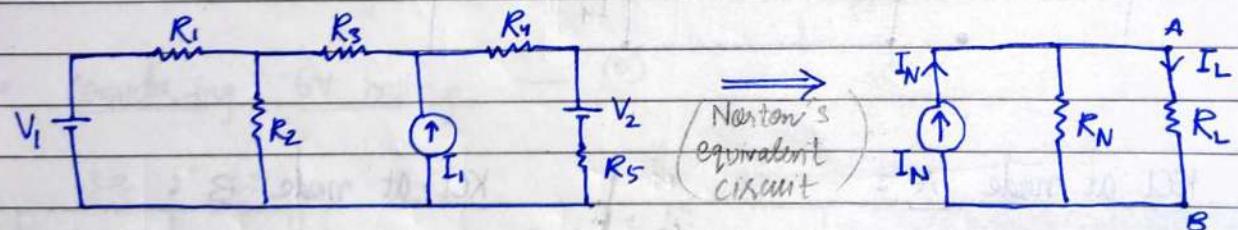→ It states that any linear bilateral circuit consisting of independent or dependent sources (voltage or current) can be replaced by an equivalent circuit consisting of a current source in parallel with a resistance (R_N). (I_N)



Step 1 : Remove R_L and short circuit the branch through which current is to be calculated.

Step 2 : Obtain current through the short circuited branch using any simplification method. And this current is Norton's current (I_N).

Step 3 : Calculate R_N by open circuiting R_L (load resistance). And

And replacing the active sources with their internal resistances.
 (If no internal resistance, then short ckt. voltage sources)
 And open ckt. current sources.



Step 4: Draw Norton's equivalent circuit across the terminals of interest.

Step 5: find I_L .

$$I_L = I_N \times \frac{R_N}{R_N + R_L}$$

(Using current divider Rule.)

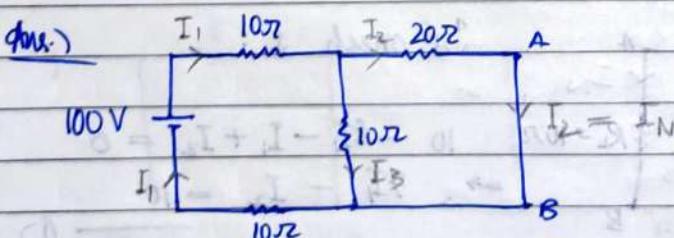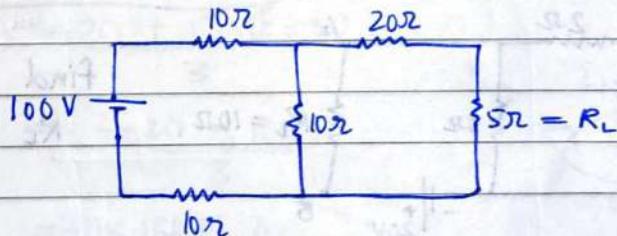Ques) Calculate the value of current in 5Ω resistance using Norton's Theorem.



$$\begin{aligned} R_{eq} &= 10 + 10 + (10//20) \\ &= 20 + \frac{200}{30} \\ &= \frac{80}{3} \Omega \end{aligned}$$


So,

$$\begin{aligned} I_1 &= \frac{V}{R_{eq}} = \frac{100}{\frac{80}{3}} \\ &= \frac{30}{8} A \end{aligned}$$

$$\text{So, } I_2 = I_N = I_1 \times \frac{10}{10+20}$$

$$\rightarrow I_N = \frac{30}{8} \times \frac{1}{3} = \frac{10}{8}$$

$$\boxed{I_N = 1.25 A}$$

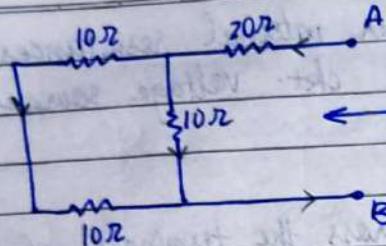

$$R_N = [(10+10) \parallel 10] + 20$$

$$\therefore R_N = (20 \parallel 10) + 20$$

$$\therefore R_N = \frac{200}{30} + 20$$

$$\therefore R_N = \frac{80}{3} \Omega$$



So,

$$I_L = I_N \times \frac{R_N}{R_N + R_L}$$


$$\Rightarrow I_L = \frac{10}{8} \times \frac{\frac{80}{3}}{\frac{80}{3} + 5}$$

$$\Rightarrow I_L = \frac{10}{8} \times \frac{80}{95}$$

$$\Rightarrow I_L = 1.052 \text{ A}$$

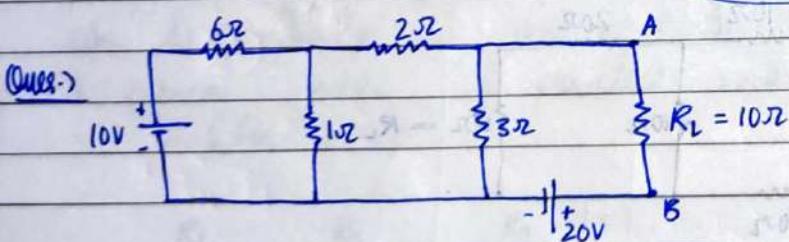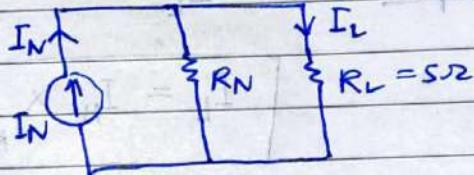

find I_L through
 $R_L = 10\Omega$.

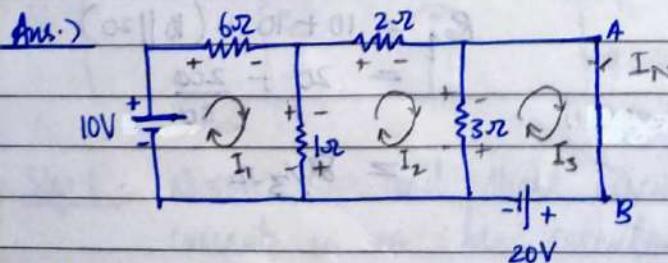

In mesh 1:

$$10 - 6I_1 - I_1 + I_2 = 0$$

$$7I_1 - I_2 = 10 \quad \text{--- (i)}$$

In mesh 2:

$$-I_2 + I_1 - 2I_2 - 3I_2 + 3I_3 = 0$$

$$\Rightarrow I_1 - 6I_2 + 3I_3 = 0 \quad \text{--- (ii)}$$

In mesh 3:

$$-20 - 3I_3 + 3I_2 = 0$$

$$3I_2 - 3I_3 = 20 \quad \text{--- (iii)}$$

Subtracting eqn. (II) - eqn. (I) :

$$\begin{aligned} 3I_2 - 3I_3 &= 20 \\ \cancel{7I_1 + I_2 = 10} \\ -7I_1 + 4I_2 - 3I_3 &= 10 \end{aligned}$$

(a)

Adding eqn. (I) & (II) :-

$$\begin{aligned} I_1 - 6I_2 + 3I_3 &= 0 \\ -7I_1 + 4I_2 - 3I_3 &= 10 \\ -6I_1 - 2I_2 &= 10 \end{aligned}$$

(b)


Subtracting eqn. (I) $\times 2$ - eqn. (b) :-

$$\begin{aligned} 14I_1 - 2I_2 &= 20 \\ \cancel{+6I_1 + 2I_2 = 10} \\ 20I_1 &= 10 \\ I_1 &= 0.5 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{So, } I_2 &= 7 \times 0.5 - 10 \\ \Rightarrow I_2 &= -6.5 \text{ A} \end{aligned}$$


$$\begin{aligned} \text{So, } I_3 &= -20 + 3 \times (-6.5) \\ \Rightarrow I_3 &= -20 - 19.5 \\ \Rightarrow I_3 &= -13.1667 \text{ A} \end{aligned}$$
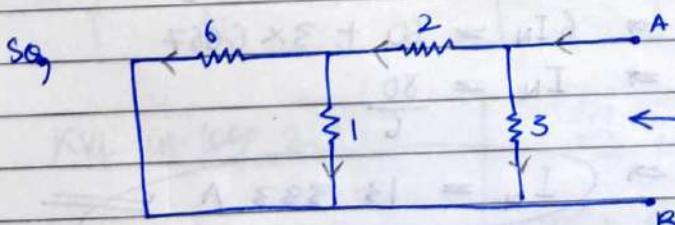
$$\begin{aligned} \text{So, } I_N &= I_3 \\ \Rightarrow I_N &= -13.1667 \text{ A} \end{aligned}$$




$$\begin{aligned} R_N &= [(6/1) + 2] \parallel 3 \\ \Rightarrow &= \left(\frac{6}{7} + 2\right) \parallel 3 \\ \Rightarrow &= \frac{20}{7} \parallel 3 \end{aligned}$$

$$\Rightarrow R_N = 1.4634 \Omega$$

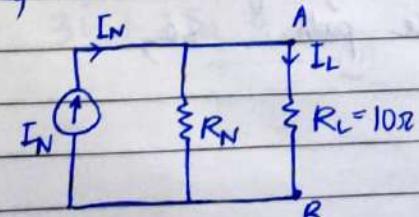


$$I_L = I_N \times \frac{R_N}{R_N + R_L} = -13.2 \times \frac{1.4634}{1.4634 + 10}$$

$$\Rightarrow I_L = 1.685 \text{ A}$$

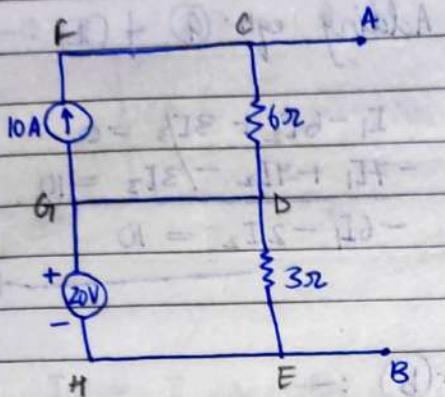Ques.

Replace the given circuit by Norton's Equivalent circuit across A & B.

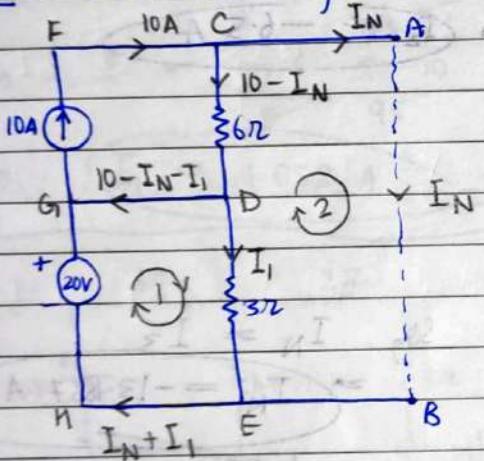Ans. Short circuiting AB :

KVL in loop 1 :

$$20 - 3I_1 = 0$$

$$\Rightarrow I_1 = \frac{20}{3}$$

$$\Rightarrow I_1 = 6.667 \text{ A}$$

KVL in loop 2 :

$$6(10 - I_N) + 3I_1 = 0$$


$$\Rightarrow 60 - 6I_N + 3I_1 = 0$$

$$\Rightarrow 6I_N = 60 + 3 \times 6.667$$

$$\Rightarrow I_N = \frac{80}{6}$$

$$\Rightarrow I_N = 13.333 \text{ A}$$

Now,

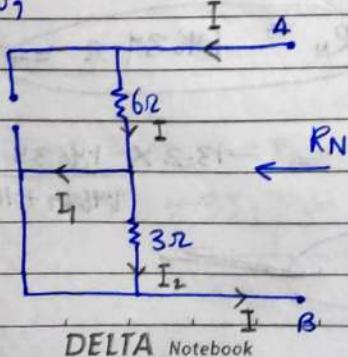


we know: current always follows min. resistance path. So,

$$I_2 = 0$$


$$I_1 = I$$

$$R_N = 6\Omega$$

So, Newton's equivalent circuit :-

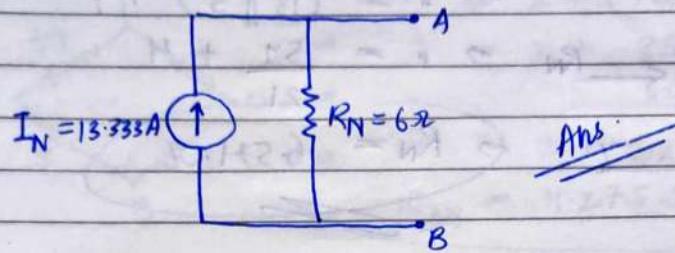


Ques:-

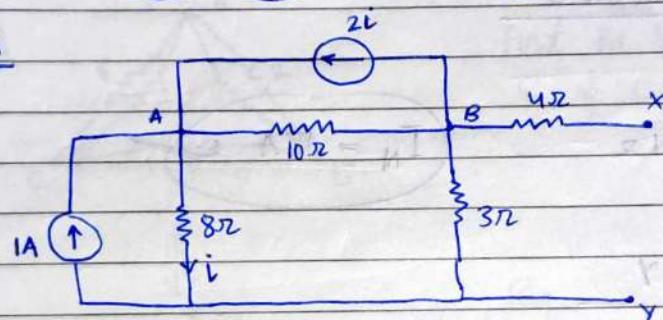

Determine the values of I_N , R_N & i .

Ans:- Short circuiting XY :-

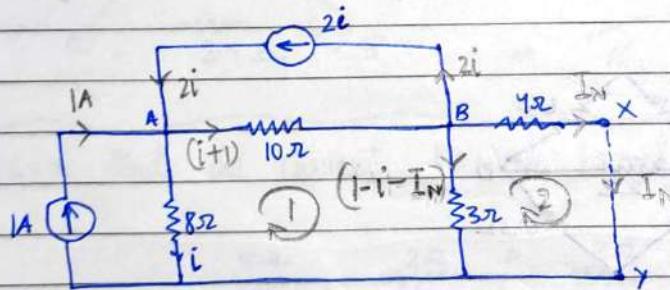

KVL in loop 1 :-

$$8i - 10(i+1) - 3(1-i-I_N) = 0$$

$$\Rightarrow 8i - 10i - 10 - 3 + 3i + 3I_N = 0$$

$$\Rightarrow i + 3I_N = 13 \quad \text{--- (1)}$$

KVL in loop 2 :-

$$3(1-i-I_N) - 4I_N = 0$$

$$\Rightarrow 3 - 3i - 3I_N - 4I_N = 0$$

$$\Rightarrow 3i + 7I_N = 3 \quad \text{--- (2)}$$

Solving eqn. (1) x 3 - (2) :-


$$3i + 9I_N = 39$$

$$\cancel{3i} + 7I_N = 3$$


$$2I_N = 36$$

$$\Rightarrow I_N = 18A$$

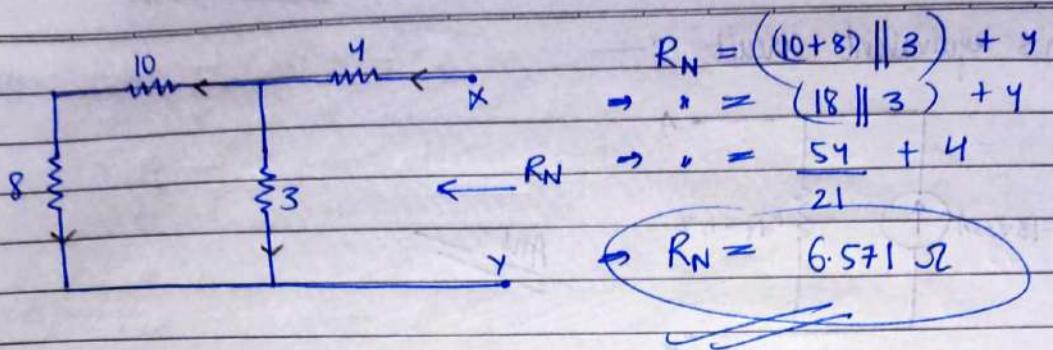So,
 $i = 13 - 3I_N$
 $i = 13 - 54$
 $\Rightarrow i = -41A$




Sol. Norton's equivalent circuit :-

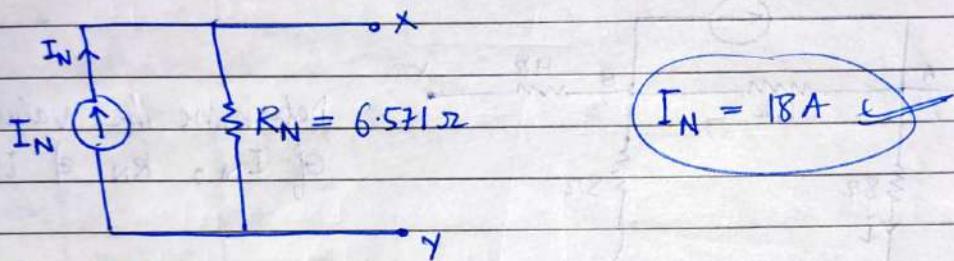


Extra Questions

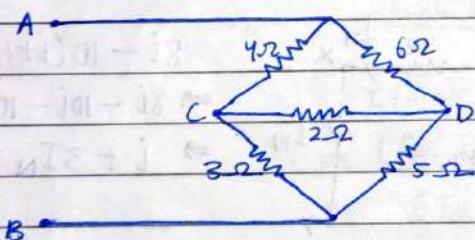Ques. 1) find the resistance between A - B using star delta transformation.



Ans.)

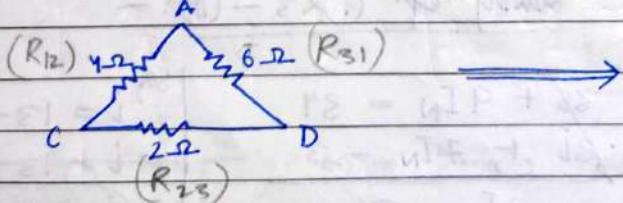


$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{4 \times 6}{4 + 2 + 6}$$

$$\Rightarrow R_1 = 2 \Omega$$



$$R_2 = \frac{2 \times 4}{4 + 2 + 6}$$

$$\Rightarrow R_2 = \frac{2}{3} \Omega$$

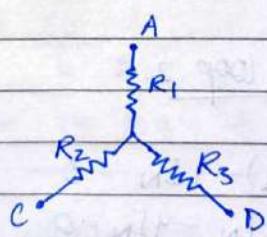


$$R_3 = \frac{2 \times 6}{4 + 2 + 6}$$

$$\Rightarrow R_3 = 1 \Omega$$

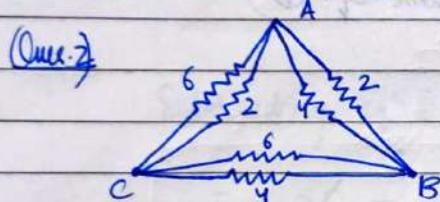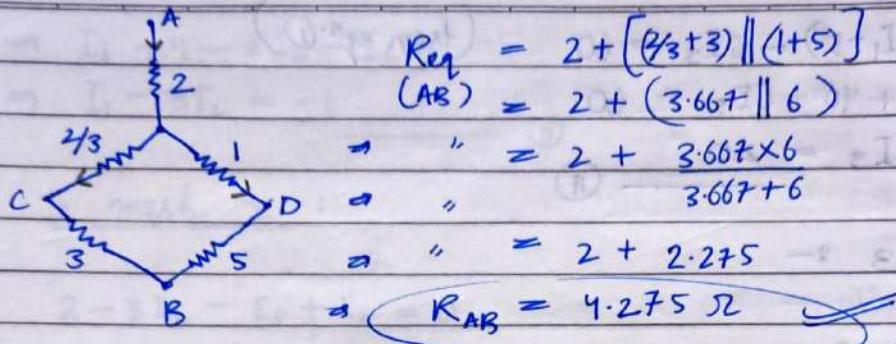


Find the resistance b/w terminals
 $B \neq C$.

Ans.)

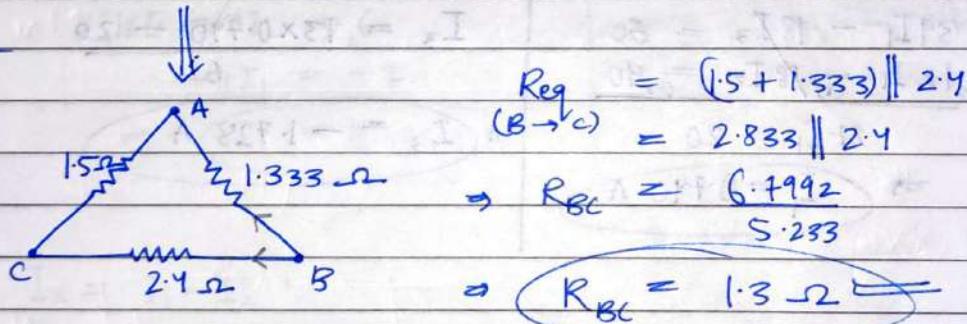

Ques. 3 find the current through branch A-B using mesh analysis.

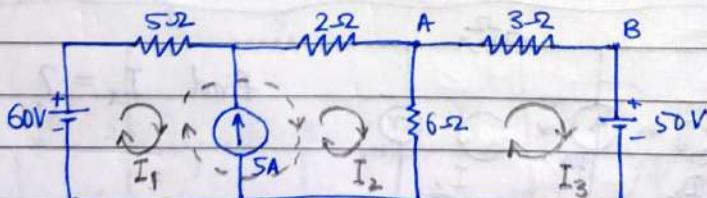

Ans. 3.) $I_2 - I_1 = 5A$ _____ ①

In supermesh (1 + 2) :-

$$60 - 5I_1 - 2I_2 - 6I_2 + 6I_3 = 0$$

$$\rightarrow 5I_1 + 8I_2 - 6I_3 = 60$$

$$\rightarrow 5I_1 + 8(I_1 + 5) - 6I_3 = 60 \quad (\text{from eqn. } ①)$$

$$\rightarrow 5I_1 + 8I_1 + 40 - 6I_3 = 60$$

$$\rightarrow 13I_1 - 6I_3 = 20 \quad ⑪$$

In mesh 3 :-

$$-50 - 6I_3 + 6I_2 - 3I_3 = 0$$


$$\rightarrow 6(I_1 + 5) - 9I_3 - 50 \quad (\text{from eqn. } ①)$$

$$\rightarrow 6I_1 - 9I_3 = 20 \quad ⑫$$

Now, Subtracting eqn. ⑪ × 3 - eqn. ⑫ × 2 :-

$39I_1 - 18I_3 = 60$ $\hookrightarrow 12I_1 + 18I_3 = 40$ $27I_1 = 20$ $\Rightarrow I_1 = 0.740 \text{ A}$	$I_3 = \frac{13 \times 0.740 - 20}{6}$ $\Rightarrow I_3 = -1.728 \text{ A}$
---	--

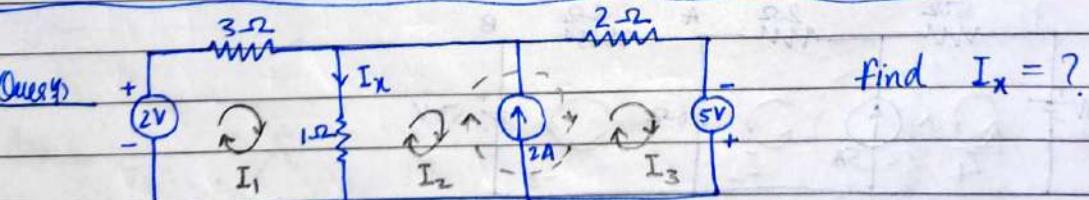So, current through branch AB = $I_3 = -1.728 \text{ A}$



Ans.) $I_3 - I_2 = 2 \quad ①$

In supermesh (2 & 3) :-

$$-I_2 + I_1 - 2I_3 + 5 = 0$$

$$\Rightarrow I_1 - 2(2 + I_2) - I_2 = -5 \quad (\text{from eqn. } ①)$$

$$\Rightarrow I_1 - 4 - 2I_2 - I_2 = -5$$

$$\Rightarrow I_1 - 3I_2 = -1 \quad \text{--- (ii)}$$

In mesh 1 :

$$2 - 3I_1 - I_1 + I_2 = 0$$

$$\Rightarrow 4I_1 - I_2 = 2 \quad \text{--- (iii)}$$

Subtracting eqn. (ii) - eqn. (iii) $\times 3$:-

$$I_1 - 3I_2 = -1$$

$$\underline{-12I_1} \quad \underline{+3I_2} = \underline{-6}$$

$$-11I_1 = -7$$

$$\Rightarrow I_1 = 0.6363 \text{ A}$$

$$I_2 = 4 \times 0.6363 - 2$$

$$\Rightarrow I_2 = 0.5454 \text{ A}$$


So,

$$I_x = I_1 - I_2$$

$$\Rightarrow I_x = 0.6363 - 0.5454$$

$$\Rightarrow I_x = 0.0909 \text{ A} \downarrow$$

(Ans. 5)

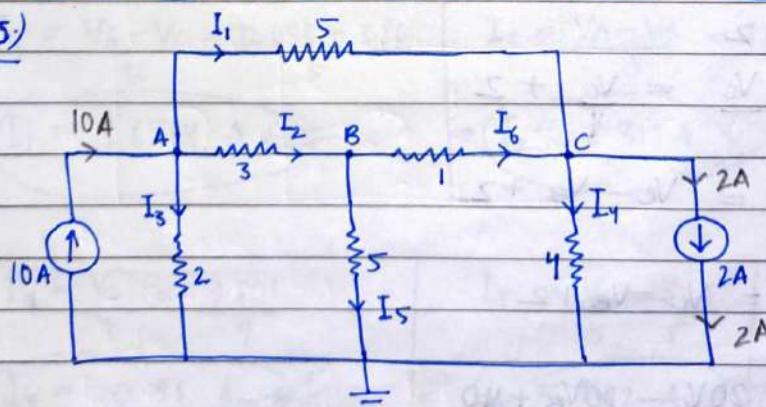

find the currents in the various resistors using nodal analysis.

Ans.)

Applying KCL at node A :

$$I_1 + I_2 + I_3 = 10$$

$$\Rightarrow \frac{V_A - V_C}{5} + \frac{V_A - V_B}{3} + \frac{V_A}{2} = 10$$

$$\Rightarrow \frac{6V_A - 6V_C + 10V_A - 10V_B + 15V_A}{30} = 10$$

$$\Rightarrow 31V_A - 10V_B - 6V_C = 300 \quad \text{--- (1)}$$

KCL at node B :

$$I_5 + I_6 = I_2$$

$$\Rightarrow \frac{V_B}{5} + \frac{V_B - V_C}{1} = \frac{V_A - V_B}{3}$$

$$\Rightarrow \frac{V_A - V_B}{3} - \frac{V_B}{5} = \frac{V_B - V_C}{1}$$

$$\Rightarrow \frac{5V_A - 5V_B - 3V_B}{15} = V_B - V_C$$

$$\Rightarrow 5V_A - 8V_B = 15V_B - 15V_C$$

$$\Rightarrow 5V_A - 23V_B + 15V_C = 0 \quad \text{--- (II)}$$

KCL at Node C :

$$I_1 + I_6 = I_4 + 2$$

$$\Rightarrow \frac{V_A - V_C}{5} + \frac{V_B - V_C}{1} = \frac{V_C}{4} + 2$$

$$\Rightarrow \frac{V_A - V_C}{5} - \frac{V_C}{4} = V_C - V_B + 2$$

$$\Rightarrow \frac{4V_A - 4V_C - 5V_C}{20} = V_C - V_B + 2$$

$$\Rightarrow 4V_A - 9V_C = 20V_C - 20V_B + 40$$

$$\Rightarrow 4V_A + 20V_B - 29V_C = 40 \quad \text{--- (III)}$$

$$D = \begin{vmatrix} 31 & -10 & -6 \\ 5 & -23 & 15 \\ 4 & 20 & -29 \end{vmatrix} = 31(667 - 300) + 10(-145 - 60) - 6(100 + 92) \\ = 11377 - 2050 - 1152 \\ = 8175$$

and,

$$D_x = \begin{vmatrix} 300 & -10 & -6 \\ 0 & -23 & 15 \\ 40 & 20 & -29 \end{vmatrix} = 300(667 - 300) + 40(-150 - 138) \\ = 110100 - 11520 \\ = 98580$$

$$D_y = \begin{vmatrix} 31 & 300 & -6 \\ 5 & 0 & 15 \\ 4 & 40 & -29 \end{vmatrix} = -300(-145 - 60) - 40(465 + 30) \\ = 61500 - 19800 \\ = 41700$$

$$D_z = \begin{vmatrix} 31 & -10 & 300 \\ 5 & -23 & 0 \\ 4 & 20 & 40 \end{vmatrix} = 300(100 + 92) + 40(-73 + 50) \\ = 57600 - 26520 \\ = 31080$$

59,

$$V_A = \frac{D_x}{D} = \frac{98580}{8175}$$

$$V_B = \frac{D_y}{D} = \frac{41700}{8175}$$

$$V_C = \frac{D_z}{D} = \frac{31080}{8175}$$

$$\Rightarrow V_A = 12.058 \text{ V}$$

$$\Rightarrow V_B = 5.1 \text{ V}$$

$$\Rightarrow V_C = 3.801 \text{ V}$$

60,

$$I_1 = \frac{V_A - V_C}{5} = \frac{12.058 - 3.801}{5}$$

$$\Rightarrow I_1 = 1.6514 \text{ A}$$

$$I_2 = \frac{V_A - V_B}{3} = \frac{12.058 - 5.1}{3}$$

$$\Rightarrow I_2 = 2.319 \text{ A}$$

$$I_3 = \frac{V_A - V_B}{2} = \frac{12.058 - 5.1}{2}$$

$$\Rightarrow I_3 = 6.029 \text{ A}$$

$$I_4 = \frac{V_C}{4} = \frac{3.801}{4}$$

$$\Rightarrow I_4 = 0.95 \text{ A}$$


$$I_5 = \frac{V_B}{5} = \frac{5.1}{5}$$

$$\Rightarrow I_5 = 1.02 \text{ A}$$

$$I_6 = \frac{V_B - V_C}{1} = 5.1 - 3.801$$

$$\Rightarrow I_6 = 1.299 \text{ A}$$

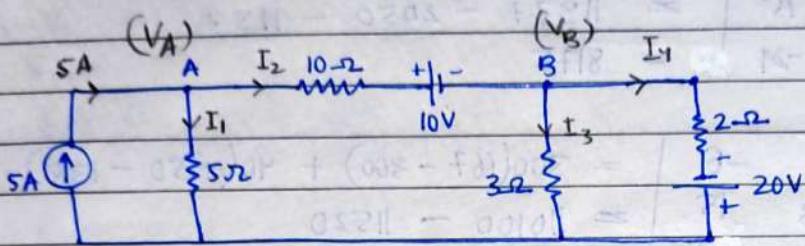Ques. 6) find current and voltage across 2-Ω resistor.



Ans. 1 KCL at node A :-

$$I_1 + I_2 = 5$$

$$\Rightarrow \frac{V_A}{5} + \frac{V_A - V_B - 10}{10} = 5$$

$$\Rightarrow 2V_A + V_A - V_B - 10 = 50$$

$$\Rightarrow 3V_A - V_B = 60 \quad \text{--- (1)}$$

KCL at node B :-

$$I_2 = I_3 + I_4$$

$$\Rightarrow \frac{V_A - V_B - 10}{10} = \frac{V_B}{3} + \frac{V_B - (-20)}{2}$$

$$\Rightarrow V_A - V_B - 10 - 5V_B - 100 = \frac{V_B}{3}$$

$$\Rightarrow 3V_A - 18V_B = 330 \quad \text{--- (11)}$$

eqn. (1) - eqn. (11) :-

$$3V_A - V_B = 60$$

$$\cancel{3V_A} \cancel{- 28V_B} = \cancel{330}$$

$$27V_B = -270$$

$$\Rightarrow V_B = -10 \text{ V}$$

$$V_A = \frac{60 + (-10)}{3}$$

$$\Rightarrow V_A = 16.667 \text{ V}$$

So,

$$I_4 = \frac{V_B + 20}{2} = \frac{-10 + 20}{2}$$

$$\Rightarrow I_4 = 5 \text{ A}$$

Voltage across 2-Ω resistor :-

$$V_{2\Omega} = IR$$

$$\Rightarrow V_{2\Omega} = 5 \times 2$$

$$\Rightarrow V_{2\Omega} = 10 \text{ V}$$

Some Ques can be done by mesh analysis by firstly converting 5A current source to voltage source (+25V)