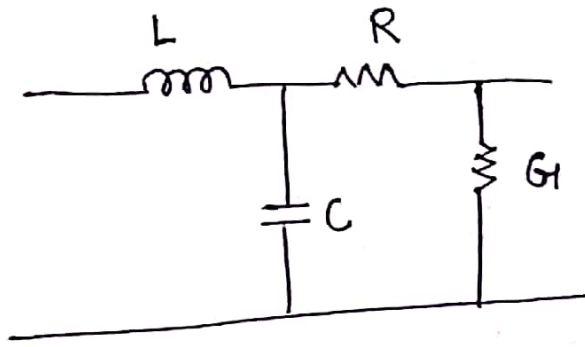


Transmission Line Equation

①




L, R, C, G are constant parameters & its unit is per unit length

$L/m \rightarrow$ to overcome it, multiply 'm' to get absolute value

R/m

C/m

G/m

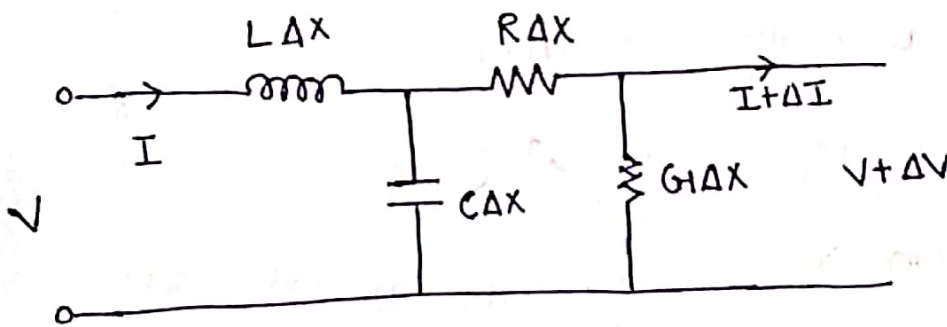

$$\Delta V = -(R\Delta x + j\omega L\Delta x)I$$

(-ve) sign indicate that ' ΔV ' is less the input ' V '

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta V}{\Delta x} = -(R + j\omega L)I$$

$$\frac{dV}{dx} = -(R + j\omega L)I \quad \text{--- ①}$$

Similarly ΔI

$$\Delta I = -(G\Delta x + j\omega C\Delta x)V$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta I}{\Delta x} = -(G + j\omega C)V$$

$$\frac{dI}{dx} = -(G + j\omega C)V \quad \text{--- ②}$$

Double differentiate of Eq (1)

(2)

$$\frac{d^2 V}{dx^2} = -(R + j\omega L) \frac{dI}{dx}$$

put the value of $\frac{dI}{dx}$

$$\frac{d^2 V}{dx^2} = \cancel{(R + j\omega L)} (G + j\omega C) V$$

R, L, G and C are primary constant

$$\frac{d^2 V}{dx^2} = \cancel{R + j\omega L} \gamma^2 V$$

$$V(x, t) = V^+ e^{-\gamma x} + V^- e^{+\gamma x}$$

It is a sinusoidal in nature, ^{if} we want instantaneous, just multiply $e^{j\omega t}$ with these Equation

$$V(x, t) = (V^+ e^{-\gamma x} + V^- e^{+\gamma x}) e^{j\omega t}$$

gamma) $\gamma \rightarrow$ propagation Const.

$$\gamma \rightarrow \alpha + j\beta$$

$\alpha \rightarrow$ attenuation constant

$\beta \rightarrow$ phase constant.

~~For Lossless Medium~~ (if $\alpha = 0$)

$$V(x, t) = V^+ e^{-(\alpha + j\beta)x} e^{j\omega t} + V^- e^{+(\alpha + j\beta)x} e^{j\omega t}$$

For Lossless Medium ($\alpha = 0$)

$$V(x, t) = V^+ e^{-j\beta x} e^{j\omega t} + V^- e^{j\beta x} e^{j\omega t}$$

$$V(x, t) = V^+ e^{j(\omega t - \beta x)} + V^- e^{j(\omega t + \beta x)}$$

$$\Rightarrow V^+ \cos(\omega t - \beta x) + V^- \cos(\omega t + \beta x)$$

travelling in +ve direction

travelling in -ve direction

Characteristic Impedance

(3)

$$\frac{dv}{dx} = -(R + j\omega L) I$$

$$\frac{d(V^+ e^{-\gamma x} + V^- e^{+\gamma x})}{dx} = -(R + j\omega L) (I^+ e^{-\gamma x} + I^- e^{+\gamma x})$$

$$V^+ e^{-\gamma x} (-\gamma) + V^- e^{+\gamma x} (\gamma) = -(R + j\omega L) (I^+ e^{-\gamma x} + I^- e^{+\gamma x})$$

taking part of travelling forward

$$V^+ e^{-\gamma x} (-\gamma) = -(R + j\omega L) (I^+ e^{-\gamma x})$$

$$\frac{V^+}{I^+} = \frac{R + j\omega L}{\gamma}$$


$$\left(\text{where } \gamma^2 = (R + j\omega L)(G + j\omega C) \right)$$
$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\frac{V^+}{I^+} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\boxed{\frac{V^+}{I^+} = Z_0}$$

$Z_0 \rightarrow$ It is the Ratio of (+ve) travelling voltage wave to current wave at any point on the line.

Lossless Tx Line

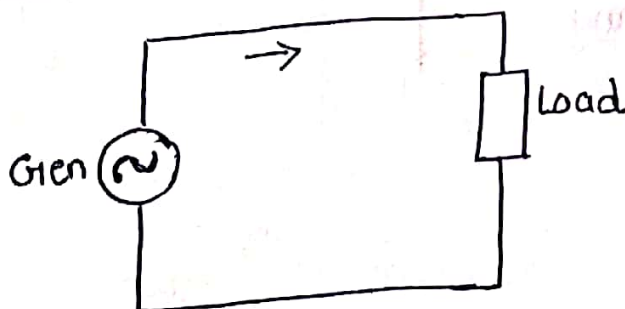

④ A wave or voltage is travelling over a line, their loss should be zero.

$$\boxed{R=0, G=0}$$

Now find propagation constant (γ) & Characteristic Impedance

→ Propagation Constant (γ)

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

put $R=G=0$

$$\gamma = \sqrt{j^2 \omega^2 LC}$$

$$\boxed{\gamma = j\omega \sqrt{LC}} \quad \text{--- (1)}$$

propagation constant (γ) is nothing but $\alpha + j\beta$

$$\alpha \neq \beta \neq \frac{1}{\sqrt{LC}}$$

Compare is it

$$\boxed{N = \alpha + j\beta} \quad \text{--- (2)}$$

Compare these 2 Equation & we get

$$\alpha = 0$$

$$\boxed{\beta = \omega \sqrt{LC}} \quad \text{---}$$

$\alpha \rightarrow$ attenuation constant and it is zero, that means no any attenuation is happening.

Characteristic Impedance

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

put $R=G=0$

$$\boxed{Z_0 = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}}}$$

$$\beta = \omega \sqrt{LC}$$

$$\frac{2\pi}{\lambda} = 2\pi f \sqrt{LC}$$

$$\boxed{f\lambda = \frac{1}{\sqrt{LC}}}$$

$$\boxed{V_p = \frac{1}{\sqrt{LC}}}$$

$V_p \rightarrow$ phase velocity

Distortionless Transmission Line

(5)

A Transmission Line is said to be Distortionless if
attenuation constant (α) \rightarrow independent of frequency
phase constant (β) \rightarrow Linearly dependent on frequency

$$\frac{R}{L} = \frac{G}{C}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

taking 'R' and 'G' common

$$\gamma = \sqrt{R \left(1 + j\omega \frac{L}{R}\right) G \left(1 + j\omega \frac{C}{G}\right)}$$

$$\Rightarrow \sqrt{RG \left(1 + j\omega \frac{C}{G}\right)^2}$$

$$\gamma \Rightarrow \sqrt{RG} \left(1 + j\omega \frac{C}{G}\right)$$

we know that

$$\gamma = \alpha + j\beta$$

$$\alpha + j\beta = \sqrt{RG} \left(1 + j\omega \frac{C}{G}\right)$$

By Comparing

$$\alpha = \sqrt{RG}$$

$$\beta = \sqrt{RG} \omega \frac{C}{G}$$

$$Z_0 = \frac{\sqrt{R + j\omega L}}{\sqrt{G + j\omega C}}$$

$$\Rightarrow \frac{\sqrt{R \left(1 + j\omega \frac{L}{R}\right)}}{\sqrt{G \left(1 + j\omega \frac{C}{G}\right)}}$$

$$\boxed{\frac{R}{L} = \frac{G}{C}} \rightarrow \text{Distortionless Condition}$$

$$Z_0 = \sqrt{\frac{R}{G}}$$


In another way

$$Z_0 = \frac{\sqrt{j\omega L \left(1 + \frac{R}{j\omega L}\right)}}{\sqrt{j\omega C \left(1 + \frac{G}{j\omega C}\right)}}$$

$$Z_0 = \sqrt{\frac{j\omega L}{j\omega C}} \Rightarrow \sqrt{\frac{L}{C}}$$

Input Impedance of short Circuit

⑥

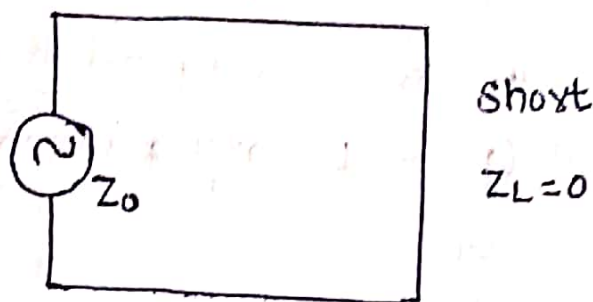

In short circuit, the o/p terminal is short instead of load that means no any load is connected. so $Z_L = 0$

The formula of input impedance is


$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right] \quad \text{--- ①}$$

put $Z_L = 0$ in Equation 1

$$Z_{in} = Z_0 \left[\frac{0 + jZ_0 \tan \beta l}{Z_0 + 0} \right]$$

$$Z_{in} \Rightarrow jZ_0 \tan \beta l$$

Input impedance of Open Circuit

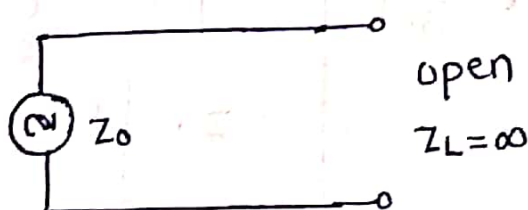

$$\begin{aligned} Z_{in} &= Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right] \\ &= Z_0 \times Z_L \frac{(1 + j \frac{Z_0}{Z_L} \tan \beta l)}{Z_L (\frac{Z_0}{Z_L} + j \tan \beta l)} \end{aligned}$$

~~$Z_{in} = Z_0$~~

When $Z_L = \infty$, we know that any denominator is ∞ then that value becomes zero

$$Z_{in} = \frac{Z_0}{j \tan \beta l} \Rightarrow \boxed{Z_{in} = -j Z_0 \cot \beta l}$$

~~$Z_{in} = -j Z_L \cot \beta l$~~

~~$Z_{in} = \frac{Z_0}{j \tan \beta l}$~~

✱ Relationship b/w voltage standing wave Ratio (VSWR) and Reflection co-efficient (K)

$$|V_{max}| = |V_i| + |V_R| \text{ --- (1)}$$

$$|V_{min}| = |V_i| - |V_R| \text{ --- (2)}$$

where $V_i \rightarrow$ incident voltage
 $V_R \rightarrow$ Reflected voltage

For Current standing wave Ratio

$$S = \frac{I_{max}}{I_{min}}$$

Similarly for voltage

$$VSWR = S = \frac{|V_{max}|}{|V_{min}|} \text{ --- (3)}$$

put Eq (1) & (2) in Eq (3)

$$VSWR = S = \frac{|V_i| + |V_R|}{|V_i| - |V_R|}$$

$$S = \frac{|V_i| \left(1 + \frac{|V_R|}{|V_i|}\right)}{|V_i| \left(1 - \frac{|V_R|}{|V_i|}\right)}$$

$$S = \frac{\left(1 + \frac{|V_R|}{|V_i|}\right)}{\left(1 - \frac{|V_R|}{|V_i|}\right)} \quad \text{--- (4)}$$

then $K = \frac{|V_R|}{|V_i|}$

$$S = \frac{(1 + |K|)}{(1 - |K|)}$$

$$S(1 - |K|) = 1 + |K|$$

$$S - S|K| = 1 + |K|$$

$$S - 1 = S|K| + |K|$$


$$S - 1 = |K|(S + 1)$$

$$\boxed{|K| = \frac{S - 1}{S + 1}} \quad \text{--- (5)}$$

Equation 5th Show the Relationship b/w VSWR & K

* Lines of Different Length

① $\lambda/4$

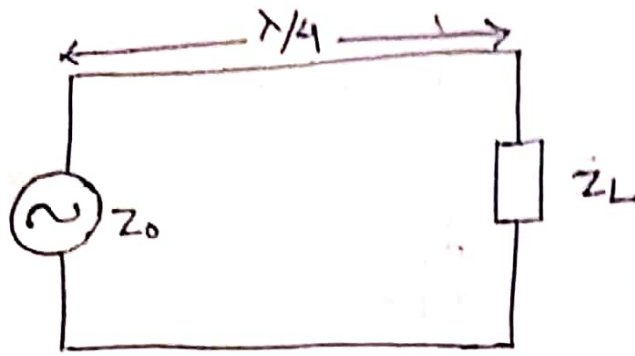

As we know that Input Impedance (Z_{in})

$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$$

where $\beta = \frac{2\pi}{\lambda}$ and $l = \frac{\lambda}{4}$

$$\beta \times l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4} \Rightarrow \frac{\pi}{2}$$

$$Z_{in} = Z_0 \tan \beta l \left(\frac{\frac{Z_L}{\tan \beta l} + jZ_0}{\tan \beta l \left(\frac{Z_0}{\tan \beta l} + jZ_L \right)} \right)$$


put $\beta l = \frac{\pi}{2}$

$$\Rightarrow Z_0 \left(\frac{\frac{Z_L}{\tan \pi/2} + jZ_0}{\left(\frac{Z_0}{\tan \pi/2} + jZ_L \right)} \right) \quad (\tan \pi/2 = \infty)$$

$$Z_{in} \Rightarrow Z_0 \frac{(jZ_0)}{(jZ_L)} \Rightarrow \frac{Z_0^2}{Z_L}$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

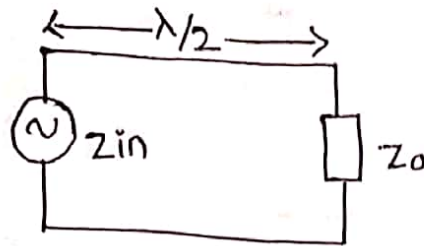2) Half wave Transmission Line ($\lambda/2$)



$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$$

$$\beta = \frac{2\pi}{\lambda}, \quad l = \frac{\lambda}{2}$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{2} = \pi$$

$$\beta l = \pi$$

$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan \pi}{Z_0 + jZ_L \tan \pi} \right) \quad (\tan \pi = 0)$$

$$Z_{in} = Z_0 \left(\frac{Z_L + 0}{Z_0 + 0} \right)$$

$$Z_{in} = Z_L$$

← Smith chart →

what is Smith chart


- ① Smith chart is a graphical method to solve transmission line problem.
- ② It is graph b/w Resistance Component (R/z_0) and Reactance Component ($\pm jX/z_0$)
- ③ where R is normalized Resistance
- ④ z_0 is characteristic impedance and X is normalized Reactance.

← Construction →

→ Smith chart consist of two type of circles

① The Constant R- circles

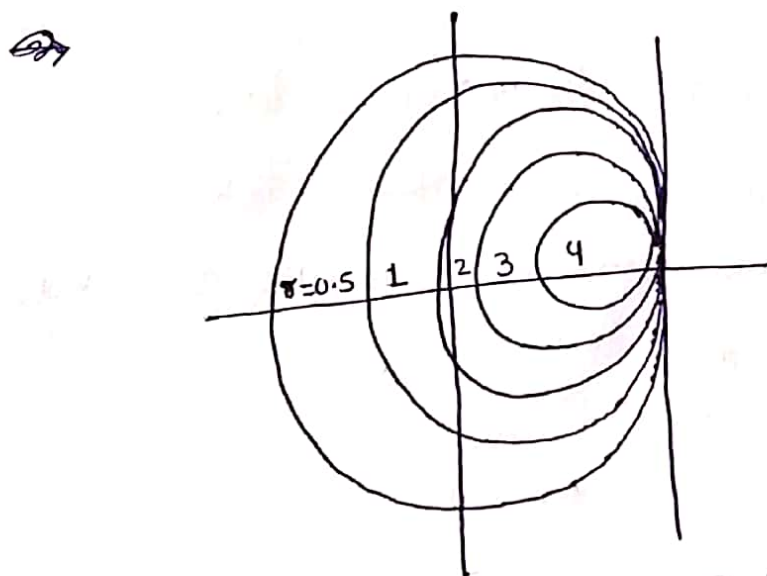
→ Smith chart basically an impedance chart containing two set of lines.



→ All lines are tangent to each other at Right hand & the value of 'R' is decreasing from Left to Right.

② The constant x -circle

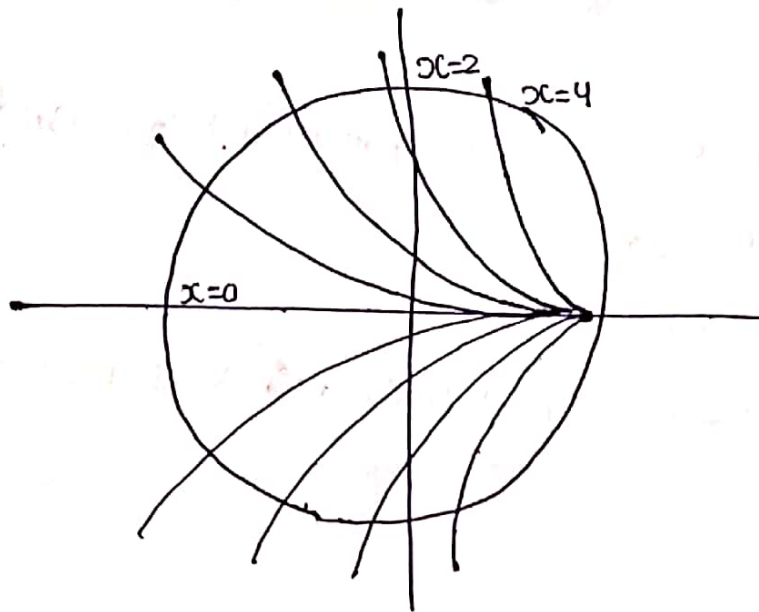→ There is another set of lines called Constant Reactance lines.



→ The lines in the upper half represent (+ve) Reactance while other in the lower represent (-ve) Reactance.

→ The complete Smith chart is obtained by the superposition of the two sets of x -circle & R -circle.

Application

- ① Calculate Admittance on any transmission line
- ② Calculate Impedance on any transmission line
- ③ Calculate the length of a transmission line to provide Capacitance & Inductance Reactance.

* Losses in Transmission Line

① Copper losses

- This type of loss is in the form of heat being dissipated in the line conductor.
- This type of loss appears due to Existence of Resistance in the Conductor
- It Expressed as I^2R

② Dielectric loss

- In transmission Lines, air acts as dielectric medium b/w Conductor & Earth but in Co-axial Cable, the dielectric medium may be channel Compound.
- Dielectric medium losses are also in the form of heat.
- Dielectric loss \propto voltage across dielectric
- Dielectric loss $\propto \frac{1}{Z}$ (in Co-axial Cable)

③ Radiation loss

- Radiation loss arise when the line act as an antenna
- Radiation loss \propto distance b/w 2 Conductor
- Radiation loss $\propto F^2 \rightarrow$ frequency

④ Reflection Loss


- It is also known as Mismatch loss
- When signal is flowing from source to Receiver End & ~~at~~ at Receiving End it starts Reflect back to source.

This phenomenon is known as Reflection loss

- This happens when air & glass are interfere together, this occurs in OFC.


→ In Decibel = $20 \log_{10} \left| \frac{Z_1 + Z_2}{2 \sqrt{Z_1 \times Z_2}} \right|$ (dB)

✱ Impedance Matching

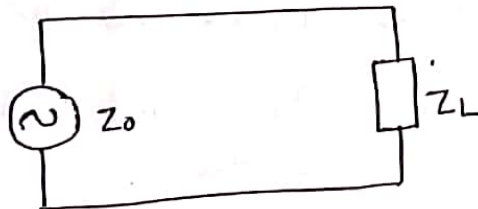


- Impedance matching is, if $Z_0 = Z_L$ then maximum power deliver from source to a Load. (100% power deliver)
- But if $Z_0 \neq Z_L$ then Γ power will be Reflect back. (60% Receive and 40% Reflect back)
- For Impedance matching, put Matching Unit b/w them
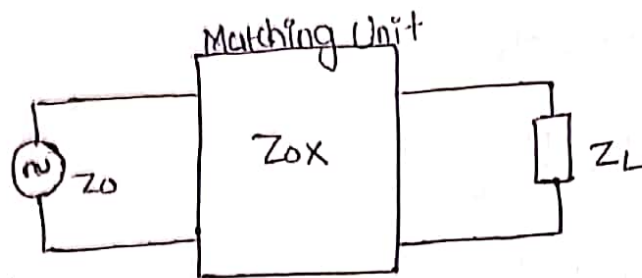
$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$



1) Resistive Load

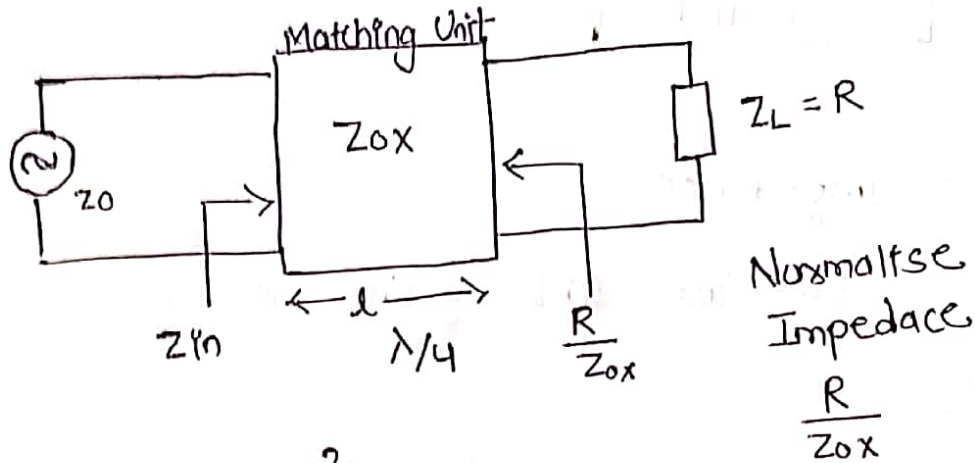

$$Z_{in} = \frac{(Z_{0X})^2}{R} = Z_0$$

$$Z_{0X} = \sqrt{R Z_0} = Z_L$$

* Standing wave Ratio

When the transmission line is not correctly terminated, the traveling EM wave is reflected back. The interference of incident & reflected wave give standing wave of current and voltage along the line.

It is the Ratio of Maximum to minimum, current or voltage on the line.

SWR = standing wave Ratio

$$= \left| \frac{V_{max}}{V_{min}} \right|$$

S = give ~~star~~ amount of mismatch b/w Inci. & Ref.

$S > 1 \rightarrow$ Mismatch

$S = 1 \rightarrow$ totally match.

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

* Input Impedance

There are two cases (1) Lossy line (2) Lossless line

Lossy Line

$$Z_{in} = Z_0 \left[\frac{Z_L + Z_0 \tanh \beta l}{Z_0 + Z_L \tanh \beta l} \right]$$

\rightarrow For short circuit, $Z_L = 0$

$$Z_{in} = Z_0 \left[\frac{0 + Z_0 \tanh \beta l}{Z_0 + 0} \right] \Rightarrow \boxed{Z_0 \tanh \beta l}$$

\rightarrow For Open Circuit, $Z_L = \infty$

$$Z_{in} = Z_0 \times \frac{1 + \frac{Z_0 \tanh \beta l}{Z_L}}{\frac{Z_0}{Z_L} + \tanh \beta l}$$

$$\Rightarrow Z_0 \left[\frac{1 + 0}{0 + \tanh \beta l} \right] \Rightarrow \frac{Z_0}{\tanh \beta l}$$

$$\boxed{Z_{in} = Z_0 \coth \beta l}$$

② Loss Less Line

$$Z_{in} = Z_0 \left[\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

→ For short Circuit, $Z_L = 0$

$$Z_{in} = Z_0 \left[\frac{0 + j Z_0 \tan \beta l}{Z_0 + 0} \right]$$

$$\boxed{Z_{in} = j Z_0 \tan \beta l}$$

→ For Open Circuit, $Z_L = \infty$

$$Z_{in} = Z_0 \times Z_L \left[\frac{1 + \frac{j Z_0 \tan \beta l}{Z_L}}{\frac{Z_0}{Z_L} + j \tan \beta l} \right]$$

$$\Rightarrow Z_0 \left[\frac{1 + 0}{0 + j \tan \beta l} \right]$$

$$\Rightarrow \frac{Z_0}{j \tan \beta l} \Rightarrow -j Z_0 \cot \beta l$$

Loading of transmission Line


Loading is a process in which inductance is ~~adding~~ artificially increase in order to get distortion less condition.

How to increase

- By installation of co-axial cable in series with the line
- By adding induction in lumped form at specific location.

* Single stub Matching

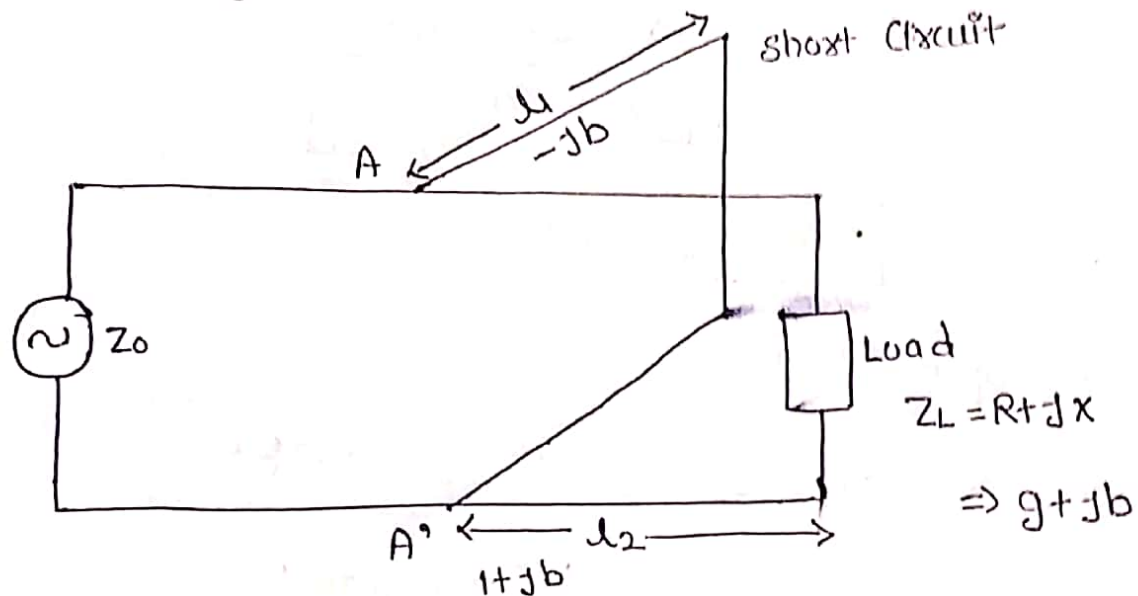- Stub Matching is another way of impedance matching, In IM, The Matching Unit is used for matching but they are only for Resistive Load, not Complex.
- stub Matching is used for Resistance as well as Complex.



- Input wave flowing from source, At point A & A', some will flow toward Z_L & some will flow toward short ckt.
- These are reflect back from both, at A & A', if at this point ~~Reflection~~ if the Reflection is out of phase & Equal in amplitude, both the Reflection is Canceled.
- At A and A', Reflection is zero and it is only possible when impedance is matching.