

Resonance in series L

It is condition ^{in which phasor sum}, at which applied voltage & current are in same phase

In this, impedance of circuit become minimum & current become max.

(At resonance $X_L = X_C$)

$$Z = \sqrt{X_L^2 + R^2}$$

$$Z = \sqrt{R^2} \quad \boxed{\Rightarrow Z = R}$$

Z is min so, current is max

Resonant frequency is frequency at which resonance occurs

(At resonance $X_L = X_C$)

$$\omega L = 1/X_C$$


$$\omega \times \omega = \frac{1}{LC}$$

$$2\pi f \times 2\pi f = \frac{1}{LC}$$

$$4\pi^2 f^2 = \frac{1}{LC}$$

$$f^2 = \frac{1}{4\pi^2 LC}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

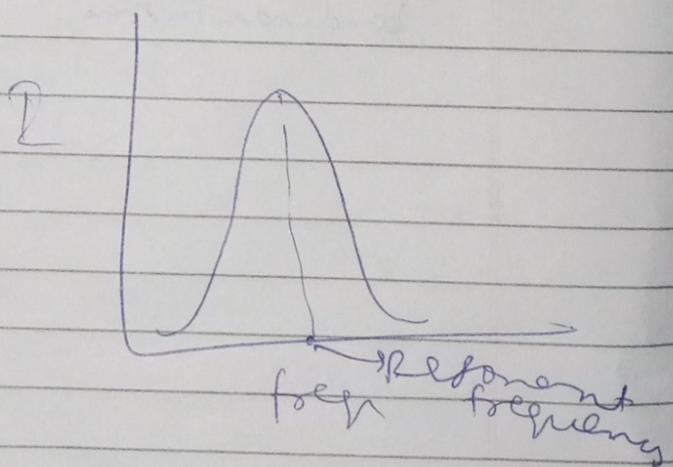

Audley factor is ratio of potential drop across L or C to potential drop across R .

$$\varphi = \frac{V_r \text{ or } V_L}{V_R}$$

$$\alpha = \frac{I X_L}{I R} \Rightarrow \varphi = \frac{\omega L}{R}$$

~~$$\alpha = \frac{2\pi f L}{R} \Rightarrow \alpha = 2\pi f \frac{L}{R}$$~~

$$\text{But } f = \frac{1}{2\pi\sqrt{LC}}$$


$$\alpha = \frac{2\pi I L}{2\pi\sqrt{LC} R}$$

$$\alpha = \frac{I L^2}{R \sqrt{LC}}$$

$$\boxed{\alpha = \frac{I}{R} \sqrt{\frac{L}{C}}}$$

Bandwidth

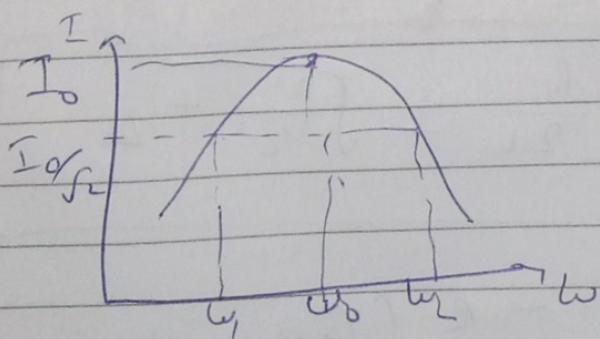The difference between lower half power frequencies
is lower half power frequency.



$$\Delta \omega = \omega_2 - \omega_1$$

$$I_{max} = \frac{V}{R}$$

At half power

$$\frac{I^2}{2} = \frac{I_{max}^2}{2} = \frac{V^2}{2R}$$

\Rightarrow Impedance at half power
 $\Rightarrow R$

\Rightarrow Now let's find ω_1 & ω_2
 $\Rightarrow Z = \sqrt{2} R$

$$\Rightarrow R + j(\omega L - \frac{1}{\omega C}) = R + jR$$

$$\Rightarrow \omega L - \frac{1}{\omega C} = \pm R$$

$$\Rightarrow \omega L - \frac{1}{\omega C} = R \quad (\text{For Inductive})$$

$$\Rightarrow \omega_2 L - \frac{1}{\omega_2 C} = R$$

$$\Rightarrow \omega_2^2 LC - 1 = \omega_2 CR$$

$$\Rightarrow \omega_2^2 LC - \omega_2 CR - 1 = 0$$

$$\Rightarrow \omega_2^2 - \frac{R}{L} \omega_2 - \frac{1}{LC} = 0$$

$$\Rightarrow \omega_2 = \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\Rightarrow \boxed{\omega_2 = \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}}$$

$$\Rightarrow \omega L - \frac{1}{\omega C} = -R \quad (\text{Capacitive})$$

$$\Rightarrow \omega_1 L - \frac{1}{\omega_1 C} = -R$$

$$\omega_1^2 LC - 1 = -RC\omega_1$$

$$\omega_1^2 LC + RC\omega_1 - 1 = 0$$

$$\omega_1^2 + \frac{R}{L}\omega_1 - \frac{1}{LC} = 0$$

$$\Rightarrow \omega_1 = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}}{2}$$

$$\Rightarrow \omega_1 = \frac{-\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}}{2}$$

\Rightarrow Bandwidth $\Rightarrow \Delta\omega = \omega_2 - \omega_1$

$$\Rightarrow \Delta\omega = \left[\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} \right]$$

$$- \left[-\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} \right]$$

$$\Rightarrow \boxed{\Delta\omega = \frac{R}{L}}$$