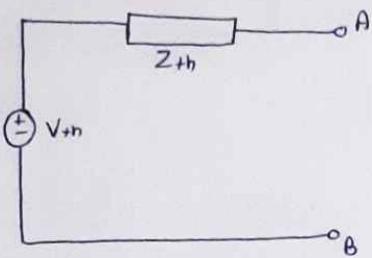


Thevenin's Theorem :-

With respect to terminal pair AB, the network N replaced by the voltage source ~~Vth~~ and internal impedance of the circuit Z_{th} . The voltage source V_{th} is called Thevenin's voltage is the potential difference ($V_A - V_B$) between the terminal A and B.

Z_{th} is the internal impedance of voltage source shorted and the current source open circuited having the resistance impedance.


The series combination of V_{th} , ~~Z_{th}~~ and is known as Thevenin's Theorem.



Norton's Theorem:-

With respect to the terminal AB, the Network N may be replaced with the current source parallel to the internal impedance of ~~Z_N~~ Z_N . The current source, I_N called as Norton's current. The current that would flow from the A to B terminal are shorted together and The current impedance.

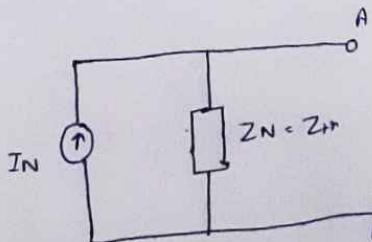
The parallel combination of I_N and Z_N is the N Network is known as Norton's equivalent.



$$I_L = \frac{V_{th}}{R_L + R_{th}}$$

~~$I_L = \frac{I_N \cdot V_{th}}{Z_{th} + Z_L}$~~

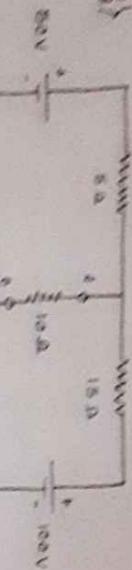
$$I_L = \frac{I_N \cdot V_{th}}{Z_{th} + Z_L}$$



Find current across the load Resistor $R_L = 10\Omega$

Sol: Removing the load Resistor and converting into open circuit
By the KVL
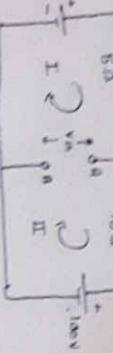
$$V_{th} = 50 + 5I_o \{ \text{loop I} \}$$



Also

$$V_{th} = 100V - 15I_o \quad [\text{loop II}]$$

$$-50 + 5I_o = 100V - 15I_o$$

$$5I_o + 15I_o = 100 + 50$$

$$20I_o = 150$$

$$I_o = 2.5$$

$$\boxed{I_o = 15A}$$

$$V_{th} = -50 + 5I_o \Rightarrow -50 + 5(2.5)$$

$$\cancel{V_{th} = 50 + 12.5}$$

$$\boxed{V_{th} = 62.5V}$$


Now, R_{th}/Z_{th} will be;

$$Z_{th} = 5//15 \Rightarrow 3.75$$

$$\boxed{Z_{th} = 3.75\Omega}$$

$$T_L = \frac{V_{th}}{Z_{th} + Z_L} \Rightarrow \frac{62.5}{3.75 + 10} \Rightarrow$$

$$\boxed{T_L = 4.54A}$$

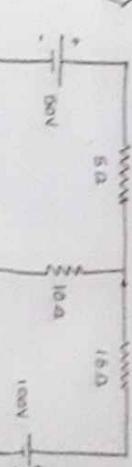

Rev. Terminal A and B : Short circuiting the Load Resistor 10Ω .
Join the Tn from the load Resistor

By the KVL

$$-50 + 4.5I_n \cancel{\Rightarrow 0} = 0$$

$$8I_n \cancel{\Rightarrow 50} = 50 \Rightarrow 0$$

Join loop II ;

$$100 - 16I_2 \cancel{\Rightarrow 0}$$

$$16I_2 = 100 \Rightarrow 10$$

$$I_N = I_1 + I_2$$

$$I_N = 10 + 6.667$$

$$\boxed{I_N = 16.667}$$

$$\text{By } Z_{th} ; \text{ will be } 5//15 \Rightarrow \frac{5 \times 15}{5+15}$$

$$\boxed{Z_{th} = 3.75\Omega}$$

Thus By the Norton's equivalent :


$$T_L = I_N \left(\frac{Z_{th}}{Z_{th} + Z_L} \right)$$

$$T_L = 16.667 \left[\frac{3.75}{3.75 + 10} \right] \Rightarrow 16.667 \left[\frac{3.75}{13.75} \right]$$


$$\boxed{T_L = 4.54A}$$

Network Theorems

Star Delta Transformations :-

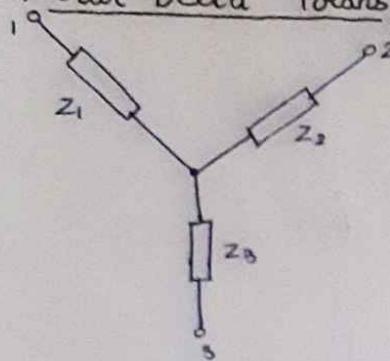

Star Connection

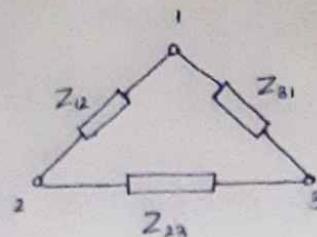

Delta connection

Delta to star connection:-

$$Z_1 = \frac{Z_{12} Z_{31}}{Z_{12} + Z_{23} + Z_{31}}$$

$$Z_2 = \frac{Z_{23} Z_{12}}{Z_{12} + Z_{23} + Z_{31}}$$

$$Z_3 = \frac{Z_{31} Z_{23}}{Z_{12} + Z_{23} + Z_{31}}$$

Star to Delta Connection :-

$$Z_{12} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

$$Z_{23} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_{31} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

Q) Find the voltage across the impedance
then transform voltage source and $10 < 30^\circ \Omega$
to an equivalent current source:

By the KVL:


$$V_1 = 50 < 20^\circ \times \frac{10 < 30^\circ}{10 < 30^\circ + 8 < 20^\circ} \Rightarrow \frac{500 < 50^\circ}{17.9 < 25.6^\circ}$$

$$V_1 = 27.9 < 24.4^\circ V$$

$$V_2 = 50 < 20^\circ - 27.9 < 24.4 \Rightarrow 22.1 < 14.4^\circ$$

$$I = \frac{V}{10 < 30^\circ} \Rightarrow \frac{50 < 20^\circ}{10 < 30^\circ} \Rightarrow 5 < -10^\circ A$$
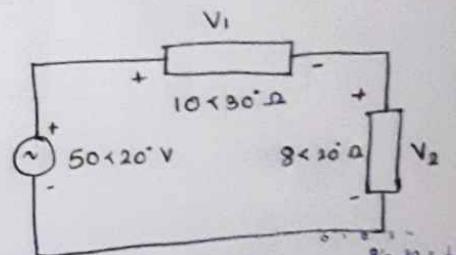
$$V = R_{th} \times I \Rightarrow 22.1 < 14.4^\circ$$




Rough

$$10 < 30^\circ \quad \tan^{-1}(\tan 30)$$

$$10 < \tan^{-1} \frac{1}{\sqrt{3}}^\circ$$

$$1 + \sqrt{3}j$$

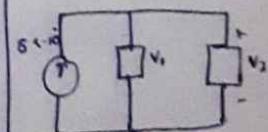

Kirchhoff's current law:

The algebraic sum of all branch currents leaving or entering a node is zero at all instants of time

According to the statement

$$-i_1 - i_2 + i_3 - i_4 + i_5 + i_6 = 0$$

$$\boxed{i_3 + i_5 + i_6 = i_1 + i_2 + i_4}$$


Kirchhoff's voltage law:

The algebraic sum of drop in all branch voltages in closed circuit around a loop is zero at all instant of time

$$\sum V_i = 0$$


$$V_1 + V_2 + V_3 + V_4 - V_5 = 0$$

$$\boxed{V_1 + V_2 + V_3 + V_4 = V_5}$$

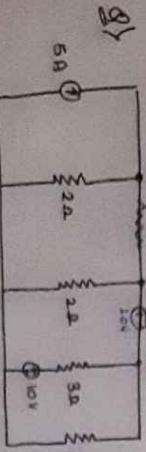

$$V_2 - V_3 = 20 \Rightarrow V_3 = V_2 - 20$$

Calculate the current in 3Ω resistor.

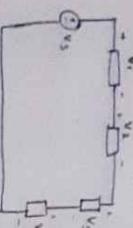

By the Node analysis

at node 1

$$5 = \frac{V_1}{2} + \frac{V_1 - V_2}{1}$$

$$\Rightarrow 5 = \frac{V_1 + 2V_1 - 2V_2}{2}$$

$$10 = 3V_1 - 2V_2 \quad \text{---(1)}$$

at node 2 and 3

$$\frac{V_2 - V_1}{2} + \frac{V_2 - 10}{2} + \frac{V_2 - 20}{2} = 0 \Rightarrow 6V_2 - 6V_1 + 3V_2 + 2V_3 - 90 + 3V_3 = 0$$

$$9V_2 - 6V_1 + 5V_3 = 0$$

$$9V_2 - 6V_1 + 5V_3 = 0$$

$$9V_2 - 6V_1 + 5V_3 = 0$$

$$\begin{aligned} 9V_2 - 6V_1 + 5V_3 &= 100 \\ 14V_2 - 6V_1 &= 100 \quad \text{---(2)} \\ 8V_1 - 2V_3 &= 10 \end{aligned}$$

$$\begin{array}{r} -6V_1 + 14V_2 = 100 \\ 6V_1 - 4V_2 = 20 \\ \hline 10V_2 = 120 \end{array}$$

$$\boxed{V_2 = 12}$$

$$\boxed{V_3 = -8}$$

$$\text{Given eq: } 3V_1 - 2V_2 = 10$$

$$-6V_1 + 9V_2 + 5V_3 = 20$$

$$V_2 - V_3 = 20 \Rightarrow V_3 = V_2 - 20$$

$$-6V_1 + 9V_2 + 5(V_2 - 20) = 20$$

$$-6V_1 + 9V_2 + 5V_2 - 100 = 20$$

$$-6V_1 + 14V_2 = 120$$


$$6V_1 - 4V_2 = 20$$

$$\begin{array}{r} 10V_2 = 140 \\ \hline V_2 = 14 \end{array}$$

$$\boxed{V_2 = 14}$$

$$V_3 = V_2 - 20 = 14 - 20 = -6$$

$$\boxed{V_3 = -6}$$

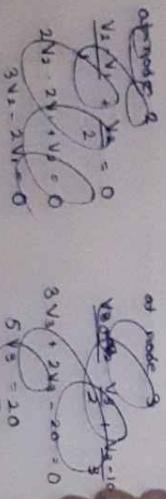

Super mesh Analysis :-

Q) calculate the current in 3Ω resistor

Ans) Applying the KVL (mesh 1 and 3)

$$7 = 1(I_1 - I_2) + 3(I_3 - I_2) + I_3$$

$$7 = I_1 - I_2 + 3I_3 - 3I_2 + I_3$$

$$7 = I_1 - 4I_2 + 4I_3 \quad \text{---(i)}$$

In mesh 2 :

$$1(I_2 - I_3) + 2I_2 + 3(I_2 - I_3) = 0$$

$$T_2 - T_1 + 2I_2 + 3I_2 - 3I_3 = 0$$

$$-T_1 + 6I_2 - 3I_3 = 0 \quad \text{---(ii)}$$

Also from the given circuit

$$T_2 - T_3 = 3T_1 \quad \text{---(iii)}$$

$$T_1 = T_2 + T_3$$

$$\Rightarrow 7 = T_1 + T_2 - 4I_2 + 4I_3 \quad | - (7 + T_3) + 6I_2 - 3T_1 \\ -7 = T_3 + 6I_2 - 3T_1 \quad | 0$$

$$T_3 = T_1 + 5I_2 - 4I_2$$

$$5I_3 - 4I_2 = 0$$

$$20T_3 - 16I_2 = 0 \quad | 5T_3 - 4(2.5) = 0 \\ -20I_2 + 30I_2 = 35 \quad | 5I_3 - 10 = 0$$

$$[I_3 = 2A]$$


$$T_1 = T_2 + T_3$$

$$T_1 = 7A$$

Current from 3Ω resistor

$$T_1 = T_2 + T_3 \Rightarrow 2.5 - 2$$

$$[T_1 = 9A]$$

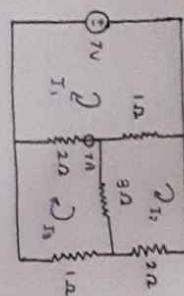

Q) Calculate the V on the circuit?

By the Ohm's law :

$$I_1 = \frac{V}{R} = \frac{36}{20 \times 10^3}$$

$$I_1 = 1.8 \times 10^{-3}$$

$$[I_1 = 1.8mA]$$

By the KVL at node 1

$$I_2 = I_1 + 10I_2$$

$$I_2 = 1.8 + 10I_2$$

$$-9I_2 = 1.8$$

$$[I_2 = -0.2mA]$$

Finally the voltage at 5kΩ will be ;

$$V = RI_2$$

$$V = 5 \times 10^3 [10 \times 0.2 \times 10^{-3}]$$

$$[V = 10V]$$

Q) Determine the current ?

By the KVL :

$$-12 + 2I + V_1 = 0$$

$$V_1 = 12 - 2I \quad \text{---(i)}$$


$$\text{and. } -12 + 2I + 6I - 2V_1 = 0$$

$$2I + 6I - 2(12 - 2I) = 12 \quad [\text{from eq(i)}]$$

$$2I + 6I - 24 + 4I = 12$$

$$8I = 12 + 24$$

$$[I = 3A]$$

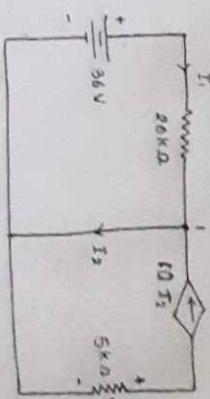

Q) Determine the current I through 10Ω resistance;

a) Nodal Analysis

b) Mesh Analysis

Ans)

a) Nodal Analysis :-

Apply KCL at node 1:

$$\frac{V-50}{5} + \frac{V}{10} + \frac{V-100}{15} = 0$$

$$6V - 300 + 3V + 2V - 200 = 0$$

$$8V = 500$$

$$IV = 500 = 0$$

$$V = \frac{500}{11}$$

$$V = 45.45V$$


Current from 10Ω resistance;

$$I = \frac{V}{R} = \frac{45.45}{10}$$

$$I = 4.543A$$

b) Mesh Analysis:

By the KVL at Loop 1:

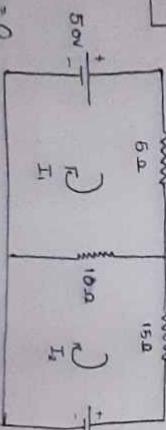

$$-50 + 5I_1 + 10(I_1 - I_2) = 0$$

$$5I_1 + 10I_1 - 10I_2 = 50$$

$$15I_1 - 10I_2 = 50$$

$$3I_1 - 2I_2 = 10$$

Now, at Loop 2:

$$100 - 15I_2 - 10(I_2 - I_1) = 0 \Rightarrow 100 - 15I_2 - 10I_2 + 10I_1 = 0$$

$$10I_1 - 25I_2 + 100 = 0$$

$$2I_1 - 5I_2 = 20$$

Now, from the eq (1) and eq (2);

$$3I_1 - 2I_2 = 10$$

$$2I_1 - 5I_2 = 20$$

$$6I_1 - 4I_2 = 20$$

$$I_1 - 15I_2 = 60$$

$$11I_2 = -40$$

$$I_2 = -\frac{40}{11}$$

$$3I_1 - 2\left(-\frac{40}{11}\right) = 10$$

$$3I_1 + \frac{80}{11} = 10 \Rightarrow 10 - \frac{80}{11}$$

$$3I_1 = \frac{110 - 80}{11}$$

$$3I_1 = \frac{30}{11}$$

$$I_1 = \frac{10}{11}$$

Current through 10Ω resistance;

$$I = I_1 - I_2$$

$$I = \frac{10}{11} - \left(-\frac{40}{11}\right)$$

$$I = \frac{50}{11} \Rightarrow 4.545A$$

$$I = 4.545A$$

Q) obtain the thvenin and Norton's equivalent parameters

By the Thevenin's;

$$V_{th} = \frac{(5+j5)(5+j5)}{5+5+10+j5+j5} 5 < 80^\circ$$


$$\sqrt{V_{th}} = \frac{(5\sqrt{3} < 45^\circ)^2}{20+10j} 5 < 90^\circ$$

$$\sqrt{V_{th}} = \frac{250 < 120^\circ}{20+3.5j} 5 < 90^\circ$$

$$\boxed{V_{th} = 11.21 < 97.49^\circ V}$$

Now, short circuiting the independent source we will get

$$Z_{th} = [(5+5j)+10] // (5+5j)$$

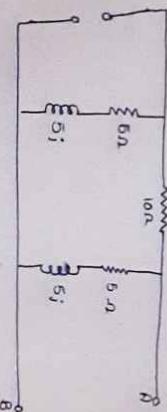

$$Z_{th} = [15+5j] // (5+j5)$$

$$Z_{th} = \frac{(15+5j)(5+j5)}{15+5j+5+5j} = \frac{75+75j+22j-25}{20+10j} = \frac{75+97j}{20+10j} = 7.5 + 9.7j$$

$$Z_{th} = \frac{50+97j}{20+10j} \Rightarrow \frac{10.9 \cdot 12 < 1.78^\circ}{20+3 < 22.5}$$

$$\boxed{Z_{th} = 4.89 < -20.72^\circ \Omega}$$

for the Norton's parameter;

$$I_N = \frac{V_{th}}{Z_{th}} = \frac{11.21 < 97.49^\circ}{4.89 < -20.72^\circ} = 2.29$$


$$\boxed{I_N = 2.29 < 76.78 A}$$

$$\boxed{Z_{th} = Z_N = 4.89 < -20.72^\circ \Omega}$$

Q) Find the Thvenin's equivalent circuit at terminals AB;

$$V_{th} = \text{Voltage across } (-j5) \Omega$$
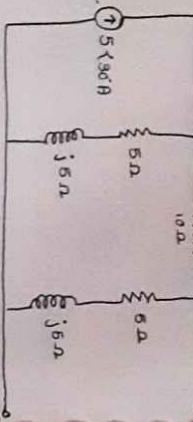
$$V_{th} = \frac{20 < 30^\circ}{(3+j10) \Omega} \cdot (-j5)$$



$$V_{th} = \frac{-50\sqrt{3}j}{3+5j} - (-1)^{50} \Rightarrow \frac{50-50\sqrt{3}j}{3+5j} = \frac{100 < -60^\circ}{5.83 \angle 59.03^\circ} = 10\sqrt{3} < 10.0j$$


$$\boxed{V_{th} = 17.15 < -119^\circ V}$$

for the calculation of Z_{th} short circuiting the Independent source;

$$Z_{th} = [3+10j] - j5 + (5\Omega)$$

$$Z_{th} = \frac{[3+10j] [-j5]}{3+10j - 5j} + 5$$

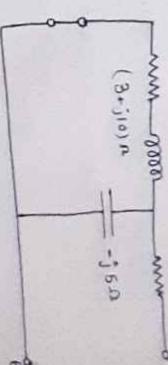
$$Z_{th} = -\frac{15j}{3+5j} + 5 \Rightarrow -\frac{15j+50}{3+5j} + 5$$



$$Z_{th} = -\frac{15j+50 + 15+25j}{3+5j} \Rightarrow \frac{65+10j}{3+5j} \Rightarrow \frac{65.76 < 8.74^\circ}{5.83 \angle 59.03^\circ}$$

$$\boxed{Z_{th} = 11.279 < -50.29^\circ \Omega}$$

Thevenin equivalent will be;

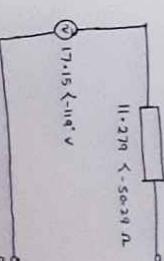

Q) Find the Norton's Equivalent circuit across terminals from A-B

Applying the KVL

$$-12V + 10i_o = 0$$

$$10i_o = 12$$

$$i_o = 1.2A$$

At the node A the current will be;

$$I_N = i_o + 2i_o$$

$$I_N = 1.2 + 2(1.2) \Rightarrow 1.2 + 2.4$$

$$\boxed{I_N = 3.6A}$$

Voltage across the 5Ω will be;

~~Use Δ rule~~

$$V_m = 5 \times (\text{Current through } 5\Omega \text{ resistor})$$

Applying KVL;

$$-12 + 10i_o + 5(i_o + 2i_o) = 0$$

$$25i_o = 12$$


$$i_o = \frac{12}{25}$$

~~Use Δ rule~~

$$V_m = \frac{15 \times 12}{25}$$

~~Use Δ rule~~

$$\boxed{V_m = 7.2V}$$

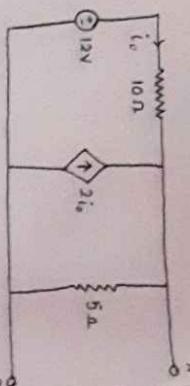


Superposition Theorem :-

In an active linear network containing several sources:

In any branch in the network equals the algebraic sum of the response of each individual source.

Voltage Source \Rightarrow short circuited [internal impedance will be zero]

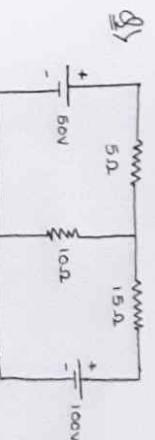Current source \Rightarrow open circuited [internal impedance will be infinite]



In the first situation;

$$V_1 = 50V \text{ and } V_2 = 100V$$

The V_2 independent source that will replace by the internal resistance will be short circuited.

$$R_{eq} = (15/10) + 5$$

$$R_{eq} = \frac{15 \times 10}{15+10} + 5 \Rightarrow \frac{150 + 125}{25} = \frac{275}{25}$$

$$\boxed{R_{eq} = 11.2}$$


$$I_T = \frac{V}{R_{eq}} = \frac{50}{11}$$

By the Current Division Rule

$$I_x = I_T \cdot \frac{R_T}{R_x + R_T}$$

$$I' = \frac{50}{11} \times \frac{15}{15+10} \Rightarrow \frac{50}{11} \times \frac{15}{25} = \frac{30}{11}$$

$$\boxed{I' = \frac{30}{11} A}$$

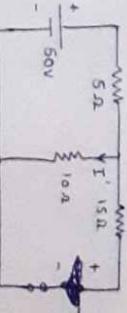


Now, V_L will be short circuited and taking the $V_S = 100V$

$$R_{eq} = (5 + 10) + 15 \Rightarrow \frac{50}{15} + 15$$

$$R_{eq} = \frac{50 + 225}{15} \Rightarrow \frac{275}{15}$$

$$\boxed{R_{eq} = 18.334 \Omega}$$

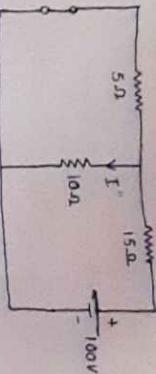

$$I'_r = \frac{V_r}{R_{eq}} = \frac{100}{18.334} \Rightarrow \boxed{I'_r = 5.454 A}$$

$$\text{Thus, } I'' = I'_r \times \frac{5}{5+10}$$

$$I'' = \frac{5 \cdot 454 \times 5}{15}$$

$$\boxed{I'' = 1.818 A}$$

Hence, By Superposition Theorem we will get;

$$I = I' + I''$$

$$I = 2.72 + 1.818$$

$$\boxed{I = 4.545 A}$$

Maximum Power Transfer :-

Maximum power transferred output is obtained from an A.C. circuit when the load impedance is equal to the internal impedance of the circuit.

Any network can be converted into single voltage source with series impedance.

In fact DC circuit :-

Load resistance = Internal resistance [Thévenin's theorem]

\Rightarrow For AC circuit :-

\Rightarrow Load Impedance = complex conjugate of Internal Impedance

\Rightarrow Load Resistance = Magnitude of internal impedance

$$P_{max} = \frac{V_m^2}{4R_L}$$

Q) Calculate current I by superposition Theorem;

Case 1:- When 70V source acts alone

By KVL:

$$-70 + 20(i_x - I_1) - 2(i_x - I') = 0$$

$$20i_x - 20I_1 - 2i_x + 2I' = 70$$

$$18i_x - 20I_1 + 2I' = 70 \quad (i)$$

$$-2I_1 + 2(I' - i_x) + 10I' = 0$$

$$12I' - 2I_1 + 2i_x = 0 \quad (ii)$$



$$4I_1 + 2I_1 + 20(I_1 - i_x) = 0$$

$$6I_1 + 20I_1 - 20i_x = 0$$

$$26I_1 - 20i_x = 0 \quad (iii)$$

By putting the value of I_1 in eqn (i) and (ii)

$$\boxed{I' = 3.425 A}$$

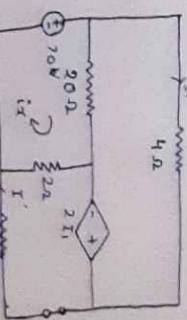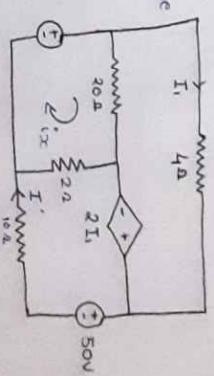

$$\boxed{I_1 = \frac{10}{13} A}$$

Case 2: when 50V source acts alone:

By KVL equation;

$$-50 + 10\text{I}'' + \frac{20}{11}(\text{I}'' - \text{I}_1) - 2\text{I}_1 = 0$$

$$10\text{I}'' + \frac{20}{11}\text{I}'' - \frac{20}{11}\text{I}_1 - 2\text{I}_1 = 50$$

$$\frac{130}{11}\text{I}'' - \frac{42}{11}\text{I}_1 = 50$$

$$130\text{I}'' - 42\text{I}_1 = 550$$

$$4\text{I}_1 + 2\text{I}_1 + \frac{20}{11}(\text{I}_1 - \text{I}''') = 0$$

$$6\text{I}_1 + \frac{20}{11}\text{I}_1 - \frac{20}{11}\text{I}''' = 0$$

$$6\text{I}_1 + \frac{10}{11}\text{I}''' = 0$$

$$6\text{I}_1 = \frac{20}{11}\text{I}''' = 0$$

$$\text{Putting } \text{I}_1 \text{ into equation (1) and}$$

$$\boxed{\text{I}''' = 4.572\text{A}}$$

By the super-position Theorem;


$$\text{I} = \text{I}' + \text{I}''$$

$$\text{I} = 3.425 + 4.572$$

$$\boxed{\text{I} = 7.997\text{A}}$$

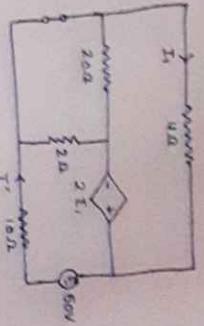(i) Determine the current in capacitor branch by superposition theorem

Case 1 :-
when voltage source acts alone,



$$\text{I}' = \frac{4 \times 0'}{(3 + 4j) + (3 - 4j)} \Rightarrow \frac{4 \times 0'}{6}$$

$$\boxed{\text{I}' = \frac{2}{3} \times 0' \text{A}}$$

Case 2 :- when current source acts alone
Voltage source is short circuited

$$\text{I}'' = 2 \angle 90^\circ \left[\frac{3+4j}{(3+4j) + (3-4j)} \right]$$


$$\text{I}'' = 2 \angle 90^\circ \left[\frac{3+4j}{6} \right] = 2j \left[\frac{3+4j}{6} \right]$$

~~RECKS PRACTICE~~


$$\text{I}'' = R + \text{j}X$$

$$\text{I}'' = \frac{6j - 8}{6} \Rightarrow j - \frac{4}{3} \text{A}$$

$\angle 90^\circ$

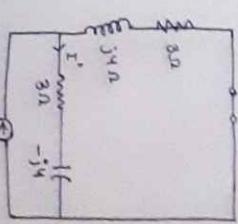

$\angle 90^\circ$

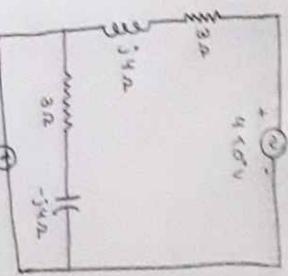

$\angle 90^\circ$

Hence, By the super position Theorem;

$$\text{I} = \text{I}' + \text{I}''$$

$$\text{I} = \frac{2}{3} - \frac{4}{3} + j \Rightarrow -\frac{2}{3} + j$$

$$\boxed{\text{I} = 1.2 \angle 123.7^\circ \text{A}}$$

$\angle 90^\circ = 2 \angle 90^\circ + j 2 \angle 90^\circ$

$\Rightarrow j^2$

~~The synthesis of one Port Network is [by two elements]~~

Impedance and Admittance :-

Impedance is the measure of the opposition to electrical flows it is defined as the voltage across an element divided by the current

Represented by Z

$$Z = R \pm j\omega$$

where, R = Resistance

ω = Reactance

and $+$ \Rightarrow Lagging

$-$ \Rightarrow Leading

$$\text{Also } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Impedance Formula:

(Series)

$$RL \Rightarrow Z = \sqrt{R^2 + X_L^2}$$

$$RC \Rightarrow Z = \sqrt{R^2 + X_C^2}$$

~~$LC \Rightarrow Z = X_L - X_C$~~

$$RLC \Rightarrow \sqrt{R^2 + (X_L - X_C)^2}$$




(Parallel)

$$(RL) \therefore Z = \frac{RX_L}{\sqrt{R^2 + X_L^2}}$$

$$(RC) \therefore Z = \frac{RX_C}{\sqrt{R^2 + X_C^2}}$$

$$(LC) \therefore Z = \frac{X_L X_C}{X_L - X_C}$$
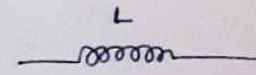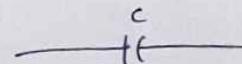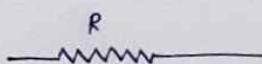
$$(RLC) \therefore Z = \frac{RX}{\sqrt{R^2 + X^2}} \quad [X = \frac{X_L X_C}{X_L + X_C}]$$



$$G = \frac{1}{R} = \text{conductance}$$

$$X_C = \frac{1}{\omega C}$$

$$X_L = \omega L$$

$$B_C = \frac{1}{X_C} = \omega C$$

$$B_L = \frac{1}{X_L} = \omega L$$

Admittance is expression of the case which Allowing current (A_C) flows through a complex circuit or system.

Admittance is expression of the case which Allowing
flow through a complex circuit or system.

Pilobolus displaced by

$$\text{Efficiency} = \frac{I}{\text{Impulse}}$$

۲۸

where σ is the conductance

60 The Subscription

卷之三

$$Y_3 = (5-j2)H(3+1)/j4$$

$$Y_{\text{in}} = \frac{(5 - j2)(3 + j)(-j^4)}{5 + j2 + 3 + j - j^4} \Rightarrow \frac{-j^4 [15 + 5j - 6j - (-1)^2]}{8 - 5j}$$

Nepal - 1992

$$\frac{-j^4}{8-5j} [18-j]$$

$$Y_{44} = -\frac{70j + (-1)^4}{8+5j} \Rightarrow -\frac{70j - 4}{8-5j} \Rightarrow \frac{(70j + 4) \times 8+5j}{64 - (-1)25}$$

$$y_{eq} = - \frac{(676j + (-1)360 + 32 + 20j)}{64 + 25} \Rightarrow \frac{(-828 + 546j)}{89}$$

$$Y_{41} = \frac{328 - 596j}{89} \rightarrow \underline{\underline{3.635 - 6.69j}}$$

join the input Impedance;


$$T_{in} = 30 \text{ H} \delta \alpha / (40 + 10j)$$

$$T_{in} = \frac{30 \times 60 \times (40 + 10)}{80 + 60 + 40 + 10} \Rightarrow \frac{1800 (40 + 10)}{130 + 10} \Rightarrow \frac{180 (40 + 10)}{130}$$

$$T_{1^{\circ}} = \frac{7200 + 1800}{13+1} \times \frac{13-j}{13+j}$$

$$T_{in} = \frac{95400 + 16200}{170} \Rightarrow 561.17 + 95.26 \Rightarrow$$

$$T_{in} = 561.17 + 95.26j$$

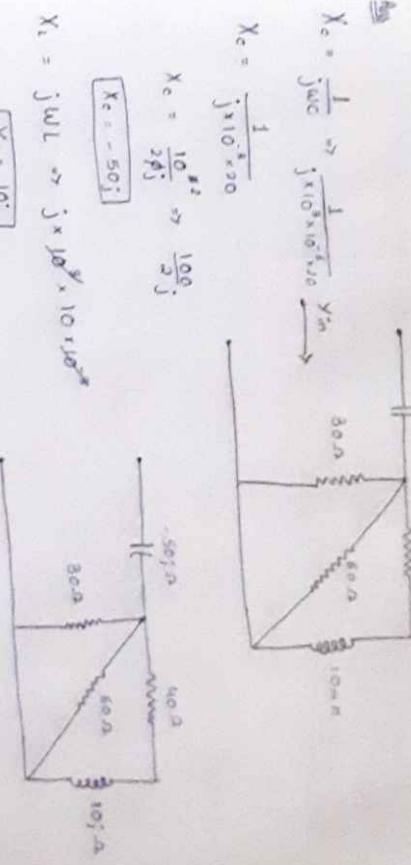

Q) At $\omega = 10^3 \text{ rad/sec}$. Find the input admittance.

Ans) Join the susceptance?

$$B_L = j\omega C = j \times 10^3 \times 12.5 \times 10^{-6}$$

$$B_C = j \times 10^3 \times 12.5$$

$$[B_L = 12.5 j \text{ mho}]$$

$$B_L = \frac{1}{j\omega L} \Rightarrow j \times 10^3 \times 20 \times 10^{-6} = \frac{1}{20j}$$

$$[B_L = -\frac{1}{20j}]$$

$$Y_{in} = (60 + 12.5j) // (-\frac{1}{20j})$$


$$Y_{in} = \frac{[60 + 12.5j] * (-\frac{1}{20j})}{60 + 12.5j - \frac{1}{20j}}$$

$$\Rightarrow \frac{\frac{1}{20j} + 12.5 \times \frac{1}{20}(-1)}{60 + 12.5j}$$

$$Z_{in} = \frac{V}{I}$$

$$X_o = \frac{1}{j\omega L} = -100j$$


$$X_o = -100j$$

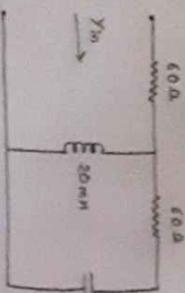

$$2\pi H \Rightarrow X_L = j\omega L$$

$$X_L = j \times 20 \times 10^{-3} \times 10^3 \text{ rad/sec}$$

$$[X_L = 20j]$$

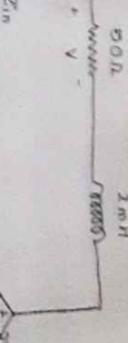

$$2\pi H \Rightarrow X_L = j\omega L$$

$$[X_L = 20j]$$

Q) For the circuit; find the input impedance Z_{in} at 10 rad/sec .


Converting into phasor form

$$50 \Omega$$

$$2 \text{ mH}$$

$$1 \text{ A F}$$

$$V_o$$

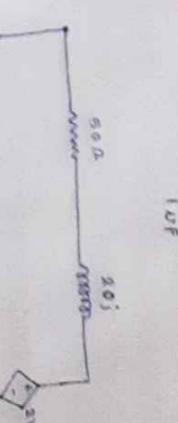

By the KVL;

$$-\sqrt{a} + 50(\frac{1}{2}) + 20j(\frac{1}{2}) + 2 + (-100j)(t) = 0$$

$$-\sqrt{a} + 50(0.5) + 20j(0.5) + 2 - 100j = \sqrt{a}$$

$$50 + 20j + 2 - 100j = \sqrt{a}$$

$$\sqrt{a} = 52 - 80j$$

Thus, the Input Impedance will be;

$$Z_o = \frac{52 - 80j}{1}$$

$$[Z_o = 52 - 80j]$$

Resonant Circuit :-

- It describes circuit condition in which Inductive and capacitive effect neutralized to each other.
- Impedance of circuit will be Resistive.
- Power factor will be unit.

Input voltage and Input current will be in same phase.

Resonance describes the energy transformation b/w Inductor and capacitor at a some frequency i.e. Resonance frequency

According to the impedance

$$V = \sqrt{R + j(X_L - X_C)}$$

$$Z = R + j(X_L - X_C)$$

By Resonance condition

$$\text{Im}[V] = 0$$

$$V_L - V_C = 0$$

$$V_L = V_C \quad [V = IR]$$

$$IX_L = IC$$



$$\boxed{X_L = X_C}$$

for the Resonance frequency:

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 = \frac{1}{LC} \Rightarrow \frac{1}{\sqrt{LC}}$$
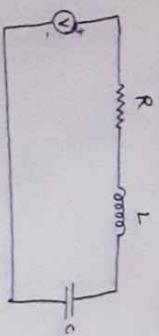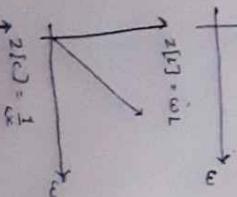
$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}}$$



Note: Shows RLC Resonant circuit also referred as acceptance circuit because it accepts maximum current in Resonance.

Parallel RLC Resonance Circuit :-

$$I = IR + j(I_C - I_L)$$

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$Y = \frac{1}{R} + j \left[\omega C - \frac{1}{\omega L} \right]$$

Condition of Resonance:


$$\text{Im}[Y] = 0 \quad \text{or} \quad \text{Re}[Y] = 0$$

$$\omega_0 - \frac{1}{\omega L} = 0$$


$$\omega_0 = \frac{1}{\omega L}$$

$$\omega_0^2 = \frac{1}{LC}$$
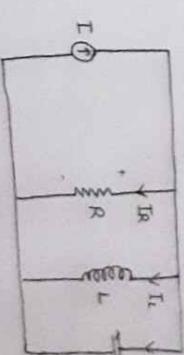
$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}}$$



ω_0	$R/L/C$	P/F
$\omega < \omega_0$	L	Leading
$\omega > \omega_0$	C	Lagging

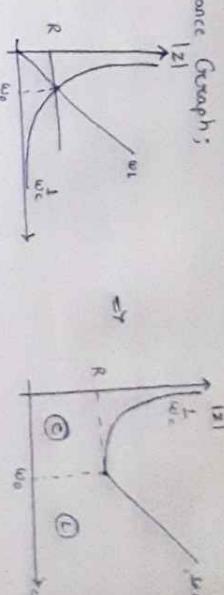

Resonance Graph;

Filter Synthesis :-

Filter network are widely used in communication systems to separate various voice channels in carrier frequency telephone circuits.

It is necessary to transmit a limited range of frequency.

Active filters are widely used in place of passive filters.
Inductors cannot be fabricated with high Quality I.C.
Resistance capacitance circuit can't device ~~useless~~ active replace the conventional LC filter.

Parameter of a Filter :-

Parameter characterize a typical filter.

Characteristic Impedance Z_{C0} or Z_0 :-

Impedance of a filter must be chosen

i.e. the filter fit \rightarrow given line and below two types

Pass Band :-

Band in which \Rightarrow ideal filters have to pass all frequencies without any reduction in magnitude.

Stop Band :-

Band in which \Rightarrow ideal filters have to stop the frequencies.

Cut-off frequency :-

The frequency which separates the Pass Band and Stop Band.

Unit of Attenuation :-

The attenuation of wave filter can be expressed as decibel or Neper or Bel.

f_{c1} = lower cut off frequency
 f_{c2} = upper cut off frequency

Similarly, V_o , I_o , P_o referred as output Voltage, output current and output power respectively.

Then $\frac{V_o}{V_i}$ will represent the voltage gain and $\frac{P_o}{P_i}$ represents as the power gain. If $P_i > P_o$ so that $\frac{P_i}{P_o}$ is given by attenuation.

Classification of Filters :-

The filter have any number of pass bands that is separated by the attenuation bands.

Low pass filter:-

Filters reject the all frequencies which is above the cut-off frequency.

The pass band for low pass filter range from 0 to f_c and

The stop band for low pass filter range from above f_c .

Pass band \rightarrow transmission band
Stop band \rightarrow attenuation band

High Pass Filter:-

Filter reject the all frequencies which is below the cut-off frequency.


The pass band of the high pass filter is above the f_c

The stop band of the high pass filter is below the f_c

Band Pass Filter:-

This filter allows the transmission of all frequencies b/w two designated cut-off frequencies but rejects all the other frequency.

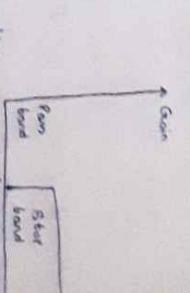A band pass filter has two cut-off frequencies and draw the pass band



$$f_{c1} = \text{lower cut off frequency}$$

$$f_{c2} = \text{upper cut off frequency}$$


$$f_c = \text{center cut off frequency}$$

$$f_c = \text{center cut off frequency}$$


Y Band Stop or Band Elimination :-

This filter passes all frequencies lying outside the range. It attenuate all frequencies between the two frequencies f_{c_1} and f_{c_2} .


Gain (G_b)

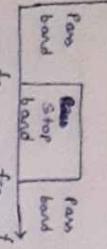

Block Representation :-

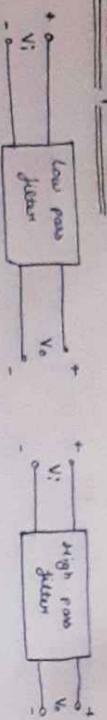

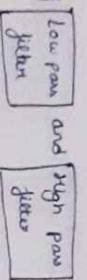Band Pass filter \rightarrow series connection of **Low pass filter** and **High pass filter**



Cut-off frequency of high pass filter f_{c_1} is less than the cut-off frequency of low pass filter f_{c_2}


$$[f_{c_1} < f_{c_2}]$$

Band pass filter \rightarrow parallel connection of **Low pass filter** and **High pass filter**


$$Z_1 \cdot Z_2 = k^2$$

Cut-off frequency of high pass filter f_{c_1} is greater than the cut-off frequency of low pass filter

$$[f_{c_1} > f_{c_2}]$$

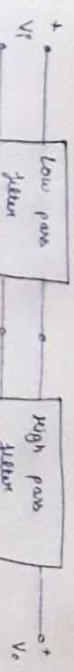

BP = L * P * R * P

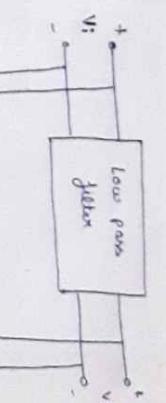

$$BS = L * P * R * P$$

Band Stop Filter

Passive Filters
It is classified as:

i) Constant-K or Prototype Filters :-

A network is said to be constant-k type if the series impedance Z_1 and the shunt impedance Z_2 satisfy the relation

$$Z_1 \cdot Z_2 = k^2$$

$k \Rightarrow$ real constant { independent of frequency }
i.e. Resistance

$$\Rightarrow Z_1 \cdot Z_2 = k^2 = R_0^2$$

The constant-k type is known as the prototype because other more complex network can be derive from it.



ii) Modified Filters :- In this filter $Z_1, Z_2 \neq k^2$. Some characteristic impedance as the corresponding constant k and have much sharper attenuation characteristic.

Filter Networks :-

Ideal Filter have zero attenuation in the pass band.
when the element of filter are dissipation less [loss section]


Filter made symmetrical \rightarrow T and π networks

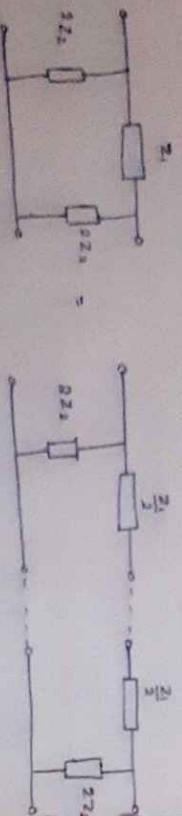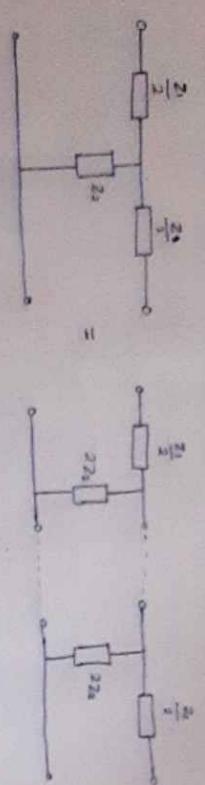Both T and π network can be considered as combinations of unbalanced T or π networks.



Characteristics of Filter Network :-

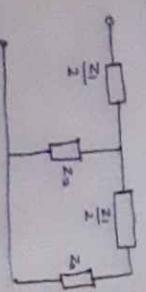1) Characteristic Impedance (Z_0) -
When image impedance at input port and output port are equal to each other. The image impedance is called the characteristic impedance Z_0 .



$$\text{Ans} \quad Z_{0r} = \sqrt{\frac{2Z_1}{2Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}} \quad (\text{r networks})$$

$$Z_{0r} Z_{0m} = Z_1 Z_2 = k^2 = R_s^2$$

Propagation Constant :-

Propagation constant γ is the same for both T and π -networks given by;

$$\cosh Y = \frac{1 + \frac{Z_1}{2Z_2}}{1 - \frac{Z_1}{2Z_2}}$$

3) Attenuation Constant :-

$$\alpha = 0 \quad (\text{pass band})$$

$$\alpha = 2 \cosh^{-1} \sqrt{\left| \frac{Z_1}{4Z_2} \right|} \quad (\text{stop band})$$

4) Phase constant :-

$$\beta = 2 \sin^{-1} \sqrt{\left| \frac{Z_1}{4Z_2} \right|} \quad (\text{pass band})$$


$$\beta = n\pi; n = 0, 1, 2, \dots \quad (\text{stop band})$$

5) Cut-off frequency :-

$$Z_1 = 0$$

$$\text{and } Z_1 + 4Z_2 = 0$$

Constant K Low Pass Filter :-

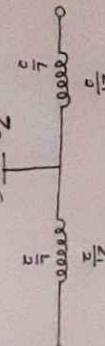

T-network

For T and π network:

Given Impedance $Z_1 = j\omega L$ and shunt impedance $Z_0 = \frac{1}{j\omega C}$, then

$$Z_1 Z_2 = K^2 = R_0^2$$

$$j\omega L \times \frac{1}{j\omega C} = R_0^2$$

$$R_0^2 = \frac{L}{C}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

At cut-off frequency :-

The cut-off frequency are given by;



$$Z_1 = 0 \text{ and } j\omega L = 0, \omega_c = 0, f_c = 0$$

By the cut-off frequency $Z_1 + 4Z_2 = 0$

$$j\omega_c L + 4 \times \frac{1}{j\omega_c C} = 0 \Rightarrow j\omega_c L = -\frac{4}{j\omega_c C}$$

$$\omega_c^2 = -\frac{4}{LC}$$

$$\omega_c = \sqrt{\frac{2}{LC}}$$

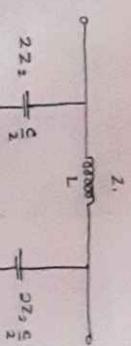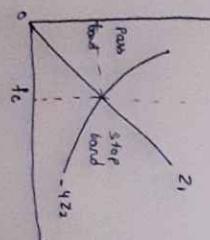

π-network

$$\text{In pass band: } \alpha = 2 \cos h^{-1} \left[\sqrt{\frac{Z_1}{4Z_2}} \right]$$

$$\text{In stop band: } \alpha = 2 \cos h^{-1} \left(\frac{f}{f_c} \right)$$

Phase constant :- [Pass Band]

$$\text{In stop band: } \beta = \pi$$

$$\text{and pass band: } \beta = 2 \sin^{-1} \sqrt{\frac{Z_1}{4Z_2}}$$

$$Z_1 = j\omega_c L$$

$$Z_2 = \frac{1}{j\omega_c C}$$

Characteristic Impedance :-

$$Z_1 = j\omega_c L \text{ and } Z_2 = \frac{1}{j\omega_c C}$$

$$Z_{01} = j\omega_c L \times \frac{1}{j\omega_c C} \left[1 + \frac{j\omega_c L}{4j\omega_c C} \right]$$

$$Z_{01} = \sqrt{\frac{1}{C} \left[1 + \frac{(\omega_c^2 LC)^2}{4} \right]} \Rightarrow \sqrt{\frac{L}{C} \left[1 - \frac{\omega_c^2 LC}{4} \right]} = \sqrt{\frac{L}{C} \left[1 - \left(\frac{f}{f_c}\right)^2 \right]}$$


$$Z_{01} = R_0 \sqrt{1 + \left(\frac{f}{f_c}\right)^2}$$

$$Z_{01} = \sqrt{\frac{2jZ_2}{\left(1 + \frac{Z_1}{4Z_2}\right)}} \Rightarrow \sqrt{\frac{j\omega_c L \times \frac{1}{j\omega_c C}}{\left(1 + \frac{j\omega_c L}{4j\omega_c C}\right)}} \Rightarrow \sqrt{\frac{L}{C} \left[1 + \left(\frac{f}{f_c}\right)^2 \right]}$$

$$\alpha = 2 \sin^{-1} \left(\frac{f}{f_c} \right)$$

$$Z_{01} = \sqrt{\frac{R_0}{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$\omega_c = \sqrt{\frac{1}{LC}}$$

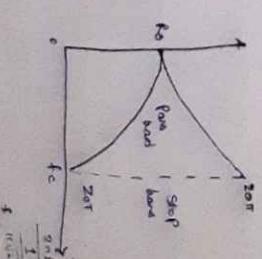

The constant K pass band The pass band of constant K low pass filter extends from 0 to $\frac{1}{\omega_c^2 LC}$

Q) Design a high pass filter (both π and T) drawing a cut-off frequency of 2 kHz with load resistance 3000 Ω .

$$\text{Given } f_c = 2000 \text{ Hz} \quad \text{and} \quad R_o = k = 3000 \Omega$$


We know that;

$$L = \frac{k}{4\pi f_c} = \frac{3000}{4\pi \times 2000 \times 10^3} = 0.0119$$

$$\boxed{L = 11.94 \text{ mH}}$$

$$C = \frac{1}{4\pi k f_c} \Rightarrow \frac{1}{4 \times 3.14 \times 3000 \times 2000} = 0.01326 \text{ F}$$

Thus, the T and π network will be;

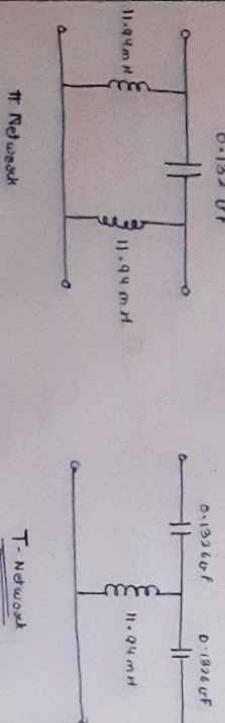

π Network

T -Network

Series capacitance: $C = \frac{1}{4\pi f_c k}$

$$C = \frac{1}{4\pi \times 3.14 \times 8000 \times 600} \Rightarrow 1.658 \times 10^{-9}$$

$$\boxed{C = 0.01658 \mu\text{F}}$$

The value of components will be;

$$\partial L = 11.94 \text{ mH}$$

$$C = 0.0166 \text{ F}$$

Characteristic Impedance; at $f = 10 \text{ kHz}$

$$Z_{on} = \sqrt{\frac{R_o}{1 - \left(\frac{f_c}{f}\right)^2}} \Rightarrow \sqrt{1 - \left(\frac{600}{10^4}\right)^2}$$

$$\boxed{Z_{on} = 805 \Omega} \text{ at } 10 \text{ kHz}$$

Characteristic Impedance; at $f = 0.8 \text{ kHz}$

$$Z_{an} = \sqrt{\frac{600}{1 - \left(\frac{8}{800}\right)^2}} \Rightarrow \boxed{Z_{an} = 603 \Omega} \text{ at } 0.8 \text{ kHz}$$

Phase constant at $f = 12000 \text{ Hz}$

$$\beta = 2 \sin^{-1} \left(\frac{f_c}{f} \right)$$

$$\beta = 2 \sin^{-1} \left(\frac{8000}{12000} \right) \Rightarrow 2 \sin^{-1} \left(\frac{2}{3} \right)$$

$$\boxed{\beta = 83.6^\circ}$$

Attenuation constant at $f = 800 \text{ Hz}$ (0.8 kHz)

Now,


$$\text{Shunt Inductance: } L = \frac{k}{4\pi f_c} \Rightarrow \frac{600}{4 \times 3.14 \times 8000} \Rightarrow 5.971 \times 10^{-3} \text{ H}$$

$$\boxed{L = 5.971 \text{ mH}}$$

$$\begin{aligned} \alpha &= \frac{2}{Z_{on}} \\ \alpha &= 2 \tan^{-1} \left(\frac{f_c}{f} \right) \\ \alpha &= 2 \tan^{-1} \left(\frac{8000}{800} \right) \Rightarrow 2 \tan^{-1} (10) \end{aligned}$$

$$\boxed{\alpha = 5.99 \text{ nepers}}$$

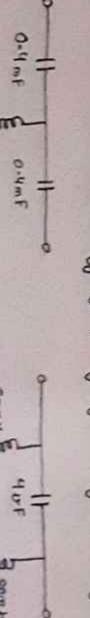Q) Determine the cut-off frequency for high pass filter:




T network

Now For the T Network;

$$2C = 0.4 \text{ mF} \Rightarrow C = 0.2 \text{ mF}$$


$$L = 18 \text{ mH}$$

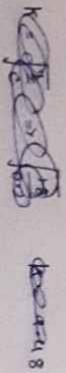

T-network

$$\# \text{ Constant } K \text{ Band Pass Filter} :-$$
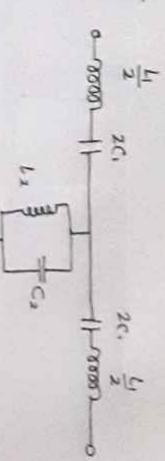
$$R_o = \sqrt{\frac{L_2}{C_1}} = \sqrt{\frac{L_1}{C_2}}$$



$$Z_1 + 4Z_2 = 0$$

$$Z_1 = -4Z_2$$

The cut-off frequency will be :

$$f_o = \sqrt{f_{c1} f_{c2}}$$

ii) Find component values :-

$$C_1 = \frac{f_{c1} - f_{c2}}{4\pi R_o f_{c1} f_{c2}}$$

$$L_1 = \frac{R_o}{\pi(f_{c1} - f_{c2})}$$

$$L_2 = \frac{(f_{c2} - f_{c1}) R_o}{4\pi f_{c1} f_{c2}}$$

$$C_2 = \frac{1}{4\pi R_o (f_{c1} - f_{c2})}$$

Q) Design a constant K band pass filter with cut-off frequencies of 3 kHz and 7.5 kHz and characteristic impedance $R_o = 900 \Omega$.

Given : $R_o = 900 \Omega$, $f_{c1} = 3 \text{ kHz}$ and $f_{c2} = 7.5 \text{ kHz}$

$$L_1 = \frac{R_o}{\pi(f_{c2} - f_{c1})} \Rightarrow \frac{900}{3.14(7.5 - 3)} \Rightarrow 63.66 \text{ mH}$$

For the T network;

$$2L = 80 \times 10^{-3} \quad C = 4 \text{ mF}$$

$$L = 40 \times 10^{-3} \text{ H} \quad C = 4 \times 10^{-6} \text{ F}$$

$$\text{Cut-off frequency} \quad f_c = \frac{1}{4\pi \sqrt{LC}} \Rightarrow \frac{1}{4\pi \sqrt{3.14 \times 40 \times 10^{-3} \times 4 \times 10^{-6}}} \text{ Hz}$$

$$f_c = 199.04 \text{ Hz}$$


$$f_c = 199.04 \text{ Hz}$$

$$C_1 = \frac{f_{c2} - f_{c1}}{4\pi R_o f_{c1} f_{c2}} \Rightarrow \frac{4.5}{3.14 \times 4 \times 900 \times 7.5 \times 3} \Rightarrow 0.017 \text{ uF}$$

$$L_2 = \frac{(f_{c2} - f_{c1}) R_o}{4\pi f_{c1} f_{c2}} \Rightarrow \frac{4.5 \times 900}{4 \times 3.14 \times 7.5 \times 3} \Rightarrow 14.33 \text{ mH}$$

$$C_2 = \frac{1}{\pi R_o (f_{c2} - f_{c1})} \Rightarrow \frac{1}{3.14 \times 900 \times 84.5} \Rightarrow 0.078 \text{ uF}$$
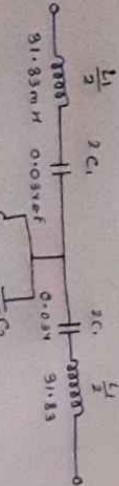
$$\text{Hence, } \frac{L_1}{2} = 31.83 \text{ mH and } 2C_1 \Rightarrow 0.034 \text{ uF}$$



Limitations of Passive Filters :-

Passive Filter have may & limitations are as follows:-

1) The use of inductors in filter element is not desirable at low frequencies ($< 1 \text{ kHz}$)

In these frequencies pure practical inductors of reasonable & tends to costly, Bulky, large, heavy.

2) High range of & factors is not possible.

or need of an external amplifier to provide suitable \Rightarrow gain.

3) Cascade many sections to give a composite filter cascading different sections of filter \rightarrow bigger and no isolation amplifier is required to power the load of circuit.


due to above limitation the passive filter became obsolete.

Graph Theory :-
Graph is obtained from arbitrary circuit replacing with open circuit and short circuit

Passive Elements and Independent Voltage source \rightarrow short circuit


Independent current source \rightarrow open circuit

unloaded

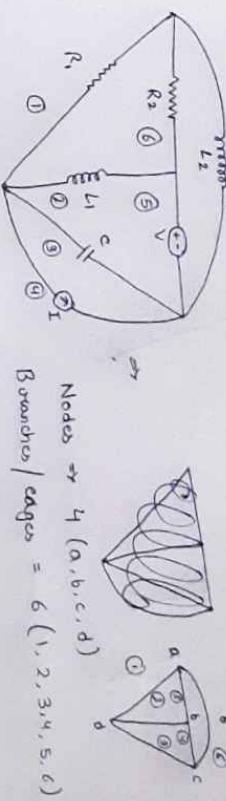

Graph is defined as collection nodes and Branches or vertices and edges.

Directed Graph:-

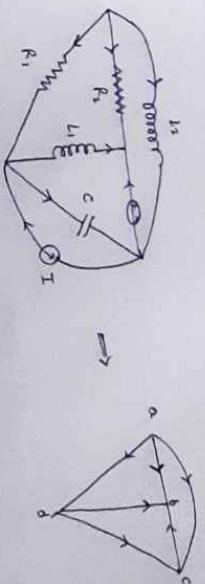

4) Rank of Graph = $n - 1$ [n = no of nodes]

5) Degree of node :-
[no of incoming branches across any node]

$$\begin{cases} D[a] = 0 \\ D[b] = 2 \\ D[c] = 2 \\ D[d] = 1 \end{cases} \Rightarrow 2 + 2 + 1 = 5$$

6) Complete Graph :-
only one line segment from every one node pair



Node pairs = ab, bc, cd, bd, ad, ac

No of Branches [complete graph] $\Rightarrow n^2 - \frac{n(n-1)}{2}$

No of Branches = $\frac{n(n-1)}{2}$


Connected Graph

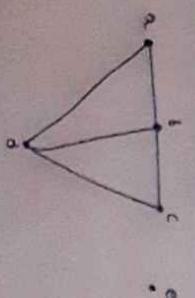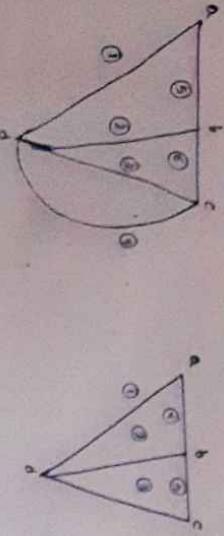In connected all node pair contains atleast one branch
Should be connected



Net Connected Graph

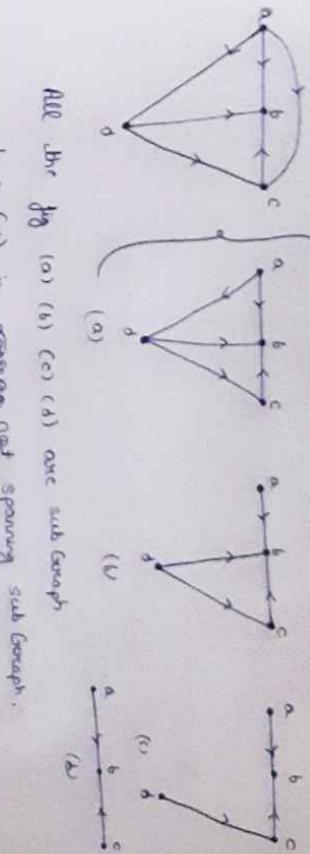In unconnected Graph all node pair contains atleast one branch
Should be connected but there will be one isolated node



All the fig (a) (b) (c) (d) are sub graph
but (e) is spanning net spanning sub graph.

Trees & Co-Trees

Trees is connected subgraph which contains all nodes without forming any closed loop
Tow is also a spanning subgraph, without forming closed loop.

Tow Branch \Rightarrow Twigs $(n-1)$ [Present Tow Branches]

Awest Tow Branch \Rightarrow Links / chords = 1

Total no of branches in graph = $T_{\text{W}} + L$

$$B_T = n-1 + l$$

$$l = B_T - n + 1$$

Spanning Tree :-

Rank of Tow = $n-1$

For Complete Graph :-

\rightarrow It contains less number of branch from other branch
 \rightarrow complete graph

Number of node pair voltage = $\frac{n(n-1)}{2}$

for both complete and incomplete graph

Sub Graph

It contains less number of branch from other branch.

Spanning Sub Graph :-

It contains all the real basic nodes of original Graph

Sub Graph

It contains less number of branch from other branch.


Tree Branch \Rightarrow Twigs } no closed loop
Co Tree Branch \Rightarrow Links }

But co Tree Branch cannot closed loop.

Notes

$$\text{no of Tree Branch} = \text{no of co Tree Branch in complete Tree} = f(n-1)$$

Q) Find the number of chords;

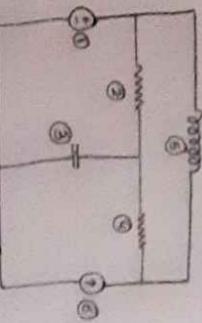


no of nodes = 6

no of Branches = 5

Twigs = $n-1 = 6-1 = 5$

$$\begin{aligned}\text{no of chords / link} &= B - n + 1 \\ &= 5 - 6 + 1\end{aligned}$$

$\Rightarrow 2$

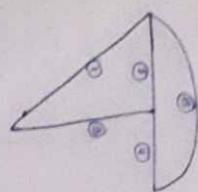

Incidence Matrix :- [Complete Incidence Matrix]
Incidence Matrix describes the information regarding incoming and outgoing Branches across any graph.



Rank :-

$$\boxed{\text{Rank [IM]} = \text{Rank [Graph]} = \text{Rank [Tree]} = n-1}$$

Incidence Matrix = $[A]_{n \times B}$

$n = \text{No of nodes} = \text{no of node}$

$B = \text{column} = \text{no of Branch}$

$$A = \begin{bmatrix} a & 1 & 2 & 3 & 4 & 5 & 6 \\ b & -1 & -1 & -1 & 0 & 0 & 0 \\ c & 0 & 0 & 1 & 0 & -1 & -1 \\ d & 0 & 1 & 0 & -1 & 1 & 0 \\ e & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}_{4 \times 6}$$

$$\left\{ \begin{array}{l} \text{Outgoing} = 1 \\ \text{Incoming} = -1 \end{array} \right\}$$

The Algebraic sum of column = 0 } (Join all column Matrix)

Reduced Incidence Matrix :-

$$[R]_{n \times B}$$

$a \quad 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6$

$$[A] = \boxed{0} \quad \left\{ \begin{array}{l} \text{Singular Matrix} \\ \text{Rank Reduced Incidence Matrix} \end{array} \right\}$$

$$[R]_{n-1 \times B}$$

$a \quad 1 \quad 0 \quad 0 \quad 1 \quad 0 \quad 1$

$b \quad -1 \quad -1 \quad -1 \quad 0 \quad 0 \quad 0$

$c \quad 0 \quad 0 \quad 1 \quad 0 \quad -1 \quad 0$

TJ The Algebraic sum of column is not 0
Then Reduced Incidence Matrix

$$\boxed{\text{No of trees} = \det [R \cdot R^T]}$$

Q) Find the no of possible tree by Reduce Tridiagonal Matrix.

$$[R] = \begin{bmatrix} 1 & 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 & 0 \\ -1 & 0 & -1 & -1 & 0 \end{bmatrix}$$

$$[R^T] = \begin{bmatrix} 1 & 0 & -1 \\ -1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$[R \cdot R^T] = \begin{bmatrix} 3 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

-1 + 0 + 1 = 0


$$\det |R \cdot R^T| = 3(6-1) - (-1)[-3-1] + (-1)[1-(-2)]$$

$$= 15 - 4 - 3$$

$$\therefore \underline{\underline{8}}$$

Rank

-

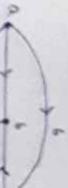

$$\boxed{\text{Rank } [\text{Tie-Set}] = B-n+1}$$

$$[\tau]_{1,8}$$

$$\boxed{\text{No of fundamental loop current} = d = B-n+1}$$

$$\det \text{link } L = T_1, T_2, T_3$$

$$B = 6 \\ n = 4 \\ \text{link} = 6-4+1 \Rightarrow 3$$

$$A = \begin{bmatrix} T_1 & -1 & 1 & 0 & 1 & 0 \\ T_2 & 0 & -1 & 1 & 0 & 0 \\ T_3 & -1 & 0 & -1 & 0 & 0 \\ T_4 & 0 & 1 & 0 & 1 & 0 \\ T_5 & 1 & 0 & 1 & 0 & 1 \\ T_6 & 0 & 1 & 0 & 1 & 0 \end{bmatrix}$$



$$\text{Branch Current} = j_1, j_2, j_3, j_4, j_5, j_6$$

In tie set matrix we determine Branch current in terms of loop current.

$$\bar{J}_1 = -I_1 - I_3 \quad \bar{J}_4 = I_1$$

$$\bar{J}_2 = I_1 - I_2 \quad \bar{J}_5 = I_2$$

$$\bar{J}_3 = I_2 - I_3 \quad \bar{J}_6 = I_3$$

$$\boxed{\text{No of KVL} = \text{No of lines} = \text{No of Fundamental loop current}} \\ \therefore B-n+1$$


$$\left. \begin{aligned} J_1 &= -V_1 + V_2 + V_4 \\ J_2 &= -V_2 + V_3 + V_5 \\ J_3 &= -V_1 - V_3 + V_6 \end{aligned} \right\} \text{KVL equation}$$

$$\boxed{\text{Tie-Set Matrix / Fundamental Loop Matrix}}$$

Tie-Set Matrix is a Link dependent Matrix

Cut-Set Matrix :-

It is tangle dependent Matrix :-

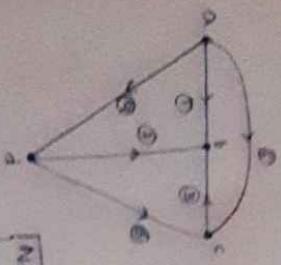

$$\text{No. of cut-set Matrix} = T = n-1$$

$$\text{Rank [cut-set]} = n-1$$

$$T = 4n - 3 \quad [C_1, C_2, C_3]$$

in form complete graph

one cut set can only contain one Tangle

$$\text{order of cut-set Matrix} = [C^H]_{n, b}$$



$$[C]_{n, b} = C_1 \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & -1 \\ 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 0 & 1 \\ 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 \end{bmatrix}$$

To cut set Matrix we determine branch voltage in terms of induced voltage.






$$\begin{aligned} V_1 &= E_1 & V_2 &= E_2 - I_2 R_2 \\ V_3 &= E_2 & V_4 &= E_2 - E_3 \\ V_5 &= E_2 + E_3 & V_6 &= E_1 - E_2 \end{aligned}$$

$$\text{No. of KCL equation} = \text{No. of Tangles} = n-1$$

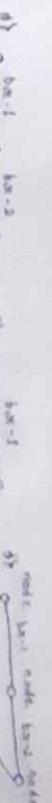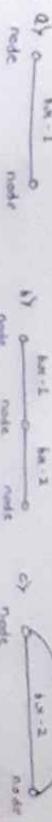Q) Draw the node and branch of the network:



Q) Draw the graph of the Network:

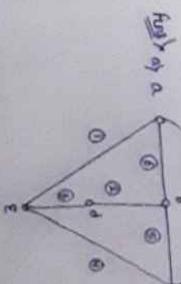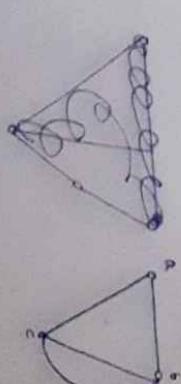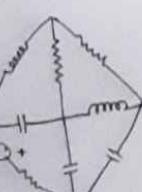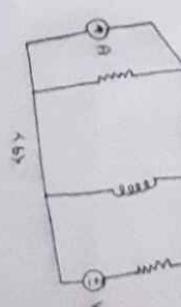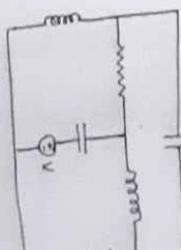

Tree (Trunks)

Links

(1, 2, 4)

(5, 3)

(2, 1, 6)

(4, 3)

(1, 2, 3)

(5, 4)

(1, 2)

(4, 5, 3)

(1, 4, 3)



(2, 3, 5)

(1, 3, 5)

(2, 4, 5)

(1, 4, 3)

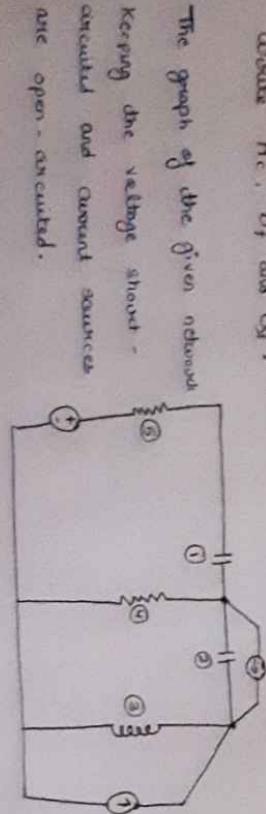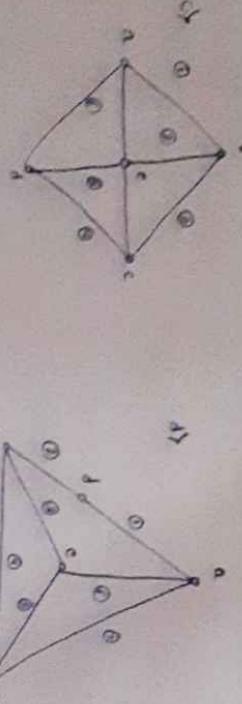- Q) For the Given Network:
 Determine all the tree and co-tree for the graph of network
 Consider the tree formed by the branches (1, 2, 5)
 choose A₁, B₁ and C₁.




The graph of the given network
 Keeping the voltage source -
 connected and constant sources
 are open - arcuated.

$$\text{no. of loops} = 0 - 1 = 4 - 1 = 3$$

$$\text{no. of links} = b - n + 1 = 5 - 4 + 1 = 2$$

No of Possible Trees could be;

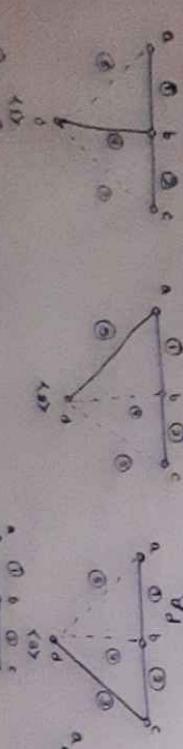

$$\text{Reduced Incidence Matrix:}$$

$$[A] = \begin{bmatrix} a & 1 & 0 & 0 & 1 \\ b & -1 & 1 & 0 & 0 \\ c & 0 & -1 & 1 & 0 \\ d & 0 & 0 & -1 & -1 \end{bmatrix}$$

$$[A_e] = A = \begin{bmatrix} a & 1 & 0 & 0 & 1 \\ b & -1 & 1 & 0 & 0 \\ c & 0 & -1 & 1 & 0 \\ d & 0 & 0 & -1 & -1 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 2 & 5 & 1 & 3 & 4 \\ 1 & 0 & 1 & 1 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$\text{Now form The Set Matrix:}$$


$$\text{no. of Tie-set} = b - n + 1 = 5 - 4 + 1 = 2$$

$$\text{Tie-set } (3, 4), \quad B_{\text{set}} = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \end{bmatrix}$$

$$[B_1] = \begin{bmatrix} 3 & 1 & 1 & 0 & -1 \\ 1 & 0 & 0 & 1 & -1 \end{bmatrix}$$

$$\text{for the Branch } (1, 2, 5):$$
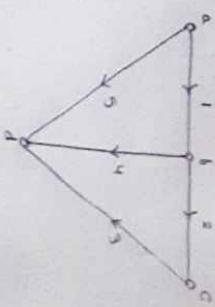
$$[B_4] = \begin{bmatrix} 3 & 1 & 1 & -1 & 0 \\ 4 & 1 & 0 & -1 & 0 \end{bmatrix}$$




Find cut-set Matrix :-

$$\text{No of cut-set} = n-1 = 4-1 = 3$$

Cut Set : 1 , Cut Set : 2 , Cut Set : 3
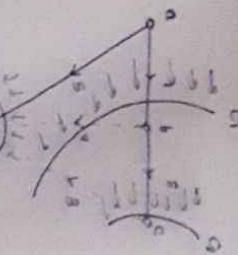
$$[S] = \begin{bmatrix} 1 & 1 & 2 & 5 & 3 & 4 \\ 2 & 0 & 0 & -1 & -1 & \\ 3 & 0 & 1 & 0 & -1 & 0 \\ 4 & 0 & 0 & 1 & 1 & \\ 5 & 0 & 0 & 1 & 1 & \\ \end{bmatrix}$$




Q) Find the given graph; consider the tree branch (2,3,4)

Determine A, B_f, and S_f?

Ans from the Given Graph;

Incidence Matrix for complete Graph;
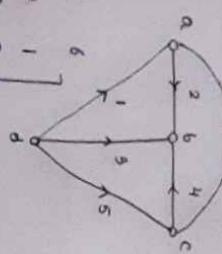
$$A_c = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 2 & 0 & -1 & -1 & -1 & 0 \\ 3 & 0 & 0 & 0 & 1 & -1 \\ 4 & 0 & 1 & 0 & 1 & 0 \\ 5 & 0 & 0 & 1 & 0 & 0 \\ 6 & 0 & 1 & 0 & 0 & 1 \end{bmatrix}$$



Reduced Incidence Matrix eliminating any Row;

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & -1 \\ 0 & 0 & 0 & 1 & -1 & -1 \end{bmatrix}$$

for the branch 2 3 4


$$B_f = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 2 & 0 & 0 & -1 & 0 & 1 \\ 3 & 1 & 0 & 1 & 0 & 0 \\ 4 & 0 & 0 & 0 & 1 & -1 \\ 5 & 0 & 0 & 1 & -1 & -1 \\ 6 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

Find the Tie-Set Matrix [B_f];

$$\Rightarrow 6 - 4 + 1 = 3$$

Tie set will be 1, 5, 6
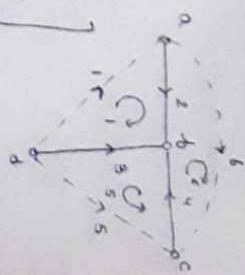
$$B_f = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 0 & 0 & 0 & 0 & 0 \\ 5 & 0 & -1 & 1 & 0 & 0 \\ 6 & -1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \end{bmatrix}$$



for the branch 2 3 4 will be

$$B_f = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 2 & -1 & 1 & 0 & 0 & 1 \\ 3 & 1 & 0 & 1 & 0 & 0 \\ 4 & 0 & 0 & 0 & 1 & -1 \\ 5 & 0 & 0 & 1 & -1 & -1 \end{bmatrix}$$

Find the Cut Set Matrix [S_f];

$$\text{No of cut set} = n-1 = 4-1 = 3$$

Cut set and branch cut Twigs will be 2 4 3

$$S_f = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 2 & -1 & 1 & 0 & 0 & 1 \\ 3 & 1 & 0 & 1 & 0 & 0 \\ 4 & 0 & 0 & 0 & 1 & -1 \\ 5 & 0 & 0 & 1 & -1 & -1 \end{bmatrix}$$

for the branch (2,3,4)

$$B_f = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 1 & 0 & 0 & -1 & 0 & 1 \\ 3 & 0 & 1 & 0 & 1 & 0 \\ 4 & 0 & 0 & 1 & 0 & -1 \end{bmatrix}$$

Relation between B_{4t} and δ_{4t} :

We know: $B_{4t} = -A_{4t} A_{4t}' \quad \text{---(1)}$

$$\delta_{4t} = -A_t' A_t \quad \text{---(2)}$$

from the above eq (1) and (2)


$$-B_{4t}' = \delta_{4t}$$

or

$$B_{4t} = -\delta_{4t}'$$

Two point Networks :-
 Current entering or incoming \rightarrow [equal and opposite] \rightarrow other terminal of the port
 from one terminal

Thus is called a port.

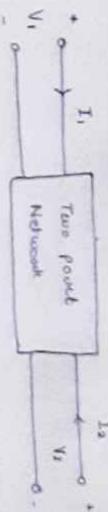

Two point Network consists four variables i.e. Two voltages (V_1, V_2) and Two current (I_1, I_2) which are available for measurements and relevant for the analysis of two point Networks.

Open Circuit Impedance (z) Parameters :-

Two point voltages in terms of two point current

$$[V_1, V_2] = f[I_1, I_2]$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = z[I]$$


Here, z is the open circuit impedance matrix and Z_{ij} are the open circuit impedance parameter

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11}I_1 + Z_{12}I_2 \\ Z_{21}I_1 + Z_{22}I_2 \end{bmatrix}$$

$$\text{Thus, } V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Here, Z_{11}, Z_{12} and Z_{21}, Z_{22} are the current controlled source voltage

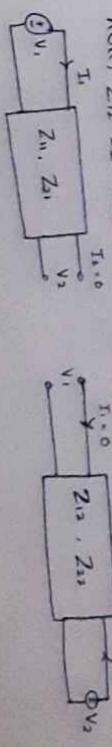

Case 1 :- Output port open circuited

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{T_2=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{T_2=0}$$

Case 2 :- Input port open circuited

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{T_1=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{T_1=0}$$

Short circuit Admittance (Y) parameter :-

Two port current in terms of Two port voltage

$$(I_1, I_2) = f(V_1, V_2)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[Y] = [Y_1][Y]$$



Here, Y is the short circuit Admittance matrix and Y_i are the short circuit Admittance parameters.

$$\begin{bmatrix} Y_1 \\ Y_2 \end{bmatrix} = \begin{bmatrix} Y_{11}V_1 + Y_{12}V_2 \\ Y_{21}V_1 + Y_{22}V_2 \end{bmatrix}$$

$$Y_1 = Y_{11}V_1 + Y_{12}V_2$$

$$Y_2 = Y_{21}V_1 + Y_{22}V_2$$

Determination of Y parameters -

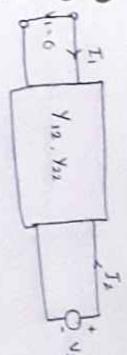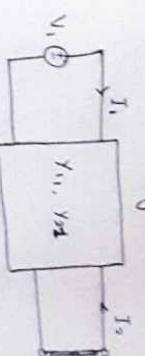

Case 1 :- when output short circuited


$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

Case 2 :- when Input port short circuited

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

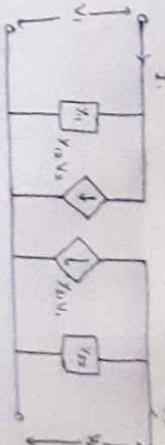

Transmission (T) or chain or ABCD Parameters

One port variable in terms of other port variables.


$$(V_1, I_1) = f(V_2, I_2)$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

T parameters are used in the analysis of power transmission line.


Input port \rightarrow sending end
output port \rightarrow receiving end
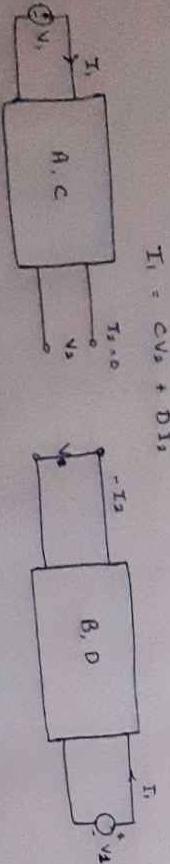
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A V_2 + B I_2 \\ C V_2 + D I_2 \end{bmatrix}$$




$$V_1 = A V_2 + B I_2$$

$$I_1 = C V_2 + D I_2$$

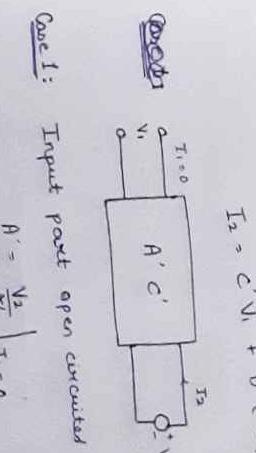

Case 1: Input port open circuited

$$A' = \frac{V_1}{V_2} \Big|_{I_1=0} \quad C' = \frac{I_1}{V_2} \Big|_{V_1=0}$$

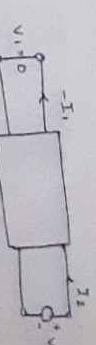

Case 2: Input port short circuited

$$B' = \frac{V_2}{V_1} \Big|_{I_1=0} \quad D' = \frac{I_2}{V_1} \Big|_{V_1=0}$$

Case 1: Output port open circuited;

$$A'' = \frac{V_1}{V_2} \Big|_{I_2=0} \quad C'' = \frac{I_1}{V_2} \Big|_{I_2=0}$$

Case 2: Output port short circuited;

$$B'' = \frac{V_1}{I_2} \Big|_{V_2=0} \quad D'' = \frac{I_1}{I_2} \Big|_{V_2=0}$$

Inverse Transmission (T') Parameters :-

Output port variable in terms of input port variable

$$(V_2, I_2) = f(V_1, -I_1)$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

where, A', B', C', D' is called as an inverse transmission parameter (T')

$$V_2 = A' V_1 + B' (-I_1)$$

$$I_2 = C' V_1 + D' (-I_1)$$

Hybrid (h) Parameters :-

The hybrid (h) parameters are wide usage in electronic circuits. Join modelling transistors.

Voltage input point and current output point in terms of voltage output point and current input point.

$$(V_1, I_2) = f(V_2, I_1)$$


$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ I_1 \end{bmatrix}$$

$$\begin{bmatrix} V_2 \\ I_1 \end{bmatrix} = \begin{bmatrix} h_{11} V_2 + h_{12} I_1 \\ h_{21} V_2 + h_{22} I_1 \end{bmatrix}$$


The matrix equation define h -parameters and h -parameters matrix known as hybrid matrix.

$$V_1 = h_{11}V_2 + h_{12}I_1 \quad h_{11}I_1 + h_{12}V_2$$
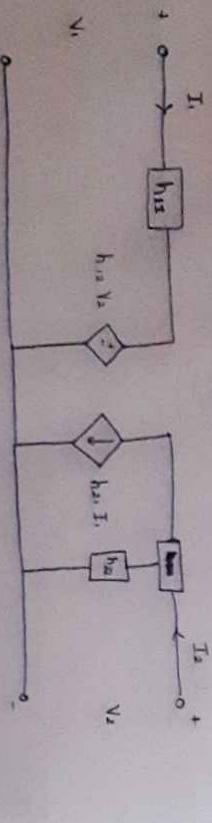
$$I_2 = h_{21}V_2 + h_{22}I_1 \quad h_{21}I_1 + h_{22}V_2$$



Determination of h parameters

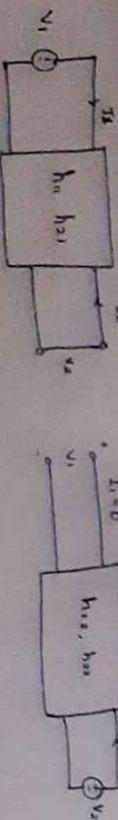

Case 1 :- output point short circuited

Case 2 :- input point open circuited

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad h_{12} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad h_{21} = \frac{V_2}{I_2} \Big|_{V_1=0} \quad h_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

Inverse hybrid (β) parameter
Hybrid parameter and inverse hybrid parameter are dual of each other.

$$[\beta] = [h]^{-1}$$


$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \beta_{11} & \beta_{12} \\ \beta_{21} & \beta_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \beta_{11}V_1 + \beta_{12}I_2 \\ \beta_{21}V_1 + \beta_{22}I_2 \end{bmatrix}$$

$$I_1 = \beta_{11}V_1 + \beta_{12}I_2$$

$$V_2 = \beta_{21}V_1 + \beta_{22}I_2$$

Determination of β - parameters :-

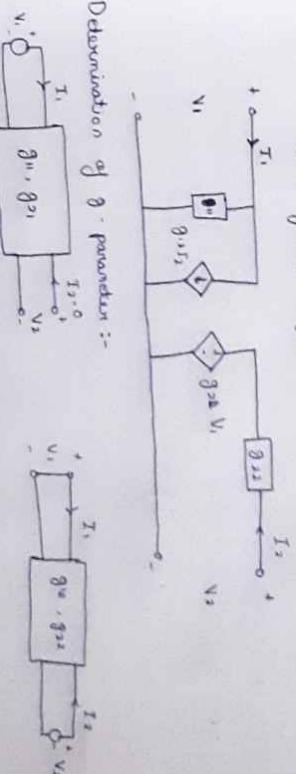

Case 1 :- output point open circuited

Case 2 :- input point short circuited

$$\beta_{11} = \frac{I_1}{V_1} \Big|_{I_2=0}$$


$$\beta_{12} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

$$\beta_{21} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

$$\beta_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

Conclusion from Symmetry :-

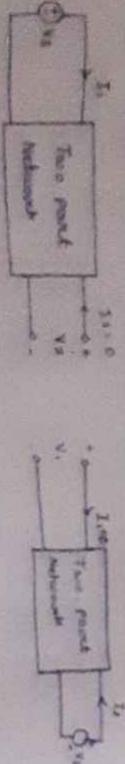Two port networks can said to be **Symmetric** if port can unchanged without changing the voltage and current pair.



\Rightarrow In terms of Z :

$$Z_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}, \quad Z_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

$$\boxed{Z_{11} = Z_{22}}$$

\Rightarrow In terms of Y :

$$Y_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}, \quad Y_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

$$\boxed{Y_{11} = Y_{22}}$$

\Rightarrow In terms of T parameter:

$$A = \frac{V_1}{I_1} \Big|_{V_2=0}, \quad D = \frac{V_2}{I_2} \Big|_{V_1=0}$$

$$\boxed{A = D}$$

\Rightarrow In terms of Γ parameter:

$$B = \frac{V_1}{I_2} \Big|_{V_2=0}, \quad D' = \frac{V_2}{I_1} \Big|_{V_1=0}$$

$$\boxed{B = D'}$$

\Rightarrow In terms of h parameter:

$$h_{11} = h_{22}, \quad h_{12} = h_{21}, \quad h_{11} \cdot h_{22} - h_{12} \cdot h_{21} = 1$$

or In terms of θ parameter:

$$\begin{bmatrix} \theta_{11} & \theta_{12} \\ \theta_{21} & \theta_{22} \end{bmatrix} = 1 \left\{ \theta_{11}\theta_{22} - \theta_{12}\theta_{21} = 1 \right\}$$

T-connection of Two port Network :-

1) Series Connection:-

$$(V_{10}, V_{20}) = f(T_{10}, T_{20})$$

$$\begin{bmatrix} V_{10} \\ V_{20} \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} T_{10} \\ T_{20} \end{bmatrix}$$

$$\text{Similarly for Network } N_2:$$

$$(V_{11}, V_{21}) = f(T_{11}, T_{21})$$

$$\begin{bmatrix} V_{11} \\ V_{21} \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} T_{11} \\ T_{21} \end{bmatrix}$$

(i.e.) Know that:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Then we get:


$$Z_{11} = Z_{12} + Z_{21}$$

$$Z_{21} = Z_{12} + Z_{22}$$

$$Z_{11} = Z_{21} + Z_{12}$$

$$Z_{21} = Z_{12} + Z_{22}$$

$$\boxed{[Z] = [z_0] + [z_1]}$$

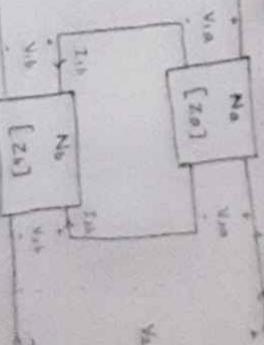

→ Parallel connection
→ Series connection
→ General Parallel
→ General Series
→ Series Parallel
→ Parallel Series

4) Parallel Generation :-

Current point in terms of voltage V_1 & I_2

$$(I_1, I_2) = f(V_1, V_2)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_1 & h_2 \\ h_3 & h_4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Similarly for Network No. 2;

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} r_1 & r_2 \\ r_3 & r_4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

By the 1 parameter nature we the parallel connection

$$[Y] = [h] + [r]$$

3) Cascade Connection :-



Input current and voltage in terms output current and voltage

$$(V_1, I_1) = f(V_2, -I_2)$$

Join Network No. :

$$\begin{bmatrix} V_{12} \\ I_{12} \end{bmatrix} = \begin{bmatrix} A_{12} & B_{12} \\ C_{12} & D_{12} \end{bmatrix} \begin{bmatrix} V_{12} \\ I_{12} \end{bmatrix}$$

By the 1 parameter nature in cascade connection

$$[M] = [T_{12}][r]$$

4) Series - Parallel Connection :-

$(V_1, I_2) = f(I_1, V_2)$

Join Network No. :

$$\begin{bmatrix} V_{12} \\ I_{12} \end{bmatrix} = \begin{bmatrix} h_{12} & h_{22} \\ h_{12} & h_{22} \end{bmatrix} \begin{bmatrix} I_{12} \\ V_{12} \end{bmatrix}$$

from Network No. 1;

$$\begin{bmatrix} V_{12} \\ I_{12} \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_{12} \\ V_{12} \end{bmatrix}$$

In nature from the 1 parameter of series parallel connection

$$[h] = [h_a] + [h_b]$$

5) Parallel Series Connection :-

~~(P.S.C)~~

$$(I_1, V_2) = f(V_1, I_2) \quad V_1$$

Join Network No. :

$$\begin{bmatrix} I_{12} \\ V_{12} \end{bmatrix} = \begin{bmatrix} g_{112} & g_{122} \\ g_{212} & g_{222} \end{bmatrix} \begin{bmatrix} V_{12} \\ I_{12} \end{bmatrix}$$

Join Network No. :

$$\begin{bmatrix} I_{12} \\ V_{12} \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_{12} \\ I_{12} \end{bmatrix}$$

In nature from the 1 parameter of parallel series connection

$$[g] = [g_1] + [g_2]$$

For the Network shown:

Calculate: $\text{v}_1 Z \rightarrow Y \rightarrow T \rightarrow T' \rightarrow h$ and $\text{v}_1 Z$ parameters

By the loop equation:

Applying the KVL:

$$\text{V}_1 = \text{T}_1 + 3(\text{T}_1 + \text{T}_2)$$

$$\text{O.H. } \text{V}_1 = 4\text{T}_1 + 3\text{T}_2 \quad (\text{eq. 1})$$

$$\text{V}_2 = 2\text{T}_2 + 3(\text{T}_1 + \text{T}_2)$$

$$\text{on. } \text{V}_2 = 3\text{T}_1 + 5\text{T}_2 \quad (\text{eq. 2})$$

\Rightarrow Z parameter will be:

$$Z_{11} = \frac{\text{V}_1}{\text{T}_1} \Big|_{\text{T}_2=0} \Rightarrow \frac{4\text{T}_1}{\text{T}_1} = 4\Omega$$

$$\text{Z}_{12} = 4\Omega$$

$$Z_{21} = \frac{\text{V}_2}{\text{T}_1} \Big|_{\text{T}_2=0} \Rightarrow \frac{3\text{T}_2}{\text{T}_1} = 3\Omega$$

$$Z_{22} = \frac{\text{V}_2}{\text{T}_2} \Big|_{\text{T}_1=0} \Rightarrow \frac{3\text{T}_2}{\text{T}_2} = 3\Omega$$

$$Z_{12} = \frac{\text{V}_2}{\text{T}_1} \Big|_{\text{T}_2=0} \Rightarrow \frac{5\text{T}_2}{\text{T}_1} \Rightarrow 5\Omega$$

$$\boxed{\text{Z}_{11} = 4\Omega} \quad \boxed{\text{Z}_{21} = 3\Omega} \quad \boxed{\text{Z}_{12} = 3\Omega} \quad \boxed{\text{Z}_{22} = 5\Omega}$$

\Rightarrow Y parameter will be:

from the eq.(1) and eq.(2) converting into terms of current

$$4\text{T}_1 = \text{V}_1 - 3\text{T}_2$$

$$\text{T}_1 = \frac{\text{V}_1}{4} - \frac{3}{4}\text{T}_2 \quad (\text{eq. 3})$$

~~$$\text{V}_2 = 3\text{T}_1 + 5\text{T}_2$$~~

$$\text{T}_2 = \frac{\text{V}_2}{5} - \frac{3}{5}\text{T}_1 \quad (\text{eq. 4})$$

Case 1 :- when $\text{V}_2 = 0$ from eq(1) and eq(2)

$$\text{V}_2 = 3\text{T}_1 + 5\text{T}_2$$

$$3\text{T}_1 = -5\text{T}_2 \Rightarrow \frac{11}{5}\text{T}_1$$

$$\text{V}_1 = 4\text{T}_1 - \frac{3}{5}\text{T}_1 \Rightarrow \frac{11}{5}\text{T}_1$$

$$\text{V}_1 = \frac{11}{5}\text{T}_1 \text{ and } \text{V}_2 = -\frac{11}{5}\text{T}_2$$

$$Y_{11} = \frac{\text{T}_1}{\text{V}_1} \Big|_{\text{V}_2=0} \Rightarrow -\frac{5}{22}\text{A} \Rightarrow \frac{5}{11}\text{V}$$

$$Y_{21} = \frac{\text{T}_2}{\text{V}_1} \Big|_{\text{V}_2=0} \Rightarrow -\frac{3}{22}\text{A} \Rightarrow -\frac{3}{11}\text{V}$$

Case 2

when $\text{V}_1 = 0$ from eq(1) and eq(2)

$$4\text{T}_1 = -3\text{T}_2$$

$$\text{V}_2 = -\frac{11}{3}\text{T}_1 \text{ and } \text{V}_2 = \frac{11}{4}\text{T}_2$$

$$Y_{12} = \frac{\text{T}_1}{\text{V}_2} \Big|_{\text{V}_1=0} \Rightarrow -\frac{9}{22}\text{A} \Rightarrow -\frac{9}{11}\text{V}$$

$$Y_{21} = \frac{\text{T}_2}{\text{V}_1} \Big|_{\text{V}_2=0} \Rightarrow -\frac{4}{22}\text{A} \Rightarrow \frac{4}{11}\text{V}$$

$$\boxed{Y_{11} = \frac{5}{11}\text{V}}$$

$$\boxed{Y_{12} = -\frac{3}{11}\text{V}}$$

$$\boxed{Y_{21} = -\frac{3}{11}\text{V}}$$

$$\boxed{Y_{22} = \frac{4}{11}\text{V}}$$

iii) T parameters:

$$(V_1, I_1) = f(V_2, -I_2)$$

$$V_1 = A V_2 + B(-I_2)$$

$$I_1 = C V_2 + D(-I_2)$$

Case 1 :- when $I_2 = 0$ from eq(1) and eq(2)

$$V_1 = 4 I_1$$

$$V_2 = 3 I_1$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} \Rightarrow \frac{4 I_1}{3 I_1} \Rightarrow \frac{4}{3}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} \Rightarrow \frac{I_1}{3 I_1} = \frac{1}{3} \text{ v}$$

Case 2 :- when $V_2 = 0$ from eq(1) and eq(2)

$$3 I_1 = -5 I_2$$

$$V_1 = -\frac{11}{3} I_2$$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} \Rightarrow \frac{-\frac{11}{3} I_2}{-\frac{5}{3} I_2} \Rightarrow \frac{11}{3} \text{ v}$$

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0} = \frac{\frac{5}{3} I_2}{-\frac{5}{3} I_2} \Rightarrow \frac{5}{3}$$

iv) T' parameters:

$$(V_1, I_1) = f(V_2, I_2)$$

Case 1 :- when $I_1 = 0$; $V_1 = 3 I_2$

$$A' = \frac{V_1}{V_2} \Big|_{I_1=0} = \frac{\frac{5}{3} I_2}{\frac{1}{3} I_2} \Rightarrow \frac{5}{3}, \quad B' = \frac{I_2}{V_1} \Big|_{I_1=0} = \frac{\frac{1}{3} I_2}{\frac{5}{3} I_2} = \frac{1}{5} \text{ v}$$

Case 2 :- when $V_1 = 0$; $4 I_1 = -3 I_2$, $V_2 = -\frac{1}{3} I_2$

$$C' = \frac{V_1}{I_2} \Big|_{V_1=0} \Rightarrow \frac{-\frac{11}{3} I_2}{-\frac{1}{3} I_2} \Rightarrow -3 \text{ v}, \quad D' = \frac{I_2}{I_1} \Big|_{V_1=0} \Rightarrow \frac{-\frac{1}{3} I_2}{-\frac{4}{3} I_2} = -\frac{1}{4}$$

v) h -parameters :-

$$(V_1, I_1) = f(V_2, V_3)$$

Case 1 :- when $V_3 = 0$;

$$3 I_1 = -5 I_2$$

$$V_1 = \frac{11}{5} I_1$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_3=0} = \frac{\frac{11}{5} I_1}{I_1} \Rightarrow \frac{11}{5} \text{ v} \quad h_{21} = \frac{I_1}{I_1} \Big|_{V_3=0} = \frac{-3}{5} \text{ A} \Rightarrow -\frac{3}{5}$$

Case 2 :- when $I_1 = 0$;

$$V_2 = 5 I_2$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = \frac{\frac{11}{5} I_1}{5 I_2} \Rightarrow \frac{3}{5} \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = \frac{I_1}{5 I_2} = \frac{1}{5} \text{ v}$$

vi) g -parameters :-

$$(I_1, V_2) = f(V_1, I_2)$$

Case 1 when $I_2 = 0$;

$$V_1 = 4 I_1, \quad V_2 = 3 I_1$$

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} = \frac{I_1}{4 I_1} = \frac{1}{4} \text{ v}; \quad g_{12} = \frac{V_1}{I_2} \Big|_{I_2=0} = \frac{3 I_1}{4 I_1} = \frac{3}{4}$$

Case 2 :- when $V_1 = 0$:-

$$4 I_1 = -3 I_2$$

$$V_2 = \frac{11}{4} I_2$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0} = -\frac{3}{\frac{11}{4}} = -\frac{3}{4}, \quad g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0} = \frac{\frac{11}{4} I_2}{I_2} = \frac{11}{4} \text{ a}$$

Phase Difference

At $t=0$,

$$i(0') = 0$$

Inductor does not allow the change in current and also a open circuit.

$$i(0') \text{ at } t=0$$

$$i(0') = k_1 e^{j\omega t} + k_2 e^{-j\omega t} \Rightarrow k_1 + k_2$$

$$\text{Ans At } t=0. \text{ By the KVL:}$$

$$\frac{di(0')}{dt} \frac{d^2i(0')}{dt^2} \text{ and } i(0')$$

$$-V_s + V_R + V_C + V_L = 0$$

$$-V_s + V_R + V_C + V_L = 0$$

By the laws we know:

$$V_R = IR, \quad V_C = \frac{1}{C} \int I dt \text{ and } V_L = L \frac{di}{dt}$$

Thus, we get

$$i(0')R + \frac{1}{C} \int i(0')dt + L \frac{di(0')}{dt} = V_s$$

$$6i(0') + 4 \int i(0')dt + 2 \frac{di(0')}{dt} = 0 \quad (1)$$

Multiplying with the $\frac{d}{dt}$ to eqn. (1), we get

$$6 \frac{di}{dt}(0') + 4i(0') + 2 \frac{d^2i(0')}{dt^2} = 0$$

Assuming the $\frac{d^2i(0')}{dt^2}$ as ρ and $\frac{di(0')}{dt}$ as θ

$$6\rho + 4 + 2\rho^2 = 0$$

$$\rho^2 + 6\rho + 2 = 0$$

$$(\rho+2)(\rho+1)=0$$

$$(\rho_1+2)(\rho_2+1)=0$$

$$\rho_1 = -2 \text{ and } \rho_2 = -1$$

$$\text{Thus, } i(0') = e^{-t} - e^{-2t}$$

$$\text{Since } \frac{di(0')}{dt} = \frac{V_s}{L} \Rightarrow \frac{2}{2} = 1$$

$$\frac{di(0')}{dt} = 1 \text{ Am / sec}$$

$$\frac{d^2i(0')}{dt^2} = -3 \text{ Am/sec}^2$$

Now, we know

$$\frac{d^2i(0')}{dt^2} + 3 \frac{di(0')}{dt} + 2i(0') = 0$$

$$\frac{d^2i(0')}{dt^2} + 3(-1) + 2(0) = 0$$

$$\left[\frac{d^2i(0')}{dt^2} = -3 \text{ Am/sec}^2 \right]$$

The complete solution will be solved by $k_1 + k_2 = 0$ and $-k_1 - 2k_2 = 1$

$$\begin{cases} k_1 + k_2 = 0 \\ -k_1 - 2k_2 = 1 \\ \therefore k_1 = -2k_2 \\ \therefore k_2 = -1 \end{cases}$$

$$8k_2 = 1 \text{ and } k_2 = 1$$

The general solution will be: $i(t) = k_1 e^{-t} + k_2 e^{-2t}$