


Transformed Circuit elements

(24)

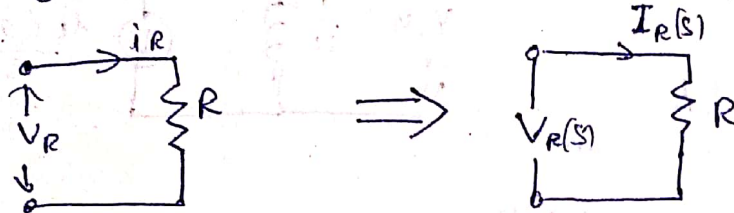1. Resistor:

$$V_R = i_R R \quad \rightarrow \text{Time Domain}$$

$$\mathcal{L}[V_R = i_R R] \xrightarrow{s \text{ Domain}} V_R(s) = I_R(s) R$$




2. Capacitor:

$$i_C = C \frac{dv_C}{dt}$$

$$I_C(s) = C [sV_C(s) - V_C(0^+)]$$

$$I_C(s) = sC V_C(s) - C V_C(0^+)$$

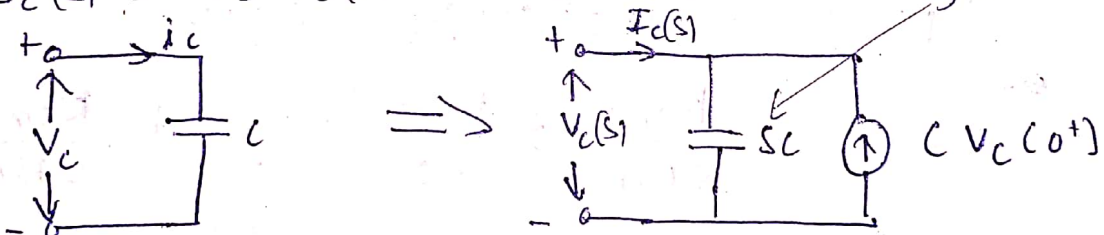


$$\frac{1}{C} \int_0^t i_C dt = \int_{V_C(0^+)}^{V_C} dv_C$$

$$\frac{1}{C} \int_0^t i_C dt = V_C - V_C(0^+)$$

$$\frac{1}{C} \frac{I_C(s)}{s} = V_C(s) - \frac{V_C(0^+)}{s}$$
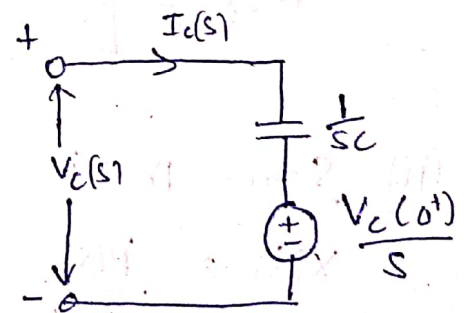
$$V_C(s) = \frac{1}{sC} I_C(s) + \frac{V_C(0^+)}{s}$$





3. Inductor:

$$V_L = L \frac{di_L}{dt}$$

$$V_L(s) = L [sI_L(s) - I_L(0^+)]$$


$$V_L(s) = sL I_L(s) - L I_L(0^+)$$

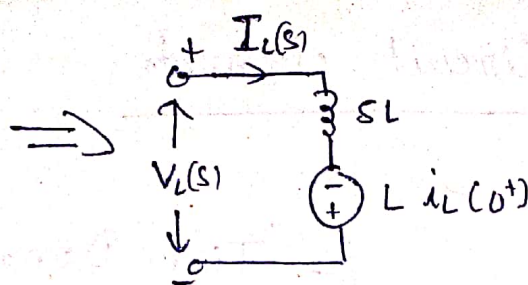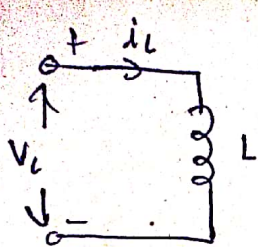

$$\int_{i_L(0^+)}^{i_L} di_L = \frac{1}{L} \int_0^t V_L dt$$

$$i_L - i_L(0^+) = \frac{1}{L} \int_0^t V_L dt$$
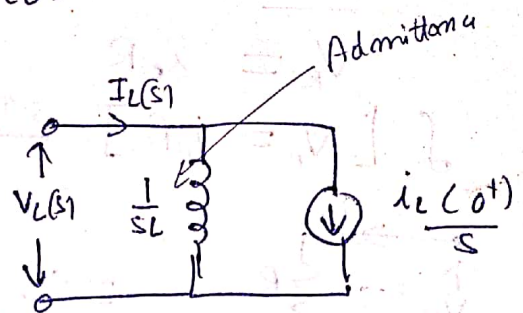
$$I_L(s) = \frac{1}{L} \frac{V_L(s)}{s} + \frac{i_L(0^+)}{s}$$



Partial Fraction Expansion

(i) Simple Zeros

$$X(s) = \frac{p(s)}{q(s)} = \frac{p(s)}{(s+s_1)(s+s_2)\dots(s+s_m)}$$

$$= \frac{k_{s1}}{s+s_1} + \frac{k_{s2}}{s+s_2} + \dots + \frac{k_{sm}}{s+s_m}$$

$$k_{sj} = \left[(s+s_j) \frac{p(s)}{q(s)} \right]_{s=-s_j}$$

(ii) Some Multiple Zeros

$$X(s) = \frac{p(s)}{q(s)} = \frac{p(s)}{(s+s_1)(s+s_2)\dots(s+s_i)^n(s+s_m)}$$

$$X_s = \frac{k_{s1}}{s+s_1} + \frac{k_{s2}}{s+s_2} + \dots + \frac{k_{sm}}{(s+s_m)} + \frac{A_{i1}}{s+s_i} + \frac{A_{i2}}{(s+s_i)^2}$$

$$+ \dots + \frac{A_{in}}{(s+s_i)^n}$$

$$\text{where } A_{in} = \left[(s+s_i)^n \frac{p(s)}{q(s)} \right]_{s=-s_i}$$

$$A_i(\pi-1) = \frac{d}{ds} \left[(s+s_i)^{\pi} \frac{p(s)}{q(s)} \right]_{s=-s_i}$$

$$A_i(\pi-2) = \frac{1}{2!} \frac{d^2}{ds^2} \left[(s+s_i)^{\pi} \frac{p(s)}{q(s)} \right]_{s=-s_i}$$

$$A_i 1 = \frac{1}{(\pi-1)!} \frac{d^{(\pi-1)}}{ds^{(\pi-1)}} \left[(s+s_i)^{\pi} \frac{p(s)}{q(s)} \right]_{s=-s_i}$$

Q Find Inverse Laplace transform

(i) $X(s) = \frac{5s+3}{(s+1)(s+2)(s+3)}$

Sol $\frac{5s+3}{(s+1)(s+2)(s+3)} = \frac{k_1}{(s+1)} + \frac{k_2}{(s+2)} + \frac{k_3}{(s+3)}$

$$k_1 = \left[\cancel{(s+1)} \frac{5s+3}{(s+1)(s+2)(s+3)} \right]_{s=-1} = \frac{-5+3}{(-1+2)(-1+3)} = -1$$

$$k_2 = \left[\cancel{(s+2)} \times \frac{5s+3}{(s+1)(s+2)(s+3)} \right]_{s=-2} = \frac{-10+3}{(-2+1)(-2+3)} = 7$$

$$k_3 = \left[\cancel{(s+3)} \times \frac{5s+3}{(s+1)(s+2)(s+3)} \right]_{s=-3} = \frac{-15+3}{(-3+1)(-3+2)} = -6$$

$$X(s) = \frac{-1}{(s+1)} + \frac{7}{(s+2)} - \frac{6}{(s+3)}$$

$$x(t) = -e^{-t} + 7e^{-2t} - 6e^{-3t}$$

(ii) $X(s) = \frac{1}{s(s+1)^3(s+2)}$

$$X(s) = \frac{k_1}{s} + \frac{k_2}{s+2} + \frac{A_1}{(s+1)^3} + \frac{A_2}{(s+1)^2} + \frac{A_3}{(s+1)}$$

$$k_1 = \frac{1}{2}, \quad k_2 = \frac{1}{(-2)(-2+1)^3} = \frac{1}{2}$$

$$A_1 = \left[\frac{(s+1)^3}{s(s+1)^3(s+2)} \right]_{s=-1} = \frac{1}{(-1)(-1+2)} = -1$$

$$A_2 = \left[\frac{d}{ds} \left[\frac{(s+1)^3}{s(s+1)^3(s+2)} \right] \right]_{s=-1} = \left[\frac{-(2s+2)}{s^2(s+2)^2} \right]_{s=-1}$$

$$= 0$$

$$\begin{aligned} A_3 &= \frac{1}{2!} \frac{d^2}{ds^2} \left[\frac{(s+1)^3}{s(s+1)^3(s+2)} \right]_{s=-1} = \frac{1}{2} \frac{d}{ds} \left[\frac{-(2s+2)}{s^2(s+2)^2} \right]_{s=-1} \\ &= \frac{1}{2} \left[\frac{-s^2(s+2)^2(2) + (2s+2)(4s^3+8s+12s^2)}{s^4(s+2)^4} \right]_{s=-1} \\ &= \frac{1}{2} \left[\frac{-(1)^2(1)^2(2) + 0}{(-1)^4(1)^4} \right] = \frac{1}{2}(-2) = -1 \end{aligned}$$

$$X(s) = \frac{1}{2} \cdot \frac{1}{s} + \frac{1}{2} \cdot \frac{1}{(s+2)} - \frac{1}{(s+1)^2} + \frac{0}{(s+1)^2} - \frac{1}{(s+1)}$$

$$X(t) = \frac{1}{2} + \frac{1}{2} e^{-2t} - \frac{1}{2} t^2 e^{-t} - e^{-t}$$

$$(iii) \quad X(s) = \frac{1}{s^2 + 4s + 8}$$

$$\underline{\text{Sol.}} \quad X(s) = \frac{1}{(s+2+2j)(s+2-2j)} = \frac{k_1}{(s+2+2j)} + \frac{k_2}{(s+2-2j)}$$


$$\begin{aligned} k_1 &= \left[\frac{(s+2-2j) \cdot 1}{(s+2+2j)(s+2-2j)} \right]_{s=-2-2j} \\ &= \frac{1}{(-2-2j)(2-2j)} = \frac{1}{-4j} = \frac{j}{4} \end{aligned}$$

$$k_2 = -\frac{j}{4}$$

$$X(s) = \frac{j}{4} \frac{1}{(s+2+2j)} - \frac{j}{4} \frac{1}{(s+2-2j)}$$

$$x(t) = \frac{j}{4} e^{(-2+2j)t} - \frac{j}{4} e^{(-2-2j)t} = \frac{1}{2} e^{-2t} \sin 2t$$

Q

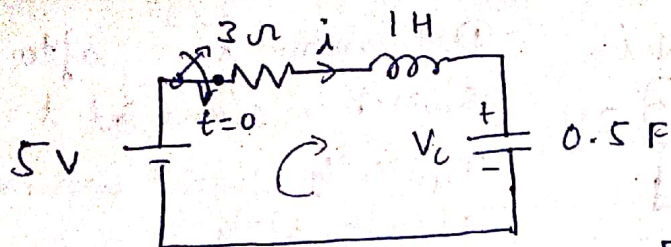

If initial conditions

$$\text{are } V_c(0^-) = 2V$$

$$\text{and } i_L(0^-) = 2A$$

Find $i(t)$ after switch is closed at $t=0$

(26)

Sol Apply KVL

$$5 - 3i - 1 \frac{di}{dt} - \left[2 \int_0^t i dt + V_c(0^+) \right] = 0$$

Laplace both sides

$$\frac{5}{s} - 3I(s) - [sI(s) - i_L(0^+)] - \left[2 \frac{I(s)}{s} + \frac{V_c(0^+)}{s} \right] = 0$$

$$\text{Since } i_L(0^+) = i_L(0^-) = 2A$$

$$V_c(0^+) = V_c(0^-) = 2V$$

$$\therefore \frac{5}{s} - 3I(s) - sI(s) + 2 - 2 \frac{I(s)}{s} - \frac{2}{s} = 0$$

$$s^2 I(s) + 3s I(s) + 2 I(s) = 2s + 3$$

$$I(s) = \frac{2s + 3}{s^2 + 3s + 2} = \frac{2s + 3}{(s+1)(s+2)}$$


$$I(s) = \frac{k_1}{s+1} + \frac{k_2}{s+2}$$

$$k_1 = \frac{2(-1) + 3}{(-1+2)} = 1 \quad ; \quad k_2 = \frac{2(-2) + 3}{(-2+1)} = -1$$

$$I(s) = \frac{1}{s+1} + \frac{-1}{s+2}$$

$$i(t) = \text{inverse of } I(s)$$

$$= e^{-t} - e^{-2t}$$

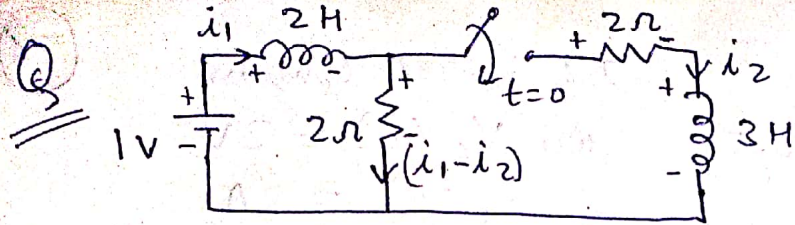

Determine i_2 , after the switch is closed at $t=0$. Initially circuit was in steady state.

Sol $i_1(0^-) = 0.5 \text{ A}$, $i_2(0^-) = 0$

KVL in left side loop, (after $t=0$)

$$1 - 2 \frac{di_1}{dt} - 2(i_1 - i_2) = 0 \Rightarrow 2 \frac{di_1}{dt} + 2i_1 - 2i_2 = 1$$

Laplace both sides

$$2[sI_1(s) - i_1(0^+)] + 2I_1(s) - 2I_2(s) = \frac{1}{s}$$

$$2sI_1(s) - 1 + 2I_1(s) - 2I_2(s) = \frac{1}{s}$$

$$I_1(s) = \frac{2sI_2(s) + s + 1}{2s^2 + 2s} \rightarrow \text{--- (I)}$$

KVL in Right side loop

$$2(i_1 - i_2) - 2i_2 - 3 \frac{di_2}{dt} = 0$$

Laplace both sides

$$2I_1(s) - 2I_2(s) - 2I_2(s) - 3[sI_2(s) - i_2(0^+)] = 0$$

$$2I_1(s) - 4I_2(s) - 3sI_2(s) = 0$$

$$2 \left[\frac{2sI_2(s) + s + 1}{2s^2 + 2s} \right] - 4I_2(s) - 3sI_2(s) = 0 \quad (\text{using I})$$

$$-3s^2 I_2(s) - 7s I_2(s) - 2s I_2(s) + s + 1 = 0$$


$$I_2(s) = \frac{s+1}{3s^2 + 7s + 2} = \frac{1}{3} \frac{(s+1)}{s(s+\frac{1}{3})(s+2)}$$

$$I_2(s) = \frac{1}{3} \left[\frac{k_1}{s} + \frac{k_2}{s+\frac{1}{3}} + \frac{k_3}{s+2} \right]$$

$$k_1 = \frac{3}{2} ; k_2 = -\frac{6}{5} ; k_3 = -\frac{3}{10}$$

$$I_2(s) = \frac{1}{3} \left[\frac{3}{2} \cdot \frac{1}{s} - \frac{6}{5} \frac{1}{s+\frac{1}{3}} - \frac{3}{10} \frac{1}{s+2} \right]$$
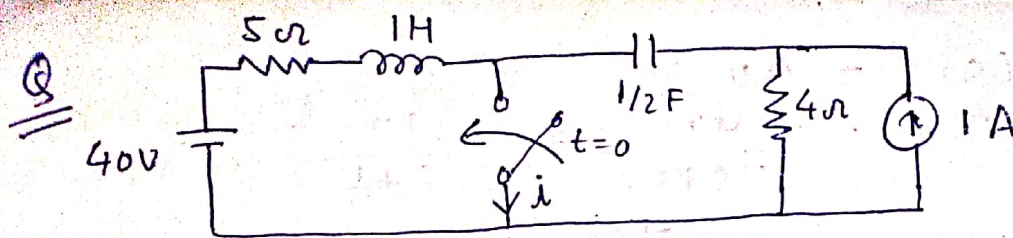
$$i_2(t) = \frac{1}{2} - \frac{2}{5} e^{-\frac{1}{3}t} - \frac{1}{10} e^{-2t} \quad \underline{\underline{\text{Solution}}}$$




Initially Circuit (27) was in steady state. Switch was closed at $t=0$.

Find $i(t)$ (current through switch).

Sol.

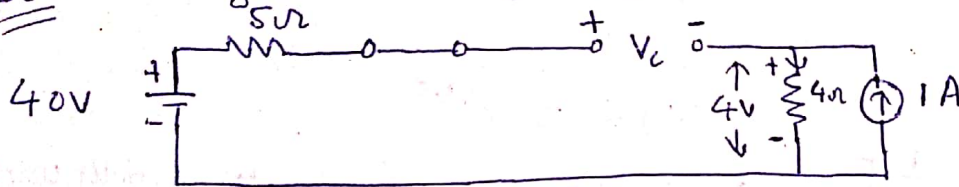
Before closing switch, circuit was in steady state.



Circuit before closing switch (steady state)

$$i_L(0^-) = 0 \quad ; \quad V_C(0^-) = 36V$$

Circuit after closing switch

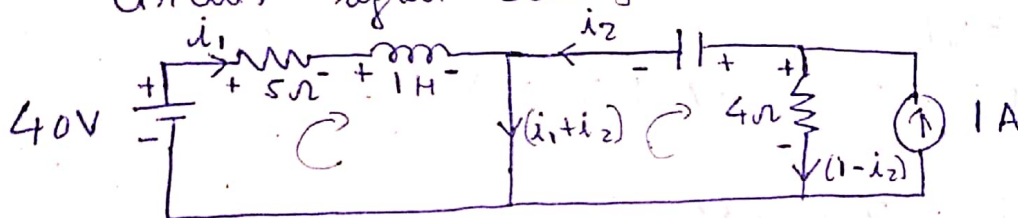

$$i_1(0^+) = i_L(0^-) = 0$$

$$V_C(0^+) = V_C(0^-) = 36V = -36V$$

KVL in left side loop

$$40 - 5i_1 - 1 \frac{di_1}{dt} = 0$$

Laplace both sides

$$\frac{40}{s} - 5I_1(s) - [sI_1(s) - i_1(0^+)] = 0$$

$$\frac{40}{s} - 5I_1(s) - sI_1(s) = 0$$

$$I_1(s) = \frac{40}{s^2 + 5s} = \frac{40}{s(s+5)}$$

$$= \frac{8}{s} - \frac{8}{s+5}$$

$$i_1(t) = 8 - 8e^{-5t}$$

KVL in right side loop

$$2 \int_0^t i_2 dt + V_C(0^+) - (1 - i_2)4 = 0$$

$$2 \int_0^t i_2 dt - 36 = 4 - 4i_2$$

Laplace both sides

$$2 \frac{I_2(s)}{s} - \frac{36}{s} = \frac{4}{s} - 4I_2(s)$$


$$(4s+2) I_2(s) = 40$$

$$I_2(s) = \frac{40}{4s+2} = \frac{10}{s+\frac{1}{2}}$$

$$i_2(t) = 10 e^{-1/2 t}$$

Current through switch, $i = i_1 + i_2$

$$i(t) = 8 - 8 e^{-5t} + 10 e^{-1/2 t}$$

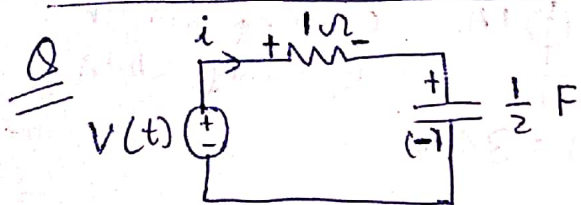

$$V(t) = 2 e^{-0.5t}$$

$$V_C(0^+) = 0 \quad (\text{Capacitor initially uncharged})$$

Find the expression for $i(t)$

Sol. Apply KVL

$$V(t) = 1i + 2 \int_0^t i dt + V_C(0^+)$$

$$2 e^{-0.5t} = i + 2 \int_0^t i dt$$

Laplace both sides

$$2 \cdot \frac{1}{(s+0.5)} = I(s) + 2 \frac{I(s)}{s}$$

$$I(s) = \frac{2s}{(s+0.5)(s+2)} = \frac{k_1}{(s+0.5)} + \frac{k_2}{(s+2)}$$


$$k_1 = \frac{2(-0.5)}{(-0.5+2)} = \frac{-1}{1.5} = -\frac{2}{3}$$

$$k_2 = \frac{2(-2)}{(-2+0.5)} = \frac{8}{3}$$

$$I(s) = -\frac{2}{3} \frac{1}{(s+0.5)} + \frac{8}{3} \frac{1}{(s+2)}$$

Inverse Laplace transform

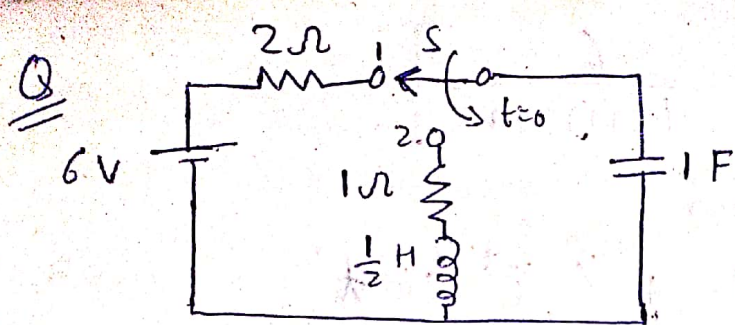
$$i(t) = -\frac{2}{3} e^{-0.5t} + \frac{8}{3} e^{-2t}$$



Initially switch was at position 1 and circuit was in steady state. Switch is moved to position 2 at $t=0$. Find voltage across capacitor.

Sol. When switch was at Position 1, Voltage across capacitor in steady state was 6V. (i.e. $V_C(0^-) = 6V$)

Circuit when switch is in Position 2.

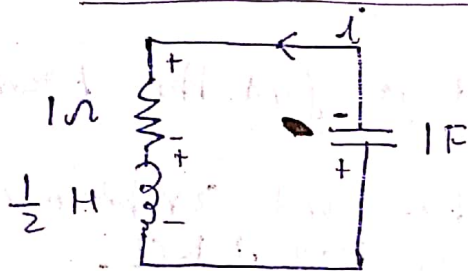

Apply KVL

$$1i + \frac{1}{2} \frac{di}{dt} + \left[\frac{1}{1} \int_0^t i dt + (-6) \right] = 0$$

Laplace transform both sides

$$I(s) + \frac{1}{2} [sI(s) - i(0^+)] + \frac{I(s)}{s} - \frac{6}{s} = 0$$

$$I(s) + \frac{1}{2} [sI(s) - 0] + \frac{I(s)}{s} - \frac{6}{s} = 0$$

$$I(s) = \frac{12}{s^2 + 2s + 2}$$

$$V_C + i(1) + \frac{1}{2} \frac{di}{dt} = 0$$

Laplace both sides

$$V_C(s) + I(s) + \frac{1}{2} [sI(s) - 0] = 0$$

$$V_C(s) = -I(s) - \frac{1}{2} sI(s)$$

$$V_C(s) = - \left[I(s) \left(1 + \frac{s}{2} \right) \right]$$

$$V_C(s) = - I(s) \left(\frac{s+2}{2} \right)$$

$$V_C(s) = - \frac{12}{s^2 + 2s + 2} \left(\frac{s+2}{2} \right)$$

$$= - \frac{6(s+2)}{s^2 + 2s + 2}$$

$$35) V_c(s) = - \left[\frac{6(s+1)}{(s+1)^2 + 1} + \frac{6}{(s+1)^2 + 1} \right]$$

Inverse Laplace Transform

$$V_c(t) = - \left[6 e^{-t} \cos t + 6 e^{-t} \sin t \right]$$

Graph Theory

- Any electrical network can be solved by applying KVL and KCL.
- When we apply KVL / or KCL in any electric network, we get network equations. Network equations can be solved to find the branch voltages & currents.
- But when network is very complex and complicated, then it becomes very difficult to apply KVL & KCL.
- Such complicated and complex networks can be solved easily using graph theory.
- Graph theory is used in Computer Aided Electric network analysis.
- Application of Graph Theory :-
 - (i) It is used in Power System Analysis.
 - (ii) It can be used as a tool to construct software programs related to electric network analysis & simulation.
- Graph theory is very generalized approach to solve (or analysis) any complex electric network.
- Graph theory uses network topology i.e. only the geometrical pattern of a network is considered. Various ^{standard} matrices are formed (or constructed) for a given network topology. These matrices manipulation (or calculations) are used to form network equations and hence find the solution of a given network.