

$$P = VI = I^2 R = \frac{V^2}{R}$$

Page No.	
Date	

10/4/23

Unit 1

Ohm's Law \rightarrow The current passing through the circuit is directly proportional to voltage keeping the temperature constant

Current \propto Voltage

Voltage \propto Current

Sources \rightarrow batteries, generators etc.


Sink \rightarrow RLC

Thermal limit

$$T \propto V$$



$$V = IR$$

$$R = \frac{\rho l}{A}$$

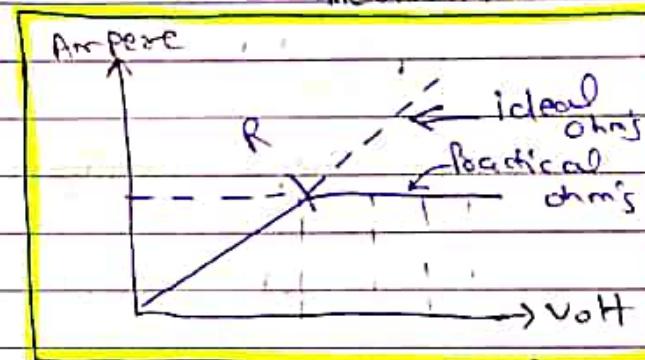

- \rightarrow Resist R is directly proportional to length of wire
- \rightarrow R is inversely proportional to its area
- \rightarrow ρ is constant that depends upon the material and is called specific resistance and resistivity

Resistance Variation with temperature

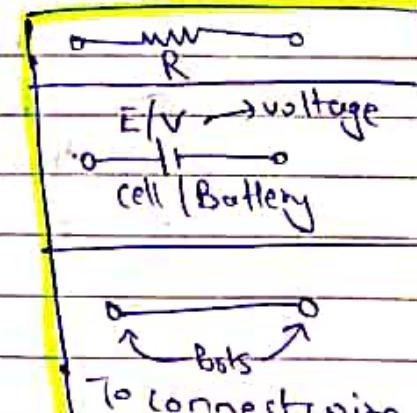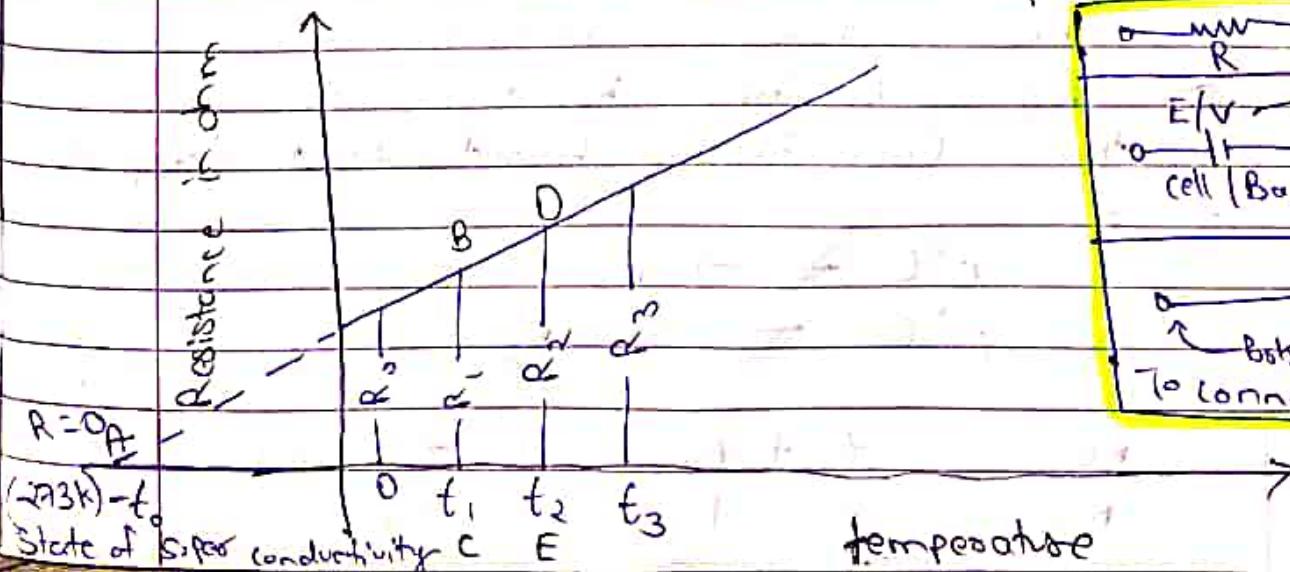

- For all pure metallic conductors Resistance increases with increase in temperature.
- For all non-conductors materials the Resistivity / ρ decreases with increase in temperature.

$$\text{Slope of } ABC = \frac{R_1}{t_1 + t_0}$$

$$\text{Slope of } ADE = \frac{R_2}{t_2 + t_0}$$

Slope Slopes are equal

$$\frac{R_1}{t_1 + t_0} = \frac{R_2}{t_2 + t_0}$$

$$\frac{R_2}{R_1} = \frac{t_2 + t_0}{t_1 + t_0}$$

If R_1 & t_1 are known (Resistance at a particular temperature) is known then Resistance at t_2 can be calculated using the above formula
 Let R_0 be the Resistance at zero (0°C) and the conductor is heated to a temperature at t

$$0^\circ\text{C} \longrightarrow R_0$$

$$t^\circ\text{C} \longrightarrow R_t$$

$$\frac{R_t}{R_0} = \frac{t + t_0}{t_0 + 0} = \frac{t + t_0}{t_0}$$

$$R_t = R_0 + \frac{t}{t_0} R_0$$

$$R_t - R_0 = \frac{t}{t_0} R_0$$

$\Delta R = \alpha R_0 t$ ← temperature
 change in temperature coefficient Resistance at 0°C

~~Ques~~
 A coil of zelby is made up of Copper wire.
 At 20°C the resistance is 400 ohm:
 calculate the resistance of a coil at
 80°C . The α of copper is 0.0038 ohm
 at 0°C .

Sol) $20^\circ\text{C} \rightarrow 400 \text{ ohm}$

$80^\circ\text{C} \rightarrow ?$

$\alpha_0 = 0.0038$

$\alpha_{20} = \frac{1}{\frac{1}{\alpha_0} + t} = \frac{1}{\frac{1}{0.0038} + 20} = 0.003533$

$R_{80^\circ\text{C}} = R_{20} [1 + \alpha_{20} (t_2 - t_1)]$

$R_{80^\circ\text{C}} = 400 [1 + 0.003533 (80 - 20)]$
 $= 484.8 \Omega$

System


Electrical component when connected in a particular manner to perform a particular task is called a System.

In electrical term a System is called circuit.

The different circuit are connected in the following 3 . manner.

- Series connection
- Parallel connection
- Series + Parallel connection

a) Series connection (Current Same)

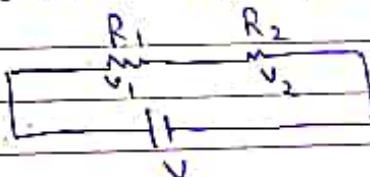

$$R_{\text{eff}} = R_1 + R_2$$

$$V = IR$$

$$I = \frac{V}{R_1 + R_2}$$

$$V = V_1 + V_2$$

$$\text{Power} = I^2 R = \frac{V^2}{R} = VI$$

$$\text{Power battery} = VI$$

$$\text{Power } R_1 = I^2 R_1$$

$$\text{Power } R_2 = I^2 R_2$$

$$P_{\text{battery}} = P_{R_1} + P_{R_2}$$

- a) The same current flows through all part of the circuit.
- b) The applied voltage is equal to the sum of voltage drops across different parts of the circuit.
- c) Voltage drop & Power are additive
- d) Resistance is additive.

(Q) 3 Resistors are connected in series in through a 12 V battery. The value $R_1 = 1\Omega$.
 ~~R_2~~ the voltage drop across the 2nd
 Resistance is 4V

The power dissipated in the 3rd Resistor
 is 12 watts.

Find the value of R_1 , R_2 , R_3


$$\text{Voltage drop } P_2 = 4V = V_2$$

$$R_{\text{eff}} = R_1 + R_2 + R_3$$

$$V = 12V$$

$$I = \frac{12}{R_1 + R_2 + R_3}$$

$$I = \frac{12}{1 + R_2 + R_3}$$

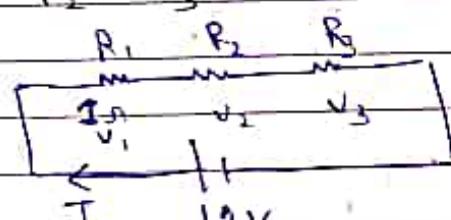

$$V_1 + V_2 + V_3 = 12$$

$$V_1 + V_3 = 8$$

Power dissipated

$$P = VI$$

$$12 = V_3 I$$

$$V_3 = \frac{12}{I}$$

Now

$$P = VI = I^2 R = \frac{V^2}{R}$$

Page No.	
Date	

$$V_1 + V_3 = 8$$

$$\frac{I}{1} + \frac{12}{I} = 8$$

$$I^2 + 12 = 8I$$

$$I^2 - 8I + 12 = 0$$

$$I^2 - 6I - 2I + 12 = 0$$

$$I(I-6) - 2(I-6) = 0$$

$$[I=2, I=6]$$

$$I=6$$

$$V_2 = IR_2$$

$$R_2 = \frac{4}{6}$$

$$[R_2 = \frac{2}{3}]$$

$$R_3 = \frac{P}{I^2} = \frac{12}{36} = 1\Omega$$

$$I=2$$

$$V = 2R_2$$


$$[R_2 = 2]$$

$$R_3 = \frac{12}{4} = 3\Omega$$

$$[R_3 = 3\Omega]$$

$$[R_3 = \frac{1}{3}]$$

b) Parallel connection (Potential same)

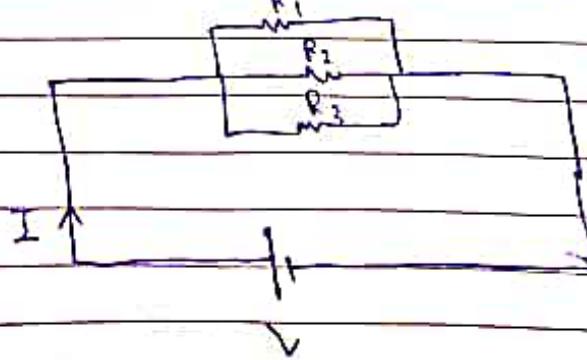

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_1 = \frac{V}{R_1}$$


$$I_2 = \frac{V}{R_2}$$

$$I_3 = \frac{V}{R_3}$$

$$I = I_1 + I_2 + I_3$$

- a) Same voltage appears all the branches of circuit
- b) Each branch has its own individual current.
- c) Branch current are additive
- d)
- e)
- 3) Series Parallel circuit
- Q) Two Resistances of $20\ \Omega$ & $30\ \Omega$ are placed in parallel to each other which is then placed in series with a $15\ \Omega$ resistor. The current through $15\ \Omega$ resistance is 3 Amperes. Find the total power consumed by $20\ \Omega$ & $30\ \Omega$ resistor.
- The current through $20\ \Omega$ & $30\ \Omega$ resistor
 - The voltage across the whole circuit.
 - The total power consumed.

(Sol.)

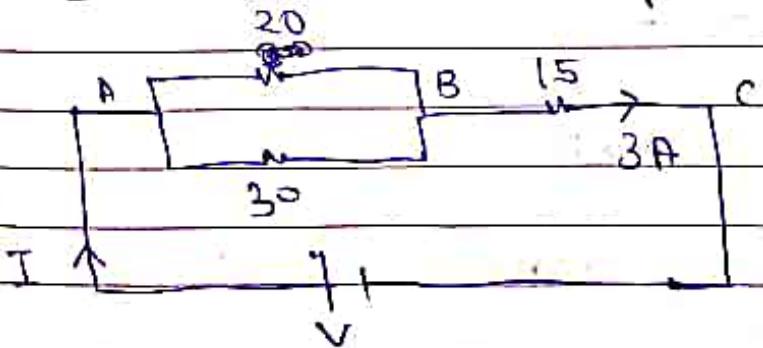

$$R_{\text{eff}} = \frac{20 \times 30}{20+30} + 15$$

$$R_{\text{eff}} = \frac{20 \times 30}{50} + 15 = \frac{60}{5} + 15$$

$$R_{\text{eff}} = 27 \Omega$$

$$V = IR$$

$$V = 3 \times 27$$

$$\boxed{V = 81 \text{ V}} \quad \text{across the circuit}$$

$$\text{Power} = VI = 3 \times 81 = 243 \text{ W}$$

$$\boxed{\text{Power} = 243 \text{ W}}$$

i)

$$V = IR$$

$$I \cancel{= \frac{V}{R}}$$

$$I_{20} = \frac{81}{20}$$

$$I_{30} = \cancel{\frac{81}{30}}$$

$$V_{PB} + V_{BC} = V$$

$$V_{PB} + 15 \times 3 = 81$$

$$\boxed{V_{PB} = 36 \text{ V}}$$

$$I_1 = \frac{36}{20} = 1.8 \text{ A}$$

$$I_2 = \frac{36}{30} = 1.2 \text{ A}$$

Type No.	
Date	

Circuit Analysis and Energy Source

Energy source is a device that convert chemical, mechanical, thermal or some other form of energy into electrical energy.

Energy consumer also known as load convert electrical energy into other form of energy (such as lamp heating element, electric motor etc.)

While transmission from generators to load if the amplitude / magnitude of voltage of current remains constant these are known as DC ~~dis~~ (Direct current) circuit. If the voltage of current magnitude changes with time they are known as alternating current circuit AC \leftrightarrow circuit.

- The element which supply energy to network are known as active ~~source~~ elements.
Example :- Battery, Solar cell, Wind Turbine

The component which dissipate or store energy are known as passive elements ex) Resistor, capacitor, inductor.

Parameters	Basic Relationship	VI characteristic
------------	--------------------	-------------------

R

$$V = iR$$

$$V_R = R_i$$

$$i_R = \frac{V_R}{R}$$

L

$$\Psi = L i$$

$$V_L = \frac{L di_L}{dt}$$

$$i_L = \frac{1}{L} \int_{-\infty}^t V_L dt$$

C

$$q = CV \quad V_C = \frac{1}{C} \int_{-\infty}^t i_C dt \quad i_C = C \frac{dV_C}{dt}$$

These are broad categories of source


① Dependent source

② Independent source

Dependent Source are the one which depend on ~~other~~ ^{some} source quantity in the circuit which can either be voltage or current. The relationship may be linear or non-linear.

The are two broad category source of dependent sources

i) voltage dependent voltage source.

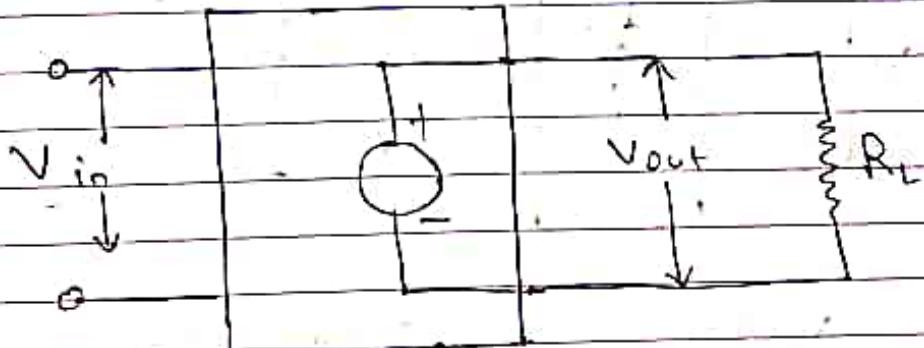

VDCS

$$V_{out} = K_1 V_{in}$$


K_1 = constant

When the strength of voltage or

current in the source

for any change in

the connected network

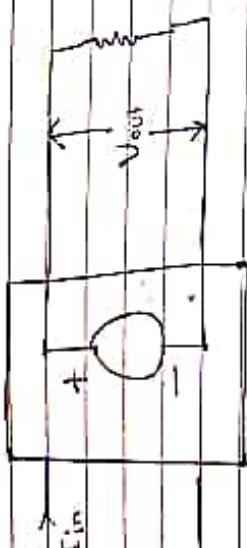

$$V_{out} = k_2 I_{in} \quad k_2 \rightarrow \text{constant}$$



CVS like $V = R I$



$$I_{out} = k_1 I_{in} \quad k_1 = \text{constant}$$

DCS

Independent Source

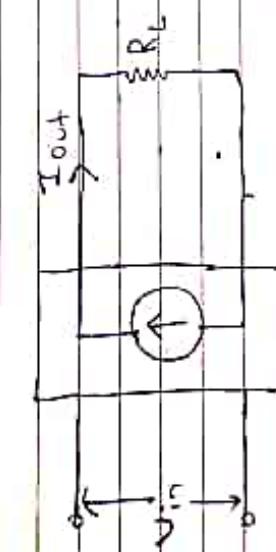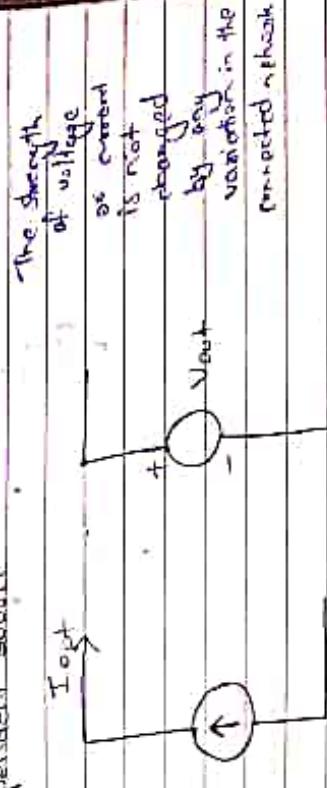

$$\text{IVS} \quad I_{out} = k_3 V_{in}$$

k_3 in mho (resistance in ohm)

$$V = I R$$

$$I = \frac{V}{R}$$

A source is said to be independent if its value remain constant and is independent of any other quantity in the circuit

Ideal and practical Sources

Elements that provide constant current and constant voltage with zero internal resistance are called ideal sources

Page No.	
Date	


Practical Sources experienced a current or voltage drop because of internal resistance offered by them.

Note: ideal & practical sources are dependent on independent both are possible


The current & voltage depending from the ~~constant~~ chemical electrical energy, Mechanical, Thermal process

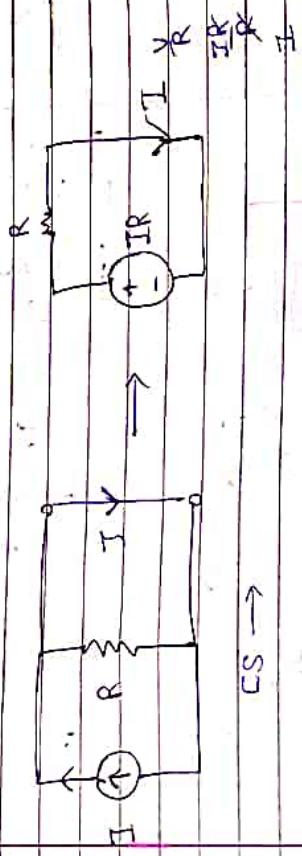example phone charges convert 220 A to 5 A so it is convert with the help of K


Resistor at 0°C & -273K it become resistance free & behaves like ideal



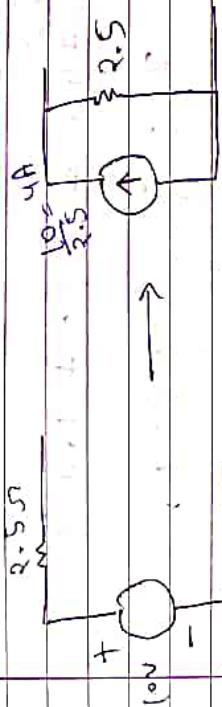(Current Source converted into voltage source)



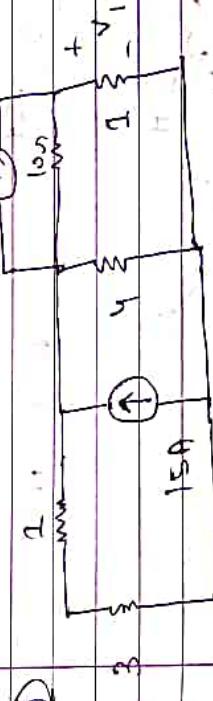
Voltage Source converted into Current Source



No resistance means short circuit

$$R_{eq} = \frac{V}{I} = \frac{V}{I+q} = \infty$$

NC
②

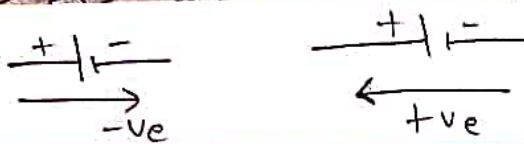


Date : / /

Page No.

KCL

$$\sum I = 0$$

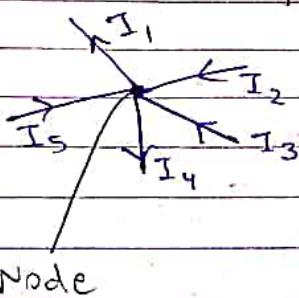(Sum of all incoming current) = (sum of all outgoing current)



KVL In a closed loop


$$\sum V + \sum E = 0$$

According to Ohm's law $V = IR$



$$\sum IR + \sum E = 0$$

① Always consider clockwise current

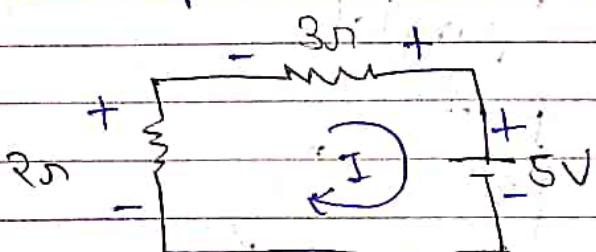③ Some component \rightarrow Different Terminal
Diff component \rightarrow Same Terminal




④

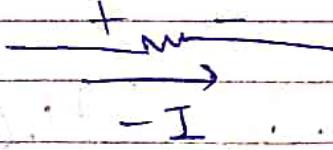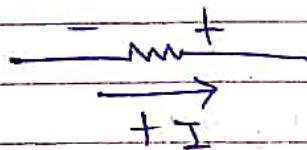



⑤ अधिक लक्षित सौर वोल्टेज दो (battery) तो इसका पॉल्यूटरी वाले की मूल नहीं और signs convention है।

⑥ इन वाले में दो कर्पत जो होंगे एक (+,-) और दूसरे (-,+)


- Q) Find the current through each loop

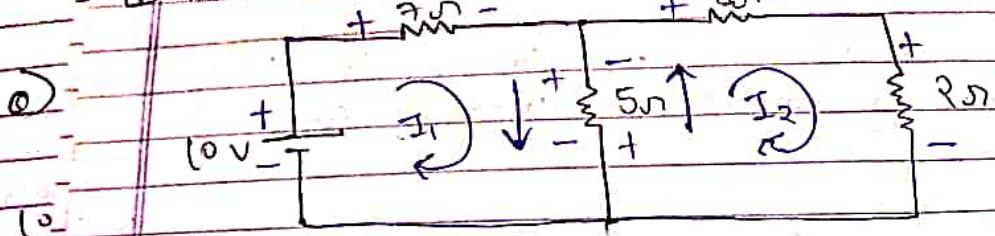

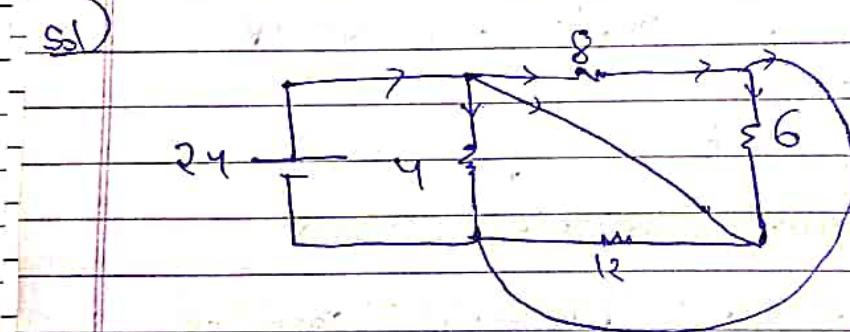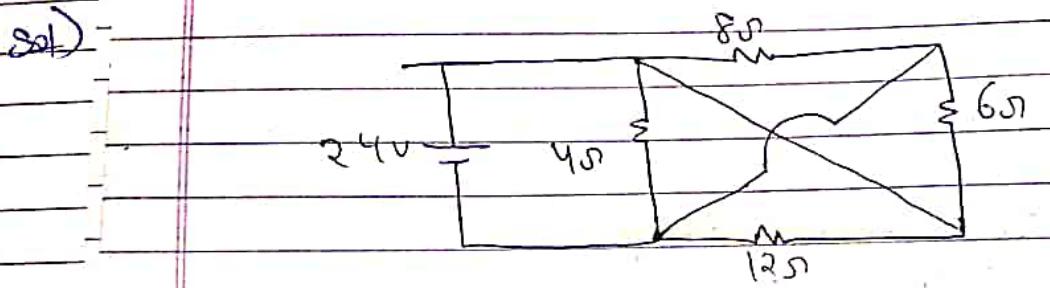- Q) Calculate battery current and effective resistance of the circuit



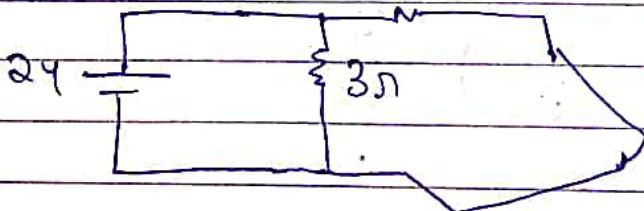8, 6 are in parallel
4, 12 are in parallel
 $3 \cdot 43 \Omega$




$24 \parallel \frac{1}{\frac{1}{4} + \frac{1}{8}} = 1.6$

$I = 24$

1.6

$I = 1.5$


Date: / /
Page No.

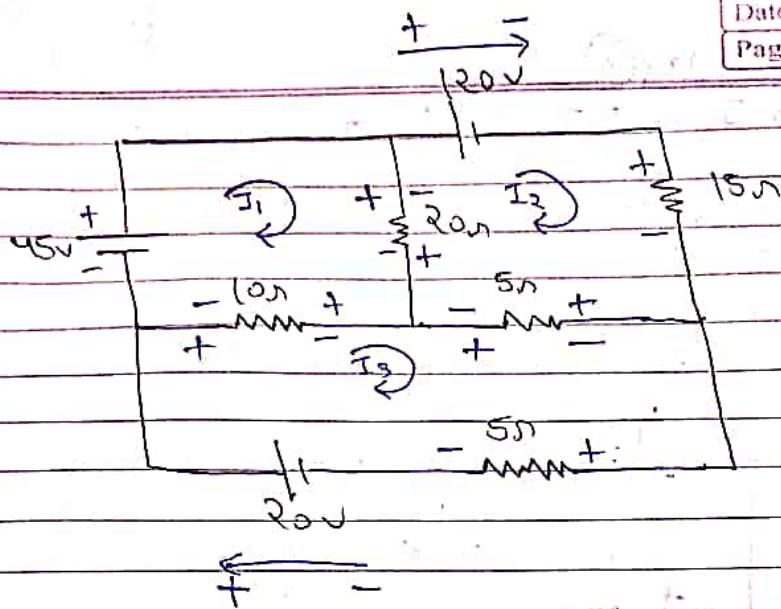

Mesh analysis (KCL & KVL application)

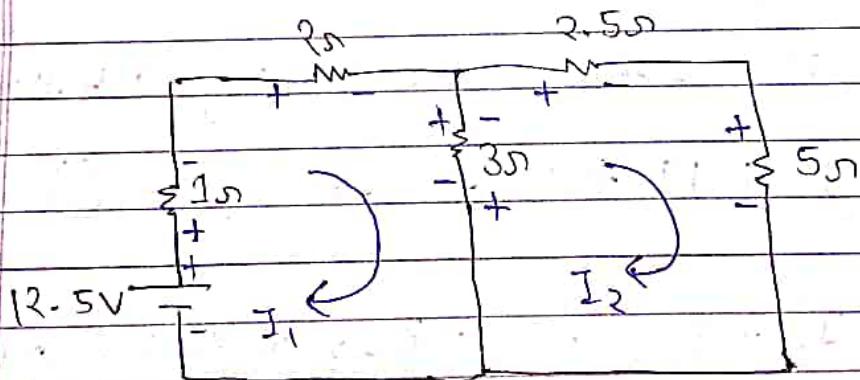(a) with the help of Mesh current Method

Find the current \rightarrow through 3Ω resistor
& its direction



(b) Step 1) Making the different Nodes &
current with direction.

Apply KVL to Mesh loop ①

$$12.5 - I_1 - 2I_1 - 3I_1 + 3I_2 = 0$$

loop(2)


$$-2.5I_2 - 5I_1 - 3I_2 + 3I_1 = 0$$

②

$$[I_1 = 2.43 \text{ A}]$$

- ② By Mesh analysis find on unknown first
in the network which causes the Net
current I_1 to be zero

③ ② Red current through all loops

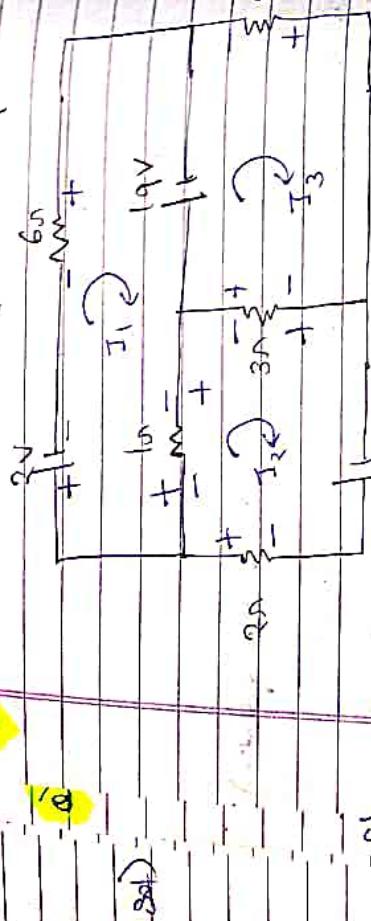

④ 25V

ignore the battery after taking 1 battery

loop ①
 $-2 + 6I_1 + 19 + I_1 - I_2 = 0 \quad -\text{(1)}$

loop ②

$$2I_2 + I_3 + 3I_2 - I_1 - 3I_3 + 25 = 0 \quad -\text{(2)}$$

loop ③

$$I_1 = 6 \text{ given} \quad -\text{(3)}$$

Date : / /


Page No.:

Date : / /

Page No.:


$$-2.5I_2 - 5I_1 - 3I_2 + 3I_1 = 0$$

$$[I_1 = 2.43 \text{ A}]$$

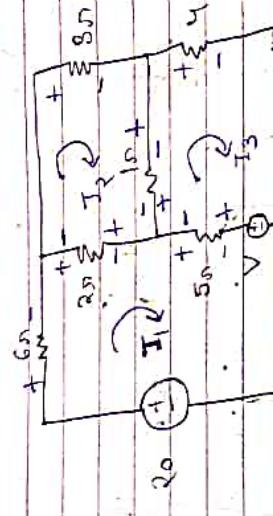

$$20I_1 - 6I_2 - 2I_3 - 5I_1 - 5I_3 + 2I_2 = 0$$

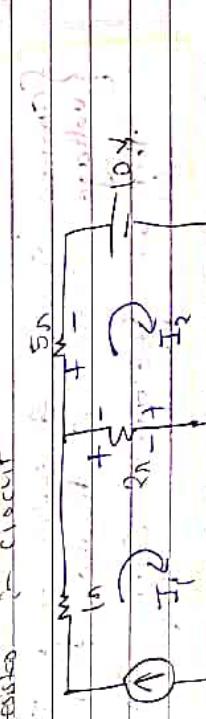② By Mesh analysis find the current in
resistor 2 circuit



② By Mesh analysis find the current in
resistor 2 circuit

loop ②


$$-2I_2 + 2I_1 - 5I_2 - 10 = 0$$

$$I_2 = 0.285 \text{ A}$$

Current through 2 resistors
 $I_1 - I_2 = 6 - 0.285 = 5.71 \text{ A}$

Super Nodes

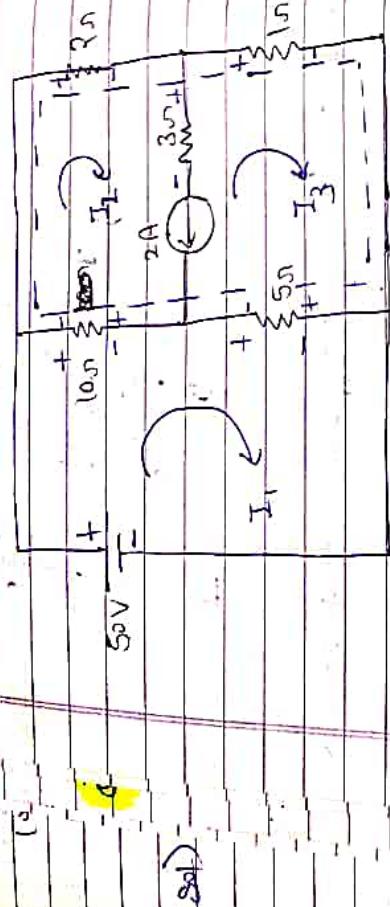
② Find the current through S_{3N} resistor in the circuit.



apply KVL to Super mesh

$$-2I_2 - I_3 - 5I_3 + 5I_1 - 10I_1 = 0$$

Star Delta Transformation

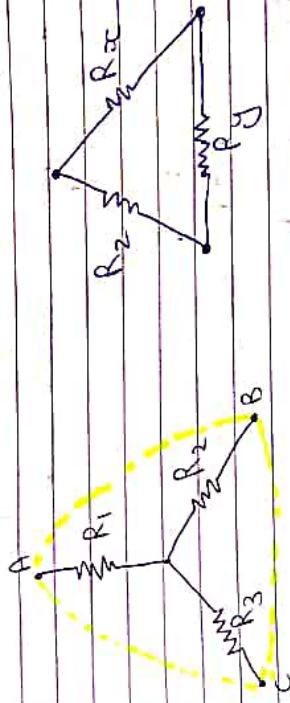

Delta

Current Source & Series & R_{parallel}
 Voltage Source & Parallel R_{parallel}
 they are Redundant

S_{3N} resistor become Redundant

$$\frac{I_2 + 2}{I_2} = \frac{I_3}{I_2 - I_3} = X$$

$$\boxed{I_2 - I_3 = 2}$$


loop ①

$$50 - 10I_1 - 5I_2 + 10I_3 + 5I_3 = 0$$

$$R_2 = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

R_1

Delta to Star


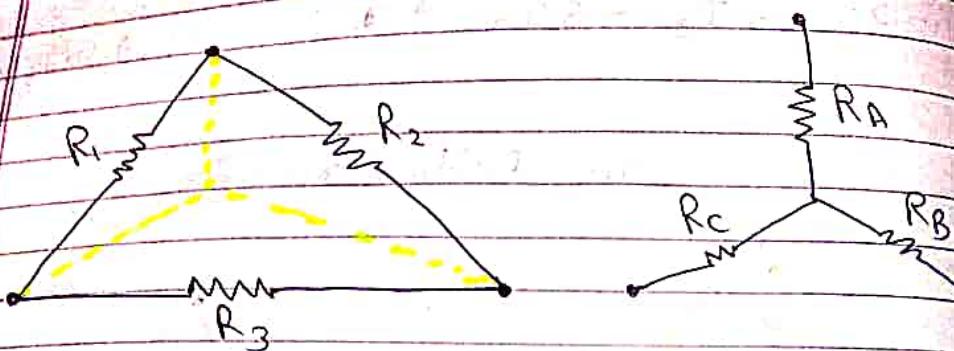


$$R_A = \frac{R_1 \times R_2}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_2 \times R_3}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_1 \times R_3}{R_1 + R_2 + R_3}$$

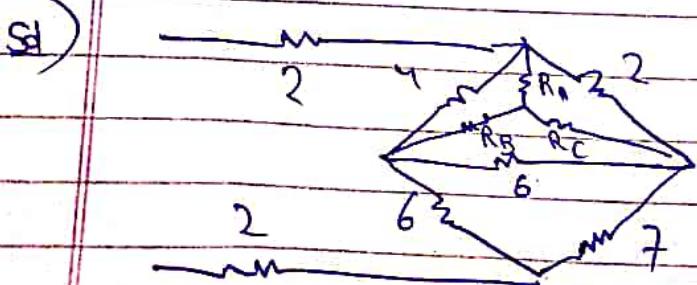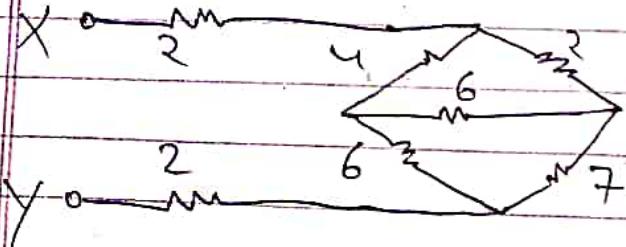- Q) Find the equivalent Resistance 'between terminals X and Y' in the network.



$$R_A = \frac{8}{12} = 0.6$$

$$R_B = \frac{24}{12} = 2$$

$$R_C = \frac{12}{12} = 1$$

Current come at Node taken won't be
current going out from Node taken -ve


Date: /

Page No.

Nodal Analysis (only KCL use)

$$V = IR \quad I = \frac{V}{R} = \frac{V_2 - V_1}{R}$$

Q)

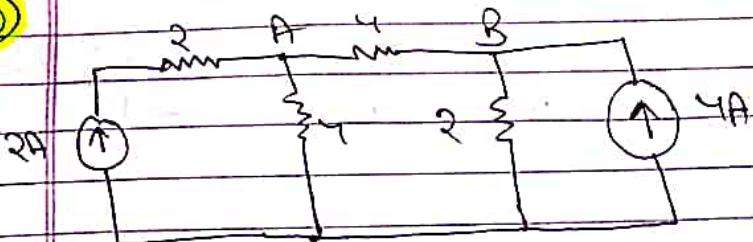


So) KCL at node A

$$2 = \frac{V_A}{4} + \frac{V_A - V_B}{4} \quad \text{--- (1)}$$

KCL at node B

$$4 = \frac{V_B}{2} + \frac{V_B - V_A}{4} \quad \text{--- (2)}$$

Q)

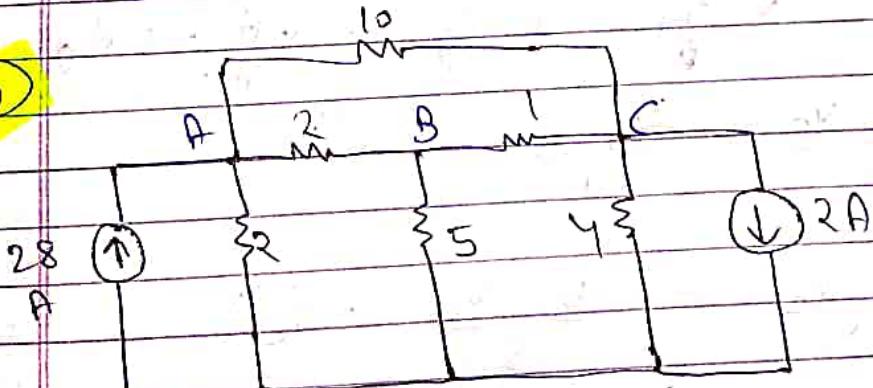

So) three Node A, B, C

at A

$$28 = \frac{V_A}{2} + \frac{V_A - V_B}{2} + \frac{V_A - V_C}{10} \quad \text{--- (1)}$$

At A, C

$$0 = \frac{V_C - V_A}{10} + \frac{V_C - V_B}{1} + \frac{V_C}{4} \quad \text{--- (2)}$$

At B


$$0 = \frac{V_B - V_A}{2} + \frac{V_B}{5} + \frac{V_B - V_C}{1} \quad \text{--- (3)}$$

$$V = IR$$

Thevenin

Determine
in the n

$$10V \frac{+}{-}$$

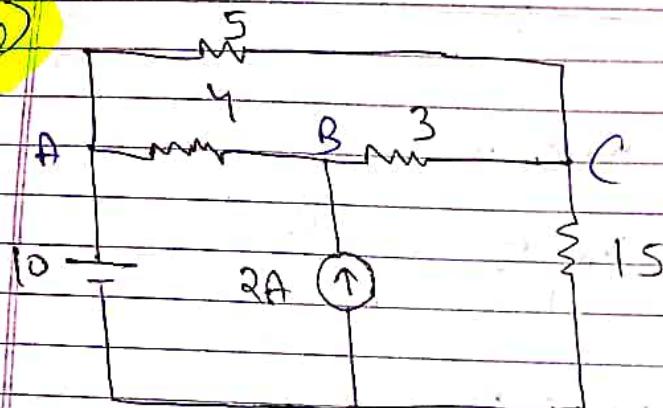

Step 1
Here R_f
calculated
Step 1

$$10 \frac{+}{-} I_1$$

Step 1) A, B, C are Nodes

at A $V = IR$ $I = \frac{V}{R}$ at volt not R give it is not taken

$$0 = \frac{V_A - V_C}{5} + \frac{V_A - V_B}{4} \quad \text{--- (1)}$$

at B

$$0 = \frac{V_B - V_A}{4} + \frac{V_B - V_C}{3} \quad \text{--- (2)}$$

at C

$$0 = \frac{V_C - V_B}{3} + \frac{V_C}{15} + \frac{V_C - V_A}{5}$$

loop 1

10 - 6 I

loop 2

-10 (I)

$$\boxed{I_2 = 0}$$

Now I

V_{TH}

$$\boxed{V_{TH}}$$


Thevenin's theorem

$$V = IR$$

$$\text{Thevenin circuit} = I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

load current

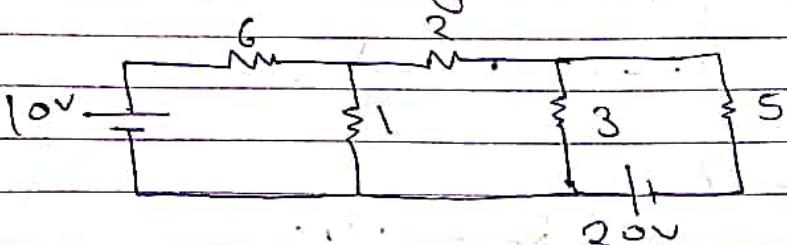- ③) Determine the current through 5Ω resistor in the network by Thevenin's Theorem.




Sol)

a) Here $R_L = 5$

① Calculation of V_{TH}

for V_{TH} finding
 R_L at open circuit

Step 1

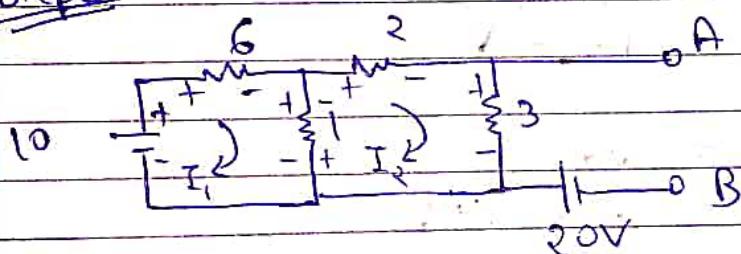

~~Short the load resistance~~

loop ①

$$10 - 6I_1 - 1(I_1 - I_2) = 0 \quad \text{--- (1)}$$

loop ②

$$-10(I_1 - I_2) + 2I_2 - 3I_2 = 0 \quad \text{--- (2)}$$

$I_2 = 0.244 \text{ A}$

downward

Now $I_{30} = 0.244 \text{ A}$



$$V_{TH} = V_{AB}$$

$$= 20 + 3I_2$$

$V_{TH} = 20.732 \text{ V}$

② Calculation for R_{TH}

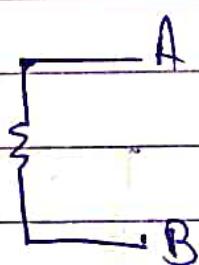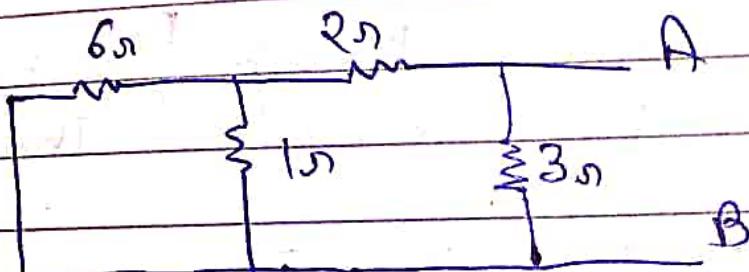Voltage \rightarrow Short Circuit
Current \rightarrow Open Circuit



$$R_{TH} = 1.46$$


③

$$\rightarrow I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$= \frac{20}{5 + 1.46}$$

$$= 3.21 \text{ A downward}$$

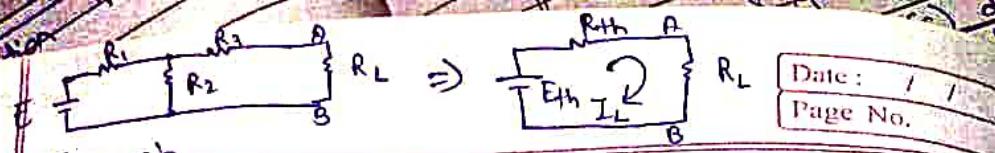④ Determine the current through 1.5 ohm resistor



Thevenin's Statement: A linear network consisting of a no. of voltage sources & resistances can be replaced by an equivalent network having a single voltage source called Thevenin voltage (V_{Th}) & a single resistance called Thevenin's resistance (R_{Th}) & load resistance (R_L).

Norton's theorem

$$I_L = \frac{I_N R_N}{R_N + R_L}$$

$$R_N = R_{Th}$$


Concept

for $I_N \Rightarrow R_L$ short circuit

— o —
open circuit


— o —
short circuit

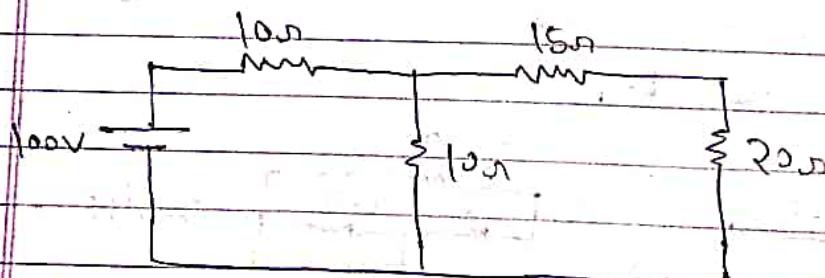- ① By Norton's theorem find current in 20Ω in the Network



(a) $R_L = 20\Omega$

Step 1 Calculation of I_N

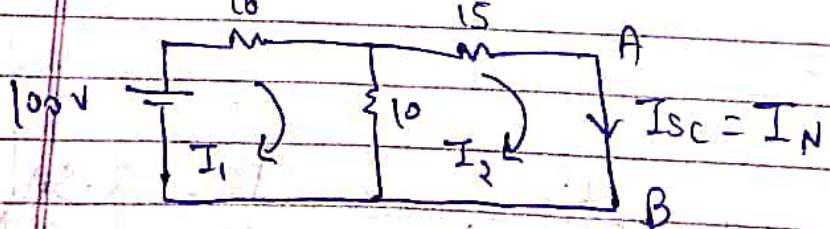

Apply KVL in Mesh ①

$$100 - 10I_1 - 10(I_1 - I_2) = 0 \quad \text{--- (1)}$$


KVL in ②

$$-10(I_2 - I_1) - 15I_2 = 0 \quad \text{--- (2)}$$

$$I_2 = 2.5A$$

$$I_N = I_{SC} = I_2 = 2.5A$$


Step 3 Calculation of R_N

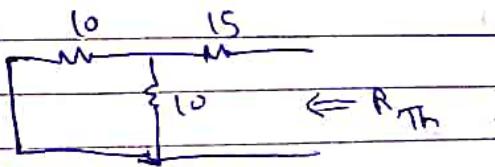


$$R_N = 20\Omega$$

$$\text{Step 3} \quad I_L = \frac{I_N R_N}{R_N + R_L}$$
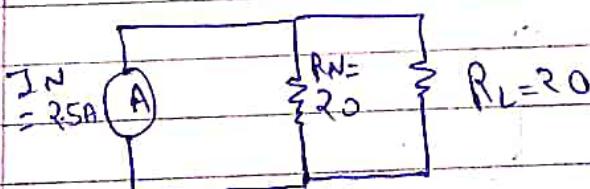
$$I_L = \frac{2.5 \times 20}{20 + 20} = 1.25A$$



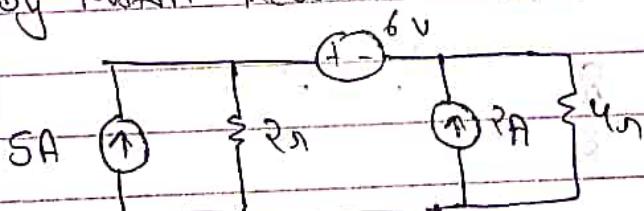Q) By Norton theorem find current in Y_N network




Norton's theorem


Any linear, active, bilateral complicated network across its load terminals can be replaced by single current source & one parallel resistance.

OR

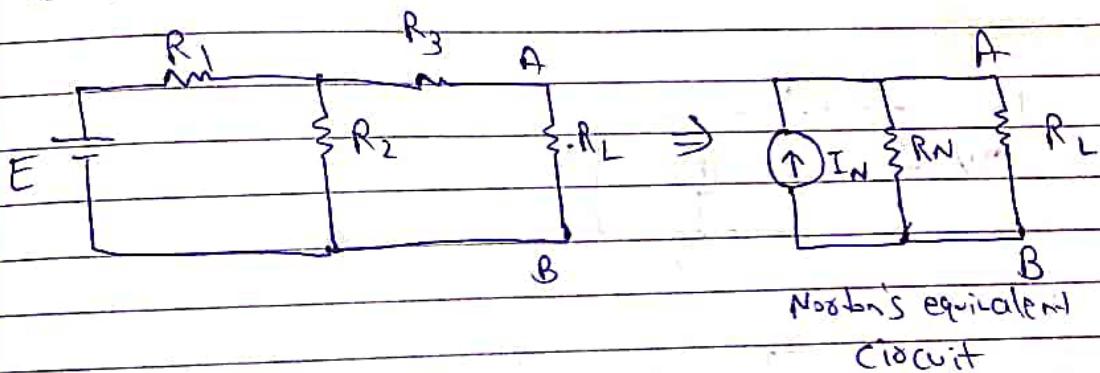
A linear network consisting of a no. of voltage source & resistance can be replaced by an equivalent network having a single current source (I_N) & a single resistance (R_N).



Source transformation

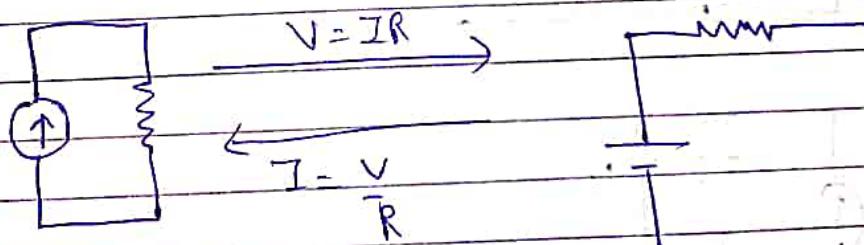


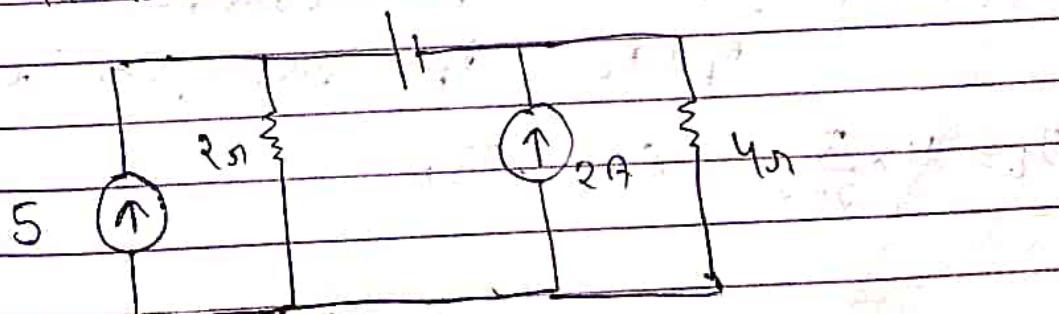- (i) By Source transformation find the current in 4Ω resistor



So)


$$R_L = 4\Omega$$

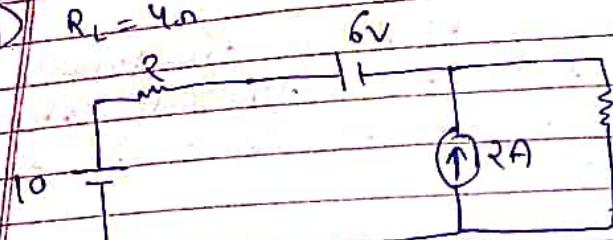




Date :

1/1/2010

DF
BE

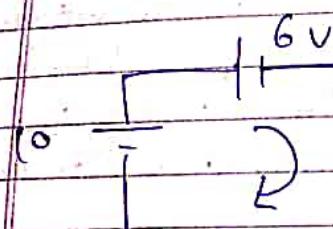

$$10 - 6 = 4V$$

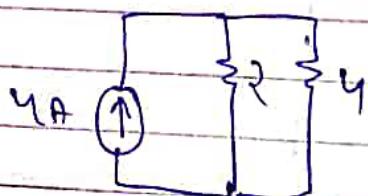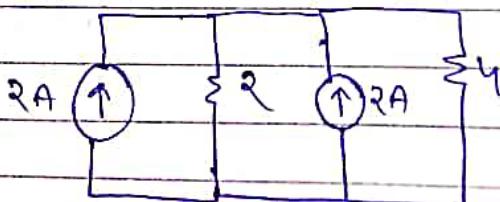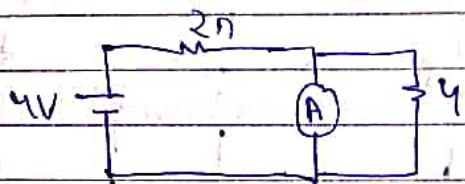

$$I_L = R_L \times \frac{R_P}{R_P + R_L}$$


R_L = Load Resist

R_P = Resist parallel to load

$$I_L = 4 \times \frac{2}{2+4} = \frac{8}{6} = 1.33A$$


Superposition Theorem

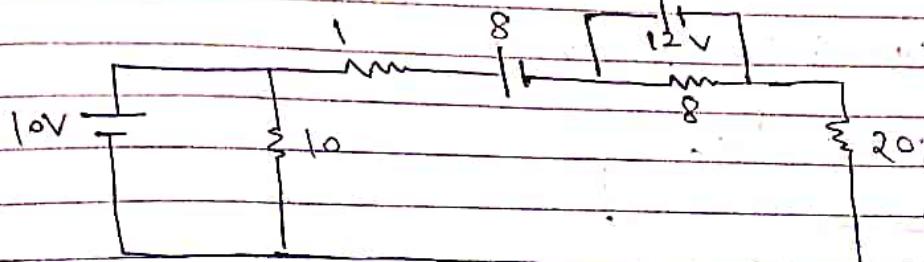- Q) Determine the current in 10Ω resistor in the network by Superposition Theorem.



Sol)
Step 1



10V Source is acting

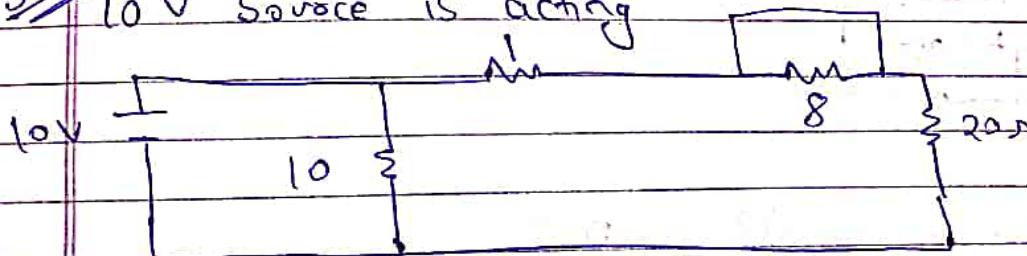

WZ

अधिक
resistance
दो साथ
होती
branch
मिशन
circuit
रिट्रॉ
Resistance
out ECL
दोनों को


8Ω resistor becomes redundant

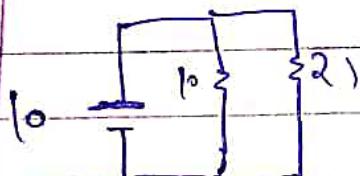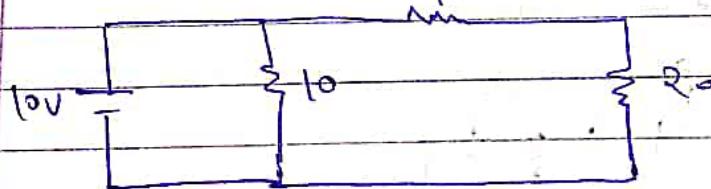


$$I_{10\Omega} = \frac{10}{2} = 0.476 \text{ A}$$

$$I_{10\Omega} = -0.476$$


Step 2 12 V acting alone

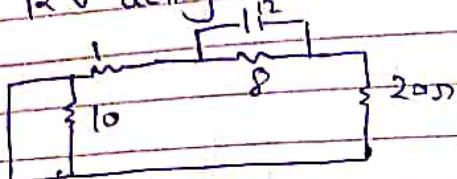

10Ω becomes redundant

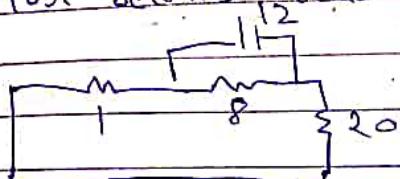


12V

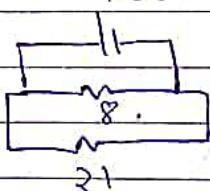


$$I = \frac{V}{R} = \frac{12}{2\Omega} = 0.5$$

Step 3 8V is acting alone

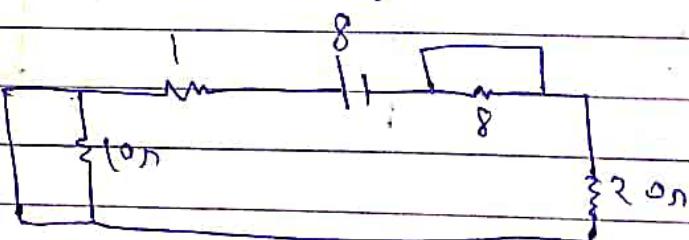

10 & 8 are redundant

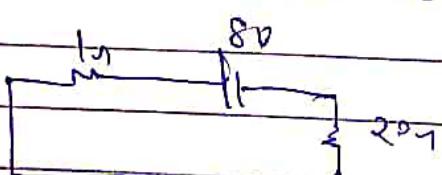

$$I = \frac{V}{R} = \frac{8}{2\Omega + 1} = 0.381 \text{ A}$$

$$I_{\text{Total}} = I_1 + I_2 + I_3$$

$$= -0.476 + 0.571 + 0.38 \\ = 0.476 \text{ A}$$

Statement

If no of voltage sources or current source acting in a linear network then the resulting current in any branch is the algebraic sum of all the current that would be produced in it when each source act alone ^{while} all the other independent source are replaced by their internal resistances.

Maximum Power Transferred theorem

$$\text{Power} = VI = I^2 R = \frac{V^2}{R}$$

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

Step 1 Calculation of R_{Th}

- ① Voltage \rightarrow Short circuit
- Current \rightarrow Open circuit


- ② $R_L \rightarrow$ open

Step 2 Calculation of V_{Th}


- ① $R_L \rightarrow$ open

- ② KVL | KCL | Ohm's

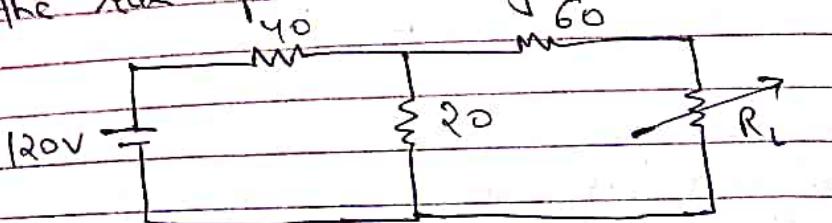Q1) Calculate the value of R_L so it to be absorbed the Max power and find the Max power through it.




S1) Calculation of R_{Th}

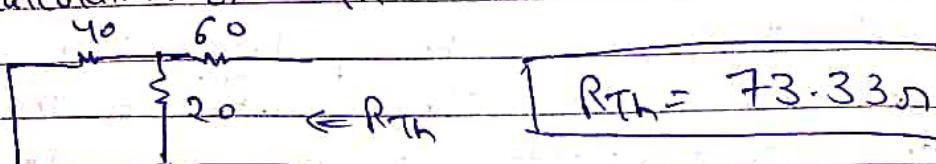

$$R_{Th} = 73.33\Omega$$

calculation of V_{Th}

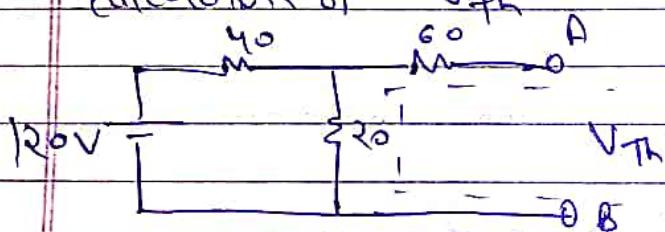

में ये 60 और 40 की दोनों ओपेरेटिंग वोल्टेज का एक साथ उपलब्ध है।

$$I = \frac{V}{R} = \frac{20}{60} = \frac{1}{3} A$$


$$V_{Th} = V_{AB}$$

$$= 2 \times 20 = 40 V = [V_{Th} = 40 V]$$

$$P_{Max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{40 \times 40}{4 \times 73.33} = 5.45 W$$

$$P_{Max} = 5.45 W$$

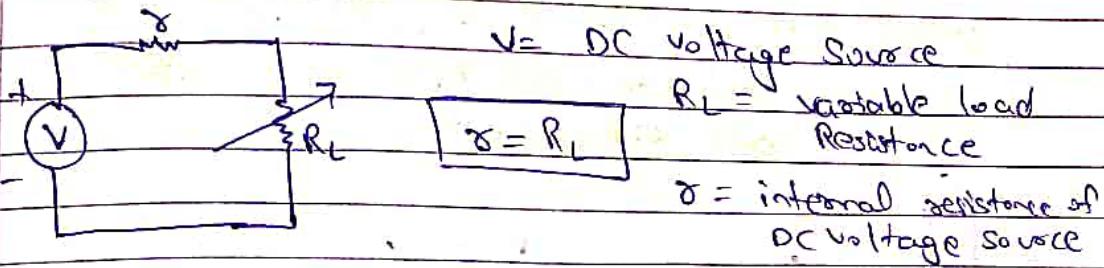Statement (Max power transferred theorem)
 It states that the DC voltage source will deliver Maximum power to the variable load resistance only when the load resistance is equal to the source resistance.



Let I_L be the current flowing through load resistor R_L

$$I_L = \frac{V}{r + R_L} \quad (\text{Ohm's law}) \rightarrow ①$$

Power transferred to the load resistance (R_L) is

$$P_L = I_L^2 R_L$$

$$P_L = \left(\frac{V}{r + R_L} \right)^2 R_L = \frac{V^2 R_L}{(r + R_L)^2} \rightarrow ②$$

For P_L to be Maximum $\frac{dP_L}{dR_L} = 0$

$$\Rightarrow 0 = V^2 \left[(r + R_L)^2 \cdot 1 - R_L \cdot 2(r + R_L) \cdot 1 \right] / (r + R_L)^4$$


$$r = R_L \quad \text{cancel}$$

$$P_L = \frac{V^2 R_L}{(r + R_L)^2}$$

$$(P_L)_{\text{Max}} = \frac{V^2 r}{(r + r)^2} = \frac{V^2 r}{4r^2} = \frac{V^2}{4r} \quad \text{Power}$$

Time Domain Analysis of 1st ordered RC circuit (for charging of capacitor)

RC circuit

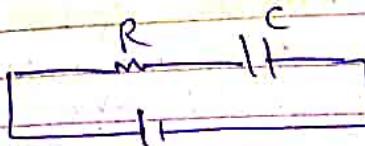


1st order circuit \rightarrow यहाँ का circuit तभी होता है जबकि विद्युतीय energy को store करने वाले device रखा गया है।

C

$t=0 \quad q=0$
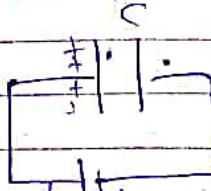
$$\begin{aligned} Q &= CV \\ V &= 0 \end{aligned}$$



$t=f \quad q=q$


$$Q = CV$$

$$V = \frac{Q}{C} = \frac{q}{C} = V$$

with respect to time

the study of charge, current,

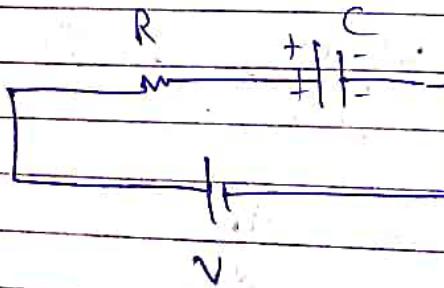voltage is known as Time Domain analysis.



$$\Delta V = iR$$

$$i = \frac{\Delta V}{R}$$

$$i = \frac{V - \frac{q}{C}}{R}$$

$$i = \frac{CV - q}{RC}$$

$$dq = \frac{CV - q}{RC} dt$$

Date : / /
Page No.

$$\frac{dq}{CV-q} = \frac{dt}{RC}$$

$$\Rightarrow \int_0^q \frac{dq}{CV-q} = \int_0^t \frac{dt}{RC}$$

$$\Rightarrow \left[\ln(CV-q) \right]_0^q = \left[\frac{t}{RC} \right]_0^t$$

$$\ln(CV-q) - \ln(CV) = -\frac{t}{RC}$$

$$\ln \left(\frac{CV-q}{CV} \right) = -\frac{t}{RC}$$

$$1 - \frac{q}{CV} = e^{-t/RC}$$

$$\frac{q}{CV} = 1 - e^{-t/RC}$$

$$q = q_0 \left(1 - e^{-t/RC} \right)$$

Max charge

$$q = q_0 \left(1 - e^{-t/\tau} \right)$$


$$\tau = RC$$

$$q = q_0 [1 - e^{-1}]$$

$$q = q_0 (1 - 0.37)$$

$$q = 0.639 q_0$$

$$q = q_0 0.639$$

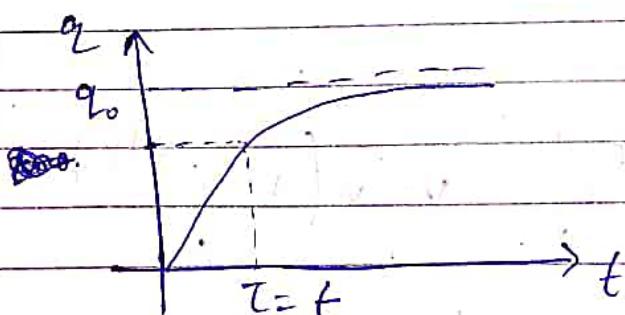

$$i = \frac{dq}{dt}$$

$$i = \frac{d}{dt} [q_0 (1 - e^{-t/RC})]$$

$$i = \frac{q_0}{RC} e^{-t/RC}$$

$$i = \frac{CV}{RC} e^{-t/RC}$$

$$q = CV$$

$$i = \frac{V}{R} e^{-t/RC}$$


$$i = i_0 e^{-t/RC}$$

$$i = i_0 e^{-t/\tau}$$

$$\tau = RC$$

$$i = i_0 e^{-t}$$

$$i = 0.37 i_0$$

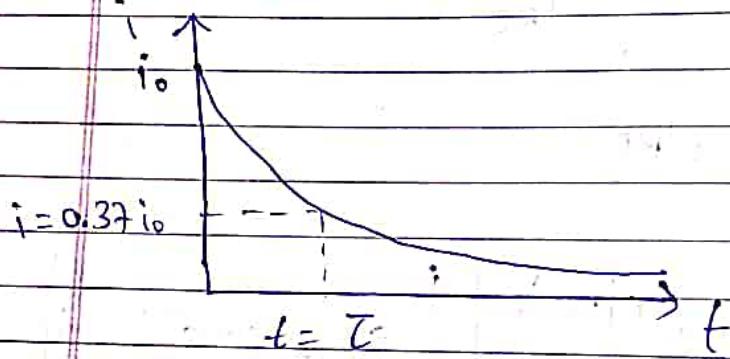

$$V = \frac{q}{C}$$


$$V = q_0 (1 - e^{-t/RC})$$

$$V = V_0 (1 - e^{-t/RC})$$

$$V = V_0 (1 - e^{-t/\tau})$$

$$t = \tau$$


$$q = 0$$

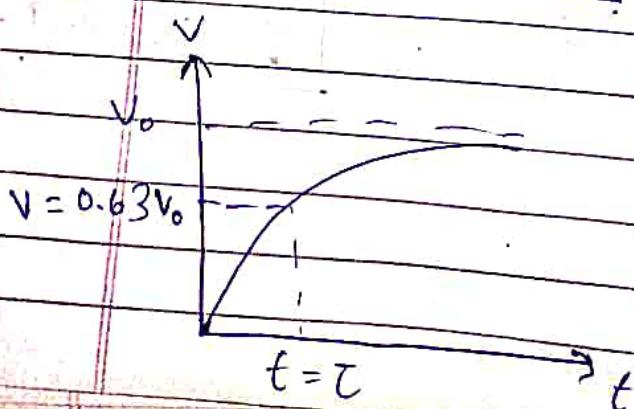

$$V = 0.63V_0$$

$$V = V_0 0.63$$

Discharging of Capacitor

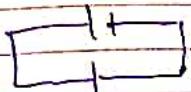

$$t=0 \quad q=0$$

$$t=t \quad q=q$$

$$t=\infty \quad q=q_{\max}$$

Here

$$t=0 \quad q=q_{\max}$$

$$t=t \quad q=q$$

$$t=\infty \quad q=0$$

$$V = iR$$

$$i = \frac{V}{R}$$

$$i = \frac{\frac{q}{R}}{R} = \frac{q}{RC}$$

$$-\frac{dq}{dt} = \frac{q}{RC}$$

$$-\int_{q_0}^{\frac{q}{q}} \frac{dq}{q} = \int_{t=0}^{t=t} \frac{dt}{RC}$$


$$q_0 \quad t=0$$

$$q = q_0 e^{-t/RC}$$

$$q = q_0 e^{-t/RC}$$

$$t=T$$

$$q$$

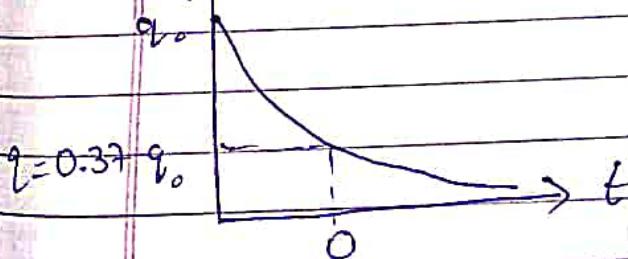

$$q = q_0 e^{-t/RC}$$

$$q = 0.37 q_0$$

$$i = -\frac{dq}{dt}$$

$$i = -\frac{dq}{dt}$$

$$e^{-t} = 0.37$$

$$i = \frac{d}{dt} (q_0 e^{-t/RC})$$


$$i = -q_0 e^{-t/RC} \times -\frac{1}{RC}$$

$$i = \frac{q_0}{RC} e^{-t/RC}$$

$$i = i_0 e^{-t/RC}$$

$$i = i_0 e^{-t/RC}$$

$$i = 0.37 i_0$$

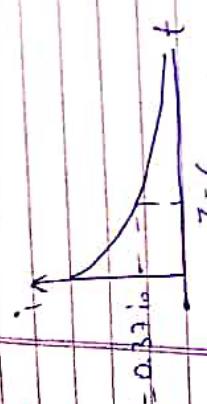

$$V = i R$$

$$V = i_0 e^{-t/RC} \times R$$

$$V = V_0 e^{-t/RC} \times R$$

$$V = V_0 e^{-t/RC} \quad V_0 = V_0 e^{-t/RC}$$

$$t = ?$$

$$V = 0.37 V_0$$

at

$t = ?$

so


$$C=0 \quad i=0$$

$$t=f \quad i=i$$

$$-iR = 0$$

$$+V - L \frac{di}{dt} = 0$$
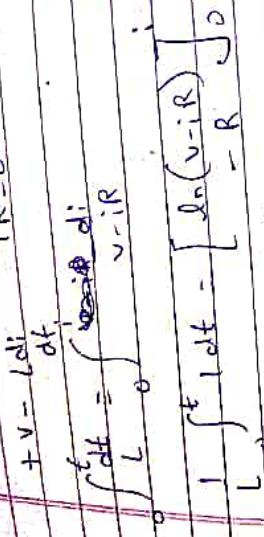
$$\int L \frac{di}{dt} dt = \int V - iR dt$$




$$i = i_m \left(1 - e^{-\frac{Rt}{L}}\right)$$

$$\frac{i}{i_m} = 1 - e^{-\frac{Rt}{L}}$$

$$\frac{t}{T} = \frac{Rt}{L}$$

$$T = \frac{L}{R}$$

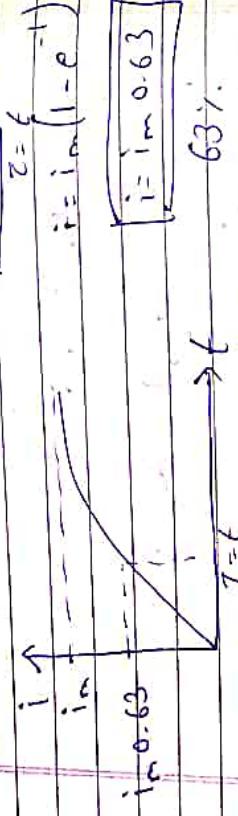


T is a time when the current grows in inductor
its value is equal to 63% of its Max Value

(a) A coil having a resistance of 20Ω and

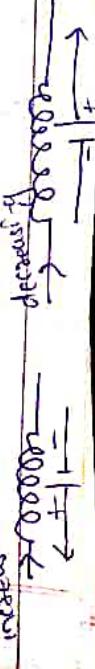- (b) Inductance of $1H$ is connected to a constant supply voltage & source of $100V$. Find
- Rate of change of current at the instant of closing the switch
 - Focal steady value of current
 - Time constant

- Time taken for current to reach a value of $4A$
- Time taken for current to reach a value of $0.37 i_m$

- Time taken for current to reach a value of $0.63 i_m$
- Time taken for current to reach a value of $0.9 i_m$



(Q1) $R = 20\Omega$

$L = 12\text{H}$

$V = 100\text{V}$

charging case Σ because battery E

$$i = i_m (1 - e^{-t/\tau})$$

i) $V = L \frac{di}{dt}$

$$\frac{di}{dt} = \frac{V}{L} = \frac{100}{12} = 8.33 \text{ A/sec}$$

ii) $V = iR$

$$i_m = \frac{V_m}{R}$$

$$i_m = \frac{V}{R} = \frac{100}{20} = 5 \text{ Ampere}$$

iii) $\tau = \frac{L}{R}$

$$\tau = \frac{12}{20} = 0.6$$

iv)

$$i_m = 5$$

$$i = 4$$

$$4 = 5 (1 - e^{-t/\tau})$$

$$4 = 5 (1 - e^{-t/0.6})$$