

Truth table of full adder

Inputs			Outputs	
A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

K-map for Sum

A \ BC				
	00	01	11	10
0	0	1	3	2
1	1	4	5	6

$$\begin{aligned}
 S &= A\bar{B}\bar{C}_{in} + \bar{A}B\bar{C}_{in} + \bar{A}\bar{B}C_{in} \\
 &= C_{in}(A\bar{B} + \bar{A}B) + \bar{C}_{in}(\bar{A}\bar{B} + A\bar{B}) \\
 &= C_{in}(\overline{A \oplus B}) + \bar{C}_{in}(A \oplus B)
 \end{aligned}$$

Experiment 3(A)



DATE _____

PAGE 7

Aim: To verify the operation of full adder.

Apparatus: Bread Board, connecting wires, power supply, IC 7408, 7486, 7432, LED display board.

Theory: It is a logic gate circuit that outputs three binary digits as its input and generates two output i.e. sum and carry inputs from previous stage.

$$\begin{aligned}\text{Sum} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\ &= A \oplus B \oplus C\end{aligned}$$

$$\text{Carry} \Rightarrow \text{Cout} = BC + AC + AB$$

Full adder output is sum + carry Out
i.e. $\Rightarrow (A \oplus B \oplus C) + (AB + BC + AC)$

Procedure:

- Connect circuit diagram as per the circuit diagram.
- Input IC's on bread board.
- Give V_{cc} & ground to all IC's
- Verify the truth table.

Let,

$$A \oplus B = \chi$$

$$= C \ln \bar{x} + \bar{C} \ln x$$

$$= x + C_1 n$$

$$S = A \oplus B \oplus C_{in}$$


k-map for Carry

$$C_{out} = B C_{in} + A C_{in} + \overline{A} B$$

$$= A\bar{B}Cin + ABCin + ABCint + A\bar{B}\bar{C}in$$

$$= C_{in}(\overline{A}B + A\overline{B}) + AB(C_{in} + \overline{C}_{in})$$

$$C_{out} = AB + C_{in}(A \oplus B)$$

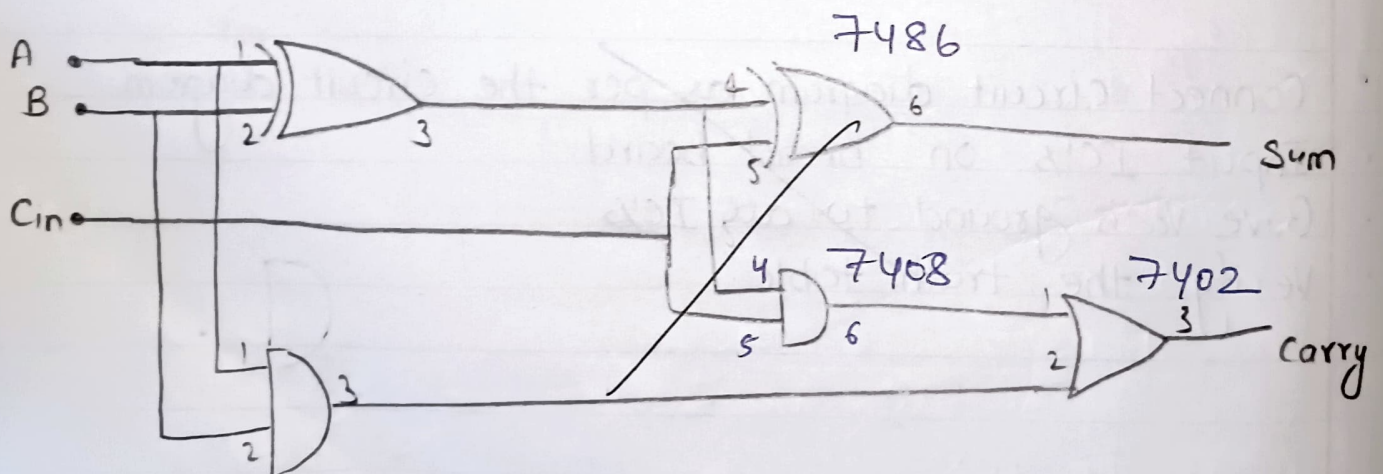



Result: operation of full adder has been verified.

Precautions: • Input the IC carefully in bread board without damaging.

• Switch off bread board when not in use.

abir