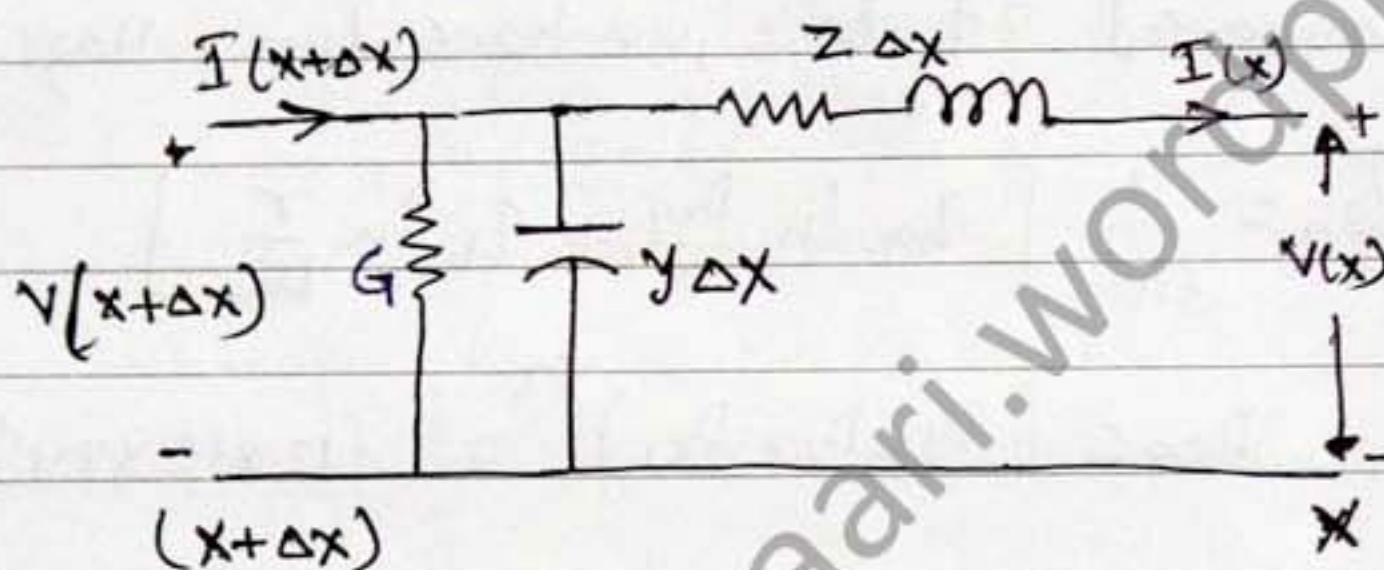


TRANSMISSION LINE MODELINGLesson Summary:

1. Distributed Vs Lumped parameter model
2. Short line Model
3. Medium line Model
4. Long line Model
5. Voltage Regulation



A transmission line is cutted with length Δx .
Let $Z = \text{Impedance/unit length}$.

For 60Hz line G is negligible. So, we neglect conductance.

Lumped Parameter model:

For Sinusoidal waves on overhead lines


$$\lambda = \frac{c}{f} \quad \text{where } c = 3 \times 10^8 \text{ m/s.}$$

for 50Hz frequency $\lambda = 6000 \text{ km}$.

So, for 6000km long transmission line distributed effect is considered

→ When the line length is $< 250 \text{ km}$ then one can neglect the distributed effect and in this case distributed network can be considered as lumped n/w i.e., we can make the lumped network of distributed n/w when transmission line $< 250 \text{ km}$ otherwise not.

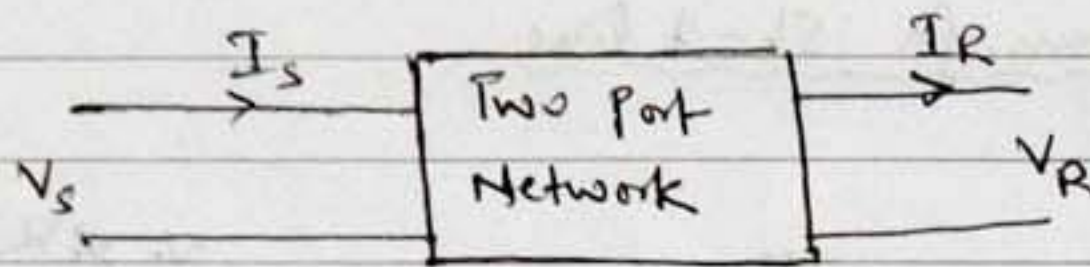→ Once we make lumped parameter n/w then ~~it will be~~ we can consider this transmission line like Two port Network.



$$V_s = AV_R + BI_R \quad \text{Volts}$$

$$I_s = CV_R + DI_R \quad \text{Ampere}$$


$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} \quad \boxed{AD - BC = 1}$$

→ For transmission line $< 80\text{km}$ long, we neglect the effect of capacitance bcoz the charging current is not very large. Also these lines are medium/low voltage lines so capacitive effect can be neglected.

SHORT LINE MODEL

- Line Length $< 80\text{km}$
- Generally Medium/Low voltage lines
- Capacitance can be neglected.

$$Z = (R + j\omega) \cdot l$$

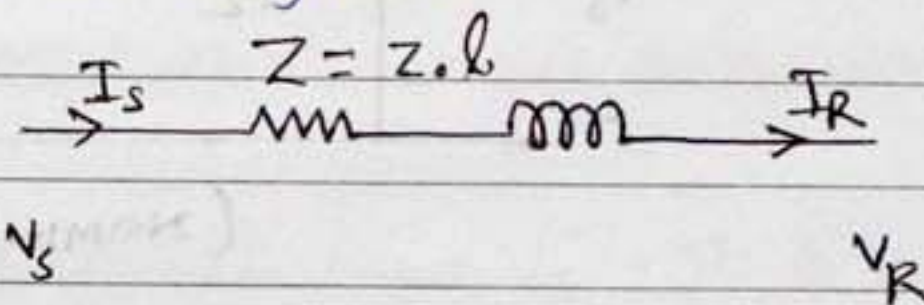

From this circuit, $I_s = I_R$.

$$V_s = V_R + Z I_R$$

$$I_s = I_R$$

$l = \text{Length of F.L.}$

$Z = \text{Impedance/length}$


$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$A = D = 1 \text{ per unit}$$


$$B = Z \Omega$$

$$C = 0 \Omega^{-1}$$

Phasor diagram for short line

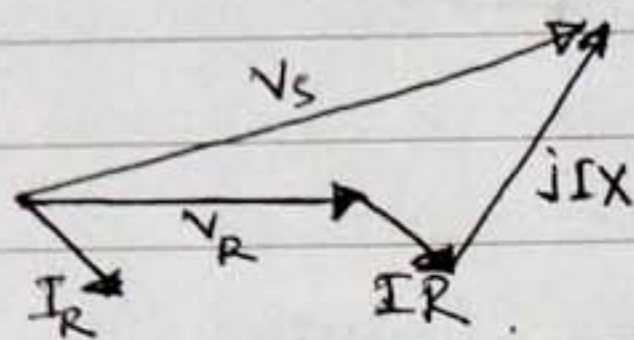

(Lagging P.f.)

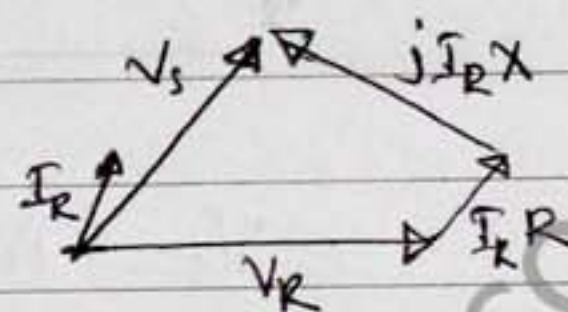


(Leading P.f.)

→ In case of Leading P.f. the sending end voltage magnitude ~~may~~ ^{can} be lower than receiving end voltage magnitude.

→ For short line $V_s = V_R$ at No Load. (bcoz $I_R = 0$)

MEDIUM LINE MODEL

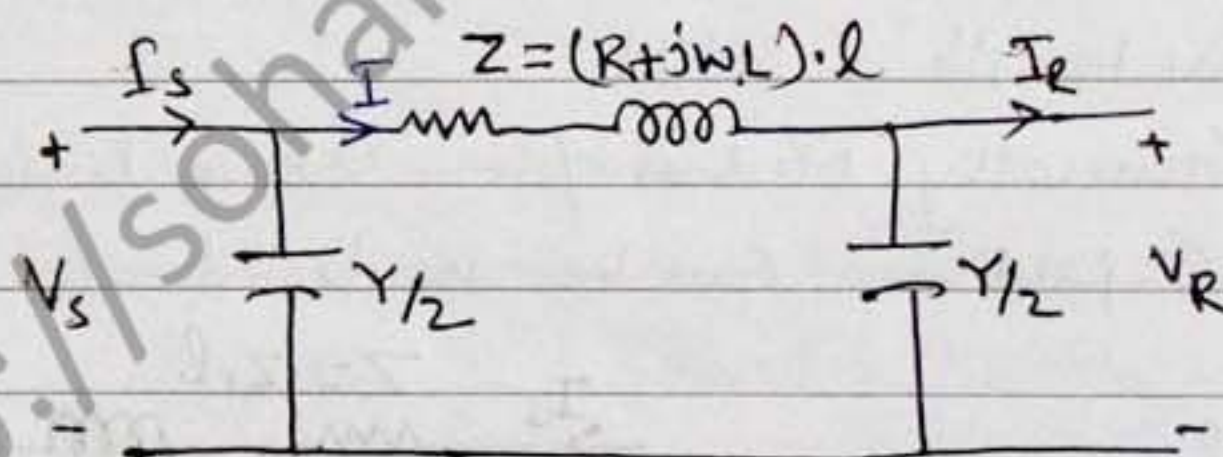- $80\text{KM} < \text{length} < 250\text{KM}$
- Capacitance can't be Neglected
- EHV or HV lines.



(NOMINAL π Circuit)

$$V_s = V_R + IZ = V_R + (I_R + V_R Y/2) Z$$

$$V_s = \left(1 + \frac{ZY}{2}\right) V_R + Z I_R$$

$$\begin{aligned} I_s &= I_R + V_R \frac{Y}{2} + V_s \frac{Y}{2} \\ &= I_R + V_R \frac{Y}{2} + \left(\left(1 + \frac{YZ}{2}\right) V_R + I_R Z \right) \frac{Y}{2} \end{aligned}$$

$$I_s = Y \left(1 + \frac{YZ}{4}\right) V_R + \left(1 + \frac{YZ}{2}\right) I_R$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 + YZ/2 & Z \\ Y(1 + \frac{YZ}{4}) & (1 + \frac{YZ}{2}) \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$A = D = 1 + YZ/2 \quad \text{Per unit}$$

$$B = Z \, \Omega$$

$$C = Y(1 + \frac{YZ}{4}) \, \text{S or } \Omega^{-1}$$

VOLTAGE REGULATION

It tells us how much the voltage drop in the transmission line in terms of rated voltage or sending end voltage.

$$\%VR = \frac{|V_{R(\text{no load})}| - |V_{R(\text{full load})}|}{|V_{R(\text{full load})}|} \times 100$$

For short line $V_{R(\text{no load})} = V_s$.

For medium line $V_{R(\text{no load})} = AV_s$


→ While designing a transmission line we must take care of VR i.e. VR must be less than 8-10%.

→ For leading P.f., V_R may be greater than V_s . If it becomes very high then it may damage the insulator of transmission line.

ABCD Matrix

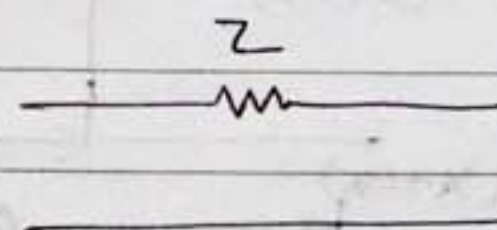
(a) Series Impedance

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$




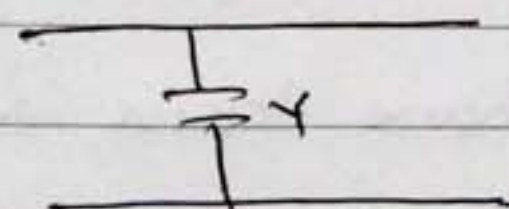(b) Shunt Admittance


$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$



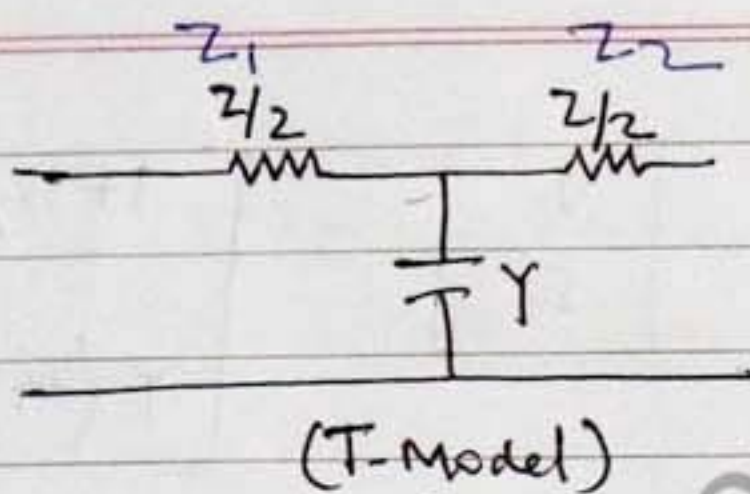
$$\begin{bmatrix} 1+YZ_1 & Z_1+Z_2+YZ_1Z_2 \\ Y & 1+YZ_2 \end{bmatrix}$$


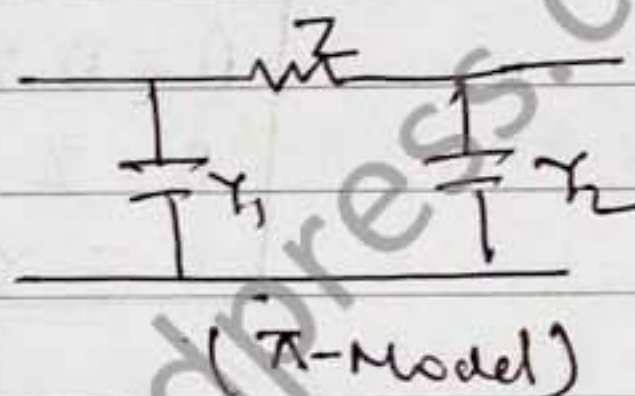
$$\begin{bmatrix} 1+Y_2Z & Z \\ Y_1+Y_2+Y_1Y_2Z & 1+Y_1Z \end{bmatrix}$$



$$AD-BC=1$$

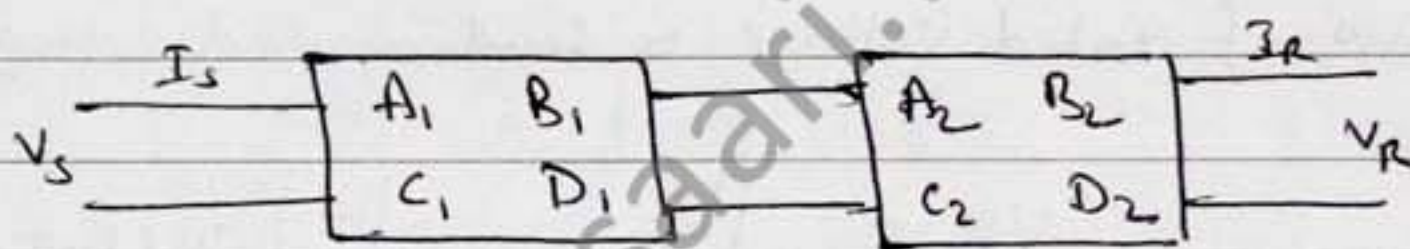


Cascaded n/w.

$$\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} = \begin{bmatrix} (A_1A_2+B_1C_2) & (A_1B_2+B_1D_2) \\ (C_1A_2+D_1C_2) & (C_1B_2+D_1D_2) \end{bmatrix}$$

LONG LINE MODEL

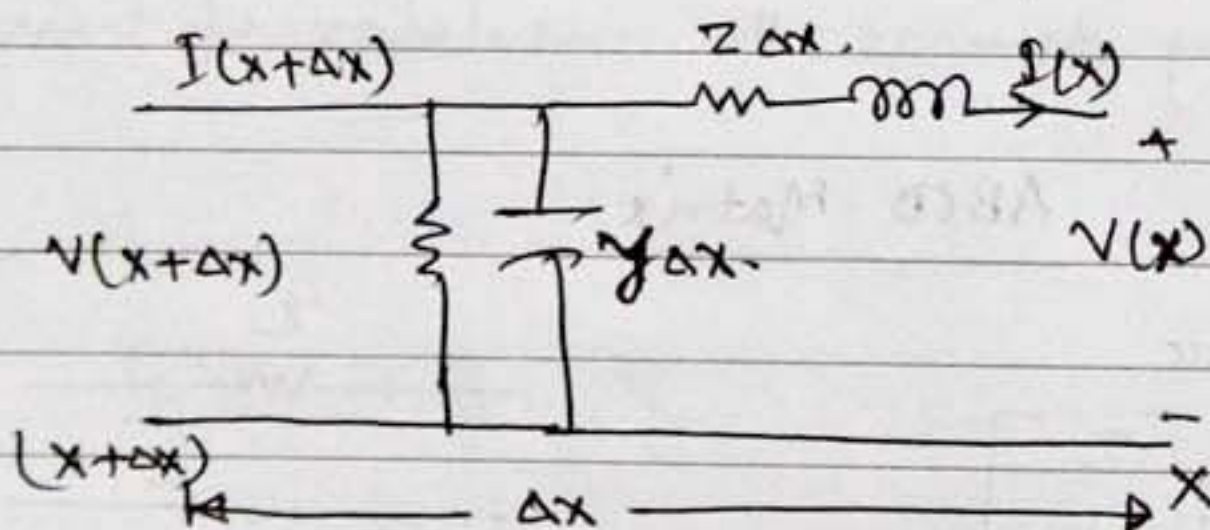- Distributed Effect can't be Neglected bcoz T.L. > 250km.
- We can't use Lumped Model



(Distributed Parameter Model)

- We have taken a section of transmission line for operation.
- Conductance is neglected for 50-60Hz transmission line

Let voltage at a distance x from receiving end = $V(x)$

Let voltage at a distance $(x+\Delta x)$ from receiving end = $V(x+\Delta x)$

By using KVL.

$$V(x+\Delta x) = V(x) + I(x) Z \Delta x.$$

$$Z I(x) = \frac{V(x+\Delta x) - V(x)}{\Delta x} = \frac{dV(x)}{dx}$$

$$Z I(x) = \frac{dV(x)}{dx} \quad \text{--- (I)}$$

By KCL

$$I(x+\Delta x) = I(x) + V(x+\Delta x) Y \Delta x.$$

$$V(x+\Delta x) Y = \frac{I(x+\Delta x) - I(x)}{\Delta x} = \frac{dI(x)}{dx}$$

Taking $\lim_{\Delta x \rightarrow 0}$, we have $V(x+\Delta x) = V(x)$.

$$\therefore Y V(x) = \frac{dI(x)}{dx} \quad \text{--- (II)}$$

~~For~~ Differentiating (I) w.r.t x .

$$\frac{d^2 V(x)}{dx^2} = Z \frac{dI(x)}{dx} = Z Y V(x).$$

$$\boxed{\frac{d^2 V(x)}{dx^2} - Z Y V(x) = 0.}$$

$$\boxed{V(x) = A_1 e^{yx} + A_2 e^{-yx} \text{ volts}}$$

$$y = \sqrt{ZY} \text{ m}^{-1}.$$

$$\frac{dV(x)}{dx} = A_1 y e^{yx} - y A_2 e^{-yx} = Z I(x).$$

$$I(x) = \frac{A_1 e^{yx} - A_2 e^{-yx}}{(Z/Y)}$$

$$\boxed{I(x) = \frac{A_1 e^{yx} - A_2 e^{-yx}}{Z_c}}$$

Where $Z_c = Z/Y$
Characteristic Impedance

$$\text{Characteristic Impedance} = \frac{Z}{\gamma} = \frac{Z}{\sqrt{ZY}} = \sqrt{\frac{Z}{Y}} \Omega$$

γ → Gamma Y → Admittance

$$Z_c = \sqrt{\frac{Z}{Y}} \Omega$$

→ Using Boundary condition.

$$\text{At } x=0 \quad V(0) = V_R$$

$$I(0) = I_R$$

$$\therefore V_R = A_1 + A_2$$

$$I_R = \frac{A_1 - A_2}{Z_c}$$

$$\therefore A_1 = \frac{V_R + Z_c I_R}{2}, \quad A_2 = \frac{V_R - Z_c I_R}{2}$$

$$\therefore V(x) = \left(\frac{V_R + Z_c I_R}{2} \right) e^{\gamma x} + \left(\frac{V_R - Z_c I_R}{2} \right) e^{-\gamma x}$$

γ → Gamma

$$V(x) = \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) V_R + Z_c \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) I_R$$

$$V(x) = \cosh(\gamma x) V_R + Z_c \sinh(\gamma x) I_R$$

$$I(x) = \frac{1}{Z_c} \sinh(\gamma x) V_R + \cosh(\gamma x) I_R \quad (\gamma = \text{Gamma})$$

$$\begin{bmatrix} V(x) \\ I(x) \end{bmatrix} = \begin{bmatrix} A(x) & B(x) \\ C(x) & D(x) \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

At sending end $x=l$.

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{aligned} A &= D = \cosh(\gamma l) \text{ Per unit} \\ B &= Z_c \sinh(\gamma l) \Omega \\ C &= \frac{1}{Z_c} \sinh(\gamma l) S \end{aligned}$$

γ → Gamma