

Combinational ckt

- PROM → Programmable ROM
- ✓ - PAL → Programmable Array logic
- ✓ - PLA → Programmable Logic Array
- ✓ - ALU → Arithmetical logical unit

Data

- Binary, Hex, Octal

PLA

- Programmable logic array

Truth table

A	B	C	$Y_1$	$Y_2$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1



$$Y_1 = A \bar{B} \bar{C} + A \bar{B} C + A B C$$

$$Y_1 = A \bar{B} + A C$$


$$\boxed{\begin{array}{l} Y_1 = A \bar{B} + A C \\ Y_2 = \bar{B} C + A C \end{array}}$$


no of functions

(I) No of I/P buffer

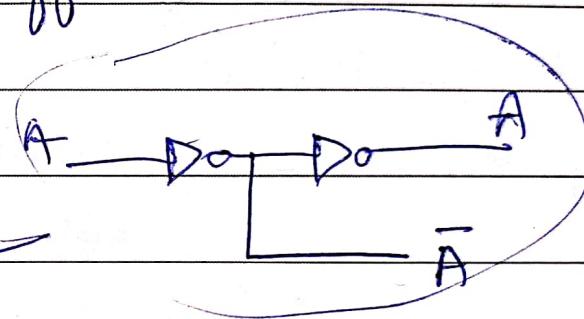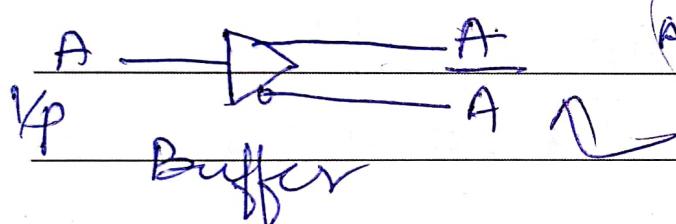


No of I/P buffers = 3

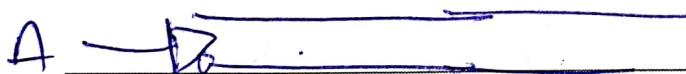

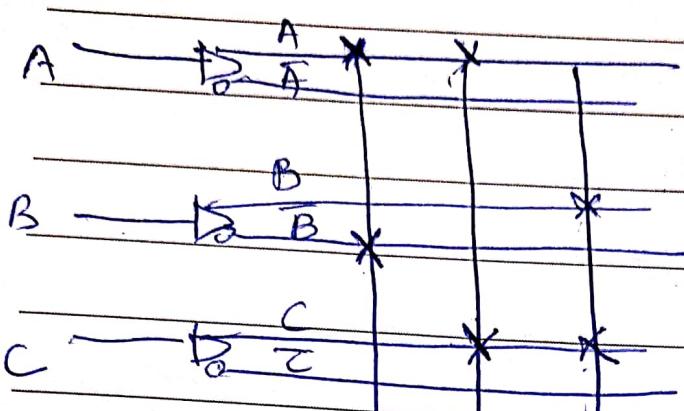

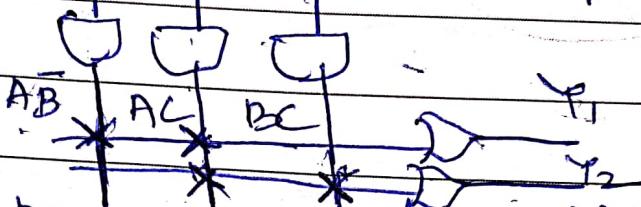Full implementation  
of  
boolean  
functions  
using  
PLA



II

No of programmable AND gates = No of minterms which are not repeated = 3

$$AB, AC, BC$$

IV

No of programmable OR gates =

$$\text{No of functions} = Y_1 \cdot Y_2 = 2$$

$$Y_1 = AB + AC$$

$$Y_2 = BC + AC$$

PLA  $\left[ \begin{array}{l} \text{programmable AND array} \\ \text{programmable OR array} \end{array} \right]$

TM: Trademark are under license from SIGNUTRA INC., USA

### P A L

- Programmable Array Logic
- Programmable AND gates array
- Fixed OR gates Array

Ex - ~~X(A)~~ Given:

$$f_1(A, B, C) = \sum_m(2, 3, 5, 7)$$


$$f_2(A, B, C) = \sum_m(0, 1, 5)$$

$$f_3(A, B, C) = \sum_m(0, 2, 3, 5)$$

$$f_1(A, B, C) = \overline{A}\overline{B} + AC \quad ]^2$$

$$f_2(A, B, C) = \overline{A}\overline{B} + \overline{B}C \quad ]$$
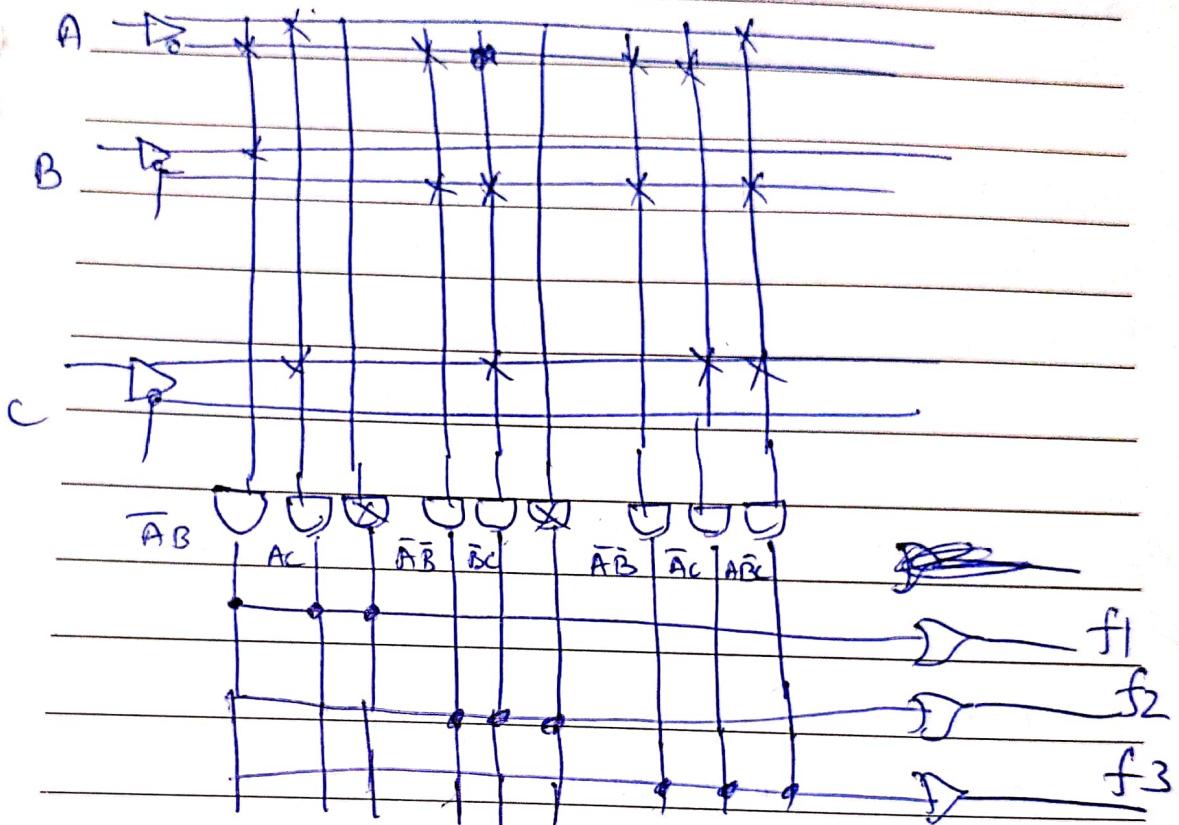
$$f_3(A, B, C) = \overline{A}\overline{B} + \overline{A}C + A\overline{B}C \quad ]^3.$$



No of OR gates = No of functions

No of AND gates in each OR gate =

No of minterms (highest)

No of input buffers = No of variables

MinimizationMethod Quine-McCluskeyQM method

- minimization method
- Prime Implicant - No of 1's
- Essential Prime Implicant - Prime implicant which can not be combined with any other.

Ex  $\Sigma m(A, B, C, D) = \Sigma m(0, 1, 3, 7, 8, 9, 11, 15)$

---

ABCD

0 - 0 0 0	M <sub>0</sub>
1 - 0 0 1	M <sub>1</sub>
3 - 0 0 1 1	M <sub>3</sub>
7 - 0 1 1 1	M <sub>7</sub>
8 - 1 0 0 0	M <sub>8</sub>
9 - 1 0 0 1	M <sub>9</sub>
11 - 1 0 1 1	M <sub>11</sub>
15 - 1 1 1 1	M <sub>15</sub>

---

Step 1column-1      column 2      column-2

Group      Minterm      Binary Representation

A    B    C    D

0 (0 1's)	M <sub>0</sub>	0 0 0 0 ✓
1 (1 1's)	M <sub>1</sub> ↗ M <sub>8</sub> ↘	0 0 0 1 ✓ 1 0 0 0 ✓
2 (2 1's)	M <sub>3</sub> M <sub>9</sub>	0 0 1 1 1 0 0 1 ✓
3 (3 1's)	M <sub>7</sub> M <sub>11</sub>	0 1 1 1 ↵ 1 0 1 1 ↵
4 (4 1's)	M <sub>15</sub>	1 1 1 1 ↵

Step 2

- ① compare  $n^{\text{th}}$  with  $(n+1)^{\text{th}}$  group
- |                     |                     |
|---------------------|---------------------|
| $0 \text{ with } 1$ | $1 \text{ with } 2$ |
| $2 \text{ with } 3$ | $3 \text{ with } 4$ |
- ② single variable change

<u>Groups</u>	<u>Matched</u>	<u>Bin. Pep.</u>
	<u>Pair</u>	<u>ABCD</u>
0	$M_0 - M_1$	000 - ✓ (D eliminated)

$M_0 - M_8$  -000 ✓ (A eliminated)

1	$M_1 - M_3$	0/0 - 1 ✓ (C eliminated)
	$M_1 - M_9$	-001 ✓ (A eliminated)
	$M_8 - M_9$	100 - ✓

2  $M_3 - M_7$  0 - 11 ✓

$M_3 - M_{11}$  -011 ✓

$M_9 - M_{11}$  10 - 1 ✓

3  $M_7 - M_{15}$  -111 ✓

$M_{11} - M_{15}$  1 - 11 -

Pair

$M_0 - M_1$  000 -

$M_1 - M_3$  006 - 1

) variables  
changing, so not  
matched  
pair

**Signutra**

signature nutrition

Step 3

Group	Matched Pairs	Binary Pep
-------	------------------	---------------

A B CD

0	M <sub>0</sub> -M <sub>1</sub> -M <sub>8</sub> -M <sub>9</sub>	-O O -
---	--	--------

	M <sub>0</sub> -M <sub>8</sub> -M <sub>1</sub> -M <sub>9</sub>	-O O -
--	--	--------

1	M <sub>1</sub> -M <sub>3</sub> -M <sub>9</sub> -M <sub>11</sub>	-O - I
---	---	--------

	M <sub>1</sub> -M <sub>9</sub> -M <sub>3</sub> -M <sub>11</sub>	-O - I
--	---	--------

2	M <sub>3</sub> -M <sub>7</sub> -M <sub>11</sub> -M <sub>15</sub>	-- II
---	--	-------

	M <sub>3</sub> -M <sub>11</sub> -M <sub>7</sub> -M <sub>15</sub>	-- II
--	--	-------

**Signutra**

signature nutrition

M<sub>0</sub>-M<sub>1</sub>

M<sub>1</sub>-M<sub>2</sub>

0 0 0  
0 0 1

2 variables change  
not matched  
pair

M<sub>0</sub>-M<sub>1</sub>

M<sub>1</sub>-M<sub>2</sub>

6 0 0  
- 0 0 1 2

2 variables

change

not

matched pair

M<sub>0</sub>-M<sub>1</sub>

M<sub>2</sub>-M<sub>3</sub>

1 0 0  
1 0 0

only 1

variable

change

#### Step 4

→ Again find matched pair.

→ But we will find that

there are no matched  
pair after that.

Group

A B C P

0

- 0 0 -

{  $\bar{B} \bar{C}$  }

- 0 0 -

1

- 0 - 1

{  $\bar{B} \bar{D}$  }

- 0 - 1

2

- - 1 1

{  $C O$  }

- If some pairs are not matched
- then write them as it is

Step 5

### Prime Implicant Table (PI Table)

P-I	Minterms involved	0	1	3	7	8	9	11	15	(given minterms)
$\bar{B}\bar{C}$	0, 1, 8, 9	(X)	X		(X)	X				EPI
$\bar{B}D$	1, 3, 9, 11			X	X		X	X		
$CD$	3, 7, 11, 15				X	(X)		X	(X)	EPI

- This table helps to find essential P-I.

- Circle those crosses which are alone in the column

$$f = \bar{B}\bar{C} + CD$$

B0 = eliminated because  
not essential  
prime implement

carry look ahead adder

CIA

- Presists the carry before it is actually calculated

A	B	Cin	Co
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Go

$$\begin{array}{r} C_2 \ C_1 \ C_0 \\ A_3 \ A_2 \ A_1 \ A_0 \\ B_3 \ B_2 \ B_1 \ B_0 \\ \hline C_3 \ S_3 \ S_2 \ S_1 \ S_0 \end{array}$$

$$C_0 = A \cdot B + (A \oplus B) \cdot C_{in}$$


(carry) (carry)

generator propagator

(G<sub>i</sub>) (P)

(No dependency on C<sub>in</sub>) (dependency on C<sub>in</sub>)

$$C_0 = G_i + P_i C_{in}$$

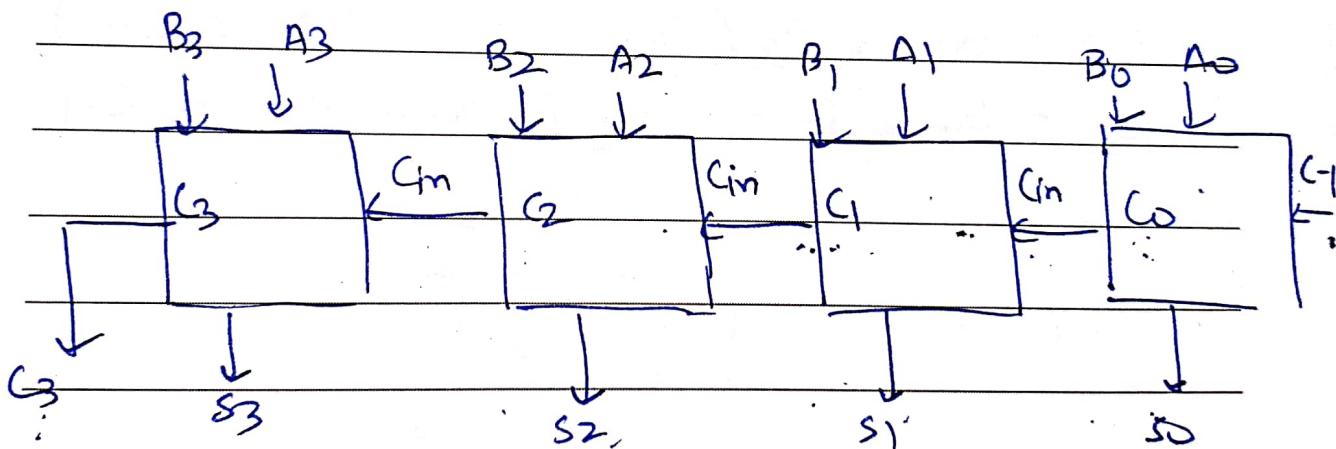

$$G_i = G_{i-1} + P_i C_{i-1} \quad (\text{Generalised form})$$

If i = 0

$$C_0 = G_0 + P_0 C_{-1} \quad (1)$$

B

If i = 1

$$C_1 = G_1 + P_1 C_0 \quad (2)$$

$$C_1 = G_1 + P_1 (G_0 + P_0 C_{-1})$$

$$= G_1 + P_1 G_0 + P_1 P_0 C_{-1}$$

(don't wait for  
any carry)

for 1st add to  
wait for  $C_0$ )


for  $i=2$  -

③

$$C_2 = G_2 + P_2 C_1$$

$$C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_{-1})$$
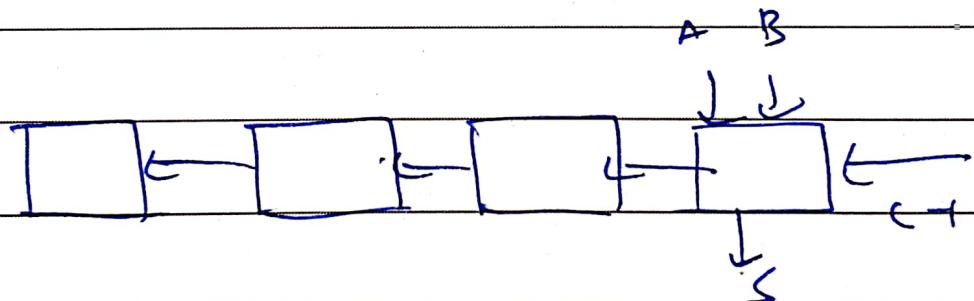
$$C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{-1}$$




for  $i=3$

$$C_3 = G_3 + P_3 C_2$$

$$C_3 = G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{-1})$$

$$C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 C_{-1}$$

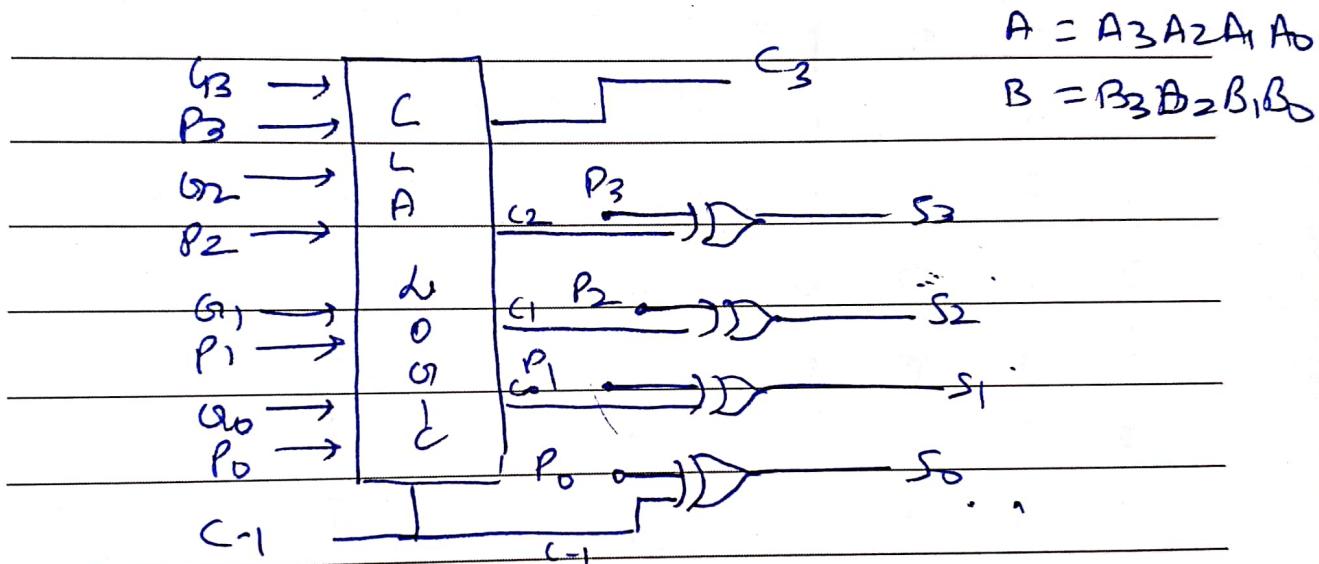All  $G_3, G_2, G_1, G_0 \Rightarrow$  All have  $C_{-1}$



$$G_3 = A_3 \cdot B_3$$

$$P_3 = A_3 \oplus B_3$$

$$P_2 = A_2 \oplus B_2$$

$$P_1 = A_1 \oplus B_1$$

$$P_0 = A_0 \oplus B_0$$

$$S_3 = P_3 \oplus G_2$$

$$= A_3 \oplus B_3 \oplus G_2$$

$$S_2 = P_2 \oplus C_1$$

$$= A_2 \oplus B_2 \oplus C_1$$

$$S_1 = P_1 \oplus C_0$$

$$= A_1 \oplus B_1 \oplus C_0$$

$$S_0 = P_0 \oplus C_{-1}$$

$$= A_0 \oplus B_0 \oplus C_{-1}$$

Even Parity Generatorany same adderParity GeneratorDesign of 4 bit even Parity Generator

$b_3$	$b_2$	$b_1$	$b_0$	$p_0$	$m$
0	0	0	0	0	0
0	0	0	1	1	1
0	0	1	0	1	2
0	0	1	1	0	3
0	1	0	0	1	4
0	1	0	1	0	5
0	1	1	0	0	6
0	1	1	1	1	7
1	0	0	0	1	8
1	0	0	1	0	9
1	0	1	0	0	10
1	0	1	1	1	11
1	1	0	0	0	12
1	1	0	1	1	13
1	1	1	0	1	14
1	1	1	1	0	15

K-map

LGB

		b <sub>1</sub> b <sub>0</sub>	$\bar{b}_1 b_0$	b <sub>1</sub> $\bar{b}_0$	$\bar{b}_1 \bar{b}_0$
		00	01	11	10
		00	1	0	1
		01	1	1	0
		11	1	1	1
		10	1	1	0
		12	1	1	1
		13	1	1	1
		14	1	1	1
		15	1	1	1
		16	1	1	1
		17	1	1	1

4 variable

K-map

(SOP)

- check board configuration

$$\begin{aligned}
 P_0 = & \bar{b}_3 \bar{b}_2 b_1 b_0 + \bar{b}_3 b_2 b_1 \bar{b}_0 \\
 & + \bar{b}_3 b_2 \bar{b}_1 \bar{b}_0 + \bar{b}_3 b_2 b_1 b_0 \\
 & + b_3 b_2 \bar{b}_1 b_0 + b_3 b_2 b_1 \bar{b}_0 \\
 & + b_3 \bar{b}_2 \bar{b}_1 \bar{b}_0 + b_3 \bar{b}_2 b_1 b_0
 \end{aligned}$$

$$\begin{aligned}
 P_0 = & \bar{b}_3 \bar{b}_2 (\bar{b}_1 b_0 + b_1 \bar{b}_0) \\
 & + \bar{b}_3 b_2 (\bar{b}_1 \bar{b}_0 + b_1 b_0) \\
 & + b_3 b_2 (\bar{b}_1 b_0 + b_1 \bar{b}_0) \\
 & + b_3 \bar{b}_2 (\bar{b}_1 \bar{b}_0 + b_1 b_0)
 \end{aligned}$$

TM: Trademark are under license from SIGNUTRA INC., USA

$$P_0 = \bar{b}_3 \bar{b}_2 (b_1 \oplus b_0) \\ + \bar{b}_3 b_2 (b_1 \odot b_0) \\ + \overline{b_3} b_2 (b_1 \oplus b_0) \\ + b_3 \bar{b}_2 (b_1 \odot b_0)$$

$$P_0 = b_1 \oplus b_0 (\bar{b}_3 \bar{b}_2 + b_3 b_2) \\ + b_1 \odot b_0 (\bar{b}_3 b_2 + b_3 \bar{b}_2)$$

$$P_0 = b_1 \oplus b_0 (b_3 \odot b_2) \\ + b_1 \odot b_0 (b_2 \oplus b_3)$$

$$P_0 = b_1 \oplus b_0 (\bar{b}_2 \oplus b_3) + (\bar{b}_1 + b_0)(b_2 \oplus b_3)$$

$$\text{let } A = b_1 \oplus b_0$$

$$B = b_2 \oplus b_3$$


$$P_0 = A \bar{B} + \bar{A} B$$

$$P_0 = A \oplus B$$

$$\text{so } P_0 = \cancel{b_3 \odot 1}$$

$$\text{so } P_0 = (b_1 \oplus b_0) \oplus (b_2 \oplus b_3)$$
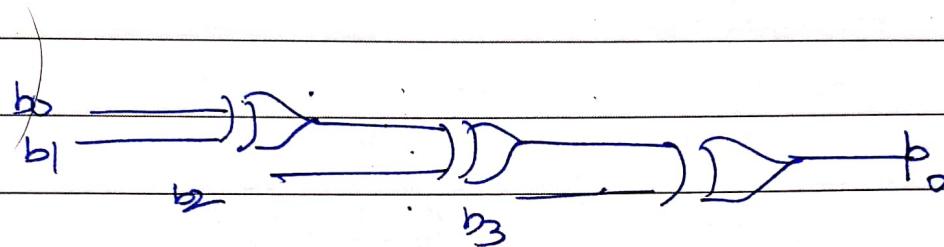
$$P_0 = b_0 \oplus b_1 \oplus b_2 \oplus b_3$$



4-Bit Even Parity

Generator


ALU

## Arithmetic logic Unit

- Arithmetic operations
  - Logic operations

35

$$S = 0$$

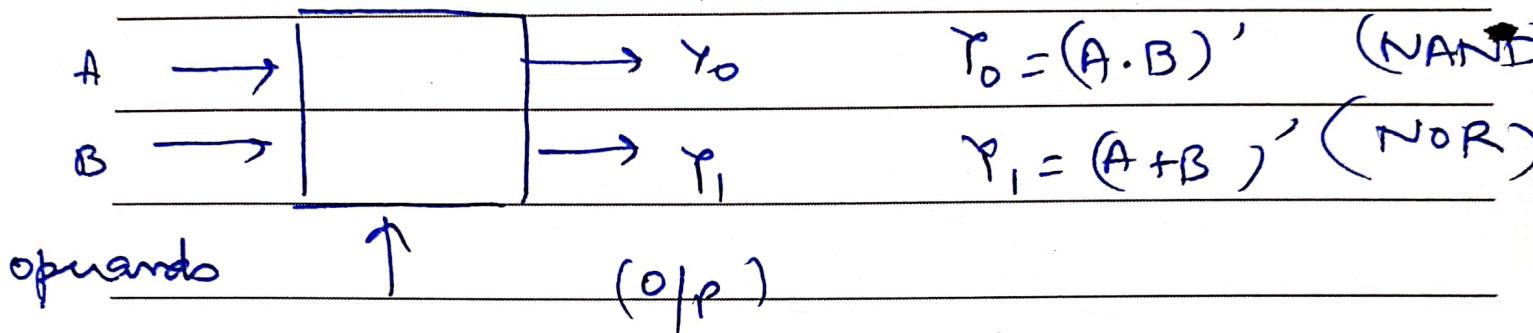

S  
Select  
Y/P

21

S = 1

$$Y_0 = \overline{A}B + A\overline{B}$$

(sum bit of HA)

$$Y_1 = A \ B$$


(Lazy bit of HA)

$$Y_0 = \bar{s} (A \cdot B)' + s (A+B)'$$

$$\gamma_1 = \bar{s}(\bar{A} + B)' + s(A\bar{B})$$

Function Table

$S_1$	$S_0$	$Cin$	$Y$	$P$
0	0	X	$Y = (A \cdot B)'$	(NAND)
0	1	X	$Y = (A + B)'$	(NOR)
1	0	0	$Y = A$	
1	0	1	$Y = A \text{ PLUS } 1$	
1	1	0	$Y = A \text{ PLUS } B$	
1	1	1	$Y = A \text{ PLUS } B \text{ PLUS } 1$	

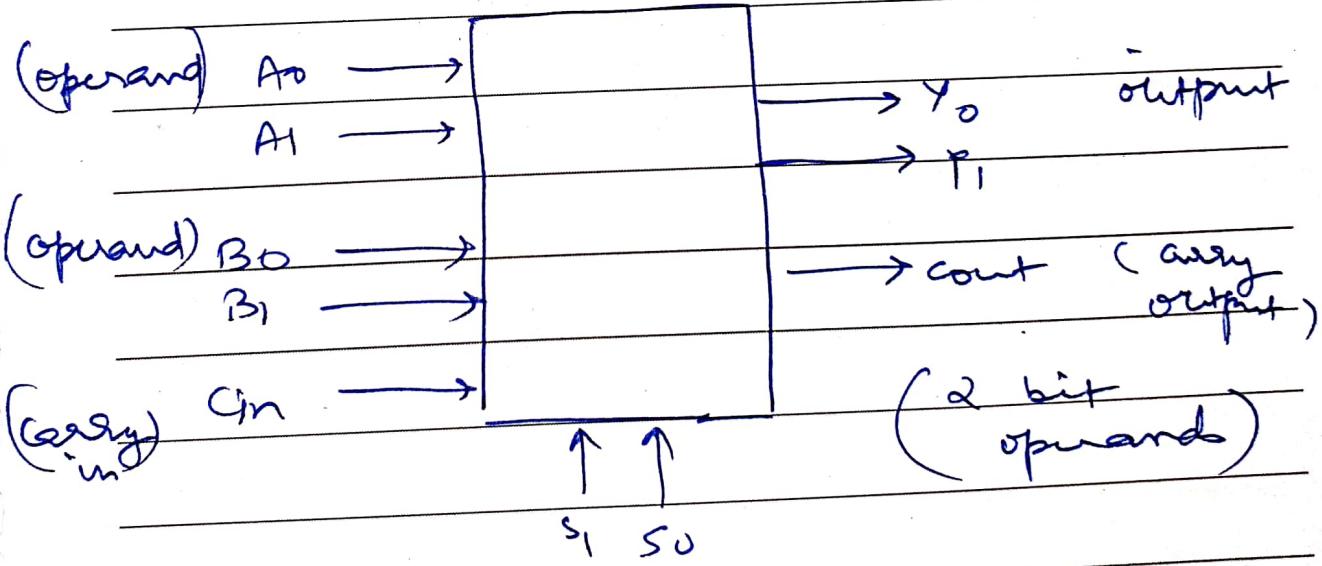

logic operation: Bitwise

Arithmetic operation: 2 bit Number

$\bar{A}o\bar{B}o \quad A\bar{o}Bo \quad Ao\bar{B}o \quad A\bar{o}\bar{B}o$

$S_1 S_0$	1	1	0	1
$S_1 S_0$	1	0	0	0
$S_1 S_0$	0	0	1	1
$S_1 \bar{S}_0$	0	1	0	1

$P_o$

for  $a_{in}=0$