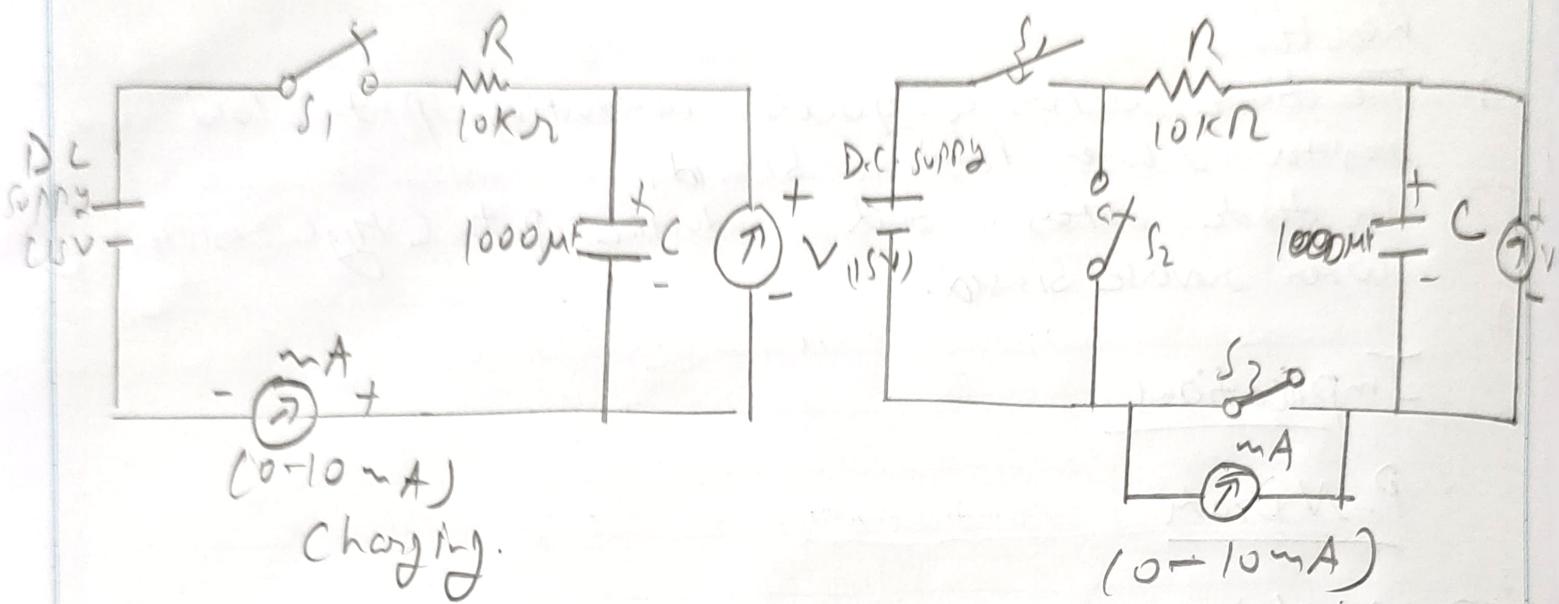


Circuit Diagram



Observation

least count of milliammeter = 0.05 mA

least count of voltmeter = 0.2 V

For charging.

S.No	Time (Seconds)	Current (I) division \times l.c. (mA)	Voltage div \times l.c. (V)
1.	5	$12 \times 0.05 = 0.6$	$2.6 - 0.2 = 0.52$
2.	10	$8 \times 0.05 = 0.4$	$4.7 \times 0.2 = 0.9$
3.	15	$5 \times 0.05 = 0.25$	$6.3 \times 0.2 = 1.26$
4.	20	$4 \times 0.05 = 0.2$	$6.2 \times 0.2 = 1.34$
5.	25	$3 \times 0.05 = 0.15$	$6.9 \times 0.2 = 1.38$
6.	30	$2.5 \times 0.05 = 0.125$	$8.1 \times 0.2 = 1.62$

Experiment No. - 3

Object: To study charge and discharge of a condenser through a resistor.

Apparatus required: D.C. supply (15 volt, 25mA), Resistance (10kr, 50kr), Capacitors (500μF, 1000μF), D.C. voltmeter (0-25V), D.C. milliammeter (0-10mA) - ~~Tidy~~, Switches, stop clock

Formula used:

- (1) Charging equation for the capacitor, C through a resistor R is given by
- $$q = q_0 (1 - e^{-t/RC})$$

where RC is the constant and q_0 is maximum charge required by the capacitor. The corresponding current equation is

$$\frac{dq}{dt} = \frac{q_0}{RC} e^{-t/RC} = \frac{CE}{RC} e^{-t/RC} = i_0 e^{-t/RC}$$


- (2) The discharge equation are
- $$q = q_0 e^{-t/RC}$$
- $$i = -i_0 e^{-t/RC}$$

Where $i_0 = E/R$ and time constant is RC .

Procedure:

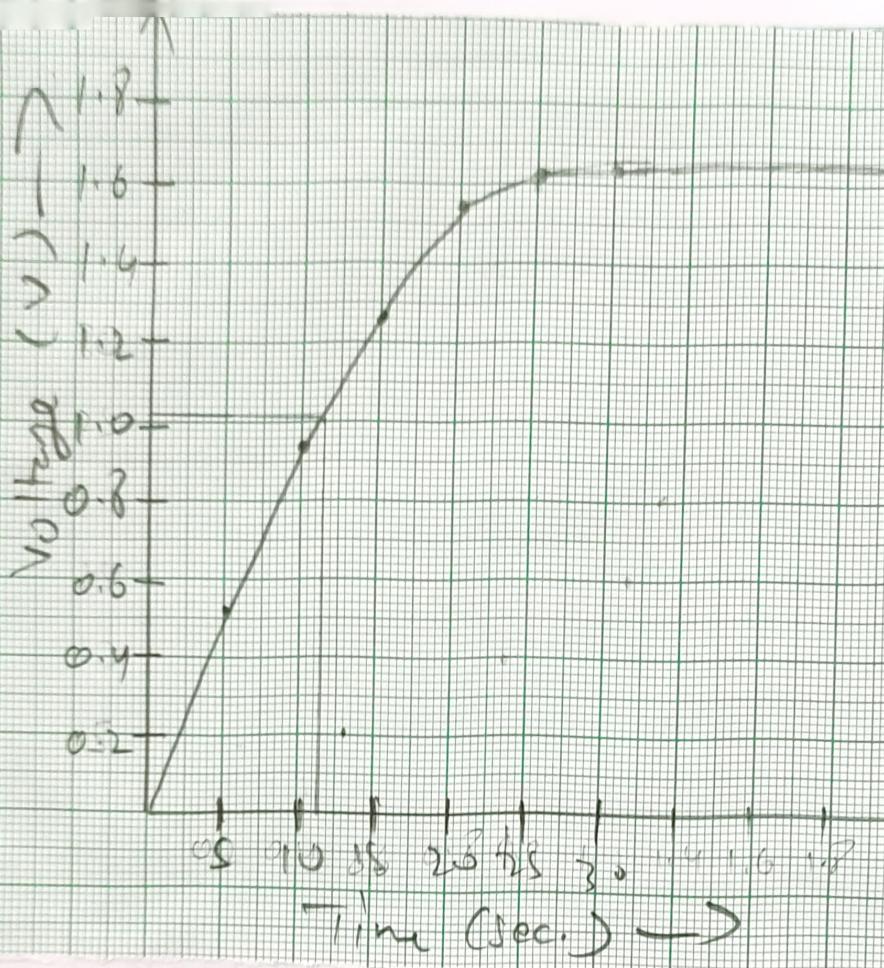
- (A) For charging a condenser:

- Link the circuit as shown in fig. switch S_1 is open
- Close switch S_1 and simultaneously start a stop clock.
- Reading in voltmeter will increase while current in milliammeter will decrease. Record readings of voltmeter and milliammeter after every 5 sec. till voltage reaches a maximum.



Scale : X-axis
1 unit = 5 sec

Y-axis :
1 unit = 0.2 V

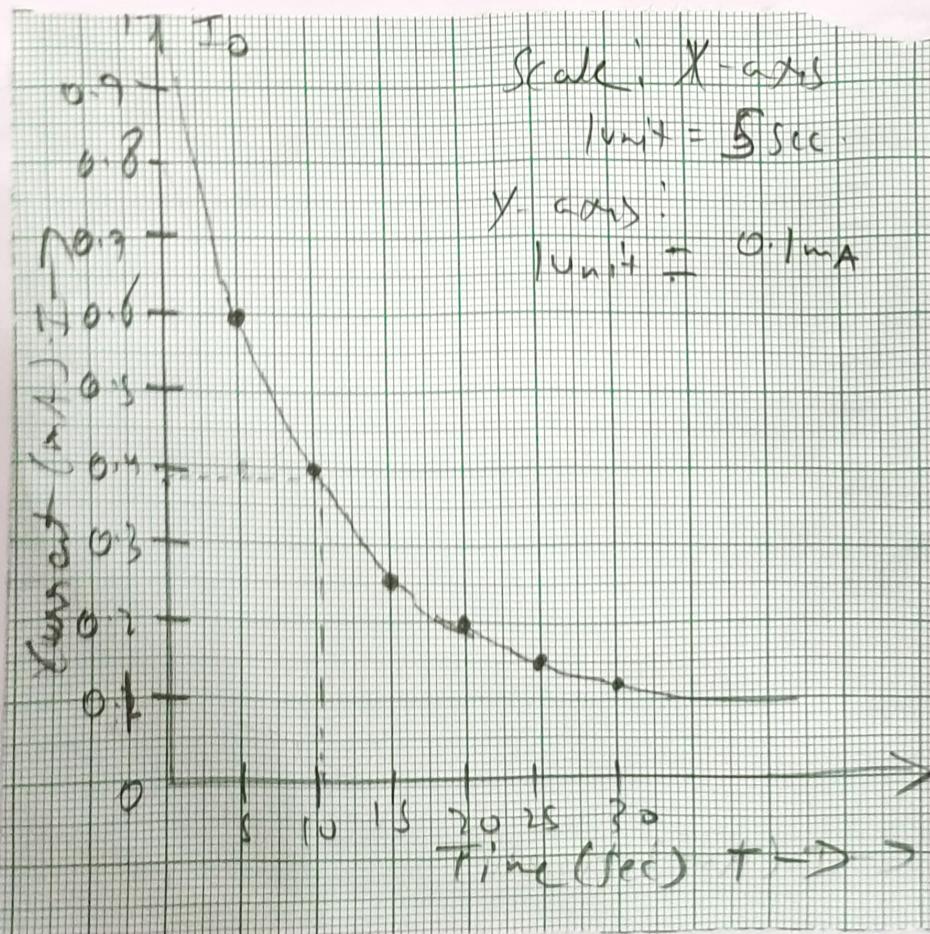

Scale : X-axis
1 unit = 5 sec

Y-axis :
1 unit = 0.1 mA

and repeat a minimum.

iv) Repeat the experiment by changing R and C

(B) For discharge of condenser:


- i) Link the circuit as shown in figure 2 keeps S_1 and S_2 switches open while S_3 closed
- ii) Close S_1 till reading in voltmeter reaches maximum value
- iii) Then open S_1 , close S_2 , S_3 is already closed. Condenser will start discharging across R , Reading in voltmeter will decrease. Take reading of voltmeter after every 5 seconds, till reading becomes to minimum.
- iv) For discharge current, open S_2 again close S_1 , so that reading in voltmeter reaches a maximum. Then open S_1 , open S_3 and close S_2 , Reading in milliammeter will start increasing. Take its reading after every 5 seconds

Calculations:

- (A) for charging of condensers: Plot a graph in voltage and time and other in current and time.
If maximum voltage reached is V_0 then time constant is the time corresponding to the point where voltage $0.63V_0$. Compare it with theoretical value of RC .
- (B) For discharge curves: Plot one graph in voltage and time and other in current and time. Find time constant which is the time corresponding to the point where voltage is $0.37V_0$. Compare it with theoretical value.

For Discharging

S.No.	Correct Time t. (sec)	Current Div X L.C. (mA)	Voltage Div X L.C. (v)
1.	5	$25 \times 0.05 = 1.2$	$5 \times 0.2 = 1.2$
2.	10	$16 \times 0.05 = 0.8$	$14 \times 0.2 = 2.8$
3.	15	$10 \times 0.05 = 0.5$	$16 \times 0.2 = 3.2$
4.	20	$6 \times 0.05 = 0.3$	$17.5 \times 0.2 = 3.5$
5.	25	$4 \times 0.05 = 0.2$	$18.5 \times 0.2 = 3.7$
6.	30	$2.5 \times 0.05 = 0.125$	$19 \times 0.2 = 3.8$

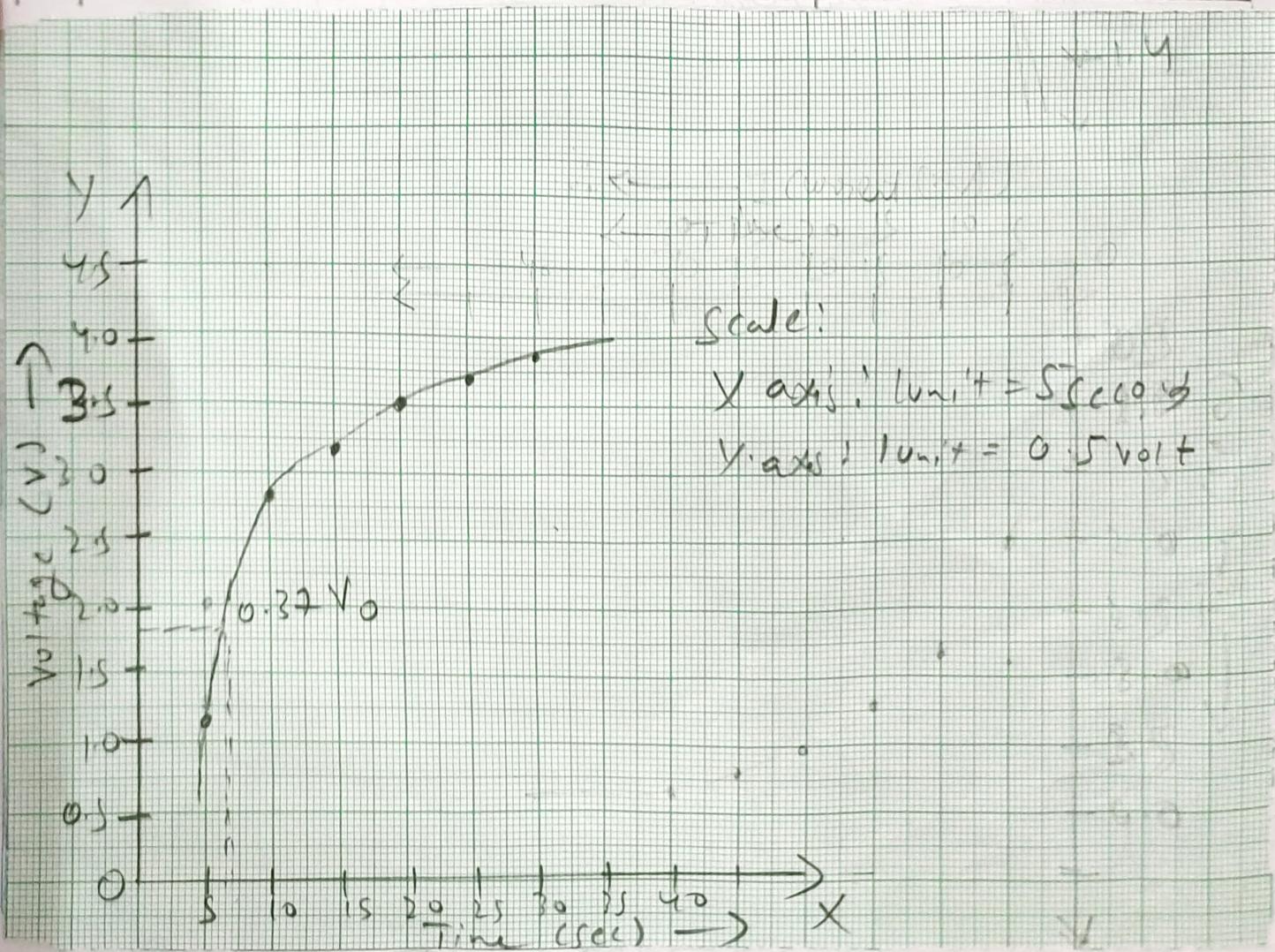

Result:


1. Time constant of circuit from the graph 10 sec.
2. Theoretical value of time constant = $\frac{10}{10}$ sec.

Sources of errors and Precautions:

- i) It is better to use voltmeters and milliammeters having small least count.
- ii) Condenser should not be leaky.
- iii) Appropriate values of R and C after quite a good number of observations should be used.

Implication

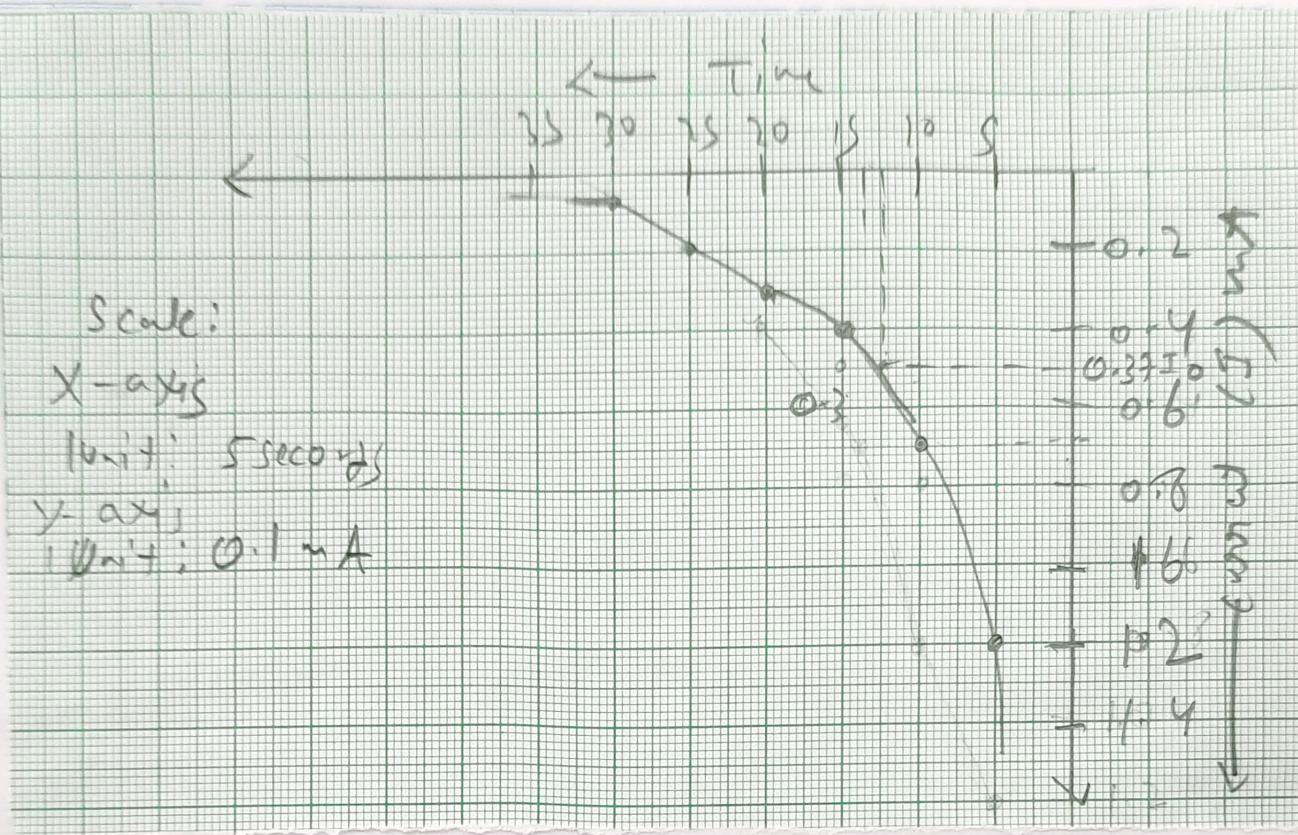1. Capacitors can store electric energy during charging it can dissipate stored energy and can be used like temporary battery.
2. Capacitors can provide upto 360 J/l of energy density. Can be used in car audio system for amplifier to be use as demand.
3. Basically constructed low inductance high voltage capacitors can be used in supplying large pulse of current for many pulsed applications, pulsed supply can be used in electromagnetic forming, Generators, Pulsed laser, particle research particle accelerator.



Calculation

$$\begin{aligned} \text{Time constant } (T_C) &= RC \\ &= 10k\Omega \times 1000\mu F \\ &= 10 \text{ seconds} \end{aligned}$$

$$\text{Maximum current in charging} = I_0 = 0.6 \Rightarrow 0.63 \times I_0 = 0.37 I_0$$

$$\text{Time corresponding to } 0.63 V_0 = 10 \text{ seconds} \quad \checkmark$$

$$\text{Maximum value of voltage in charging} = V_0 = 1.62 \Rightarrow 0.63 V_0 = 1.02$$

$$\text{Time corresponding to } 0.63 V_0 = 10 \text{ seconds}$$

$$\text{Maximum current in discharge} = I_0 = 1.2$$

$$0.37 I_0 = 0.37 \times 1.2 = 0.444 \text{ mA}$$

$$\text{Time corresponding to } 0.37 I_0 = 12.5 \text{ seconds}$$

$$\text{maximum value of voltage in discharge} = V_0 = 3.8$$

$$\text{Time corresponding to } 0.37 V_0 = 7 \text{ seconds}$$