

END TERM EXAMINATION

THIRD SEMESTER [B.TECH] JANUARY 2024

Paper Code: ECC-207

Subject: Digital Logic & Computer Design

Time: 3 Hours

Maximum Marks: 75

Note: Attempt five questions in all including Q.No.1 which is compulsory.
Select one question from each unit. Assume missing data, if any.

Q1 Attempt all questions:

(3×5=15)

- a) Reduce the Boolean Expression $+^-(+^-)$ ✓
 b) What are don't care terms?
 c) Differentiate a decoder from a Demultiplexer.
 d) Draw the state table and excitation table of T flip flop.
 e) Write about Virtual memory.

UNIT-I

- Q2 a) What is meant by duality in Boolean algebra? State and prove Associative and Distributive theorems. (7)
 b) Minimize the expression $(, , ,) = \sum(0,1,2,5,8,9,10)$ using K-map and obtain (i) minimal SOP and (ii) minimal POS expression. (8)
- Q3 a) Explain the operation of a magnitude comparator? (7)
 b) Implement a full subtractor using 8:1 MUX. (8)

UNIT-II

- Q4 a) What is Race Around condition? And how is it overcome in JK Flip-Flop? Explain with diagram. (5)
 b) Design a Mod-5 synchronous counter using JK Flip-Flop. (10)
- Q5 a) Explain designing of T Flip-Flop using JK Flip-Flop. (7)
 b) Write short notes on: (i) Shift registers (ii) PLA & PAL (8)

UNIT-III

- Q6 a) Differentiate between hardwired control and micro programmed control and explain organizations of micro programmed control unit with neat diagram. (10)
 b) What is addressing mode? Explain different types of addressing modes. (5)
- Q7 a) What are the different phases of an instruction cycle? Explain with the help of flowchart. (7)
 b) What is assembly language? Explain basic computer instruction formats with suitable diagram. (8)

P.T.O.

UNIT-IV

Q8

a)

Define DMA. Explain its need. Explain DMA transfer in detail with the help of suitable diagram.

(7)

b)

What is an interrupt? Explain interrupt cycle with the help of flowchart.

(8)

Q9 Write short notes on:

a) Modes of data transfer

(5)

b) Cache memory

(5)

c) Associative memory

(5)
