

if I_1 entering 1 terminal of a pair is equal + 1 opposite to the I_2 leaving other terminal of the pair then this type of terminal pair is called as a "port".

2-port N/w - represented by 4 variables.
2 voltages (V_1, V_2) & 2 currents (I_1, I_2)

Relationship of 2 port Variables :

no. of possible Combi generated by 4 variables taken 2 at a time = 6.. so total 6 Combi are there with which we can analyse any type of 2-port N/w.

(1) open circuit Impedance parameters or Z-para.


$$(V_1, V_2) = f(I_1, I_2)$$

Q.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

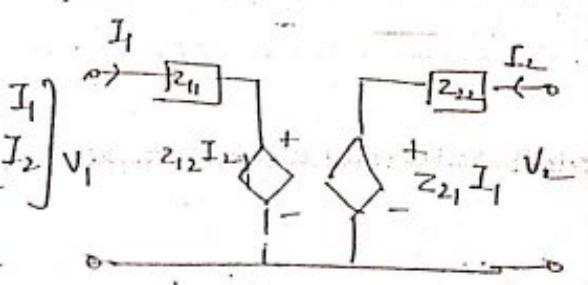

$$\begin{array}{l} \text{Q} \\ \frac{V_2 = 0}{V_1 = V_1} \\ I_1 = ? \quad V_2 = ? \end{array}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{Q/p during point impedance} \quad (2)$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad \text{fwd transfer impedance}$$

$$\begin{array}{l} \text{Q} \\ \frac{I_1 = 0}{V_2 = V_2} \quad V_1 = ? \\ I_2 = ? \quad I_1 = 0 \end{array}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{reverse transfer impedance}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad \text{Q/p during pt imp.}$$

② short ckt admittance or Y-par.

$$(I_1, I_2) = f(V_1, V_2)$$

$$[I] = [Y][V]$$

$$Y = Z^{-1}$$

$$\therefore Y_{ij} \neq \frac{1}{Z_{ij}}$$

(3) Transmission (T) or chain or $-ABCD$ para. (2)

$$(V_1, I_1) = f(V_2, -I_2)$$

T -para is used in the analysis of transmission line.
D/P port \rightarrow receiving end
S/P port \rightarrow sending end.

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

2

(4) Inverse T parameters

$$(V_2, I_2) = f(V_1, -I_1)$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

(5) Hybrid parameters (h -para).


widely used in electronic ckt's, esp in constructing models for transistors.

$$(V_1, I_2) = f(I_1, V_2)$$

(6) Inverse hybrid or g -para:

$$[g] = [h^{-1}]$$

$$(I_1, V_2) = f(V_1, I_2)$$

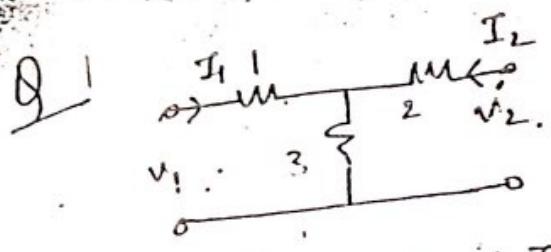

Calc. ① Z, Y, T, Δ -parameters

$$\text{loop eq: } \begin{aligned} V_1 &= 1I_1 + 3(I_1 + I_2) = 4I_1 + 3I_2 \\ V_2 &= 2I_2 + 3(I_1 + I_2) = 3I_1 + 5I_2 \end{aligned}$$

$$\textcircled{1} Z\text{-para } (V_{11}, V_2) = f(I_1, I_2)$$

$$(a) I_2 = 0$$

$$V_1 = 4I_1$$

$$V_2 = 3I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{V_1}{\frac{V_1}{4}} = 4\Omega$$

$$Z_{21} = \frac{V_2}{I_1} = 3$$

$$(b) I_1 = 0$$

$$V_1 = 3I_2 \quad \& \quad V_2 = 5I_2$$

$$Z_{12} = 3 \quad \& \quad Z_{22} = 5$$

$$\textcircled{2} Y\text{-para } (I_{11}, I_2) = f(V_1, V_2)$$

$$a) V_2 = 0$$

$$3I_1 = -5I_2$$

$$V_1 = 4I_1 + 3I_2$$

$$V_1 = 4I_1 + 3\left(-\frac{3}{5}I_1\right)$$

$$V_1 = \left(\frac{20-9}{5}\right)I_1$$

$$V_1 = \frac{11}{5}I_1$$

$$Y_{11} = \frac{5}{11}V_1$$

$$V_1 = 4\left(-\frac{5}{3}I_2 + 3I_2\right)$$

$$V_1 = \frac{(9-20)}{3}I_2$$

$$V_1 = -\frac{11}{3}I_2$$

$$Y_{21} = -\frac{3}{11}V_1$$

(3)

$$\frac{V_1 = 0}{Y_{12}} = -\frac{3}{11} u \quad Y_{22} = \frac{4}{11} u$$

(3) I-parameter

$$(V_{11}, I_1) \text{zf} (V_{21}, I_2)$$

3

$$(a) \quad I_2 = 0$$

$$V_1 = 4 I_1$$

$$V_2 = 3 I_1$$

(b)

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{4}{3}$$

$$C_2: \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{3} u$$

$$(b) \quad V_2 = 0.$$

$$3 I_1 = -5 I_2 \quad V_1 = 4 \left(-\frac{5}{3} I_2 \right) + 3 I_2 = -\frac{11}{3} I_2$$

(c)

$$B = \left. \frac{V_1}{-I_2} \right|_{I_2=0} = \frac{11}{3} \Omega$$

$$D = \left. \frac{I_1}{-I_2} \right|_{I_2=0} = \frac{5}{3}$$


Condition for Reciprocity

2-port N/W is reciprocal if the ratio of excitation to response is invariant to an interchange of their positions.

6

N/W having $R, L, C \rightarrow$ reciprocal

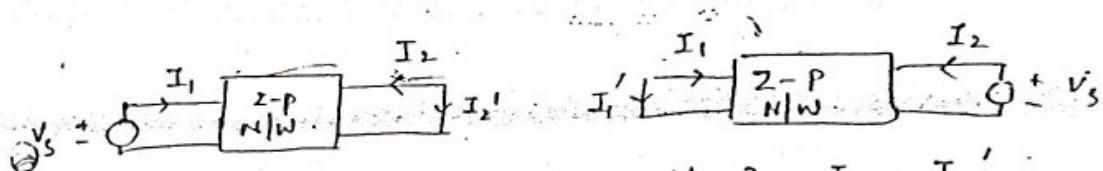" " dependent sources \rightarrow non-reciprocal.



$$V_1 = V_S, I_1 = I_1, \\ V_2 = 0, I_2 = I_2$$

$$V_1 = 0, I_1 = I_1' \\ V_2 = V_S, I_2 = I_2'$$

$$\frac{V_S}{I_2'} = \frac{V_S}{I_1'} \quad \text{or} \quad I_2' = I_1'$$

(1) In terms of Z-parameters

$$\textcircled{1} \quad V_1 = z_{11} I_1 + z_{12} I_2 \quad (\text{a})$$

$$\textcircled{2} \quad V_2 = z_{21} I_1 + z_{22} I_2 \quad (\text{b})$$

$$\begin{aligned} V_1 &= V_S, \quad I_1 = I_1, \\ V_2 &= 0, \quad I_2 = -I_2 \end{aligned}$$

$$\begin{aligned} V_S &= z_{11} I_1 + z_{12} I_2' \quad \text{--- (1)} \\ 0 &= z_{21} I_1 - z_{22} I_2' \quad \text{--- (2)} \end{aligned}$$

$$\text{from (1)} \quad I_1 = \frac{z_{22} I_2'}{z_{21}}$$

$$\therefore V_S = \left(z_{11} \frac{z_{22} I_2'}{z_{21}} - z_{12} \right) I_2'$$

$$I_2' = \frac{V_s Z_{21}}{Z_{11} Z_{22} - Z_{12} Z_{21}} \quad -\textcircled{3}$$

11 by putting in a + b.

$$V_2 = V_s \quad I_2 = I_2$$

$$V_1 = 0 \quad I_1 = -I_1'$$

we get

$$I_1' = \frac{V_s Z_{12}}{Z_{11} Z_{22} - Z_{12} Z_{21}} \quad -\textcircled{4}$$

On comparing $\textcircled{3}$ & $\textcircled{4}$

$$\boxed{Z_{21} = Z_{12}}$$

2) In terms of Y -parameters

$$Y_{21} = Y_{12}$$

3) T-parameters

$$V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

$$V_1 = V_s \quad I_1 = I_1'$$

$$V_2 = 0 \quad I_2 = -I_2'$$

$$V_s = B I_2' \Rightarrow I_2' = \frac{V_s}{B} \quad -\textcircled{1}$$

$$I_1' = D I_2'$$

$$V_2 = V_S \quad I_2 = -I_2$$

$$V_1 = 0 \quad I_1 = -I_1$$

$$0 = A V_S + B (-I_2) \Rightarrow I_2 = \frac{A}{B} V_S \quad \text{Eqn 8}$$

$$-I_1' = C V_S + D (-I_2)$$

$$-I_1' = C V_S + -\frac{DA}{B} V_S$$

$$\textcircled{1} \quad I_1' = \frac{(-BC + DA) V_S}{B} \quad \textcircled{2}$$

Comparing $\textcircled{1}$ & $\textcircled{2}$

$$\boxed{\begin{aligned} AD - BC &= 1 \\ \text{or } \Delta T &= 1 \end{aligned}}$$

(4) In terms of T' -parameters.

$$\underline{A'D' - B'C'} = 1 \quad \text{or } \underline{\Delta T'} = 1$$

(5) h -parameters



$$h_{12} = -h_{21}$$

(6) g -parameters

$$g_{12} = -g_{21}$$

or Symmetry -

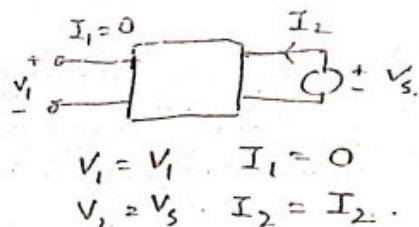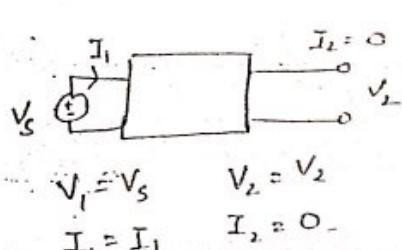A port N/w. is symmetrical if the ports can be interchanged without changing the port voltages & currents.



∴

$$\left. \frac{V_s}{I_1} \right|_{I_2=0} = \left. \frac{V_s}{I_2} \right|_{I_1=0}$$

(1) In terms of Z-parameters :

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

~~$$\left. \frac{V_s}{I_1} \right|_{I_2=0} = Z_{11}$$~~

$$\left. \frac{V_s}{I_2} \right|_{I_1=0} = Z_{22}$$

(2) Y-params

$$Y_{11} = Y_{22}$$

(3) T-parameters

$$A = D$$

T'-parameters

$$A' := D'$$

10

(5) h-para

$$h_{11} h_{22} - h_{12} h_{21} = 1$$

$$\text{or } \Delta h = 1$$

(6) g-para

$$\Delta g = 1 \quad \text{or} \quad g_{11} g_{22} - g_{12} g_{21} = 1$$

Relationships b/w parameter Sets:

① Z-parameters in terms of other

(a) Z in terms of Y-para.

$$[I] = [Y] [v]$$

$$[V] = [Z] [I].$$

$$\therefore [Z] = [Y]^{-1}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \frac{1}{\Delta Y} \begin{bmatrix} Y_{22} & -Y_{11} \\ -Y_{21} & Y_{11} \end{bmatrix}$$

$$Z_{11} = \frac{Y_{22}}{\Delta Y} \quad Z_{12} = -\frac{Y_{11}}{\Delta Y} \quad Z_{21} = -\frac{Y_{21}}{\Delta Y}$$

$$Z_{22} = Y_{11}$$

(b) V_2 in terms of T-para.

$$V_1 = A V_2 + B(-I_2) \quad \text{--- (1)}$$

$$I_1 = C V_2 + D(-I_2). \quad \text{--- (2)}$$

↓

$$V_2 = \frac{1}{C} I_1 + \frac{D}{C} I_2. \quad \boxed{6}$$

$$\boxed{Z_{21} = \frac{1}{C}; \quad Z_{22} = \frac{D}{C}}$$

from (1)

$$V_1 = A \left[\frac{1}{C} I_1 + \frac{D}{C} I_2 \right] - B I_2$$

$$V_1 = \frac{A}{C} I_1 + \left(\frac{AD}{C} - B \right) I_2$$

$$\boxed{Z_{11} = \frac{A}{C}, \quad Z_{12} = \frac{AD - BC}{C} = \frac{\Delta T}{C}.}$$

c) T' -para.

$$Z_{21} = \frac{1}{C'}, \quad Z_{22} = \frac{D'}{C'}$$

$$Z_{11} = \frac{A'}{C'} \quad \& \quad Z_{12} = \frac{\Delta T'}{C'}$$

parameters:

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$V_2 = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1$$

$$\Rightarrow Z_{21} = -\frac{h_{21}}{h_{22}} \quad \& \quad Z_{22} = \frac{1}{h_{22}}$$

$$V_1 = h_{11} I_1 + h_{12} \left(\frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1 \right)$$

$$\therefore h_{22} h_{11} - h_{21} h_{12} \quad I_1 + \frac{h_{12}}{h_{22}} I_2$$

So

$$\Rightarrow Z_{11} = \frac{\Delta h}{h_{22}} \quad \& \quad Z_{12} = \frac{h_{12}}{h_{22}}$$

(e) g-parameters:

$$Z_{11} = \frac{1}{g_{11}} \quad ; \quad Z_{12} = -\frac{g_{12}}{g_{11}} \quad ; \quad Z_{21} = -\frac{g_{21}}{g_{11}}$$


$$Z_{22} = g \cdot \frac{\Delta g}{g_{11}}$$

Interconnection of two-Port N/w.

2-port N/w can be connected as series, parallel, cascade, Series-parallel & parallel-series connection.

for each configuration certain set of parameters may be more useful than others to describe the n/w.

① Series Connection:

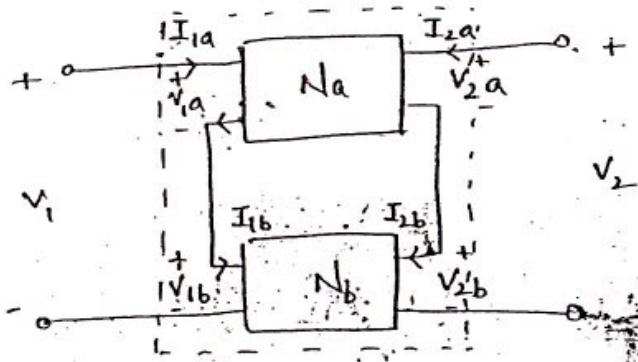

Na

$$\begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} = \begin{bmatrix} Z_{11a} & Z_{12a} \\ Z_{21a} & Z_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix}$$

Nb

$$\begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} = \begin{bmatrix} Z_{11b} & Z_{12b} \\ Z_{21b} & Z_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$

Series Connection

$$I_1 = I_{1a} = I_{1b}, \quad I_2 = I_{2a} = I_{2b}$$

$$V_1 = V_{1a} + V_{1b}, \quad V_2 = V_{2a} + V_{2b}$$

$$V_1 = V_{1a} + V_{1b} = Z_{11a} I_{1a} + Z_{12a} I_{2a} + Z_{11b} I_{1b} + Z_{12b} I_{2b}$$

$$V_1 = (Z_{11a} + Z_{11b}) I_1 + (Z_{12a} + Z_{12b}) I_2$$

By $V_2 = V_{2a} + V_{2b}$

$$= (Z_{21a} + Z_{21b}) I_1 + (Z_{22a} + Z_{22b}) I_2$$

$$Z_{11} = Z_{11a} + Z_{11b}$$


$$Z_{12} = Z_{12a} + Z_{12b}$$

$$Z_{21} = Z_{21a} + Z_{22b}$$

$$Z_{22} = Z_{22a} + Z_{22b}$$

$$\text{So } [Z] = [Z_a] + [Z_b]$$

(2) Parallel Connection:

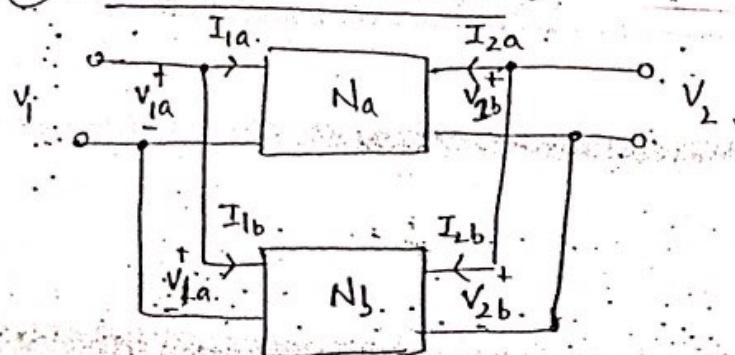

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix}$$

$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} Y_{11b} & Y_{12b} \\ Y_{21b} & Y_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

8

for || connection \rightarrow

$$V_1 = V_{1a} = V_{1b} \quad V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} + I_{1b} \quad (1) \quad I_2 = I_{2a} + I_{2b} \quad (2)$$

in (1).

$$I_1 = Y_{11a} V_{1a} + Y_{12a} V_{2a} + Y_{11b} V_{1b} + Y_{12b} V_{2b}$$

$$I_1 = (Y_{11a} + Y_{11b}) V_{1a} + (Y_{12a} + Y_{12b}) V_{2b}$$

$$\text{So } || \text{ by } \quad I_2 = (Y_{21a} + Y_{21b}) V_1 + (Y_{22a} + Y_{22b}) V_2$$

$$\text{So } [Y] = [Y_a] + [Y_b]$$

$$Y_{11} = Y_{11a} + Y_{11b} \quad Y_{22} = Y_{22a} + Y_{22b}$$


$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$

cascade connection : (Tandem)

(1)

16

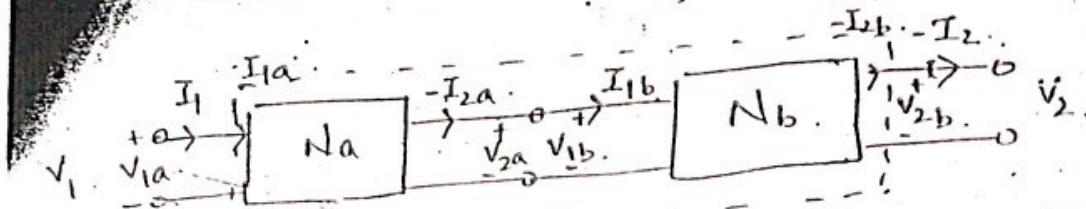

This is the simplest possible interconnection
2-N/w r cascaded when O/P of 1st N/w
is the I/P of the 2nd N/w.

$$\underline{\underline{N_a}} \quad \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

$$\underline{\underline{N_b}} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

In Cascade

$$V_1 = V_{1a}; \quad V_{2a} = V_{1b}$$

$$V_2 = V_{2b}$$

$$I_1 = I_{1a} - I_{2a} = I_{1b} \quad I_{2b} = I_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} =$$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{1b} \\ -I_{1b} \end{bmatrix}$$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$
9

$$\text{so } \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

$$A = A_a A_b + B_a C_b, \quad C = C_a A_b + D_a C_b.$$


$$B = B_a B_b + B_a D_b, \quad D = C_a B_b + D_a D_b.$$

$$[T] = [T_a] \cdot [T_b]$$

In terms of T' -parameters

$$[T'] = [T'_b] \cdot [T'_a].$$

(4) Series-parallel

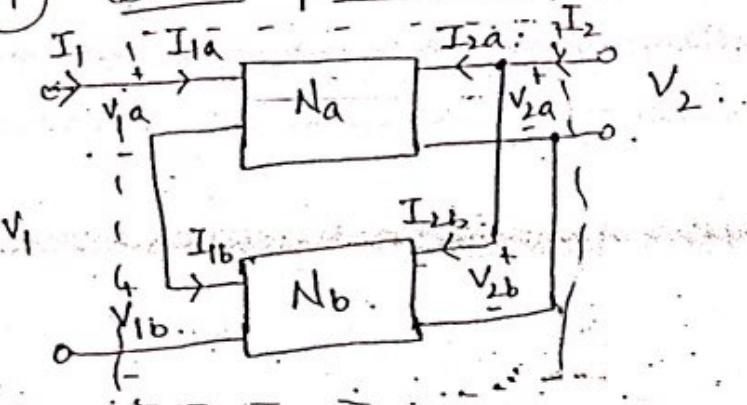


Series - parallel

$$V_1 = V_{1a} + V_{1b}, \quad V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} = I_{1b}, \quad I_2 = I_{2a} + I_{2b}.$$

here $[h] = [h_a] + [h_b]$.

(5) Parallel - Series

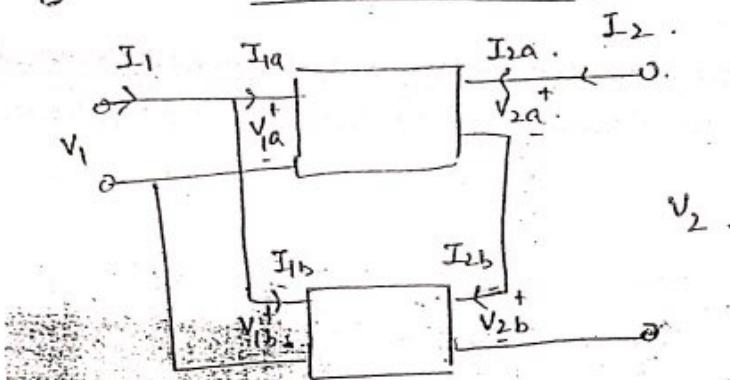

$$V_1 = V_{1a} = V_{1b}, \quad I_1 = I_{1a} + I_{1b}$$


$$V_2 = V_{2a} + V_{2b}, \quad I_2 = I_{2a} = I_{2b}$$

here

$$[g] = [g_a] + [g_b]$$

Ques:

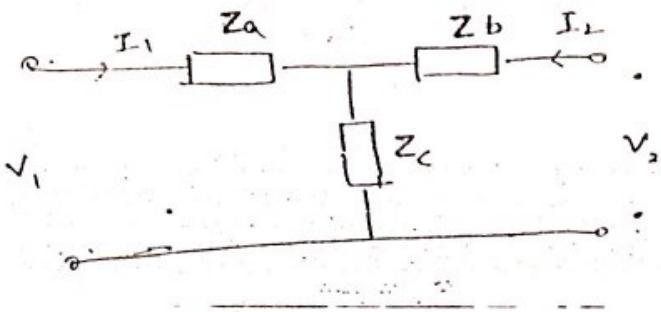- ① For the T-n/w shown find Z-parameters.



(1)

10

$$v_1 = Z_a I_1 + Z_c (I_1 + I_2)$$

$$v_2 = (Z_a + Z_c) I_1 + Z_c I_2$$


$$v_2 = Z_b I_2 + Z_c (I_1 + I_2)$$

$$= Z_c I_1 + (Z_b + Z_c) I_2$$

$$Z = \begin{bmatrix} Z_a + Z_c & Z_c \\ Z_c & Z_b + Z_c \end{bmatrix}$$


6

②

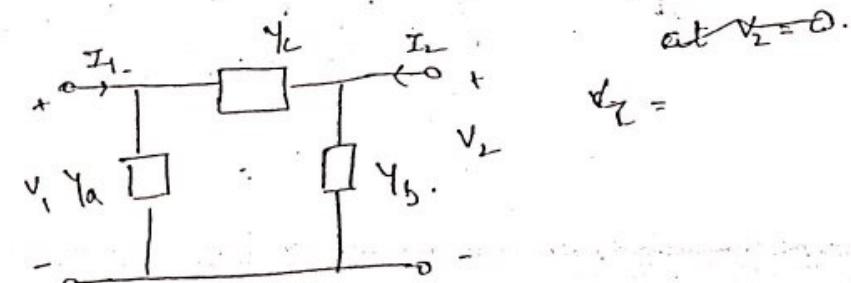

at $v_2 = 0$.

$$Y_2 =$$

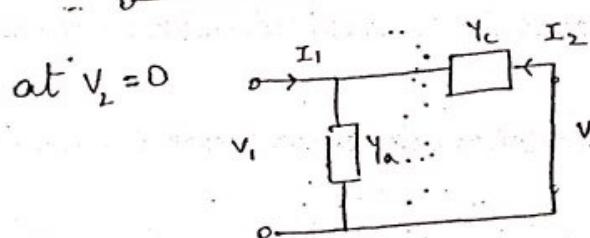

$$\left. \begin{aligned} v_1 &= \frac{(I_1 + I_2)}{Y_a} \\ v_1 &= -\frac{I_2}{Y_c} \end{aligned} \right\} \quad (1)$$

$$\text{at } v_1 = 0 \quad v_2 = \frac{(I_1 + I_2)}{Y_b} \quad \& \quad v_2 = -\frac{I_1}{Y_c} \rightarrow (2)$$

①

②

$$I_2 = (-Y_c) V_1$$

$$V_1 = [I_1 + V_1(-Y_c)] \frac{1}{Y_a}$$

20

$$(Y_a + Y_c) V_1 = I_1$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = Y_a + Y_c$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -Y_c$$

from ② &

$$V_1 = 0$$

$$V_2 = (I_1 + I_2) \frac{1}{Y_b}$$

$$V_2 = -\frac{I_1}{Y_c} \quad \Rightarrow \quad Y_{12} = \frac{I_1}{V_2} = -Y_c$$

$$V_2 = (-Y_c V_2 + I_2) \frac{1}{Y_b}$$

$$Y_b V_2 + Y_c V_2 = I_2$$

$$Y = \begin{bmatrix} Y_a + Y_c & -Y_c \\ -Y_c & Y_b + Y_c \end{bmatrix}$$

$$(Y_b + Y_c) V_2 = I_2$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = Y_b + Y_c$$

open wkt + short wkt impedances

open wkt impedances \rightarrow measurement at S/P port while O/P \rightarrow is open

$$Z_{10} = \frac{V_1}{I_1} \Big|_{I_2=0} \equiv Z_{11}$$

$$Z_{20} = \frac{V_2}{I_2} \Big|_{I_1=0} \equiv Z_{22}$$

short wkt impedances \rightarrow

$$Z_{1S} = \frac{V_1}{I_1} \Big|_{V_2=0} \equiv \frac{1}{Y_{11}}$$

$$Z_{2S} = \frac{V_2}{I_2} \Big|_{V_1=0} \equiv \frac{1}{Y_{22}}$$

In terms of T-parameters

$$V_1 = AV_2 - BI_2$$

$$BI_1 = CV_2 - DI_2$$

T-para. in terms of O.C & S.C. Imped

$$A = \pm \sqrt{\frac{Z_{10}}{Z_{20} - Z_{2S}}}$$

$$Z_{10} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{A}{C} \quad | \quad B = \pm Z_{2S} \sqrt{\frac{Z_{10}}{Z_{20} - Z_{2S}}}$$

$$Z_{20} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{D}{C} \quad | \quad C = \pm \sqrt{\frac{1}{Z_{10}(Z_{20} - Z_{2S})}}$$


$$Z_{1S} = \frac{V_1}{I_1} \Big|_{V_2=0} = \frac{B}{D} \quad | \quad D = \pm \sqrt{\frac{Z_{20}}{Z_{10}(Z_{20} - Z_{2S})}}$$

$$Z_{2S} = \frac{V_2}{I_2} \Big|_{V_1=0} = \frac{B}{A}$$

Input impedance

If load imp. z_L is connected to D/P port.

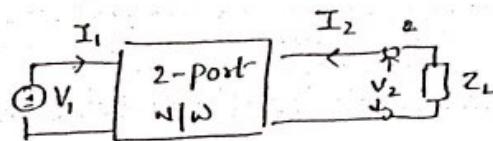then $z_{ip} = \frac{v_1}{I_1}$ is D/P Z.



⇒ 12

① z_{ip} in terms of z

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_2 = -I_2 z_L$$

$$-I_2 z_L = Z_{21} I_1 + Z_{22} I_2$$

$$I_2 = \frac{-Z_{21}}{Z_{22} + z_L} I_1$$

$$V_1 = Z_{11} I_1 + Z_{12} \left[\frac{-Z_{21}}{Z_{22} + z_L} \right] I_1$$

$$z_{ip} = \frac{V_1}{I_1} = \frac{Z_{11} Z_{22} - Z_{21} Z_{12} + Z_{11} z_L}{Z_{22} + z_L}$$

② in terms of T-para.

$$z_{ip} = \frac{V_1}{I_1} = \frac{A z_L + B}{C z_L + D}$$

Imp. in terms of h-parameters:

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$V_2 = -I_2 Z_L$$

$$V_2 = -Z_L (h_{21} I_1 + h_{22} V_2)$$


$$V_2 = \frac{-h_{21} Z_L}{1 + h_{22} Z_L} I_1$$

$$V_1 = h_{11} I_1 + h_{12} \left[-\frac{h_{21} Z_L}{1 + h_{22} Z_L} \right] I_1$$

$$Z_{IP} = \frac{V_1}{I_1} = h_{11} - \frac{h_{12} h_{21} Z_L}{1 + h_{22} Z_L}$$

O/P Impedance

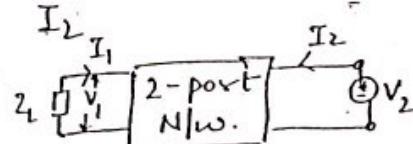- ④ If a load imp. Z_L is connected to g/p port
then $Z_{OP} = \frac{V_2}{I_2}$ is termed as O/P Imp.



O/P Imp. in terms of Z-parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = -I_1 Z_L$$

$$I_1 = - \frac{(Z_{11} I_1 + Z_{12} I_2)}{Z_L}$$

$$I_1 = - \frac{Z_{12}}{Z_{11} + Z_L} I_2$$

$$V_2 = Z_{21} \left[-\frac{Z_{12}}{Z_{11} + Z_L} \right] I_2 + Z_{22} I_2 \quad .13$$

$$Z_{op} = \frac{V_2}{I_2} = \frac{Z_{11} Z_{22} - Z_{21} Z_{12} + Z_{22} Z_L}{Z_{11} + Z_L}$$

(2) in terms of I_{-par}


$$Z_{op} = \frac{D Z_L + B}{C Z_L + A}$$

(3) h -par

$$Z_{op} = \frac{h_{11} + Z_L}{h_{11} h_{22} - h_{12} h_{21} + h_{22} Z_L}$$

Image Impedances :

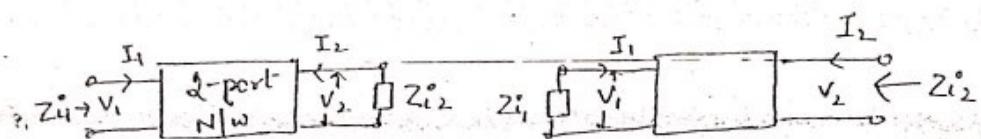In a 2-port N/w, if the imp. at g/p port with imp. Z_{i1} connected across g/p port be Z_{i2}^o , & the imp. at o/p port with imp. Z_{i2}^o connected across g/p port be Z_{i1}^o , then Z_{i1}^o & Z_{i2}^o are image imp.



For symmetrical n/w

$Z_{i1} = Z_{i2}^o$ & is called characteristic or iterative imp. Z_c .

$$Z_{i1} = \frac{V_1}{I_1} \quad (\text{driving point imp. at g/p port})$$

$$Z_{i2}^o = \frac{V_2}{I_2} \quad (\text{u u u u o/p}).$$

Image Imp. in terms of I/P & O/P Imp.

$$Z_{i1} = Z_{ip} \quad \& \quad Z_{i2}^o = Z_{op}$$

in terms of T-parameters

$$Z_{i1} = Z_{ip}$$

$$\frac{Z_{i1}}{Z_{ip}} = \frac{A + Z_{i2}^o}{C Z_{i2}^o + D} \quad \text{--- (1)}$$

$$Z_{i2}^o = Z_{op} = D Z_{i1} + B \quad \text{--- (2)}$$

Solving (1) & (2).

$$Z_{i1}^o = \sqrt{\frac{AB}{CD}}$$

$$Z_{i2}^o = \sqrt{\frac{BD}{AC}}$$



In terms of open circuit & short circuit impedances:

$$\text{PT } Z_{i_1} = \sqrt{\frac{AB}{CD}} = \sqrt{\frac{A}{C} \cdot \frac{B}{D}} = \sqrt{Z_{10} \cdot Z_{1S}}$$

$$Z_{i_2} = \sqrt{\frac{BD}{AC}} = \sqrt{\frac{D}{C} \cdot \frac{B}{A}} = \sqrt{Z_{20} \cdot Z_{2S}}$$

16

π to T transformation.

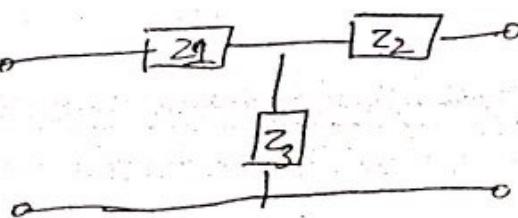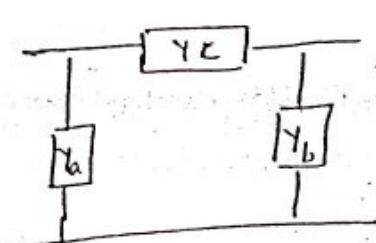


π to T

$$Z_1 = \frac{\frac{1}{Y_a} \cdot \frac{1}{Y_c}}{\frac{1}{Y_a} + \frac{1}{Y_b} + \frac{1}{Y_c}} = \frac{\frac{1}{Y_a Y_c}}{\frac{1}{Y_a} + \frac{1}{Y_b} + \frac{1}{Y_c}} = \frac{Y_b}{Y_a Y_b + Y_b Y_c + Y_c Y_a}$$

T to π

~~Ans~~ | Calc. Z-param. of the Net shown & find out whether its reciprocal or symmetrical or none

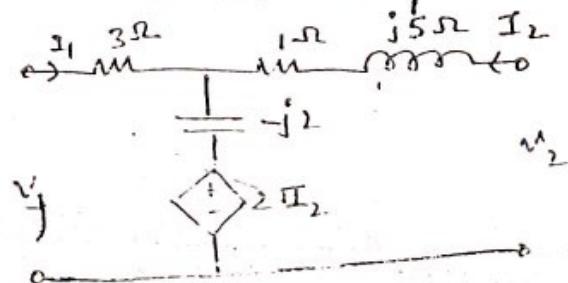

$$V_1 = 3I_1 - j2(I_1 + I_2) + 2I_2$$

$$V_1 = (3 - j2)I_1 + 2I_2 / (1 - j)$$

$$V_2 = I_2 + j5I_2 - j2(I_1 + I_2) + 2I_2$$

$$V_2 = (3 + 3j)I_2 - j2I_1$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = (3 - j2)\Omega$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = -j2\Omega$$


$$Z_{12} = (2 - j2)\Omega$$

$$Z_{22} = (3 + 3j)\Omega$$

Since $Z_{12} \neq Z_{21}$ so not reciprocal

$Z_{11} \neq Z_{22}$ so not sym.

Q. Obtain 2-parameters of the N/w.

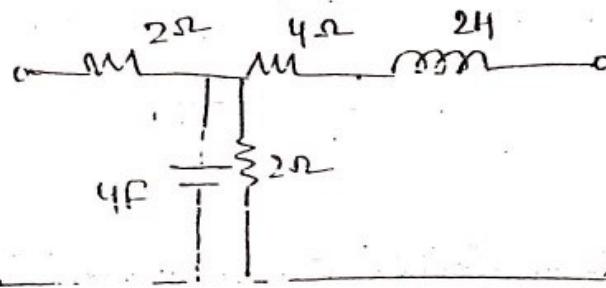


$$Z = R \equiv Ls = \frac{1}{Cs}$$

$$Y = \frac{1}{R} = \frac{1}{Ls}$$

15

Converting into S-domain

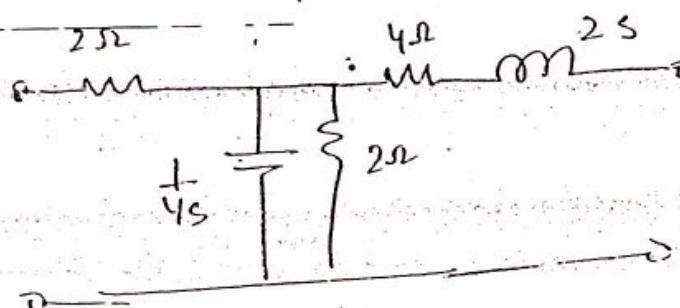

$$\frac{1}{4s} \parallel 2\Omega = \frac{2}{1+8s}$$

$$Z_a = 2\Omega \quad Z_b = 4+2s$$


$$Z_C = \frac{2}{1+8s}$$

$$\text{So } Z_{11} = Z_a + Z_C = 2 + \frac{2}{1+8s} = \frac{4+16s}{1+8s}$$

$$Z_{12} = Z_{21} = Z_C = \frac{2}{1+8s}$$

$$Z_{22} = Z_b + Z_C = 4+2s + \frac{2}{1+8s} = \frac{6+34s+16s^2}{1+8s}$$

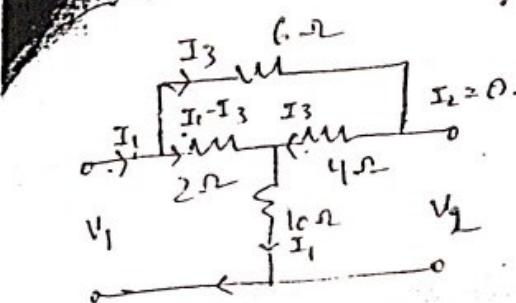1. obtain the open circuit param. of the NW.



$$\underline{I_2 = 2 \Omega}$$

$$V_1 = 2(I_1 - I_3) + 10 I_1$$

$$V_1 = 12 I_1 - 2 I_3$$

$$V_2 = 4 I_3 + 10 I_1$$

$$I_3 = I_1 \times \frac{2}{2+4+4} \quad \text{or} \quad \underline{\frac{2 I_1}{12} = \frac{I_1}{6}}$$

$$V_1 = 2\left(I_1 - \frac{I_1}{6}\right) + 10 I_1$$

$$= \frac{10}{6} I_1 + 10 I_1$$

$$\frac{70}{6} I_1 = \frac{35}{3} I_1$$

$$V_2 = 4 \cdot \frac{I_1}{6} + 10 I_1 = \frac{32}{3} I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{35}{3} \Omega$$


$$Z_{21} = \frac{32}{3} \Omega$$

$$\underline{V_1 = 2 I_4 + 10 I_2}$$

$$V_2 = 4(I_2 - I_4) + 10 I_2 =$$

$$Z_{12} = \frac{32}{3} \Omega \quad \therefore Z_{22} = \frac{38}{3} \Omega$$

Q1 for the lattice N/w find 2-param

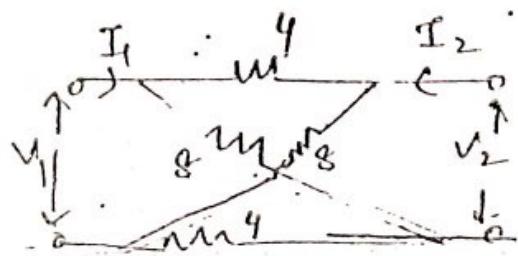

16

case 1 $I_2 = 0$

$$V_1 = 4 \frac{I_1}{2} + 8 \frac{I_1}{2} = 6I_1$$

$$V_2 = 8 \frac{I_1}{2} - 4 \frac{I_1}{2} = 2I_1$$


case 2 $I_1 = 0$

$$V_1 = 8 \frac{I_2}{2} - 4 \frac{I_2}{2} = 2I_2$$

$$V_2 = 6I_2$$

$$Z_{11} = Z_{22} = 6\Omega$$

$$Z_{12} = Z_{21} = 2\Omega$$

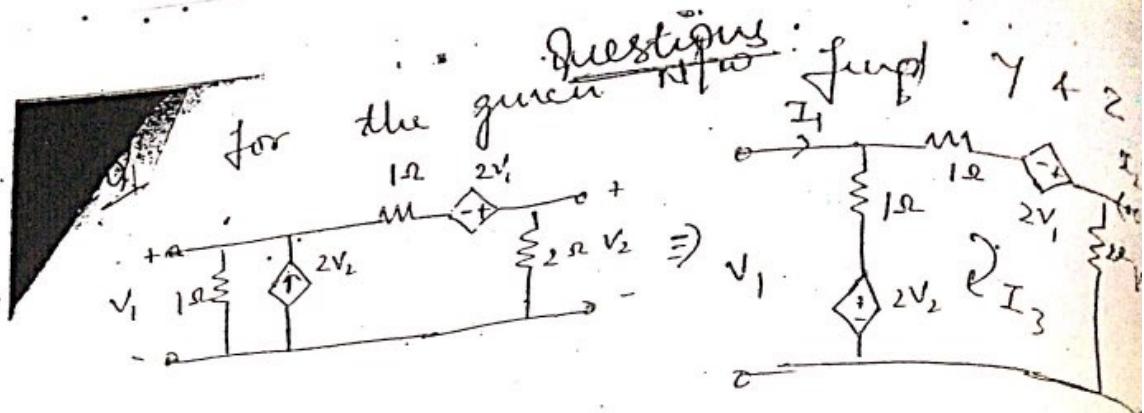

$$\text{So} \rightarrow V_1 = 1(I_1 - I_3) + 2V_2$$

$$V_1 = I_1 - I_3 + 2V_2$$

$$I_3 = I_1 + 2V_2 - V_1$$

$$\rightarrow 1 \cdot I_3 = 2V_1 + 2(I_2 + I_3) - 2V_2 + 1(I_1)$$

$$4I_3 + 2I_2 - I_1 = 2V_1 + 2V_2 - (1)$$

$$\rightarrow V_2 = 2(I_2 + I_3) - (2)$$

$$\text{Putting } I_3 \text{ in } (1) \\ 2V_1 + 2V_2 = 4(I_1 + 2V_2 - V_1) + 2I_2 - 4$$

$$0 = 3I_1 + 6V_2 - 6V_1 + 2I_2$$

$$6(V_1 - V_2) = 3I_1 + 2I_2 \leftarrow \\ \text{Putting } I_3 \text{ in } (2)$$

$$\& V_2 = 2I_2 + 2(I_1 + 2V_2 - V_1)$$

$$0 = 2I_2 + 2I_1 + 5V_2 - 2V_1$$

$$2V_1 - 3V_2 = 2(I_2 + I_1) \leftarrow$$

$$(3) - (4)$$

$$\underline{\underline{4V_1 - 3V_2 = I_1}} \leftarrow (5)$$

$$180 \quad I_1 = 4V_1 - 3V_2 \quad \text{--- (a)}$$

Putting (b) in (a)

$$2V_1 - 3V_2 \Rightarrow 2(4V_1 - 3V_2) + 2I_2$$

$$I_2 = -\frac{6}{2}V_1 + \frac{3}{2}V_2 \quad \text{--- (b)} \quad 17$$

$$\frac{1}{2} - 3V_1 + \frac{3}{2}V_2$$


Using (a) & (b)

$$Y = \begin{bmatrix} 4 & -3 \\ -3 & \frac{3}{2} \end{bmatrix}$$

$$Z = [Y]^{-1} = \begin{bmatrix} \frac{1}{2} & -1 \\ -1 & \frac{4}{3} \end{bmatrix}$$

Ans


Find Y-param.

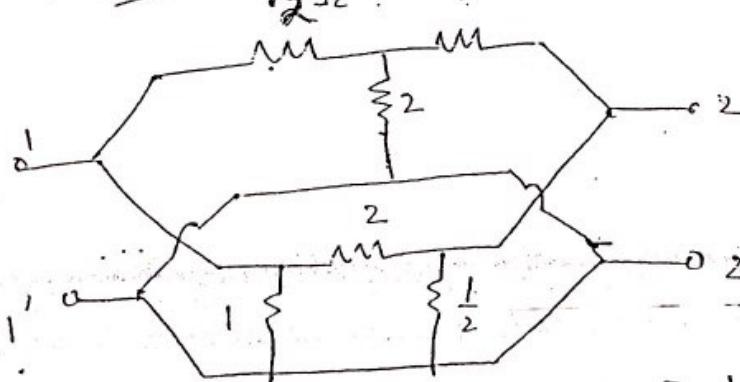

$$Y_A = [Z_A]^{-1} = \begin{bmatrix} \frac{1}{2} + 2 & 2 \\ 2 & 2 + 1 \end{bmatrix}^{-1} = \begin{bmatrix} \frac{6}{7} & -\frac{4}{7} \\ -\frac{4}{7} & \frac{5}{7} \end{bmatrix}$$

$$Y_B = \begin{bmatrix} \frac{1}{2} + \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} + 2 \end{bmatrix} = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{5}{2} \end{bmatrix} \quad Y = Y_A + Y_B$$

for the given N/W find image para.

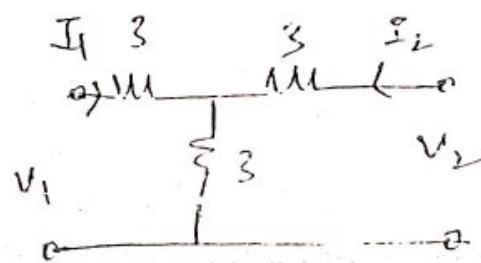


$$A = \frac{v_1}{v_2} = \frac{I_1}{I_2}$$

$$B = 9 \Omega = \frac{v_1}{I_1}$$

$$C = \frac{1}{3} \Omega = \frac{I_1}{v_2}$$

$$D = 2 \cdot \frac{I_1}{I_2}$$
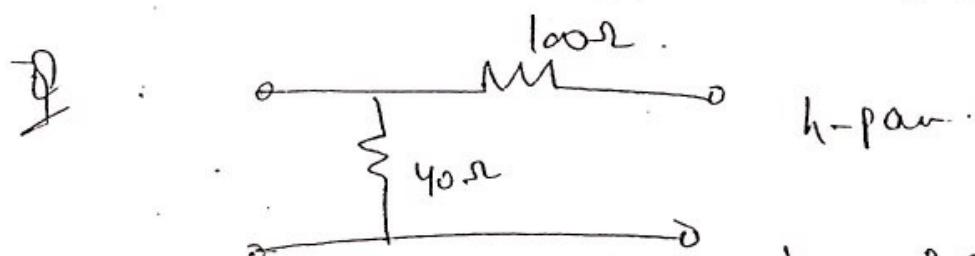
$$Z_{II} = \sqrt{\frac{AB}{CD}} = \sqrt{\frac{2 \times 9}{\frac{1}{3}}} = \sqrt{27} = 5.2 \Omega$$




$$h_{11} = \frac{200}{7}$$


$$h_{21} = -2$$

$$h_{12} = \frac{2}{7}$$

$$h_{22} = \frac{1}{140}$$

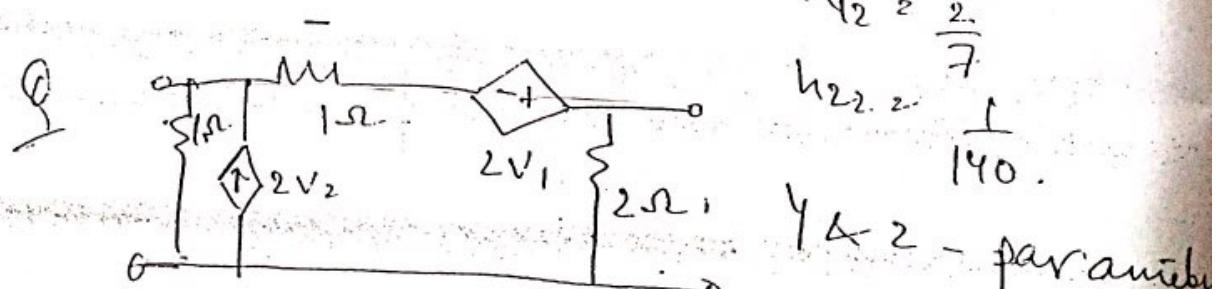

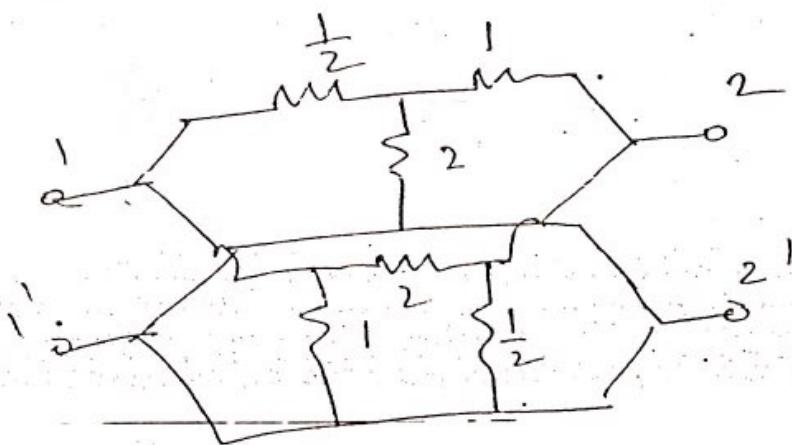
$$\therefore Y = \begin{bmatrix} 4 & -3 \\ -3 & \frac{3}{2} \end{bmatrix} \quad \therefore Z = \begin{bmatrix} \frac{1}{2} & -1 \\ -1 & \frac{4}{3} \end{bmatrix}$$



Y-parameters:

35


Q Determine T-parameters.

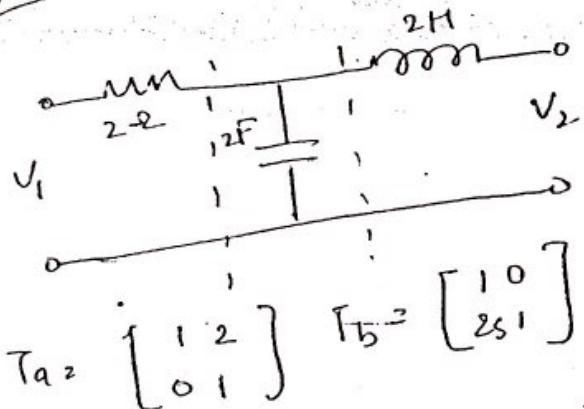

$$T_a = \begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix}, \quad T_b = \begin{bmatrix} 1 & 0 \\ 2s & 1 \end{bmatrix}, \quad T_c = \begin{bmatrix} 1 & 2s \\ 0 & 1 \end{bmatrix}.$$

$$T = \begin{bmatrix} 4s+1 & 2(4s^2+s+1) \\ 2s & 4s^2+1 \end{bmatrix}$$

Q Find Y-parameters

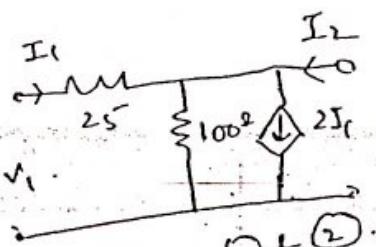

$$I_1 + I_2 = \frac{V_2}{100} + 2I_1 \quad \text{Form } ① \perp ②.$$

$$I_1 = -\frac{V_2}{100} + 5_2 \quad \text{From } ① - ②$$

$$\text{Also } I_1 = \frac{V_1 - V_2}{25} \quad \text{From } ③ \quad \text{From } ① - ②$$

$$\frac{V_1 - V_2}{25} = \frac{-V_2}{100} + 5_2$$

$$I_2 = \frac{1}{25} V_1 - \frac{3}{100} V_2$$

$$Y_{11} = \frac{1}{25}, \quad Y_{12} = \frac{1}{25}$$



N/W Theorems

36

→ electric ckt / N/W

→ star-delta transformation.


→ Source trans.

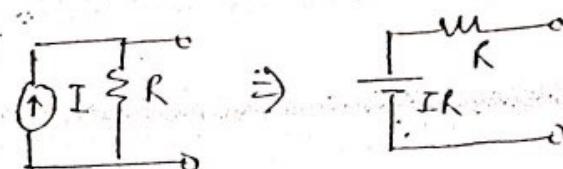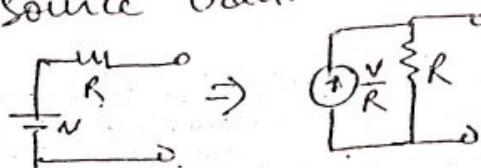

→ Kirchoff's Law \rightarrow KCL + KVL

→ Super node Analysis

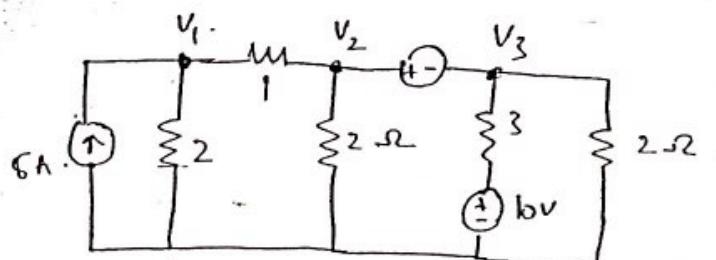↳ If a branch has only a V.S. then the adjacent nodes are considered as 1 node & KCL is applied as usual.



At node

$$5 = \frac{V_1}{2} + \frac{V_1 - V_2}{1}$$

$$3V_1 - 2V_2 = 10$$

At Super node (i.e. 2 & 3)

$$\frac{V_2 - V_1}{1} + \frac{V_2}{2} + \frac{V_3 - 10}{3} + \frac{V_3}{2} = 0$$

$$1 - 6V_1 + 9V_2 + 5V_3 = 20$$

$$\rightarrow V_2 - V_3 = 20$$

$$V_3 = 12V$$

$$I_2 = \frac{V_3 - 10}{3} = \underline{\underline{\frac{2}{3}A}}$$


3x

Super-mesh Technique

If a branch in the circuit has a C.S., then applying KVL is difficult so we may apply super-mesh tech., in which a super-mesh is constituted by 2 adjacent loops that have a common C.S.

Find I

Super mesh 1 & 3

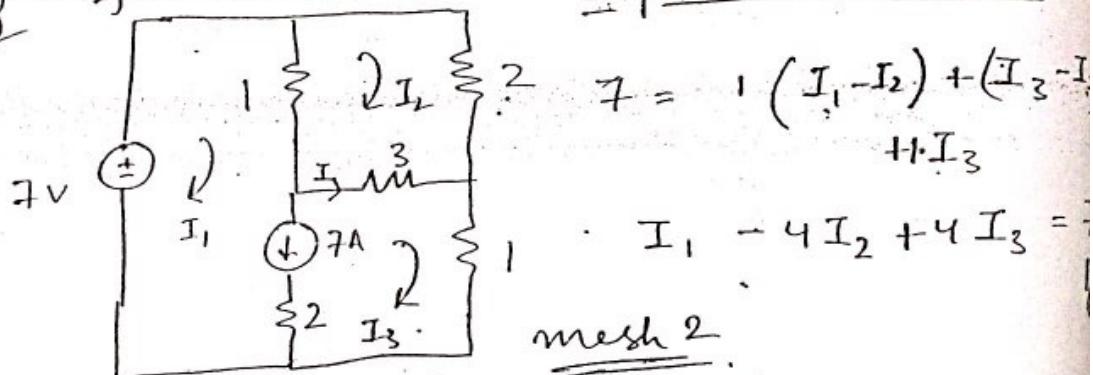

$$1(I_2 - I_1) + 2I_2 + 3(I_2 - I_3) = 0.$$

$$-I_1 + 6I_2 - 3I_3 = 0. \quad (2)$$

$$I_1 - I_3 = 7 \quad (3) \Rightarrow I_1 = 7 + I_3.$$

Solving eq (1) (2) & (3).

$$I_1 = 9A, I_2 = 2.5A \text{ & } I_3 = 2A$$

$$I = I_2 - I_3 = 5A$$

Superposition theorem :

In an active linear n/w containing several sources, the overall response in any branch in the n/w equals the algebraic sum of the responses of each individual source considered separately with all other sources made inoperative.

Applⁿ → ① any linear ckt having time varying or time-invariant elements.

② → ckt any analysis when large no. of independent sources are present.

Limitations → ① not applicable to ckt containing dependent sources only. & non-linear elements
also to

② not useful for ckt having like diode etc less than 2. independent sources.

Reciprocity theorem

ratio of excitation to response remains invariant on changing the point of applⁿ of both.

Applⁿ → to linear, time-invariant n/w


of passive n/w elements.

This thrm provides bilateral property of n/w.

Limitations:

- ① w/A to dependent source
- ② w/A to any time varying element.
- ③ w/o the non-linear elements.

Dues
①

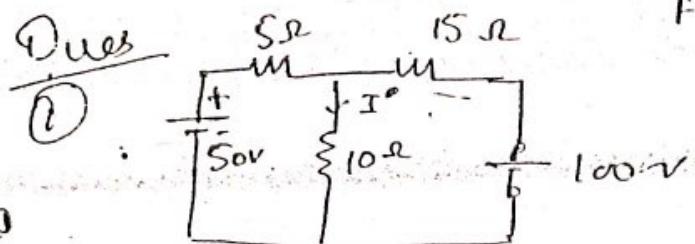

Find I by Superpos.
theorem.


$$I' = \frac{30}{11}$$

$$I'' = \frac{20}{11}$$

$$I = \frac{80}{11} = 4.5 \text{ A}$$


$$I_2 = \frac{20 \times 4}{4+2+2} = 10 \text{ A}$$

Q-

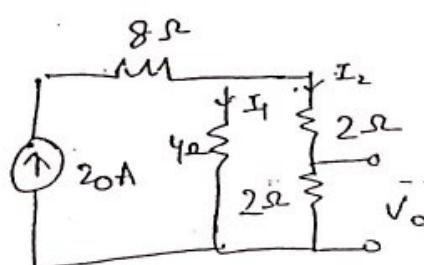

$$V_o = 2 \times 10 = 20 \text{ V}$$

→ Verify reciprocity theorem

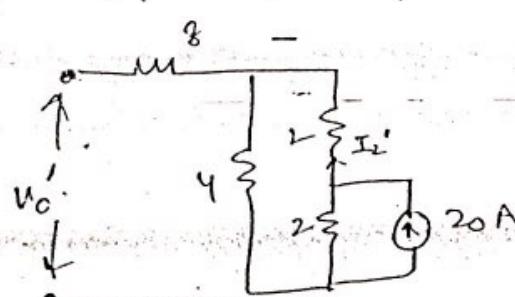


$$I_2' = \frac{2 \times 20}{2+(4+2)} = 5 \text{ A}$$

$$V_o' = 5 \times 4 = 20 \text{ V}$$

Thevenin's Theorem

find I

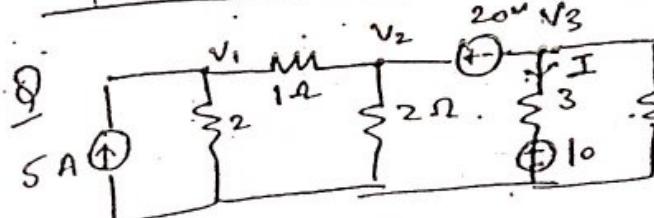

node 1

$$5 = \frac{V_1}{2} + \frac{V_1 - V_2}{2} \Rightarrow \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 5 \quad (1)$$

node 2 & 3

$$\frac{V_2 - V_1}{2} + \frac{V_2}{2} + \frac{V_3 - 10}{2} + \frac{V_3}{2} = 0 \quad (2)$$

$$\Rightarrow -6V_1 + 9V_2 + 5V_3 = 20 \quad (2)$$

$$V_2 - V_3 = 20 \quad (3)$$

from (1) & (2)

$$3V_1 - 2V_3 = 50 \quad (1)$$


$$\Rightarrow V_1 = \frac{50 + 2V_3}{3}$$

Neville's theorem :

With respect to terminal pair AB, the n/w N may be replaced by a volt. source V_{th} in series with an int. imp. Z_{th} . Then

V_{th} = Th. volt. pot. diff. b/w A & B.

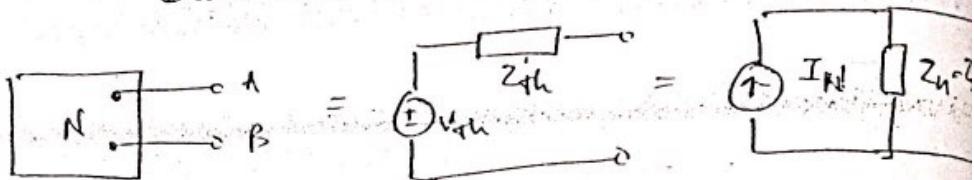Z_{th} = int. imp. of N/w N as seen from terminals A & B. with all sources sets



$$I_L = \frac{V_{th}}{Z_{th} + Z_L}$$

Norton's theorem :

With respect to terminal pair AB, the N/w N may be replaced with a I.S (1). I_N in II will

I_N = I from A to B. on S.C. A & B.

$$Z_N = Z_{th}$$

$$Z_L = V_{th} \quad I_L = I_N \cdot \frac{Z_N}{Z_L + Z_N}$$

Case I Ckt having only independent sources.

Let all sources at 0 values

i.e. v.s \rightarrow shorted circuit

& c.s \rightarrow open circuit

{ leaving behind
their internal resis.

Case II independent + dependent

calc. V_{th} & I_N then

$$Z_{th} = Z_N = \frac{V_{th}}{I_N}$$

Case III only dependent sources


Apply voltage V at AB terminal
current I flow due to this V .

$$\text{Now } Z_N = \frac{V}{I}$$

Applicability ① replacement of a large complicated
n/w by simple equivalent.


② Imp. Limitations:

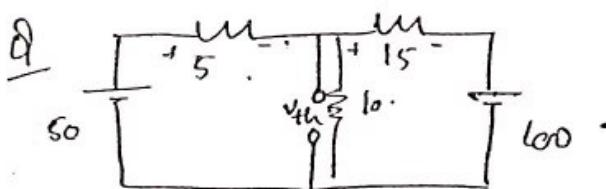- ① N/A to unilateral elements
- ② N/A to non linear elements
- ③ ?




$$V_{th} = 50 - 5 I_o = 15 I_o + 100 \Rightarrow 15(-2.5) + 100 = 62.5$$
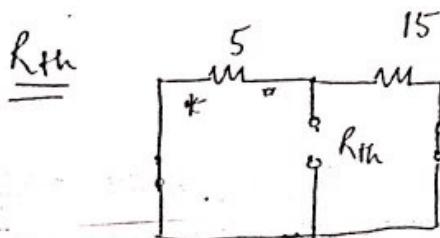
$$I_o = \frac{50 - 100}{20} = -2.5 \text{ A}$$



$$R_{th} = 5 \parallel 15 = \frac{5 \cdot 15}{20} = 3.75$$
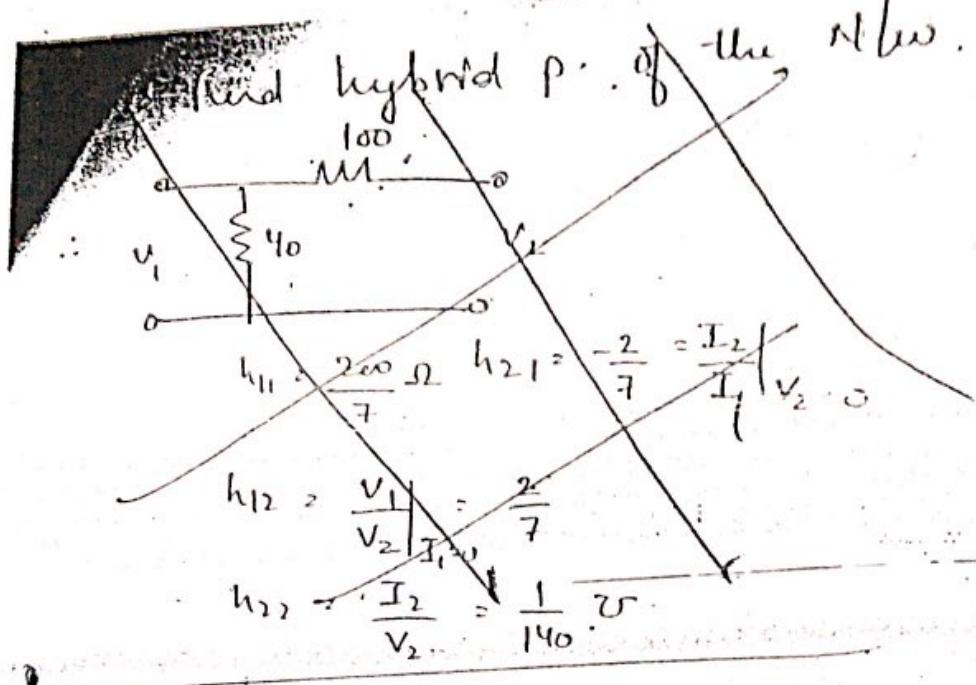
$$I = \frac{V_{th}}{R_{th} + 10} = \frac{62.5}{3.75 + 10} = \frac{62.5}{13.75} = 4.548 \text{ A}$$



Millman's theorem:


Can be used for v.s or c.s.

(A) for v.s.:

If for n voltage sources having series imp. operating in parallel, then by Millman's theorem, we can determine E_m , the equivalent v.s & Z_m the series imp.

$$E_m = \frac{\sum E_i^o Y_i^o}{\sum Y_i^o}$$


$$Z_m = \frac{1}{\sum_{i=1}^n Y_i^o}$$

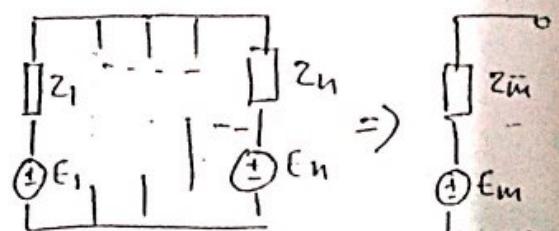

Proof v.s. to c.s transformation.

$$I_i = \frac{E_i^o}{Z_i^o} = E_i^o Y_i^o$$

$$\therefore Y_i^o = \frac{1}{Z_i^o}$$

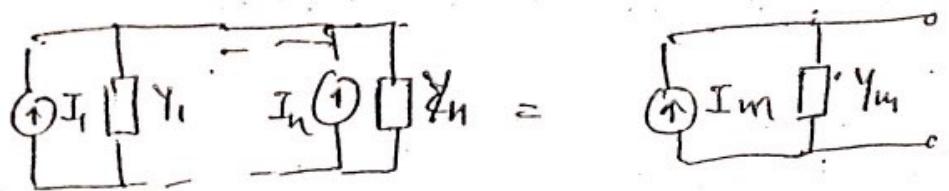

$$I_m \cdot \sum I_i^o = \sum E_i^o Y_i$$

$$Y_m = \sum Y_i$$

$$E_m = \frac{I_m}{Y_m} = \frac{\sum E_i^o Y_i}{\sum Y_i}$$


II by for L.S connected
in no. of a.C.s with II imp. in series

$$\text{then } I_m = \frac{E_m}{Z_m} = \frac{\sum I_i^o Z_i^o}{\sum Z_i}$$

Appl (1) applies only to independent

MPTT is used for analysing comm. circuits where the transfer of max. power from source to load is not highest.

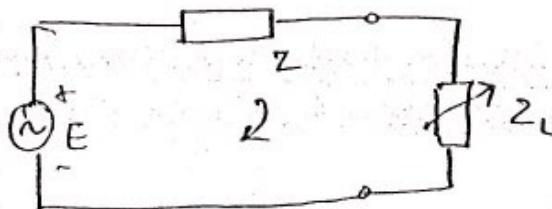Max. Power O/P is obtained from an A.C. circuit when the load imp. = the complex conjugate of the int. imp. of the ckt as seen from terminals of the load.



→ MPTT aims at finding Z_L such that the power dissipated in it is max.

$$I = \frac{E}{(Z+Z_L)^2}$$

$$P = |I|^2 R_L$$

$$Z = R + jX \quad \& \quad Z_L = R_L + jX_L$$

$$P = \frac{E^2}{(R+R_L)^2 + (X+X_L)^2} \cdot R_L$$

for max. Power

$$\frac{\partial P}{\partial X_L} = 0. \quad \frac{\partial P}{\partial X_L} = \frac{0 - E^2 \cdot R_L \cdot 2(X+X_L)}{\left[(R+R_L)^2 + (X+X_L)^2 \right]^2}$$

$$E^2 \cdot R_L \cdot 2(X+X_L) = 0$$

$$\Rightarrow X + X_L = 0 \quad \Rightarrow \quad X = -X_L$$

Putting $x_L = -x$.

$$P = \frac{E^2 R_L}{(R + R_L)^2}$$

$$\frac{\partial P}{\partial R_L} = 0$$

$$\frac{\partial P}{\partial R_L} = \frac{(R + R_L)^2 \cdot E^2 \cdot 1 - E^2 R_L \cdot 2 \cdot (R + R_L)}{[(R + R_L)^2]^2}$$


$$E^2(R + R_L) - 2E^2 R_L = 0$$

$$R_L = R$$

$$\therefore Z_L = Z^*$$

$$\lim_{R_L \rightarrow \infty} \frac{E^2}{4R_L} = \frac{(E/2)^2}{R_L}$$

(B)

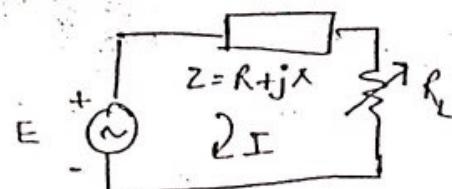

In this case

$$R_L = \sqrt{R^2 + x^2} = |Z|$$

Various Cases

① D.C. case

$$R_L = R \text{ (Thv.'s resistance)}$$


② for A.C. case

(a) $Z_L = \frac{V}{I}$


(b) $R_L = |Z| \sqrt{R^2 + x^2}$

for the ckt when $Z_L = jX_L$ is fixed

$$R_L^2 = R^2 + (X + X_L)^2$$

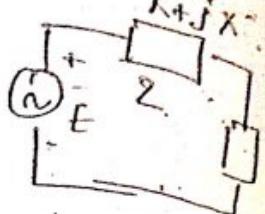


(9)

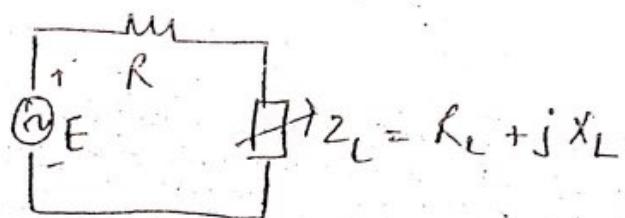

$$R_L^2 = R^2 + X_L^2$$

Tellegen's theorem

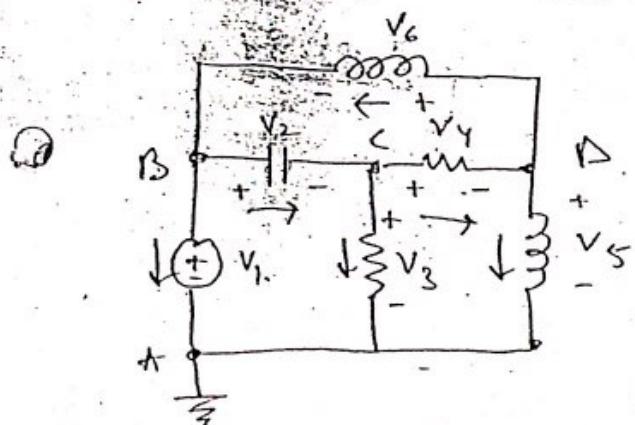- Completely independent of nature of elements.
- based on KVL & KCL.




If the ckt having
nodes & b branches w/
branch voltage be v_k
the " current be i_k

$k \rightarrow 1 \text{ to } b$.

Tellegen's thm states that

$$\sum_{k=1}^b v_k i_k = 0$$

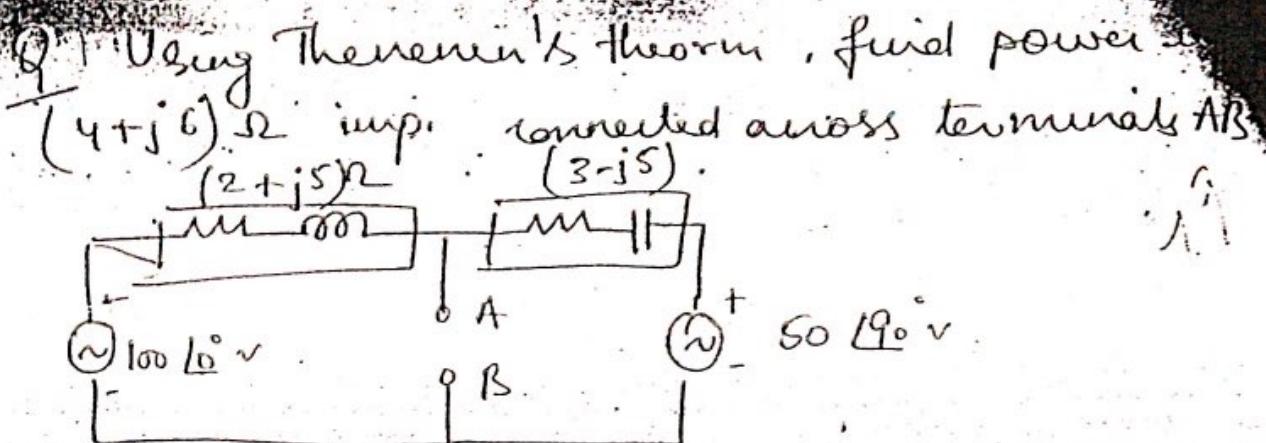This implies that the sum of instt power delivered to all branches of a circuit is



$$\text{for } V_{th} = 100 - \text{drop in } (2+j5)$$

$$= \text{drop in } (3-j5) + 50\angle 19^\circ$$

$$= 100\angle 10^\circ - (2+j5) \left(\frac{100\angle 10^\circ - 50\angle 19^\circ}{(2+j5) + (3-j5)} \right)$$

$$= 100\angle 10^\circ - (2+j5) \left(\frac{100 - j50}{5} \right)$$

$$= 100\angle 10^\circ - [40 + j100 - j20 + 50]$$

$$= 100 - j80 = 80.62 \angle -82.87^\circ \text{ V}$$

~~$\Rightarrow (2+j5) \parallel (3-j5)$~~

$$\Rightarrow \frac{(2+j5)(3-j5)}{(2+j5) + (3-j5)} = \frac{31+j5}{5} = (6.2+j1)\Omega$$

$$I_L = \frac{V_{th}}{Z_{th} + Z_L} = \frac{80.62 \angle -82.87^\circ}{(6.2+j1) + (4+j6)}$$

$$= \frac{80.62 \angle -82.87^\circ}{12.371 \angle 34.61^\circ} = 6.52 \angle -117.33^\circ \text{ A}$$

$$\text{Power} = I_i^2 \times R_L = (6.52)^2 \times 4 = 170.04 \text{ W}$$

Properties:

- ① N_1 & $N_2 \rightarrow$ 2 diff. crts having same graph with same reference directions assigned to the branches in the 2 crt.
 Let for $N_1 \rightarrow V_{1K}^o$ & i_{1K}^o
 $N_2 \rightarrow V_{2K}^o$ & i_{2K}^o

All V_s^o 's & I_s^o 's satisfy Kirchhoff's laws

Sc by Tellegen's theorem


$$\sum_{k=1}^b V_{1K}^o i_{2K}^o = 0 \text{ & } \sum_{k=1}^b V_{2K}^o i_{1K}^o = 0$$

- ② If t_1 & t_2 are 2 diff. instt of obs. it still follows that

$$\sum_{k=1}^b V_k(t_1) \cdot i_k(t_2) = 0$$

Tellegen's \Rightarrow

Verify -

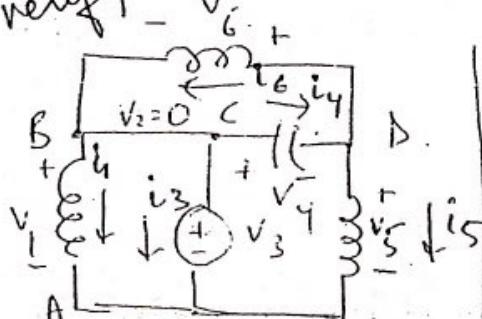

$$V_1 = 5V, V_4 = 2V$$

$$V_2 = 0 \text{ & } i_1 = 2A, i_3 = 1A$$

ABCDA

$$\underline{\text{SOP}} \quad V_1 = V_3 = 5$$

ACBDA

$$V_5 = V_3 - V_4 = 5 - 2$$

BEDB

$$-V_4 - V_6 = 0$$

$$\therefore V_6 = -V_4 = -2$$


$$\text{at Node B: } i_6 = i_1 + i_2 = 2A$$

$$\therefore i_2 = i_3 + i_4 \Rightarrow i_4 = -i_3 = -1A$$

$$\therefore i_5 = i_4 - i_6 = -3A \therefore$$

in
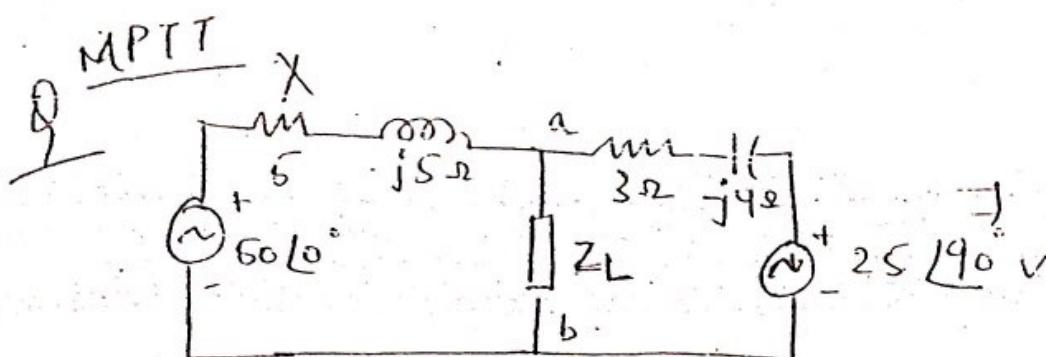
$$(5.2) + 0.0 + 5.1 + 2 \cdot (-1) + 3 \cdot (-3) + (-2) \cdot (2) = 0$$



Z_L is varying in $R_2 - X_2$

find Z_L for Max. power using Nillman theorem.
also calc. max. power.

soln

$$E_1 = 50 \angle 0^\circ = 50 \quad Y_1 = \frac{1}{Z_1} = \frac{1}{5+j5} = 0.1 - 0.1j$$

$$Z_1 = (5 + j5) \Omega$$

$$E_2 = 25 \angle 90^\circ = 25 \cos 90^\circ + j 25 \sin 90^\circ$$

$$= +j 25 \text{ V}$$

$$Z_2 = 3 - j 4 \Omega$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{3-j4} \frac{3+j4}{3+j4} = \frac{3+j4}{9-j16} = \frac{3+j4}{25}$$


$$E_m = \frac{E_1 Y_1 + E_2 Y_2}{Y_1 + Y_2} = \frac{1-j2}{0.22+j0.06} = 9.807 \angle -78.65^\circ \text{ V}$$

$$Z_m = \frac{1}{Y_1 + Y_2} = \frac{1}{0.22+j0.06} = 4.385 \angle -15.25^\circ$$

$$= 4.23 - j 1.15$$


$$Z_L = Z_m^* = 4.385 \angle 15.25^\circ = 4.23 + j 1.15$$
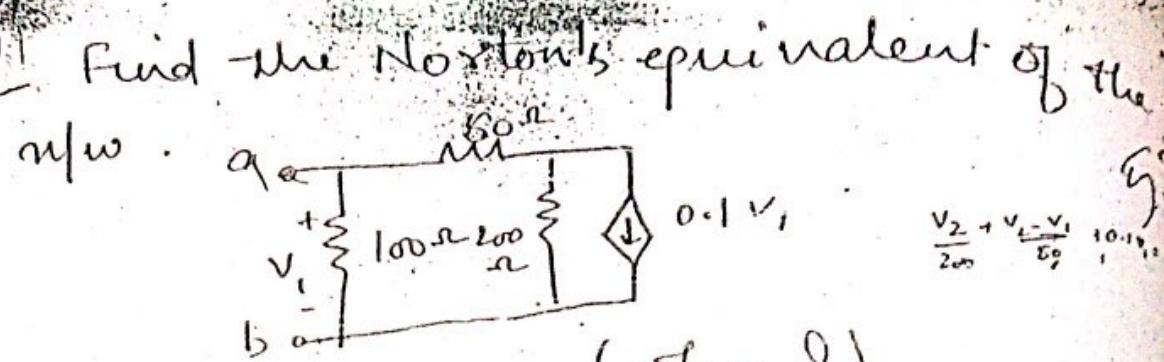
$$P_m = \frac{E_m^2}{4R_L} = \frac{(9.807)^2}{4 \times 4.23} = 5.68 \text{ W}$$



$$I_{SC} = I_N = 0 \quad (\text{why?})$$

$$R_N \rightarrow \\ \equiv :$$

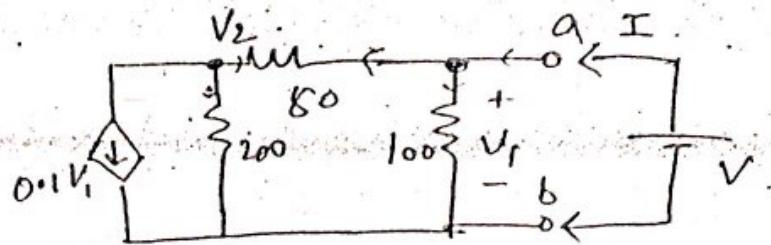

$$\text{Now } R_N = \frac{V}{I}$$

$$I = \frac{V_1}{100} + \frac{V_1 - V_2}{50} \Rightarrow 100I = 3V_1 - 2V_2$$

$$\frac{V_1 - V_2}{50} = \frac{V_2 + 0.1V_1}{200} \Rightarrow V_2 = -\frac{16}{5}V_1 \quad (1)$$


$$\text{also } V = V_1 \quad (2)$$

from (1) & (2)

$$100I = 3V_1 - 2\left(-\frac{16}{5}V_1\right)$$

$$\underline{\underline{R_N = \frac{V_1}{I} = \frac{500}{47} = 10.63}}$$

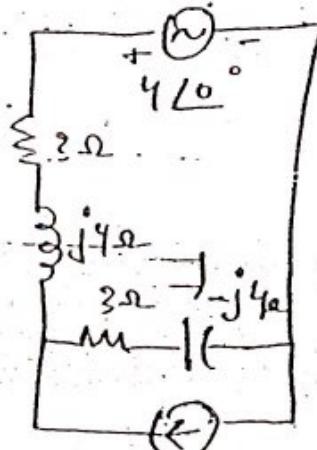Ques: Determine I in capacitor by superposition theorem.



$$\textcircled{1} \quad \underline{V \cdot S} \rightarrow 4\angle 0^\circ$$

$$I' = \frac{4\angle 0^\circ}{(3+j4)+(3-j4)} = \frac{4\angle 0^\circ}{6} = \frac{2}{3}\angle 0^\circ$$

$$\textcircled{2} \quad \underline{6\angle 0^\circ} \rightarrow 2\angle 90^\circ$$

$$I'' = 2\angle 90^\circ \times \frac{3+j4}{(3+j4)+(3-j4)}$$

$$= 2j \times \frac{3+j4}{6} = \frac{-4+j3}{3}$$


$$I = I' + I'' = \left(-\frac{4}{3} + j\frac{3}{3}\right) A$$

$$= \frac{2}{3} - \frac{4}{3} + j = -\frac{2}{3} + j \approx 1.2 / 123.7^\circ A$$

Verify reciprocity theorem

10

54

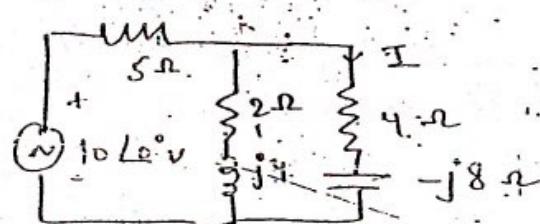

Case I

$$Z_{eff} = [(4-j8) || (2+j4)] + 5$$

$$= \frac{(4-j8)(2+j4)}{(4-j8)+(2+j4)} + 5$$

$$= \frac{8+j16-j16+32}{6-j4}$$

$$= \frac{40}{6-j4} + 5 = \frac{70-j20}{6-j4} + 5$$

$$= \frac{72.8 \angle -15.94^\circ}{7.21 \angle -33.69^\circ}$$

$$< 10.1 \angle 17.75^\circ$$

$$I = \frac{10 \angle 0^\circ}{10.1 \angle 17.75^\circ} \cdot \frac{(2+j4)}{(2+j4)+(4-j8)}$$

$$= 0.614 \angle 79.73^\circ A$$

Case II

$$Z_{\text{eff}} = \left[5 \parallel (2+j^4) \right] + (4-j^8) \quad \underline{\underline{65}}$$
$$= \frac{10+j^{20}}{7+j^4} + (4-j^8), \quad \frac{10-j^{20}}{7+j^4}$$

$$\frac{72.8 \angle -15.2^\circ}{8.06 \angle 29.74} = 9.03 \angle -45.64^\circ$$

$$I' = \frac{10 \angle 0^\circ}{9.03 \angle -45.64^\circ} \cdot \frac{2+j^4}{5+(2+j^4)}$$
$$= 0.614 \angle 79.3^\circ \text{ A} \quad \underline{\underline{}}$$

N/w Synthesis
 Elements of Realizability theory:
 $\text{① } \rightarrow T(s) = \frac{N(s)}{E(s)}$ Response
 Excitation

①
 $E(s)$

(j)

① Causality & Stability

↓
 response of an $n/w = 0$ must be for $t < 0$.

for n/w to be

Stable: \rightarrow following 3 condit' must be satisfied.

① $T(s)$ can't have poles in right half of s -pla

② $T(s)$ can't have multiple poles in the $(j\omega)$ axis

③ degree of $N(s)$ of $T(s)$ can't exceed the degree of $d(s)$ by more than unity.

$$T(s) = \frac{N(s)}{D(s)}$$

② Hurwitz Polynomial

It is the $D(s)$ polynomial of the n/w func' satisfying certain condit'

A polynomial $P(s)$ is Hurwitz if

① $P(s)$ is real when s is real

② roots of $P(s)$ have real parts which are 0

or negative

Properties of Hurwitz

$$P(s) = a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0$$

- ① All coefficients a_i must be +ve.
- ⇒ none of the coeff. b/w highest order term in s & the lowest order term may be 0. unless the polynomial is even or odd.
- ② Both odd & even parts of a Hurwitz polynomial $P(s)$ have roots on $j\omega$ axis only.

even $\rightarrow M(s)$

odd $\rightarrow N(s)$

$$\text{so } P(s) = M(s) + N(s).$$

then $M(s)$ & $N(s)$ have roots on $j\omega$ axis only.

- ③ If $P(s) \rightarrow$ either even or odd, all its roots are on $j\omega$ axis.

- ④ Continued fraction expansion of the ratio odd to even or vice versa.

yields all the quotient terms

$$\text{As } \Psi(s) = \frac{N(s)}{M(s)} \text{ or } \frac{M(s)}{N(s)}$$

$$\Psi(s) = q_1 s + \frac{1}{q_2 s + \frac{1}{q_3 s + \dots}}$$

• (5) If $P(s) \rightarrow$ Hurwitz poly.
 & $w(s) \rightarrow$ multiplicative factor
 then $P_1(s) = P(s) \cdot w(s)$ is also Hurwitz
 if $w(s)$ is Hurwitz polynomial.

(6) If $P(s) \rightarrow$ only odd or even then
 cont. fraction expansion is not poss.
 so $P(s) \rightarrow$ Hurwitz by $\frac{P(s)}{P'(s)}$ gives
 a continued fr. ex.

Q Check whether the given polynomial
 $P(s) = s^4 + s^3 + 5s^2 + 3s + 4$ is Hurwitz or not

① all coeff. of $P(s)$ are pos. so $P(s) \rightarrow$ real
 for $s \text{ real}$

② even & odd

$$M(s) = s^4 + 5s^2 + 4$$

$$N(s) = s^3 + 3s$$

$$\frac{M(s)}{N(s)} = \frac{s^3 + 3s}{s^4 + 5s^2 + 4} = \frac{s^3 + 3s}{s^4 + 2s^2 + 2s^2 + 4}$$

$$= \frac{s^3 + 3s}{s^2(s^2 + 2s + 4)}$$

$$= \frac{s^3 + 3s}{s^2(s+2)^2}$$

$$= \frac{s(s+3)}{s^2(s+2)^2}$$

$$= \frac{s+3}{s(s+2)^2}$$

$$Q. \quad P(s) = s^4 + s^3 + 2s^2 + 4s + 1$$

~~Q1~~ is satisfied.

$$\textcircled{2} \quad M(s) = s^4 + 2s^2 + 1$$

$$N(s) = s^3 + 4s.$$

$$\Psi(s) = \frac{M(s)}{N(s)}$$

$$(s^3 + 4s) \Big| s^4 + 2s^2 + 1 \quad (s.$$

$$\frac{s^4 + 4s^2}{-2s^2 + 1} \Big| s^3 + 4s \quad \left(-\frac{1}{2}s \right) <$$

$$\frac{s^3 - \frac{s}{2}}{-2s^2}$$

$$\frac{\frac{9}{2}s}{-2s^2} \Big| -2s^2 + 1 \quad \left(-\frac{2}{9} \cdot 2s = -\frac{4}{9}s \right) <$$

$$1) \frac{9}{2}s \Big| \frac{9}{2}s$$

not Hurwitz.

Coef of -ve quotient term $s \frac{\frac{9}{2}s}{-2s^2}$

Q. Find the range of values of a so that

~~Q1~~ $P(s) = s^4 + s^3 + as^2 + 2s + 3$ is Hurwitz.

~~Q1~~ All a_i must be true so $a > 0$.

~~Q2~~ $M(s) / N(s)$

$$a > 2 \quad \cancel{a > 3.5} \\ \text{so } a > 3.5$$

Positive Real func

$$T(s) = \frac{N(s)}{D(s)}$$

satisfied

- (1) $T(s)$ is real for s real.
- (2) $N(s)$ is Hurwitz polynomial.
- (3) $T(s)$ may have poles on the $j\omega$ axis.

- (4) real part of $T(s)$ is greater than or equal to 0 for real part of $s \geq 0$.

$$\operatorname{Re}[T(s)] \geq 0 \quad \operatorname{Re} s \geq 0$$

$$T(s) = \frac{N(s)}{D(s)} = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)}$$

$$T(s) = \frac{M_1 + N_1}{M_2 + N_2} \cdot \frac{M_2 - N_2}{M_2 - N_2}$$

$$\frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2}, \quad \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2}$$

$$\operatorname{Ev}[T(s)] = \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2}$$

$$\operatorname{odd}[T(s)] = \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2}$$

$$\text{if } s = j\omega$$

even part \rightarrow real

odd part \rightarrow imag.

$$\operatorname{Re} [T(j\omega)] = \operatorname{Ev}[T(s)]|_{s=j\omega}$$

$$\text{if } \operatorname{Im} [T(j\omega)] = \operatorname{oob}[T(s)]|_{s=j\omega}$$

so To prove this correct

$$\operatorname{Re} [T(j\omega)] \geq 0 \text{ for all } \omega$$

$$\text{or } M_1(j\omega) \cdot M_2(j\omega) - N_1(j\omega)N_2(j\bar{\omega}) \geq 0$$

Since Denominator is always +ve.

Properties:

(1) If $T(s) \rightarrow P + \gamma$ then $\frac{1}{T(s)} \rightarrow P + \gamma$

If $Z(s) \rightarrow P + \gamma$

then $Y(s) \rightarrow \text{also } P + \gamma$

(2) Sum of $P + \gamma$ & $P' + \gamma'$ can't be

(3) Poles & zeros of a $P + \gamma$ in the right half of s-plane

in addition only simple poles with real the residues can exist on jw-axis

(4) poles & zeros of a p.d.f are real occur in conjugate pair.

(5) highest power of $N(s)$ & $D(s)$ may differ atmost by unity

\Rightarrow prohibits multiple poles or zeros at $s=0$.

(6) lowest power of $D(s)$ & $N(s)$ may differ by atmost unity
 \Rightarrow prohibits multiple poles or 2 at $s=0$.

Necessary & sufficient condⁿ for $T(s)$ to be p.d.f

(1) $D(s)$ must be hurwitz.

(2) This condⁿ is checked only when the poles of $T(s)$ are on the jw-axis otherwise not.

is tested by making partial fraction expansion of $T(s)$ & checking whether the residues of the poles on jw-axis are +ve & real.

Carlet^u 3 $\rightarrow \operatorname{Re}[T(j\omega)] \geq 0$ for all ω . 63 ✓

$M_1(j\omega) M_2(j\omega) - N_1(j\omega) N_2(j\omega) \geq 0.$

(1) show them. $f(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$ is pos.

~~sol~~ $G \cdot D(s) \rightarrow$ Hurwitz:

(2) \rightarrow doesn't exist.

(3) $M_1 = s^2 + 8 \quad N_1 = 6s$

$M_2 = s^2 + 3 \quad N_2 = 4s$

$M_1 M_2 - N_1 N_2 \geq 0$

$(s^2 + 8)(s^2 + 3) - (6s)(4s) \geq 0$

$s^4 + 13s^2 + 24 \geq 0$

$A(\omega) = \omega^4 + 13\omega^2 + 24 \geq 0$ for all ω .

$$\frac{-3s}{s^2 + 1} \xrightarrow[s \rightarrow \infty]{} \begin{matrix} -3j \\ j^2 + 1 \end{matrix}$$

$$f(s) = \frac{s^3 + s^2 + 3s + 5}{s^2 + 6s + 8}$$

Ansatz: $M(s) = s^3 + 8 \quad N(s) = 6s^3$
 $D(s) \rightarrow \text{Koeffiz.}$

(2) \rightarrow no poles on $j\omega$

$$(3) M_1 = s^2 + 8 \quad M_2 = s^2 + 8$$

$$N_1 = s^3 + 3s \quad N_2 = 6s$$

$$A(\omega^2) = M_1 M_2 - N_1 N_2 \geq 0.$$

$$(s^2 + s)(s^2 + 8) - (s^3 + 3s)(6s) \geq 0.$$

$$-5s^4 - 5s^2 + 40 \geq 0$$

$$-5\omega^4 - 5\omega^2 + 40 \geq 0 \quad (s = j\omega)$$

Since all coeff. \neq not true.

So we use Sturm's test.
 Put $\omega^2 \rightarrow x$.

$$A_0(x) = -5x^2 + 5x + 40.$$

$$A_1(x) = \frac{dA_0}{dx} = -10x + 5$$

$$\frac{A_2(x)}{A_1(x)} = \frac{(K_2x + k_0) - A_1(x)}{A_1(x)} =$$

$$A_1(x)$$

Q Determine whether the func is p.r. or n
~~s+1~~ $Z(s) = \frac{2s^2 + s}{s^3 + s}$

$$\textcircled{1} \quad D(s) = s^3 + s$$

$$\text{then } D(s) = 3s^2 + 1$$

$D(s) \rightarrow$ limit ∞ .


$$\textcircled{2} \quad Z(s) \rightarrow \text{Poles} \Rightarrow s = \pm j1$$

$$Z(s) = \frac{-3s}{s^2 + 1} + \frac{s}{s}$$

$$\text{is } \left| \frac{2s^2 + s}{s(s^2 + 1)} (s^2 + 1) \right|_{s^2 = -1} = \frac{-2 + 5}{-1} = -3$$

Since residue of the poles at
 $s = \pm j1$ is -ve.

so it's not p.r.f.

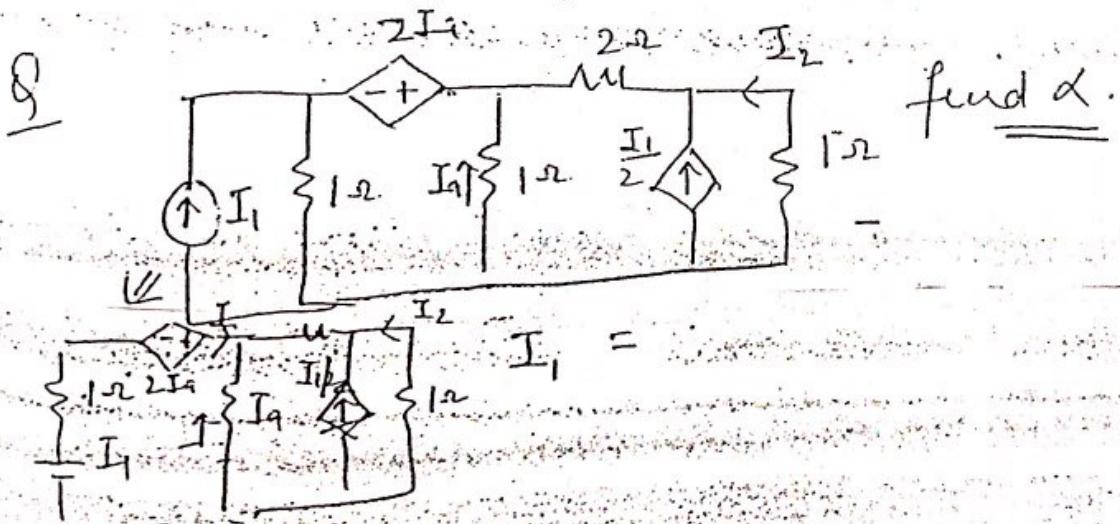

$$\begin{array}{r} \cancel{A_0} - 10x + 5 \\ - 5x^2 + 5x + 40 \quad \left(\frac{x}{2} - \frac{1}{4} \right) \\ - 5x^2 + \underline{5x} \\ \hline 40 \\ \frac{5}{2}x + 40 \\ \frac{5}{2}x + \underline{\frac{5}{4}} \\ \hline \frac{165}{4} \end{array}$$

$$\frac{A_0(x)}{A_1(x)} = \left(\frac{5}{2}x + \frac{1}{4} \right) + \frac{165/4}{-10x + 5}$$

$$A_2 x = -165/4$$

	A_0	A_1	A_2	No. of sign change
$x=0$	+	+	-	$S_{\infty} = 1$
$x=\infty$	-	-	-	$S_{\infty} = 0$

$$S_{\infty} \approx S_0 = 1$$

$\therefore A(\omega^2) \neq 0$ for all ω .

hence given function is not a p.d.f.

Content Feedback

Feel free to submit your issues, suggestions and ratings regarding this course content

[Click Here](#)

Join & Share WhatsApp Group of COLLATE

(Click the button to join group)

MSIT

Semester 3

CSE

IT

ECE

Semester 5

CSE

IT

MAIT

Semester 3

CSE

IT

ECE

Semester 5

CSE

IT

ADGITM (NIEC)

Semester 3

CSE

IT

ECE

Semester 5

CSE

IT

GTBIT

Semester 3

CSE

IT

ECE

Semester 5

CSE

IT

BVP

Semester 3

CSE

IT

ECE

Semester 5

CSE

IT

BPIT

Semester 3

CSE

IT

ECE

Semester 5

CSE

IT

HMR

Semester 3

CSE

IT

ECE

Semester 5

CSE

IT