

Experiment-6

* Aim:- To study the operation of Half Subtractor

* Apparatus:- Connecting wires, power supply, IC ~~7408~~ 7408, IC 7486, IC 7404, LED Display, breadboard.

* Theory:- The half subtractor is a combinational circuit which is used to perform the subtraction of two bits. It has inputs x and y and two outputs 'D' difference and 'Bout' borrow out from the truth table. It is clear that the difference output is 0 if $x = y$ and output is 1 if $x \neq y$. The borrow is one whenever $x < y$

* Procedure:-

1. Connect the IC's on the breadboard as per the circuit diagram.
2. Give +5 V to pin 14 and ground at pin
3. Connect input pins A and B of IC from the binary switch.
4. Connect the output pins D and Bout of an IC from LED.
5. Switch off the power supply and change the combination of A and B and observe the output on LED's.
6. Verify the output from truth table.

* Result:- the truth table of Half Subtractor has been verified and its operation has been studied.

* Precautions:-

1. Input and detach the IC carefully from the breadboard without damaging the pins.

Teacher's Signature _____


Date _____

Expt. No. _____

Page No. 14

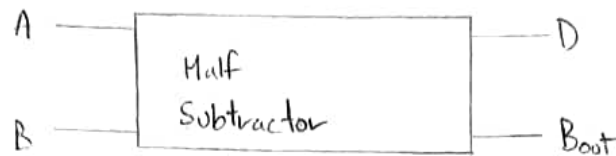2. Take care while supplying voltage to an IC
3. Connecting of IC's should be strictly according to diagram.





★ Truth table

A	B	D	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

★ K-Map for D (Difference)

	B	0	1
A	0		(1)
	1	(1)	

$$D = \bar{A}B + A\bar{B}$$

$$= A \oplus B$$

★ K-Map for Bout (Borrow Out)

	B	0	1
A	0		(1)
	1		

$$B_{out} = \bar{A}B$$

* Circuit Diagram for Half Subtractor

