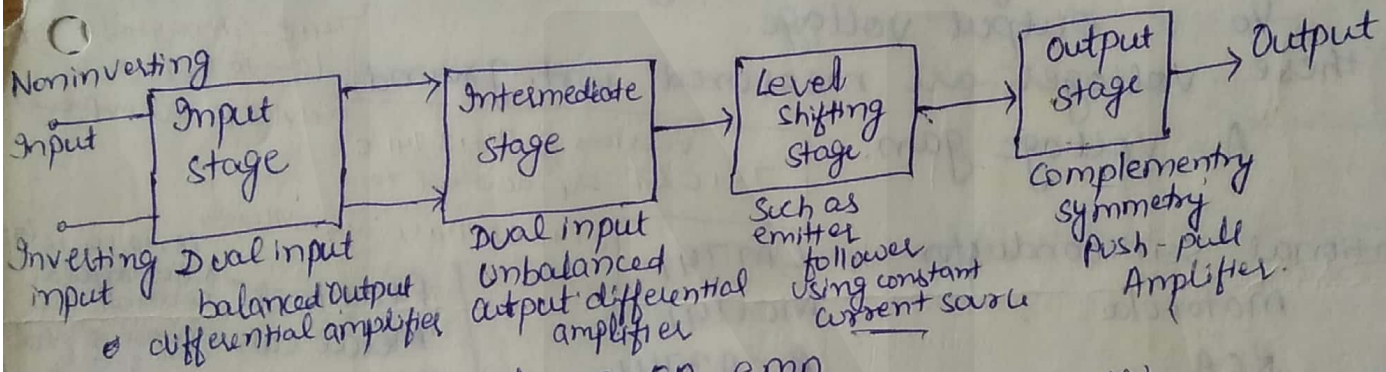




Operational Amplifier:- is a direct coupled, high gain usually consisting of one or more differential amplifier and followed by a level translator and an output stage. It can be used to amplify dc as well as ac ^{input} signals. Operational amplifier is named such as because it was originally designed for mathematical operation such as addition, subtraction, integration and differentiation. Now a days it can be used for dc and ac signal amplification, active filters, oscillators, comparators, regulators etc.



Block Diagram of an op-amp.

The first stage provide most of the voltage ^(60dB) gain of the amplifier. & it provides the ~~most of voltage~~ input resistance of op amp. The intermediate stage is usually driven by output of first stage. Next stage is level shifting stage. As direct coupling is used, the dc voltage at output of intermediate stage is well above the ground potential. Hence a level shift stage is used after the intermediate stage to shift the dc level at o/p of intermediate stage to shift the dc level at output of inter downward to zero volts w.r. ground. The output stage is usually a complementary amplifier output stage. The output stage increases the output voltage swing & raising the current supplying capability of op amp. It also establishes the low output resistance. Output of opamp is measured at output of this final stage push pull amplifier w.r. ground.

Symbol of Op-amp :-

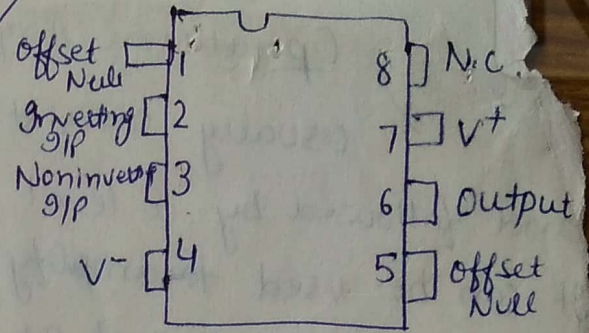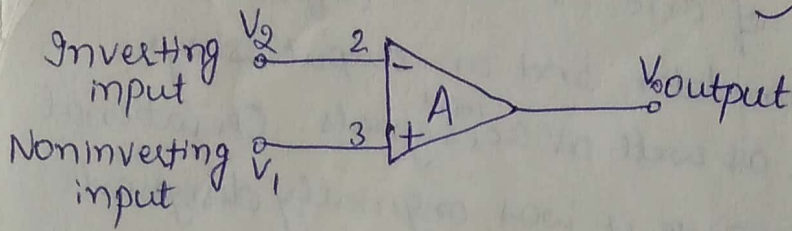

The ac signal (dc voltage) applied to ~~the~~ ⁽⁺⁾ input produces an inpt (same polarity) signal at output. On the ~~other~~ other hand (-) input produces an 180° out of phase (opposite polarity) signal at o/p.

V_1 = voltage at noninverting input

V_2 = voltage at inverting input

V_o = output voltage.

All these voltages are measured wrt. ground.

A = Voltage gain.

National Semiconductor = LM741

Motorola

RCA

Texas instruments

Signetics

MC1741

CA3741

SN52741

N5741

versions of 741 & 741C
741C & E are identical to

741 & 741SC are military (8, 10, 14, 16)

Flat Pack - rectangular ceramic case


Metal can - metal or plastic case 3, 5, 8, 14, 12

Dual in line Package (DIP)

mounted inside a plastic or ceramic case. It is mostly used $\because$ it can be mounted easily. 8 pin DIP. 12, 14, 16, 20.


Power Supplies Connections :-

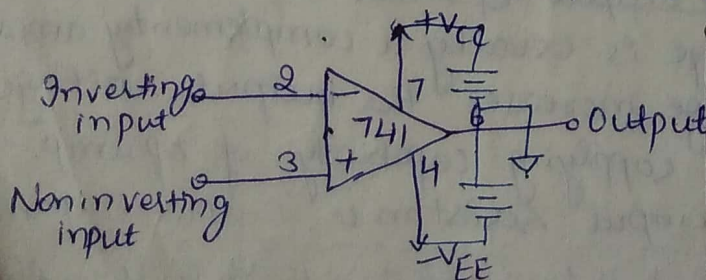For operation of op amp bipolar voltages are required i.e. two voltages are required, one +ve & other equal in magnitude but negative. These voltages must be referenced to a common point of ground. Fairchild :- (V^+ , V^-), Motorola uses. ($+V_{CC}$ & $-V_{EE}$).



Temp. Range
Military temp. -55 to 125°C
Industrial -20 to 85°C
Comm. temp. Range 0 to 70°C

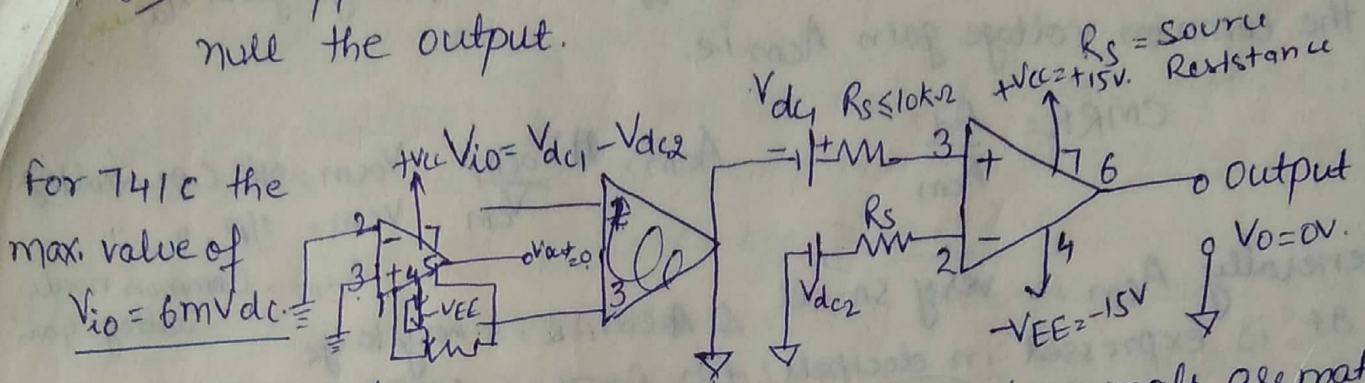
DC Input offset Voltage (V_{io}) :- It is the voltage that must be applied between two input terminal of an op amp to null the output.



Smaller the value of V_{io} better the input terminals are matched.

DC Input offset Current (I_{io}) :- The algebraic difference between the currents into inverting and noninverting terminals. is referred as input offset current I_{io} .

$$I_{io} = I_{B1} - I_{B2}$$

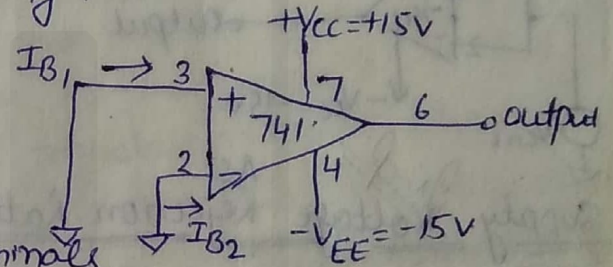

Smaller the I_{io} better the input terminals are matched. for 741C is 200nA max .

DC Input Bias Current (I_B) :- Input bias I_B is the average of currents that flow into inverting and noninverting input terminals of op amp.

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$


$I_B = 500\text{nA}$ I_{B1} & I_{B2} are base current of first diff. amp. stage.

DC Error: Thermal drift - off c/n & offset volt. change with temp. eg. we have nulled at 25°C . Later at 40°C it is no longer nulled. It is called drift.

Differential Input Resistance (R_i) :- It is the resistance that can be measured at either inverting & noninverting input terminal with other terminal connected to ground. for 741C it is $2\text{M}\Omega$.

Input Capacitance (C_i) :- It is the equivalent capacitance that can be measured at either inverting & noninverting terminal with the other terminal connected to ground. 1.4pF for 741C.

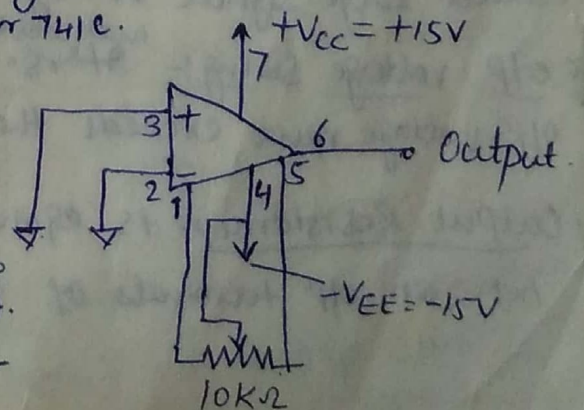Offset Voltage Adjustment Range :- is the range through which input voltage offset can be adjusted by varying the $10\text{k}\Omega$ potentiometer. output offset voltage can be reduced to zero volt. for 741C the offset volt. adjustment range is $\pm 15\text{mV}$.



✓ Common Mode Rejection Ratio:-

It is defined as the ratio of differential voltage gain A_d to the common voltage gain A_{cm} i.e.

$$CMRR = \frac{A_d}{A_{cm}}$$

$$A_{cm} = \frac{V_{ocm}}{V_{cm}}$$


V_{ocm} = o/p C.M. voltage
 V_{cm} = i/p " "

A_{cm} = Common mode voltage gain

Generally A_{cm} is very small & $CMRR$ is very large.

It is expressed in decibels (dB). For 741C $CMRR$ is 90dB typically.

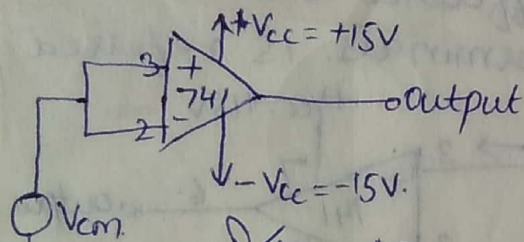The higher the value of $CMRR$, the better is matching bet. two input terminals & smaller is the output common mode voltage.



Supply Voltage Rejection Ratio:- It is the change in input offset voltage V_{io} caused by variation in supply voltage is called supply voltage rejection ratio (SVRR). It is called power supply rejection ratio (PSRR) or power supply sensitivity (PSS).

$$SVRR = \frac{\Delta V_{io}}{\Delta V} \quad \frac{\mu V}{V} \quad SVRR = 20 \log(\Delta V)$$

Lower the value of SVRR in microvolts/volt, the better for opamp performance

Large Signal Voltage Gain:- opamp amplifies the difference bet. two i/p terminals.

$$A_o = \text{Voltage Gain} = \frac{\text{output voltage}}{\text{differential i/p voltage}} = \frac{V_o}{V_{id}} = \frac{V_o}{2 \frac{V_{41C}}{100,000}} \quad V_o = \pm 10V$$

∵ o/p signal amp. is much larger than i/p signal, the voltage gain is called large signal voltage gain.

o/p voltage Swing:- It is value of +ve & -ve sat. voltage of opamp. indicates the o/p voltage never exceeds these limits for given supply voltages $+V_{cc}$ & $-V_{EE}$. $\pm 13V$ for $R_L \geq 2K\Omega$

Output Resistance:- is equivalent resistance that can be measured between o/p terminals of opamp & the ground. It is 75Ω for 741C opamp.

Supply Current:- I_s is the current drawn by the op amp from the power supply. For 741C op-amp the supply current $I_s = 2.8 \text{ mA}$.

Power Consumption:- P_c is the amount of quiescent power ($V_{in} = 0$) that must be consumed by op amp in order to operate properly. The amount of power consumed by 741C is 85 mW .

AC Transient Response:- The response of any practically useful N/w to a given signal is composed of two parts: transient & steady state response.

Transient response:- is that portion of complete response before O/P attains some fixed value. Once reached this fixed value remains at that level & is referred as steady state value. The response of N/w after it attains a fixed value is independent of time & is called steady state response. Transient response is time variant.

Rise time & % of overshoot are char. of transient response. The time required by O/P to go from 10% to 90% of its final value is called rise time. Overshoot is max. amount by which O/P deviates from steady state value. It is expressed as a %. $\text{Rise time} \propto \frac{1}{\text{unity gain BW}}$. Smaller the rise time higher is BW.

AC Slow Rate:- It is the max. rate of change of O/P voltage per unit

time & is expressed volts per microseconds. $V_{in} = V_{in} \sin \omega t$
 $V_{out} = V_{out} \sin \omega t$
 $\left. \frac{dV_{out}}{dt} \right|_{\text{max}} = V_{out} \omega \cos \omega t = V_{out} \omega = 2\pi f V_{out} = \text{SR}$


Slow rate indicates how rapidly the output of op amp can change in response to change in the input frequency. Slow rate is one of the important factors in selecting the op amp for ac applications.

741C has low slow rate ($0.5 \text{ V}/\mu\text{s}$) which limit its use at high freq. applications i.e. oscillators, filters, comparators etc. LM318 has slow rate $70 \text{ V}/\mu\text{s}$.

Gain Bandwidth product:- The GB product is the B/W of op amp when voltage

gain is 1. For an ideal op amp, open loop gain is very large & does not vary with freq.

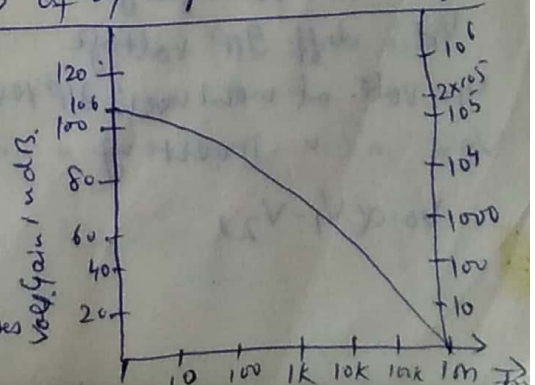But these assumptions are not good for an actual op amp. The dc & very low freq. open loop gain is abt. 2×10^5 which is finite. With increase in freq. the gain decreases prop. 741C has a critical freq. f_c of 10 Hz . Above f_c gain decreases 20 dB/decade until it reaches 1 at freq. of 1 MHz .



Unity gain buffer is the case where voltage gain is unity. Unity gain is 1MHz. 741C unity is 1MHz. So 741C can amplify the signal up to 1MHz. Beyond 1MHz voltage gain is less than unity & it is useless.

Ideal op-amp:

1. open loop gain is ∞
2. Infinite i/p resistance means i/p current (current drawn from source) is zero. & so it does not load the source. Ideal diode is voltage controlled device.
3. Output resistance is zero so that o/p can drive an ∞ no. of other devices. V_{out} is independent of current drawn by the load.
4. Zero output voltage when i/p voltage is zero. (perfect balance).
5. Infinite BW so that any freq. signal from 0 to ∞ Hz can be amplified without attenuation (DC and AC both signal can be amplified).
6. Common CMRR is ∞ . so that amplifier is free from common thermal noise, pick up etc.
7. Slew rate is ∞ so that output voltage change occurs simultaneously with i/p voltage changes.
8. Output voltage is zero when i/p voltage is zero i.e. offset voltage is zero.
9. Drift of char. with temp. is nil.

① Equivalent ckt of an op-amp:-

A_{vid} is the Theremin equivalent voltage source.
 R_o is the Theremin equivalent resistance looking back into the o/p terminal of an op-amp.

$$V_o = A_{vid} = A(V_1 - V_2)$$



A = Voltage gain

V_{id} = diff. i/p voltage

V_1 = volt. at non-inver. i/p terminal w.r. to ground

V_2 = " " inverting " " " " " "

$$V_o \propto (V_1 - V_2)$$

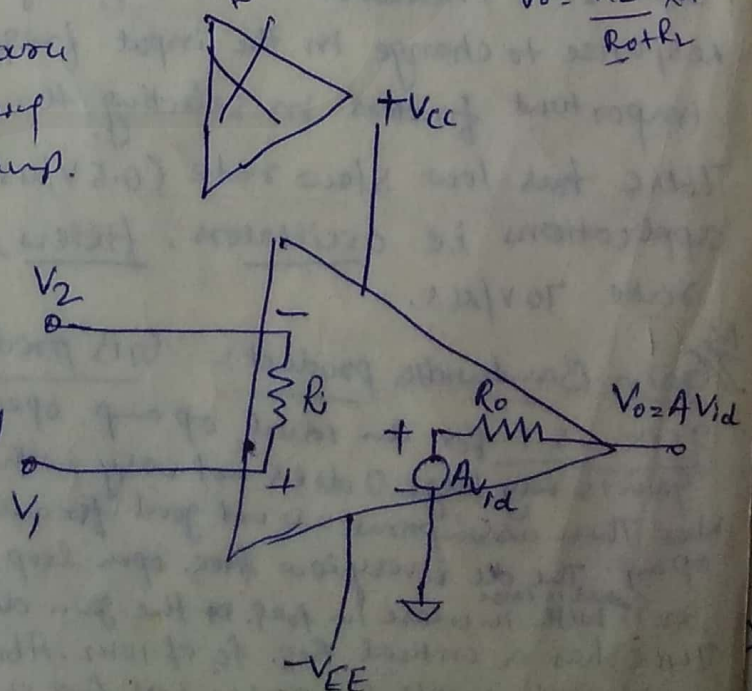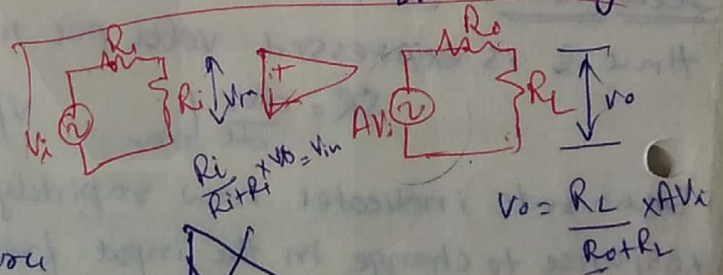

Ideal Voltage Transfer Curve


(9)

is ideal voltage transfer curve

cal: off offset voltage is zero. Gain const.

curve will be almost vertical because of very large value of A.

+ve Saturation
 $+V_{sat} < +V_{CC}$

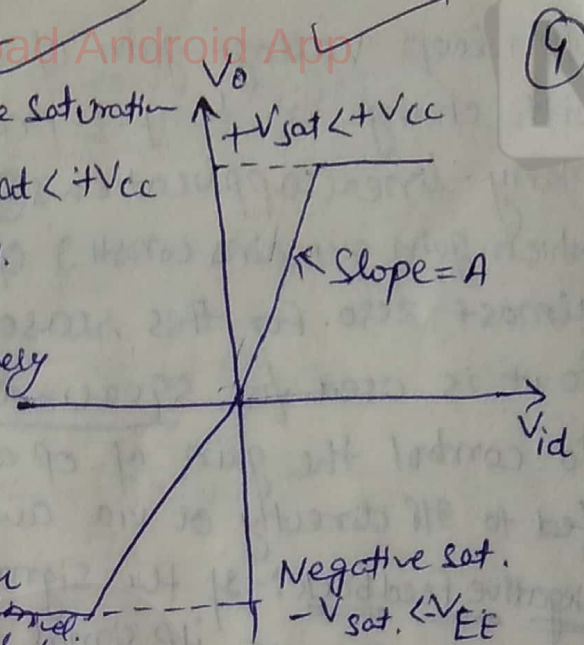

open loop indicates there is no connection either direct or via another N/W exists bet. O/P & I/P terminals.

Open loop op amp configurations: means there is no f/b

In open loop it is high gain amplifier.


Three open loop config: Differential amplifier, Inverting, Non inverting amplifier.

Differential Amplifier

$V_1 = V_{in1}$ & $V_2 = V_{in2}$ R_{in1} & R_{in2} are negligibly small as compared to O/P resistors.

$$V_{O2} = A(V_{in1} - V_{in2}) = A(V_1 - V_2)$$

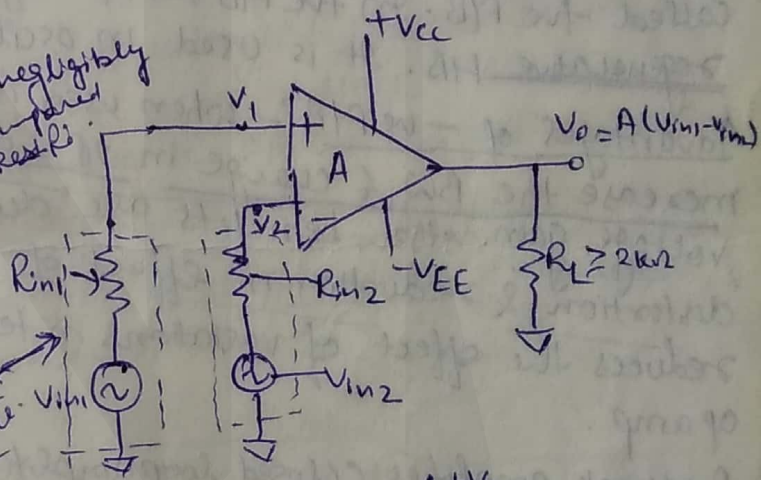polarity of O/P voltage is depends on polarity of I/P diff. voltage ($V_{in1} - V_{in2}$). Gain A is referred as open loop gain.




Inverting Amplifier

$V_1 = 0V$ & $V_2 = V_{in}$

$$V_{O2} = -A V_{in}$$

-ve sign indicates that O/P voltage is out of phase w.r.t. by 180° or phase inversion.

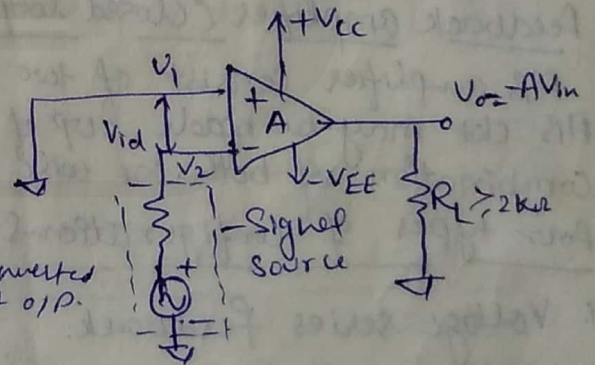In inv. amp. i/p signal is amplified by gain A & is also inverted at O/P.




Non inverting Amplifier

$V_1 = V_{in}$ $V_2 = 0V$

$$V_{O2} = A V_{in}$$

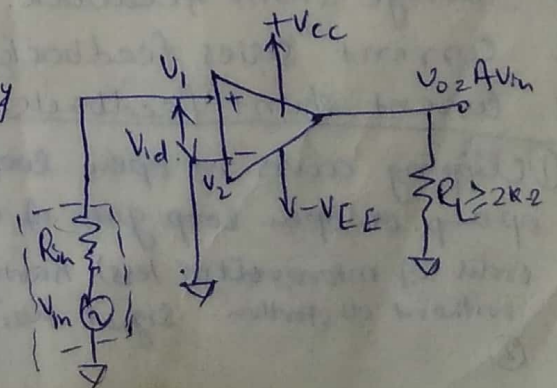In open loop conf. any i/p signal that is only slightly greater than zero drives the O/P to sat. level. This is due to very high gain (A) of op amp. Thus, when operated open loop, the O/P of op amp is either -ve or +ve sat. or switches bet. +ve & -ve sat. levels. For this reason, open loop op amp conf. are not used in linear applications.



Open loop voltage gain of op amp is not constant it varies with change in temp. & power supply. So it is unsuitable for many linear applications. (3) The bandwidth (band of freqs. for which gain remains const.) of most open loop op amp is negligibly small almost zero. For this reason ^{open loop} op amp is ~~reg~~ impractical in ac applications. So it is used for square wave applications.

To control the gain of op amp we use the feedback i.e. an O/P signal, fed to I/P directly or via another N/W.

Negative Feedback:- If the signal fed back is of opposite polarity or out of phase by 180° w.r.t. I/P signal then it is called -ve feedback (degenerative feedback). When it is used it degenerates (reduces) the O/P voltage amplitude & in turn reduces the voltage gain.

Positive Feedback:- If the signal fed back is in phase with I/P signal F/B is called +ve F/B. In +ve F/B the F/B signal aids the I/P signal. Also called regenerative F/B. It is used in oscillator circuits.

Advantages of -ve F/B:- When used in amplifiers, -ve F/B stabilizes the gain, increases the BW & change in I/P & O/P resistances. But it reduces the voltage gain. Other benefits are decrease in nonlinearity & harmonic distortion & reduction in effect of I/P offset voltage at O/P. It also reduces the effect of variations in temp. & supply voltage on the O/P of op amp.

Feedback amplifier (closed loop amplifier):- An op





F/B amplifier consists of two parts: an op amp & a feedback circuit. F/B ckt may be made up of either passive or active components or combination of both. We will use only purely resistive F/B ckt.

Four types of configurations:-

1. Voltage series feedback.
2. Voltage shunt feedback.
3. Current series feedback.
4. Current shunt feedback.

Clipping occurs in open loop confs. when O/P exceeds the sat. level of op amp. If open loop gain of op amp is very high (only smaller signal of order of microvolt or less) having very low freq. may be amplified accurately without distortion. Signal too small are very suscep.

(2)

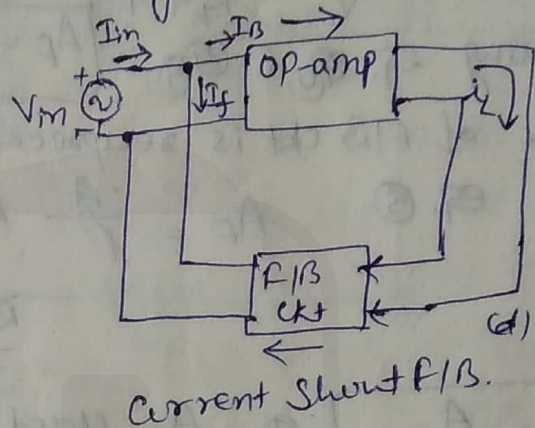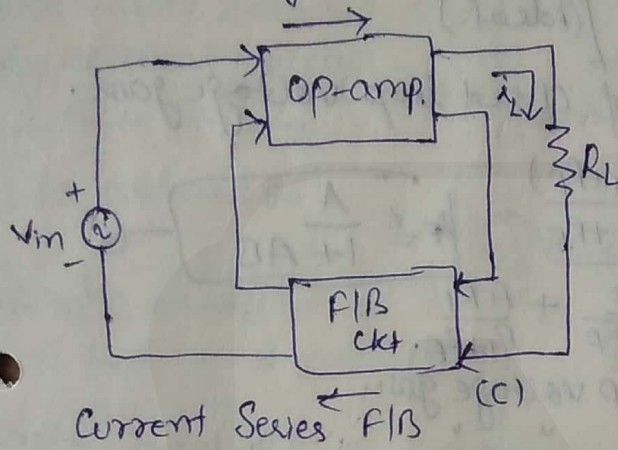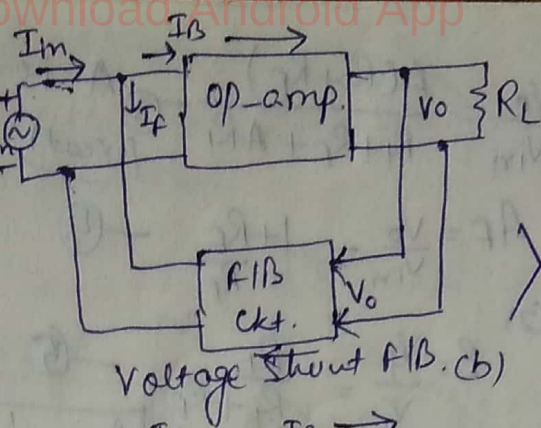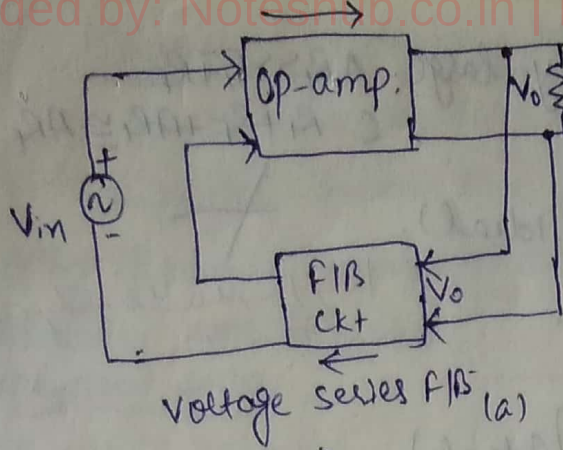

In fig. (a) & (b) voltage across R_L is i/p voltage to F/B ckt. The F/B qty (volt. or ch) is o/p of F/B ckt & is p.p. to o/p voltage. In fig. (c) & (d) the load ch i_L flows into the F/B ckt. The o/p of F/B ckt (volt. or ch) is p.p. to load current i_L .

Non inverting Amplifier :- (closed loop non inverting amplifier) :- It uses the F/B & i/p signal is applied to non inverting i/p terminal of op-a.p.

Open loop voltage gain $A = \frac{V_o}{V_{id}}$

Closed " " " " $A_F = \frac{V_o}{V_{in}}$

Gain of F/B circuit $B = \frac{V_f}{V_o}$

Apply KVL for i/p loop is

$$V_{id} = V_{in} - V_f \quad \text{--- (1)}$$

In above eqn. F/B voltage always oppose the i/p volt. hence F/B is -ve.

$$\text{We know } V_o = A(V_1 - V_2)$$


$$V_1 = V_{in} \quad V_2 = V_f = \frac{R_1 V_o}{R_1 + R_f} \quad \text{--- (2)}$$

$$V_o = A \left(V_{in} - \frac{R_1 V_o}{R_1 + R_f} \right)$$

$$V_o = A \left(\frac{V_{in}(R_1 + R_f) - R_1 V_o}{R_1 + R_f} \right)$$

$$V_o \left(A + \frac{AR_1}{R_1 + R_f} \right) = A V_{in}$$
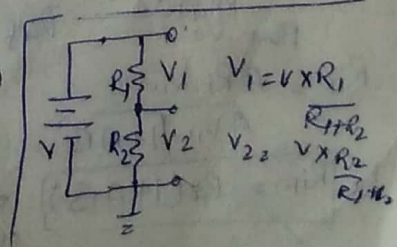
$$V_o \left(\frac{R_1 + RA + R_1}{R_1 + R_f} \right) = A V_{in}$$



Provided by: www.indiabix.com

$$A_f = \frac{V_o}{V_{in}} = \frac{A(R_i + R_f)}{R_i + R_f + A R_i} \quad \text{--- (3) (exact)}$$

A is very large. $A R_i \gg R_i + R_f$
 $\therefore R_i + R_f + A R_i \cong A R_i$

So $A_f = \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i} \quad \text{--- (4) (ideal)}$

From (2) $B = \frac{V_f}{V_o} = \frac{R_i}{R_i + R_f} \quad \text{--- (5)}$

Comparing eq. (4) & (5) $A_f = \frac{1}{B}$ (ideal.)

So Gain of A/B ckt is reciprocal of closed loop voltage gain.

From eq. (3) $A_f = \frac{A(R_i + R_f)}{\frac{R_i + R_f}{R_i + R_f} + \frac{A R_i}{R_i + R_f}} \quad \text{--- (6)}$

$$A_f = \frac{A}{1 + AB}$$

$$A_f = \frac{A}{1 + AB} \quad \text{--- (7)}$$

A_f = closed loop voltage gain

A = open u

B = Gain of A/B ckt.

AB = loop gain.

Difference input voltage ideally zero :-

$V_{id} = \frac{V_o}{A}$ Since A is very large (ideally ∞)

$V_{id} \cong 0$ i.e. $V_1 \cong V_2$ (ideal) --- (a)

$V_1 = V_{in}$ $V_2 = V_f$
 $= \frac{R_i V_o}{R_i + R_f}$

Put V_1 & V_2 in eq. (a)

$V_{in} = \frac{R_i V_o}{R_i + R_f}$

$$A_f = \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i}$$

O/P Resistance with A/B :-

$R_{if} = \frac{V_{in}}{I_{in}} = \frac{V_{in}}{V_{id}/R_i} \quad \text{--- (b)} \quad V_{id} = \frac{V_o}{A}$

and $V_o = \frac{A}{1 + AB} V_{in}$

Put V_{id} in eq. (b)


$R_{if} = R_i \frac{V_{in}}{V_o/A}$
 Put V_o

$R_{if} = \frac{A R_i V_{in}}{V_o}$

$R_{if} = \frac{A R_i V_{in}}{A V_{in}/(1 + AB)}$

So $R_{if} = R_i (1 + AB)$

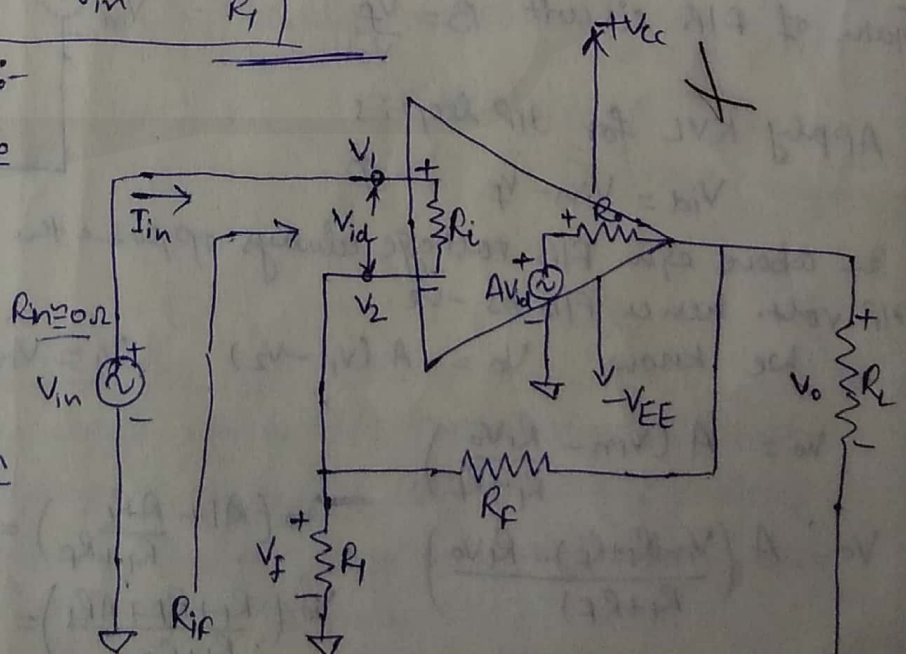So O/P resis. of opamp with A/B is $(1 + AB)$ times that without A/B.



Output Resistance with feedback :-

It is the resistance determined looking back into the A/B amplifier from the O/P terminal.

We apply Thevenin Theorem to cal.

O/P resistance with A/B. (R_{of})

for dependent source.

Reduce V_{in} to zero & apply external voltage V_o & then cal. i_o .

R_{of} is defined as

$$R_{of} = \frac{V_o}{i_o} \quad \text{--- (1)}$$

Write Kirchhoff's c/v eqn. at node N.

$$i_o = i_a + i_b$$

Since $(R_f + R_1) \parallel R_i \gg R_o$ & $i_a \gg i_b$

$$\therefore i_o \approx i_a$$

Current i_o can be found by writing Kirchhoff's voltage eqn. from O/P loop.

$$V_o - R_o i_o - A V_{id} = 0$$

$$i_o = \frac{V_o - A V_{id}}{R_o} \quad \text{--- (2)}$$

$$V_{id} = V_1 - V_2$$

$$V_{id} = 0 - \frac{R_1 V_o}{R_1 + R_f} = -B V_o$$


Put V_{id} in eqn. (2)

$$\therefore i_o = \frac{V_o + AB V_o}{R_o}$$

Put value in eq. (1)

$$R_{of} = \frac{V_o}{(V_o + AB V_o)/R_o} = R_{of} = \frac{R_o}{1 + AB}$$

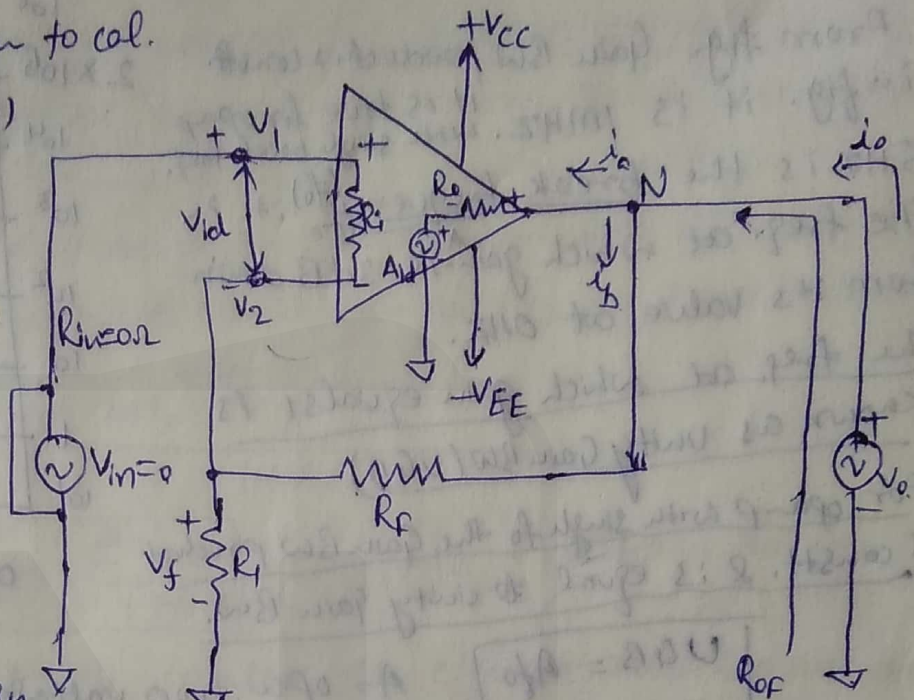So O/P resistance of voltage series A/B amp. is $\frac{1}{1 + AB}$ times the O/P resistance R_o of the op amp. i.e. O/P resistance of op amp with A/B is much smaller than O/P resistance without A/B.




Bandwidth with feedback:

BW is defined as the band (range) of freqs. for which gain remains constt.

From fig. Gain BW product is constt. in fig. it is 1MHz. it is true for opamp with single break freq. 5Hz is the break frequency (f_0), it is the freq. at which gain is 3dB down from its value at 0Hz.

The freq. at which gain equals 1 is known as unity Gain BW (UGB)

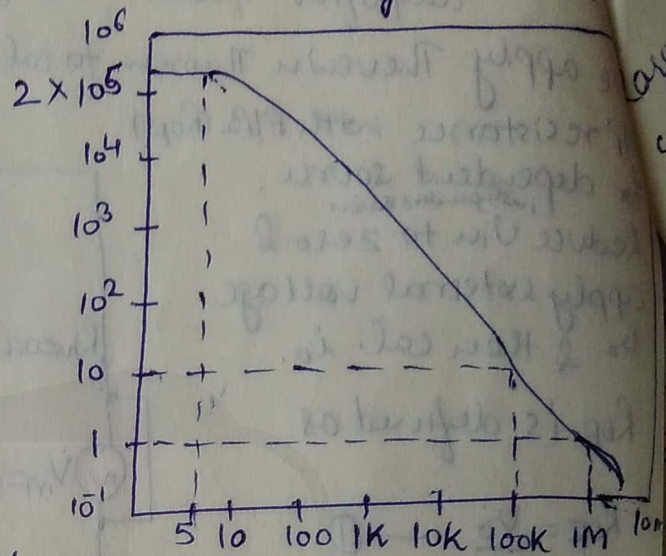For opamp with single f_0 the Gain BW product is constt. & is equal to unity Gain BW.



open loop gain vs freq. curve for 741C.

$$UGB = A f_0$$

A = open loop voltage gain
 f_0 = break freq. of an opamp.

Or only for a single break frequency opamp.

$$UGB = (A_F f_F)$$

A_F = Closed loop voltage gain
 f_F = BW with F/B.

$$A f_0 = A_F f_F$$

$$f_F = \frac{A f_0}{A_F}$$

For non inverting amplifier with F/B.

$$A_F = \frac{A}{1+AB}$$

Substitute A_F in above eqn.

$$f_F = \frac{A f_0}{A/(1+AB)} =$$

$$f_F = \frac{f_0 (1+AB)}{1}$$

eqn. show that BW of noninverting amplifier with feedback f_F is equal to $(1+AB)$ times to its BW without F/B (f_0).

✓ Total Output Offset Voltage with FIB :-

(7)

In an op-amp when i/p is zero, o/p is also expected to zero. $\therefore$ of effect of i/p offset voltage & c/n, the o/p is significantly

larger $\therefore$ of very high open loop gain. We call this enhanced o/p voltage is called total o/p offset voltage V_{OOT} . In open loop op-amp total o/p offset voltage is either equal to +ve or -ve sat. voltage.

Due to FIB gain of non-inver. amp. changes from A to $A/(1+AB)$. So total o/p offset voltage with FIB must also be $1/(1+AB)$ times the volt. without FIB.

$$\text{Total o/p offset voltage with FIB} = \frac{\text{Total o/p offset voltage without FIB}}{1+AB}$$

$$V_{OOT} = \frac{\pm V_{sat}}{1+AB}$$

$1/(1+AB)$ is always less than 1.

Higher the value of $(1+AB)$, smaller the effect of noise & of variations in supply voltages & change in temp. on o/p voltage of a noninverting amplifier.

Voltage follower:- When the noninverting amplifier is configured for unity gain is called a voltage follower. $\therefore$ o/p voltage is equal to & in phase with i/p. In voltage follower the o/p follows the i/p. It is similar to discrete emitter follower. The voltage follower is preferred $\therefore$ it has much higher i/p res. & o/p amplifier amplitude is exactly to i/p.

open R_i & short R_F

$$B = 1$$

$$A_f = \frac{A}{1+AB}$$

$$R_{if} = R_i(1+AB)$$

$$R_{of} = \frac{R_o}{1+AB}$$

$$f_{cf} = (1+AB)f_o$$

$$V_{OOT} = \frac{\pm V_{sat}}{1+AB}$$

$$A_f = \frac{A}{1+AB}$$


$$R_{if} = A R_i$$

$$R_{of} = \frac{R_o}{A}$$

$$f_{cf} = A f_o$$


$$V_{OOT} = \frac{\pm V_{sat}}{A}$$

Since $(1+AB) \approx A$

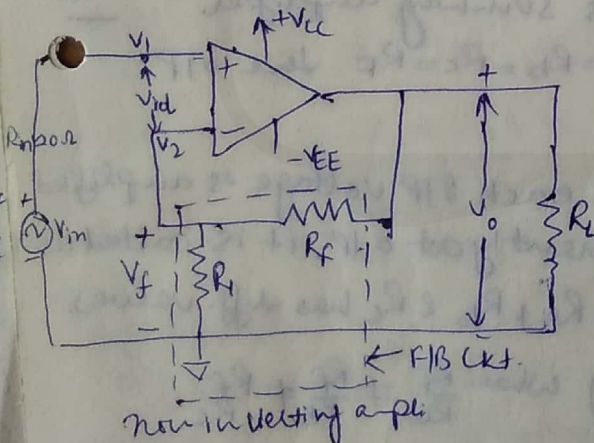


voltage follower.

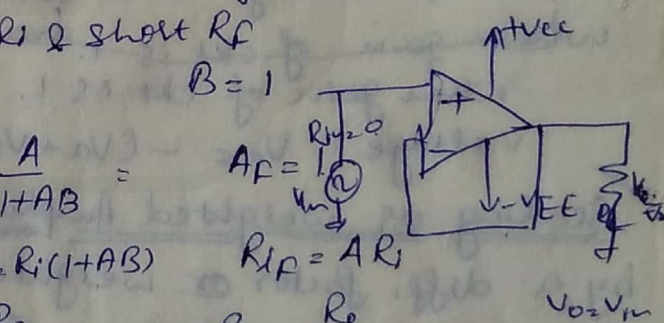is also called noninverting buffer. $\therefore$ removes the loading on first N/w.



Summing, Scaling & Averaging Amplifier :-

Inverting Configuration :-

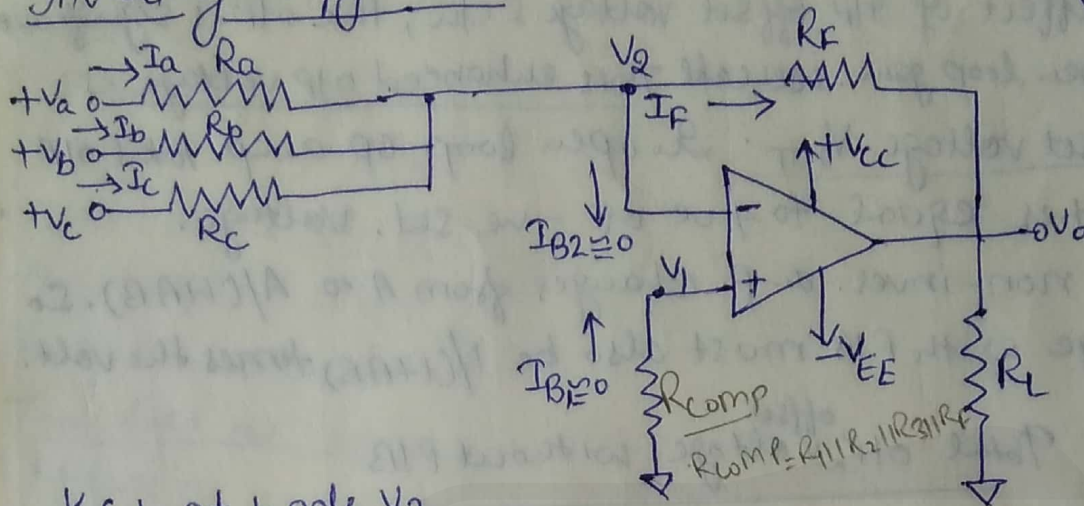

KCL at node V_2

$$I_a + I_b + I_c = I_B + I_f, \therefore \frac{V_a - V_2}{R_a} + \frac{V_b - V_2}{R_b} + \frac{V_c - V_2}{R_c} = \frac{V_2 - V_o}{R_f}$$

Since R_i & A are ideally ∞ , $I_B = 0A$, & $V_1 = V_2 = 0V$

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = -\frac{V_o}{R_f}$$

$$V_o = -\left(\frac{R_f V_a}{R_a} + \frac{R_f V_b}{R_b} + \frac{R_f V_c}{R_c}\right)$$

Gain Inverting
 $A_d = -\frac{R_f}{R_i}$

Summing amplifier :- If $R_a = R_b = R_c = R$

$$\text{then } V_o = -(V_a + V_b + V_c) \frac{R_f}{R}$$

So o/p voltage is -ve sum of all i/p's times the gain of ckt $\frac{R_f}{R}$.

when gain of ckt is 1.

hence it is summing amplifier.

when gain of ckt is 1. i.e. $R_a = R_b = R_c = R_f$ the o/p voltage $V_o = -(V_a + V_b + V_c)$.

Scaling or weighted Amplifier :- If each i/p voltage is amplified by a diff. factor or weighted differently at o/p, it is called as

Scaling or weighted amplifier :- If R_a, R_b & R_c has diff. values.

$$V_o = -\left(\frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c\right) \text{ when } \frac{R_f}{R_a} \neq \frac{R_f}{R_b} \neq \frac{R_f}{R_c}$$

Average circuit :- in which o/p volt. is equal to avg. of all i/p voltages. So $R_a = R_b = R_c = R$ or gain by which each i/p is amplified must be equal to 1 over no. of i/p's i.e.

$$\frac{R_f}{R} = \frac{1}{n}$$

where $n = \text{no. of i/p's}$

$$\frac{R_f}{R} = \frac{1}{3}$$

$$V_o = -(V_a + V_b + V_c)$$



In ckt we want $\frac{R_f}{R} = \frac{1}{3}$ So

Imp


$$So \Rightarrow V_o = -\frac{(V_a + V_b + V_c)}{3}$$

Use These ckt are used in analog computers & audio mixers in which a no. of 9IPs are added up (mixed) up to produce a desired o/p.

In practical ckt 9IP bias c/n compensating resistor R_{comp} should be provided. To find R_{comp} make all 9IPs $V_1 = V_2 = V_3 = 0$ So that effective 9IP resis. $R_i = R_1 \parallel R_2 \parallel R_3 \therefore R_{comp} = R_i \parallel R_f = R_1 \parallel R_2 \parallel R_3 \parallel R_f$.

Non Inverting Summing Amplifier:-

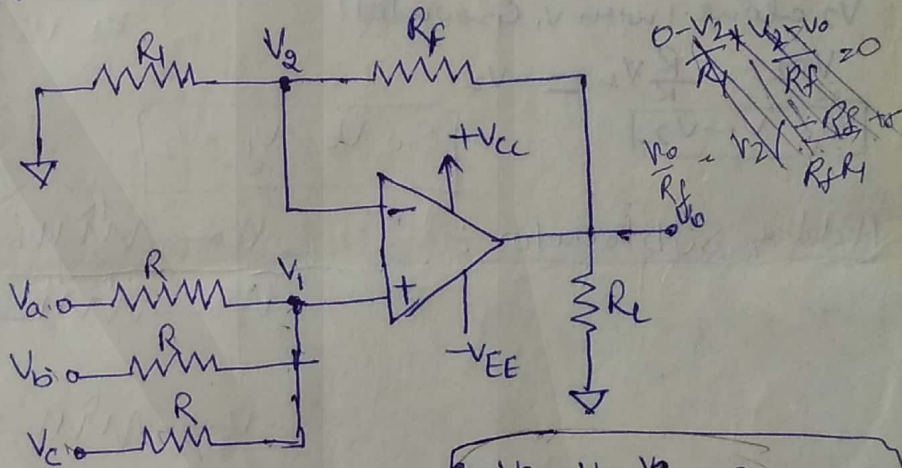A summer that gives noninverted sum is noninverting summing amplifier



$$-R_1 V_2 + R_f V_o - V_2 R_f = 0$$

$$R_f V_o = V_2 R_f + V_2 R_1$$

$$V_o = V_2 \left(1 + \frac{R_1}{R_f} \right)$$

$$\frac{V_a - V_1}{R} + \frac{V_b - V_1}{R} + \frac{V_c - V_1}{R} = 0$$

$$So \quad V_1 = \frac{V_a + V_b + V_c}{3}$$

Hence o/p voltage is $\frac{V_o}{R_f} = \frac{V_2}{R_1} + \frac{V_2}{R_f}$

$$V_o = \left(1 + \frac{R_f}{R_1} \right) V_1$$

$$V_o = V_2 \left(\frac{R_f}{R_1} + 1 \right)$$

$$V_o = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{V_a + V_b + V_c}{3} \right)$$

Av: Amplifier:-


o/p voltage is equal to avg. of all 9IP +ve gain of ckt $\left(1 + \frac{R_f}{R_1} \right)$
if the gain is 1, o/p voltage is equal to avg. of all 9IP voltage.

Summing amplifier - if $\left(1 + \frac{R_f}{R_1} \right)$ is equal to no. of 9IPs the o/p voltage becomes equal to sum of all 9IP voltage. i.e. if $\left(1 + \frac{R_f}{R_1} \right) = 3$

$$So \quad V_o = V_a + V_b + V_c$$

Voltage Shunt (Differential amplifier)

Subtractor:- All R are of equal value

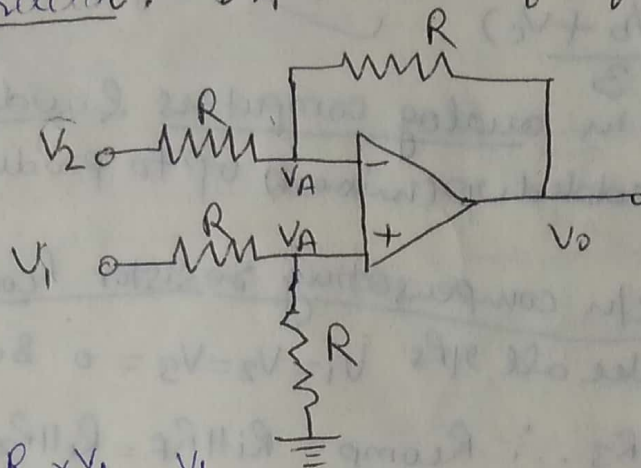

Apply Nodal

$$\frac{V_1 - V_A}{R} + \frac{0 - V_A}{R} = 0$$

$$V_A = \frac{V_1}{2}$$

$$V_A = \frac{R \times V_1}{R+R} = \frac{V_1}{2}$$

V_1 alone make $V_2 = 0$

$$V_{O1} = (1 + \frac{R}{R}) \frac{V_1}{2} = V_1$$

V_2 alone (with V_1 grounded)

$$V_{O2} = -\frac{R}{R} V_2 = -V_2$$

$$V_{O2} = V_1 - V_2$$

$$\frac{V_1 - V_A}{R} + \frac{V_2 - V_A}{R} + \frac{V_0 - V_A}{R} = 0$$

$$V_2 + V_0 - 2V_A = 0$$


$$V_0 = 2V_A - V_2$$

$$= 2 \times \frac{V_1}{2} - V_2$$

put V_A

$$So V_0 = V_1 - V_2$$

Adding Subtractor

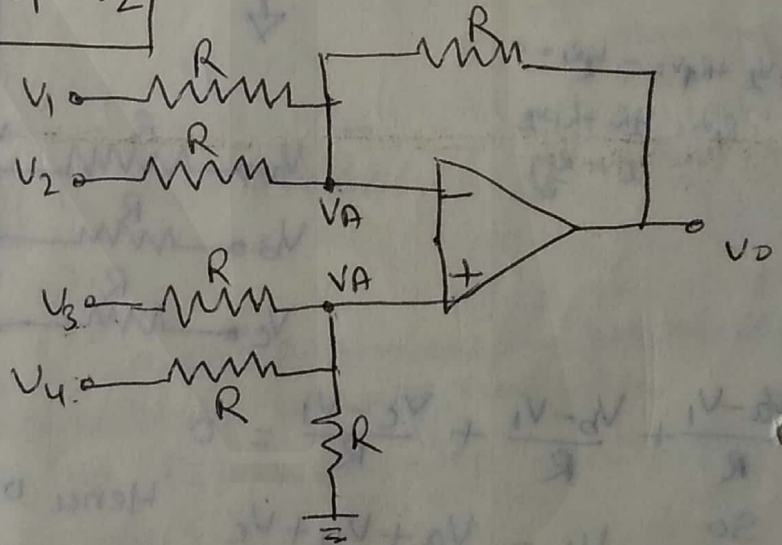

$$\frac{V_1 - V_A}{R} + \frac{V_2 - V_A}{R} + \frac{V_0 - V_A}{R} = 0$$

$$V_1 + V_2 + V_0 - 3V_A = 0$$

$$V_1 + V_2 + V_0 = 3V_A$$

①

$$\frac{V_3 - V_A}{R} + \frac{V_4 - V_A}{R} + \frac{0 - V_A}{R} = 0$$

$$V_3 + V_4 = 3V_A$$

②

from ① & ②

$$V_1 + V_2 + V_0 = V_3 + V_4$$

$$V_0 = (V_3 + V_4) - (V_1 + V_2)$$