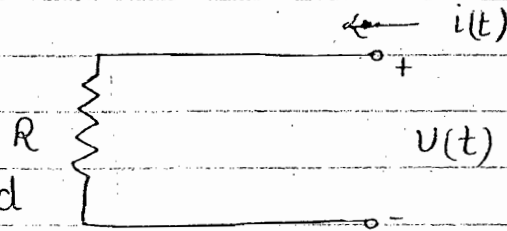


Network Theory

Components of electrical networks:-

1. Resistor

linear and bilateral.



$$\begin{aligned} V(t) &= R i(t) \\ i(t) &= \frac{1}{R} V(t) \end{aligned}$$

in time domain

$$V(s) = R I(s)$$

in s-domain

$$I(s) = \frac{1}{R} V(s)$$

$s = \text{complex freq}$
 $s = \sigma + j\omega$

$$\begin{aligned} V &= IR \\ I &= \frac{1}{R} V \end{aligned}$$

using phasor

for sinusoidal excitation


$$s = j\omega$$

$$V = |V| \angle \theta$$

$$I = |I| \angle \theta$$

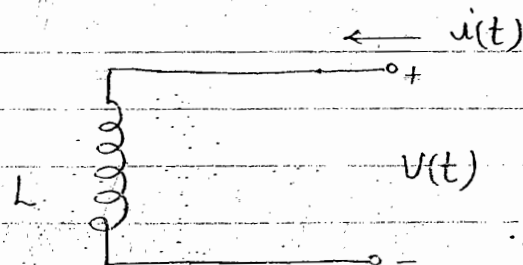2. Inductor

$$\begin{aligned} \phi_m &\propto i \\ \phi_m &= L i \end{aligned} \quad (a)$$



Inductor $\rightarrow$ linear

$$V(t) = L \frac{di(t)}{dt} \quad (i)$$

in

$$i(t) = \frac{1}{L} \int_0^t V(t) dt \quad (ii)$$

time domain

from above 2 equaⁿ it is clear that they are not linear i.e they are not directly proportional but they are derive from equaⁿ (a) so Inductor is also considered as linear element.

$$\boxed{\begin{aligned} V(s) &= sL I(s) \\ I(s) &= \frac{1}{sL} V(s) \end{aligned}} \quad \text{--- In } s \text{ domain assuming zero initial condiⁿ in } s \text{ domain}$$

above equaⁿ also shows (initial condiⁿ in linear equaⁿ s domain) ICS

$$V = j\omega L \cdot I \quad (a) \quad \text{--- using phasor}$$

$$I = \frac{1}{j\omega L} V \quad (b) \quad \text{--- for sinusoidal excitation}$$

as $j = 90^\circ$ it means V is leading I by 90° and in equaⁿ (b) $j = 90^\circ$ i.e. $I = -90^\circ V$ it means I is lagging V by 90°

$$Z_L = jL, \quad Y_L = \frac{1}{jL}$$

$$\boxed{Z_L = j\omega L \quad \& \quad Y_L = \frac{1}{j\omega L}}$$

In a linear element the variation betuⁿ the voltage and current variables is linear either in time domain or s domain or in both domain.

In a bilateral element the current flows

g/p voltage source
or g/p i "



in either direction irrespective of the type of polarity of the voltage source applied between the two terminals of a given network.

The excitation to a given n/w may be non sinusoidal or sinusoidal in nature.

When the excitation is non sinusoidal a given n/w can be analysed either in the time domain or in the Laplace domain.


When the excitation is sinusoidal the n/w can be analysed only by using phasors by substituting $s = j\omega$.

When any network is analysed in the Laplace domain the advantages are:-

- any differential or integral equation is transformed to a linear equation and the manipulation becomes simpler.
- Initial condition if any present in the element are automatically taken care of in the analysis.

Capacitor :
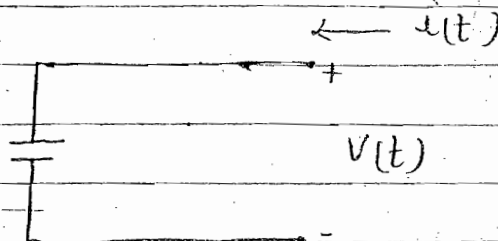
$$\begin{aligned} Q &\propto V \\ Q &= CV \end{aligned}$$



$$i(t) = C \frac{dV(t)}{dt}$$

$$V(f) = \frac{1}{C} \int_0^t i(t) dt \quad \text{in time domain}$$

$$I(s) = s C V(s)$$

$$V(s) = \frac{1}{sC} I(s)$$

in s domain assuming zero ICS

$$Y_c = sC$$


$$Z_c = 1/sC$$

$$\begin{aligned} I &= j\omega C V \\ V &= \frac{1}{j\omega C} I \end{aligned}$$

using phasors ($s = j\omega$)
for sinusoidal excitation

$$Y_c = j\omega C \quad \& \quad Z_c = 1/j\omega C \times I$$

	L	C
$\omega = \omega$	$Z_L = j\omega L$	$Z_C = 1/j\omega C$
$\omega = 0$	S. ckt.	Open ckt.
$\omega = \infty$	O. ckt.	Shunt ckt.

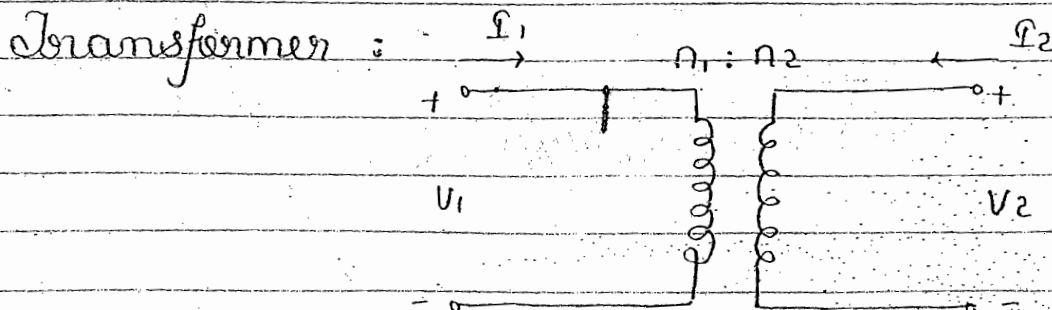

$$\frac{V_1}{V_2} = \frac{n_1}{n_2}$$

$n_2 > n_1$ --- Step up
 $n_2 < n_1$ --- Step down

$$P_1/P_2 = n_2/n_1$$

gf. $n_1 = 1$ & $n_2 = 10$

$$\frac{V_2}{V_1} = \frac{n_2}{n_1} = \frac{10}{1} ; (> 1)$$

$$\frac{P_2}{P_1} = \frac{n_1}{n_2} = \frac{1}{10}$$


$$\frac{V_2}{V_1} \times \frac{I_2}{I_1} = 1$$

ie $V_2 I_2 = V_1 I_1$

Any Step up xmen cannot work as an amplifier since power at the I/P and at O/P remains same.

For any device to work as an amplifier the power at the O/P terminals must always be more than the power at the input terminals.

Gyrator:

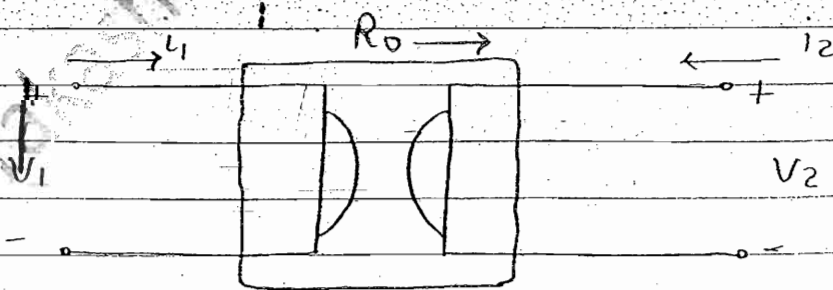

$R_o \rightarrow$ Coefficient of gyrator

$$\begin{aligned} V_1 &= +R_o I_2 \\ V_2 &= -R_o I_1 \end{aligned}$$


This device represent Impedance Inversion

A Gyrator is a four terminal or a two port device.


- It can be made by using an operational amplifier and some externally connected R & C components.
- The coefficient of the gyrator depends upon the parameters of the operational amplifier & the numerical values of R & C components.
- for a given gyrator R_0 has a fixed value.
- It can be used to simulate inductance.
- It represents an impedance inversion. $\therefore$ for a capacitive load the g/p impedance is inductive and vice versa.

6. Voltage Sources:

Independent V. Sources

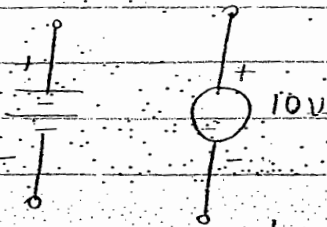

DC voltage source

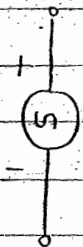


$$\begin{aligned}
 &10t \text{ V(t)} \\
 &5e^{-2t} \text{ V(t)} \\
 &20te^{-5t} \cos 200t
 \end{aligned}$$

Time varying non-sinusoidal voltage sources.



$$\begin{aligned}
 &2\angle 45^\circ \text{ V} \\
 &20 \sin 200t \text{ V} \\
 &V_m \sin \omega t
 \end{aligned}$$

Sinusoidal voltage sources.

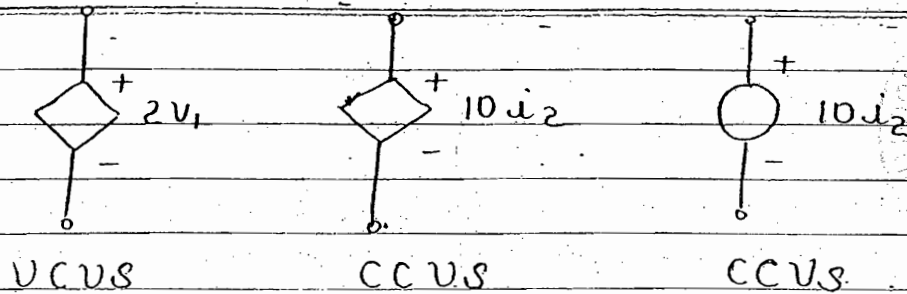

dependent on controlled-voltage source

NOTE :-

While analysing any network containing independent and dependent sources the handling of these sources remains same while writing the KVL and KCL equations except the following two cases:-


- Analysis using the superposition theorem.
- Analysis using Thevenin's & Norton's thm.




In such cases, all independent voltage sources are short ckt or replaced by their internal impedances.

All independent current sources are open circuited or replaced by their internal impedances.

All dependent voltage and current sources remain as they are & $\therefore$ these sources are neither short circuited nor open ckt.


Current Sources :

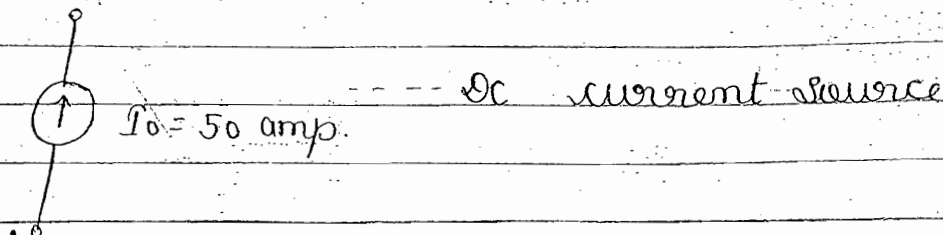

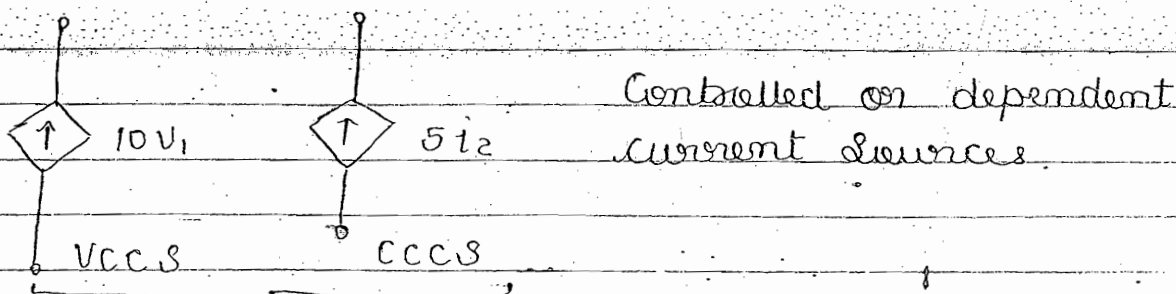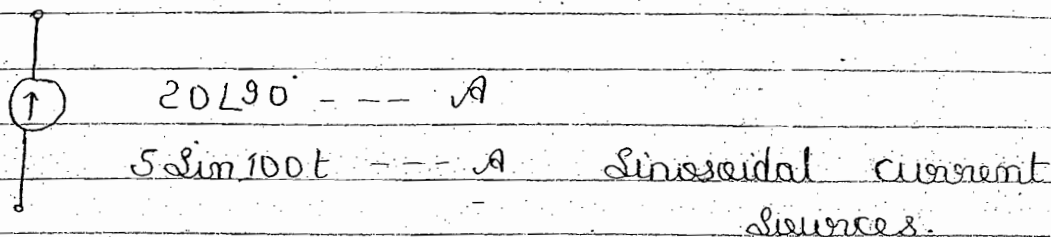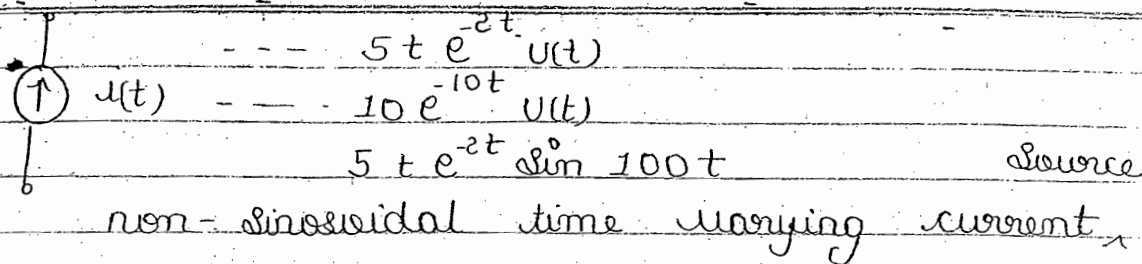


Basic functions :

Unit Impulse func?

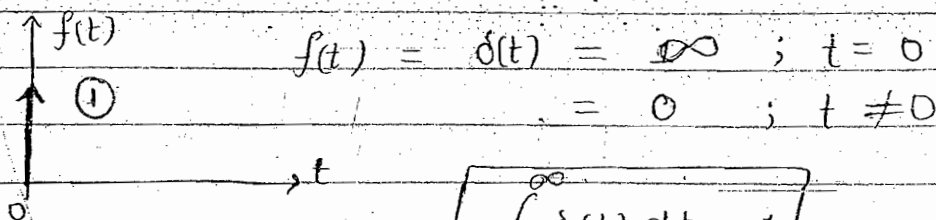

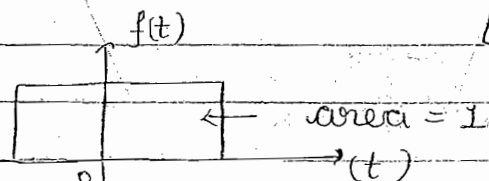
$$\int_{-\infty}^{\infty} \delta(t) dt = 1$$



$$\int_{-\infty}^{\infty} g(t) \delta(t) dt = g(t) \Big|_{t=0} = g(0)$$

exists at $t=0$

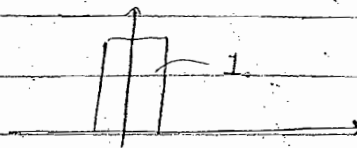


$$\int_{-\infty}^{\infty} g(t) \delta(t-T) dt = g(t) \Big|_{t=T}$$

$\delta(t) \rightarrow 1$ exists at $t=T = g(T)$

Unit Step function :

$$f(t) = u(t) = 0 ; t < 0$$

$$= 1 ; t > 0$$

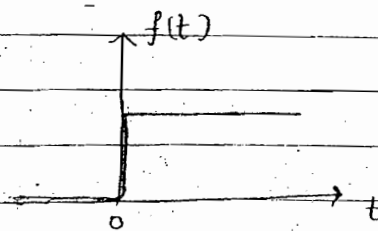


$$u(t) = 1/s$$

Unit Ramp function :

$$f(t) = 0 ; t < 0$$

$$= t ; t > 0$$

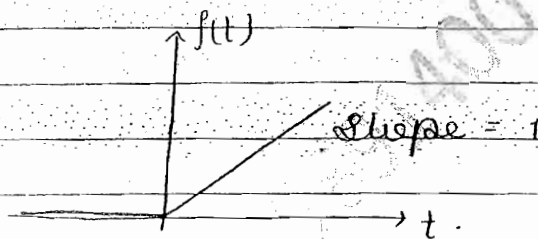



$$f(t) = t u(t)$$

$$f(t) = \delta(t)$$


$$g(t) = 1/s^2$$

Basic Concepts :


$$I_0 = 15 \text{ Amp.}$$

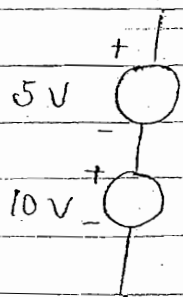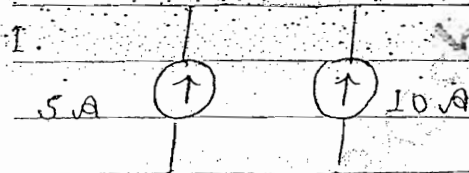


$$V_0 = 15V$$

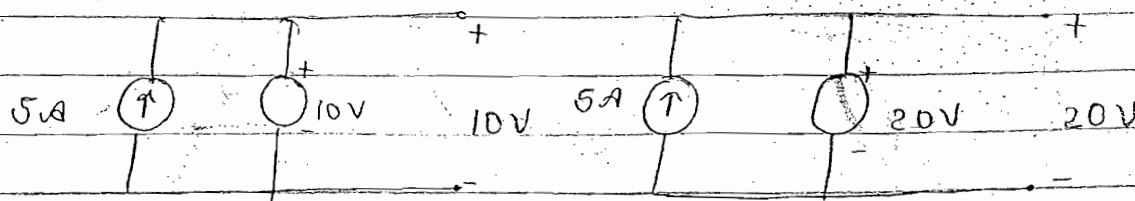

$\Rightarrow$

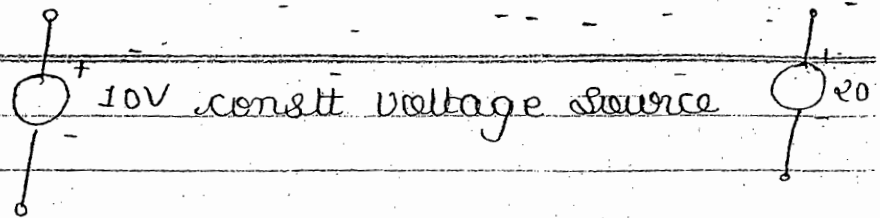

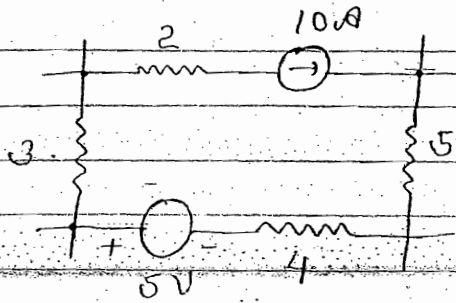
In any loop if current source is present then



A parallel combination of a voltage source or a current is equivalent to a constant voltage source.

The voltage across a current source is purely arbitrary and depends only upon externally connected voltage source or externally connected element.




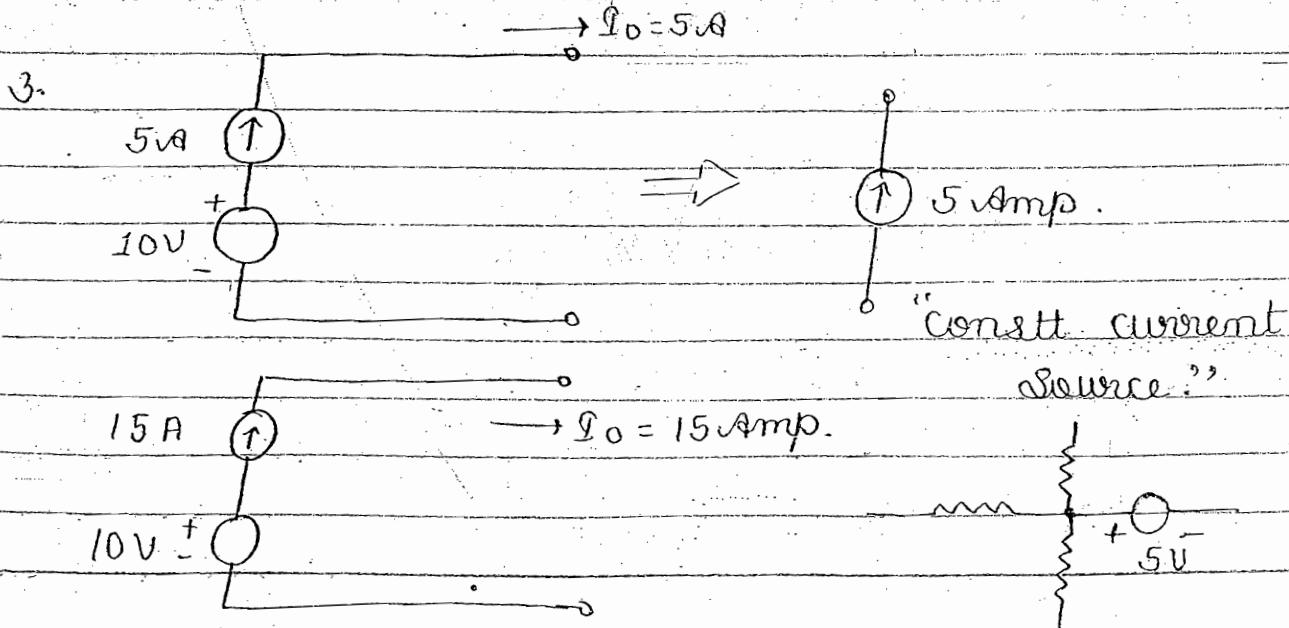
We cannot write any KVL equation in a closed loop which contains a current source since voltage across it is arbitrary and is unknown.



A series combinⁿ of a voltage source and a current source ----- is equivalent to a constt current


The current through voltage source is purely arbitrary and depends only upon externally connected current source and externally connected element.

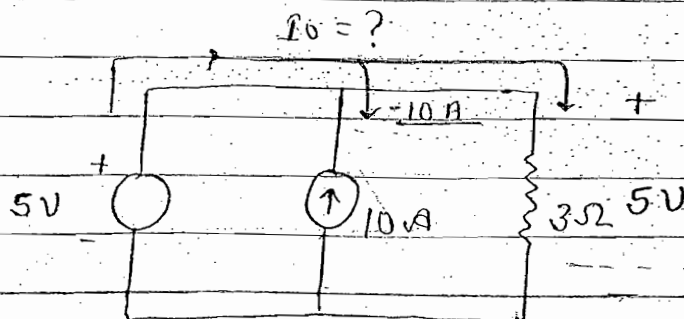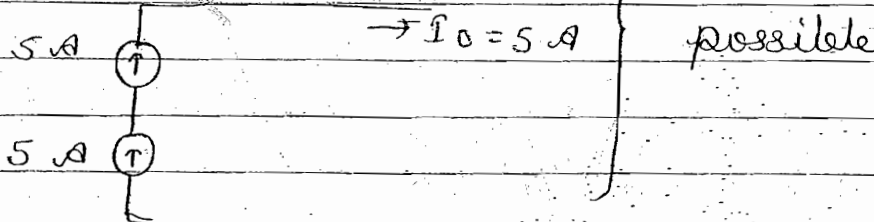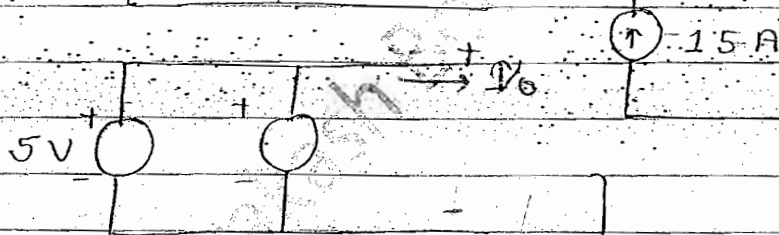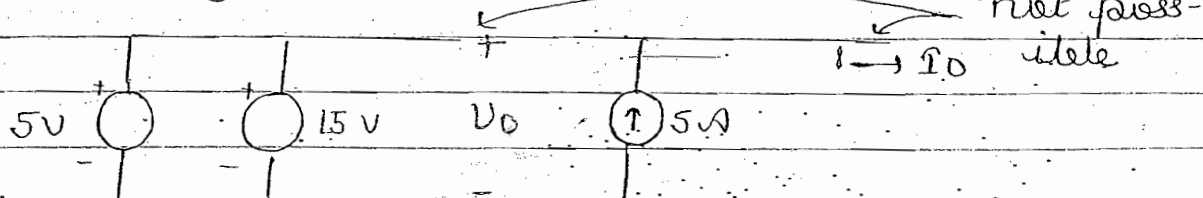We cannot write a KCL equaⁿ at particular node with which a voltage source has been connected since current through it is arbitrary and is unknown






$$I_0 = (-10 + 5/3) A$$

$$\rightarrow 5/3 \text{ amp}$$

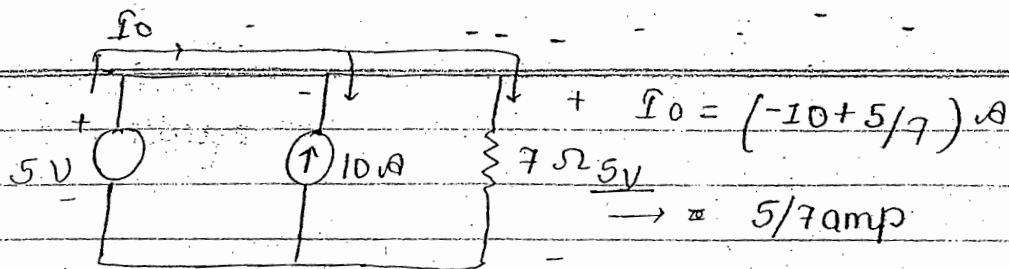


by changing R_L I_0 can be changed.

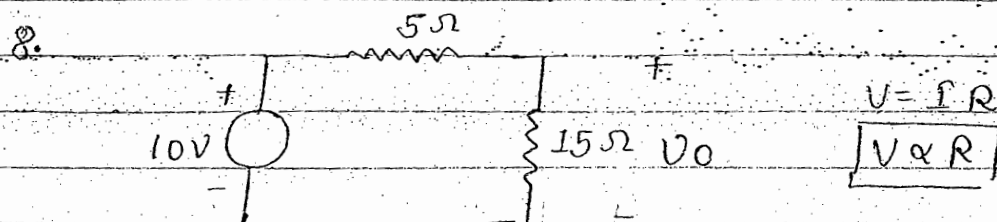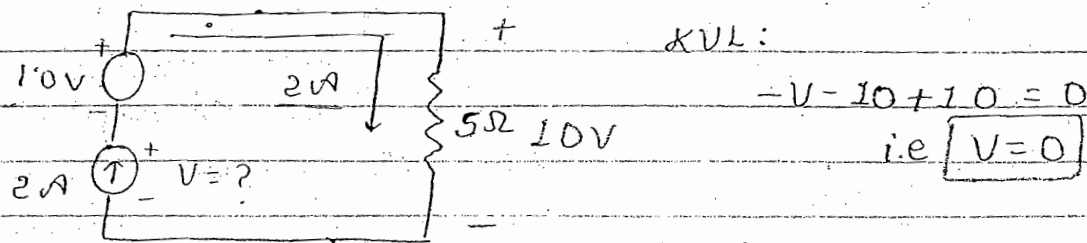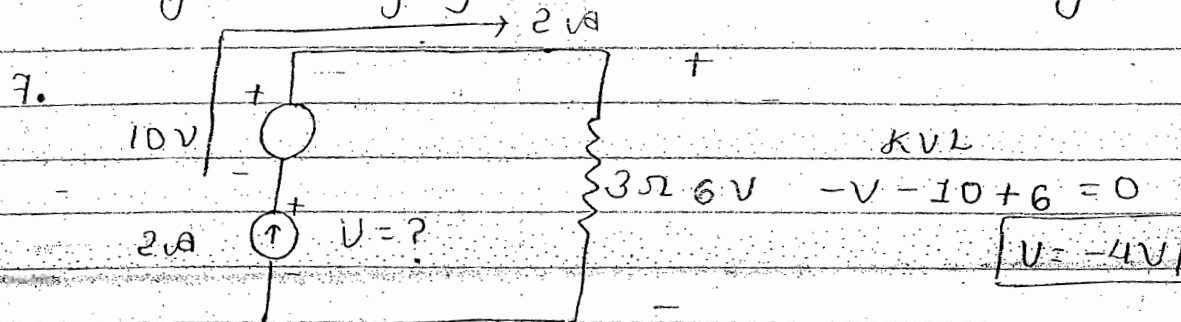

So $V_0 = \left(\frac{15}{5+15} \right) \times 10 \text{ --- V}$


Voltage dividing Theorem

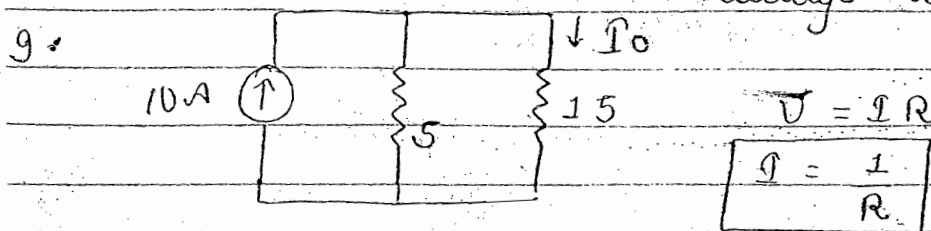

So $I_0 = \left(\frac{5}{5+15} \right) \times 10 \text{ --- A}$

Current dividing Theorem

Impulse Response of a network

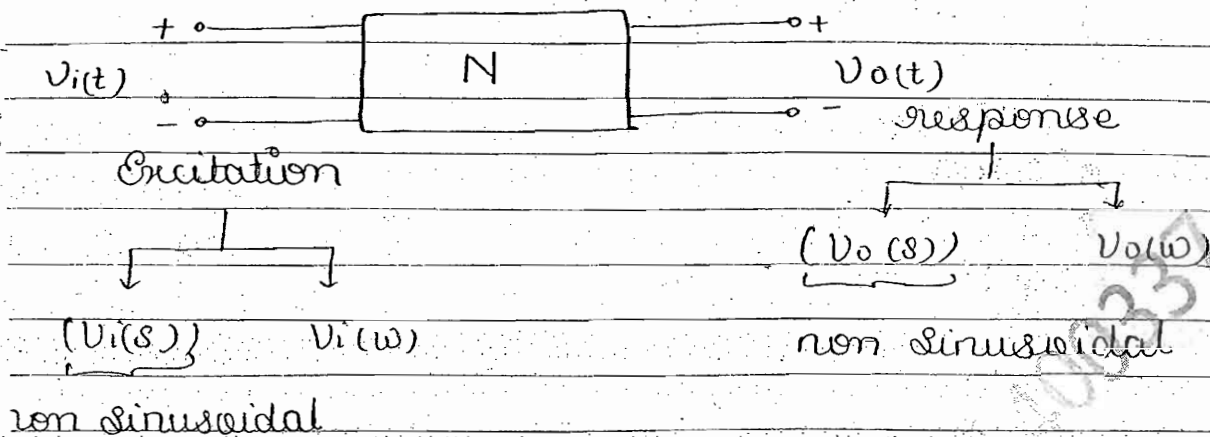

Transfer funcⁿ

$$H(s) = V_o(s) / V_i(s)$$

$$\text{If } V_i(t) = \delta(t) \text{ --- unit impulse funcⁿ}$$
$$V_i(s) = 1$$

$$V_o(s) = H(s) \cdot 1$$

$$V_o(t) = \mathcal{L}^{-1}\{H(s)\}$$

$$= h(t) \text{ --- impulse response of n/w}$$

The Transfer funcⁿ of a network represents the ratio of output voltage to the i/p voltage each in the s domain assuming all the initial condⁿs in various element contained in the n/w to be zero.

The Transfer funcⁿ helps to calculate the corresponding response of the n/w for the specified excitation. For a given n/w the T.F. always have a fixed value.

The impulse response of the network represents the o/p voltage in the time domain when the excitation is unit impulse function.

The impulse response of the network is always a fixed value and ^{also} represents the inverse Laplace transform of the transfer funcⁿ of the n/w.

Ex: If $V_i(t) = e^{-t} u(t)$ then $V_o(t) = e^{-2t} u(t)$
find $V_o(t)$ if $V_i(t) = e^{-3t} u(t)$

Case I

$$V_i(t) = e^{-t} u(t)$$

$$V_i(s) = \frac{1}{s+1}$$

$$V_o(t) = e^{-2t} u(t)$$

$$V_o(s) = \frac{1}{s+2}$$

$$\frac{V_o(s)}{V_i(s)} = \left[H(s) = \frac{s+1}{s+2} \right] \Rightarrow 1 - \frac{1}{s+2}$$

$$h(t) = \delta(t) - e^{-2t} u(t)$$

Impulse response of n/w

Case IInd

$$V_i(t) = e^{-3t} u(t)$$

$$V_i(s) = \frac{1}{s+3}$$

$$V_o(s) = H(s) V_i(s)$$

$$= \frac{s+1}{(s+2)(s+3)} \quad (\text{by partial frac})$$

$$= \frac{-1}{(s+2)} + \frac{2}{(s+3)}$$

• Laplace Transform of some Basic function

$$1. \delta(t) \longrightarrow 1$$

$$2. u(t) \longrightarrow 1/s$$

$$3. x(t) \longrightarrow 1/s^2$$

$$4. f(t-T) \longrightarrow F(s) e^{-sT}$$

$$5. e^{-at} \longrightarrow \frac{1}{s+a}$$

$$6. \sin bt \longrightarrow \frac{b}{s^2 + b^2}$$

$$7. \cos bt \longrightarrow \frac{s}{s^2 + b^2}$$

$$8. \frac{df(t)}{dt} \longrightarrow sF(s) - f(0^+); f(0^+) \equiv f(t) \Big|_{t=0^+}$$

$$9. \int_0^t f(t) dt \longrightarrow \frac{F(s)}{s} + \frac{f^{-1}(0^+)}{s}; f^{-1}(0^+) = \left(\int_0^t f(t) dt \right) \Big|_{t=0^+}$$

$$10. e^{-at} \sin bt \longrightarrow \frac{b}{(s+a)^2 + b^2}$$

$$11. e^{-at} \cos bt \longrightarrow \frac{s+a}{(s+a)^2 + b^2}$$

$$12. t e^{-at} \longrightarrow \frac{1}{(s+a)^2}$$

$$13. t^n u(t) \longrightarrow \frac{n!}{s^{n+1}}$$

- Analysis of any electrical N/w using KVL & KCL eqⁿ

KVL

Voltage fall $\Rightarrow +ve$
Voltage Rise $\Rightarrow -ve$

Convention

No. of KVL equation $= b - (n - 1)$

where $b =$ NO. of Branches

$n =$ NO. of Nodes.

What to measure:-


- (1) Branch voltage (2) Branch current
- (3) Node voltage (4) loop current.

KCL

$\bullet \rightarrow$	$\Rightarrow +ve$
$\bullet \leftarrow$	$\Rightarrow -ve$

Convention

No. of KCL equation $= n - 1$

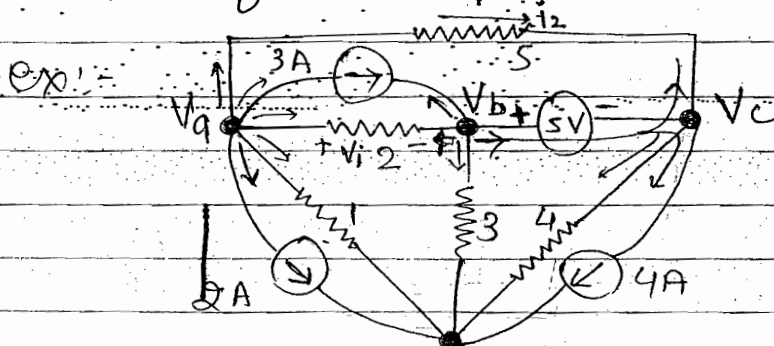

To find V_a, V_b, V_c

$$V_b - V_c = 5$$

$$V_c = V_b - 5$$

$V_c = V_b - 5$ Ref. Node

dependent or Redundant or Super-Node

- Whenever a voltage source is present b/w two Node one Node become independent and other become dependent. And this dependent get redundant


$$[V_a] \Rightarrow 2 + \frac{V_a - 0}{1} + \frac{V_a - V_b}{2} + 3 + \frac{V_a - V_c}{5} = 0 \quad \text{--- (1)}$$

$$[V_b] \Rightarrow -3 + \frac{V_b - V_a}{3} + \frac{V_b - 0}{3'} + \left[\frac{V_c - 0}{4} + 4 + \frac{V_c - V_a}{5} \right] = 0 \quad \text{--- (2)}$$

put $V_c = V_b - 5$


find $V_a, V_b, V_c = V_b - 5$

case 1 :-

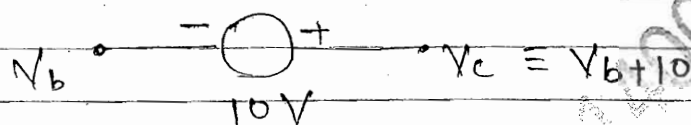

but we don't know the value of current b/w V_b & V_c

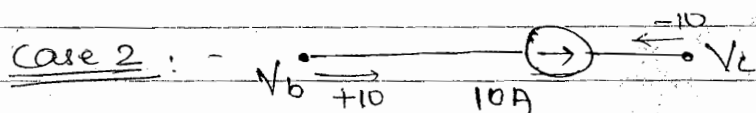2 KCL eqn :- V_a, V_b { replace all $V_c = V_b + 10$ }




3 KCL eqn :- V_a, V_b, V_c




- ✓ In this case magnitude of current will remain same
- ✓ V_b and V_c voltage value remain same. No change due to value of series resistance.
- ✓ Voltage across the dependent source is arbitrary and voltage change due to series resistance is adjusted by dep. source. So V_b, V_c remain same

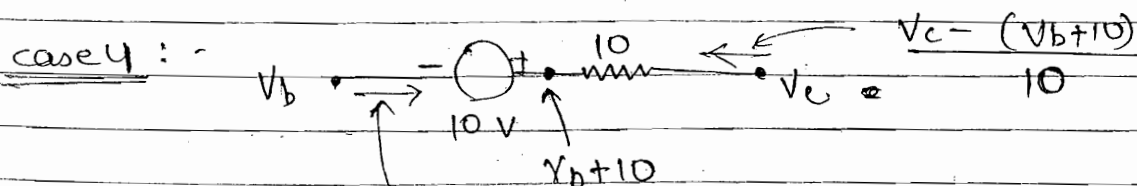
3 KCL eqn V_a, V_b, V_c --- same as case 2



3 KCL eqn :-
 V_a, V_b, V_c

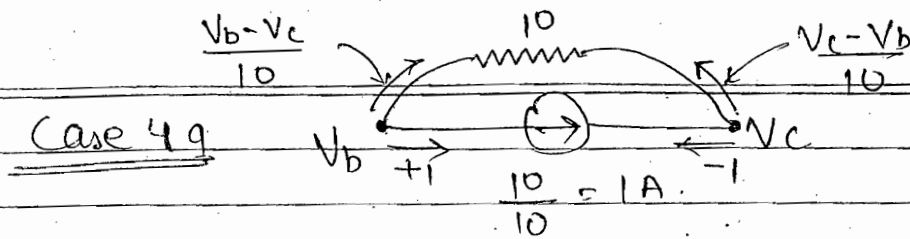


3 KCL eqn :- V_a, V_b, V_c

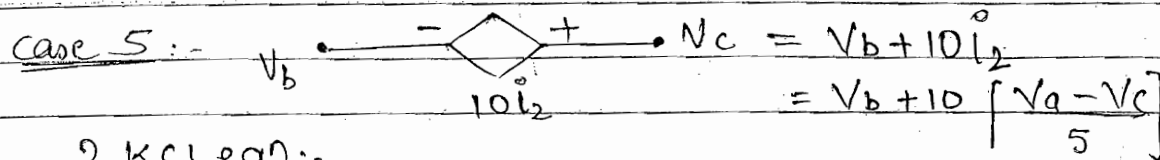


2 KCL eqn :-
 V_b, V_a


$3V_c = V_b + 2V_a$

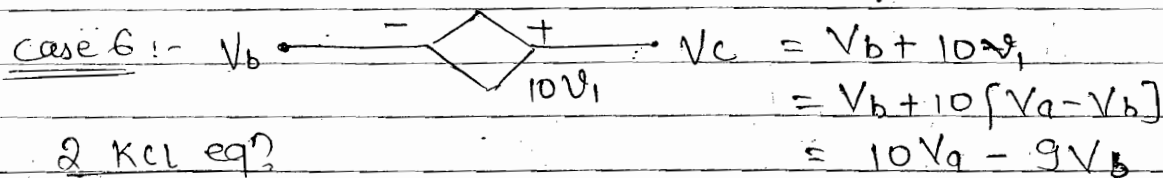

2 KCL eqn
 V_a, V_b

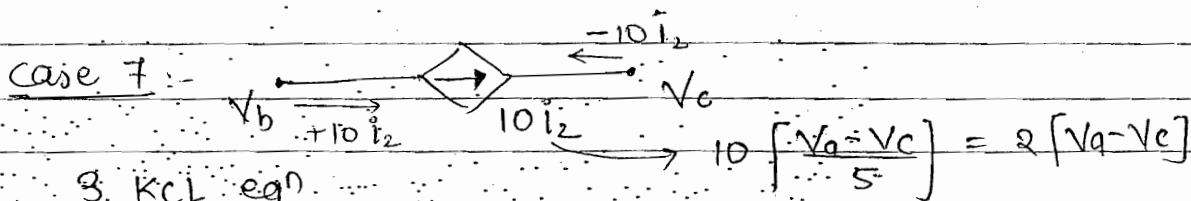


3 KCL eqn
 V_a, V_b, V_c

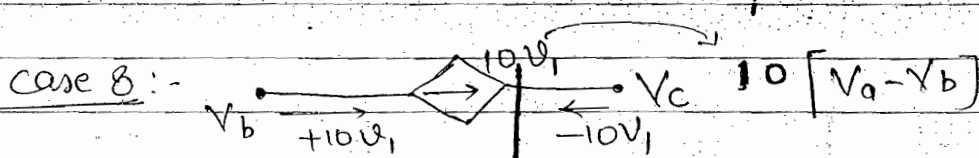


3 KCL eqn
 V_a, V_b, V_c

- Whenever any voltage dependent or independent source is present b/w two nodes in KCL, one node complex may get redundant.

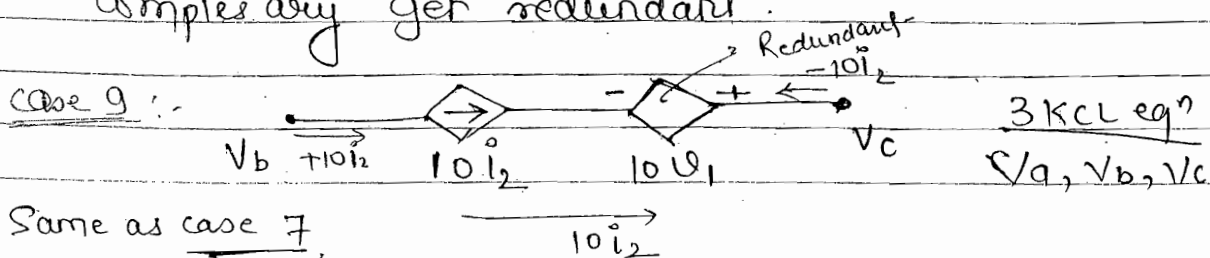

Case 10


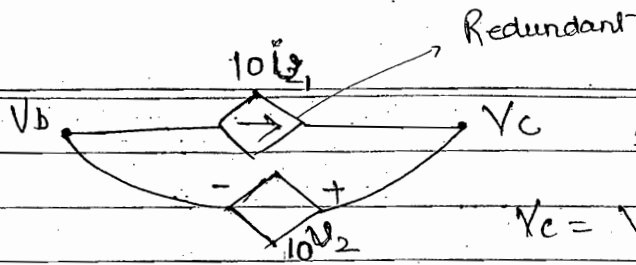


2 KCL:- V_a, V_b

$$V_c = V_b + 10i_2$$


Same as case 5.

Ex:- Series RC ckt:-

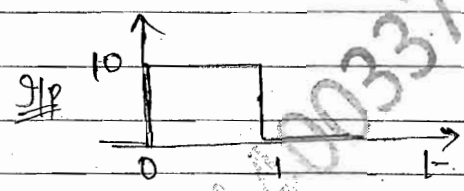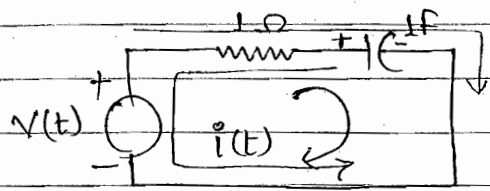

To find $i(t)$ for $t > 0$

Solution Assume: Zero initial condition

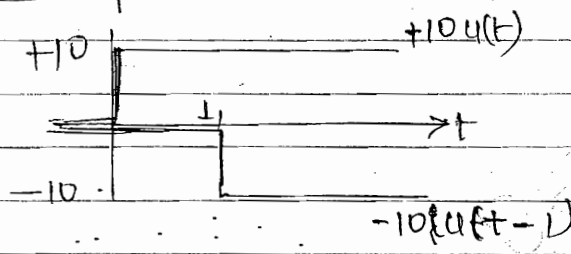

$$V(t) = 10u(t) + (-10u(t-1))$$

$$V(s) = \frac{10}{s} - \frac{10e^{-s}}{s} = \frac{10(1-e^{-s})}{s}$$

By KVL $V(t) = Ri(t) + \frac{1}{C} \int_0^t i(t) dt$

$$V(s) = I(s) + \frac{I(s)}{s}$$


$$V(s) = I(s) + \frac{I(s)}{s} + \frac{i^{-1} 10u(t)}{s}$$

$$I(s) = \frac{10(1-e^{-s})}{(s+1)s} \quad \left\{ \int_0^t i(t) dt \right\}_{t=0^+} = Q(t) \Big|_{t=0^+} = Q(0) = 0$$

when no charge, no voltage

$$I(s) = \frac{10 \cdot (1-e^{-s})}{(s+1)} = \frac{10}{s+1} - \frac{10e^{-s}}{s+1}$$
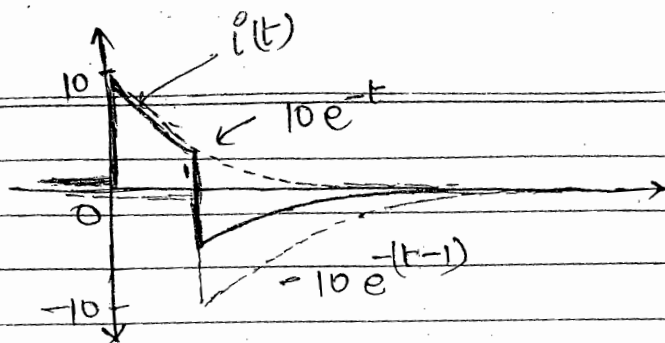
$$i(t) = \underbrace{10e^{-t}u(t)}_{(1)} - \underbrace{10e^{-(t-1)}u(t-1)}_{(2)}$$



graphical

Representation

- Reversal of current is possible because capacitor will get discharge after charged.
- Initially capacitor having no charge (NO voltage), so capacitor will act as s.c.


$\Rightarrow$ If $v(t) = V_0 u(t)$

Then $i(t) = \frac{V_0}{R} e^{-t/T} u(t)$

$T = RC$

Time constant

- Significance of Time Constant:-

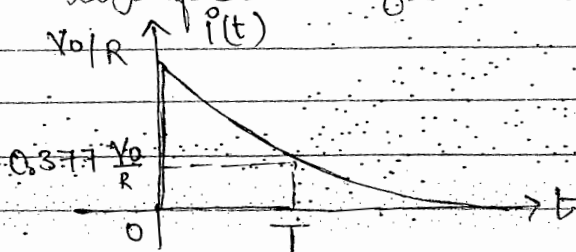


at $t = T$

$i(t) = \frac{V_0}{R} e^{-1}$

$\approx 0.377 \frac{V_0}{R}$


Summary:- (series RC ckt)

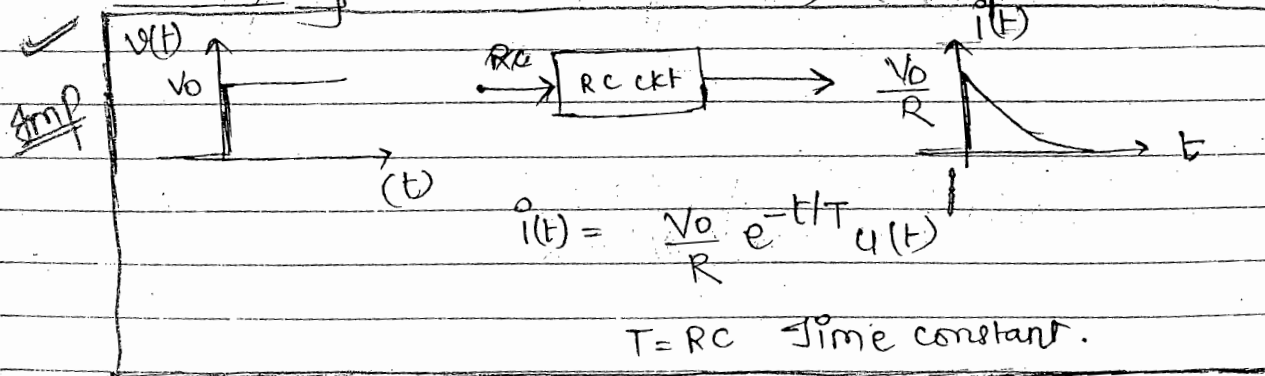

Main Points:-

- (1) Initially at $t=0$, any capacitor act as a short ckt, so that the current through RC N/w is Maximum.
- (2) At $t=\infty$, or steady state condition the capacitor acts as open ckt, so that current through RC N/w becomes zero.
- (3) For Pulse excitation Reversal of current takes place in the RC N/w
- (4) For step excitation the current through RC N/w decreases exponentially with a time constant T . This time constant controls the rate at which the current through RC N/w decreases and depends only upon numerical values of R and C components value.
- (5) The time constant of the RC N/w Represents the time at which the current through RC N/w is decreased to 37.07% of its initial value.


Ex:- Series RC ckt:-

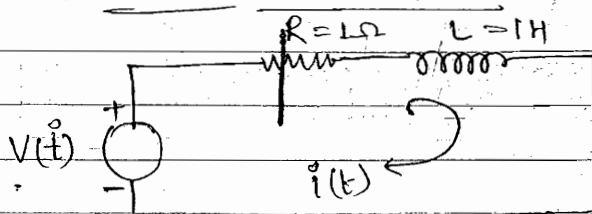

To find:-

$i(t)$ for $t > 0$

assume:- Initial condition = Zero

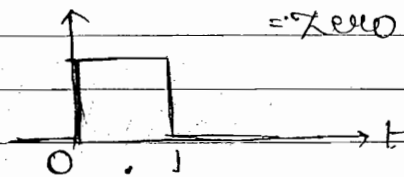

Solution

KVL:-

$$\Rightarrow V(t) = R i(t) + L \frac{di(t)}{dt}$$


$$\Rightarrow V(s) = I(s) + s I(s) - i(0^+) = \frac{10}{s} (1 - e^{-s})$$

$$I(s) = \frac{10(1-e^{-s})}{s(s+1)}$$


$$= 10 \left[\frac{1}{s} - \frac{1}{s+1} \right] (1-e^{-s})$$

$$= 10 \left[\frac{1}{s} - \frac{1}{s+1} \right] - 10 \left[\frac{1}{s} - \frac{1}{s+1} \right] e^{-s}$$
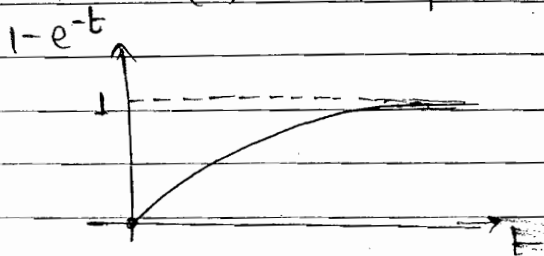
$$i(t) = 10[1-e^{-t}]u(t) - 10[1-e^{-(t-1)}]u(t-1)$$



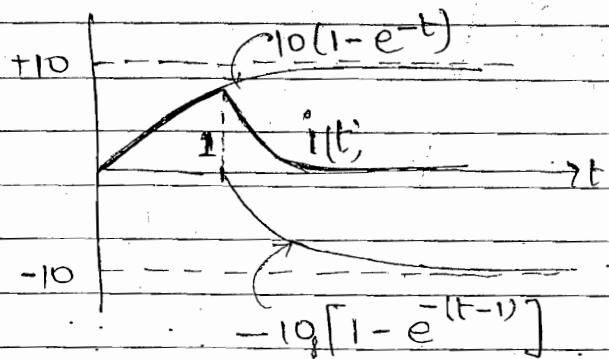$[1-e^{-t}] \Rightarrow$ at $t=0$, $1-1=0$
 $\Rightarrow$ at $t=\infty$, 1




- $\Rightarrow$ RC N/w $\Rightarrow$ Reversal of Current
- $\Rightarrow$ RL N/w $\Rightarrow$ NO. Reversal of Current

If $v(t) = V_0 \cdot u(t)$
 then $i(t) = \frac{V_0}{R} (1-e^{-t/T}) u(t)$

$T = \frac{L}{R}$
 Time constant.

Summary:- (Series RL N/w)

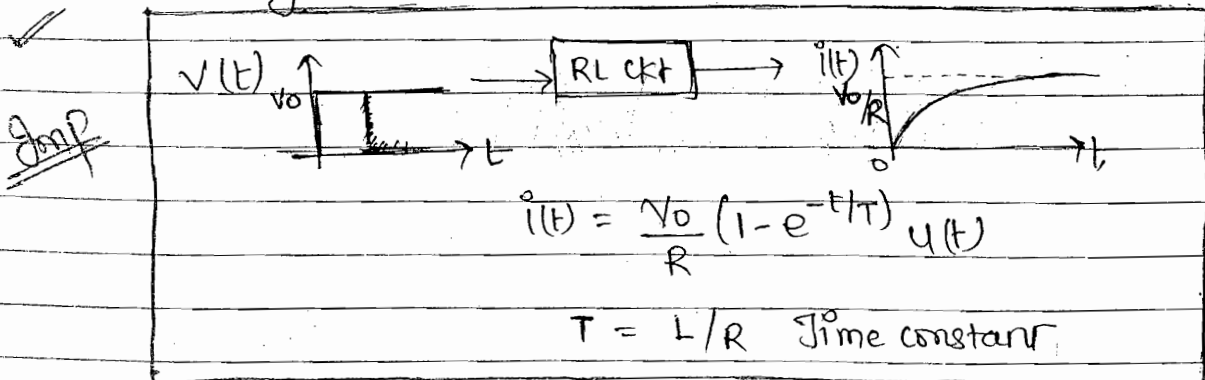

Main Points:

- (1) Initially at $t=0$, the inductor acts as an open circuit so that the current through series RL N/w is zero.
- (2) For step excitation the current through the inductor increases exponentially with some time constant T . This time constant T depends only upon the numerical values of R and L components and controls the rate at which current through N/w increases exponentially.
- (3) For pulse excitation, reversal of current takes place in a series RC N/w whereas no such reversal takes place in a series RL N/w.

Initial & Final Values of A function:-

$$f(t) \begin{cases} V(t) \\ I(t) \end{cases}$$

Initial Value:

$$f(0^+) = f(t) \Big|_{t=0^+} \quad \text{Initial condition}$$

$$\boxed{f(0^+) = \lim_{s \rightarrow \infty} s F(s)} \quad \text{Initial Value Theorem}$$

Final Value:- steady state ($s \rightarrow 0$) value.

$$f(\infty) = f(t) \Big|_{t=\infty}$$

$$\boxed{f(\infty) = \lim_{s \rightarrow 0} s F(s)} \quad \text{Final Value Theorem}$$

ex - $F(s) = \frac{s+1}{(s+2)(s+3)}$ To find $f(0^+)$
 $f(\infty)$

Solution:- $f(t) = (-e^{-2t} + 2e^{-3t})u(t)$

$f(0^+) = +1$; $f(\infty) = 0$

$s+1 = A(s+3) + B(s+2)$

put $s = -3$

$B = 2$


put $s = -2$

$A = -1$

- Cannot apply for sinusoidal s/p. (oscillatory).

• Transient Response of An electrical Network.

Transient Response

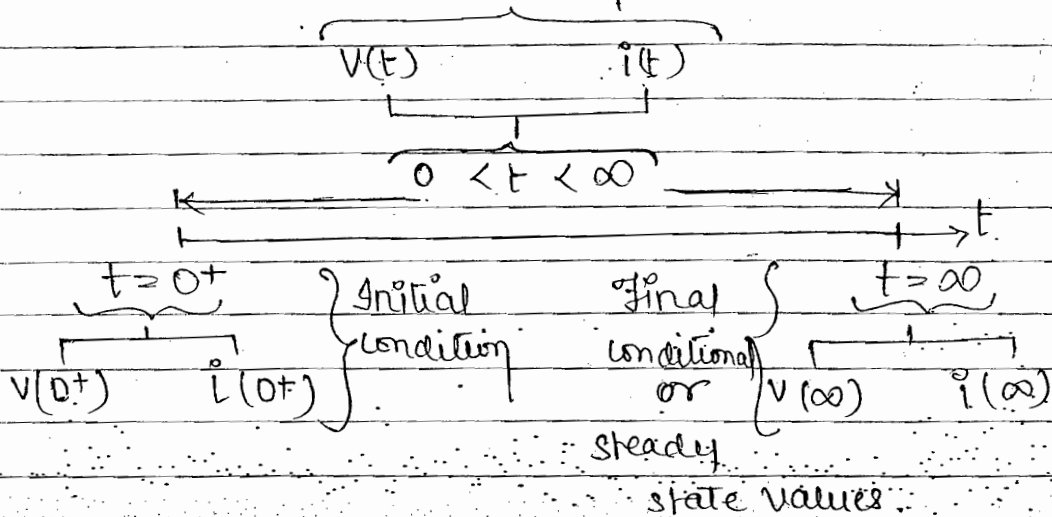


⇒ R (Resistor) do not store the energy.

✓ Behaviour of L & C

case 1 In time Domain

✓ <u>Element</u>	$t = 0^+$	$t = \infty$
✓ <u>Capacitor</u>	✓	✓
	✓	✓
	✓	

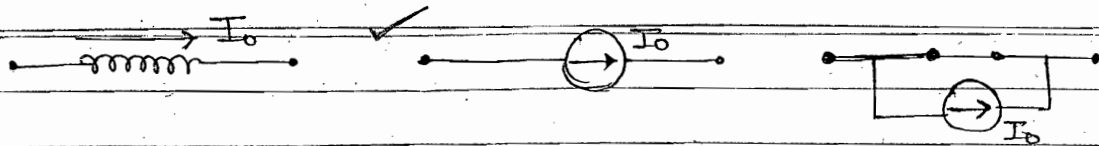


- (1) Initially at $t=0$ any capacitor act as a short ckt where as any inductor act as open ckt
- (2) at $t=\infty$ or in steady state condition, any capacitor acts as an open ckt where as any inductor acts as short ckt.
- (3) Initially at $t=0$ any capacitor with initial voltage act as a constant voltage source whereas any inductor with initial current act as a constant current source.

Case 2:- In s-domain

(a) Inductor


$$V(t) = L \frac{di(t)}{dt}$$

$$V(s) = L [sI(s) - i_L(0^+)]$$

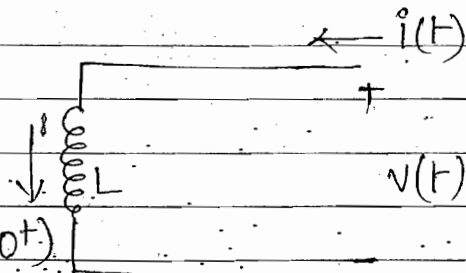

$$V(s) = sL \cdot I(s) - L i_L(0^+)$$

KVL, series ckt

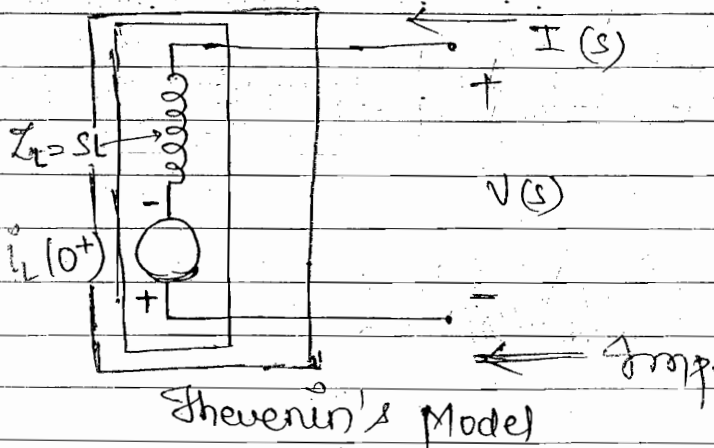


See the initial condition direction, $i_L(0^+)$ direction is downward, for downward direction of current polarity will be $+$.

Stick to Remember.

(b) Capacitor :-

$$i(t) = C \frac{dv(t)}{dt}$$


$$I(s) = C [s V(s) - v_c(0^+)]$$

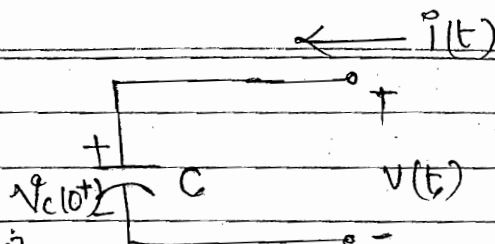

31/10/2014

$$V(s) = \frac{1}{Cs} I(s) + \frac{v_c(0^+)}{s}$$

--- KVL
series ckt.

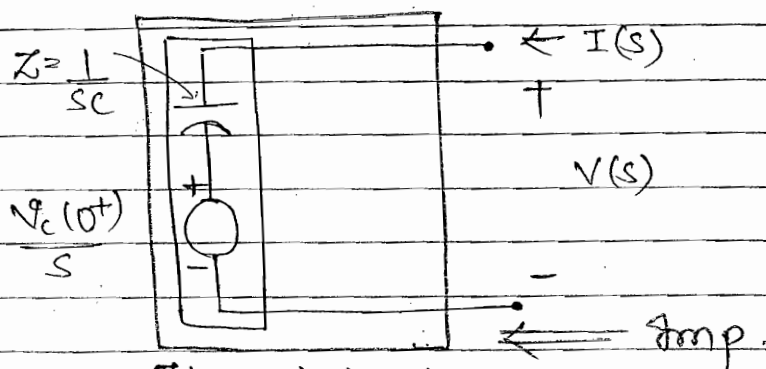


Thevenin's Model

according to polarity of $v_c(0^+)$ in initial Model, same to thevenin's Model, if $v_c(0^+) = -$ In Model also $\frac{v_c(0^+)}{s}$

Ex:- In the circuit shown the switch is initially open. The switch is closed at $t=0$. Find the current and the rate of change of current through the N/w at $t=0^+$

Solution

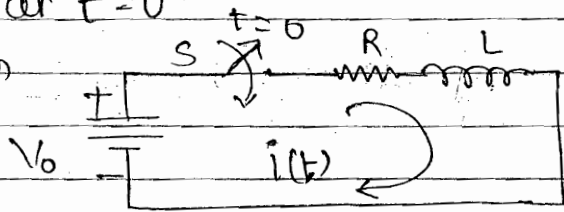

To find $i(0^+)$
 $\frac{di(0^+)}{dt}$

• at $t=0^-$


S = open

$$i(0^-) = 0$$

• at $t=0^+$

S = close

$L \Rightarrow \text{o.c}$

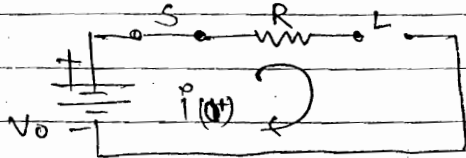

$$i(0^+) = 0$$

--- Amp.

Imppt


The current through the inductor and voltage through

very imp.

$$\boxed{\begin{aligned} i_L(0^-) &= i_L(0^+) \\ V_C(0^-) &= V_C(0^+) \end{aligned}}$$

the capacitor don't change instantaneously. Therefore these values remain same just before and just after the switch has been closed.]

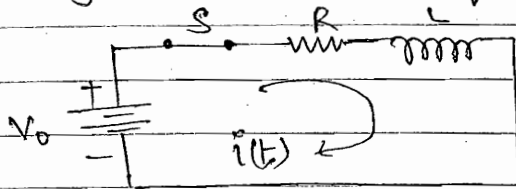General circuit for $t > 0$ [btw 0^+ and ∞) neither behave O.C and nor S.C]



$$V_0 = R i(t) + L \frac{di(t)}{dt}$$


at $t = 0^+$

$$R \underbrace{i(0^+)}_{=0} + L \frac{di(0^+)}{dt} = V_0$$

$$\frac{di(0^+)}{dt} = + \frac{V_0}{L} \quad \text{Amp/sec}$$


Ex:- In the circuit shown the switch is initially at position a for a long time till the steady state reach. The switch is moved to position b. Find an general expression of a current through the N/o for $t \geq 0$.

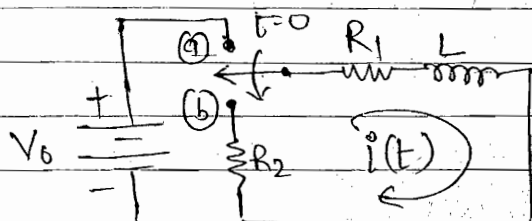Solution whenever long time till the steady state reach terminology given consider final values



To find $i(t)$ for $t > 0$

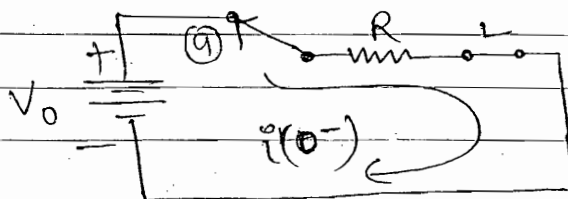$t = 0^-$: switch at (a) position. [steady state conditⁿ/ final values]
 $L \rightarrow$ S.C




$$i(0^-) = \frac{V_0}{R_1}$$

$$i(0^-) = \frac{V_0}{R_1} = i(0^+)$$


$$\therefore \text{as } i(0^-) = i(0^+)$$

$t > 0$; switch at (b) position.

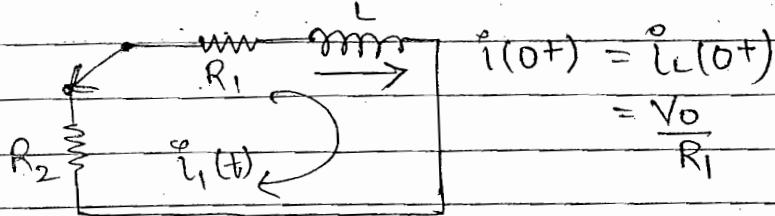

$$i(0^+) = i_L(0^+) = \frac{V_0}{R_1}$$

$$i_L(0^+) = V_0 / R_1$$

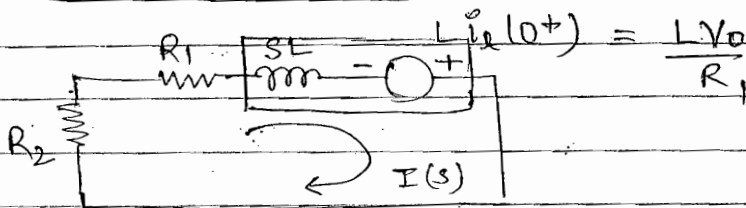

$$L i_L(0^+) = \frac{L V_0}{R_1}$$

$$\therefore L i_L(0^+) = \frac{L V_0}{R_1}$$

$$\Rightarrow I(s) (R_2 + R_1 + sL) - V_0 L / R_1 = 0$$

$$\Rightarrow I(s) = \frac{V_0 L}{R} \cdot \frac{1}{L(s+a)} \quad ; \quad a = \frac{R_1 + R_2}{L}$$


$$I(s) = \frac{V_0}{R} \cdot \frac{1}{(s+a)}$$

$$i(t) = \frac{V_0}{R} e^{-at} \cdot u(t)$$

$$i(t) = i(0^+) e^{-t/T} \cdot u(t)$$

$$i(0^+) = \frac{V_0}{R}$$
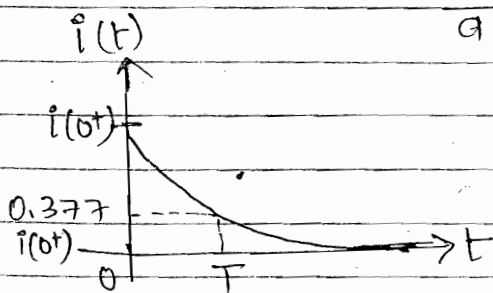
$$\text{where } T = \frac{1}{a} = \frac{L}{R_1 + R_2} = \frac{L}{R_{eq}}$$



at $t = T$

$$i(t) = i(0^+) e^{-1} \approx 0.377 i(0^+)$$

Imp

pt

In an RL N/w the time constant represents the time at which the current through the N/w

is decrease to 37.7% of its initial value.


✓ This time constant controls the rate of exponential decay of the current, and depends purely upon the numerical values of R and L components.

• Summary:- series RL circuit


$$i(t) = \frac{V_0}{R} e^{-t/T} u(t)$$

$$i(t) = \frac{V_0}{R} (1 - e^{-t/T}) u(t)$$

$$T = L/R$$

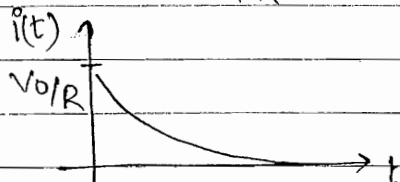

$$T = L/R$$

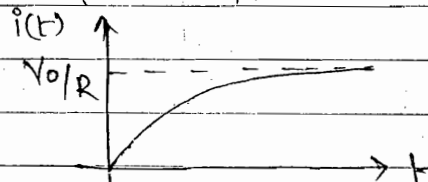

- valid when IC is finite

- valid when I.C. = 0


Chap2 (7)

at $t = 0^-$ Switch $\rightarrow$ open

S.S condition / Final value

L $\Rightarrow$ S.C.

C $\Rightarrow$ O.C.

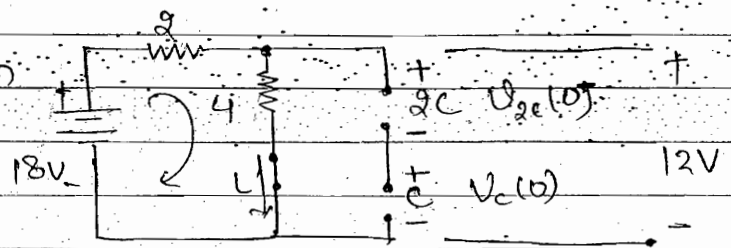

$$i(0^-) = i(0^+) = \frac{18}{6} = 3 \text{ Amp.}$$


$$V_{2C}(0^-) = V_{2C}(0^+) = 4$$

$$V_C(0^-) = V_C(0^+) = 8$$

$$\text{const.} = CV$$

$$V \propto \frac{1}{C}$$

at $t = 0^+$ switch $\rightarrow$ close

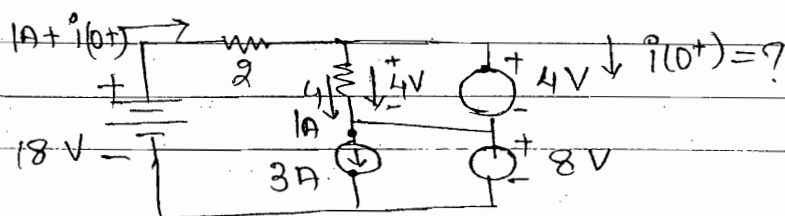


• KVL:- $-18 + 2(1 + i(0^+)) + 4 + 8 = 0$

$i(0^+) = 2 \text{ Amp. Am.}$

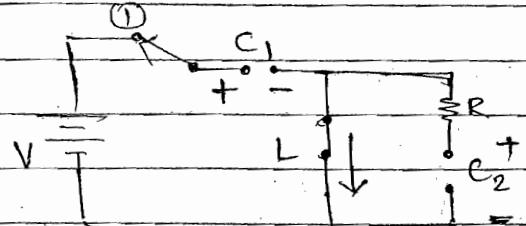Q. 22 at $t = 0^-$

Switch at (1). (S.S. $\rightarrow$ Final Value)

$L \Rightarrow \text{S.C.}$ $C \Rightarrow \text{O.C.}$



$i(0^-) = i(0^+) = 0$


$V_{C1}(0^-) = V_{C2}(0^+) = V_{C2}(0^-) = V_{C2}(0^+) = 0$
 $\equiv V$

$i_{C1}(0^-) \neq i_{C1}(0^+) \equiv 0$

at $t = 0^+$ switch at (2)

KVL eqn.

$i_1(0^+) = -\frac{V}{2R}$


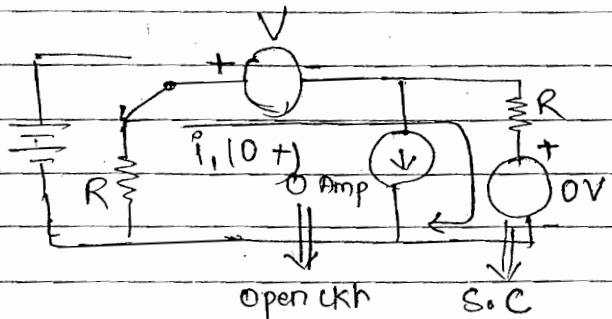


Q. 25 at $t = 0^-$

switch is closed S.S./F.C.

$L \Rightarrow \text{S.C.}$

at $t > 0$ switch is open

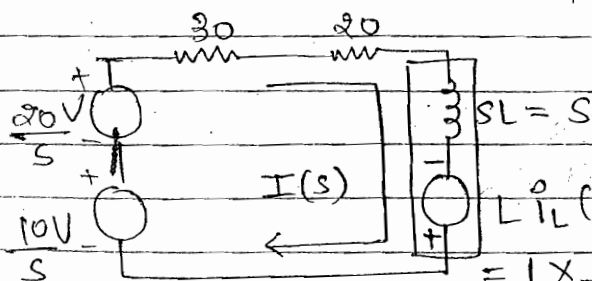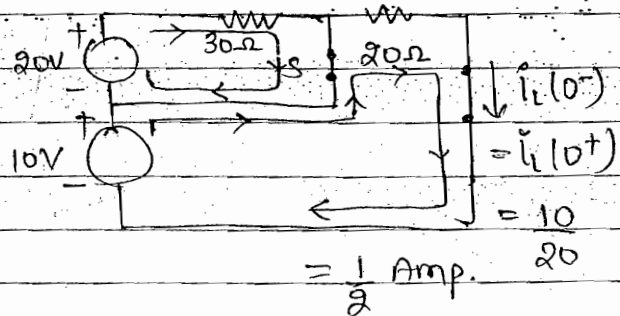

$\Rightarrow \frac{20+10}{s} = \frac{1}{2} = I(s) [50+s]$

$= 1 \times \frac{1}{2} = \frac{1}{2} \Rightarrow \frac{40+20+s}{2s} = I(s) [50+s]$


$\Rightarrow I(s) = \frac{60+s}{2s[50+s]}$

$\Rightarrow \frac{(60+s)/2s}{50+s} = I(s)$


$i(t) = 0.6 - 0.1 e^{-50t} \text{ Avg}$

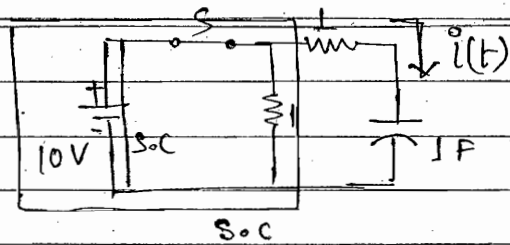Q.19 $t > 0$ switch is closed

$$T = RC = 1 \times 1 = 1 \text{ sec Ans}$$



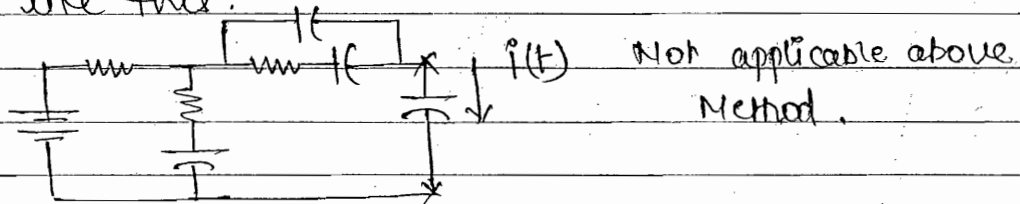this method of $T = RC$ only applicable for this ques. If given like this.



for such Nlw. how to find Time Constant: -


$$T = R_{eq} C_{eq} \text{ ----- } RC \text{ ckt}$$

$$= \frac{L_{eq}}{R_{eq}} \text{ ----- } RL \text{ ckt}$$

Q.4 At $t = 0^-$ switch-closed

S.O.S / F.O.C

$C \Rightarrow O.C$; $L \Rightarrow S.C$

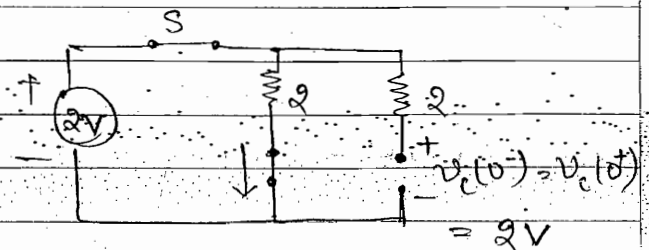


$$i(0^-) = i(0^+) = 2/2 = 1 \text{ Amp.}$$

At $t > 0$ switch-open

$\Rightarrow$ KVL eqn in loop

$$\Rightarrow 1 + \frac{2}{s} = I(s) \left[\frac{2+s+1+2}{4s} \right]$$

$$I(s) = \frac{s+2}{8s+4s^2+1+8s}$$

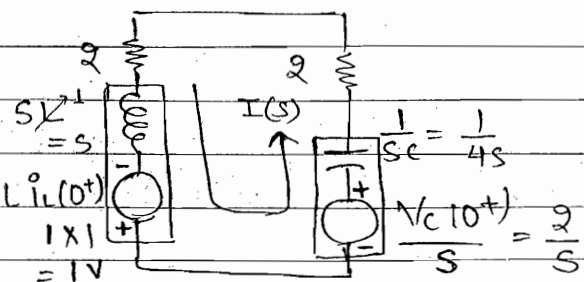


$$= \frac{(s+2)4}{4s^2+16s+1} = \frac{(s+2)4}{4(s+2)^2} = \frac{1}{s+2} \quad \& \quad i(t) = e^{-2t}$$

$$\Rightarrow i(t) = e^{-2t} \equiv e^{-t/T} \quad \therefore T = \frac{1}{2} \text{ sec Ans}$$

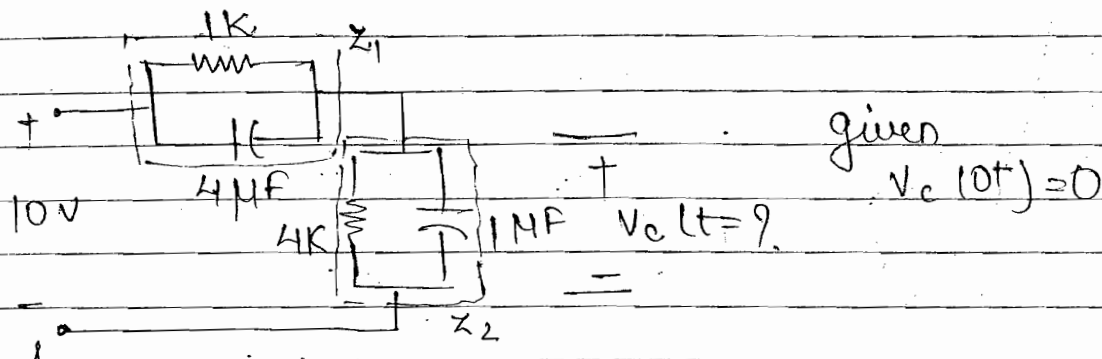Q.34 Voltage division method is Not applicable Bcoz

• product of RC in Both Z_1 and Z_2 is equal. $V_c(t) = \frac{Z_2}{Z_1 + Z_2} V_s$

If Z_1 and Z_2 having different values then only Voltage division method is applicable




• Only for RC ckt

$$V_c(t) = V_c(\infty) - [V_c(\infty) - V_c(0^+)] e^{-t/T}$$

• Only for RL ckt

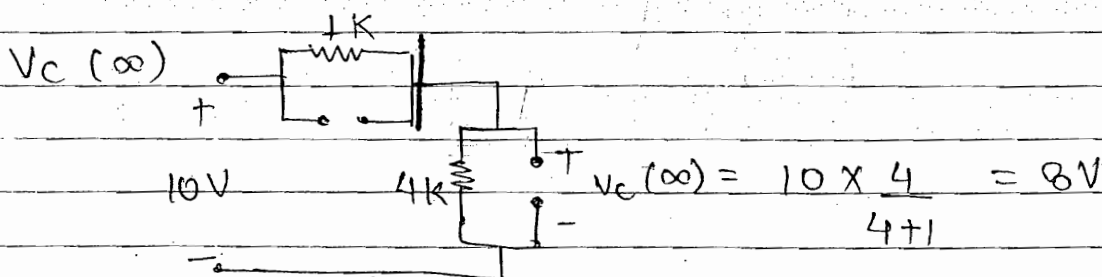
$$i_L(t) = i_L(\infty) - [i_L(\infty) - i_L(0^+)] e^{-t/T}$$



$$V_c(t) = V_c(\infty) - [V_c(\infty) - V_c(0^+)] e^{-t/T}$$

$\equiv 8$ $\equiv 0$

$$T = R_{eq} C_{eq} \quad |_{10V} \Rightarrow \infty$$

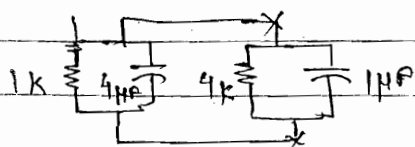

$$R_{eq} = 1 || 4 = 0.8K$$


$$C_{eq} = 4 || 1 = 5 \mu F$$

$$T = R_{eq} C_{eq} = 0.8 \times 5 = 0.004 \text{ sec.}$$

$$V_C(t) = 8 - [8 - 0]e^{-t/0.004} = 8[1 - e^{-t/0.004}] \text{ A.}$$

Q. 45 at $t=0^-$, $s \rightarrow$ open

S.S./F.c. $L \Rightarrow$ S.c.

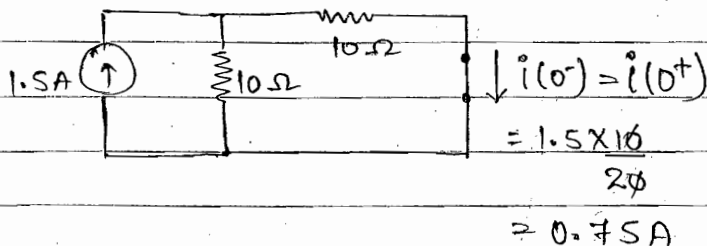

at $t > 0$ $s \rightarrow$ close.

$$i_L(t) = i_L(\infty) - [i_L(\infty) - i_L(0^+)]e^{-t/T}$$

$\underbrace{0.5 \text{ A.}}_{i_L(\infty)} \quad \underbrace{0.75 \text{ A}}_{i_L(0^+)} \quad \underbrace{10 \text{ A}}_{\text{source}} \quad \underbrace{10 \text{ ohm}}_{\text{resistor}} \quad \underbrace{10 \text{ ohm}}_{\text{resistor}} \quad \underbrace{15 \text{ mH}}_{\text{inductor}}$

$$= 0.5 - [0.5 - 0.75]e^{-t/T}$$

at $t = \infty$ $L \Rightarrow$ S.c., R comes in ||


$$\text{SO } \frac{1.5}{3} = 0.5 \text{ A.}$$

$$T = \frac{L}{R_{eq}} = \frac{15 \text{ mH}}{15 \text{ ohm}} = 1 \text{ msec}$$

$1.5 \text{ A} = \text{D.C.}$

$$\therefore R_{eq} = (10 || 10) + 10 = 15 \text{ ohm}$$
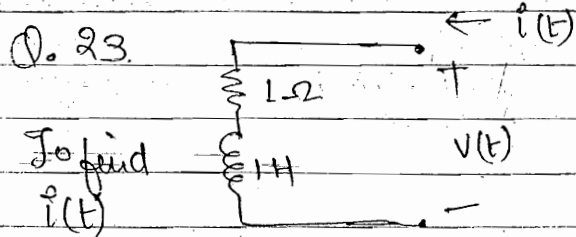
$$i_L(t) = \frac{V(t)}{10} = \frac{1}{10} \left[10 i_L(t) + L \frac{di_L(t)}{dt} \right] \quad \text{Ans (a)}$$



When the supply is sinusoidal
Now apply Laplace

$$V(t) = 10\sqrt{2} \cos(t + 10^\circ) + 10\sqrt{5} \cos(2t + 10^\circ)$$

$\omega=1$ $\omega=2$

$$Z = R + j\omega L = 1 + j\omega = 1 + j1 = \sqrt{2} \angle 45^\circ \quad \omega=1$$

$$= 1 + j2 = \sqrt{5} \angle \theta \quad \omega=2$$

$$\theta = \tan^{-1}\left(\frac{2}{1}\right) = 63.4$$

$$i(t) = \frac{10\sqrt{2}}{\sqrt{2} \angle 45^\circ} \cos(t+10^\circ) + \frac{10\sqrt{2}}{\sqrt{2} \angle 0} \cos(2t+10^\circ)$$

$$= 10 \cos(t+10^\circ-45^\circ) + 10 \cos(2t+10^\circ-0^\circ)$$

Q.15 $H(s) = \frac{1}{s+1}$ $V_i(t) = \cos t \equiv V_i \cos \omega t$ $V_o(t) = ?$

Solution $V_o(t) = V_o \cos \omega t \equiv V_o \cos t$

$$H(s) = \frac{1}{s+1} = \frac{1}{j\omega+1} = \frac{1}{j+1} = \frac{1}{\sqrt{2} \angle 45^\circ}$$

$$= \frac{V_o}{V_i} \angle -45^\circ$$

$$s = j\omega$$

$$V_o(t) = \frac{1}{\sqrt{2} \angle 45^\circ} \cos t = \frac{1}{\sqrt{2}} \cos(t-45^\circ)$$

Q.21 $v(t) = 10(t-0.01)e^{-100t}$

$$V(s) = \frac{10}{(s+100)^2} - \frac{0.1}{(s+100)} = \frac{10 + 0.1(s+100)}{(s+100)^2}$$

Denominator = $(s+100)^2$


$$= s^2 + (100)^2 + 200s = s^2 + 2\delta\omega_n s + \omega_n^2$$

$\delta = 1$, critically damped

$$2\delta\omega_n = 200$$

$$\delta = \frac{200}{2 \times 100} = 1$$

Q.20 (B)

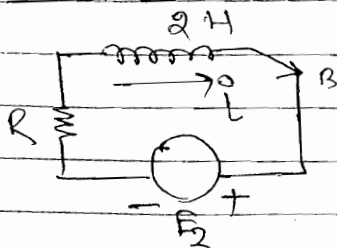

$$i(t) = i(\infty) - [i(0) - i(\infty)]e^{-t/\tau}$$

$$= 4 - [4 - (-8)]e^{-t/\tau}$$


$$= 4 - 12e^{-t/\tau}$$

$$\frac{di(t)}{dt} = \frac{12}{\tau} e^{-t/\tau}$$

$$\frac{di(t)}{dt} = \frac{-12e^{-t/\tau}}{\tau}$$

$$\frac{di(0)}{dt} = 3 = \frac{1}{T} \cdot 12 \cdot 1 \quad \boxed{T = 4}$$

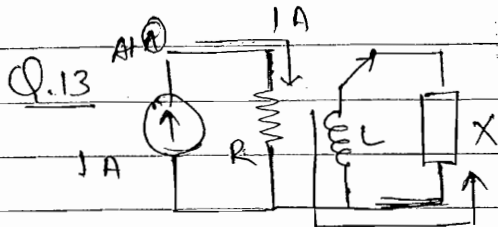
$$T = \frac{L}{R} ; R = \frac{2}{4} = \frac{1}{2} \Omega \quad \text{Ans}$$



$$i(t) = I \sin(\omega t + 30^\circ)$$

↑
leading

so X = capacitor.

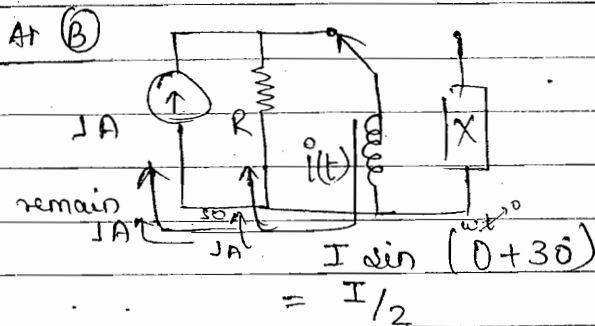

$$P = I^2 R$$

Const. Same same.


$$\frac{1}{2} I = 1A + 1A$$

$$I = 2A \quad \text{Ans}$$

Summary (Transient Response)


1st NOV 2014

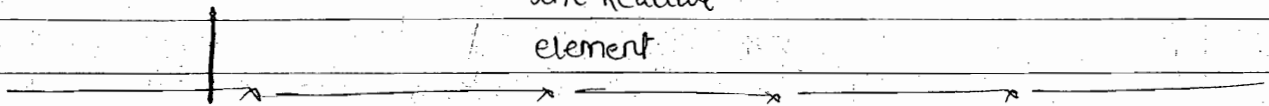Transient Response $\left[\begin{matrix} V_c(0^+) \\ i(0^+) \end{matrix} \right]$ Find I.C. in all the Reactive element (Next page)





Summary (Transient Response)


Transient
Response

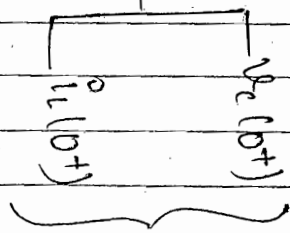

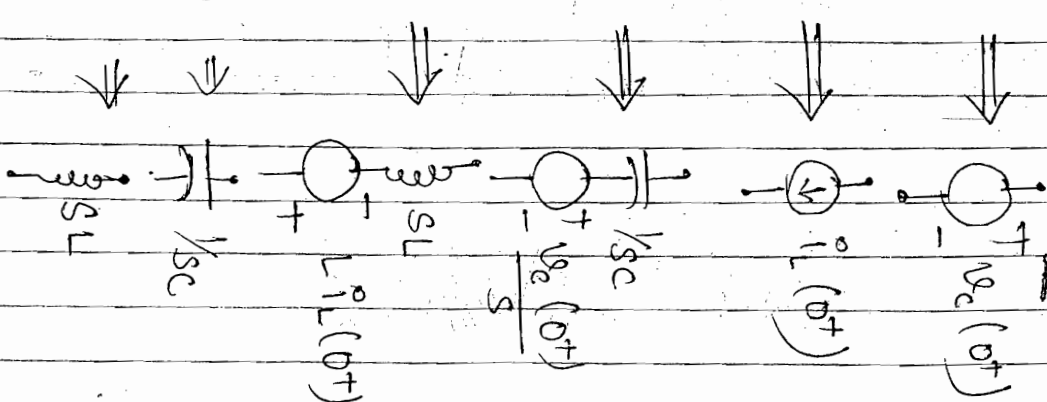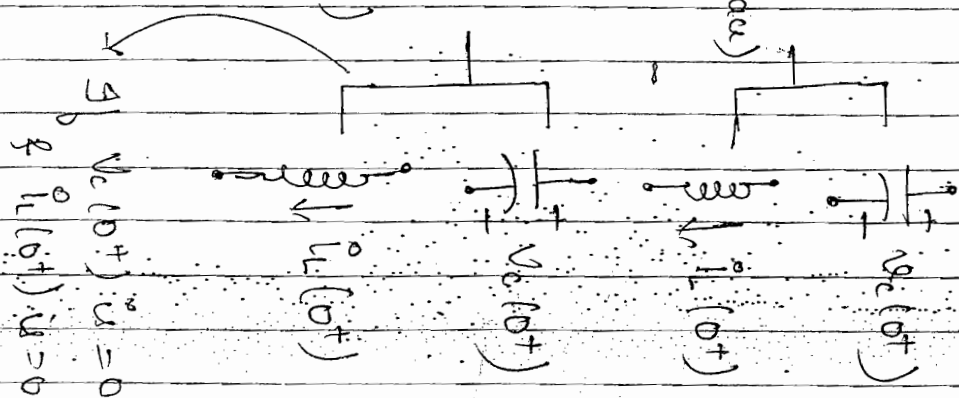$v_c(t+); i_L(t+)$
(Not use Laplace)
 $v(t); i(t)$
for $t > 0$
(for general eqn use Laplace)



Series RLC ckt

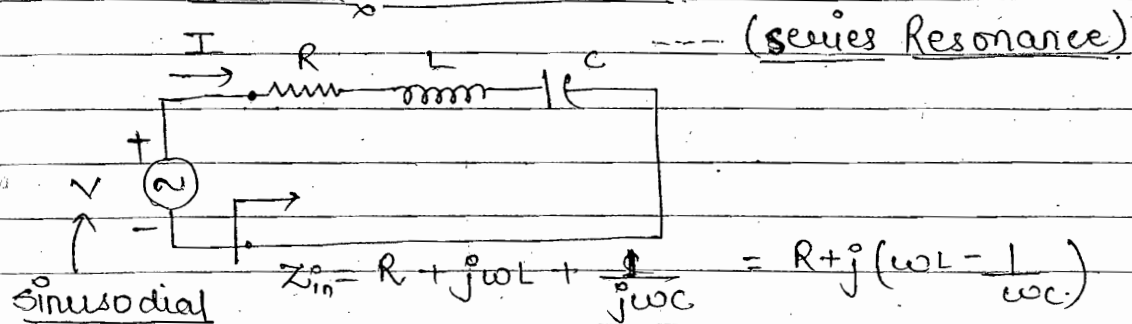

voltage source (fixed amplitude & variable freq.)

- In previous topic we study the behaviour of element when t is varying
- In this topic we study the behaviour of element when freq. is varying

	L	C	
$t = t$	L	C	} Transient response fixed freq. & variable time behaviour of ckt
$t = 0^+$	O.C	S.C	
$t = \infty$	S.C	O.C	
	$j\omega L$	$\frac{1}{j\omega C}$	
$\omega = \omega$	$j\omega L$	$\frac{1}{j\omega C}$	} Resonance fixed time instant & variable freq. behaviour of ckt
$\omega = 0^+$	S.C	O.C	
$\omega = \infty$	O.C	S.C	

at $\omega = \omega_0$; j term = 0

(*) $Z_{in} = R + j(0)$ --- minimum
 $= Z_0$

$$I_0 = \frac{V}{Z_{in}} \Big|_{\omega=\omega_0} = \frac{V}{Z_0} = \frac{V}{R} \text{ --- maximum } (I_0)$$

at $\omega = \omega_0$

$|V_L| = |V_C|$ & are out of phase by 180° .

at $\omega = \omega_0$

$$\omega_0 L - \frac{1}{\omega_0 C} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \dots \text{rad/sec}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \dots \text{Hz}$$

$$Z_{in} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$\omega = \omega_0$; Resistive

$\omega > \omega_0$; Inductive

(for this, voltage across inductor is max)

$\omega < \omega_0$; capacitive

(for this, voltage across capacitor is Max)

frequency Response:- $|I|$ vs ω

$$|I| = \frac{V}{|Z_{in}|} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$\Rightarrow$ ckt having RLC in series act as Band Pass filter.

$$I_0 = \frac{V}{R} \quad \text{max}$$

Imp Features:-


- (1) At resonance the j -term of Z_{in} impedance of the circuit is zero.
- (2) At ω_0 the N/w is resistive, Z_{in} voltage and Z_{in} current are in phase so that the power factor is unity.
- (3) At resonance Z_{in} impedance is minimum, so that current drawn by the N/w from the Z_{in} voltage source is maximum and therefore any series RLC N/w behaves as Band pass filter.
- (4) At resonance voltage across L & C are in magnitude but out of phase by 180° , so that the net voltage across LC combination is zero.
- (5) The ckt behaves differently at different frequencies of operation.

- for voltage and current gain $\rightarrow 20 \log$
- for power gain $\rightarrow 10 \log$

- (a) at ω_0 N/ω is Resistive and has p.f = unity
- (b) above ω_0 N/ω is Inductive and has p.f = lagging
- (c) Below ω_0 N/ω is capacitive and has p.f = leading

- (*) The frequency of Resonance Represent the rate at which electrical energy stored in the capacitor is transformed to the magnetic energy in the inductor and vice-versa. Transformation of these energy at a particular frequency represent phenomena of resonance

• freq. Response

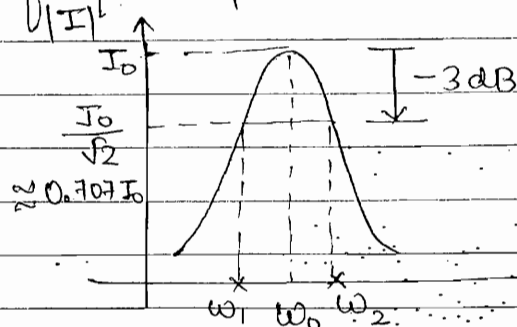

ω_1, ω_2 — cut off frequency
— half pow freq.

— -3 dB freq.

$Q_0 \rightarrow$ also voltage amplification factor.

at $\omega_2 \rightarrow$ ckt behaviour is inductive
at $\omega_1 \rightarrow$ ——— capacitive

• Quality Factor

$$Q_0 = \frac{|V_L|}{V} = \frac{|V_C|}{V} ; (\gg 1)$$

$$V_L = Q_0 V ; V_C = Q_0 V ; V_L \& V_C \text{ always greater than } V$$

$$Q_0 = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\omega_2 - \omega_1} \quad \left\{ \begin{array}{l} \omega_2 \approx \omega_0 + \frac{1}{2} \Delta\omega \\ \omega_1 \approx \omega_0 - \frac{1}{2} \Delta\omega \end{array} \right.$$

$$\Delta\omega = \omega_2 - \omega_1$$

• Quality Factor:-

$$Q_0 = \frac{|V_L|}{V} = \frac{|V_C|}{V}$$

$$\approx |V_L| = |I_0 j\omega_0 L| = I_0 \omega_0 L ; |V_C| = \left| \frac{I_0}{j\omega_0 C} \right| = \frac{I_0}{\omega_0 C}$$

$$\approx V = I_0 R$$

$$Q_0 = \frac{I_0 \omega_0 L}{I_0 R}$$

$$; Q_0 = \frac{I_0}{I_0 R \cdot \omega_0 C}$$

$$\boxed{Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} = \frac{1}{R} \sqrt{\frac{L}{C}}} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

• Bandwidth :- ($\Delta\omega$)

$$\Delta\omega = \frac{\omega_0}{Q_0} = \frac{1/\sqrt{LC}}{\frac{1}{R}\sqrt{\frac{L}{C}}} ; Q_0 = \frac{\omega_0}{\Delta\omega}$$

$$\boxed{\Delta\omega = \frac{R}{L} ; \Delta f = \frac{R}{2\pi L}} \quad \begin{matrix} \text{rad/sec} \\ \text{Hz} \end{matrix}$$


$$Q_0 \uparrow \rightarrow \Delta\omega \downarrow \quad \begin{matrix} R \downarrow \\ L \uparrow \end{matrix} \quad \text{-- not applicable}$$

- ≈ only $L \uparrow$ Applicable when req. at high cost and large size
- ≈ So we generally kept low value of R .

• Imp. Points:-

- 1) Quality factor represent the ability to select a particular desire frequency, thereby rejecting all other unwanted freq. components
- 2) For any tuned n/w the quality factor must be as high as possible.

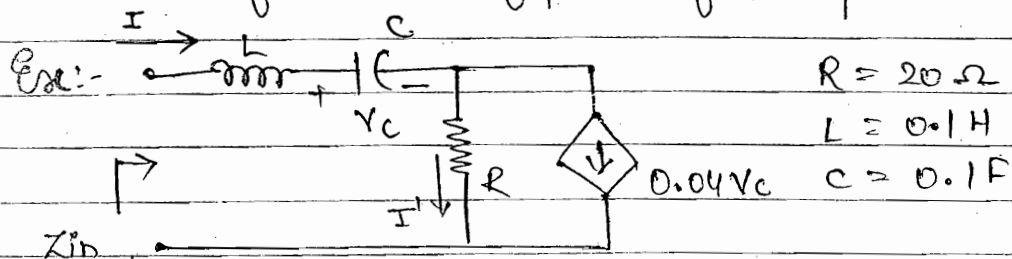- (3) The bandwidth of a N/w represents the range of freq. for which the current drawn by the N/w is decreased to 0.707 of its maximum value. For any tuned N/w the B.W. must be low to keep high quality factor.
- (4) The frequency of Resonance Represents the geometric mean of two half power frequency.



To find:- Z_{in} ; ω_0 ; $\Delta\omega$; Q ; ω_1 ; ω_2

Solution $I' = I - 0.04V_c$

$$V = j\omega L \cdot I + \frac{1}{j\omega C} \cdot I + (I - 0.04V_c)R$$

$$V = j\omega L \cdot I + \frac{I}{j\omega C} + \left(I - 0.04 \cdot \frac{1}{j\omega C} \cdot I \right) R$$


$$V = I j\omega L + \frac{I}{j\omega C} + I \left(1 - \frac{0.04}{j\omega C} \right) R$$

$$\frac{V}{I} = Z_{in} = R + j\omega L + \frac{1}{j\omega C} - \frac{0.04}{j\omega C}$$

$$= \frac{1}{j\omega C} [1 - 0.04]$$

$$= \frac{1}{j\omega \frac{C}{1-0.04}} = \frac{1}{j\omega C'}$$
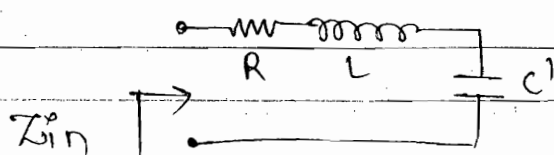
$$Z_{in} = R + j\omega L + \frac{1}{j\omega C'} \quad \text{--- series RLC CRT}$$



$$1. \omega_0 = \frac{1}{\sqrt{LC}}$$

$$= 4470 \text{ rad/sec}$$


$$2. Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= 22.4$$

$$3. \Delta\omega = \frac{\omega_0}{Q_0} = \frac{R}{L} = 199.55 \text{ rad/sec}$$

$$4. \omega_2 \approx \omega_0 + \frac{1}{2} \Delta\omega = 4569.775$$
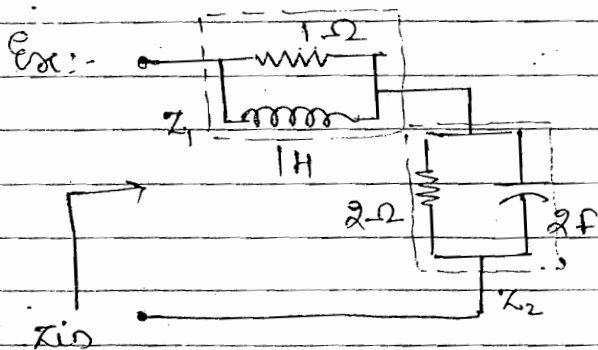
$$\omega_1 \approx \omega_0 + \frac{1}{2} \Delta\omega = 4370.225$$



To find ω_0

$$Z_{in} = Z_1 + Z_2$$

$X_C = \frac{1}{j\omega C}$

$$\text{where } Z_1 = \frac{R \times j\omega L}{R + j\omega L} = \frac{j\omega}{1 + j\omega}$$

$$Z_2 = \frac{R \times \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$$


$$Z_1 = \frac{j\omega}{1 + j\omega} \times \frac{1 - j\omega}{1 - j\omega} = \frac{j\omega + \omega^2}{1 + \omega^2}$$

$$Z_2 = \frac{2}{1 + j\omega 4} \times \frac{1 - 4j\omega}{1 - 4j\omega} = \frac{2 - j\omega 8}{1 + 16\omega^2}$$

at $\omega = \omega_0$ j terms = 0 so;

$$\frac{\omega_0}{1 + \omega_0^2} - \frac{j\omega_0 8}{1 + 16\omega_0^2} = 0$$
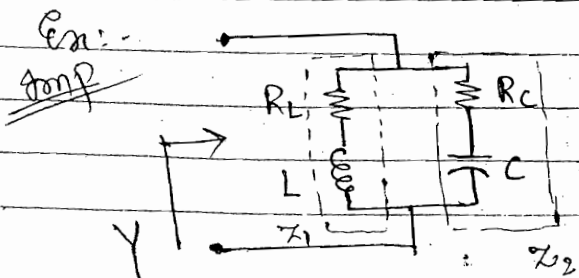
$$\omega_0 = \sqrt{\frac{7}{8}} \text{ rad/sec}$$



To find ω_0

$$Y_{in} = Y_1 + Y_2$$

$$X_L = j\omega L \quad X_C = \frac{1}{j\omega C}$$

$$Y_{in} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{R_L + jX_L} + \frac{1}{R_C - jX_C}$$

$$= \frac{R_L - jX_L}{R_L^2 + X_L^2} + \frac{R_C + jX_C}{R_C^2 + X_C^2}$$

at $\omega = \omega_0$; j^0 terms = 0

$$\Rightarrow \frac{-jX_L}{R_L^2 + X_L^2} + \frac{jX_C}{R_C^2 + X_C^2} = 0$$

$$\Rightarrow -X_L R_C^2 - X_L X_C^2 + X_C R_L^2 + X_C X_L^2 = 0$$

$$\Rightarrow -\omega_0 L R_C^2 - \omega_0 L \frac{1}{\omega_0^2 C^2} + \frac{1}{\omega_0 C} R_L^2 + \frac{1}{\omega_0 C} j\omega_0^2 L^2 = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_C^2 - L/C}} \quad \text{freq. of Resonance.}$$

• $Z_{in} = () + j() = 0$ at $\omega = \omega_0$

$Y_{in} = () + j() = 0$ at $\omega = \omega_0$


case 1 :- $R_L = 0$

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{L/C}{4LC - R_C^2}}$$

To make the result +ve


$$\frac{L}{C} - R_C^2 > 0$$

$$R_C < \sqrt{\frac{L}{C}} \quad \text{condition of Resonance}$$

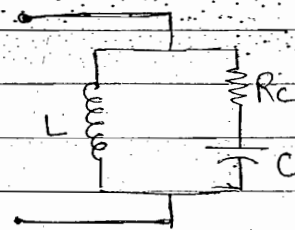

case 2 :- $R_C = 0$
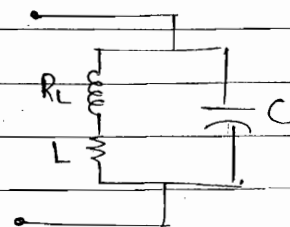
$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{1 - R_L^2 C}{L}}$$




For true Resonance $1 - \frac{R_L^2 C}{L} > 0$

$$R_L < \sqrt{\frac{L}{C}} \quad \dots \text{condition for Resonance}$$


case 3 :- $R_L = R_C = R$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

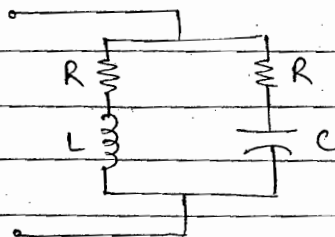

case 4: $R_L = R_C = 0$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

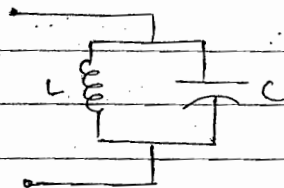

NOTE :- The frequency of Resonance does not depend upon the type of connection b/w L and C. Therefore the frequency of Resonance Remain same wheather L & C are connected in series or in parallel

~~Imp~~ case 5 :- $R_L = R_C = \sqrt{\frac{L}{C}}$

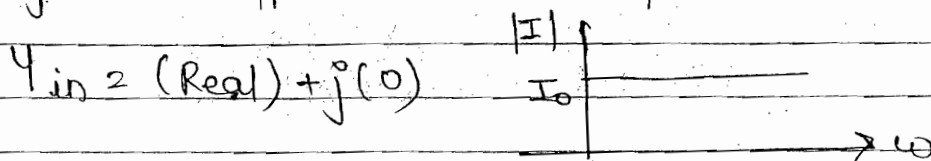Current is independent to any value of frequency.
Ap voltage and Ap current are in phase.




NOTE :- For the specified value of R_L & R_C , The imaginary part of the Ap Impedance is always zero and have only the real part. Therefore irrespective of

frequency of operation Input voltage and I/p current are always in phase.

↳ Therefore the current drawn by the N/w from I/p voltage source is always constant irrespective of the frequency of operation. No specific frequency of resonance occurs and the given ckt is resonating at all frequencies for the specified value of R_L and R_C

Chapter-7

(1) $V_{max} = 50V$

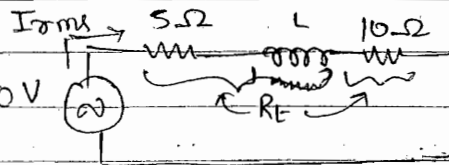

$$V_{rms} = \frac{50}{\sqrt{2}} = 35.35V$$

$$P_s = 10W = I_{rms}^2 \cdot 5 \Rightarrow I_{rms} = \sqrt{2}$$

$$p.f = \cos \theta = \frac{R_T}{|Z|} = \frac{I_{rms} \cdot R_T}{I_{rms} |Z|} \equiv \frac{V_{rms}}{V_{rms}}$$

$$= \frac{\sqrt{2} \times (5+10)}{35.35} = \frac{\sqrt{2} \times 15}{35.35} = 0.6$$

$$(2) V = 200 \sin(2000t + 50^\circ)$$

$$= 200 \sin(2000t + 90^\circ - 90^\circ + 50^\circ)$$

-40

$$= 200 \cos(2000t - 40^\circ)$$

$$i = 4 \cos(2000t + 13.2^\circ)$$

leading $\Rightarrow$ capacitive

i leads V

↳ capacitive

→ R, C elements

→ R, L, C where $X_C > X_L$

$$Q.8 \quad 1/Z(s) = Y(s) = \frac{s^2 + 0.5s + 100}{s s} = \frac{s}{s} + \frac{0.5}{s} + \frac{200}{s}$$

$$\equiv Y_1 + Y_2 + Y_3$$



$$\equiv sC_1 + \frac{1}{R_2} + \frac{1}{sL_3}$$

Beoz. it's admittance

$$C_1 = \frac{1}{5} F$$

$$R_2 = 10 \Omega$$

$$L_3 = \frac{1}{20} H$$

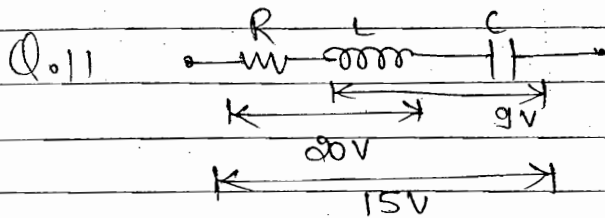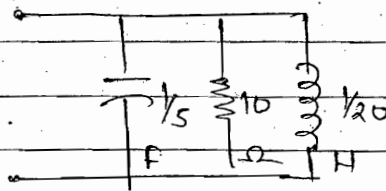

$$V_R + V_L = 20$$


wrong Bcoz R, L are not in phase, having the phase shift of 90°

$$\sqrt{V_R^2 + V_L^2} = 20 \quad \text{--- (1)}$$

$$V_L^2 - V_C^2 = 9 \quad \text{--- (2)}$$

$$V_L = 9 + V_C$$
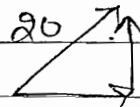
$$\sqrt{V_R^2 + (V_L - V_C)^2} = 15 \quad \text{--- (3)}$$



$$V_R = 400 - V_L^2 = 400 - (9 + V_C)^2$$

$$V_C = 7V \quad \text{Ans}$$

✓ why we don't write $V_C - V_L$

$$Z = R + jX_L - jX_C = R + j(X_L - X_C)$$

$$V = ZI$$

$$= IR + j(IX_L - IX_C) = V_R + j(V_L - V_C)$$

Q.13 Series RLC CRT

Given $R = 20 \Omega$ $\theta = -45^\circ$

$$V_L = 2V_C$$

$$IX_L = 2IX_C$$

$$X_L = 2X_C$$

$$I = \frac{V}{Z} = \frac{V}{R + j(X_L - X_C)}$$

$$\theta = \tan^{-1} \frac{X_L - X_C}{R} = -45^\circ$$

$$\frac{X_L - X_C}{R} = 1$$

$$X_L - \frac{1}{2}X_L = R$$


$$X_L = 2R = 2 \times 20$$

$$= 40 \Omega \quad \text{Ans}$$

Q.19

$$V_s = \sin \omega t$$

$$\omega_0 = 2$$

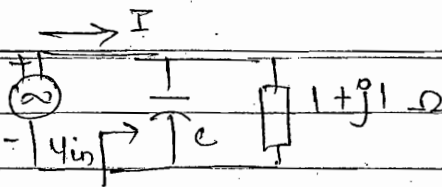

V_s & I in phase

$\Rightarrow$ circuit is in resonance at $\omega_0 = 2$


$$Y_{in} = Y_1 + Y_2 = j\omega_0 C + \frac{1}{1+j1} \times \frac{(1-j1)}{(1-j1)}$$

$$= j2C + \frac{1-j1}{1+1} = j2C + \frac{1}{2} - j\left(\frac{1}{2}\right)$$

at resonance the j terms become zero.

$$2C - \frac{1}{2} = 0 \Rightarrow C = \frac{1}{4} \text{ F Aug}$$

Q.21

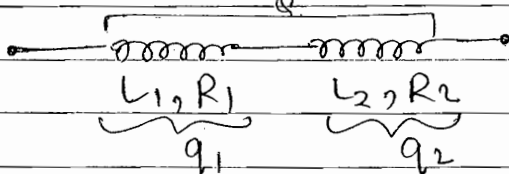

Resonance condition will not occur bcoz capacitor is not present.

$$q_1 = \frac{L_1 \omega}{R_1}$$

$$q_2 = \frac{\omega L_2}{R_2}$$

Here ω = freq. of operation.

= Supply freq.


= self resonating freq.

freq. at which resonance condition occurs

$$Q = \frac{\omega L_{eq}}{R_{eq}} = \frac{1}{R_1 + R_2} \left[\frac{\omega L_1 \times R_1}{R_1} + \frac{\omega L_2 \times R_2}{R_2} \right]$$

$$= \frac{1}{R_1 + R_2} [q_1 R_1 + q_2 R_2]$$

Q.14

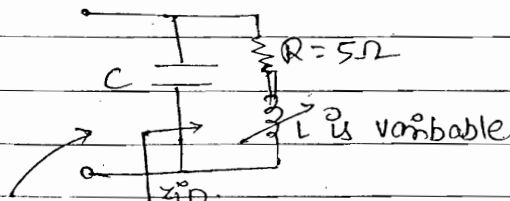

$$Z_{in} = (-jX_C) \times (R + jX_L) = -jX_C + R + jX_L$$

freq. of a/p voltage is fixed

$$= \frac{(-jX_c)(R+jX_L)}{R+j(X_L-X_c)} \times \frac{R-j(X_L-X_c)}{R-j(X_L-X_c)}$$

$$= (\text{Real}) + j(\text{Imaginary})$$

$= 0^j$ at resonance.

$$X_L = \frac{1}{2} \left[X_c \pm \sqrt{X_c^2 - 4R^2} \right]$$

$$\downarrow$$

$$X_c^2 < 4R^2$$

$X_L = \text{complex}$
Not possible

Because $X_L \rightarrow \text{Real}$
in $j \cdot X_L$

$$\downarrow$$

$$X_c^2 = 4R^2$$


one Resonance
occurs.
possible

$$\downarrow$$

$$X_c^2 > 4R^2$$

for two Resonance
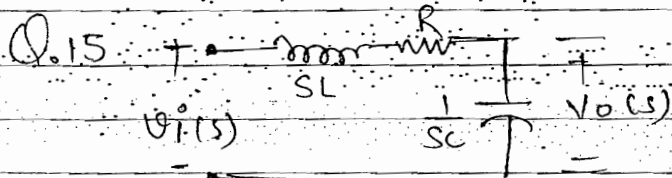
$$X_c > 2R ; \Rightarrow X_c > 2 \times 5 ; \boxed{X_c > 10 \Omega}$$



$$\frac{V_o(s)}{V_i(s)} = H(s) = \frac{1/Y_{sc}}{sL + R + 1/Y_{sc}} = \frac{1}{s^2 LC + sRC + 1}$$

$$= \frac{Y_{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\text{denominator} = s^2 + s \frac{R}{L} + \frac{1}{LC}$$

$$= s^2 + 2\delta\omega_n s + \omega_n^2$$

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$2\delta\omega_n = \frac{R}{L}$$

$$\delta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

RLC are not in parallel Bcos:- $V_{in} = V_o$

$$H(s) = T_o F = \frac{V_o}{V_{in}} = 1$$

Q.15. $\delta = \frac{R}{2} \sqrt{\frac{C}{L}}$

for NO oscillation $\delta \geq 1$

$$\frac{R}{2} \sqrt{\frac{C}{L}} \geq 1$$


$$R \geq 2 \sqrt{\frac{L}{C}}$$

Q.12 $2\delta\omega_n = \frac{R}{L} = \Delta\omega$
 $\omega_n = \frac{1}{\sqrt{LC}}$
 $Q_o = \frac{\omega_o}{\Delta\omega}$

$$H(s) = \frac{10^6}{s^2 + 20s + 10^6}$$

$$Q_o = \frac{10^3}{20} = 50 \text{ Ans.}$$

Parallel R-L-C ckt-

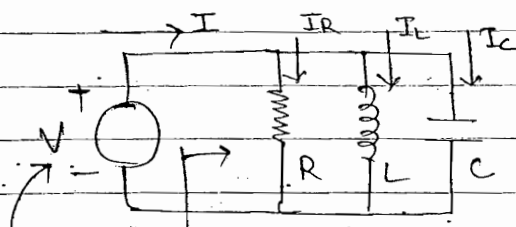

$$Y_{in} = Y_1 + Y_2 + Y_3$$

Sinusoidal source

(Variable frequency)

----- Parallel Resonance.

$$Y_{in} = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

$$= \frac{1}{R} + j\left[\omega C - \frac{1}{\omega L}\right]$$

at $\omega = \omega_o$ j term = 0

$$\omega_o C - \frac{1}{\omega_o L} = 0$$

$$\omega_o = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

at $\omega = \omega_o$

$$Y_{in} = \frac{1}{R} \text{ minimum}$$

$$Z_o = R \text{ maximum}$$

$$I_o = V \cdot Y_o \text{ minimum}$$

at $\omega = \omega_o$

$$|I_L| = |I_C|$$

I are out of phase By 180° so that the ^{net} current drawn By L & C component is zero.



$$Y_{in} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

→ $\omega = \omega_0$; Resistive

→ $\omega > \omega_0$; Capacitive

→ $\omega < \omega_0$; Inductive

frequency Response

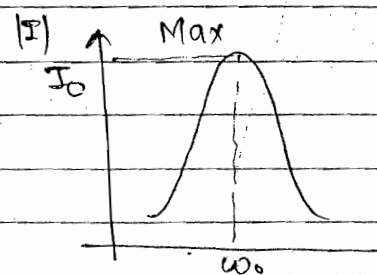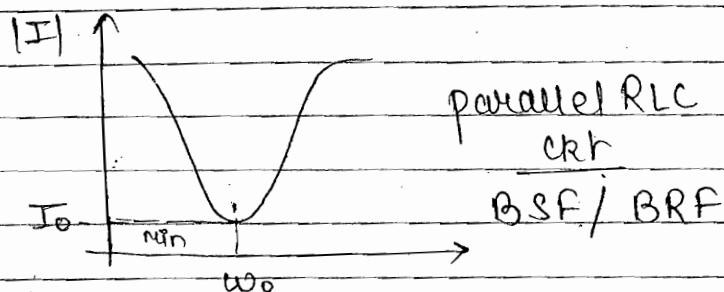

BSF → Band stop filter

BRF → Band Rejection filter

Imp

Features :-

- (1) At resonance the imaginary part of the Z_{in} Admittance is zero.
- (2) At resonance the N/w has only resistive part, Z_{in} Admittance is minimum, Z_{in} voltage and current are in phase so that the p.f. is unity.
- (3) At resonance current drawn by the N/w has minimum value so that any parallel RLC N/w behaves as a Band stop filter or a Band reject filter.
- (4) At resonance the current through the inductor and capacitor are equal in magnitude and are phase shifted by 180° . So that the net current through LC combination has zero value.
- (5) The N/w behaves differently at various frequencies.

of operation.

- (a) at ω_0 the N/w is resistive ; p.f = unity
- (b) above ω_0 the N/w is capacitive ; p.f = leading
- (c) below ω_0 the N/w is inductive ; p.f = lagging

(6) The quality factor represents the current amplification factor and for any tuned N/w the quality factor must have a high value. Therefore, at a specific frequency of resonance it must have low B.W.

• Quality Factor :-

$$Q_0 = \frac{|I_L|}{I_0} = \frac{|I_C|}{I_0}$$

$$\Rightarrow |I_L| = \frac{V}{j\omega L} = \frac{V}{\omega L} ; |I_C| = \frac{V}{1/j\omega C} = \omega C V$$

$$\Rightarrow I_0 = \frac{V}{R}$$

$$Q_0 = \frac{V}{\omega L} \cdot \frac{R}{V} ; Q_0 = \frac{\omega C V}{1/R}$$

$$Q_0 = \frac{R}{\omega_0 L} = \omega_0 C R = R \sqrt{\frac{C}{L}}$$

General Results :-

- (1) $\Delta \omega = \omega_2 - \omega_1$
- (2) $Q_0 = \omega_0 / \Delta \omega$
- (3) $\omega_0 = \sqrt{\omega_1 \omega_2}$
- (4) $\omega_2 \approx \omega_0 + \frac{1}{2} \Delta \omega$
- (5) $\omega_1 \approx \omega_0 - \frac{1}{2} \Delta \omega$

• Bandwidth :-

$$\Delta \omega = \frac{\omega_0}{Q_0} = \frac{1/\sqrt{LC}}{R\sqrt{C/L}} \therefore Q_0 = \frac{\omega_0}{\Delta \omega}$$


$$\Delta \omega = \frac{1}{RC}$$

$Q_0 \uparrow \rightarrow \Delta \omega \downarrow \rightarrow \begin{cases} R \uparrow \\ C \uparrow \end{cases}$... not advisable
(due to power losses)

✓ $\Delta \omega = \frac{1}{RC}$ parallel RLCckt ; $\Delta \omega = \frac{R}{L}$ series RLCckt


⊙ EFFECT OF MUTUAL INDUCTANCE (coupled ckt)

Case 1:

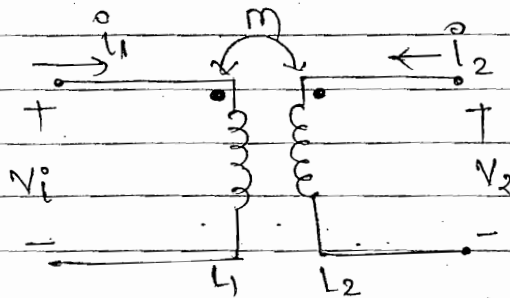

Current is entering to Dot

Case 2:

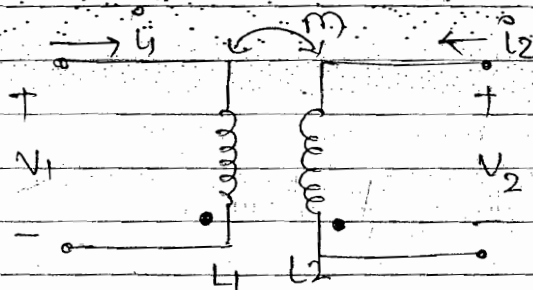


Current is leaving to Dot

→ When Both current entering or leaving the dot
Mutual inductance takes +ve

- Effect of M is +ve E_{ind} is additive case 1, 2

Physical Meaning of dot → sense of wdg (same) in above cases either clockwise or anticlockwise.


case 3 :-

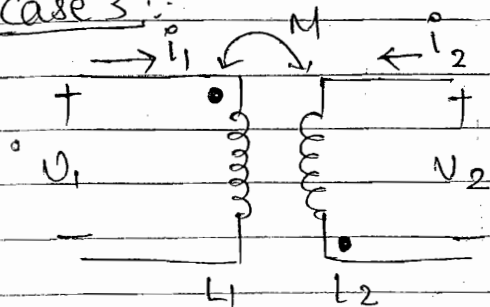

current entering
to dot

current leaving
to dot

case 4 :-

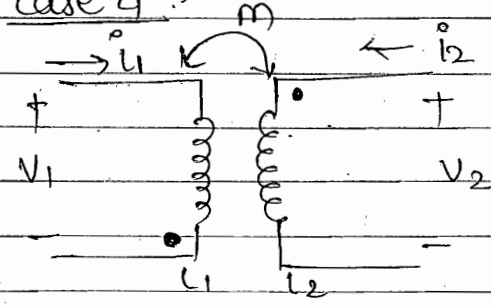

current leaving
to dot

current entering
to dot

Physical Meaning :- In above cases (3,4) if one way is clockwise other way will anti-clockwise

• Effect of Mutual is -ve E_{ind} is Subtractive case 3,4

$$\begin{aligned} V_1(t) &= L_1 \frac{di_1(t)}{dt} \pm M \frac{di_2(t)}{dt} \\ V_2(t) &= L_2 \frac{di_2(t)}{dt} \pm M \frac{di_1(t)}{dt} \end{aligned} \quad \left. \begin{array}{l} \text{--- in time domain} \\ \text{--- for non-sinu-} \\ \text{--- soidal excitatn.} \end{array} \right\}$$

$$\begin{aligned} V_1(s) &= sL_1 I_1(s) \pm sM I_2(s) \\ V_2(s) &= sL_2 I_2(s) \pm sM I_1(s) \end{aligned} \quad \left. \begin{array}{l} \text{--- in s-domain} \\ \text{--- assuming zero} \\ \text{--- I.E.s} \end{array} \right\}$$

$$\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} sL_1 & \pm sM \\ \pm sM & sL_2 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & \pm j\omega M \\ \pm j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

above Matrix is --- for sinusoidal excitation
--- using phasors $s = j\omega$

NOTE :- (1) Effect of Mutual inductance is consider whenever two inductors are placed physically closed to each other

- (2) When the current flows in first conductor, there is some magnetic field therefore some magnetic flux. Part of this magnetic flux will link with second inductor. Due to rate of change of magnetic flux and due to Faraday's law of electromagnetic induction, some emf is induced b/w the two terminals of the second inductor. The polarity of this induced voltage may be +ve or -ve and depends upon the dot convention. Therefore depends upon the relative sense of wdg of the two inductor.
- Then all the KVL equations are modified.

• Factors affecting the mutual inductance

1. M

2. K ... Coefficient of coupling [show closeness of two inductor]

$$K = \frac{M}{\sqrt{L_1 L_2}} ; M = K \sqrt{L_1 L_2}$$

Case 1: $K = 1$; $M = \sqrt{L_1 L_2}$... Critical coupling
such ckt. ... critically coupled ckt

Case 2: $K < 1$; $M < \sqrt{L_1 L_2}$... loose coupling
such ckt. ... under coupled ckt


Case 3: TURNS RATIO :-

$$\frac{V_2}{V_1} = \frac{n_2}{n_1}$$

$$\frac{I_2}{I_1} = \frac{n_1}{n_2}$$


Ex :- case 1 :-

No mutual

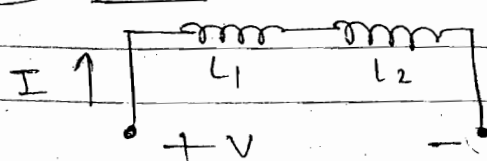

$$L_{eq} = L_1 + L_2$$

case 2:-

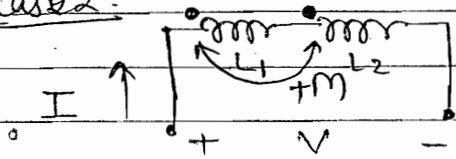


$$V = j\omega L_1 I + j\omega L_2 I + j\omega M I + j\omega M I$$

$$\frac{V}{I} = Z_{eq} = j\omega (L_1 + L_2 + 2M)$$

$$L_{eq} = L_1 + L_2 + 2M$$


case 3:-

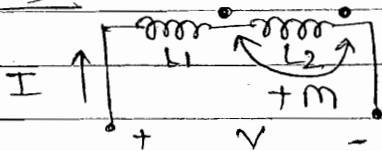

$$L_{eq} = L_1 + L_2 + 2M$$

→ Net inductance ↑
By factor 2M

case 4:-

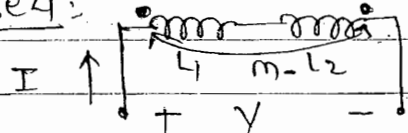


$$V = j\omega L_1 I + j\omega L_2 I - j\omega M I - j\omega M I$$

$$L_{eq} = L_1 + L_2 - 2M$$


→ Net inductance ↓
By factor 2M

case 5:-

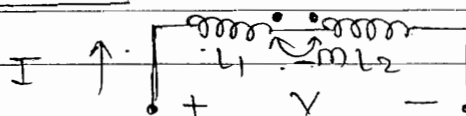

$$L_{eq} = L_1 + L_2 - 2M$$

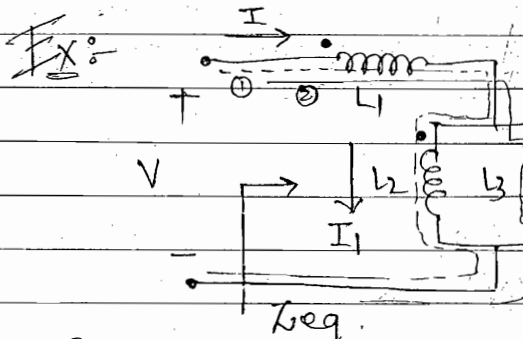Find $\frac{V}{I} = Z_{eq} = j\omega L_{eq}$ To find L_{eq}



$$L_1 = L_2 = L_3 = 10H$$

$$M_{12} = M_{21} = 1H$$

$$M_{13} = M_{31} = 2H$$

$$M_{23} = M_{32} = 3H$$

To find L_{eq}

Solution: $Z_{eq} = \frac{V}{I} = j\omega L_{eq}$

KVL loop (I):

$$V = j\omega L_1 I + j\omega L_2 I_1 + j\omega M_{21} I_1 - j\omega M_{31} (I - I_1) + j\omega M_{12} I - j\omega M_{32} (I - I_1)$$

$M_{21} \rightarrow$ Read like:- Mutual Inductance in Inductor 2 due to Inductor 1

Due to Inductor L_1 , so leave I_1 and write according to L_2 & L_3 .

$$V = j\omega(L_1 - M_{31} + M_{12} - M_{32})I + j\omega(L_2 + M_{21} + M_{31} + M_{32})I_1 \quad \text{--- (1)}$$


KVL Loop (2) :-

$$V = j\omega L_1 I + j\omega L_3 (I - I_1) + j\omega M_{12} I_1 - j\omega M_{31} (I - I_1) - j\omega M_{13} I - j\omega M_{23} I_1$$


$$V = j\omega I (L_1 + L_3 - M_{31} - M_{13}) + j\omega I_1 (-L_3 + M_{21} + M_{31} - M_{23})$$

Eliminate I_1 , find $\frac{V}{I} = X_{eq} = j\omega L_{eq} \quad ; L_{eq} = ?$

Ex

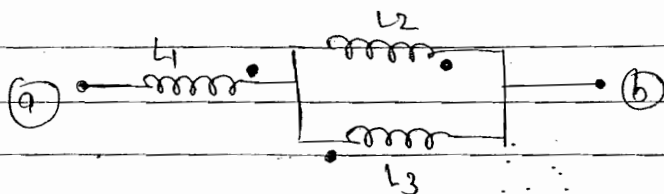

Chapter 4

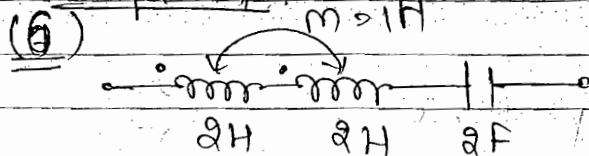


$$f_0 = \frac{1}{2\pi \sqrt{L_{eq} C}} \quad \text{Hz}$$

$L_1 + L_2 + 2M$

$$f_0 = \frac{1}{2 \times 3.14 \sqrt{12}} = \frac{1}{4\pi\sqrt{3}} \text{ Hz} = \frac{1}{2+2+2} = \frac{1}{6} \text{ Hz}$$

Chap. 1

Q.15

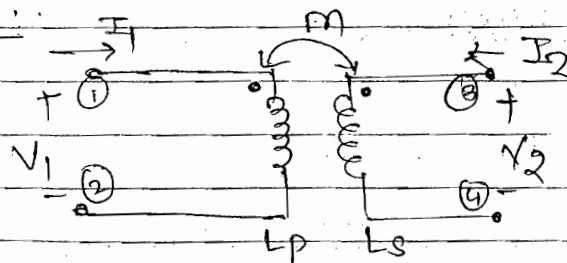

$$K = \frac{M}{\sqrt{L_p L_s}} \quad \leftarrow 2H$$

case 1:- $3-4 \Rightarrow O.C$

So $I_2 = 0$

$$\frac{V_1}{I_1} = Z_{eq} = j\omega L_{eq} = j\omega 4 \quad \text{--- (1)}$$

$$V_1 = j\omega L_p I_1 + j\omega M I_2$$

$$= j\omega L_p I_1 + 0 \quad \text{--- (2)}$$

$$\frac{V_1}{I_1} \Rightarrow j\omega L_p = j\omega 4$$

$$L_p = 4 H$$

case 2:- $3-4 \Rightarrow S.C$

So $V_2 = 0$

$$V_1 = j\omega L_p I_1 + j\omega M I_2 \quad \text{--- (3)}$$

$$V_2 = 0 = j\omega L_s I_2 + j\omega M I_1 \quad \text{--- (4)}$$

$$\frac{V_1}{I_1} = j\omega L_p = Z_{eq} = j\omega 3 \quad \text{--- (5)}$$


$$K = \frac{M}{\sqrt{L_p L_s}} = \frac{\sqrt{2}}{\sqrt{4 \times 2}} = 0.5$$

(K < 1) under-coupled circ.

• Network Functions :-

used to represent any type of Network Mathematically.

case 1: One port Networks:-

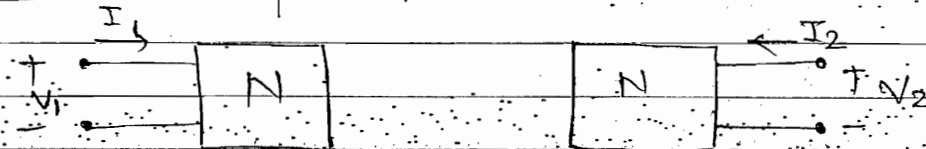

• $Z_{11} = \frac{V_1}{I_1}$ --- DRIVING POINT INPUT IMPEDANCE FUNCTION.

• $Y_{11} = \frac{I_1}{V_1}$ --- DRIVING POINT INPUT ADMITTANCE FUNCTION


→ for series element impedance finding is convenient
→ for parallel element admittance finding is convenient

• $Z_{22} = \frac{V_2}{I_2}$ --- DRIVING POINT OUTPUT IMPEDANCE FUNCTION

• $Y_{22} = \frac{I_2}{V_2}$ --- DRIVING POINT OUTPUT ADMITTANCE FUNCTION

- $Z_{11}, Z_{22}, Y_{11}, Y_{22} \rightarrow$ Driving point impedance function
↑
↑
Impedance
Admittance

Case 2: Two port Networks

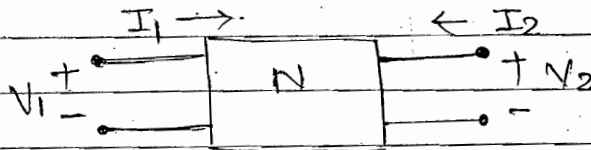

- 1) Driving point impedance function:-

$$Z_{11} = \frac{V_1}{I_1} ; Z_{22} = \frac{V_2}{I_2}$$

$$Y_{11} = \frac{I_1}{V_1} ; Y_{22} = \frac{I_2}{V_2}$$

- 2) Transfer impedance function (Ratio):-

$$Z_{12} = \frac{V_1}{I_2} ; Z_{21} = \frac{V_2}{I_1}$$

- 3) Transfer admittance Ratio:-

$$Y_{12} = \frac{I_1}{V_2} ; Y_{21} = \frac{I_2}{V_1}$$

- 4) Transfer Voltage Ratio:-

$$G_{12} = \frac{V_1}{V_2} ; G_{21} = \frac{V_2}{V_1}$$

- 5) Transfer Current Ratio:-

$$\alpha_{12} = \frac{I_1}{I_2} ; \alpha_{21} = \frac{I_2}{I_1}$$

Network Function $F(s)$

$$Z_{11}, Z_{22}$$

$$Y_{11}, Y_{22}$$


Driving pt impedance function

$$Z_{12}, Z_{21}, Y_{12}, Y_{21},$$

$$G_{12}, G_{21}, \alpha_{12}, \alpha_{21}$$

transfer function

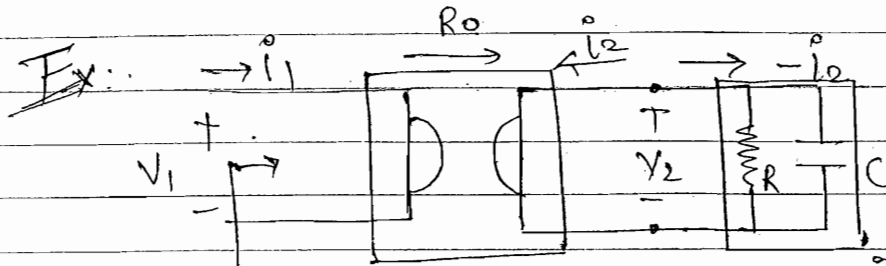NOTE: (1) for the driving point immittance function all the poles and zeros lie in left half of the complex s -plane. For Transfer function all the poles still lie in LHP whereas some of the zeros may also lie in RHP (left half plane)



$$Z_{in} = Z_{11} = \frac{V_1}{I_1} = ?$$

$$Z = R \times \frac{1}{sC} = \frac{R}{1 + Rsc}$$

$$V_1 = R_o i_2 \quad \text{--- (1)} \quad ; \quad V_2 = -R_o i_1 \quad \text{--- (2)}$$

$$V_2 = -i_2 Z = -i_2 \frac{R}{1 + Rsc} \quad \text{--- (3)}$$

eqn (2) & (3) $-R_o i_1 = -i_2 \frac{R}{1 + Rsc} \quad ; \quad i_2 = \frac{R_o i_1 (1 + Rsc)}{R}$



$$V_1 = \frac{R_o^2 (1 + Rsc)}{R} i_1$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{R_o^2 (1 + Rsc)}{R} = \underbrace{\frac{R_o^2}{R}}_{Z_1} + \underbrace{\frac{R_o^2 sc}{R}}_{Z_2}$$

$$Z_{in} = Z_1 + Z_2$$

$$= R_{eq} + s L_{eq}$$
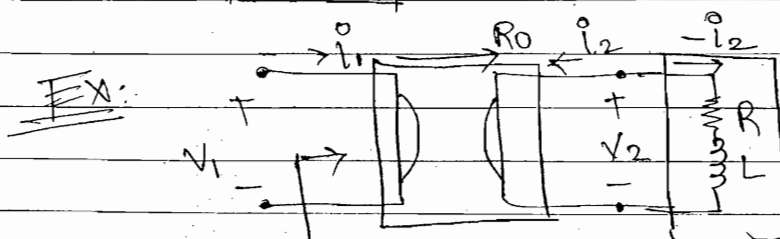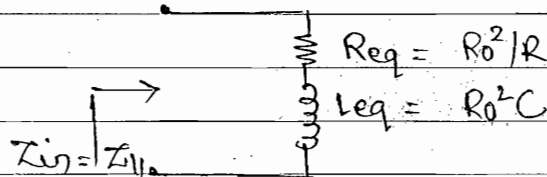
$$R_{eq} = \frac{R_o^2}{R} \quad ; \quad L_{eq} = R_o^2 C$$



$$Z = R + sL$$

$$Z_{in} = Z_{11} = \frac{V_1}{I_1}$$

Solution:- $V_1 = R_0 i_2$ — (1) ; $V_2 = -R_0 i_1$ — (2)
 $V_2 = -i_2 (R + sL)$ — (3)



$i_2 = \frac{R_0}{R + sL} i_1$ $V_1 = \frac{R_0^2}{R + sL} i_1$

$\therefore i_2 = -\frac{V_2}{R + sL}$ $\therefore V = R_0 i_2$
 $\therefore V_2 = -R_0 i_1$ $\therefore i_2 = \frac{-R_0 i_1}{R + sL}$

$\boxed{\frac{V_1}{i_1} = \frac{R_0^2}{R + sL}} = \frac{1}{Y_{11}} = \frac{1}{Y_{in}}$

$Y_{in} = \frac{R + sL}{R_0^2} = \frac{R}{R_0^2} + \frac{sL}{R_0^2}$
 $Y_{in} = Y_1 + Y_2$

$= \frac{1}{R_{eq}} + C_{eq}$

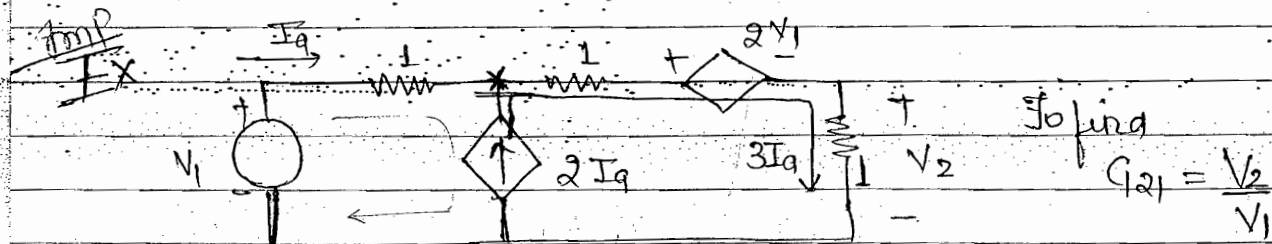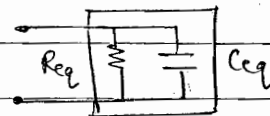

Cannot apply KVL eqn across X becoz voltage across $\uparrow 2Iq$ we don't know (arbitrary voltage)

So KVI

$\uparrow V_1 + 1 \times Iq + 1 \times 3Iq + 2V_1 + 1 \times 3Iq = 0$

$+V_1 = -7Iq$ — (1)

$V_2 = 1 \times 3Iq$ — (2)


$\frac{V_2}{V_1} = G_{21} = -\frac{3}{7}$ Ans.

Select that loop which does not contain any current source

Chap-5

Q.3 Convent:-

To find $\alpha_{21} = \frac{I_2}{I_1}$

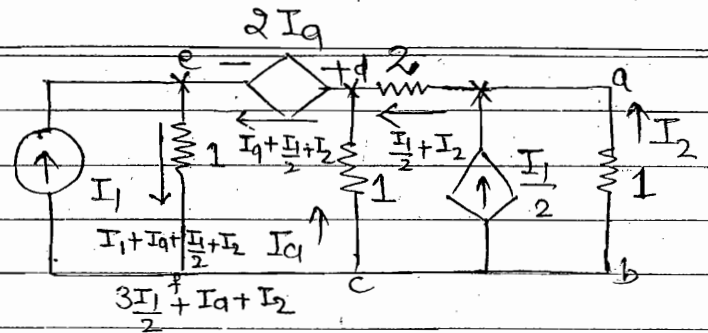

KVL loop ① b a d c b.

$$\Rightarrow I_2 + 2\left(\frac{I_1 + I_2}{2}\right) - I_a = 0$$

$$\Rightarrow I_a = I_2 + 2\left(\frac{I_1 + I_2}{2}\right) = 3I_2 + I_1 \quad \text{--- (1)}$$

KVL loop ② d e f c d

$$\Rightarrow I_a + 2I_a + 1 \cdot (I_1 + I_a + I_1/2 + I_2) = 0$$

$$\Rightarrow 4I_a + 3/2 I_1 + I_2 = 0 \quad \text{--- (2)}$$

put (1) in (2). $4[3I_2 + I_1] + \frac{3}{2} I_1 + I_2 = 0$

$$\Rightarrow 12I_2 + 4I_1 + 3/2 I_1 + I_2 = 0$$

$$\Rightarrow 13I_2 + 11/2 I_1 = 0$$

$$\alpha_{21} = \frac{I_2}{I_1} = -\frac{11}{26} \quad \text{Ans.}$$

Q For any N/w in particular N/w function is specified as follows. Find the pole-zero pattern and explain the physical significance of poles and zero.

Solution

$$F(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)} \quad \begin{matrix} \text{Numerator poly} \\ \text{Denominator poly} \end{matrix}$$

Z_{11}, Z_{22}

Z_{12}, Z_{21}

Y_{11}, Y_{22}

Y_{12}, Y_{21}

C_{12}, C_{21}

α_{12}, α_{21}

For Zeros:- Num poly = 0 ; $F(s) = 0$; $s = -1, -3$

For poles:- Deno. poly = 0 ; $F(s) = \infty$; $s = 0, -2, -4$

----- Zeros & poles
----- Singularities
----- Natural freq
(Below Imag. part is zero)


----- Complex frequencies
(cm general)

• Pole $\rightarrow$ control shape of response

• coefficient $\rightarrow$ amplitude
(zero)

$$f(t) = (A + Be^{-2t} + Ce^{-4t})u(t)$$

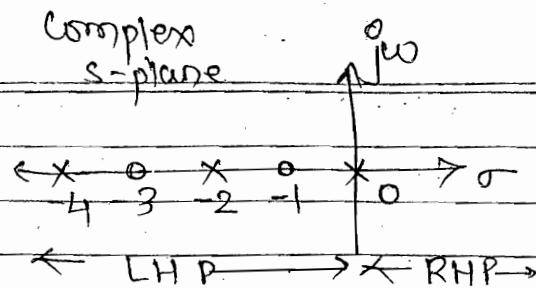Coefficient of partial fraction expansion
Residues of poles.



• Some imp. points:-

(1) The zeros represent the complex frequencies at which the numerator polynomial of the N/w functⁿ become zero. Therefore at these frequencies the N/w functⁿ become zero. The zeros control the magnitude of the response of a given N/w.

(2) The poles represent the complex frequencies where the denominator poly. of a N/w functⁿ become zero. Therefore at these freq. the N/w functⁿ become ∞ . The poles control the nature or shape of response of a given N/w.

$\Rightarrow$ Therefore these control overall stability of any given N/w.

(3) For a stable N/w $\rightarrow$ (a) No pole should exist in RHP


(b) No multiple poles should exist along the jw axis including the origin.

(4) In any N/w functⁿ the no. of zeros and no. of poles are always equal.


(5) The locatⁿ of poles and zeros control the type of elements contain in any given N/w.

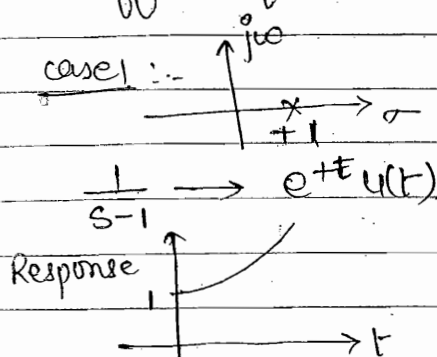(6) For immittance functⁿ all the poles and zeros lie in LHP. For transfer functⁿ all the poles lie in LHP whereas some of the zeros may also lie in RHP.


Effect of location of poles on the Response of N/w.




--- unstable N/w.

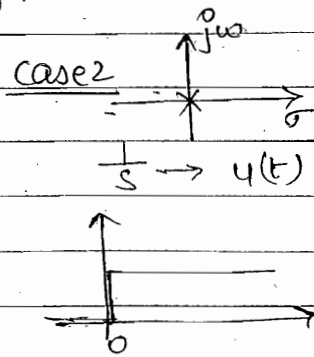

--- Ideal/lossless or stable sys.

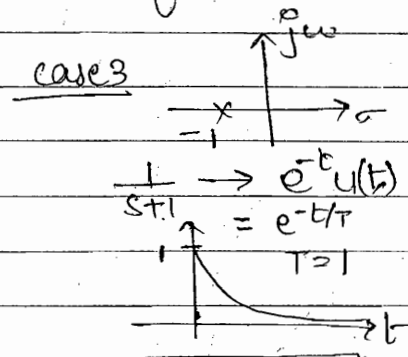


RC/RL CRK
 stable

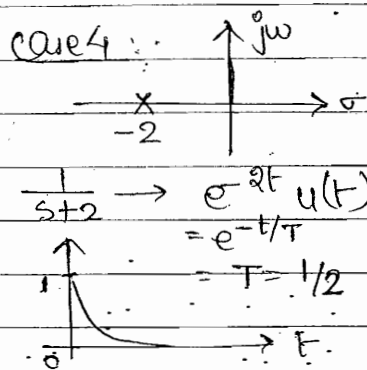


→ decay at faster rate

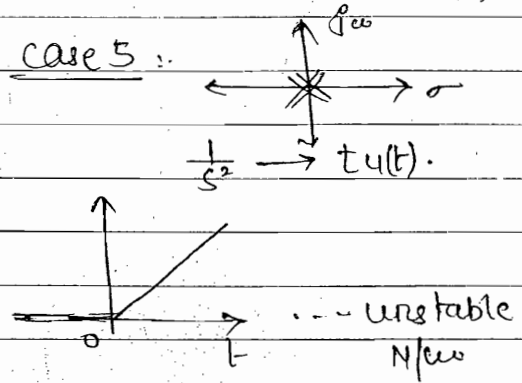• This N/w is More stable than case 3 N/w
 • pole shift to L.H.S. (stable)




- For stable N/w :- (1) The pole should not exist in RHP (case 1)
- (2) Multiple poles should not exist at the origin (case 5)
- When any pole lies along the -ve real axis the response is exponential decaying and the rate of decay depends upon the exact locatⁿ of the pole along the -ve real axis.
- When the pole is shifted away from the origin along the -ve. real axis, the rate of decay of the exponential response increases, the time constant ↓ and the N/w will become more stable.

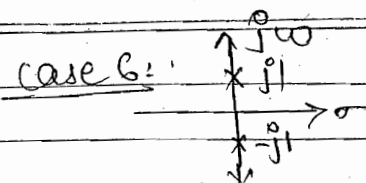


$$\frac{1}{(s-j1)(s+j1)} = \frac{1}{s^2+1} = \frac{q}{s^2+q^2}$$

$$\Rightarrow \sin t$$

$\omega = 1 \text{ rad/sec}$

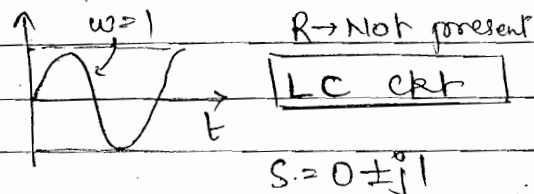



case 7:

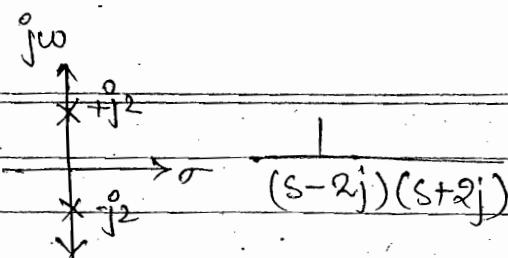

$$\frac{1}{(s-j2)(s+j2)} = \frac{1}{s^2+4} = \frac{1}{2} \cdot \frac{2}{s^2+2^2}$$


$$= \frac{1}{2} \sin 2t$$

$\omega = 2 \text{ rad/sec}$

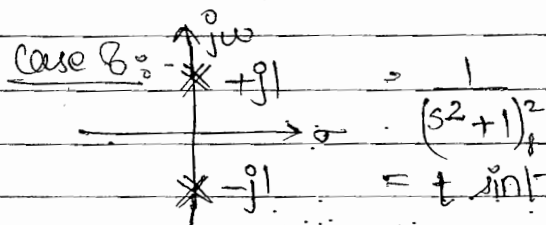
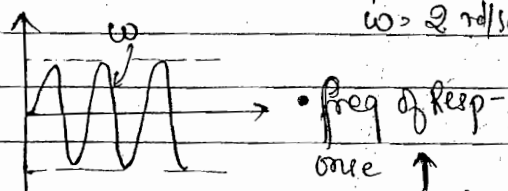


$$\frac{1}{(s^2+1)^2}$$

$$= t \sin t$$

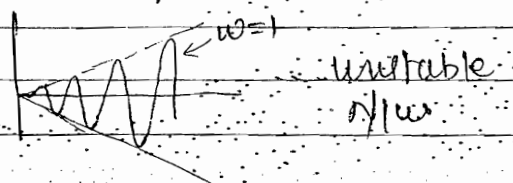


case 9

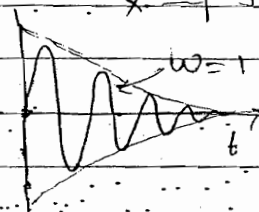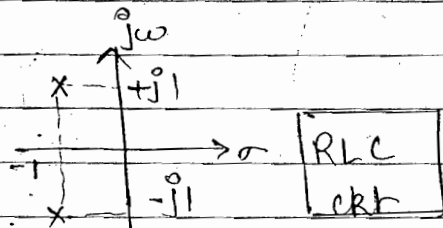

- When a pair of poles lie along the $j\omega$ axis then the response is oscillatory in nature whose freq. is controlled by the exact locatⁿ of poles along the $j\omega$ axis.
- If the poles are shifted away from the origin along the $j\omega$ axis then the freq. of sinusoidal response ↑.
- When the poles are complex conjugate in nature having both real and imaginary part in LHP. Then the response is oscillatory in nature whose amplitude ↓ exponentially.
- For stable LTI Multiple pole must not exist along the $j\omega$ axis.

Chap. 5

Q.18

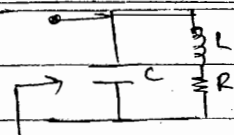

Given $Z(0) = 1$; zero $\rightarrow -1 = s$

poles: $s_1, s_2 \rightarrow \frac{1}{2} \pm j\sqrt{3}/2$

$Z(s)$

To find R, L, C .

$$Z(s) = \frac{(R + sL)(1/sC)}{(1/s) + (sL + R)} = \frac{R + sL}{1 + s^2 LC + sCR}$$

$$= \frac{L(s + R/L)}{LC[s^2 + sR/L + 1/LC]}$$

$$Z(0) = \frac{R + 0}{1 + 0 + 0} = 1 \Rightarrow R = 1 \Omega$$

✓ zero: $s = -R/L = -1$ $L = 1 H$

✓ poles: $s_1, s_2 = \frac{-R/L \pm \sqrt{(R/L)^2 - 4 \times 1/LC}}{2} = \frac{1}{2} \pm j\frac{\sqrt{3}}{2}$

$$= \frac{-R/L \pm j\sqrt{1/LC - (R/2L)^2}}{2} \rightarrow \text{compare}$$

$$= -1/2 \pm j\sqrt{3}/2$$

$$\frac{1}{LC} - \left(\frac{R}{2L}\right)^2 = \frac{3}{4}$$


$$\frac{1}{LC} = \frac{3}{4} + \left(\frac{1}{2}\right)^2 = \frac{3+1}{4} = \frac{4}{4} = 1$$

$$C = 1 F$$

• Effect of variation of R in a series RLC circuit: -

$$s^2 + 2\alpha\omega_n s + \omega_n^2$$

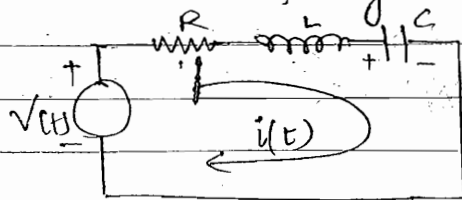$\rightarrow \delta \rightarrow$ vary only when R is varying in ckt: -



$$V(t) = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i dt$$

$$\frac{dV(t)}{dt} = R \frac{di(t)}{dt} + L \frac{d^2 i(t)}{dt^2} + \frac{1}{C} i(t)$$

Characteristic eqn in s-domain.

$$Rs I(s) + Ls^2 I(s) + \frac{1}{C} I(s) = 0$$

$$\Rightarrow R s + L s^2 + \frac{1}{C} = 0$$

$$\Rightarrow s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \quad \text{compare with } [s^2 + 2\delta\omega_n s + \omega_n^2]$$

$$\Rightarrow 2\delta\omega_n = \frac{R}{L} ; \omega = \frac{R}{2\sqrt{L}} ; \omega_n = \frac{1}{\sqrt{LC}}$$

damping coefficient natural freq.

$$s_1, s_2 = \frac{-2\delta\omega_n \pm \sqrt{(2\delta\omega_n)^2 - 4\omega_n^2}}{2}$$


$$s_1, s_2 = -\delta\omega_n \pm j\omega_n \sqrt{1-\delta^2}$$

$$\delta = \frac{R}{2\sqrt{\frac{L}{C}}} ; \omega_n = \frac{1}{\sqrt{LC}} ; \omega_d = \omega_n \sqrt{1-\delta^2}$$


POINTS:-

- Char. eqn represent the denominator poly. of any funⁿ.
- The roots of this eqn represent the poles of the N/w and control small stability of N/w.
- this eqn control the transient response of a given N/w for zero excitation.

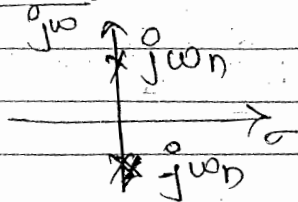Case 1. $\delta = 0 ; R = 0 ; s_1, s_2 = \pm j\omega_n$ - roots on Imag axis.




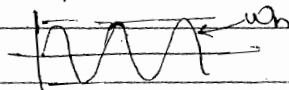
Response oscillatory with constant magnitude



undamped Response


Case 2:- ~~over damped~~ $\delta > 1 ; \delta = \frac{R}{2\sqrt{\frac{L}{C}}} ; R > 2\sqrt{\frac{L}{C}}$

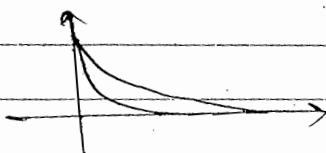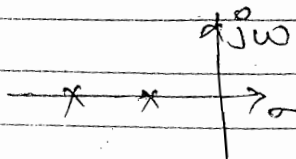s_1, s_2 :- ~~unequal~~ - unequal roots → Imag axis lie along
-a ± b -ve real axis




over damped Response

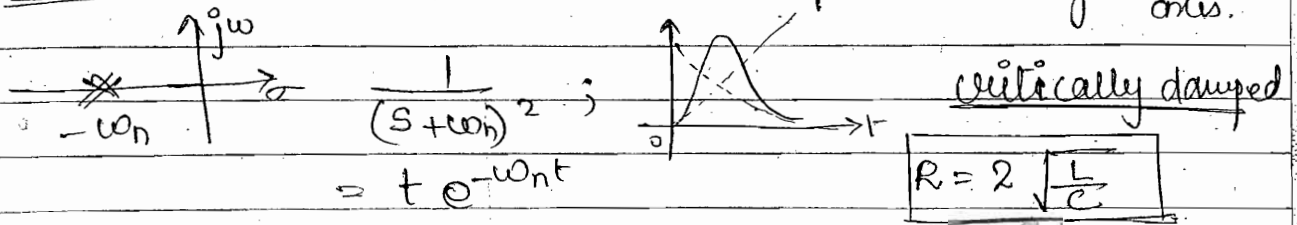Case 3 $\delta = 1$; $s_1, s_2 = -\omega_n$ - multiple roots along -ve Real axis.



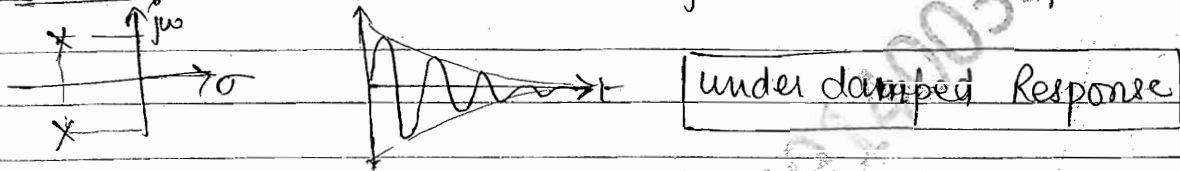
Case 4 $\delta < 1$; $s_1, s_2 = -a' \pm j b'$ roots are complex conjugate



• For NO Oscillation Condition $\delta \geq 1$

• 2 PORT N/W PARAMETERS

another way to represent the any 2-port N/w Mathematically

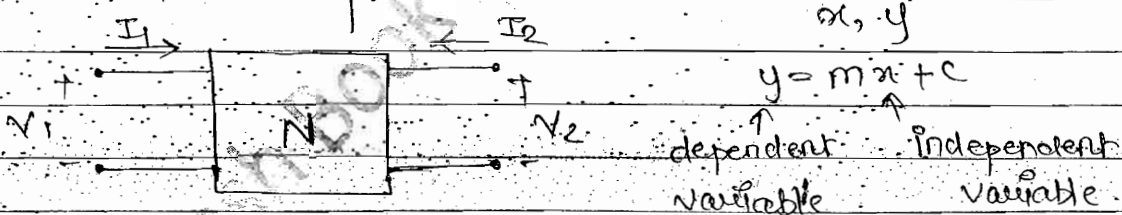

Case 1:- Z or impedance or O.C. parameters :-

$$\begin{cases} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \end{cases} \quad \begin{array}{l} \text{--- series} \\ \text{--- series} \end{array}$$

$$I_2 = 0$$

$$Z_{11} = \frac{V_1}{I_1} \Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Omega$$

$$I_1 = 0$$

$$Z_{12} = \frac{V_1}{I_2} \Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Omega$$

→ Network function

- $Z_{11}, Z_{12}, Z_{21}, Z_{22} \rightarrow$ Solve without any condition. (O.C, S.C)
- $z_{11}, z_{12}, z_{21}, z_{22} \rightarrow$ Solve without pre condition (O.C, S.C)

→ Network parameters

- (1) The Network functions are calculated without any pre condition whereas N/w parameter are calculated either By S.C or O.C the i/p or o/p port.
- (2) A single N/w functⁿ is sufficient to represent a particular N/w whereas all the four parameters are required simultaneously to represent the same N/w.

Case 2 :- Y parameter or S.C or admittance parameter.

$$\begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \end{cases} \quad \text{--- shunt}$$

$V_2 = 0$	$V_1 = 0$	i/p and o/p are short circuited $S \rightarrow \text{Siemens}$
$Y_{11} = \frac{I_1}{V_1} \quad S$	$Y_{12} = \frac{I_1}{V_2} \quad S$	
$Y_{21} = \frac{I_2}{V_1} \quad S$	$Y_{22} = \frac{I_2}{V_2} \quad S$	

Case 3: h or hybrid Parameter :-

$V_2 = 0$	$I_1 = 0$	series parallel. o/p $\rightarrow$ S.C i/p $\rightarrow$ O.C
$V_1 = h_{11} I_1 + h_{12} V_2$	$I_2 = h_{21} I_1 + h_{22} V_2$	
$h_{11} = \frac{V_1}{I_1} \quad \Omega$	$h_{12} = \frac{V_1}{V_2}$	
$h_{21} = \frac{I_2}{I_1}$	$h_{22} = \frac{I_2}{V_2} \quad S$	

Biasing $\rightarrow$ only for DC.
Model $\rightarrow$ ac.

Case 4. g parameter:

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

parallel
series.

$$I_2 = 0$$

$$V_1 = 0$$

$$g_{11} = \frac{I_1}{V_1} \text{ S}$$


$$g_{12} = \frac{I_1}{I_2}$$

d/p $\rightarrow$ S.C. o/p $\rightarrow$ O.C.

$$g_{21} = \frac{V_2}{V_1}$$

$$g_{22} = \frac{V_2}{I_1} \Omega$$

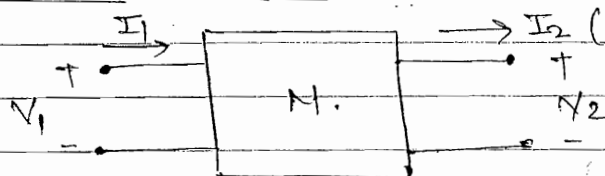Case 5: Transmission or T or ABCD parameters:-



$$\frac{I_2 = 0}{A = \frac{V_1}{V_2}}$$

$$\frac{V_2 = 0}{B = \frac{V_1}{I_2} \Omega}$$

$$V_1 = A V_2 + B I_2$$

$$I_1 = C V_2 + D I_2$$

$$C = \frac{I_1}{V_2} \text{ S}$$



$$D = \frac{I_1}{I_2}$$

$\rightarrow$ Change in Imp. will change only C, B parameters


ex: Imp. double $\Rightarrow B \rightarrow$ double, $C \Rightarrow 1/2$ Becz admittance

Interview question

Direction of I_2 :-

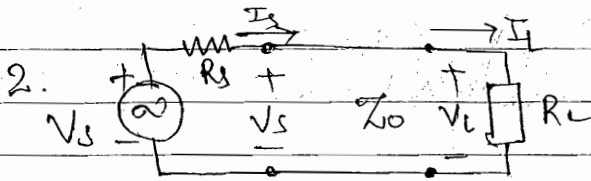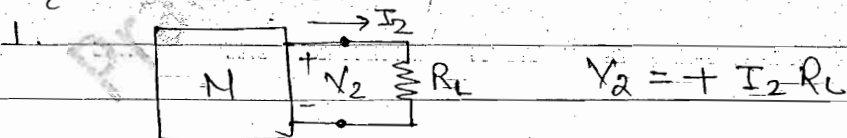

Transmission line

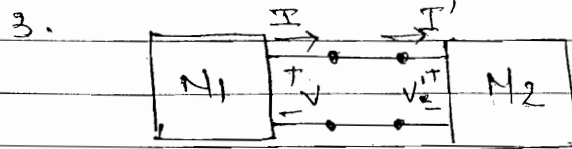

Cascading the N/ws.
(directⁿ of should in same for simplicity)

Imp

• Conditions for a Network to Be Reciprocal & Symmetrical:-

RECIPROCAL	SYMMETRICAL
• Z-parameter $z_{12} = z_{21}$	$z_{11} = z_{22}$
• Y-parameter $y_{12} = y_{21}$	$y_{11} = y_{22}$
• $\begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1$; $\Delta = 1$ $AD - BC = 1$	$A = D$
• $h_{12} = -h_{21}$	$\begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} = 1$; $\Delta_h = 1$ $h_{11}h_{22} - h_{12}h_{21} = 1$
• $g_{12} = -g_{21}$	$\begin{vmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{vmatrix} = 1$; $\Delta_g = 1$ $g_{11}g_{22} - g_{12}g_{21} = 1$

Q Calculate the parameters which are inverse of given set of parameter:-

Given : $[z]$ To find : $[y]$

Solution

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}^{-1}$$

$$= \frac{1}{\Delta_z} \begin{bmatrix} z_{22} & -z_{21} \\ -z_{12} & z_{11} \end{bmatrix}$$

So $y_{11} = \frac{z_{22}}{\Delta_z}$ $y_{12} = \frac{-z_{21}}{\Delta_z}$ $y_{21} = \frac{-z_{12}}{\Delta_z}$ $y_{22} = \frac{z_{11}}{\Delta_z}$

$$\Delta_z = z_{11} \times z_{22} - z_{12} z_{21}$$

Q Calculate the parameters by given set of parameter which are not inverse of it.

Given $[h]$ To find: $[z]$

$$h_{11} = 2 \quad h_{12} = -1 \quad h_{21} = 3 \quad h_{22} = -2$$

Solution:-

$$\begin{array}{l} h. \quad V_1 = h_{11} I_1 + h_{12} V_2 \\ \text{para.} \quad I_2 = h_{21} I_1 + h_{22} V_2 \end{array} \quad ; \quad \begin{array}{l} V_1 = 2 I_1 - V_2 \\ V_2 = 3 I_1 - 2 V_2 \end{array} \quad \left\| \begin{array}{l} \text{Substituting} \\ \Rightarrow V_2 = \frac{I_2 - 3 I_1}{2} \quad (1) \end{array} \right.$$

$$\begin{array}{l} z. \quad V_1 = z_{11} I_1 + z_{12} I_2 \\ \text{para.} \quad V_2 = z_{21} I_1 + z_{22} I_2 \end{array} \quad \Rightarrow \quad V_1 = \underbrace{\left(\frac{7}{2}\right)}_{z_{11}} I_1 + \underbrace{\left(-\frac{1}{2}\right)}_{z_{12}} I_2$$

$$\checkmark \text{ from eqn (1) } V_2 = \underbrace{\left(-\frac{3}{2}\right)}_{z_{21}} I_1 + \underbrace{\left(\frac{1}{2}\right)}_{z_{22}} I_2$$


$$[Z] = \begin{bmatrix} 7/2 & -1/2 \\ -3/2 & 1/2 \end{bmatrix} ; \Omega$$

✓ Compare $z_{11} \neq z_{22}$, $\frac{7}{2} \neq \frac{1}{2}$ — not symmetrical

Compare $[z_{12}, z_{21}]$, $z_{12} \neq z_{21}$, $-\frac{3}{2} \neq \frac{1}{2}$ — not reciprocal

$\Rightarrow$ By checking the symmetrical and reciprocal property from given set parameter — It is equal to calculated set of parameters (No need to solve for it like this)

Ex: LATTICE N/W

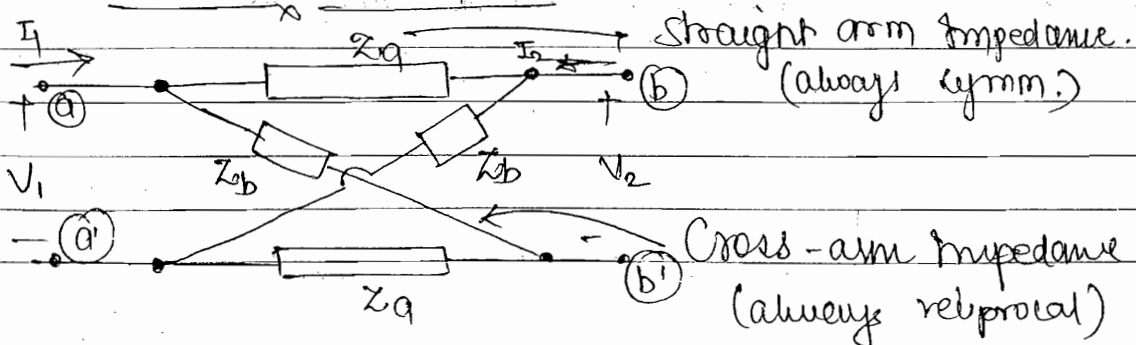


To find:- 1. $[Z]$ 2. Z_a, Z_b in terms of $[Z]$

Solution: $I_2 = 0$ $Z_{11} = \frac{V_1}{I_1}$; $Z_{21} = \frac{V_2}{I_1}$

1. A lattice Network is said to be symmetrical if the two straight arm impedances are equal i.e.
 $Z_{11} = Z_{22}$ — symmetrical type N/w. (N)

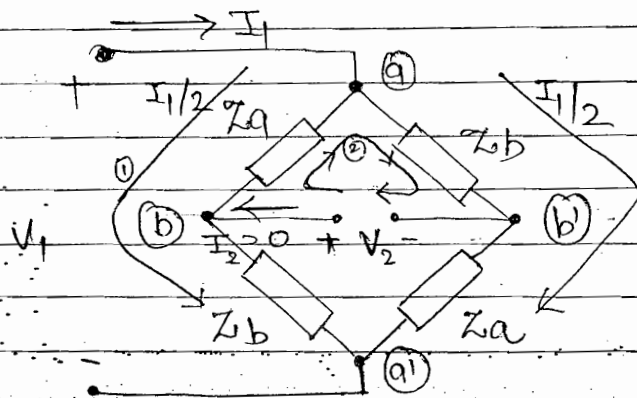2. A lattice N/w is said to be reciprocal if the two cross arm impedances are equal i.e.
 $Z_{12} = Z_{21}$ — reciprocal type N/w.



KVL equation:

$$\textcircled{1} \quad V_1 = \frac{I_1}{2} [Z_a + Z_b] \quad \textcircled{1}$$

$$\textcircled{2} \quad -V_2 - \frac{I_1}{2} Z_a + Z_b \frac{I_1}{2} = 0$$

$$V_2 = \frac{I_1}{2} [Z_b - Z_a] \quad \textcircled{2}$$

from eq ⁿ $\textcircled{1}$	$Z_{11} = \frac{V_1}{I_1} = \frac{Z_b + Z_a}{2}$	$= Z_{22}$
from eq ⁿ $\textcircled{2}$	$Z_{21} = \frac{V_2}{I_1} = \frac{[Z_b - Z_a]}{2}$	$= Z_{12}$


$$Z_a + Z_b = 2 Z_{11}$$

$$Z_b - Z_a = 2 Z_{12}$$

Add $\pm$ $2 Z_b = 2 Z_{11} + 2 Z_{12} \Rightarrow Z_b = Z_{11} + Z_{12}$

Subtract: $2 Z_a = 2 Z_{11} - 2 Z_{12} \Rightarrow Z_a = Z_{11} - Z_{12}$

series arm impedances.

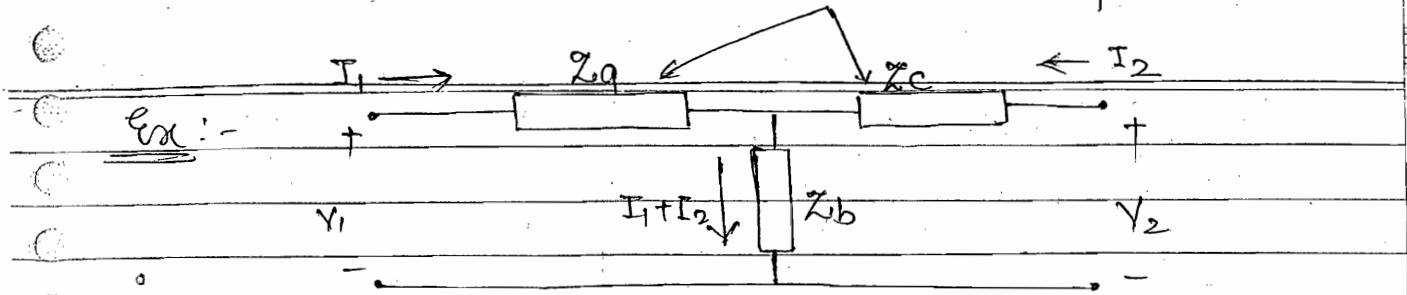

To find $[Z]$:-

T OR Y OR Star N/w

Solution

$$V_1 = [Z_a + Z_b] I_1 + [Z_b] I_2$$

$$V_2 = \underset{z_{21}}{[Z_b]} I_1 + \underset{z_{22}}{[Z_c + Z_b]} I_2$$

- N/w is ^{non} symmetrical ($z_{11} = z_{22}$) but reciprocal ($z_{12} = z_{21}$)

Imp pt

Any general T N/w is always a symmetrical reciprocal N/w but may not be symmetrical in nature. Such N/w may be symmetrical if the two series arm impedances Z_a and Z_c are equal.

$$[Z] = \begin{bmatrix} Z_a + Z_b & Z_b \\ Z_b & Z_b + Z_c \end{bmatrix}; \Delta Z$$


$$\begin{aligned} \Delta Z &= (Z_a + Z_b)(Z_b + Z_c) - Z_b^2 \\ &= Z_a Z_b + Z_a Z_c + Z_b Z_c \\ &= \sum Z_a Z_b = \sum Z_b Z_c = \sum Z_c Z_a \end{aligned}$$

$$y_{11} = \frac{1}{\Delta Z} = \frac{Z_b + Z_c}{\sum Z_a Z_b}, \quad y_{22} = \frac{1}{\Delta Z} = \frac{Z_a + Z_b}{\sum Z_a Z_b}$$

$$y_{12} = -\frac{z_{12}}{\Delta Z} = y_{21} = \frac{-Z_b}{\sum Z_a Z_b}$$

Ex Star Pie π OR Δ
Network

to find $[y]$.

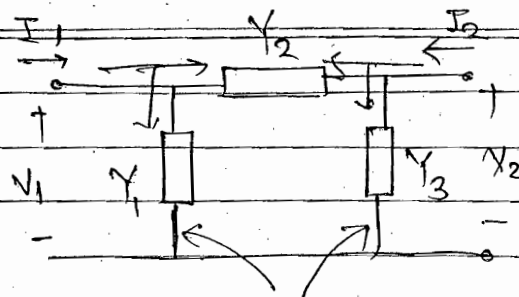

$$\begin{aligned} I_1 &= V_1 Y_1 + (V_1 - V_2) Y_2 \\ &= V_1 \underbrace{(Y_1 + Y_2)}_{y_{11}} + V_2 \underbrace{(-Y_2)}_{y_{12}} \end{aligned}$$

Shunt arm admittances

$$I_2 = (V_2 - V_1) Y_2 + V_2 Y_3 = V_2 \underbrace{(Y_2 + Y_3)}_{y_{22}} + \underbrace{(-Y_2)}_{y_{21}} V_1$$

$$[y] = \begin{bmatrix} Y_1 + Y_2 & -Y_2 \\ -Y_2 & Y_2 + Y_3 \end{bmatrix}$$

Imp pt


Any general π N/w is always a reciprocal N/w. But may not be symmetrical in nature. Such N/w may be symmetrical in nature if the two shunt arm admittances Y_1 & Y_3 are equal.

$$\begin{aligned} \Delta y &= (Y_1 + Y_2)(Y_2 + Y_3) - Y_2^2 \\ &= Y_1 Y_2 + Y_1 Y_3 + Y_2 Y_3 \\ &= \sum Y_1 Y_2 = \sum Y_1 Y_3 = \sum Y_2 Y_3 \end{aligned}$$

$$\begin{aligned} \bullet \quad z_{11} &= \frac{y_{22}}{\Delta y} = \frac{Y_2 + Y_3}{\sum Y_1 Y_2} & \bullet \quad z_{22} &= \frac{Y_1 + Y_2}{\sum Y_1 Y_2} = \frac{y_{11}}{\Delta y} \\ \bullet \quad z_{12} &= z_{21} = -\frac{y_{12}}{\Delta y} = \frac{Y_2}{\sum Y_1 Y_2} \end{aligned}$$

Chapter - 5

Q.4

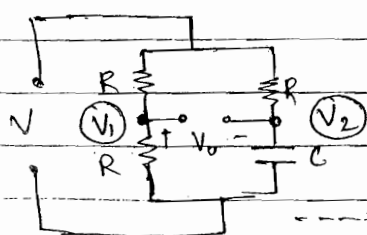

$$V_0 = V_1 - V_2$$

$$V_1 = V \cdot \frac{R}{R+R} = 10 \cdot \frac{R}{2R} = 5$$

all pass filter


$$V_2 = 10 \times \frac{V_{iwc}}{R + \frac{1}{j\omega C}}$$

$$N_o = 5 - \frac{1}{1+j\omega RC} \times 10 \times \frac{(1-j\omega RC)}{(1-j\omega RC)} = 5 - \frac{10}{1+j\omega RC}$$

$$= 5 - \frac{10(1-j\omega RC)}{1+R^2\omega^2 C^2}$$

$$= \frac{5 + 5j\omega RC - 10}{(1+j\omega RC)} = 5 \frac{-1+j\omega RC}{(1+j\omega RC)}$$

$$|V_o| = 5 \text{ V}$$

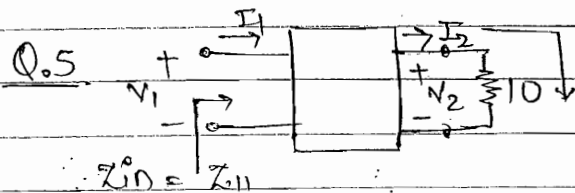

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 2 \\ 1 & 3 \end{bmatrix}$$

Solution

$$V_1 = A I_2 + B I_2 = V_2 + 2 I_2 \quad \text{--- (1)}$$

$$I_1 = C V_2 + D I_2 = V_2 + 3 I_2 \quad \text{--- (2)}$$


$$V_2 = 10 I_2 \quad \text{--- (3)}$$

put eqn (3) in (1) & (2)

$$V_1 = 12 I_2$$

$$I_1 = 13 I_2$$

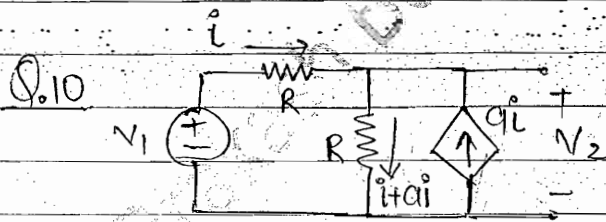
$$Z_{in} = \frac{V_1}{I_1} = \frac{12}{13} \Omega$$



$$V_1 = iR + R[i + a i] = iR + iR[1+a] \quad \text{--- (1)}$$

$$V_2 = [1+a]iR \quad \text{--- (2)}$$
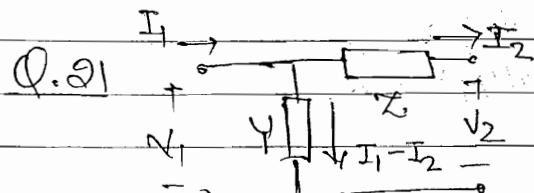
$$\frac{V_2}{V_1} = \frac{[1+a]iR}{iR[2+a]} = \frac{1+a}{2+a} \quad \text{Ans}$$



$$I_1 - I_2 = V_1 Y \quad \text{--- (1)}$$

$$V_1 = I_2 Z + V_2 \quad \text{--- (2)}$$

eqn (2)

$$V_1 = \underbrace{[1]}_A V_2 + \underbrace{[Z]}_B I_2$$

eqn (1)

$$I_1 - I_2 = [I_2 Z + V_2] Y, \quad I_1 = \underbrace{V_2 [Y]}_C + \underbrace{I_2 [ZY+1]}_D$$


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ Y & 1+YZ \end{bmatrix} \quad A$$

$A \neq D$, ~~Not~~ Neither symm, nor ~~is~~

$$AD - BC = 1 = 1(1+YZ) - YZ = 1 \quad (\text{reciprocal N/w})$$

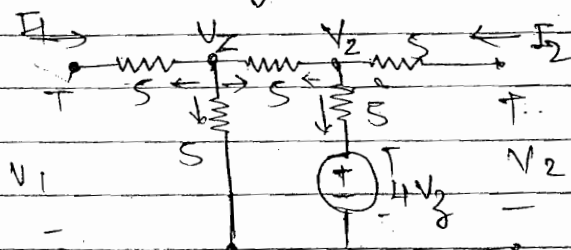Q.29 $Z_{11} = \frac{V_1}{I_1}$, $I_2 = 0$, $Z_{11} = \frac{V_1}{I_1}$

Both Z_{11} and Z_{22} are having equal value beoz load term, nal are open



Node V_2

$$\frac{V_2 - V_1}{5} + \frac{V_2}{5} + \frac{V_2 - V_2}{5} = 0$$

$$3V_2 = 20V_2 = V_1 + V_2 \quad \text{--- (1)}$$

Node V_1 $\frac{V_2 - V_2}{5} + \frac{V_2 - 4V_2}{5} = 0$

$$\Rightarrow 2V_2 - 5V_2 = 0 \quad \text{--- (2)} \quad V_2 = 5V_2$$

Left side $\Rightarrow \frac{V_1 - V_2}{5} = I_1 \quad \text{--- (3)}$

$$3V_2 = V_1 + 5V_2 \Rightarrow V_1 = 3V_2 - 5V_2 = \frac{V_2}{2}$$

Put in eqn (3) $\frac{\frac{V_2}{2} - V_2}{5} = I_1 \Rightarrow \frac{-V_2}{10} = I_1$

$$I_1 = -\frac{2V_1}{10}, \quad \frac{V_1}{I_1} = \frac{10}{-2} = -5 \quad \text{Ans}$$

Q.31 $Z_{11} = \frac{SLX(R_1+R_2)}{SL+(R_1+R_2)} = \frac{L(R_1+R_2)}{L} \frac{S}{S+9}$

$$n = \frac{R_1+R_2}{L}$$


Coefficient of S must Be 1.

$$Z_{22} = \frac{R_2 \times (R_1 + sL)}{R_2 + (R_1 + sL)} = \frac{s + R_1/L}{s + \frac{R_1 + R_2}{L}} \cdot \frac{R_2 L}{L} = R_2 \left(\frac{s+b}{s+a} \right)$$

Origin $\rightarrow$ near should be zero $\left\{ \begin{array}{l} s+2 \rightarrow \text{zero} \\ s+3 \rightarrow \text{pole} \end{array} \right.$

How the s.o.c and o.c are related to pole and zero. In
ex: $Z_{22} = \frac{V_2}{I_2}$ o/p port.

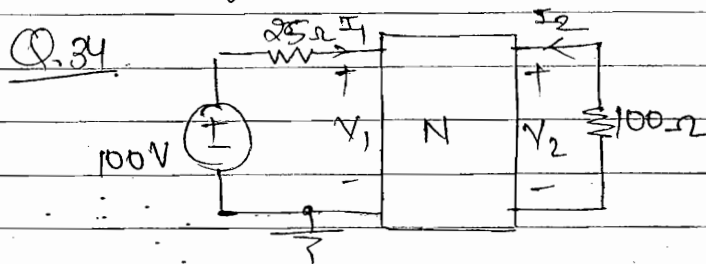If $V_2 = 0$ $Z_{22} = 0$ (zero) that mean o/p port is s.o.c
If $I_2 = 0$ $Z_{22} = \infty$ (pole) $\leftarrow$ o/p port is o.c.



To find $G_{21} = \frac{V_2}{V_1}$

Solution: $I_1 = 0.1 V_1 - 0.01 V_2$ — (1)

$I_2 = 0.01 V_1 + 0.1 V_2$ — (2)

$V_2 = -100 I_2$ — (3)

$V_1 = 25 I_1 + V$ — (4)


eqn (2) $V_2 = -100 I_2 = -100 [0.01 V_1 + 0.1 V_2]$
 $= -1 V_1 - 10 V_2$

$11 V_2 = -1 V_1$


$\therefore G_{21} = \frac{V_2}{V_1} = \frac{-1}{11} A_g$

Q.36. $V_1 = A V_2 + B I_2$

$A = \frac{V_1}{V_2} \Big|_{I_2=0}$

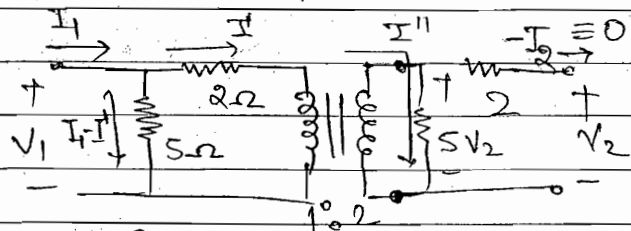

Transferring secondary to primary side

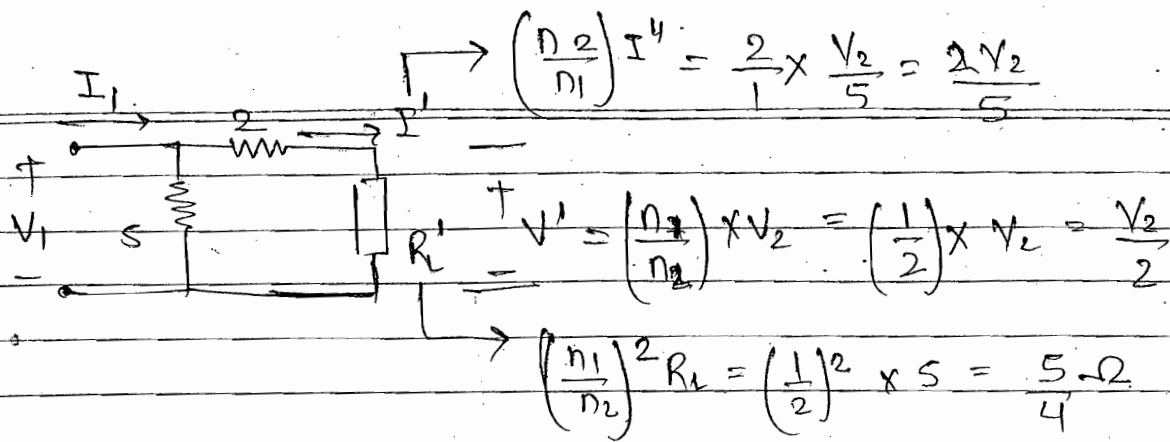


$$V_1 = 2I' + V'$$

$$= 2 \times \frac{2V_2}{5} + \frac{V_2}{2}$$

$$\therefore \frac{V_1}{V_2} = \frac{13}{10} \text{ A Ans}$$

Inter-Connection of Various 2-port Network

• case 1: Cascaded Networks

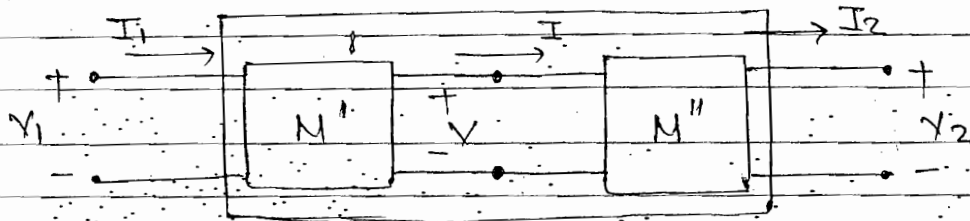

$$N': \begin{cases} V_1 = A'V + B'I \\ I_1 = C'V + D'I \end{cases}$$

$$N'': \begin{cases} V = A''V_2 + B''I_2 \\ I = C''V_2 + D''I_2 \end{cases}$$

Overall N/w:

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$


Substitute the V, I from N'' into V, I in N'
we get the V_1, I_1 in terms of V_2, I_2 .

$$\checkmark \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} A'' & B'' \\ C'' & D'' \end{bmatrix}$$

NOTE: When two N/w are connected in cascade

than the ABCD parameters of the individual N/w are multiplied to obtain overall ABCD parameters of the resulting N/w.

• Case 2: Series Network:

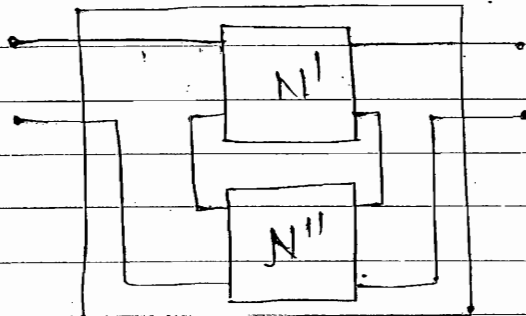


NOTE:- When two N/w are connected in series at the I/p and in series at O/p then the respective Z parameters of the two N/w are added to obtain overall Z parameters of the resultant N/w.

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z'_{11} + Z''_{11} & Z'_{12} + Z''_{12} \\ Z'_{21} + Z''_{21} & Z'_{22} + Z''_{22} \end{bmatrix}$$

$$\Rightarrow [Z] = [Z'] + [Z'']$$

• Case 3: Parallel Network:

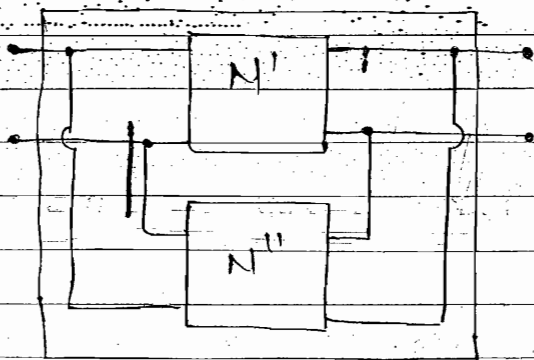


$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y'_{11} + Y''_{11} & Y'_{12} + Y''_{12} \\ Y'_{21} + Y''_{21} & Y'_{22} + Y''_{22} \end{bmatrix}$$

$$[Y] = [Y'] + [Y'']$$

NOTE:- When two N/w are connected in parallel at the I/p and in parallel at the O/p. Then respective Y parameters of the two N/w are added to obtain overall Y parameter of the resulting N/w.


Numerically:- ABCD and Y parameters are most imp.

case 4:- Series-Parallel Network

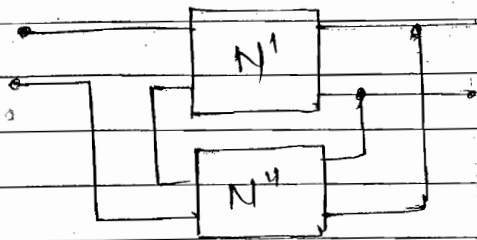


$$[h] = [h'] + [h'']$$

cases:- Parallel-Series Networks

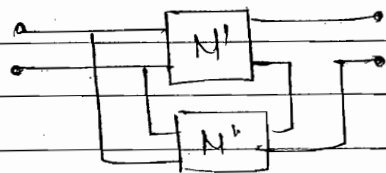

$$[g] = [g'] + [g'']$$

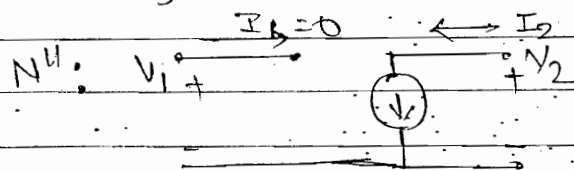Q.14. N' : $y_{11} = y_{22} = -y_{12} = -y_{21} = Y$



$V_2 = 0$	$V_1 = 0$
$y_{11} = \frac{I_1}{V_1} = 0$	$y_{12} = \frac{I_1}{V_2} = 0$
$y_{21} = \frac{I_2}{V_1}$	$y_{22} = \frac{I_2}{V_2}$


N' & N'' are connected in parallel

Overall parameters $y_{21} = y'_{21} + y''_{21}$

$$y_{21} = -Y + g$$

$$= \frac{gV_1}{V_1} = g$$

Q.1 parallel connection

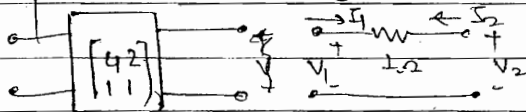

$$I_1 = -I_2 \quad \text{--- (1)}$$


$$V_1 = 1 \times I_1 + V_2$$

$$V_1 = I_1 + V_2 \quad \text{--- (2)}$$


$$\Rightarrow I_1 = [1] V_1 + [-1] V_2 ; I_2 = [-1] V_1 + [1] V_2$$


$$y = y' + y'' = \begin{bmatrix} 4 & 2 \\ 1 & 1 \end{bmatrix} + \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} = \begin{bmatrix} 5 & 1 \\ 0 & 2 \end{bmatrix} \quad \text{Ans}$$

- Whenever R is connected b/w i/p & o/p terminal. all parameters get modified.

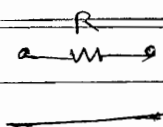Ex. ①  Same previous | find [Z]
Question.

As $\Delta Z = 0$; Z parameters donot exist.

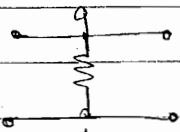
②  [y] ; [z] when o/p port is s.c., a, b also get s.c. so. $\Delta y = \infty$ 0
 $\therefore$ [y] parameters donot exist.

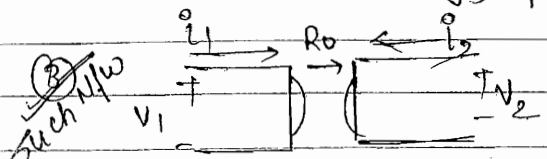Such N/w 

$$V_1 = R_0 i_2 = \underbrace{(0)}_{Z_{11}} i_1 + \underbrace{R_0}_{Z_{12}} i_2$$

$$V_2 = -R_0 i_1 = \underbrace{-R_0}_{Z_{21}} i_1 + \underbrace{(0)}_{Z_{22}} i_2$$


• Symmetrical N/w. $\Delta Z = R_0^2$; [Z] = $\begin{bmatrix} 0 & R_0 \\ -R_0 & 0 \end{bmatrix}$

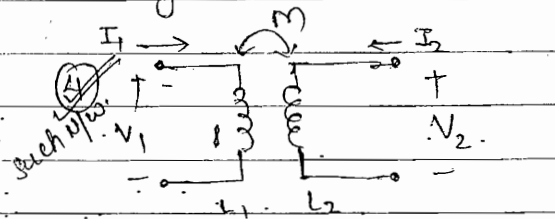
Such N/w 


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & \pm j\omega M \\ \pm j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


[Z]


Assume Sinusoidal excitatⁿ N/w is reciprocal. But NO. Symm.

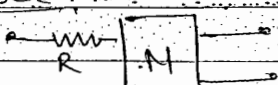Q. 29 case 1  Parameter affected: Z_{11} only

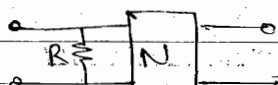case 2  Y_{11}

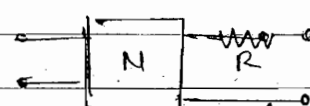case 3  Z_{22}

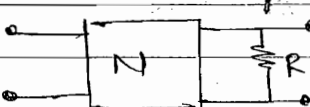
case 4  Y_{22}

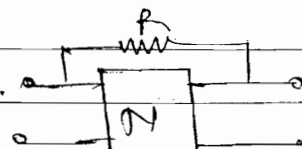case 5  $Y_{11}, Y_{21}, Y_{12}, Y_{22}$ all.

(as connected in parallel so. admittance)

freq. Selective Networks

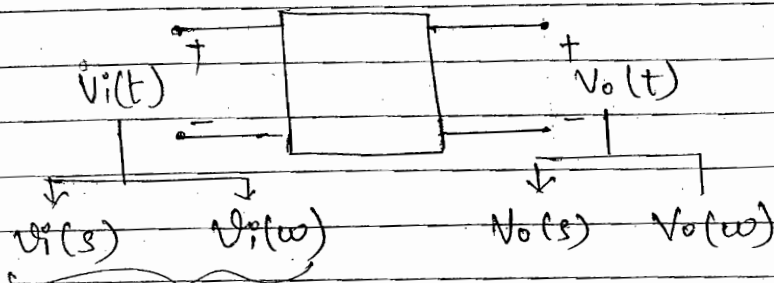- Amplitude $\rightarrow$ fixed, variable $\rightarrow$ frequency.




$$H(s) = \frac{V_o(s)}{V_i(s)} = A_v(s)$$

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = A_v(\omega)$$

fixed amplitude & variable freq.

- case 1: Low Pass filter (LPF)

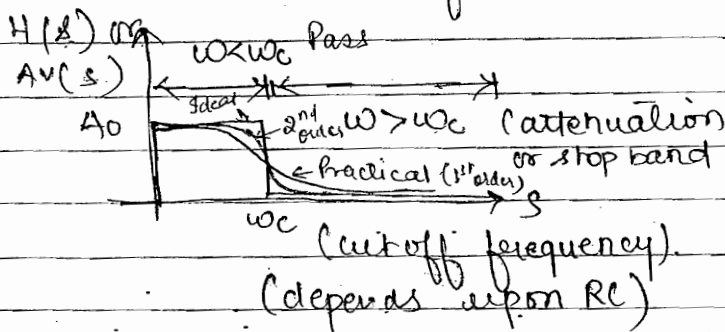

- capacitor means $\rightarrow$ determine the order. $\frac{1}{s}$

- one capacitor $\rightarrow$ 1st order (Blue colour)

- two cap. $\rightarrow$ 2nd order (Red colour)

$\uparrow$ cap. To achieve ideal charact.
 $\uparrow$ order


- gain $A_v(s)$ can be adjust By using op-amp.

$\Rightarrow$ Characteristic of a Practical filter


- The cut off frequency of any filter can be adjusted as per our requirement by suitably selecting the numerical values of R and C components.
- Any ideal filter has sharp cut off characteristic. A practical filter cannot have such sharp cut off characteristic. Since the freq. response of such filter is limited by its time constant. Therefore any practical filter has gradual cut off characteristic. These cut off characteristic may be approached to

these of ideal filter By increasing the order of the filter.
By increasing the no. of stages. which are being cascaded.
(3) The gain during a pass Band can be adjusted By including op. amp. along with a RC selection. Such filters are then called Active filter

Case 2: High pass filter (HPF)

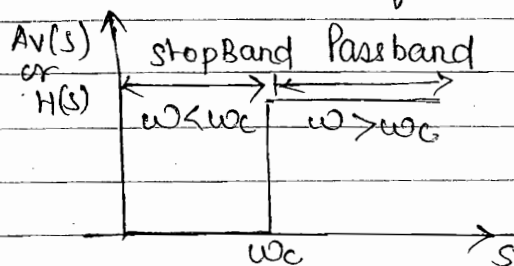


Case 3: Band Pass Filter (BPF)

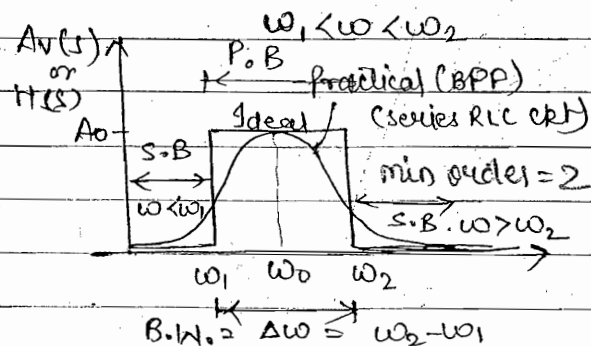

Case 4: BSF / BR

Band Stop / Band Rejection Filter

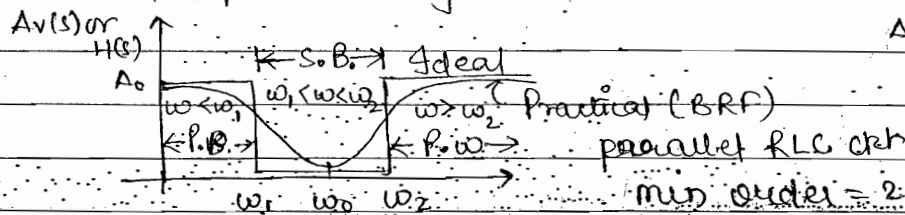


$$B.W. = \Delta\omega = \omega_2 - \omega_1 = 1/RC$$

$$\Delta f = 1/2\pi RC$$

$$B.W. = \Delta\omega = R/L \text{ rad/sec}$$

$$\Delta f = R/2\pi L \text{ Hz}$$

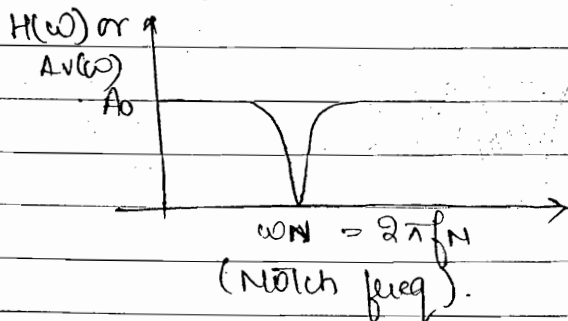Case 5: Notch Filter (special case of BRF)



→ only single frequency is rejected.

→ used in S/P of audio signal.


→ for Blocking 3rd harmonic.

⇒ A notch filter is a further special case of a Band stop filter where a single freq. called the notch freq is not


allow to enter the system.

- ✓ Such filter is used at the I/p of any audio system, where 50 Hz main freq. is not allowed to enter in the system to minimise the noise or distortion in the system.
- ✓ Such filter is also used at the I/p of any system, to minimise 3rd harmonic distortion.


case 6: APF (all pass filter)

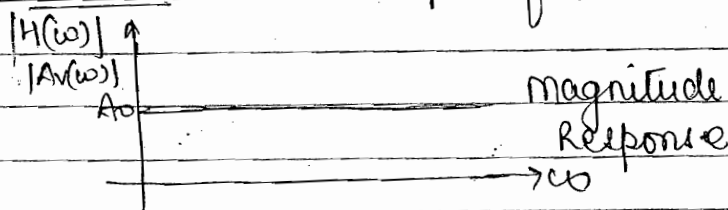

• If having RHS zero
→ surely → APF

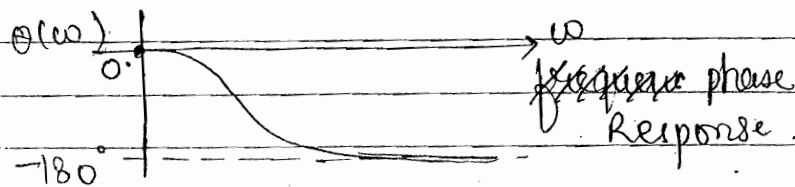


- ✓ Such filter passes all the freq. components with constant gain. But various freq. components are subjected to different amount of phase shift having a minimum value to 0° and maximum value of -180°.
- ✓ Such filter has all the zero in RHP and all the poles in LHP.
- ✓ Since any M/W the no. of zero and poles are equal. Then the no. of zero in RHP or no. of poles in LHP control the order of filter.

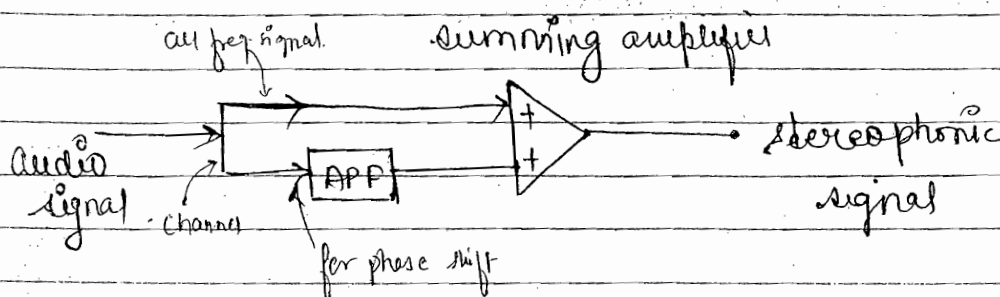

• An APF can be used to provide a stereophonic music signal.

Ex:- 1st Order LPF :-

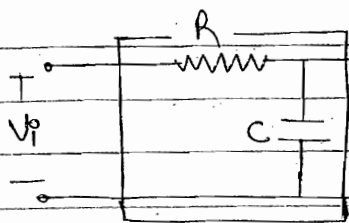(By adjusting the value of RC (time constant) same ckt can use as LPF and as integrator)



To find:

① $H(s) = T.O. = V_o(s) / V_i(s)$

② Cut off freq. ω_c

③ Zero-pole pattern

④ freq. resp. $H(s)$ Vs s

⑤ Amplitude Response $|H(\omega)|$ Vs ω .

Identificatn of filter.

shape wise No much diff. B/w Amplitude & freq. response



Solution ① $V_o(s) = H(s) = \frac{V_i(s)}{R + 1/s} = \frac{1}{1 + sRC} = \frac{1}{1 + \frac{s}{\omega_c}} \equiv H(s)$

② $\omega_c = \frac{1}{RC}$; $f_c = \frac{1}{2\pi RC}$

• cut off freq:- Where gain $\downarrow$ to value 0.707 or -3dB

③

pole zero-pattern

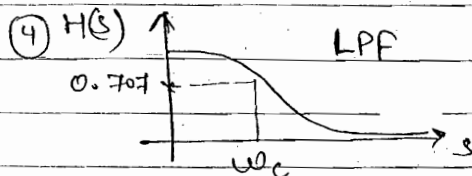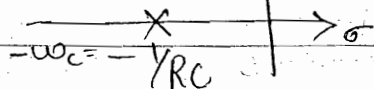

freq. Resp.

Resemble to LPF so it called LPF

or also $V_o(s) / V_i(s)$ Vs s .

⑤ put $s = j\omega$ $H(j\omega) = \frac{1}{1 + \frac{j\omega}{RC}}$; $|H(\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$; $H(\omega)$ Vs ω

1. $\omega \ll \omega_c$; $|H(\omega)| \approx 1$


2. $\omega \approx \omega_c$; $|H(\omega)| = \frac{1}{\sqrt{2}} \approx 0.707$

3. $\omega \gg \omega_c$; $|H(\omega)| \approx \frac{\omega_c}{\omega}$


method of sketching graph.

① Identification:

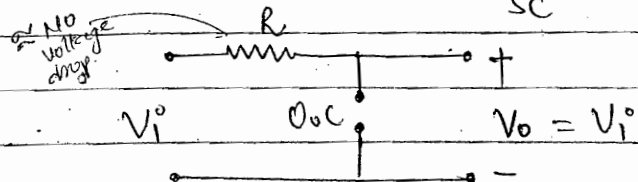
Case 1 $s=0$; $Z = \frac{1}{sC} = \infty$



magnitude response

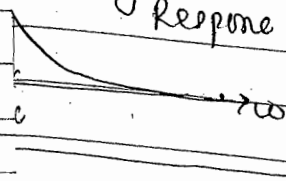

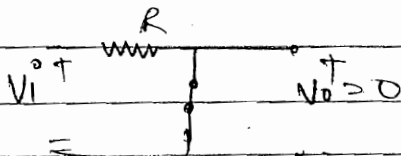Case 2 $s=\infty$; $Z = \frac{1}{sC} = 0$



some drop

$\rightarrow s$

Disadvantage

of this method: - Can't identify of seg.


Ex. 1st order HPF.

LPF


HPF

Cor

①

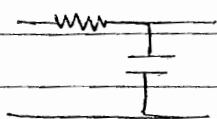

Integrator

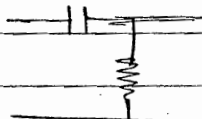

Differentiator

Interrelation of R & C

$$H(s) = \frac{1}{1 + \frac{s}{\omega_c}}$$

$$H(s) = \frac{1}{1 + \frac{1}{s\omega_c}} = \frac{s\omega_c}{1 + s\omega_c}$$



Rep

ω_c



$$\omega_c = \frac{1}{RC}$$

$$\omega_c = \frac{1}{RC}$$

④

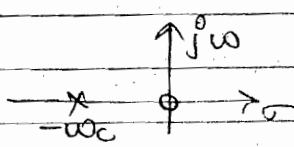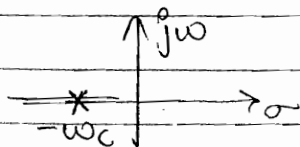


⑤

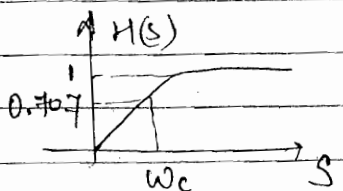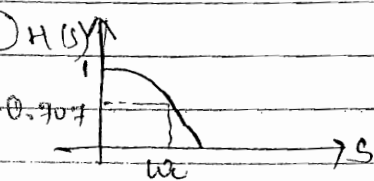

✓ An APF can be used to provide the music signal.

Ex:- 1st Order LPF :-

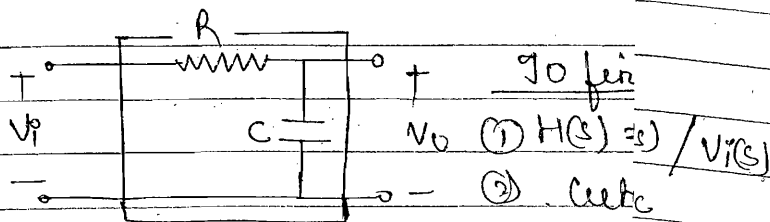(By adjusting the value of RC) same ckt can use as LPF and as HPF





(1) freq. resp. $H(s)$ Vs s
(2) Identification of filter.

Solution (1) $V_o(s) = H(s) = \frac{1}{RCs + 1}$

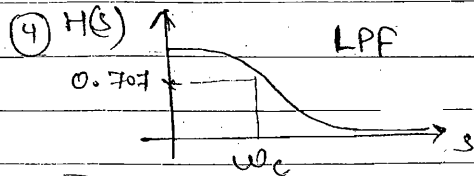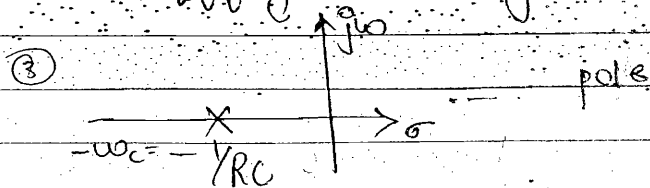(2) $\omega_c = \frac{1}{RC}$; $f_c = \frac{1}{2\pi RC}$

cut-off freq:- where gain $\downarrow$ to -3dB



(3) put $s = j\omega$ $H(j\omega) = \frac{1}{1 + j\omega RC}$

1. $\omega \ll \omega_c$; $|H(\omega)| \approx 1$


2. $\omega \approx \omega_c$; $|H(\omega)| = \frac{1}{\sqrt{2}}$ (rod of)

3. $\omega \gg \omega_c$; $|H(\omega)| \approx \frac{1}{\omega RC}$ (shing)

• An APF can be used to provide a stereophonic music signal.

Ex:- 1st Order LPF:-

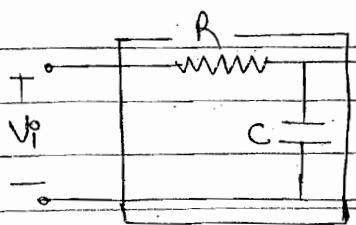(By adjusting the value of RC (Time constant) same ckt can use as LPF and as integrator)



To find:-

(1) $H(s) = T.O.F. = V_o(s) / V_i(s)$

(2) Cut off freq. ω_c

(3) Zero-pole pattern

(4) freq. resp. $H(s)$ Vs s

(5) Amplitude Response, $|H(\omega)|$ Vs ω .

~~Identificati~~ Identification of filter.


shape wise no much diff. B/w Amplitude & freq. response.

Solution (1) $V_o(s) = H(s) = \frac{V_i(s)}{R + 1/sC} = \frac{1}{(1 + sRC)} = \frac{1}{(1 + \frac{s}{\omega_c})} \equiv H(s)$


(2) $\omega_c = \frac{1}{RC}$; $f_c = \frac{1}{2\pi RC}$

• cut off freq:- Where gain $\downarrow$ To value 0.707 or -3dB

(3)

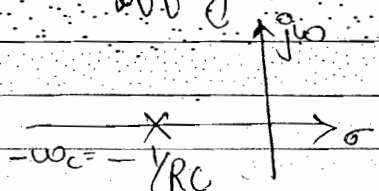

pole zero-pattern.

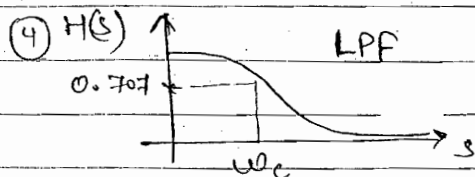

freq. Resp.

{ Resemble to LPF so it called LPF }

or also $V_o(s) / V_i(s)$ Vs s .

(5)

put $s = j\omega$ $H(j\omega) = \frac{1}{1 + \frac{j\omega}{RC}}$; $|H(\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$; $H(\omega)$ Vs ω

1. $\omega \ll \omega_c$; $|H(\omega)| \approx 1$



2. $\omega \approx \omega_c$; $|H(\omega)| = \frac{1}{\sqrt{2}} \approx 0.707$

3. $\omega \gg \omega_c$; $|H(\omega)| \approx \frac{\omega_c}{\omega}$


} method of sketching graph.

① Identification:

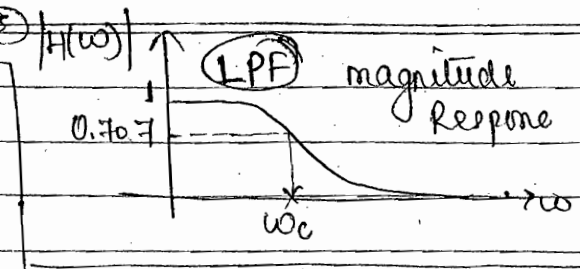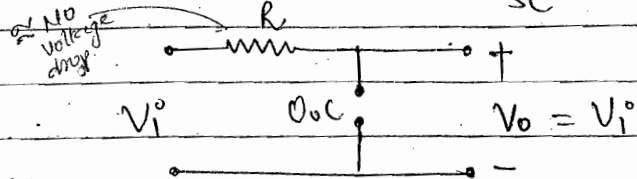
Case 1 $s=0$; $Z = \frac{1}{sC} = \infty$



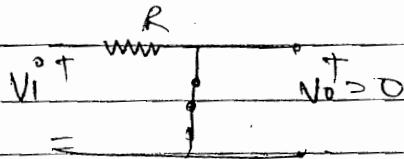Case 2 $s=\infty$; $Z = \frac{1}{sC} = 0$



But if having some drop

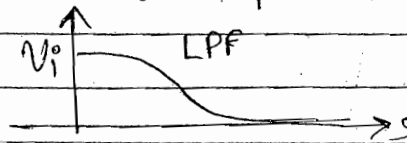

Interview



Disadvantage of this method: - Can't identify the order of sys.

Ex. 1st order HPF.

LPF

HPF

Comment

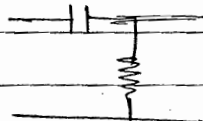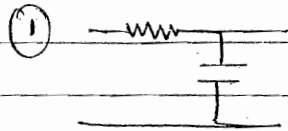

Interchange the location of R & C components

Integrator

Differentiator

$$H(s) = \frac{1}{1 + \frac{s}{\omega_c}}$$



$$H(s) = \frac{1}{1 + \frac{1}{s/\omega_c}} = \frac{s/\omega_c}{1 + s/\omega_c}$$

Replace $\frac{s}{\omega_c}$ By $\frac{1}{s/\omega_c}$



$$\omega_c = \frac{1}{RC}$$

$$\omega_c = \frac{1}{RC}$$

Cut off frequency

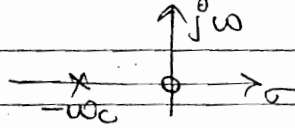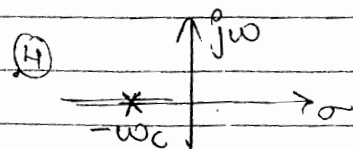

Poles - Zero plot

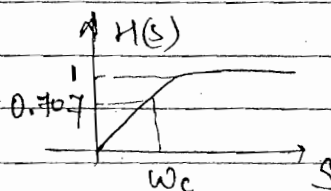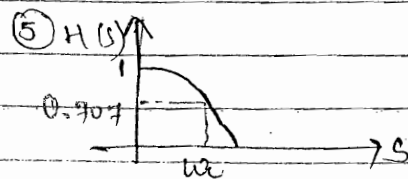

freq. Response

Ex: 1st Order APF


To find:

(1) T.o.F. $\Rightarrow H(s) = \frac{V_o(s)}{V_i(s)}$

(2) Pole-zero Pattern.

(3) $|H(\omega)|$ Vs ω .. magnitude Response

$\theta(\omega)$ Vs ω Phase response

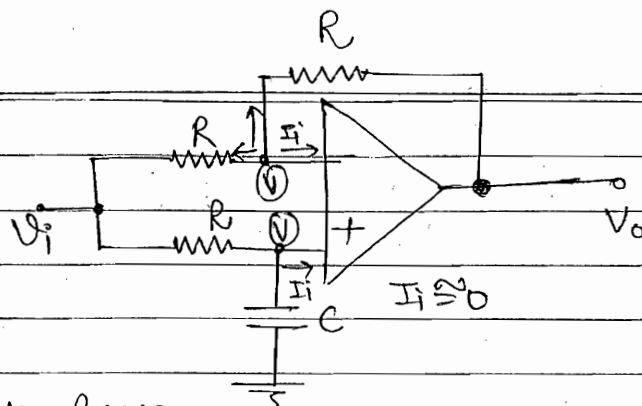

$\rightarrow$ O/p of op-amp is arbitrary $\rightarrow$ So never write the KCL at V_o (o/p)

(1) The voltages at I/p. terminals of the op-amp. are always equal since any ideal opamp. has infinite voltage

(2) The I/p current drawn by the op-amp is zero since any ideal op-amp has ∞ I/p Impedance.

(3) Always write KCL eqn at the I/p. of the op-amp.

(4) Never write KCL eqn at the O/p of op-amp unless it is terminated by load impedance. Since No load condⁿ the O/p current of the op-amp is arbitrary and is unknown.


KCL-1 $\frac{V - V_i}{R} + \frac{V - V_o}{R} + 0 = 0 \quad \Rightarrow 2V = V_i + V_o \quad \text{--- (1)}$

KCL-2 $\frac{V - V_i}{R} + \frac{V - 0}{1/sC} + 0 = 0 \quad \Rightarrow V = \frac{V_i}{1 + sRC} \quad \text{--- (2)}$

$\Rightarrow \frac{2V_i}{1 + sRC} = V_i + V_o \Rightarrow V_i \left(\frac{2}{1 + sRC} - 1 \right) = V_o$

$\Rightarrow \frac{V_o}{V_i} = \frac{1 - sRC}{1 + sRC} = H(s) = \text{T.o.F.}$

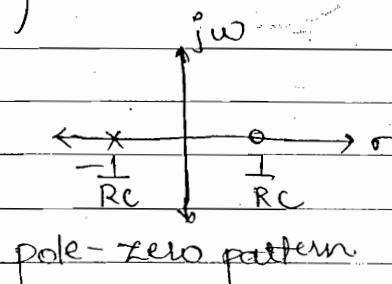$s = j\omega$
 $H(j\omega) = \frac{1 - j\omega RC}{1 + j\omega RC}$




pole-zero pattern

$|H(\omega)| = 1$

$\theta(\omega) = -2 \tan^{-1} \omega RC$



Amplitude response



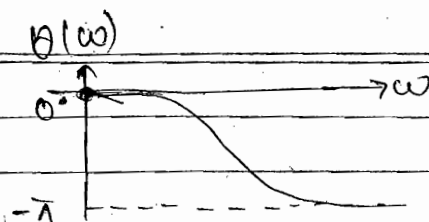


Phase response

Chapter 8

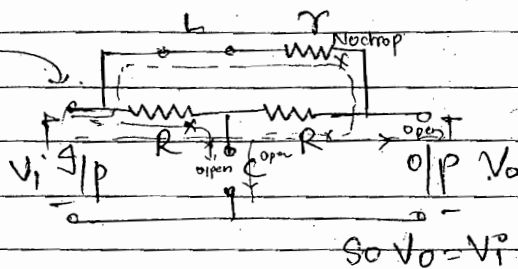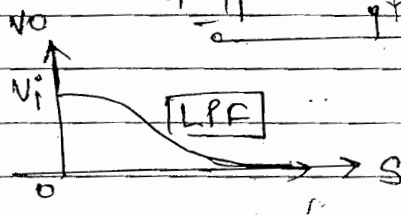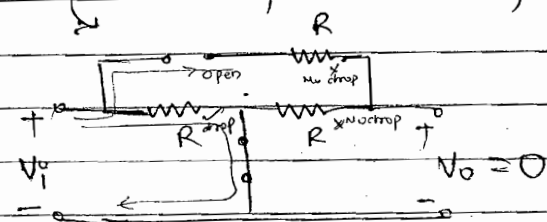
Q.2 $s=0$; $L \Rightarrow s.c$, $C \Rightarrow o.c$

$s=\infty$; $L \Rightarrow o.c$, $C \Rightarrow \infty$



$$So V_o = V_i$$

Q.3

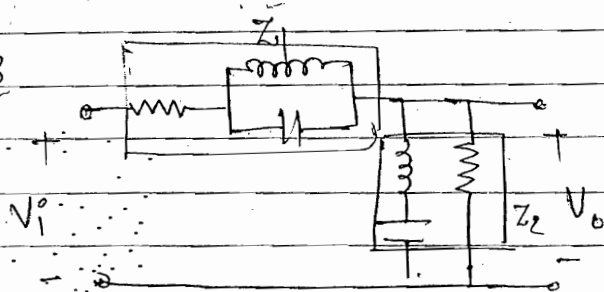

1. $s=0$, $L \Rightarrow s.c$, $C \Rightarrow o.c$



2. $s=\infty$; $L \Rightarrow o.c$, $C \Rightarrow s.c$


ckt is again same as case 1.

$$V_o = \frac{R_2}{R_1 + R_2} V_i \text{ --- finite}$$

$$V_o = \frac{R_2}{R_2 + R_1} V_i \text{ finite}$$

3. $0 < s < \infty$

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_i$$

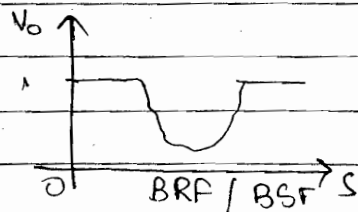


when R is in series
Total Impedance $\uparrow$
R is in parallel Total
Impedance $\downarrow$


Q.6

$$H(s) = \frac{10s}{s^2 + 10s + 100}$$

$$\text{at } s=0 = 0$$
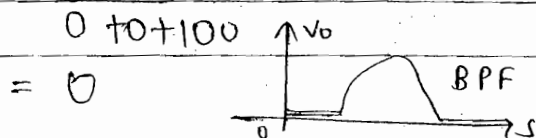
$$\text{at } s=\infty = \frac{10/s}{1 + \frac{100}{s^2}} = 0$$



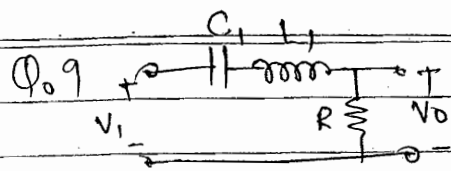


$$\Delta\omega_1 = BW_1 = B_1$$

Series

$$\Delta\omega_1 = \frac{R}{L_1}$$

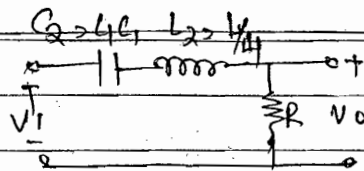
$$B_1/B_2 = \frac{R/L_1}{4R/L_1} = \frac{1}{4}$$



$$\Delta\omega_2 = BW_2 = B_2$$


$$\Delta\omega_2 = \frac{R}{L_1/4} = \frac{4R}{L_1}$$

ω_0 = Remain same.

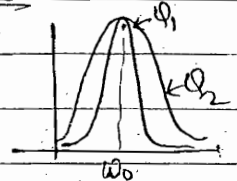

$B_1 < B_2 \Rightarrow Q_1 > Q_2$; Ch-1 Behaves as Better tuned ckt.

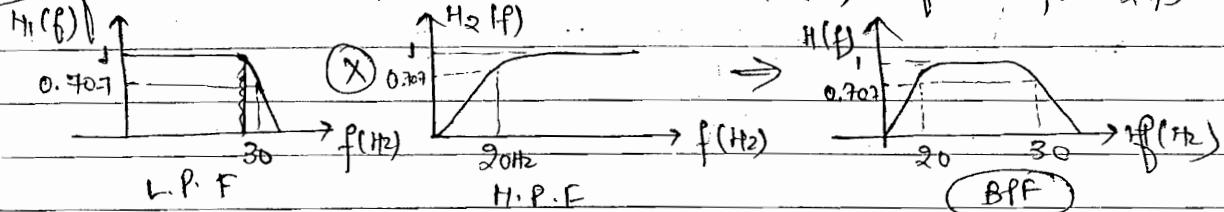Q.10 for cascaded. $N(\omega) = H_1(\omega) \cdot H_2(\omega)$; $H(f) = H_1(f) \cdot H_2(f)$



$$\Delta f = 30 - 20 = 10 \text{ Hz}$$

$$f_0 = \sqrt{f_1 f_2} = \sqrt{20 \times 30} = 10\sqrt{6} \text{ Hz}$$

$$Q_0 = \frac{f_0}{\Delta f} = \frac{10\sqrt{6}}{10} = \sqrt{6}$$

5/11/2014


Network Topology

Graph Theory

→ Another method to solve any. elect. N/w.

Ex Given: Any elect. N/w

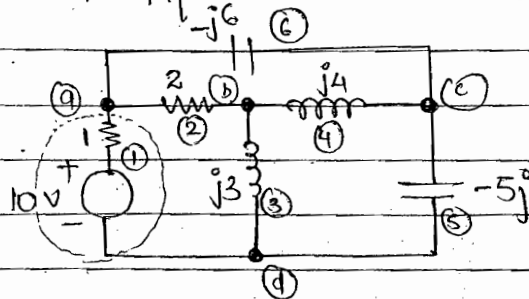- To find:-
1. Graph of N/w.
 2. Oriented Graph
 3. Tree of graph
 4. Co-tree



No. of Nodes = $n = 4$


No. of Branches $b = 6$

Graph of Network : Graph: $n: [a, b, c, d]$
 $b: [1, 2, \dots, 6]$

For fully connected graph:-

No. of Branches:


$$= {}^nC_2 = \frac{n(n-1)}{2}$$

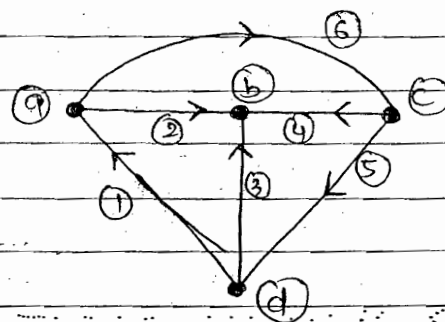

Oriented graph/
 fully connected graph

$V_2 = 2 \cdot i_2$, $V_3 = j3 i_3$
 $V_3 = j3 i_3$, $V_4 = j4 i_4$
 $V_5 = -j5 i_5$, $V_6 = -j6 i_6$

Tree-1 :-

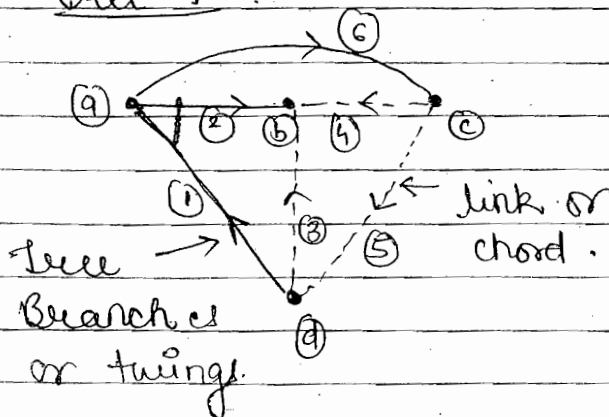

Tree: $[1, 2, 6]$ Tree Branches
 or
 twigs

Co-tree: $[3, 4, 5]$ links/
 chord.

- No. of Branches connected to a node $\rightarrow$ is degree of Node
- $\rightarrow$ fully connected graph = degree of each node is same.

- No. of Branches (Tree) $= n-1 = \text{no. of p.c.l eq}^n$
- No. of links or chords $= b-(n-1) = \text{no. of p.v.l eq}^n$
- Degree of Node $= n-1$
 $r \equiv \text{Rank of graph} = n-1$

- W-tree $\rightarrow$ each node not having same degree. Then highest degree of Node $\Rightarrow$ define Rank of Tree.

$\text{No. of Trees} = n^{(n-2)}$ ONLY FOR FULLY CONNECTED GRAPH.

$\text{No. of Tree} = \det[A A^T]$ FOR GENERAL GRAPH
 [NOT F.C. OR F.C.]

where $[A] = \text{reduced incidence matrix}$

- The N/w Topology is concerned the manner in which various elements are interconnected b/w various nodes irrespective of their values and types.
- Basic Tree of a graph.
 - (1) The tree contains all the nodes of the graph
 - (2) There is no close path and hence a tree is circuit less.
 - (3) The tree of a graph is not unique.
 - (4) If the graph contains n nodes. Then it's a tree contain $(n-1)$ tree Branches.
 - (5) The tree of the graph can be utilize to solve the given N/w using
 - (i) Tie-set Matrix
 - (ii) Cut-set Matrix.
 - (6) Any close loop in a given graph may not contain all the nodes of the graph.
 - (7) In a fully connected graph each node is connected

to every node of other graph which is with a direct Branch.

- (8) The degree of any node represents the no. of Branches which are meeting at the specified Node.
- (9) In a fully connected graph the degree of each node is equal and represents the rank of the graph.
- (10) When the graph is not fully connected, then the degree of each node is different. But the highest degree of the node represents the rank of the graph.

Main Points:

1. NO. of Branches in a fully connected graph $= {}^nC_2 = \frac{n(n-1)}{2}$

2. NO. of Trees of a graph $= n^{(n-2)}$... ONLY for F.C graph
 $= \det[AAT]$... for general graph
 [whether FC or not]


3. NO. of links / chords $= b - (n-1)$
 $= \text{NO. of KVL eq}^n$
 $= \text{NO. of fundamental loop}$
 $l = b - (n-1) \leftarrow \text{Imp.}$
 $= \text{NO. of f-tie sets}$

4. NO. of tree-Branches $= n-1$
 $= \text{NO. of KCL eq}^n$
 $= \text{degree of each node in a F.C graph}$
 $= \text{Rank of graph}$
 $= \text{Max degree of Node when graph is not F.C}$

= no. of nodes - pair voltages.
= no. of f-cut sets.

Ex:- Given : graph of a Network

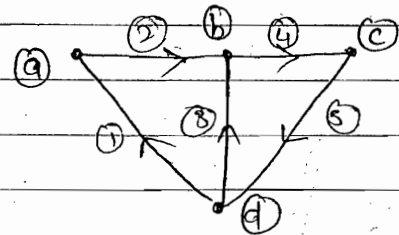To find: 1. Incidence Matrix
2. Reduce incidence Matrix [A]



Incidence Matrix

1. The incidence Matrix translates all the geometrical features of the graph into an algebraic expression.
2. Every graph has an Incidence Matrix and vice-versa.
3. Each row of the matrix contains entering of +1, -1, 0.
 $\rightarrow \Rightarrow +1$, $\leftarrow \Rightarrow -1$, $\cdot \Rightarrow 0$
4. Each column of the matrix contains only one entry of +1 and only one entry of -1. So that that algebraic sum of each column is always equal to zero.
5. The determinant of the incidence matrix of any close loop is always equal to zero.
6. The size of matrix is $[n \times b]$

where n = No. of Nodes = No. of rows in the matrix

b = No. of Branches = No. of column in the matrix


7. Two graphs having same incidence matrix are called isomorphic graph.

Solution:- Incidence Matrix

Nodes $\downarrow$ Branches $\rightarrow$

		(1)	(2)	(3)	(4)	(5)
	a	-1	+1	0	0	0
	b	0	-1	0	+1	0
	c	0	0	0	-1	+1
	d	+1	0	+1	0	-1

$[n \times b]$
 $[4 \times 5]$

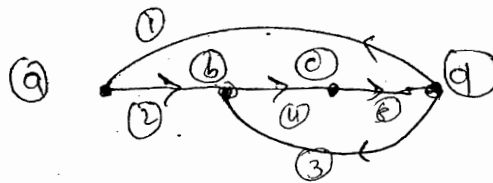

⇒ Write the Matrix ⇒ row wise
 ⇒ Draw the graph ⇒ column wise

• Reduced Incidence Matrix:

- (1) A particular Node is taken as a reference Node
- (2) Delete the row corresponding to the specific ref. node to obtain the reduced incidence Matrix.
- (3) The size of the Matrix is $[(n-1) \times b] = [3 \times 5]$
- (4) This matrix can be used to find the no. of Trees for any general graph using the result $|\det [A A^T]|$

• Taking Ref. Node: (b)

Node: Branches: →

$$[A] = \begin{matrix} \text{Node} \downarrow & \text{Branches} \rightarrow \\ \begin{matrix} (a) \\ (c) \\ (d) \end{matrix} & \begin{bmatrix} (-1) & +1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & +1 \\ +1 & 0 & +1 & 0 & -1 \end{bmatrix} \end{matrix} \quad [(n-1) \times b] = [3 \times 5]$$


Ex. Given: Tree of a graph.

To find:

- (1) f-tree set Matrix, f-loop Matrix, f Branch Matrix $[B_f]$
- (2) f-cut set Matrix $[Q_f]$

• Main points of F-Tie Sets

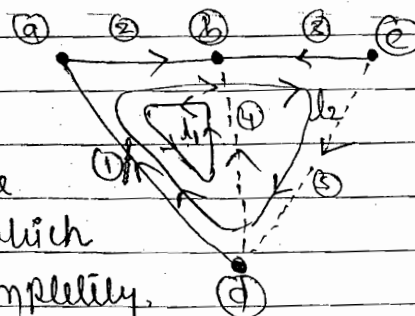1. Fundamental Tie Sets are the optimum of Tie sets with which a given ckt can be solved completely.
2. A fundamental T-set represents the no. of Branches required to form a close loop



(3) Each fundamental Tie set contain one and only one link or chord, remaining are the tree Branches.

(4) The No. of fundamental Tie set is

$$f\text{-Tie set} = \text{No. of links / chords} \\ = b - (n-1) \quad [5 - (4-1)] = 2$$

(5) The direction of fundamental Tie-set is same as the direction of link of the chord.

(6) The fundamental Tie set Matrix can be utilize to write Branch current in term of loop current.

Solution: $f\text{-Tie-Set}:-$

$$l_1: [\overset{\text{link}}{\underline{2}}, \underline{2}, \underline{(4)}] \quad l_2: [\underline{1}, \underline{2}, \underline{3}, \overset{\text{link}}{\underline{(5)}}]$$

$\Rightarrow f\text{-Tie-set Matrix}$

$$\begin{matrix} l_1 \\ l_2 \end{matrix} \begin{bmatrix} \textcircled{1} & \textcircled{2} & \textcircled{3} & \textcircled{4} & \textcircled{5} \\ -1 & -1 & 0 & +1 & 0 \\ +1 & +1 & -1 & 0 & +1 \end{bmatrix} \equiv [B_f]$$

B_t

$B_l \equiv U$

$B_t \rightarrow \text{tree}$

$B_l \rightarrow \text{link}$

$U \rightarrow \text{unity Matrix}$

$$[B_f] = [B_t \mid U]$$

Branch Current:-

$$i_1 = -I_1 + I_2, \quad i_2 = -I_1 + I_2, \quad i_3 = -I_2, \quad i_4 = +I_1, \quad i_5 = +I_2$$

• Main Points of $f\text{-Cut set}:-$

(1) Fundamental cut set are optimum no. of cut set required to solve the N/w completely

(2) Each fundamental cut set represent a group of Branches which must be cut so that the graph is divided into two parts.

(3) Each fundamental cut set contain one and only one tree branch, Remaining are links or chord.

(4) The direction of fundamental cut set is the same as the direction of tree branch.

(5) The no. of fundamental cut set is equal to the no. of tree Branch

$$f\text{-cut set} = \text{No. of tree Branches}$$

$$= n-1$$

$$(4-1) = 3.$$

(6) The fundamental cut set Matrix can be utilize to write Branches voltage in terms of Node voltages


$$C_1 : [\textcircled{1}, \textcircled{4}, \textcircled{5}]$$

$$C_2 : [\textcircled{2}, \textcircled{4}, \textcircled{5}]$$

$$C_3 : [\textcircled{3}, \textcircled{5}]$$

→ Tree Branch

f-cut set matrix

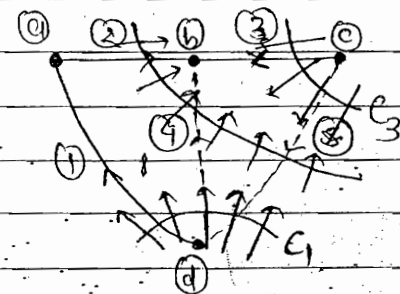

$$[Q_f] = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} C_1 \\ C_2 \\ C_3 \end{matrix} : & \begin{bmatrix} 1 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & 1 & 1 \\ 0 & 0 & 1 & 0 & 1 \end{bmatrix} \end{matrix}$$

$$Q_t \equiv u$$

$$Q_l$$

$$[Q_f] = [Q_t \quad Q_l]$$

$$[Q_f] = [u \quad Q_l]$$

$$[Q_l] = -[B^T] \quad , \quad [B] = -[Q_l^T]$$

Branch voltage:

$$V_1 = V_1, \quad V_2 = V_2, \quad V_3 = V_3, \quad V_4 = V_1 + V_2, \quad V_5 = -V_1 - V_2 + V_3$$

NOTE (i) The fundamental cut-set Matrix corresponding to link or chord is always equal to -ve of transpose of fundamental-Tie-set Matrix corresponding to tree Branches and vice versa.


- This result is always valid irrespective of the type of tree selected for a given graph.
- The tree set of eqⁿ represent the equilibrium eqⁿ. Since these equation represent the given N/w completely and uniquely.

Concluding Comment:- While designing a particular ckt and when any element value in any branch of the N/w is changed again and again then the method of analysis using KVL & KCL technique becomes more complicated.

Under this condition the method of analysis using graph theory is simplify. Since


- (i) Graph of the N/w
- (ii) Tree of the graph.
- (iii) Tie-set Matrix
- (iv) Cut set Matrix

all will remain same. Only one equation has to be modify where the Branch voltage is represented in terms of Branch current. All other eqⁿ remain unchanged.

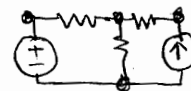

Chapt 3

Q.6.

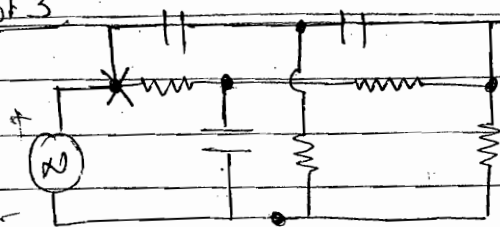

Twins-T M/c

$$n = 4, b = 7$$

$$\text{No. of f-lie set} = \text{No. of KVL eq}^n = b - (n - 1) = 4$$

$$\text{No. of f-cut set} = \text{No. of KCL eq}^n = n - 1 = 3$$

⇒ dependent source }
are not consider }

Network Theorem

→ used to simplify elect. Networks.

• Superposition Theorem: The response in any element of a linear bilateral RLC N/w containing more than one independent voltages and current source is the sum of responses produce by the source each acting alone when


- (i) All other independent voltage sources are shorted or replaced by their internal impedances.
- (ii) All other independent current sources are open ct or replaced by their internal impedances.
- (iii) All dependent voltage and current sources remain as they are and therefore these sources are neither s.c. nor o.c.

The Theorem is not applicable for → the N/w. containing single independent voltage or current source


- Non linear element junction
- unilaterial element ex: PN Diode

The Theorem is also not applicable to non-linear parameter such as power.

Ex:-

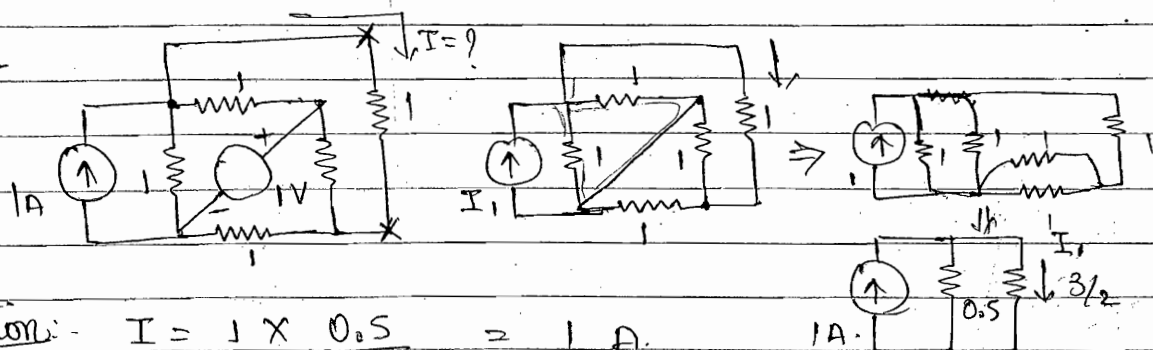

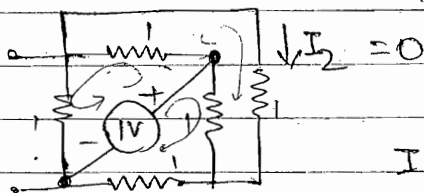
Solution:- $I = \frac{1 \times 0.5}{3/2 + 0.5} = \frac{1}{4} \text{ A}$



Showing the Balanced Bridge

$I = I_1 + I_2 = \frac{1}{4} \text{ A}$

Exa

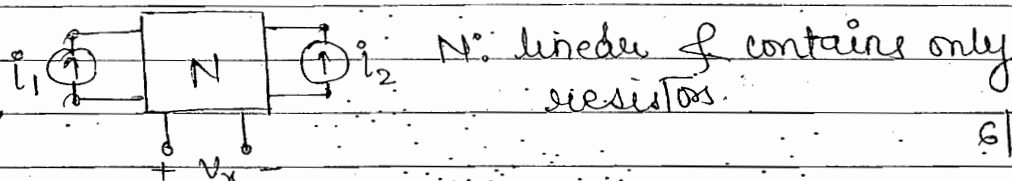

N: linear & contains only resistors.

6/11/2014

N: linear Network & contains only resistors.

If $i_1 = 8 \text{ A}$, $i_2 = 12 \text{ A}$; $V_x = 80 \text{ V}$

$i_1 = -8 \text{ A}$, $i_2 = 4 \text{ A}$; $V_x = 0 \text{ V}$

find V_x if $i_1 = i_2 = 20 \text{ A}$.

Solution: $i_2 = 0$; $V_{x1} = i_1 R_1$ $i_1 = 0$; $V_{x2} = i_2 R_2$

$V_x = V_{x1} + V_{x2}$

$V_x = i_1 R_1 + i_2 R_2$

$8R_1 + 12R_2 = 80$ } $R_1 = 5/2$

$-8R_1 + 4R_2 = 0$ } $R_2 = 5$


$V_x = i_1 R_1 + i_2 R_2 = 20 \times \frac{5}{2} + 20 \times 5 = 150 \text{ V}$

Linear OR Resistive N/w $\Rightarrow$ Superposition

0.2
2.5
1.5
3.5

$\rightarrow$ Once the condition is specified, there is no change in sign (current, voltage) if the direction is reversed.

Ex:

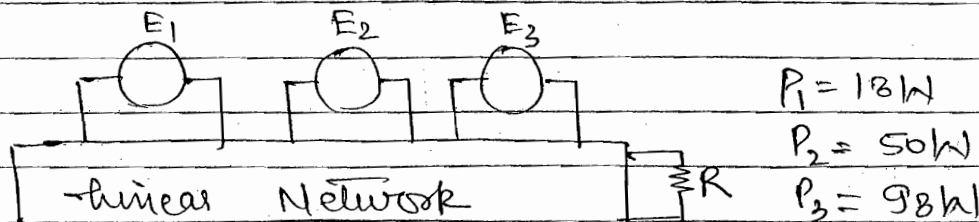

When $E_1 \rightarrow$ excited, $E_2 = E_3 = 0$ power consumption by R is 18W. Similarly for P_2, P_3 .

$$P_{\max} \neq P_3 + P_2 + P_1 \quad P_{\min} \neq P_3 - P_2 - P_1$$

$\therefore$ Power non-linear can't use superposition theorem

$$P = \frac{V^2}{R} = I^2 R \quad V = \sqrt{P} \cdot \sqrt{R}$$


$$V_{\max} = V_1 + V_2 + V_3, \quad P_{\max} = \frac{V_{\max}^2}{R}; \quad P_{\min} = \frac{V_{\min}^2}{R}$$

$$P_{\max} = (\sqrt{P_3} + \sqrt{P_2} + \sqrt{P_1})^2, \quad P_{\min} = (\sqrt{P_3} - \sqrt{P_2} - \sqrt{P_1})^2$$

$$= 450W \quad = 2W$$

Q.9 NO. 27

Q.92

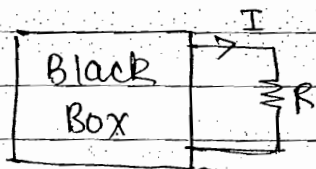

$$R = 0; \quad I = 3$$


$$R = 2; \quad I = 1.5$$

$$R = 1; \quad I = ?$$

contain resistors & independent sources

Voltage Source


Current Source

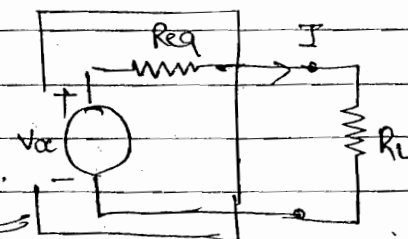

Thevenin's Model

$$V_{oc} = I [R_{eq} + R]$$
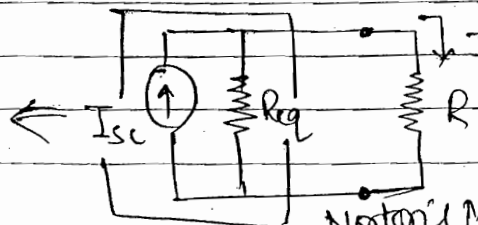
$$I = \frac{R_{eq} \cdot I_{sc}}{R_{eq} + R}$$



Norton's Model

$$V_{oc} = 1.5 (R_{eq} + 2)$$

$$\Rightarrow V_{oc} = 6$$


$$R_{eq} = 2$$

$$V_{oc} = I(R_{eq} + R)$$

$$\frac{1}{6}$$

$$\frac{1}{2} \frac{1}{1}$$

$$\Rightarrow I = 2A. \text{ As}$$

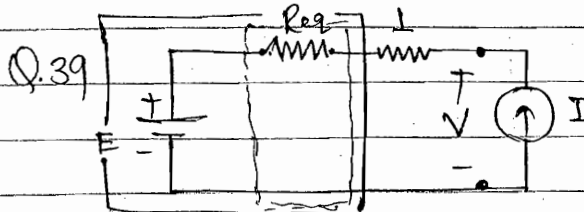

Thevenin's Model.


1. $E = E_1$, $V = 5V$, (I) removed
 $E_1 = V = 5V$

2. $E = 0$; $I = 1A$; $V = 5$

$$5 = I(1 + R_{eq}) + E_0$$

$$R_{eq} = 4$$

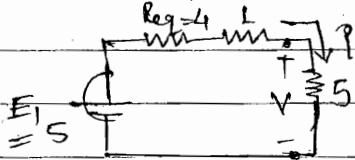
3. $E = E_1$, $I \xrightarrow{\text{replaced}} 5A$



$$V = 5 \times 5 = \frac{25}{5+5} = 2.5$$


$$I = \frac{5 \times 5}{5+5} = 1.25A$$

• Thevenin's & Norton's Theorem:-

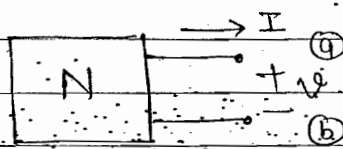


Thevenin's

Norton.

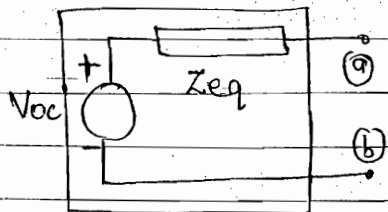

Thevenin's Model.

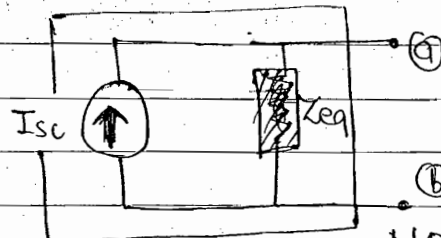

Norton's Model

V_{oc} = O.C. voltage b/w a & b when $I = 0$

I_{sc} = S.C. current B/w a & b when $V = 0$

$$\frac{V_{oc}}{I_{sc}} = Z_{eq}$$

- If the polarity of terminal voltage V is $+$ then V_{oc} also $+$
 $V_{oc} +$

- If the polarity of terminal voltage is $V -$ To satisfy it I_{sc} also $\uparrow$ I_{sc}

- Thevenin's Theorem: - A linear active RLC N/w which contains one or more independent or dependent voltage or current sources can be replaced by single voltage source V_{oc} in series with equivalent impedance. The equivalent impedance represent Z_{eq} equivalent B/w the two external terminals when

- (i) All independent voltage source are s.c. or replaced by their internal impedance.

- (ii) All independent current source are o.c. or replaced by their internal impedances.

- (iii) All dependent voltage and current sources remain as they are and therefore these sources are neither s.c. nor o.c.

The theorem is always applicable of irrespective of


- (i) Nature of the component whether reactive or resistive

- (ii) The Nature of voltage and current source whether ac or dc

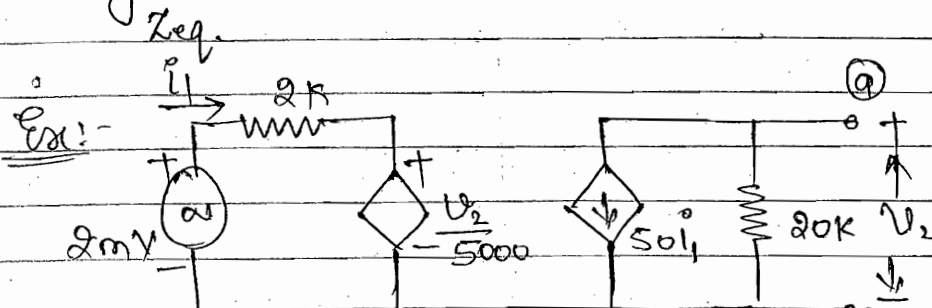- (iii) The theorem is not applicable to the N/w containing Non-linear elements, unilateral elements such as p-n junction diode.


- Norton's Theorem: A linear active RLC N/w which contains one or more independent or dependent voltage or current sources can be replaced by

single current source I_{sc} in shunt with an impedance



To find

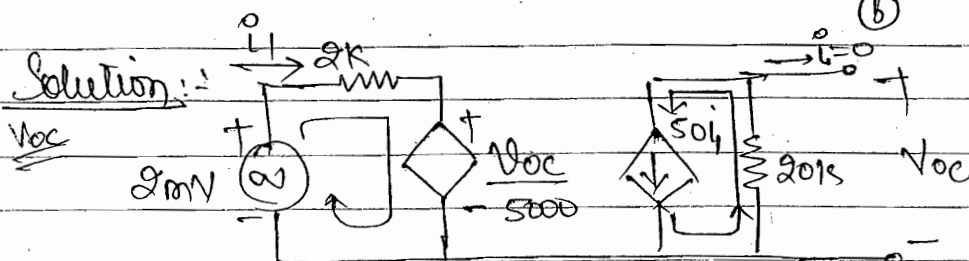1. V_{oc} ... Req. Thevenin
2. I_{sc} ... Req. Norton




$$2mV = 2kI_1 + \frac{V_{oc}}{5000}$$

$$-V_{oc} = 50I_1 \times 20 \times 10^3$$

$$2 \times 10^{-3} = \frac{1}{4} \times 2 \times 10^3 + \frac{V_{oc}}{5000}$$

$$I_1 = \frac{-V_{oc}}{50 \times 20 \times 10^3}$$
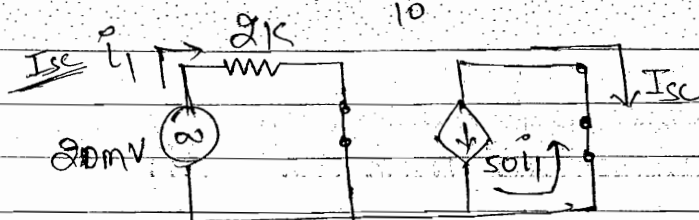
$$2 \times 10^{-3} = \frac{-V_{oc}}{50 \times 20 \times 10^3} \times 2 \times 10^3 + \frac{V_{oc}}{5000} \Rightarrow V_{oc} = \frac{-10V}{9}$$



$$I_{sc} = -50I_1 \quad \text{--- (1)}$$


$$2 \times 10^{-3} = 2 \times 10^3 \times I_1$$

$$I_1 = 10^{-6}$$

$$I_{sc} = -50 \times 10^{-6} = -50\mu A$$

$$R_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{10}{9 \times (-50 \times 10^{-6})}$$

$$= \frac{10^6}{45} = \frac{200K}{9}$$



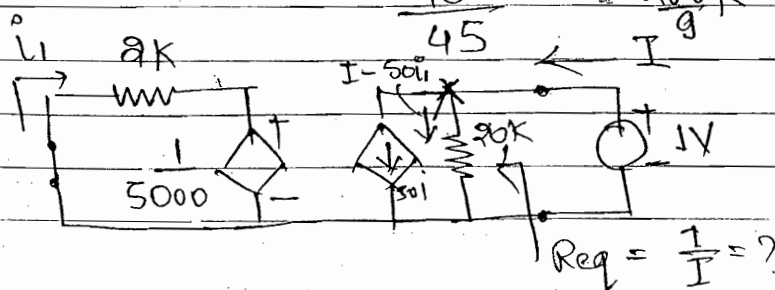


Choose any value of V , B or μ values of R Remain Same.

$$R_{eq} = \frac{1}{I} = ?$$



$$\Rightarrow 2 \times 10^3 i_1 + \frac{1}{5000} = 0 \quad \text{--- (a)} ; I = 20 \times 10^3 [I - 50i_1] \quad \text{--- (b)}$$

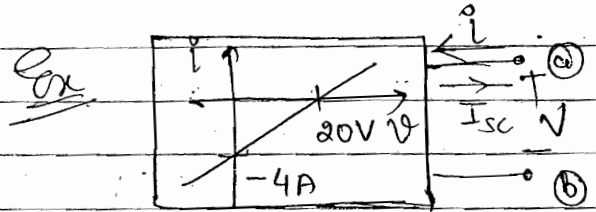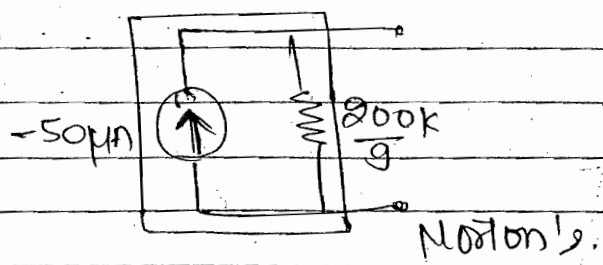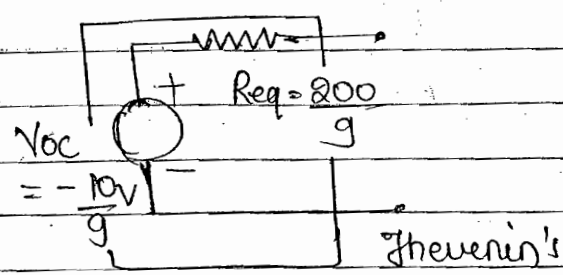from eqn (a) & (b) $R_{eq} = \frac{200k}{9}$





$$\begin{aligned} i=0 ; V &= 20V ; V_{oc} = 20V \\ V=0 ; i &= -4A ; I_{sc} = 4A \end{aligned}$$
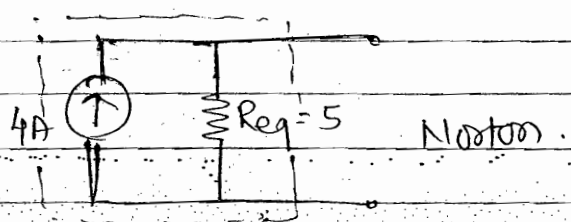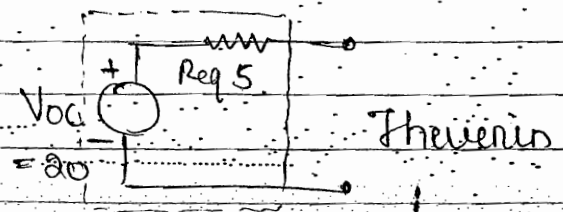
$$R_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{20}{4} \Rightarrow R_{eq} = 5 \Omega \quad \text{Ans}$$




Q7 Conventional:-

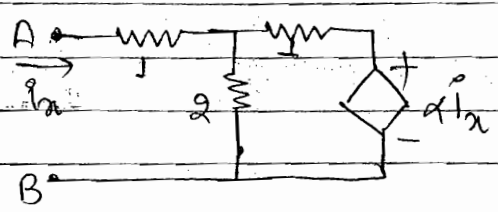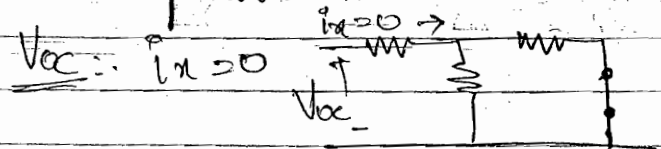

$$V_{oc} = 0$$

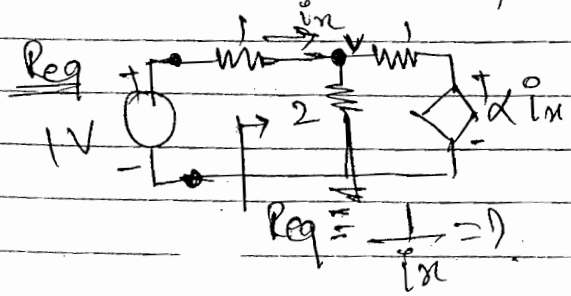Whenever V_{oc} is 0, R_{eq} find independently.



$$\begin{aligned} \frac{1-1}{1} + \frac{V}{2} + V - \alpha i_x &= 0 \\ \frac{5V}{2} - \alpha i_x - 1 &= 0 \quad \text{--- (1)} \end{aligned}$$

$$\frac{5V}{2} - x(1-x) = 0$$

$$V = \frac{(1+x)x}{2}$$

$$= \frac{2+2x}{2}$$

$$= \frac{5-2+2x}{2}$$

$$1-x-2x = 3$$

$$1-3x = 3$$

$$1x(3-2x) = 15$$

$$I_m = \frac{1-V}{1} \quad \text{--- (2)}$$



$$V = \frac{(1+I_x) \times 2}{5}$$

$$I_x = \frac{5 - (1+I_x) \times 2}{5} = \frac{5-2-2I_x}{5} = \frac{3-2I_x}{5}$$

$$\frac{5I_x + 2I_x}{5} = \frac{3}{5}$$

$$I_x = \frac{3}{(5+2)} = \frac{3}{7}$$
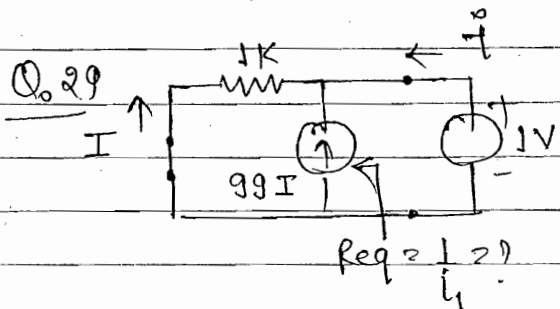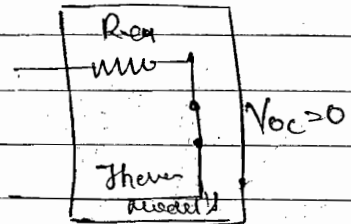
$$R_{eq} = \frac{1}{I_x} = \frac{5+2}{3}$$




$$-I = I + 99I = 100I \quad \text{--- (1)}$$

$$1V = 1K(-I)$$

$$I = -1$$

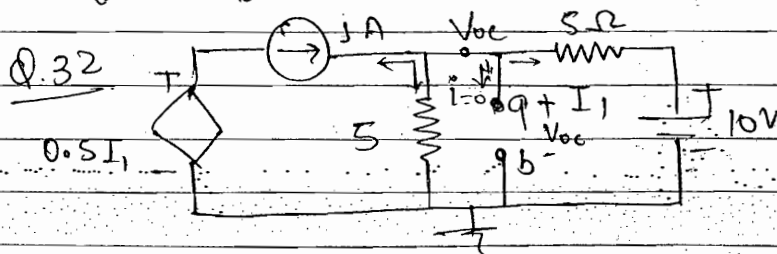
$$\text{find } \frac{1}{R_{eq}} = \frac{1}{1K} = 0.001 K = 10 \Omega \quad \text{Ans}$$



$$\Rightarrow \frac{V_{oc} - 10}{5} + \frac{V_{oc}}{5} = +1$$


$$\Rightarrow 2V_{oc} = 5 + 10$$

$$V_{oc} = \frac{15}{2} = 7.5$$

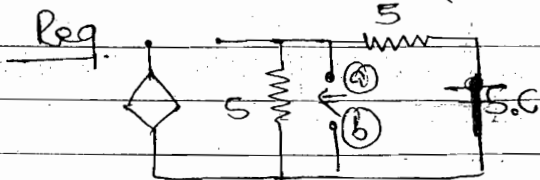


$$R_{eq} = 2.5 \Omega \quad \text{Ans}$$

Q.36

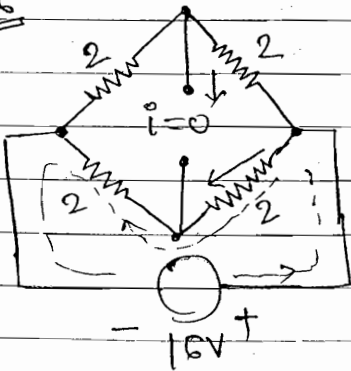



$$-16 + 2I = 0 \quad \boxed{I = 4} \text{ A.}$$

Given Balance Condition

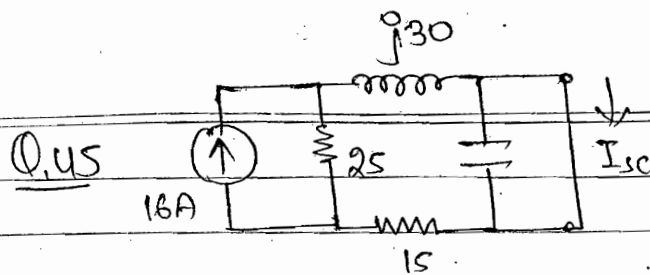

$$I_{sc} = 16 \times 25$$

$$40 + j30 = 6.4 - j4.6 \text{ A}$$

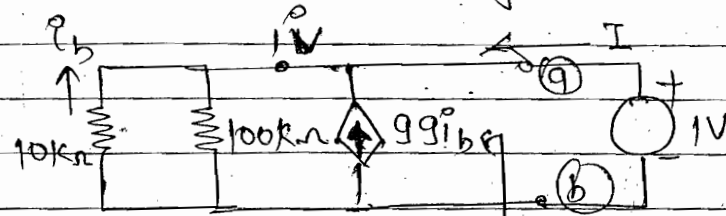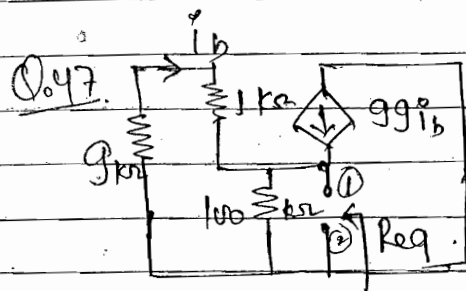


$$R_{eq} = \frac{1}{I}$$

$$\Rightarrow \frac{V}{10K} + \frac{V}{100K} = -99i_b - I \Rightarrow \frac{1}{10K} + \frac{1}{100K} = -(99i_b + I) \quad \text{--- (1)}$$

$$\Rightarrow -i_b = \frac{V - 0}{10K} = \frac{1}{10} \quad \text{--- (2)}$$

$$\text{put } i_b \text{ in (1)} \Rightarrow \frac{1}{10K} + \frac{1}{100K} = + \frac{99}{10} - I$$
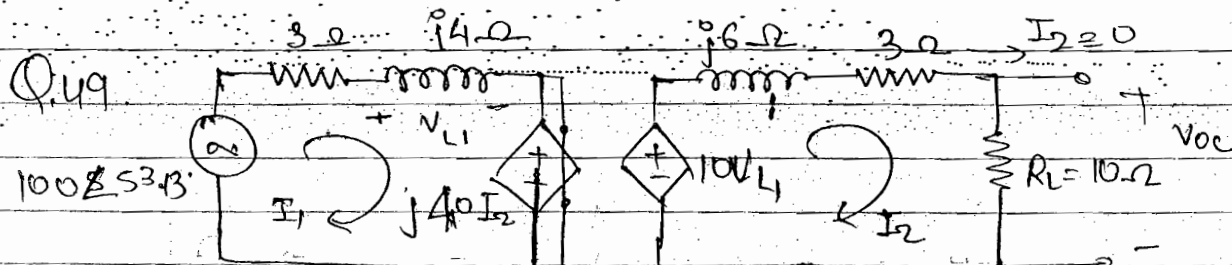
$$\frac{1}{I} = R_{eq} = 0.1K = 100 \Omega \text{ A}$$




$$I_1 = \frac{100 \angle 53.13}{3 + j4} = \frac{100 \angle 53.13}{5 \angle 53.13}$$

$$= 20 \text{ Amp}$$

$$V_{L1} = 20 \times j4 = j80$$


$$V_{oc} = 10 V_{L1} = 10 \times j80 = j800$$

$$= 800 \angle 90^\circ \text{ V A}$$

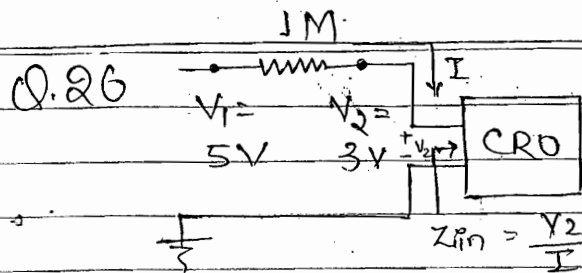


$$I = \frac{5-3}{1M} = 2 \times 10^{-6} \text{ Amp}$$
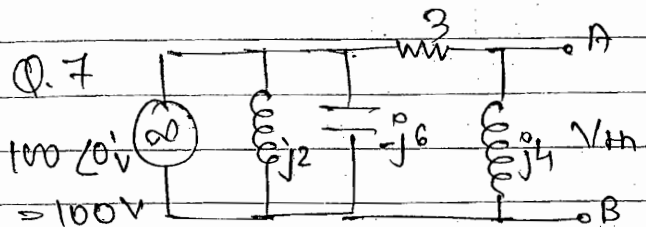
$$Z_{in} = \frac{3}{2 \times 10^{-6}} = 1.5 M\Omega$$



$$V_o = 100 \times \frac{j4}{3+j4} = j16(3-j4) \mu$$

• Max Power Transfer Theorem:

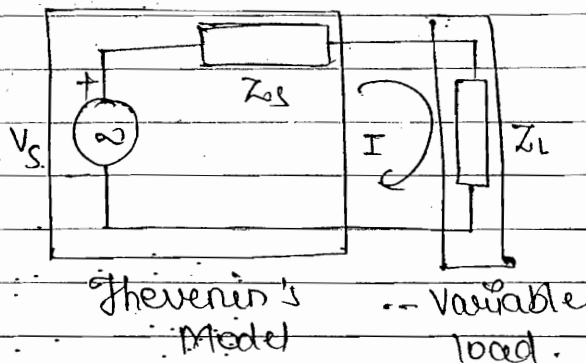

To find:- Condition for transfer of Max power from the source to the load.

$$\text{Consider } Z_L = R_L + jX_L$$

$$Z_s = R_s + jX_s$$

$$I = \frac{V_s}{Z_s + Z_L} = \frac{V_s}{(R_s + jX_s)(R_L + jX_L)} = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$P_L = |I|^2 R_L$$

$$P_L = \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

$$\text{for } P_L \text{ (max).}$$

$$\frac{\partial P_L}{\partial R_L} = 0$$

$$\Rightarrow R_L = R_s$$

$$\frac{\partial P_L}{\partial X_L} = 0$$

$$\Rightarrow X_L = -X_s$$

$$P_L = I^2 Z_L$$

$$P_L = I^2 R_L$$

$$P_L = |I|^2 Z_L$$

$$\Rightarrow P_L = |I|^2 R_L$$

Beoz deliver active (Real) power.

$$Z_L = R_L + jX_L = R_s - jX_s$$

$$Z_s = R_s + jX_s$$

$$Z_s^* = R_s - jX_s$$

$$\boxed{Z_L = Z_S^* \quad ; \quad R_S = R_L \quad ; \quad X_L = -X_S}$$

Condition for Maximum power Transfer:

- (i) Hence, in order to transfer maximum amount of power from the source to the load, the load Impedance must be complex conjugate of the source Impedance. Therefore the source and the load have equal resistive parts. They must also have equal reactive parts but opposite in sign. Therefore if the source is inductive the load must be capacitive and vice-versa.
- (ii) For maximum power transfer the load must be variable in nature.
- (iii) To apply maximum power transfer theorem any given N/S must be first transform in the standard Thevenin's model.
- (iv) The Maximum power transferred to the load is only 50% of the total power generated by the voltage source.

- (a) The Theorem is also applicable irrespective of the nature of voltage source whether it is ac or dc.
- (b) Nature of source and load whether it is resistive or reactive in nature.

cases :- General Case: - $Z_L = R_L + jX_L$
 $Z_S = R_S + jX_S$

$$\boxed{Z_L = Z_S^* \quad ; \quad R_S = R_L \quad ; \quad X_L = -X_S}$$

Imp


case 2: $Z_L = R_L$; $Z_s = R_s + jX_s$; $P_L = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$

$R_L = \sqrt{R_s^2 + X_s^2} = |Z_s|$


case 3: $Z_L = R_L$; $Z_s = R_s$... dc case ; $P_L = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$

$\Rightarrow R_L = R_s$

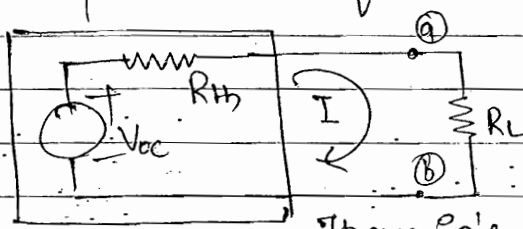Ex:- In the circuit shown. Find the value of load Resistance R_L b/w two external terminals so that maximum power is transferred to it. Hence calculate the Maximum power transferred to load.



Thevenin's Model.

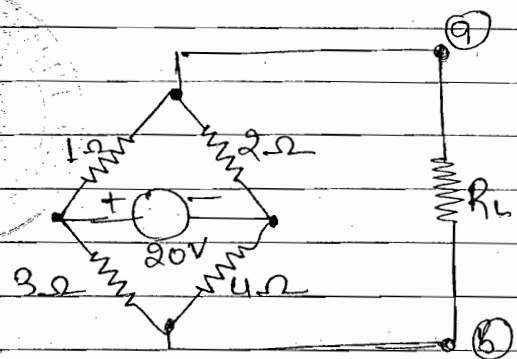


for P_{max} : $R_L = R_{eq}$
 $P_{max} = I^2 R_L = \left(\frac{V_{oc}}{R_{eq} + R_L} \right)^2 R_L = \frac{V_{oc}^2}{4 R_L}$


Sk:- $20 = I_1 + 2I_1$; $I_1 = 20/3$
 $20 = I_2(7)$; $I_2 = 20/7$


KVL

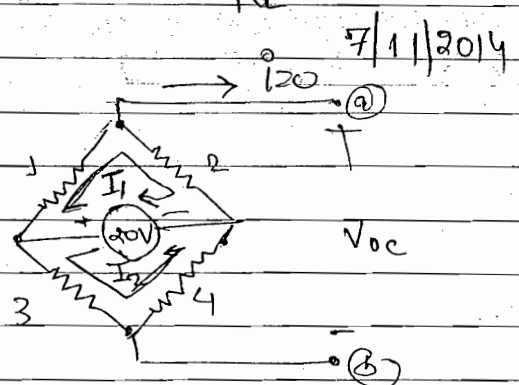$V_{oc} = 2I_1 - 4I_2$
 $= 2 \times \frac{20}{3} - 4 \times \frac{20}{7}$
 $= \frac{40}{21} \text{ Volt}$




$R_{eq} = \frac{50}{21} \Omega$

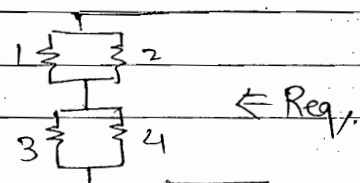

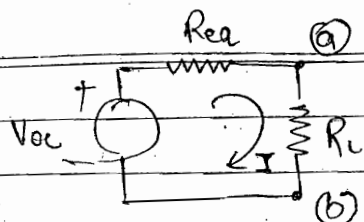

$$I = \frac{V_{oc}}{R_{eq} + R_L}; P_{max} = R_L = R_{eq} = \frac{50}{2} \Omega$$
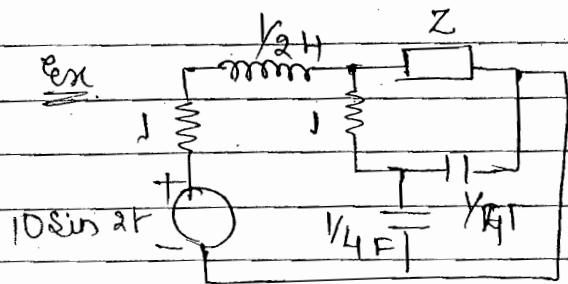
$$P_{max} = \frac{V_{oc}^2}{4R_L} = \frac{8}{2} \text{ W}$$




To find Z for P_{max} .

$$\frac{1}{2} \text{ H} \Rightarrow j\omega L = j \times 2 \times \frac{1}{2} = j1 \Omega$$

$$\frac{1}{4} \text{ F} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j \times 2 \times \frac{1}{4}} = -j2 \Omega$$


Solution: $\omega = 2 \text{ rad/sec}$
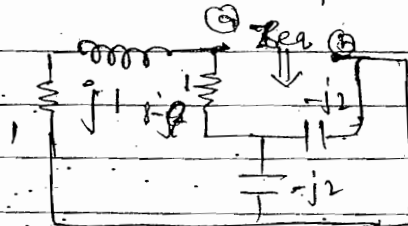
$$Z_{eq} = \frac{(1+j1)(1-j1)}{(1+j1)(1-j1)} = 1+j0$$



for $P_{max} = Z = Z_{eq}^* = 1-j0 = 1 \Omega$

Exap. 4.10

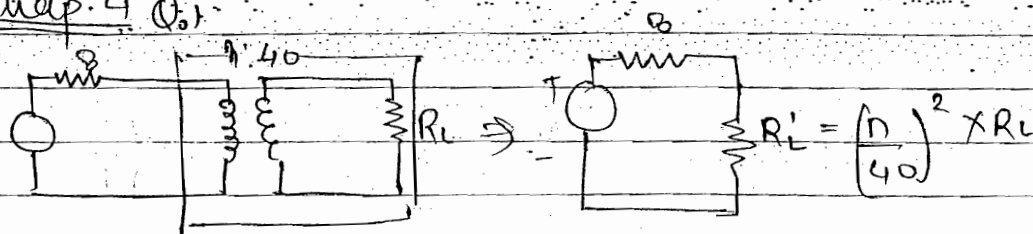


for $P_{max} R_L' = R_s \Rightarrow 8 = \left(\frac{n}{40}\right)^2 \times 2 \quad n = 80 \text{ A}$

Q.20 $R_{eq} = 16 \Omega$

KCL:

$$0.5I_1 + \frac{1-0}{80} + \frac{1-0}{40} + (-I) = 0 \quad \text{--- (1)}$$

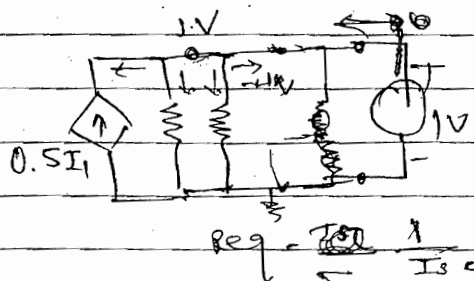
$$I_1 = \frac{1-0}{40} \quad \text{--- (2)}$$



for $P_{max}: R_L = R_{eq} = 16 \Omega$

$$P_{avg} = \frac{1}{T} = R_{eq} = \frac{1}{R} \text{ A}$$


Q.40

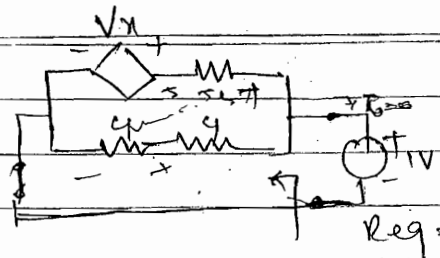

$R_{eq} = 4\Omega$
for $P_{max} \Rightarrow R_L = R_{eq} = 4\Omega$

$R_{eq} = \frac{1}{5}$


Q.44

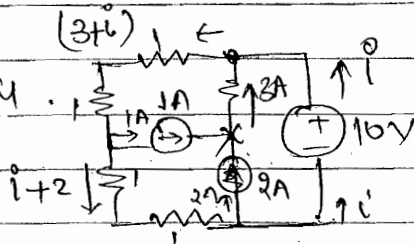

KVL $\Rightarrow 10 = 2(3+i) + 2(i+2)$
 $i = 0$ Amp.


Power delivered $= 10 \times i = 10 \times 0 = 0W$

Q.46

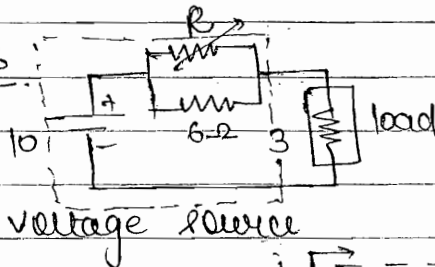


$R_L = R_s$ is NOT applicable
 $R_s = 0$ for $P_{max} \Rightarrow R = 0$

Q.48

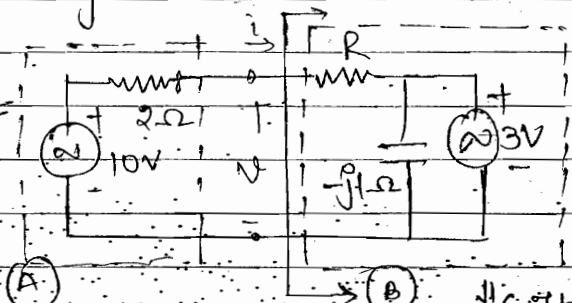

$P = Vi$
 $\frac{\partial P}{\partial R} = 0$ Find R

$i = 0$ O.C $V_{oc} = 3V$ $R_{eq} = R$

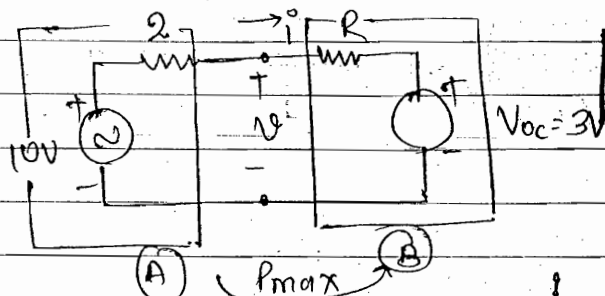

$i = \frac{10-3}{R+2}$; $V = iR + 3$
 $V = \frac{7R+3}{R+2} = \frac{7R+3R+6}{R+2}$
 $= \frac{10R+6}{R+2}$

$P = Vi = \frac{(10R+6) \times 7}{(R+2)^2}$

$\frac{\partial P}{\partial R} = 0 \Rightarrow R = 0.8\Omega$

• Tellegen's Theorem:-

In any N/w total instantaneous power absorbed by various element in different branches of N/w is always equal to zero.

In any N/w total instantaneous power delivered by various voltage and current sources is always equal to total instantaneous power absorbed by various passive element in different branches of N/w.

$$\sum_{n=1}^b V_k \cdot i_k = 0$$

b = no. of Branch.

V_k = Branch voltages


i_k = Branch currents


The theorem is always applicable irrespective of


- (i) Shape of N/w.
- (ii) Type of element contains.
- (iii) Value of each element.

This theorem is always valid so long as the KVL & KCL eqⁿ are applicable to the given N/w.

• Convention:-

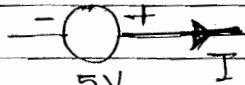
⊖  Power delivered = $5 \times I = 5I$

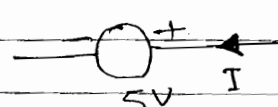⊖  Power absorbed = $V \times I$

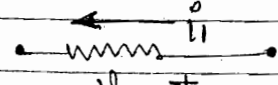✓  Power absorbed = $V_1 \times I_1$

Q In the circuit shown. Find the missing voltages and Branch current. Find instantaneous power absorbed by each element in the N/w. Hence calculate total power absorbed by various element in the given N/w.

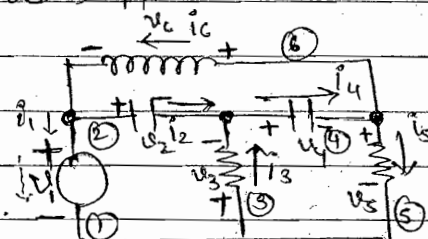Solution Given. $V_1 = 4V$ $i_1 = 2A$
 $V_2 = 2V$ $i_2 = 4A$
 $V_4 = 3V$ $i_6 = 4A$



Take randomly the direction of current.

KVL: ① $-V_1 + V_2 - V_3 = 0$

$-4 + 2 - V_3 = 0$ $V_3 = -2V$

② $-2V + V_5 + V_4 = 0$

$-2 + V_5 + 3 = 0$ $V_5 = -1V$

③ $V_2 + V_6 + V_4 = 0$

$V_6 = -5V$

KCL $i_1 + i_2 - i_6 = 0$

$i_2 = 2A$

$i_2 + i_3 - i_4 = 0$

$i_4 = +6A$

$i_4 - i_5 - i_6 = 0$

$i_5 = 2A$

	1	2	3	4	5	6
V_k	4	2	-2	3	-1	-5
i_k	2	2	4	6	2	4
$V_k i_k$	8	4	-8	18	-2	-20
	A	A	D	D	D	D

$\sum_{k=1}^6 V_k i_k = 30 - 30 = 0$ Ans.

A → absorbed D → delivered

Reciprocity Theorem:

In a linear Bilateral single source N/w the ratio of excitation to response is constant when the positions of the excitation and response are interchanged.

(i) In verifying this theorem the basic configuration of the N/w remains same, only the external conditions are changed.

(ii) The Theorem is not applicable for the N/w containing

- (a) Non-linear elements
- (b) Unilateral elements such as p-n junction diode.
- (c) Multiple independent or dependent voltage and current source.
- (d) A single dependent voltage and current source.

• The basis of Theorem is $\rightarrow$ symmetry of the Impedance and admittance matrix.


Impedance Matrix $[Z] = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix}$; $\begin{cases} Z_{12} = Z_{21} \\ Z_{31} = Z_{13} \\ Z_{23} = Z_{32} \end{cases}$

Reciprocity Theorem

is applicable


for any Reciprocal N/w

Case 1:

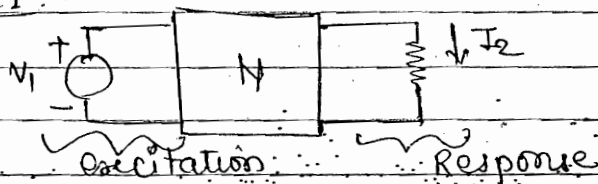

$$\frac{\text{Excitation}}{\text{Response}} = \frac{V_1}{I_2} = Z_{12}$$

Case 2:

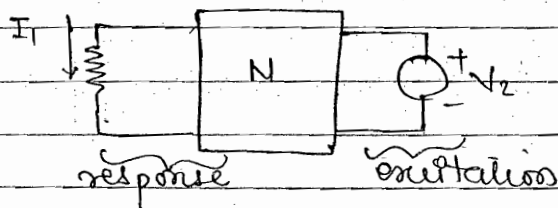


$$\frac{\text{Excitation}}{\text{Response}} = \frac{V_2}{I_1} = Z_{21}$$

$Z_{12} = Z_{21}$	for reciprocal N/w
$\frac{V_1}{I_2} = \frac{V_2}{I_1}$	

Reciprocity theorem is applicable.

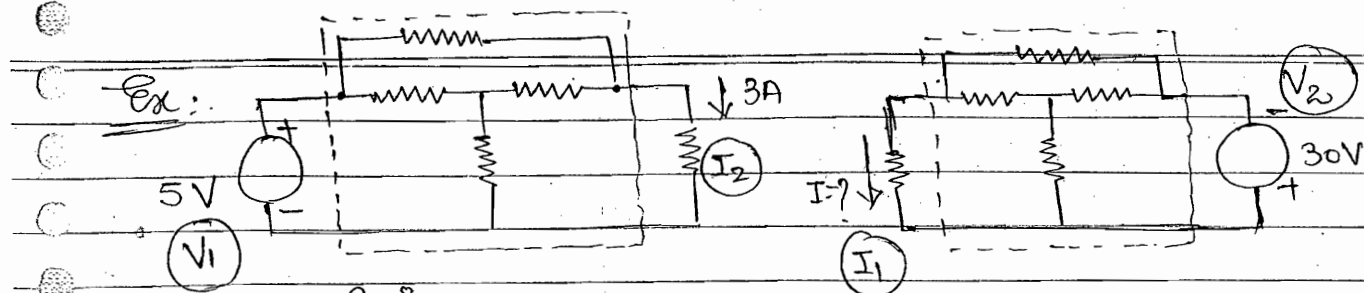- polarity of voltage and current of both N/w must same.




--- Bridged-T-Network.

Solution $Z_{12} = Z_{21}$; $5 \equiv \frac{V_1}{I_2} = \frac{V_2}{I_1} = -30$ $I = -18A$


- Millman's Theorem:

$$E = \frac{\sum E_i Y_i}{\sum Y_i}$$

$$Z = \frac{1}{\sum Y_i}$$



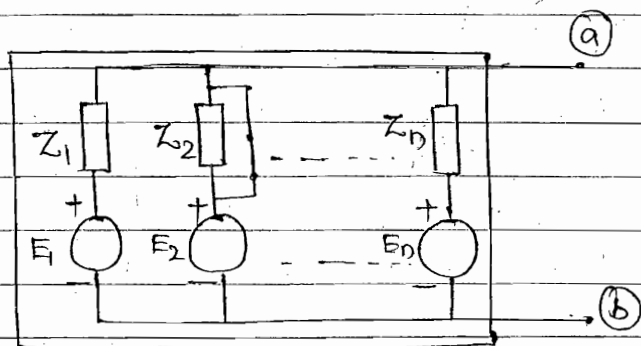


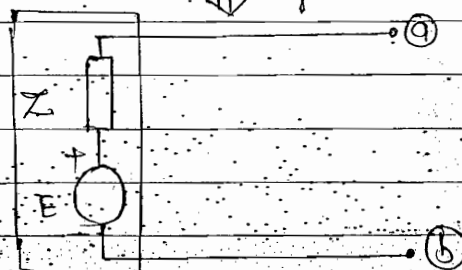Suppose $Z_2 = 0$, then voltage across a, b terminal is E_2 and value of current will be E_2 / time .




- The Theorem is an extension of the thevenin's theorem and is useful whenever there are large no. of voltage sources in any given N/w.
- The Theorem is applicable only when any given N/w can be rearranged in the standard format.
- Dual Millman's Theorem:
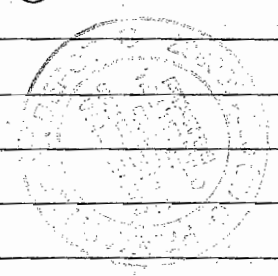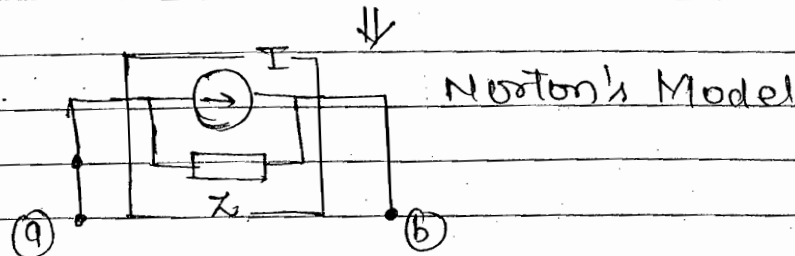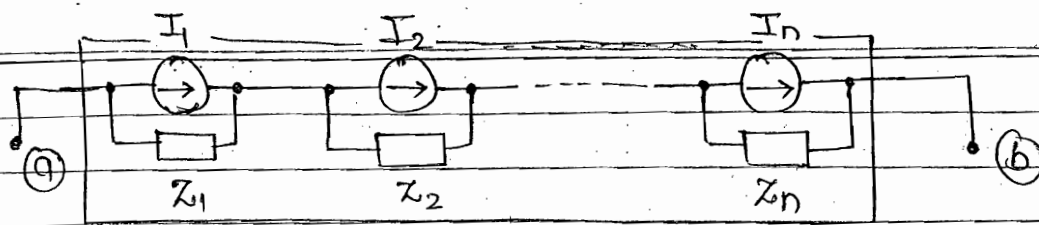
$$I = \frac{\sum I_i Z_i}{\sum Z_i} \quad Z = \sum Z_i$$





- This theorem is an extension of the Norton's theorem and is useful whenever there are large No. of current source in the N/w.
- The theorem is applicable only when any given N/w can be re-arranged in the standard format.

Chap. 2 Q.6

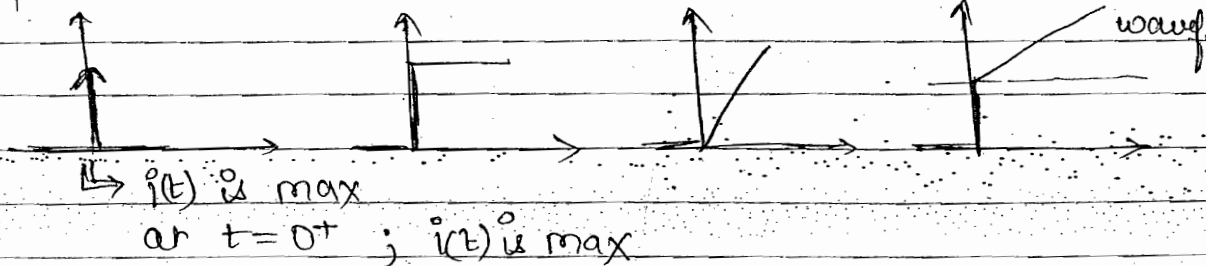

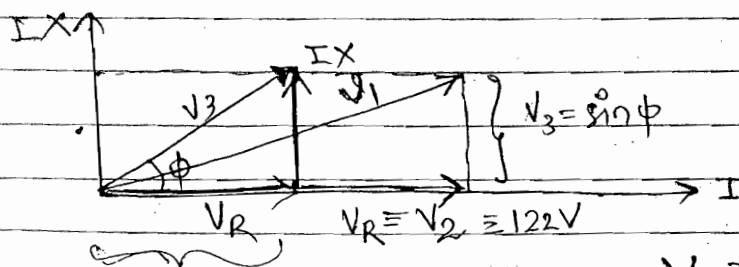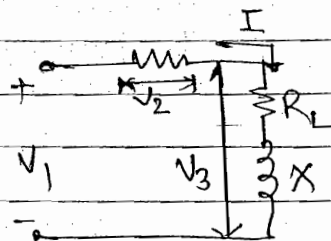Chap 1 Q.52 $N_1 = 220V$ $V_2 = 122V$
 $V_3 = 136V$



$$V_1 = \sqrt{(V_3 \cos \phi + V_2)^2 + (V_3 \sin \phi)^2}$$

$$N_R = V_3 \times \cos \phi \quad V_1^2 = V_3^2 \cos^2 \phi + V_2^2 + 2V_3 V_2 \cos \phi + V_3^2 \sin^2 \phi$$


$$220^2 = 136^2 + 122^2 + 2 \times 136 \times 122 \cos \phi + 136^2$$

$$\cos \phi = 0.45$$


Q.3
(ii)

$$P_L = \frac{V_{RL}^2}{R_L} = \frac{(V_3 \cos \phi)^2}{R_L} = 450 \text{ W}$$


Q.50

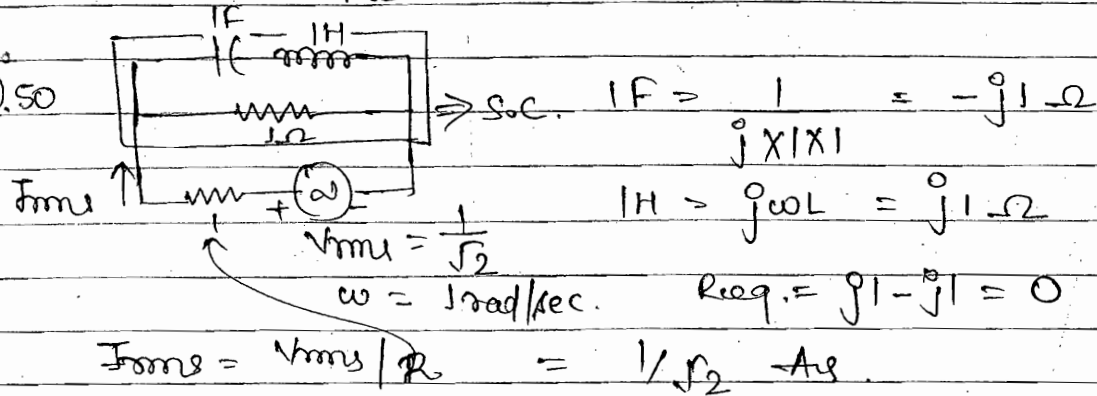

Q.41

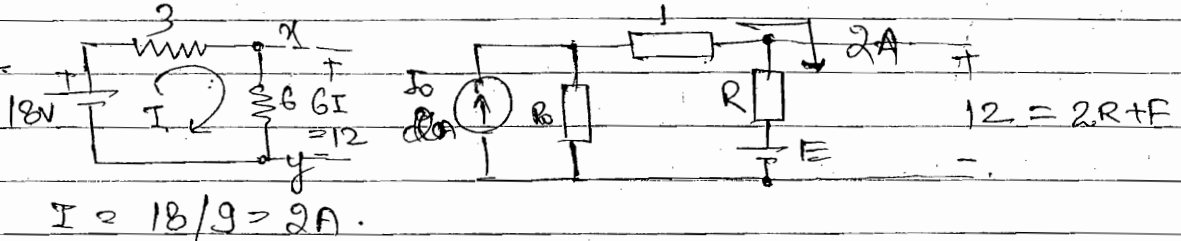

Q.40

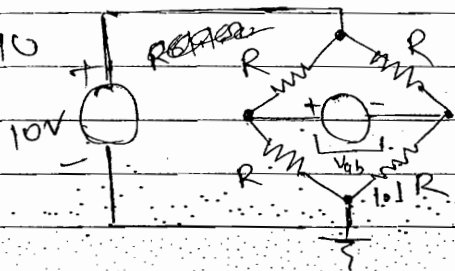

$$V_{ab} = V_a - V_b = 5 - \frac{1 \cdot 1R}{1.1R + R} \times 10 = -0.238 \text{ V}$$

Given: Any Network in Mathematical form

To find:-

1. Shape of Network


Foster's form

Cauer's form

2. Type of Element

- LC
- RC
- RL
- RLC

3. Value of each element.

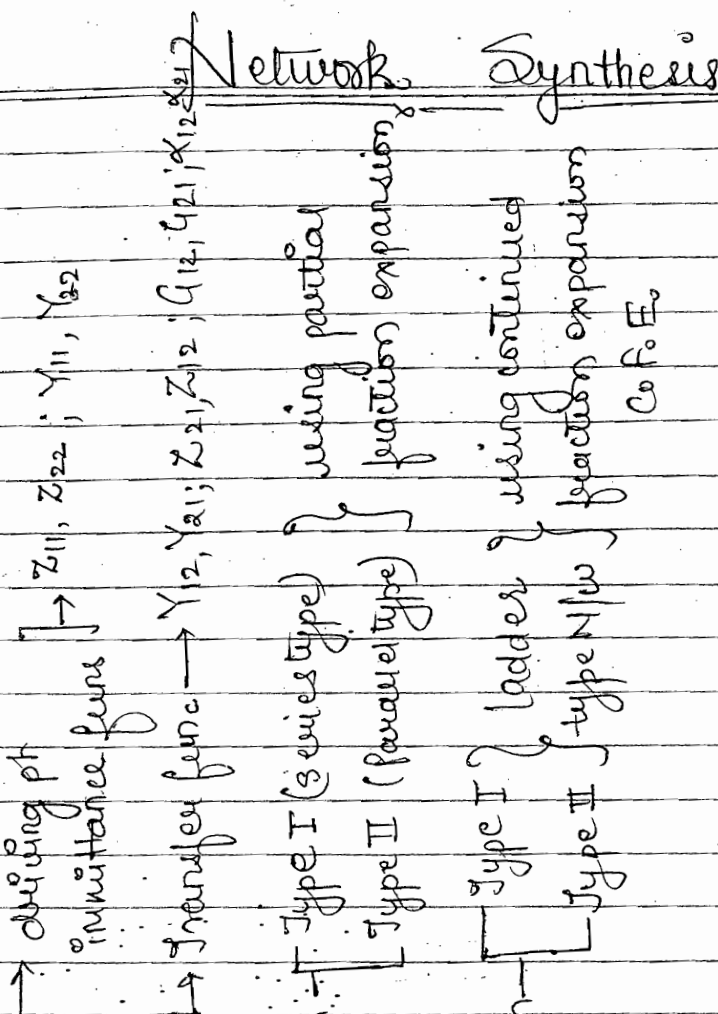


Network Synthesis

• Conditions for a Network to be:-

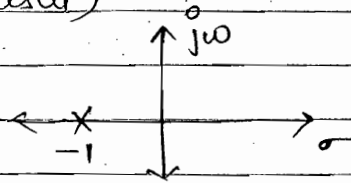1. Physically realizable (causal)
2. Stable

$$\frac{1}{s+1} \longrightarrow \underbrace{e^{-t} u(t)}$$



$$= 0; t < 0$$

$$= e^{-t}; t > 0$$

• For any network, to be a stable N/w following condition must be satisfied.

Condition 1. The N/w functⁿ $F(s)$ can't have poles in RHP.

Condition 2. The N/w functⁿ can't have multiple poles along the $j\omega$ axis including the origin.

Condition 3. The degree of ^{Numerator} of the N/w $F(s)$ can't exceed the degree of denominator by more than unity.

ex:- $\frac{s^2+s+1}{s^2+2s+1}$ ✓, $\frac{s+1}{s^2+2s+1}$ ✓, $\frac{s^3+2s^2+s+1}{s^2+s+1}$ ✓

$\frac{s^4+...}{s^2+...}$ ✗

• For a physically realizable functⁿ o/p can't exist before the i/p applied.

• For a stable N/w the response must be finite for finite excitation.

• Any functⁿ $F(s)$ with poles in LHP has inverse laplace form which is zero for $t < 0$.

• Stability Implies Causality. Therefore any stable N/w is always a physically realizable N/w. But the reverse may not be true. Hence any physically realizable N/w may or may not be stable N/w.

Hurwitz polynomial $P(s)$:-

Network functⁿ $F(s) = \frac{\text{Num poly}}{\text{Denom. poly } P(s)}$

must Be Hurwitz

all poles of $F(s)$ lie in L.H.P.

N/w must Be stable

N/w must also be physically realizable

features:

$$P(s) = \underbrace{s^6 + 4s^4 + 3s^2 + 9}_{\text{Even parts}} + \underbrace{2s^5 + 2s^3 + 5s}_{\text{odd parts}}$$

$$P_e(s) = s^6 + 4s^4 + 3s^2 + 9$$

$$P_o(s) = 2s^5 + 2s^3 + 5s$$

C.F.E. of $\frac{P_e(s)}{P_o(s)}$ has all the

quotient terms

Divisor Divident (Quotient)

$P(s) = P_1(s) \cdot P_2(s) \dots$ Both P_1 & P_2 must Hurwitz. Remainder

$\Rightarrow$ Any poly, Even or odd $\rightarrow$ all roots lie will at imag. axis.

$\rightarrow$ If odd. poly is not given. then diff. even. poly and find C.F.E. $\frac{P_e(s)}{P_o(s)}$

$\Rightarrow$ Numerical value of Quotient represent RLC element value.

(1) If s is real then $P(s)$ is also real

(2) All the coefficients of the Hurwitz poly must Be real and +ve.

(3) NO term must Be missing in the hurwitz poly unless all the even parts or all the odd parts are missing.

C.F.E.: Contin. funct exp. are the ratio of even to odd part or odd to even part. has all the quotient terms.

- The quotient terms of the continued fra. exp. represent the numerical values of RLC components of the N/w.
- If any poly is either even or odd then it is Hurwitz if the continued fraction exp. of the ratio of $P(s)/P'(s)$ has all the quotient terms.
- If the given poly. is either even or odd then all its roots lie along the jw axis only.
- If $P(s) = P_1(s) \cdot P_2(s)$ then poly. $P(s)$ is Hurwitz if the two poly. $P_1(s)$ and $P_2(s)$ are separately Hurwitz.
- The Hurwitz poly. represents the denominator poly. of a stable and physically realizable N/w. This poly. ensures all the poles of the N/w functions lie in LHP. This poly. also ensures no multiple poles exist along the jw axis including the origin.

Ex: Find whether following poly. is Hurwitz or not
 or Find whether or not following poly. represents the denominator poly. of a stable and physically realizable N/w.

Solution: $P(s) = s^4 + s^3 + 5s^2 + 3s + 4$

$$P_e(s) = s^4 + 5s^2 + 4$$

$$P_o(s) = s^3 + 3s$$

$$\begin{array}{r} s^3 + 3s \overline{) s^4 + 5s^2 + 4} \quad (s \leftarrow \\ \underline{-(s^4 + 3s^2)} \\ 2s^2 + 4 \end{array}$$

$$2s^2 + 4 \overline{) s^3 + 3s} \quad (s/2 \leftarrow$$

$$\underline{-(s^3 + 2s)} \\ 2s$$

$$s \overline{) 2s^2 + 4} \quad (2s \leftarrow$$

$$\underline{-(2s^2)} \\ 4$$

$$4 \overline{) s} \quad (s/4 \leftarrow$$

$$\underline{-(s/4)} \\ \times$$

$$CFE = \frac{P_e(s)}{P_o(s)}$$

$$= s + \frac{1}{2}$$

$$\begin{array}{c} \frac{s}{2} + \frac{1}{2s + \frac{1}{s/4}} \\ \uparrow \quad \uparrow \quad \uparrow \\ \text{+ve quotient terms} \end{array}$$

+ve quotient terms.

+ve quotient terms

$\Rightarrow P(s)$ is Hurwitz

ex: - $P(s) = s^4 + 4 \rightarrow s^2$ (even part) is missing.

✓ given poly. is not hermitz.

✗ poles: $s^4 + 4 = 0 \quad s = \pm j\sqrt{2}, \pm j\sqrt{2}$.

• multiple poles along jw axis.

Ex $P(s) = s^3 + 2s^2 + 3s + 6$

$P_e(s) = 2s^2 + 6$

$P_o(s) = s^3 + 3s$

CFE of $\frac{P_o(s)}{P_e(s)} = \frac{2s^2+6}{s^3+3s} \cdot \frac{s}{s/2}$

$\frac{s^3+3s}{s^3+3s}$

x x CFE has been terminated abruptly.

$\Rightarrow 2s^2+6$ or s^3+3s is one factor of $P(s)$.

for s^3+3s is a factor of $P(s)$ $P_1(s) = s^3+3s$

To find second factor of $P(s)$

$P(s) = \underbrace{P_1(s)}_{s^3+3s} \cdot P_2(s)$

$P_2(s) = \frac{P(s)}{P_1(s)} = \frac{s^3+2s^2+3s+6}{s^3+3s} = 1 + \frac{2s^2+6}{s^3+3s}$

$\frac{2s^2+6}{s^3+3s} = \frac{2s^2+6}{s(s^2+3)} = \frac{2s^2+6}{s(s^2+3)} = 1 + \frac{1}{s/2}$

$P(s) = P_1(s) \cdot P_2(s)$

$\frac{s^3+3s}{s^3+3s} \cdot \frac{1 + \frac{1}{s/2}}{s/2}$ Hermitz

$s(s^2+3)$

Poles: $s=0, \pm j\sqrt{3}$

also Hermitz

Both $P_1(s)$ and $P_2(s)$ hermitz

$\therefore P(s)$ is hermitz.

- PRE Positive Real functⁿ

$F(s)$

Z_{11}, Z_{22}

Y_{11}, Y_{22}

driving pt immittⁿ functⁿ

~~$Z_{12}, Z_{21}, Y_{12}, Y_{21}$~~

~~$G_{12}, G_{21}, \alpha_{12}, \alpha_{21}$~~

Transfer function

- +ve real function represent stable and physically realizable passive driving point immittance functⁿ.
- Definition of PRE $F(s)$:-

PRE if $\boxed{\operatorname{Re}[F(s)]_{s=j\omega} \geq 0}$

Any function $F(s)$ is said to be

for all ω .

$\frac{Z_{11}}{s + j\omega}$
must be zero

Features: (i) if $F(s)$ is PRE then $\frac{1}{F(s)}$ is also a PRE

$F(s) \mid \frac{1}{F(s)}$

(ii) The sum of two +ve Real function is also a PRE
 $F_1(s) + F_2(s)$ (can be use as series)

(iii) All the poles and zeros lie in LHP or along the $j\omega$ axis. All the poles and zeros either lie along the real axis or occur in complex conjugate pairs

(iv) All the poles along the $j\omega$ axis are simple including a origin.

(v) The degree of Numerator cannot exceed the degree of denominator By more than unity.

(vi) The lowest power of s of the Numerator poly. can't exceed the lowest power of s of the denominator poly. By more than unity

The necessary condition and sufficient condition

for any functⁿ $F(s)$ to be a true real functⁿ are: -

(i) the poles and zeros lie in LHP. Therefore all the poles and zeros Numerator and denominator poly must be Hurwitz.

(ii) The poles along $j\omega$ axis have +ve and real residues

This is verify by making partial fractⁿ expansion and checking the residues of only those poles which lie along the $j\omega$ axis only.

(iii) $\boxed{\operatorname{Re} [F(s)]_{s=j\omega} \geq 0}$ for all ω .

⑥ SYNTHESIS OF ELECTRICAL NETWORKS- CONTAINING SPECIFIED ELEMENTS: -

Case 1: Driving pt. i.c. Impedance functⁿ $Z_{LC}; Y_{LC}$.

features: (1) These Impedance functⁿ represent the ratio of even to odd or odd to even poly.

(2) All the poles and zeros are simple, lie along $j\omega$ axis only and they alternate

(3) There must be either a zero or a pole at the origin or at infinity.

(4) The degree of Numerator poly cannot exceed degree of denominator By more than unity.

(5) The lowest power of s of the Numerator poly and of denominator poly cannot having difference or more than unity.


✓ By for conventⁿ all ⑤ condition check

Q Find wheather or not following functⁿ are physically physically realizable and stable LC driving point admittance functⁿ.

eg: $F_1(s) = \frac{s(s^2+4)}{(s^2+1)(s^2+3)}$ Zero: $s=0; \pm j2$
Poles: $s = \pm j1, \pm j\sqrt{3}$

poles and zero are not alternate.

No can't realized.

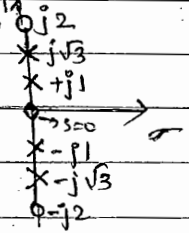

$F_2(s) = \frac{s^5+4s^3+s}{3s^4+6s^2} = \frac{s(s^4+4s^2+1)}{3s^2(s^2+2)}$

$\frac{s^5+4s^3+s}{3s^4+6s^2} \xrightarrow{\text{so missing}} \frac{s^2(3s^2+6)}{s^2(3s^2+6)}$

s^0 term is missing. Double poles at origin. NO

$F_3(s) = \frac{2(s^2+1)(s^2+9)}{(s^2+4)s}$ Zero: $s = \pm j\sqrt{1}, \pm j3$

Poles: $s = 0, \pm j2$

Yes

case2 Driving point RC Impedance functⁿ RL Admitt. functⁿ

case2 Driving point RC Impedance functⁿ RL Admittance functⁿ $Z_{RC}; Y_{RL}$

features (1) all the poles and zero lie along -ve real axis and they alternate.

(2) The singularity nearest to or at the origin must be a pole whereas the singularity nearest to or at infinity must be zero


(3) The residues of the pole must be real and +ve

Q Find wheather following functⁿ represent physically realizable and stable driving point RL impedance functⁿ or RL C admittance functⁿ

$$F_1(s) = \frac{(s+1)(s+4)(s+8)}{s(s+2)(s+6)}$$

Zero: $s = -1, -4, -8$
 Poles: $s = 0, -2, -6$
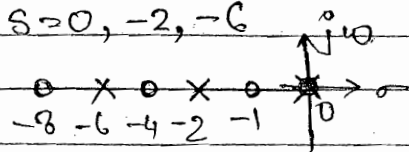
$$\frac{(s+1)(s+4)(s+8)}{s(s+2)(s+6)} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+6}$$



$$(s+1)(s+4)(s+8) = A(s+2)(s+6) + B(s)(s+6) + C(s)(s+2)$$

at $s=0$

$$F_1(s) \neq \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+6}$$

Partial only possible when power of Num is less than den.

Yes

$$F_2(s) = \frac{(s+1)(s+8)}{(s+2)(s+4)}$$

zeros: $s = -1, -8$
 poles: $s = -2, -4$

Poles and zeros do not alternate
 nearest to origin is not pole.

NO

$$F_3(s) = \frac{(s+1)(s+2)}{s(s+3)}$$

Zeros: $s = -1, -2$
 Poles: $s = 0, -3$

Poles and zeros are not alternate
 Nearest to infinity is not a zero.

NO

Case 3: Driving point RL impedance function or RC Admittance function. Z_{RL} ; Y_{RC}

features: (1) all the poles and zeros lie along the -ve real axis and they alternate.

(2) The singularity nearest to or at the origin must be a zero. whereas the singularity nearest to ∞ must be pole.

(3) The residues of the pole must be real and -ve

Q Find whether following function represents physically realizable and stable driving pt RLC impedance function or RC admittance function.

Soln $F_1(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$ Zero: $s = -1, -3$
 poles: $s = -2, -6$
 Scale factor. Yes

Due to scale factor No change in shape, only magnitude of amplitude get change.

$F_2(s) = \frac{4(s+1)(s+2)}{(s+3)(s+4)}$ poles and zeros are not alternate No

Case 4:- Driving pt RLC Impedance function Z_{RLC} ; Features (1) the driving point RLC impedance function do not follow any set rule on the location of the poles and zeros and therefore, these can lie any where in LHP.

Q Following function represents pure RLC driving pt Impedance function. Realise it in Cauer's type I form

$Z_{RLC}(s) \equiv Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$ Cauer's Type I.

Zeros: $s = \frac{-2 \pm \sqrt{4 - 4 \times 2 \times 1}}{2} = \frac{-2 \pm j2}{2} = -1 \pm j1$ (ladder type)

Poles: $s = \frac{-1 \pm \sqrt{1 - 4 \times 1 \times 1}}{2} = \frac{-1 \pm j\sqrt{3}}{2} = -0.5 \pm j0.866$

Cauer's type I → Inductor → Series } always.
Capacitor → parallel }

Cauer's type II → Capacitor → series } always.
Inductor → parallel }


CFE of $\frac{s^2+2s+2}{s^2+s+1}$ $\frac{s^2+s+1}{s^2+s+1}$ $\frac{s^2+2s+2}{s^2+s+1}$ (1 ← Z_1 (series))

$Z_1 = 1 = R_1$; $R_1 = 1 \Omega$ (series)

$Y_2 = s = sC_2$; $C_2 = 1F$ (parallel)

$Z_3 = s = sL_3$; $L_3 = 1H$ (series)

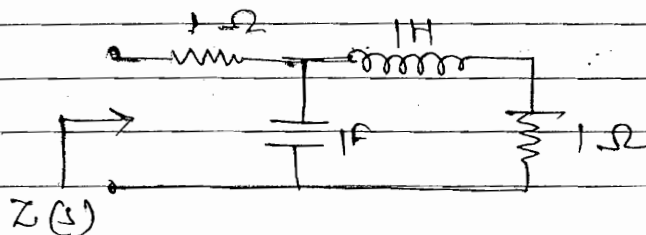$Y_4 = 1 = R_4$; $R_4 = 1 \Omega$ (parallel)



Cauer's type - I
ladder R/L/C.

• $\frac{s^2+2s+2}{s^2+s+1} \equiv 1 = R$; $R_1 = 1 \Omega$ (series)

$\frac{s^3+2s^2+2s}{s^2+s+1} \equiv s = sL$; $L_1 = 1H$ (series)

$\frac{s^4+2s^3+2s^2}{s^2+s+1} = s^2$ X

Cauer's - I
CFE of $\frac{s^2+2s+1}{s^2+s+1}$

Cauer's - II
CFE of $\frac{s^2+2s+1}{1+s+s^2}$

Reverse order of (I).

- If the given function is an Impedance function, then the first element in Cauer's N/w represents an Impedance element and is a series element.

By obtaining $\frac{s^2+1}{s^2+4s}$ finite 2 pole 2 zero so $\rightarrow$ 4 element only for RLC

- In general the total NO. of elements for RLC N/w in the Cauer's form is equal to the algebraic sum of No. finite zeros and poles.
- In Cauer's type 1 form capacitor is always a shunt element whereas inductor is always a series element. In Cauer's type 2 N/w the inductor is always in parallel element whereas capacitor is always series element.
- In Cauer's type 1 N/w continued fraction expansion is found by arranging the Numerator and Denominator polynomials in descending powers of s . In Cauer's type 2 form the continued fraction expansion is found by rearranging Numerator and Denominator polynomials in ascending powers of s .
- For any immittance function Cauer's type 1 and type 2 N/w are purely independent of each other.

The following function represents physically realizable and stable LC driving point immittance function. Because it is Foster's type 1 and type 2 form.

$$F(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+4)}$$

----- Foster's type 1 (series form)
 ----- Foster's type 2 (parallel form)

$$F(s) = \frac{2s^4 + 20s^2 + 18}{s^3 + 4s}$$

As degree of Numerator > degree of denominator

$$\begin{array}{r} s^3 + 4s \quad 2s^4 + 20s^2 + 12 \quad (2s) \\ - 2s^4 \pm 8s^2 \\ \hline 12s^2 + 12 \end{array}$$

$$F(s) = \frac{2s^4 + 20s^2 + 12}{s^3 + s} = 2s + \frac{12s^2 + 12}{s(s^2 + 4)}$$

$$\frac{A}{s} + \frac{Bs + C}{s^2 + 4}$$

$$\therefore A = 9/2 ; B = 15/2 ; C = 0$$

$$F(s) = 2s + \frac{9/2}{s} + \frac{(15/2)s}{s^2 + 4}$$

Case I:- Foster's type I - series form $\boxed{Z(s) = Z(s)}$

$$Z(s) = 2s + \frac{9/2}{s} + \frac{(15/2)s}{s^2 + 4}$$

$$= Z_1 \quad Z_2 \quad Z_3$$

$$\bullet Z_1 = 2s = s L_1 ; L_1 = 1H \quad \leftarrow$$


$$\bullet Z_2 = \frac{9/2}{s} = \frac{9}{(2/9)s} ; C_2 = \frac{2}{9} F \quad \leftarrow$$

$$\bullet Z_3 = \frac{(15/2)s}{s^2 + 4} = \frac{1}{Y_3} ; Y_3 = \frac{s^2 + 4}{(15/2)s} = \frac{s}{15/2} + \frac{8}{15s}$$

$$= Y_3' + Y_3''$$

$$Y_3' = \frac{2}{15} s = ; C_3 = \frac{2}{15} F \quad \leftarrow$$
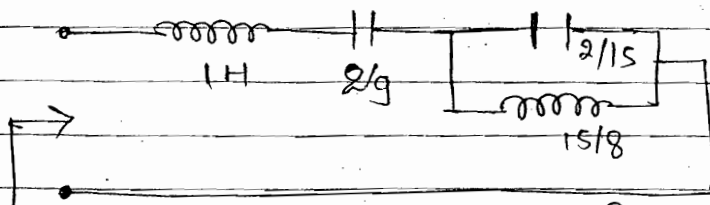
$$Y_3'' = \frac{8}{15s} = ; L_3 = \frac{15}{8} H$$



$$F(s) = Z(s)$$

Foster's type I N/w,
series form N/w

Case 2 Foster's Type 2 Parallel form: $F(s) \equiv Y(s)$

$$F(s) = 2s + \frac{9/2}{s} + \frac{(15/2)s}{s^2 + 4}$$

$$= Y_1 + Y_2 + Y_3$$


$$Y_1 = 2s \equiv sC_1 = 2F \leftarrow$$

$$Y_2 = \frac{9/2}{s} \equiv \frac{1}{sL_2} = \frac{2}{9}H \leftarrow$$

$$Y_3 = \frac{(15/2)s}{s^2 + 4} \equiv \frac{1}{Z_3} ; Z_3 = \frac{s^2 + 4}{(15/2)s} = \frac{2s}{15} + \frac{8}{15s}$$

$$Z'_1 = \frac{2s}{15} = sL_3 ; L_3 = \frac{2}{15}H$$
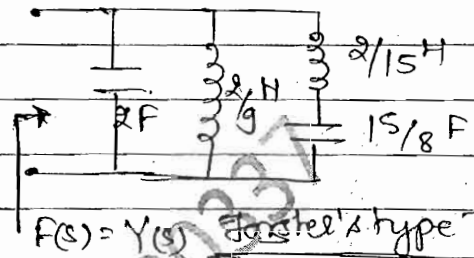
$$Z'' = \frac{8}{15s} = \frac{1}{sC_3} ; C_3 = \frac{15}{8}F$$



Foster's Type I $\xleftrightarrow[\text{N/w.}]{\text{dual}}$ Foster's Type II

Comment: The Foster's type 1 and Foster's type 2 N/w represent the dual N/w. These two N/w are NOT the equivalent N/w. and therefore the Foster's type 1 N/w cannot be replaced by Type 2 N/w.


Duality Between 2 Network:-

N₁: (series RLC CRF)

KVL

$$v(t) = Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int i dt$$


(1)

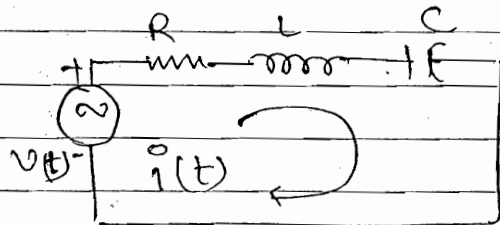

N_2 : (Parallel RLC ckt) dual N/w.

KCL:
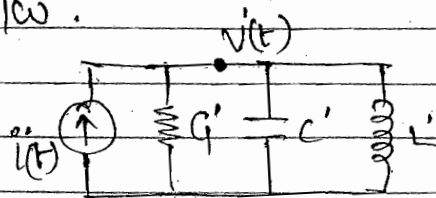
$$i(t) = v(t)G' + c' \frac{dv(t)}{dt} + \frac{1}{L} \int_0^t v(t) dt$$




(2)

N_1	dual N/w	N_2
$v(t)$	$i(t)$	
$i(t)$	$v(t)$	
Series circuit	parallel circuit	
loop	Node	
KVL	KCL	
R	G	
L	C	
C	L	
Voltage source	Current source	


Comment: (1) The N/w N_1 and the N_2 are dual of each other. These two N/w are not the equivalent N/w's and therefore the N/w N_1 cannot be replaced by its dual N/w N_2 and vice-versa.

(2) If we know the response of any N/w in terms of current variable for specified excitatⁿ then we can write the response of its dual N/w in terms of voltage variable for similar excitatⁿ directly by inspection without actually solving it using a transformⁿ shown in Table.

Ex.

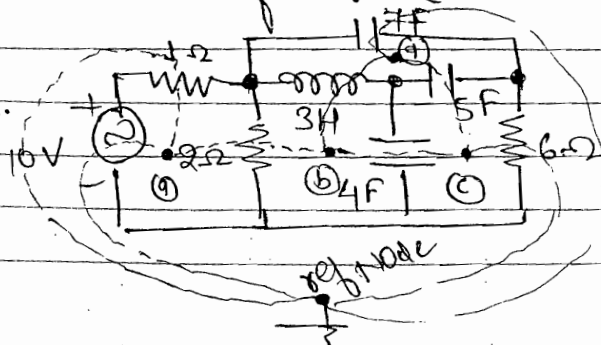


To find :- dual N/w

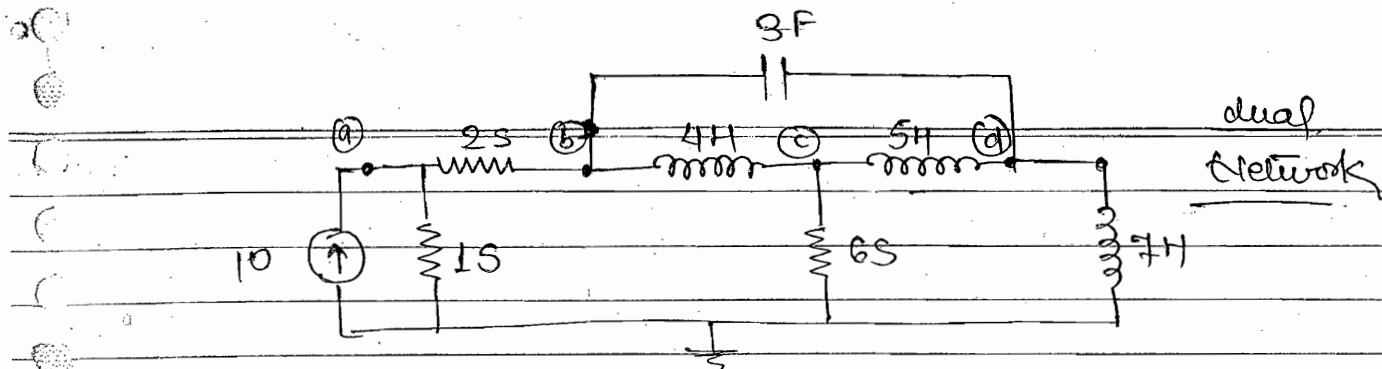

→ Numerical values remain same.

Chapter → 6.

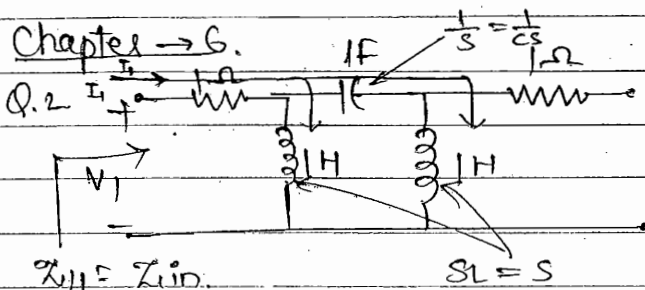


$$Z_{in} = 1 + s \times \frac{1}{s} \times sL$$

$$= 1 + \frac{s \times (1 + sL)}{s}$$

$$= 1 + \frac{s \times (\frac{1}{s} + s)}{s}$$

$$= \frac{s^3 + 2s^2 + s + 1}{2s^2 + 1}$$

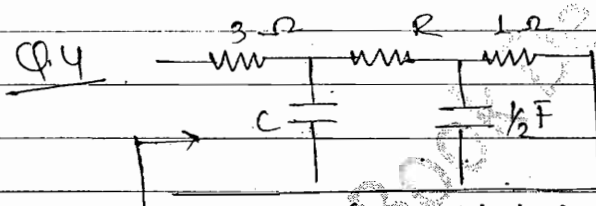∴ Inductor → parallel
∴ Capacitor → series } Cauer's type 2.



at $s=0$ $Cap = \frac{0 \times C}{0 + 1} = 0$

$$Z(0) \Rightarrow 3 + 1 + 1 = 3(0 + 0 + 3)$$

$$0 + 0 + 3 = 3$$


$$= 21 \Omega$$

$$Z(s) = \frac{3(s^2 + 6s + 3)}{s^2 + 4s + 3}$$

also $C = s \times C$... C cannot be found ... Cauer's-I.

$$CEE \text{ of } Z = \frac{(3s^2 + 18s + 24)}{s^2 + 4s + 3}$$

Q.5

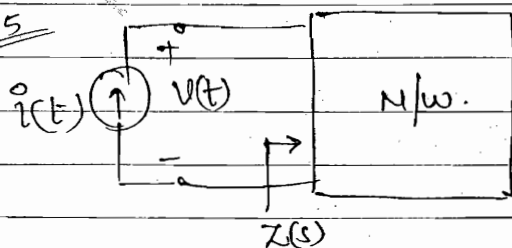


$$i(t) = u(t) \quad I(s) = \frac{1}{s}$$

$$V(t) = 1 + e^{-t/\tau}$$

$$V(s) = \frac{1}{s} + \frac{1}{s + \frac{1}{\tau}}$$

$$\frac{V(s)}{I(s)} = Z(s) = 1 + \frac{s}{s + \frac{1}{\tau}} \equiv Z_1 + Z_2$$
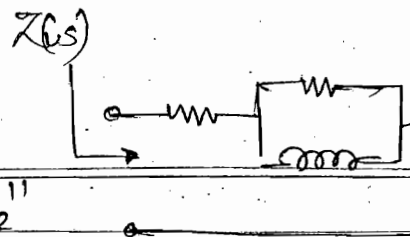
$$= Z_1 = R_1 = 1 \Omega \quad ; \quad Z_2 = R_2 = \tau \Omega$$




$$Y_2 = \frac{1}{Z_2} = 1 + \frac{1}{s\tau} = Y_2' + Y_2''$$

$$Y_2' = 1 = \frac{1}{R_2} \quad \therefore R_2 = 1 \Omega$$

$$Y_2'' = \frac{1}{s\tau} = \frac{1}{sL_2} \quad \therefore L_2 = 1 H$$

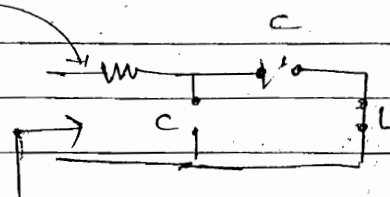Q.8 $s=0$ $C \rightarrow \infty$; $L = sC$


$s=\infty$ $C \rightarrow 0$; $L = \infty$



$$Z(\infty) = 0.75 \Omega$$

$$Z(0) \rightarrow \infty$$

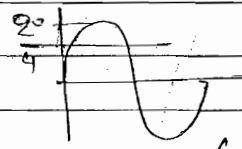$\frac{2}{s}$ cannot take otherwise exceed



$$V_n = \frac{V}{V_n} = \left(\frac{1}{2} \right)$$

① $\rightarrow \frac{1}{s}$; 0.75Ω


By 1. Not possible.

Q.10 $Z(s) = \frac{s+\alpha}{s+\beta} = \frac{V}{I} = \frac{V_{\omega+\alpha}}{I_{\omega+\beta}}$ as 9/10 sines.

V leads I ; $\theta \rightarrow +ve$

$$\theta = \tan^{-1} \omega/\alpha - \tan^{-1} \omega/\beta = +ve$$

$$[\alpha < \beta]$$

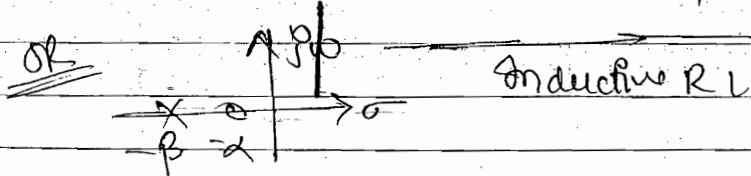

Q.13 $K_{ew} = 60, 20 \Rightarrow s = \pm j20 \pm j60$
 Pole: $\infty, \infty; \therefore s = 0, \pm j40$

$$Z|_{\omega=0} = -j70$$

$$Z(s) = K \frac{(s^2 + 20^2)(s^2 + 60^2)}{s(s^2 + 40^2)}$$

$$\frac{s^4}{s^5} = s \Rightarrow sL$$

Q.15 $\frac{V(s)}{I(s)} = Z(s) = \frac{(s+1)}{(s+\sqrt{2})(s+1/\sqrt{2})}$

$i(t) = \sin t = \text{Im} \sin \omega t$; $s = j\omega$
 $s = j1$

$Z(j\omega) = \frac{j1+1}{(j1+\sqrt{2})(j1+1/\sqrt{2})} = \frac{V}{I} \approx 1$

$|V| = \frac{\sqrt{2}}{(\sqrt{1+2})(\sqrt{1+1/2})} = \frac{2}{3}$

Q.24 $Z_{11} = K_1 \left(\frac{s+3}{s+s} \right)$

$Z_{11} = \frac{R_1 \times (R_2 + sL)}{R_1 + (R_2 + sL)}$

$= \frac{R_1 \times L (R_2/L + s)}{R_1 + L (R_2/L + s)} = \frac{R_1 \cancel{L} (R_2/L + s)}{\cancel{L} (s + \frac{R_1 + R_2}{L})}$

$K_1 = R_1$


$\frac{R_2}{L} = 3$; $\frac{R_1 + R_2}{L} = 8$; $\frac{R_1}{L} = 5$

$Z_{22} = \frac{R_2 \times (sL + R_1)}{R_2 + (sL + R_1)}$

Denominator of Z_{11} and Z_{22} remain same to get direct ans.

$= \frac{R_2 \cancel{L} (R_1/L + s)}{\cancel{L} (\frac{R_1 + R_2}{L} + s)} = K_2 \left(\frac{s+5}{s+8} \right)$

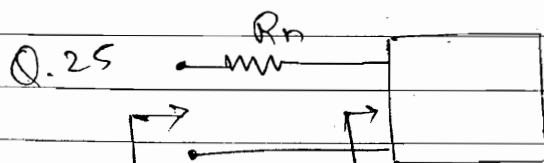$K_2 = R_2$; $\frac{R_1 + R_2}{L} = 8$; $\frac{R_1}{L} = 5$ Ans.



$Z_2 = R_n + Z_1$; $Z_1 = \frac{s+5}{s+8}$ PRF... physically realizable

$$Z_1 = R_n + Z_1$$

$$= R_n + r \pm jx$$

$$\geq 0$$


$$|R_n| \leq r$$

$$|R_n| \leq \operatorname{Re}[Z_1]$$

Q. 29

$$S_L = 2S$$

$$S_L = S$$

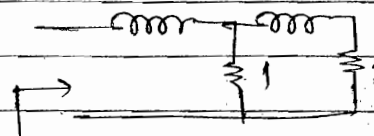

$$S = -2, \infty$$

$$Z(s) = 2s + \frac{1 \times (s+1)}{1+(s+1)}$$

Imp Question (Extra)

Following

Q. Solving function represented physically realizable, stable
of RLC, deriving point impedance function.
Realise it in Foster's type-II N/w.

$$Z(s) = \frac{(s+1)(s+4)}{(s+2)(s+3)} = Z_{RLC}(s)$$

Solution: F.T-2 is parallel N/w. Foster's Type-2.

$$\text{So, } Y(s) = \frac{1}{Z(s)} = \frac{(s+2)(s+3)}{(s+1)(s+4)} = \frac{s^2 + 5s + 6}{s^2 + 5s + 4}$$

$$= 1 + \frac{2}{(s+1)(s+4)} = 1 + \frac{2/3}{s+1} + \frac{-2/3}{s+4}$$

Due to -ve sign we cannot realise.

$\frac{2}{(s+1)(s+4)}$ $\Rightarrow$ difference in degree is also 2

$$Y(s) = \frac{(s+2)(s+3)}{s(s+1)(s+4)} = \frac{3/2}{s} + \frac{-2/3}{s+1} + \frac{1/6}{s+4}$$

$$Y(s) = \frac{3}{2} + \frac{-2/3}{s+1} + \frac{1/6}{s+4}$$

If value of resistance coming -ve $\rightarrow$ stop there $\rightarrow$ Not Realizable

Divide only that term having -ve/ value.


$$Y(s) = \frac{3}{2} - \frac{2}{3} \left[1 - \frac{1}{s+1} \right] + \frac{1}{6} \frac{s}{s+4}$$

$$\begin{array}{r} s+1 \overline{) \frac{s+1}{-s-1}} \\ \hline -1 \end{array}$$

$$Y(s) = \frac{5}{6} + \frac{2/3}{s+1} + \frac{(1/6)s}{s+4}$$


Now all terms become +ve

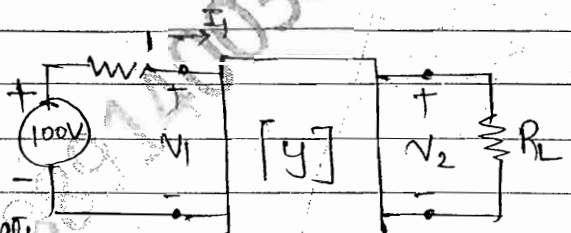Q In the ckt shown find the value of load Resistance R_L for Maximum power transferred. Hence calculate



Maximum power transferred. $[Y] = \begin{bmatrix} 5 & 4 \\ 4 & 5 \end{bmatrix} S$

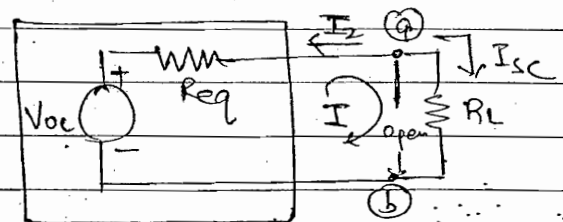Solution: For P_{max} : $R_L = R_{eq}$
 $P_{max} = \frac{V_{oc}^2}{4R_L}$



Thevenin's Model

$$I_1 = 5V_1 + 4V_2 \quad \text{--- (1)}$$

$$I_2 = 4V_1 + 5V_2 \quad \text{--- (2)}$$

$$100 = 1 \times I_1 + V_1 \quad \text{--- (3)}$$

Voc :- $V_2 = V_{oc}$; $I_2 = 0$

$$I_1 = 5V_1 + 4V_{oc} ; 0 = 4V_1 + 5V_{oc} ; 100 = I_1 + V_1$$

find V_{oc}

Isc :- $V_2 = 0$; $I_2 = -I_{sc}$

$$I_1 = 5V_1 + 0 ; -I_{sc} = 4V_1 + 0 ; 100 = I_1 + V_1$$

find I_{sc}

find $R_{eq} = \frac{V_{oc}}{I_{sc}}$


short

$$V_2 = 1V ; 100V = I_{sc}$$

$$R_{eq} = \frac{1}{I_2}$$

$$\begin{cases} I_1 = 5V_1 + 4 \\ I_2 = 4V_1 + 5 \\ 0 = I_1 + V_1 \end{cases} \quad \text{find } R_{eq} = \frac{1}{I_2}$$


Q. To find $G_{21} = \frac{V_2}{V_1}$

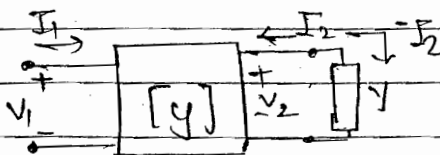

Solution

$$\begin{cases} I_1 = y_{11} V_1 + y_{12} V_2 \\ I_2 = y_{21} V_1 + y_{22} V_2 \\ -I_2 = V_2 Y_L \end{cases} \quad \left. \begin{array}{l} \text{putting value of eq}^{\text{no}} \\ \text{in eqn (2)} \end{array} \right\}$$
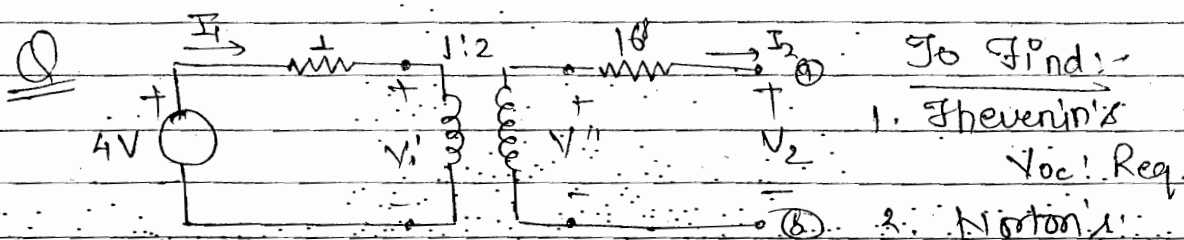
$$\begin{aligned} -V_2 Y_L &= y_{21} V_1 + y_{22} V_2 \\ -y_{21} V_1 &= V_2 (y_{22} + Y_L) \end{aligned} \Rightarrow G_{21} = \frac{V_2}{V_1} = \frac{-y_{21}}{y_{22} + Y_L}$$



Solution

$$\begin{aligned} \textcircled{1} \quad 4 &= I_1 + V' \\ \textcircled{2} \quad V_2 &= -16 I_2 + V'' \end{aligned}$$

$$\textcircled{3} \quad \frac{V'}{V''} = \frac{1}{2}, \quad V'' = 2V'$$

$$\textcircled{4} \quad \frac{I_2}{I_1} = \frac{1}{2}, \quad I_1 = 2I_2$$

V_{oc} : $I_2 = 0$; $V_2 = V_{oc}$

$$V'' = 2V'$$

$$I_1 = 0$$

$$4 = V'$$

$$V_2 = V'' = V_{oc}$$

I_{sc} : $V_2 = 0$; $I_2 = I_{sc}$

$$4 = I_1 + V'$$

$$16 I_{sc} = V''$$

$$2V' = V''$$

$$I_1 = 2 I_{sc}$$

R_{eq} :- $V_2 = 1$ $4V = S.O.C.$

$$R_{eq} = \frac{1}{I_{sc}} = \frac{1}{-I_2}$$

$$0 = I_1 + V'$$

$$V'' = 2V'$$

$$1 = -16 I_2 + V''$$

$$I_1 = 2 I_2$$

$$V_{oc} = 8V \quad R_{eq} = 20\Omega \quad I_{sc} = 2/5A$$

Prakash Book Depot - 9891400337

