

GIOVIND, 2K21/EE/119

NAS
(EE201)

Network and System

Combination


(i) Active and Passive :-

may not require external power source to operate
(Photovoltaic cell, charged inductor)
(current source, diode)

require external power source to drive them.
(Resistance, uncharged inductor and capacitor, transformer)
[power, energy remain constant.]

[Controls flow of electric current]
[transistor, → amplify power of a signal]
de → controlling flow of charge

(ii) Unilateral and bilateral :-

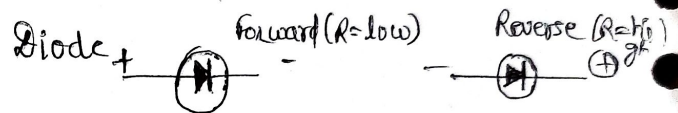

- conduction in single direction
- both direction
- Resistance, capacitor, inductor.
- (Diode)
- Polarity X
- polarity exists (Resistance different for both direction)

(iii) Linear and Non-linear :- A system is linear if it holds

parameters which follow

- superposition
- Homogeneity


$$y_1 = m_1 x + c_1$$

$$y_2 = m_2 x + c_2$$

$$y_1 + y_2 = (m_1 + m_2)x + (c_1 + c_2)$$

y x $\text{Difference } [C \neq (c_1 + c_2)]$
Occurs

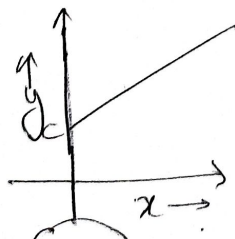Current → not follow vector law of addition



$$\begin{bmatrix} ax_1(t) + bx_2(t) \\ \rightarrow ay_1(t) + by_2(t) \end{bmatrix} \quad \begin{bmatrix} x_1(t) + x_2(t) \\ \rightarrow y_1(t) + y_2(t) \end{bmatrix}$$

Note :-
Linear,

$$x(t) = 0 \rightarrow y(t) = 0$$

$$x(n) = 0 \rightarrow y(n) = 0$$

(iv) Lumped and Distributed:-

Parameter which can't be separated and confined at one place.

change with dimension of element
Ex: Resistance of transmission line.


[V, I $\rightarrow$ vary x with dimension]
through element
Ex: Resistance in electrical circuit.

Note:
"Read after system modelling"
 $y(t) = T[x(t)]$ $T[\cdot]$ denotes a DT system
 $y[n] = T[x[n]]$
 $T[\cdot]$ operates on input signal $x(t)$ to produce output signal $y(t)$.

Systems:

$\rightarrow$ Combination and interconnection of several components to perform desired network/operation/task


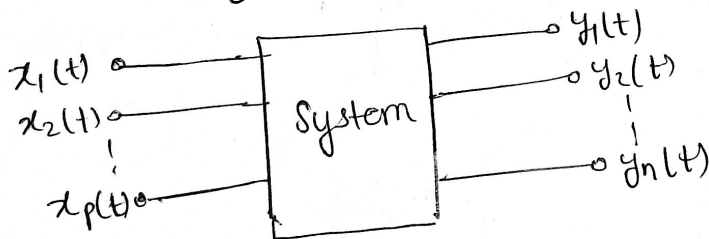
System Modelling: Linear-Time Invariant System



$x_1(t), x_2(t), x_3(t), \dots, x_n(t)$ are input or excitation or cause.

$y_1(t), y_2(t), y_3(t), \dots, y_n(t)$ are O/P or response or effect.

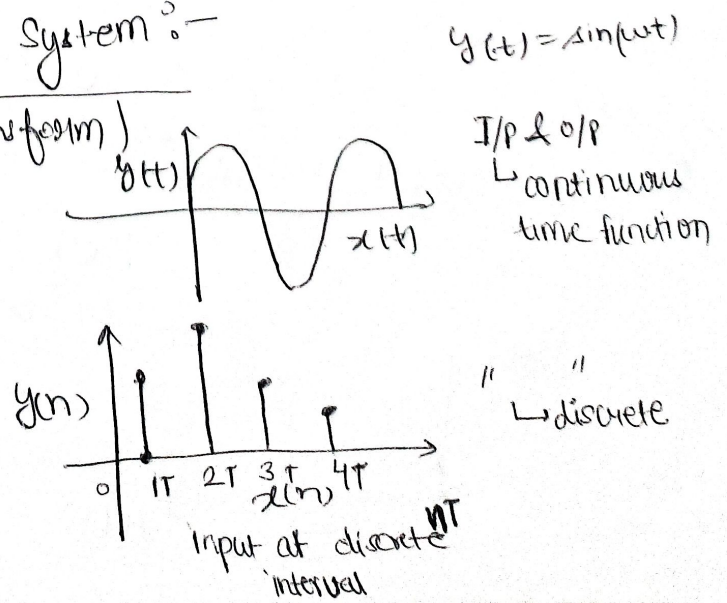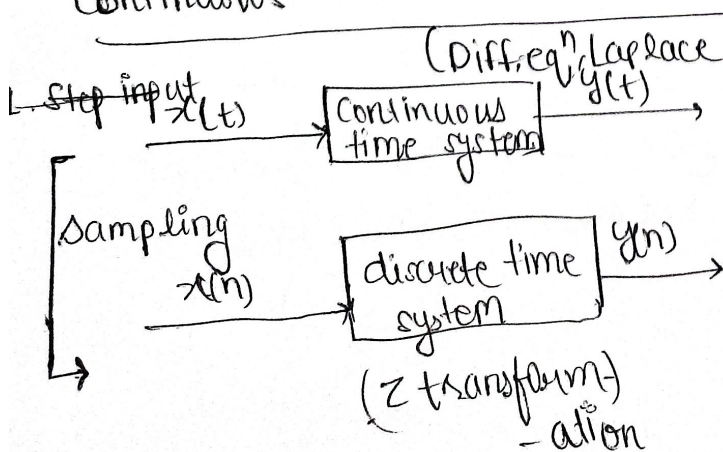(No. break) Continuous time and discrete time System:-



Ex. of continuous fⁿ:-

1. Step input

$$y(t) = 0 \quad ; \quad t < 0$$

$$= k \quad ; \quad t > 0$$



1(i) unit step

$$y(t) = 0 \quad ; \quad t < 0$$

$$= 1 \quad ; \quad t > 0$$

(DC-source)


Ex: Battery.

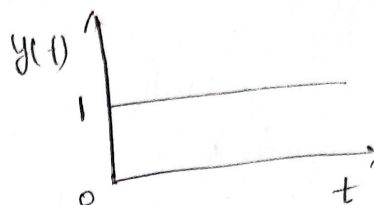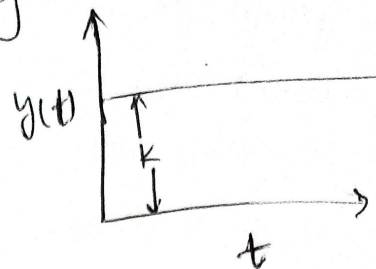


2. Ramp input

$$y(t) = kt, \quad t > 0$$

$$0, \quad t < 0$$

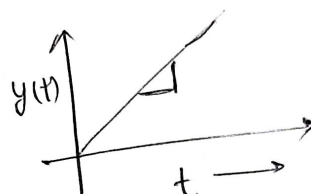


3. Step

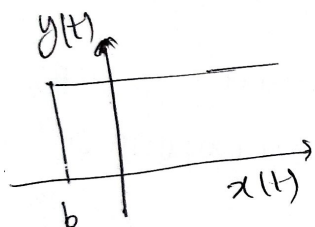


$$y = u(t-a), \quad t > a$$

$$y(t) = u(t+b)$$

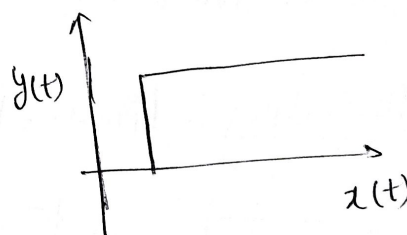

4. Gauge function:

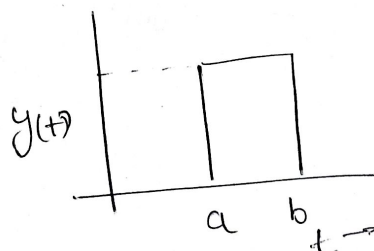


$$y(t) = u(t-a) - u(t-b)$$

5. Exponential function:-


$$y(t) = 1 - e^{-t}$$

$$= 0, \quad t < 0$$

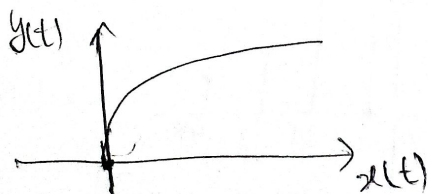

6. Parabolic f^n :-

$$y = t^2$$

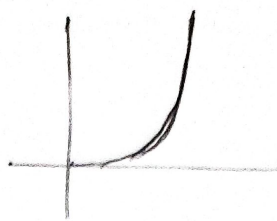

Time invariant and time varying system :

A system is a time invariant or fixed if its input, output relation-

- ship does not change with time otherwise


it is said to be time variant system. $\rightarrow$ cont. $d \in \mathbb{R}$

disc. $d \in \mathbb{Z}^+$

[Note: $y(t) = T[x(t)]$
for d if,
 $y(t-d) = T[x(t-d)]$
 $\rightarrow$ time invariant

Instantaneous and Dynamic system :-

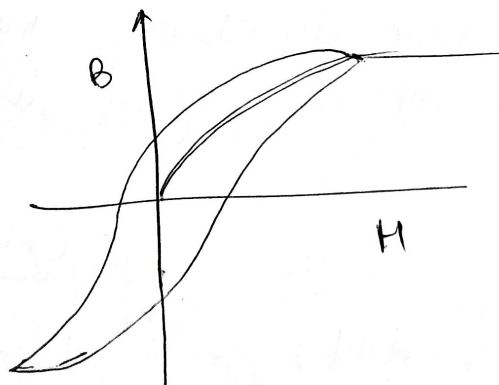$\Rightarrow$ A system for which output is a function of input at present time only is said to be instantaneous system or memory-less or zero memory system.



for all t , there exists a function, f_t such that

$$y(t) = f_t(x(t))$$


where,

$$y(t) = T[x(t)]$$


$\rightarrow$ memoryless.

In $\rightarrow$ disc.

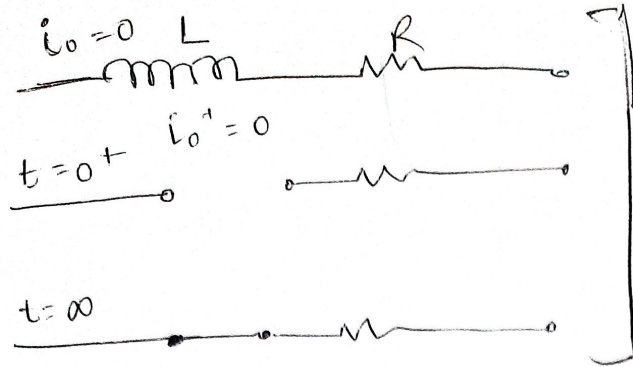$\Rightarrow$ On the other hand dynamic system is one whose output depends on past or future values of input or past output in addition to present input.



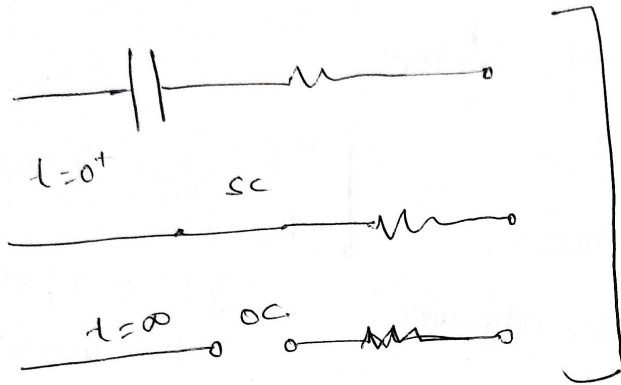$t = 0 \leftrightarrow \infty$
 middle time
 $\downarrow$
 transient state




for all $t \leq T$,
 $\Rightarrow x_1(t) = x_2(t)$
 $\Rightarrow y_1(T) = y_2(T)$

$\uparrow$ Causal
 $y_1(t) = T[x_1(t)]$
 $y_2(t) = T[x_2(t)]$

(non-anticipatory)


Causal and Non-causal System :

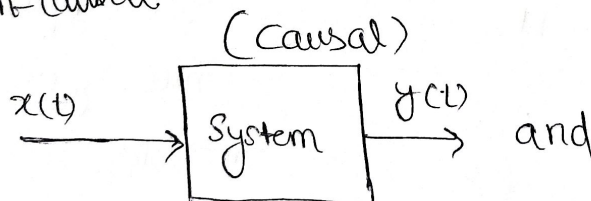- If a system is said to be causal if output of system at any time depends on value of input at present and in the past i.e. output doesn't anticipate future value.
($t=0$)
- Output of system at any time depends only input at present and past value of input otherwise system is said to be non-causal.




(Continuous)
 $y(t) = x(t+1)$

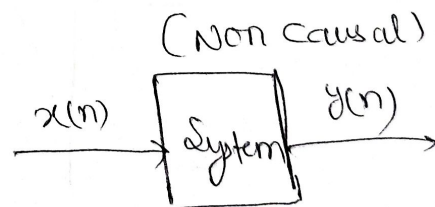non causal
 if it's output depends on
 future value of input
 $y[n] = x[n]$



(discrete)

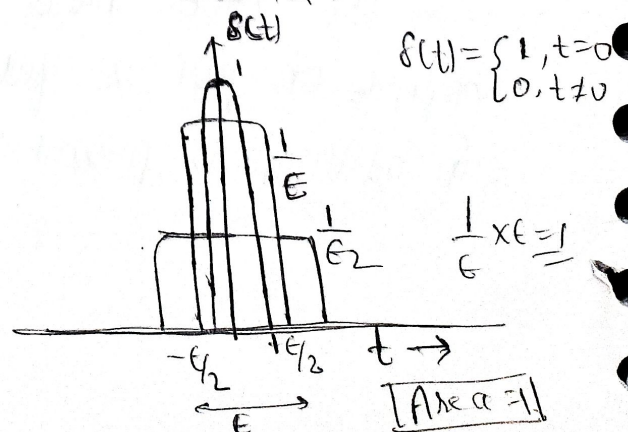

Impulse Response :- $h(t)$ of a continuous-time LTI system (T)

$$h(t) = T \{ \delta(t) \}$$

I/P $x(t)$ is represent do an arbitrary input

$$x(t) = \int_{-\infty}^{\infty} x(\tau) \delta(t-\tau) d\tau$$

$$y(t) \rightarrow \text{o/p}, \quad y(t) = T \{ x(t) \}$$

$$y(t) = \int_{-\infty}^{\infty} x(\tau) T \delta(t-\tau) d\tau$$

$\therefore$ System is Linear Time Invariant

$$h(t-\tau) = T \delta(t-\tau)$$

$$y(t) = \int_{-\infty}^{\infty} x(\tau) h(t-\tau) d\tau$$

Convolution Convolution integral,

$$y(t) = x(t) * h(t)$$

$$y(t) = \int_{-\infty}^{\infty} x(\tau) h(t-\tau) d\tau$$

Property of convolution integral :-

1. Commutative

$$x(t) * h(t) = h(t) * x(t)$$

2. Associative

$$\{ x(t) * h_1(t) \} * h_2(t) = x(t) * \{ h_1(t) * h_2(t) \}$$



3. Distributive



$$x(t) * \{ h_1(t) + h_2(t) \} = x(t) * h_1(t) + x(t) * h_2(t)$$

Ex: The input $x(t)$ and impulse response $h(t)$ of a continuous LTI system is given by, $x(t) = u(t)$, $h(t) = e^{-\alpha t}$, $\alpha > 0$, then evaluate output.

Solⁿ
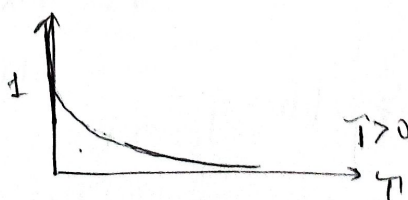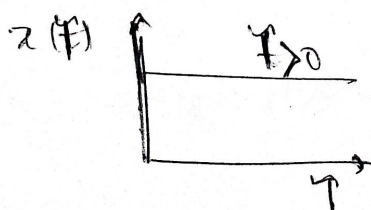
$$y(t) = x(t) * h(t) = \int_{-\infty}^{\infty} x(\tau) h(t-\tau) d\tau$$



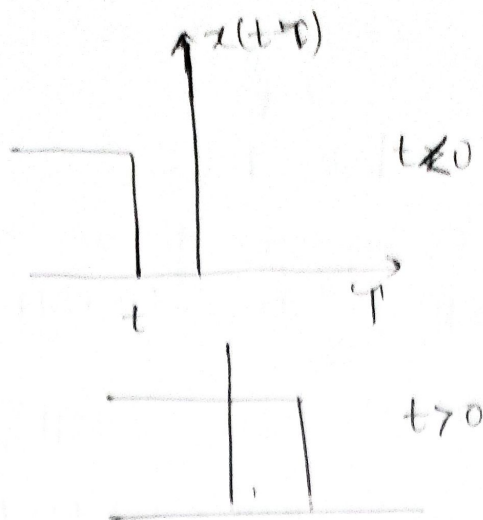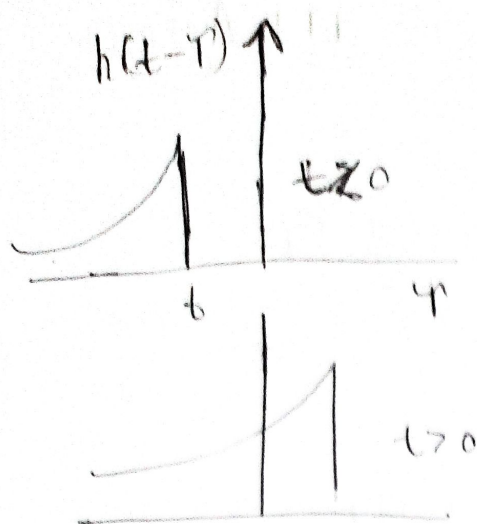

function $h(\tau)$ and $h(t-\tau)$ are shown for $t < 0$ and $t > 0$, we see that for $t < 0$, $h(\tau)$ and $h(t-\tau)$ hence donot overlap each other. Hence it will never overlap to.

for $t > 0$ they overlap from $\tau = 0$ to $\tau = t$, hence $y(t)$ for $t > 0$ will be

$$y(t) = \int_0^t e^{-\alpha(t-\tau)} d\tau$$

$$y(t) = \frac{1}{\alpha} \int_0^t \frac{e^{-\alpha\tau}}{e^{-\alpha t}} d\tau$$

$$= \frac{1}{\alpha e^{\alpha t}} (e^{\alpha t} - 1) = \frac{1}{\alpha} (1 - e^{-\alpha t})$$

Concept

Supermesh: When in a mesh, branch comprises a path around a supermesh doesn't pass through current source. Path around each mesh contained within a supermesh passes through a current source. Total no. of eq's required for a supermesh is equal to no. of meshes contained in supermesh. Supermesh requires 2 mesh eq's.

KVL for outer loop

$$7 - 1(I_1 - I_2) - 3(I_3 - I_2) - 1I_3 = 0$$


KVL for mesh(2):


$$-1(I_2 - I_1) - 2I_1 - 3(I_2 - I_3) = 0$$

$$I_1 = 9A$$

$$I_2 = 2.5A$$

$$I_3 = 2A$$

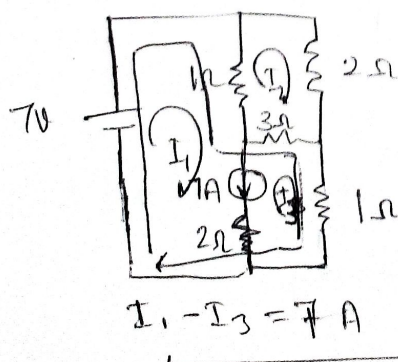

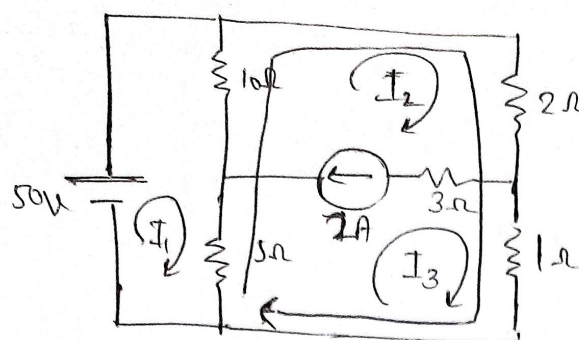

find current in 5Ω ,

$$I_2 - I_3 = 2 \rightarrow \textcircled{1}$$

KVL in outer loop:-

$$10(I_2 - I_1) + 2I_2 + I_3 + 5(I_3 - I_1) = 0 \rightarrow \textcircled{2}$$

KVL in mesh (1):-

$$10(I_1 - I_2) + 5(I_1 - I_3) = 50 \rightarrow \textcircled{3}$$

$$I_1 = 20A$$


$$I_2 = 17.33A$$

$$I_3 = 15.33A$$

Midsem Unit - 1, 3

Supernode concept: Nodes that are connected to each other by a voltage source but not to the reference node by a path of voltage source from a supernode. Supernode requires voltage eqn and remaining node voltage eqn.

Determine current in 5Ω .

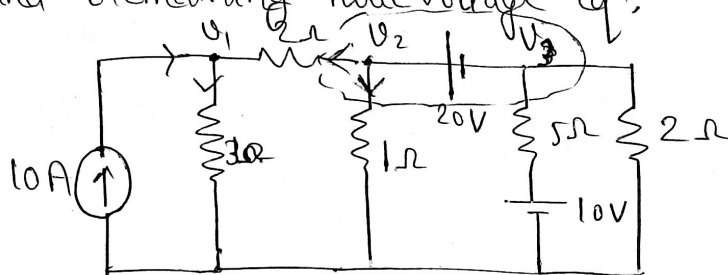

$$V_2 - V_3 = 20V. \rightarrow \textcircled{1}$$

Apply KCL at supernode:-


$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_3 - 10}{5} + \frac{V_3}{2} = 0 \rightarrow \textcircled{2}$$

KCL at node 1:-

$$10 + \frac{V_2 - V_1}{2} = \frac{V_1}{3} \rightarrow \textcircled{3}$$

NOTE: "Applicable on ^{voltage} source having no. resistance.

Superposition theorem :-

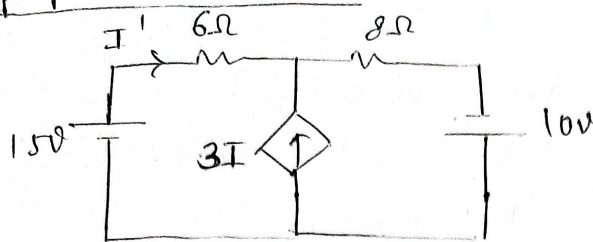


Find current in 6Ω .

$$I = 0.65A$$

Solⁿ

Considering 15V source only

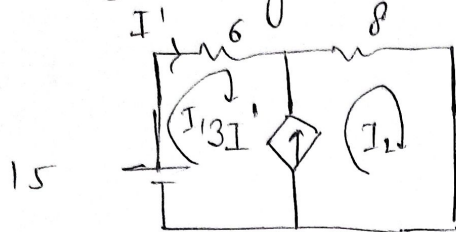

$$I_1 = I'$$

Apply KVL,

$$I_2 - I_1 = 3I'$$


$$I_2 - I_1 = 3I_1$$

$$I_2 = 4I_1 \quad \text{--- (1)}$$

$$15 - 6I_1 - 8I_2 = 0$$


$$6I_1 + 8I_2 = 15 \quad \text{--- (2)}$$

Solving (1) & (2) :-

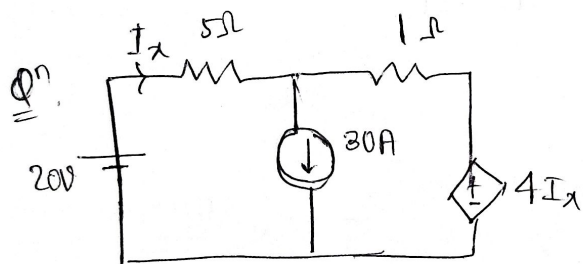

Find I_x


Solⁿ Considering 20V source only.

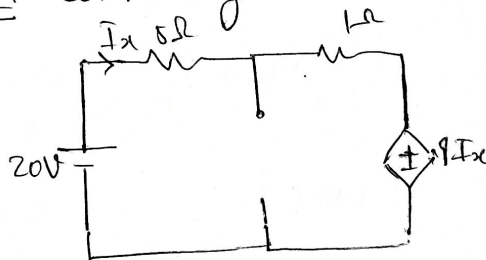

$$6I_x + 4I_x - 20 = 0$$

$$I_x = 2A$$

Considering 30A source only,

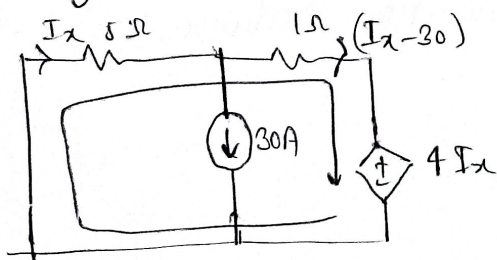


$$(I_x - 30) \times 1 + 4I_x + 5I_x = 0$$

$$10I_x = 30$$

$$I_x = 3A$$


$$I_x = 5A$$

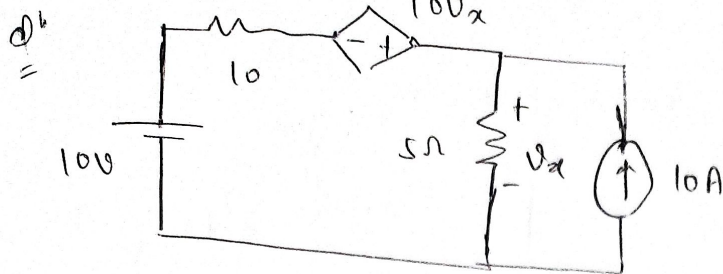

Find current in 10Ω

Solⁿ =

Considering 10V source.

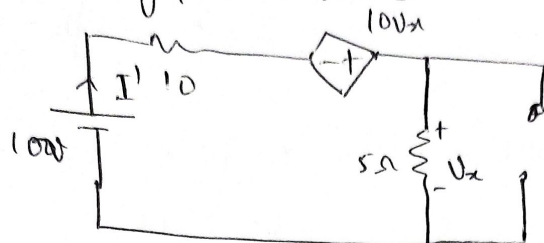

$$I' = \frac{100 - 10I' + 100x}{15}$$

$$V_x = 5 \times I'$$

$$I' = \frac{100 - 10I' + 50I'}{15}$$

$$-20I' = 100$$


$$I' = -5A$$

$$15I' = 10 - 55I'$$

$$I' = \frac{10}{7} A$$

Thvenin's theorem :-

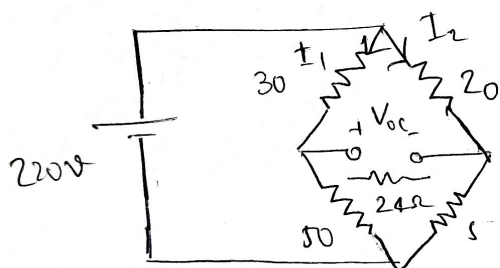⇒ It states that any 2 terminal ckt can be replaced by equivalent resistance and equivalent voltage source.



Find current in 24Ω .

Solⁿ =

$$I_1 = 2.75 A$$


$$I_2 = 8.8 \text{ Amp.}$$

$$V_{th} = 264 - 93.5V$$


$$R_{eq} = \frac{80 \times 25}{80 + 25} =$$

$R_{eq} =$


$$R_{th} = 22.75 \Omega$$

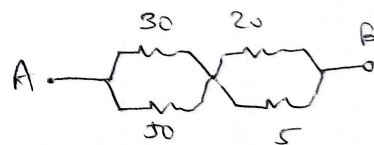

$$R_{th} = 22.75 \Omega$$

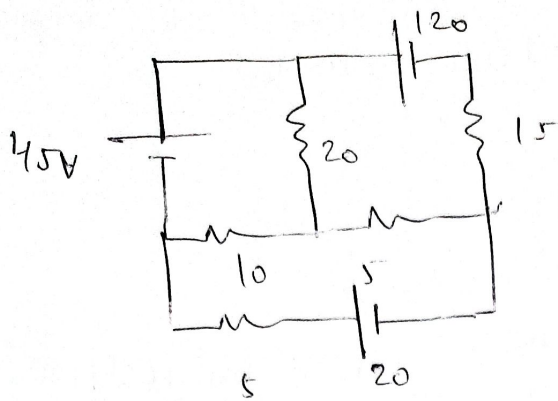

Current in $20\Omega =$

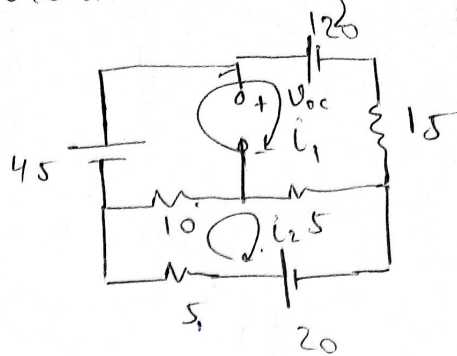

$$V_{th} = 63V$$

$$R_{th} = 4.67\Omega$$

$$30i_1 - 15i_2 - 45 + 120 = 0$$

$$30i_1 - 15i_2 = 75 \quad \text{--- (1)}$$

$$5i_1 - 3i_2 = 15 \quad \text{--- (1) } \times 3$$

$$20i_2 - 15i_1 = 20 \quad \text{--- (2)}$$

$$4i_2 - 3i_1 = 4 \quad \text{--- (2) } \times 2$$

$$5i_2 = -23$$

$$i_2 = -4.6A$$

$$i_1 = \frac{4 \times 3.612}{3} = 4.8A$$

$$11i_2 = 45 + 20$$

$$i_2 = \frac{65}{11} A$$

$$i_1 = \frac{4(i_2 - 1)}{3}$$


$$= \frac{4 \times 5.45}{3}$$

$$i_1 = \frac{72}{11} A$$

$$V_{th} = 120 - 15 \times \frac{72}{11} - \frac{3}{11} \times 5 = 0$$


$$V_{th} = 120 + 98.18 + 3.18$$

$$V_{th} = 120 - 15 \times 9.8 -$$

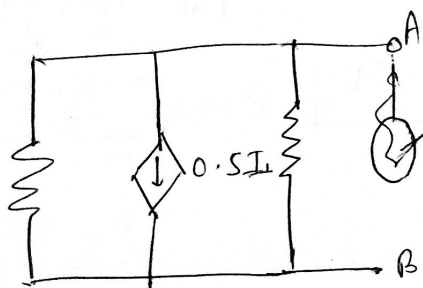


f

Norton's

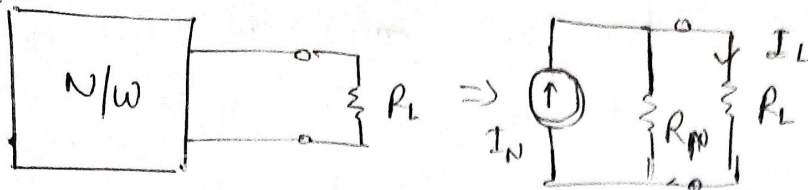
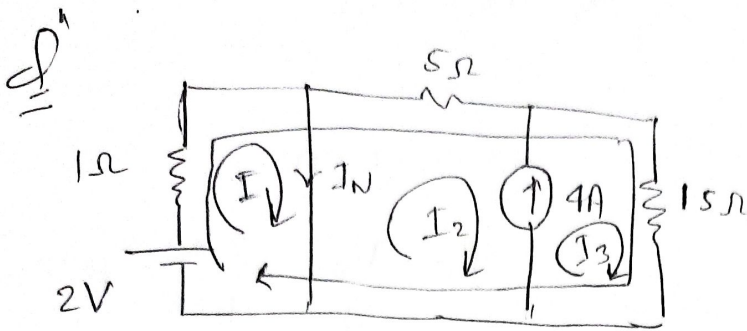
$$I_L = I_N \times \frac{R_N}{R_N + R_L}$$



$$2 - 1 \cdot I_1 - 5 I_2 - 15 I_3 = 0$$

$$2 \cdot 2 - 5 I_3 - 15 I_3 = 0$$

$$I_2 = -3 I_3$$

$$I_1 - I_2 = I_N$$

$$I_3 - I_2 = 4 \quad \text{--- (2)}$$

Loop ① :-


$$2 - I_1 \times 1 = 0$$

$$I_1 = 2A$$

$$4 I_3 = 4$$

$$I_3 = 1A$$

$$I_2 = -3A$$

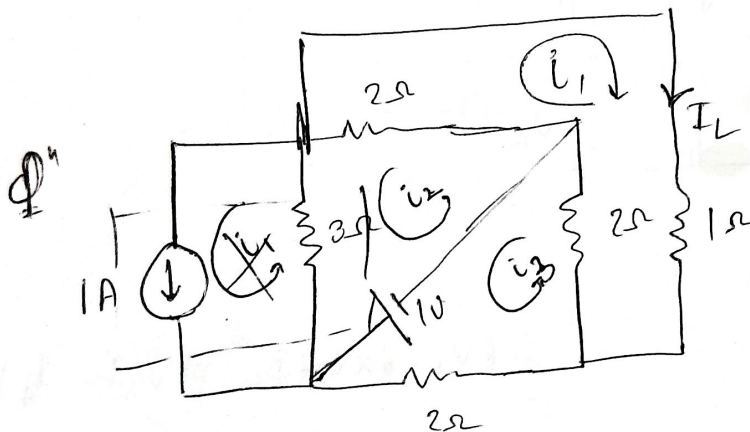

Find current in 1Ω


$$I_1 = 1A$$

$$I_2 =$$

Solⁿ

$$R_N = \frac{11}{5} \Omega$$

Qⁿ

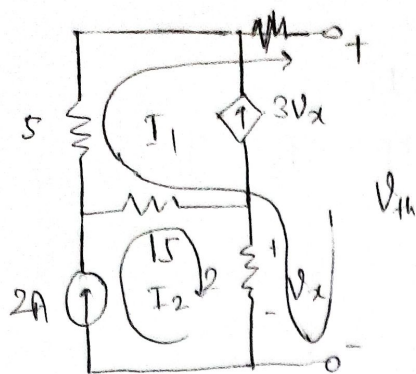

Find Norton equivalent across AB-terminals.
 I_N & R_N to be determined or
 also V_{th} or R_N

$$\rightarrow I_1 = 1.69A$$

$$V_{th} - 2I_2 + 15(I_1 - I_2) + 5I_1 = 0$$

$$V_{th} = 4$$


$$I_1 = -3V_x$$

$$V_x = 2I_2$$

$$V_{th} = \underline{274V}$$

$$R_N = \frac{V_{th}}{I_N} = \frac{274}{1.69} = 162.13$$

$$\boxed{I_2 = 2A}$$

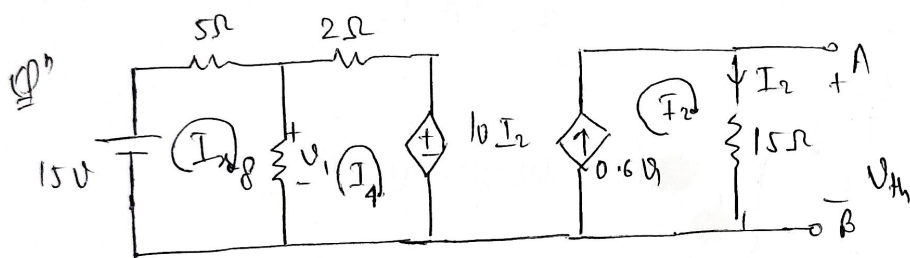

$$\textcircled{1} \quad 15 - 5I_x - 8(I_x - I_4) = 0$$

$$V_1 = 8(I_x - I_4)$$


$$0.6V_1 = 8 \times 0.6I_x = 4.8(I_x - I_4)$$

$$\textcircled{2} \quad -8(I_4 - I_x) - 2I_4 - 10I_2 = 0$$

$$\textcircled{3} \quad V_{th} = 15I_2$$


$$I_2 = 0.6V_1$$

$$V_{th} = 15 \times 0.6V_1 = 9V_1$$

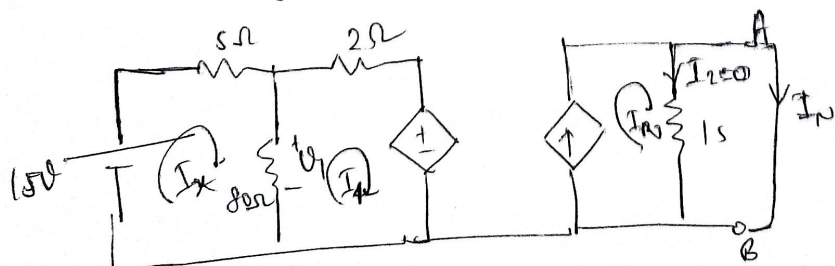

$$\boxed{I_N = 2.16A}$$

Maximum Power Transfer Theorem :-

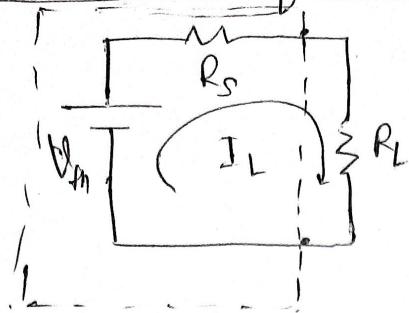


$$I_L = \frac{V_{th}}{R_s + R_L}$$

$$P_L = I_L^2 R_L$$

$$P_L \text{ will be max. if } \frac{dP_L}{dR_L} = 0 \text{ \& } = \frac{V_{th}^2}{(R_s + R_L)^2} \times R_L$$


$$\frac{d^2 P_L}{dR_L^2} = -ve$$
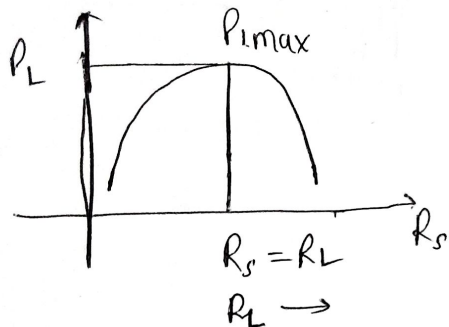
$$\frac{dP_L}{dR_L} = V_{th}^2 \left[\frac{(R_s + R_L)^2 \times 1 - R_L \cdot 2(R_s + R_L)}{(R_s + R_L)^4} \right] = 0$$



$$(R_s + R_L)^2 = 2R_L(R_s + R_L)$$

$$\boxed{R_s = R_L}$$

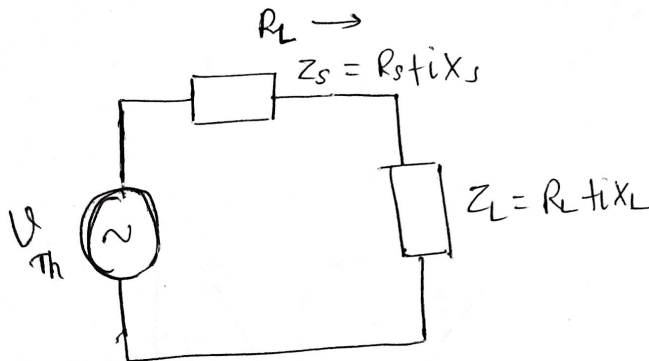

$$Z_s = Z_L^*$$

$$Z_s = R_L - jX_L$$

$$\boxed{jX_s = -jX_L}$$


$$P_{Lmax} = \frac{V_{th}^2}{4R_L^2} \times R_L = \frac{V_{th}^2}{4R_L}$$

$$\% \text{ power} = \frac{V^2}{4R_L}$$

$$\text{Input power} = \frac{V^2}{4R_L} + \frac{V^2}{4R_L} = \frac{V^2}{2R_L}$$


$$\eta\% = \text{efficiency}\% = \frac{\text{o/p}}{\text{i/p}} \times 100 = \underline{\underline{50\%}}$$

Q11

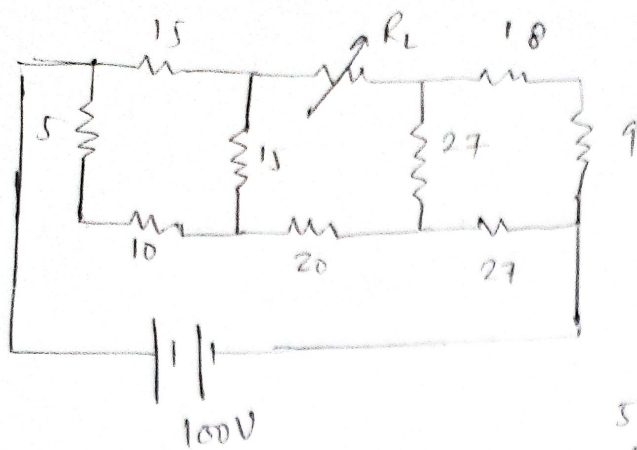

solⁿ
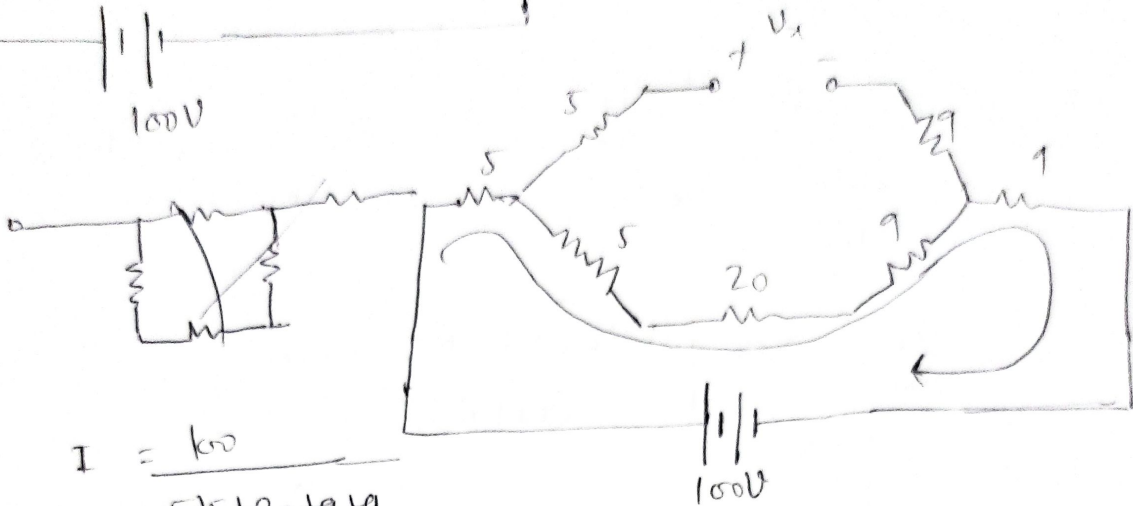
$$V \rightarrow Y \rightarrow \frac{R}{3}$$





$$I = \frac{100}{5 + 20 + 9 + 9}$$

$$= 2.07A$$

$$V_{th} = (5 + 20 + 9) \times 2.07$$



$$R_{th} =$$

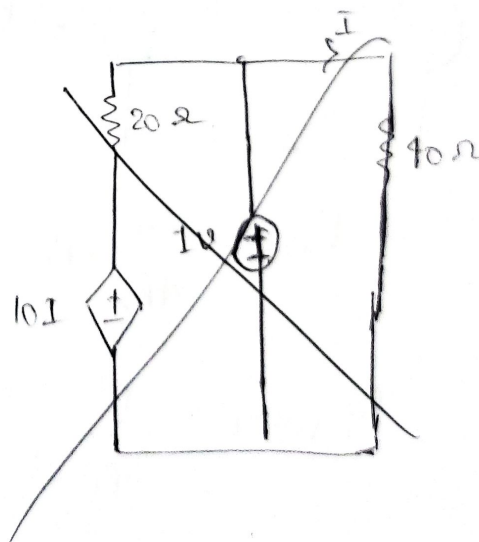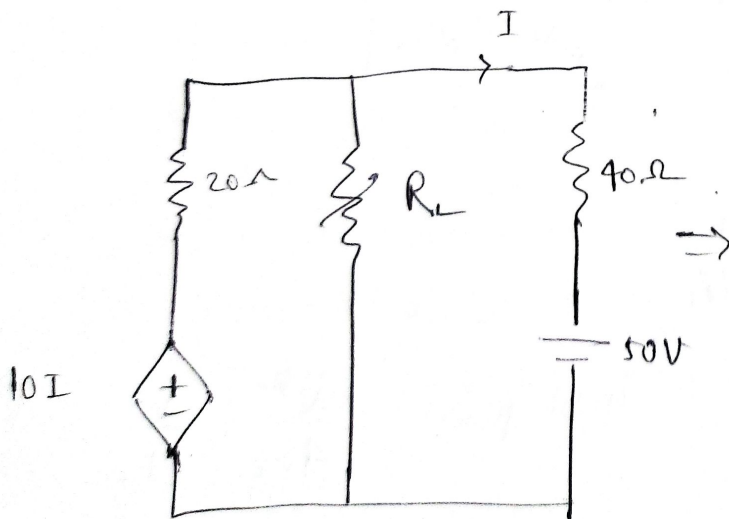

$$60I + 50 - 10I = 0 \Rightarrow \boxed{I = -1A}$$

$$V_{th} - 40(-1) - 50 = 0$$

$$\boxed{V_{th} = 10V}$$

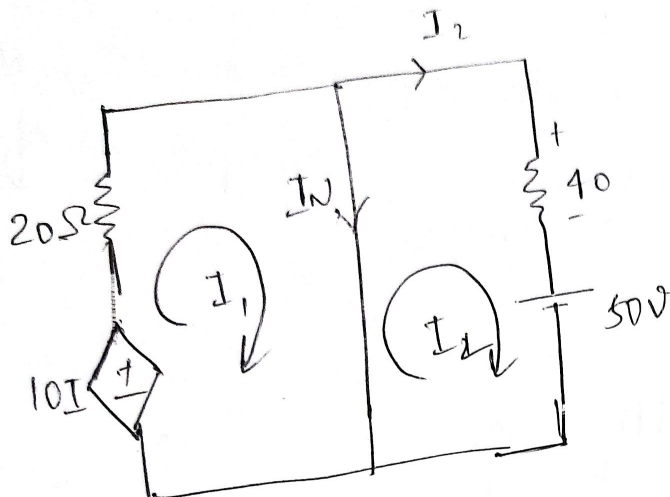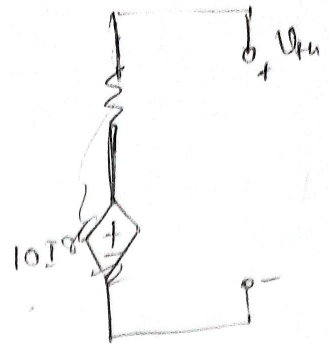

$$I_1 - I_2 = I_N \quad \text{--- (1)}$$

$$I = I_2$$

$$10I - 20I_1 = 0$$

$$10I_2 = 20I_1$$

$$I_2 = 2I_1$$


$$-1.25 + 0.625 =$$

$$50 = -40I_2$$

$$I_2 = -1.25$$

$$I_1 = \frac{I_2}{2} = -0.625A$$

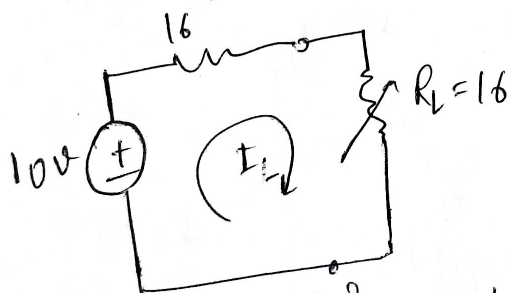
$$R_N = \frac{V_{th}}{I_N} = \frac{10}{0.625} = 16A$$



$$P_{Lmax} = \frac{V^2}{4R_L} = \frac{10^2}{4 \times 16} = 1.56W$$


Note:- Apply 1A or 1V when there are only dependent sources.

Reciprocity theorem :-

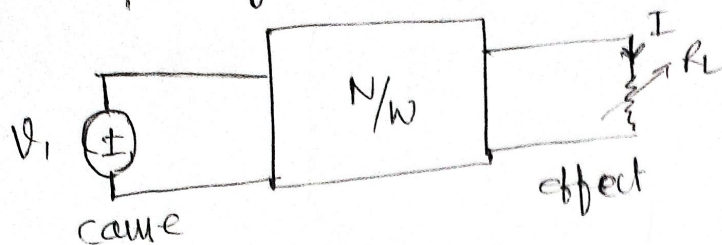


$$\frac{V_1}{I} = \frac{V_2}{I} = K$$

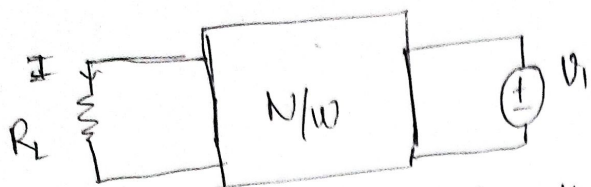
$$\frac{\text{Cause}}{\text{Effect}} = K$$



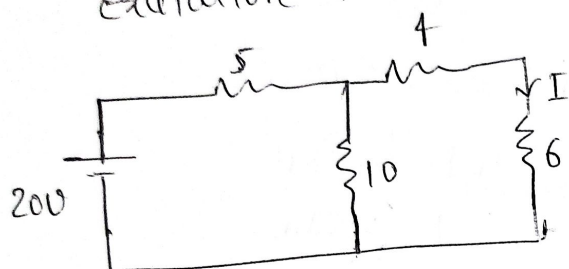⇒ In a linear bilateral active single source network, ratio of excitation to response remain same when position of excitation and response are interchanged.



$$I = 1A \quad K = \frac{20}{1} =$$

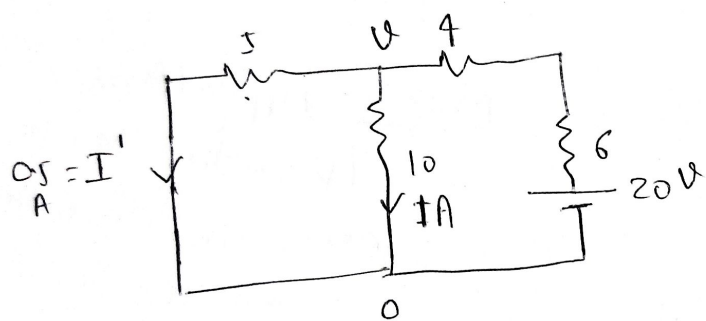


$$R_{eq} = (10 \parallel 5) + 4$$

$$= \frac{10 \times 5}{15} + 4 = \frac{10}{3} + 4$$

$$= 10 \times \frac{4}{3}$$

$$= \frac{3}{2} A$$


$$I = \frac{20}{10 \times \frac{4}{3}}$$

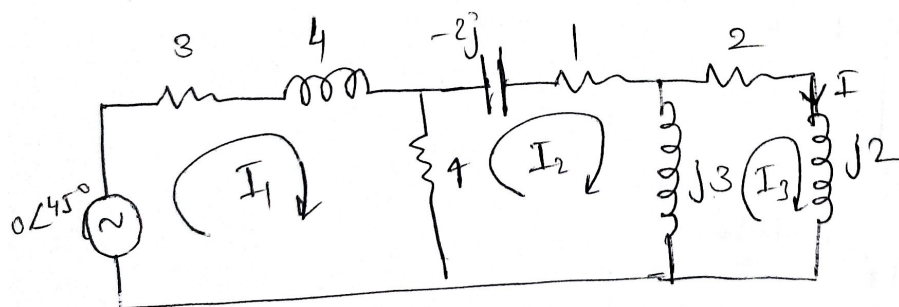

$$I_3 = 1$$


$$I_3 = 0.704 \angle 30.72^\circ$$

Millman's theorem :-

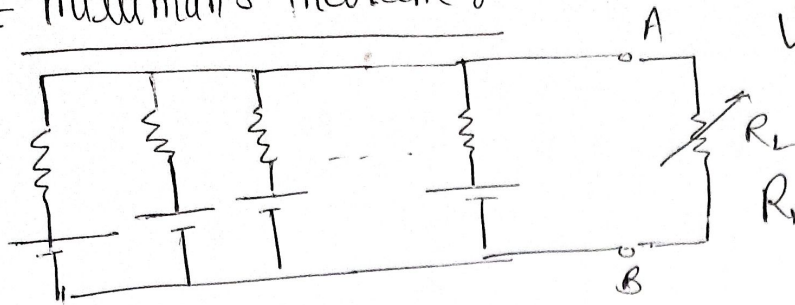



$$V_m = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + G_3 + \dots + G_n}$$
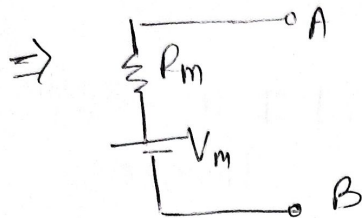
$$R_m = \frac{1}{G_m} = \frac{1}{G_1 + G_2 + G_3 + \dots + G_n}$$




$$Z = R + jX$$

$$Y = G + jB \quad \text{Susceptance}$$

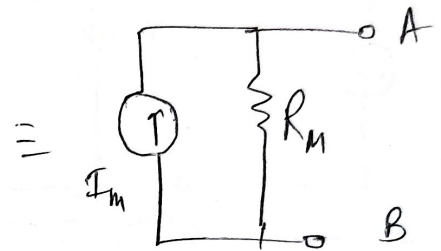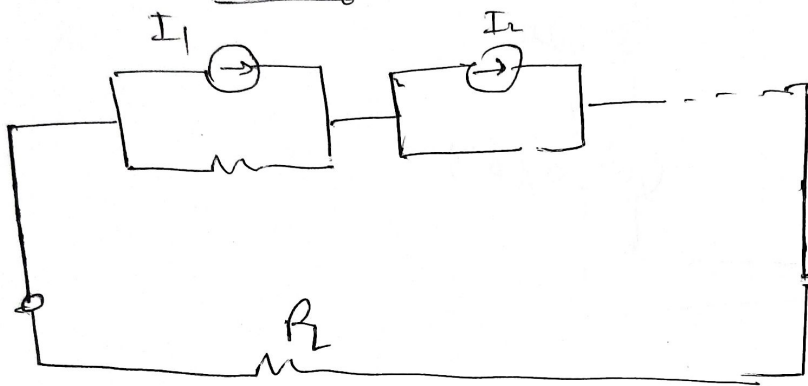
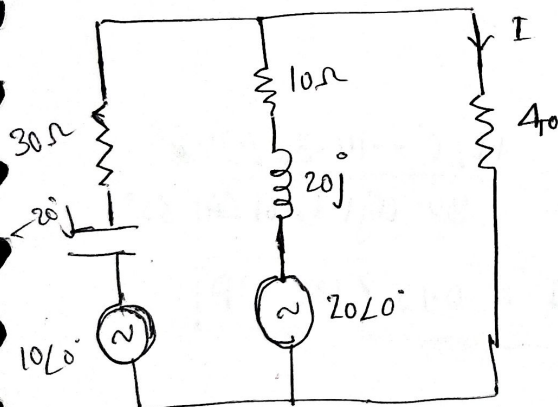
$$\left[\begin{aligned} I_m &= \frac{I_1 Z_1 + I_2 Z_2 + \dots + I_n Z_n}{Z_1 + Z_2 + \dots + Z_n} \\ R_m &= Z_1 + Z_2 + Z_3 + \dots + Z_n \end{aligned} \right]$$



find I use millman's theorem

$$V_m = \frac{10 \angle 0^\circ \times \frac{1}{30 - 20j} + 20 \angle 0^\circ \times \frac{1}{10 + 20j}}{\frac{1}{30 - j20} + \frac{1}{10 + 20j}}$$


$$V_m = 18.2 \angle -15.95^\circ$$

$$Y_m = \frac{1}{Z_m}$$

$$Y_m = Y_1 + Y_2$$


$$Z_m = \frac{1}{Y_1 + Y_2} = \frac{1}{\dots}$$

$$= 20.15 \angle 29.74^\circ$$

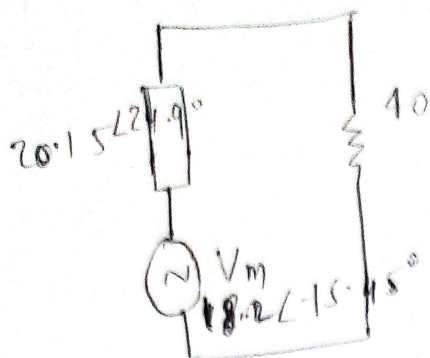

$$I_L = 0.217 \angle -25.21^\circ \text{ A}$$

find I use millman's theorem.

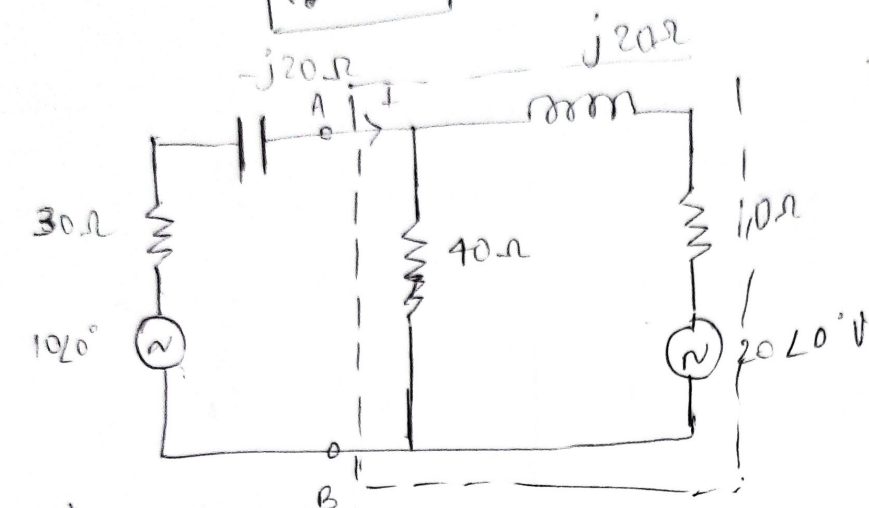


2d

$$V_{AB} = \frac{\frac{20 \angle 0^\circ}{10 + 20j} + 0}{\frac{1}{10 + 20j} + \frac{1}{40}}$$


$$= 10 \angle 0^\circ - (30 - 20j)I$$
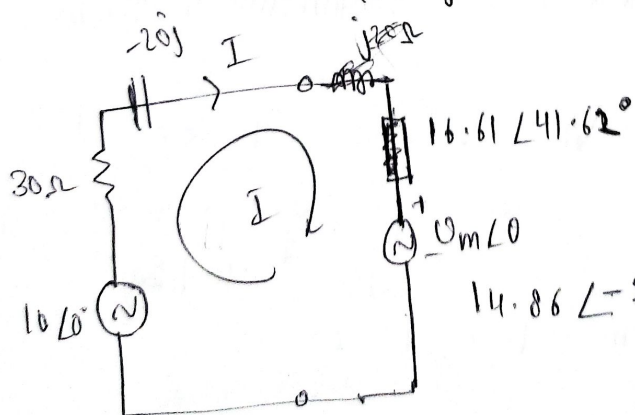
$$Z_m = \frac{1}{\frac{1}{10 + 20j} + \frac{1}{40}}$$




$$I = \frac{10 \angle 0^\circ - 14.86 \angle -21.8^\circ}{30 - 20j + 16.61 \angle 41.62^\circ}$$
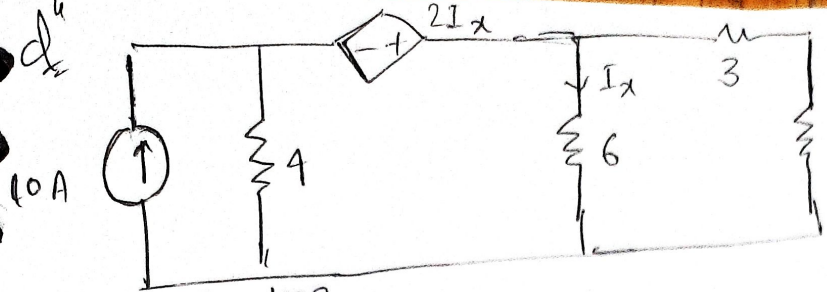
$$I = 0.15 \angle 136.5^\circ \text{ A}$$



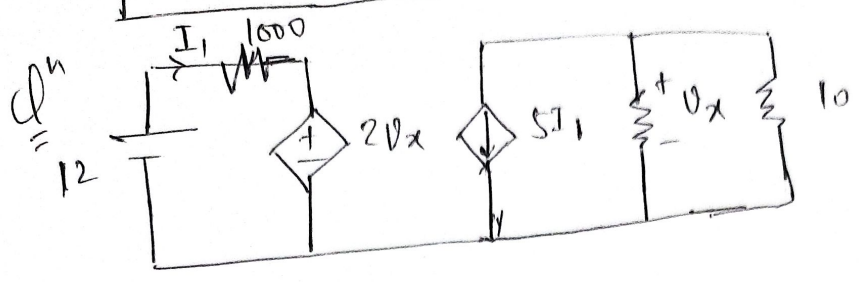Find R_L for max. power
 R_L and also find max. power.



Find current through 10 Ω .