
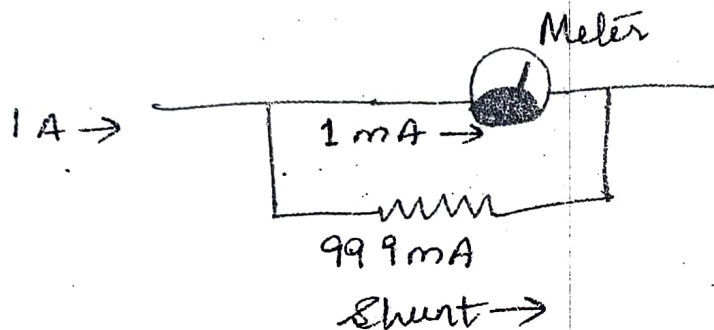


Applications:

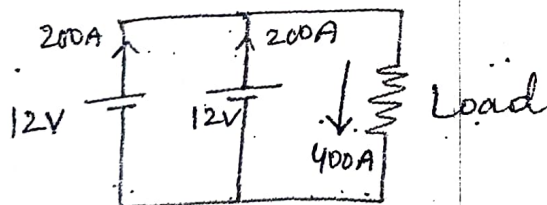
- (i) A low resistor, called a shunt is connected in parallel with an ammeter to increase the current range of the meter. If shunt is not used, the ammeter is able to measure current upto 1 mA . Use of shunt permits to measure current upto 1 A . Shunt increases the range of ammeter.



- (ii) Identical voltage sources may be connected in parallel to provide a greater current capacity.



Voltage Divider Rule :

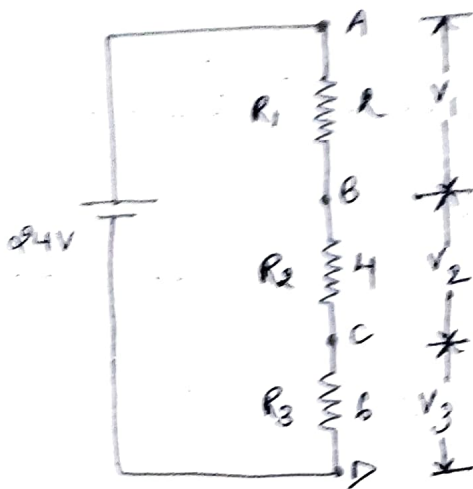

Total Resistance

$$R = R_1 + R_2 + R_3$$

Acc. to Voltage Divider Rule

$$V_1 = \frac{R_1}{R} \times V$$

$$V_2 = \frac{R_2}{R} \times V$$

$$V_3 = \frac{R_3}{R} \times V$$


eg: $R = 12\Omega$

$$V_1 = \frac{2}{12} \times 24 = 4V$$

$$V_2 = \frac{4}{12} \times 24 = 8V$$

$$V_3 = \frac{6}{12} \times 24 = 12V$$

Current Divider Rule :

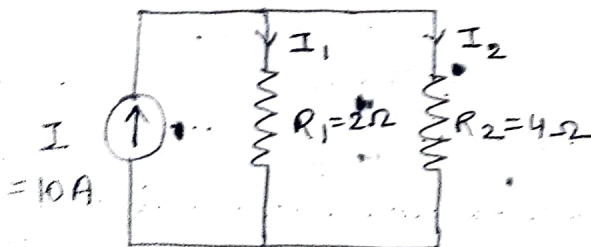

$$I_1 = \frac{R_2}{R} \times I$$

$$I_2 = \frac{R_1}{R} \times I$$

$$R = R_1 + R_2$$

$$R = 6\Omega$$

$$I_1 = \frac{4}{6} \times 10 = \frac{20}{3} A$$


$$I_2 = \frac{2}{6} \times 10 = \frac{10}{3} A$$

SHORT & OPEN CIRCUITS

SHORT CIRCUIT: When two points of circuit are connected together by a thick metallic wire.




SHORT: Zero resistance

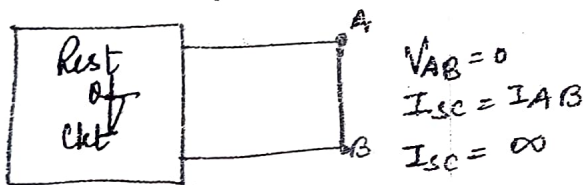- (i) no voltage can exist across it because $V = IR = I \times 0$
 $V = 0$
- (ii) current through it (short circuit current) is very large (∞)




SHORTS IN A SERIES CRT

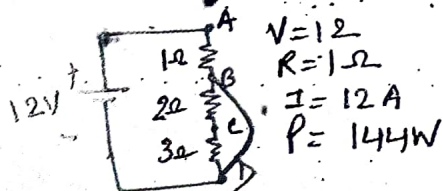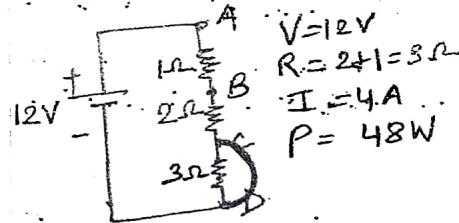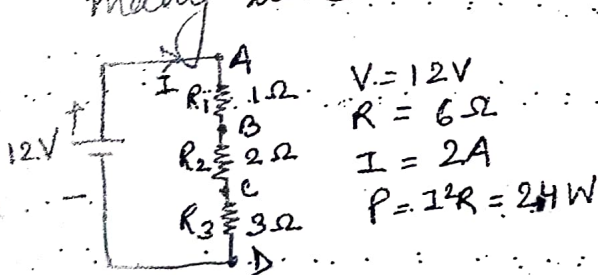A dead (or solid) short has almost zero resistance, it causes the problem of excessive current which in turn, causes power dissipation to increase many times and circuit components to burn out.




→ Due to short circuit, current become 6 times the normal value.

SHORTS IN PARALLEL CIRCUIT

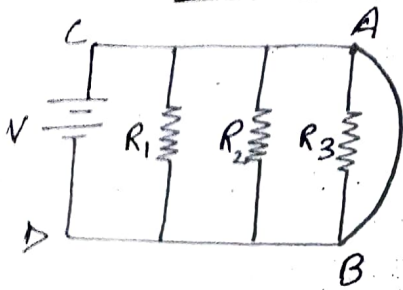

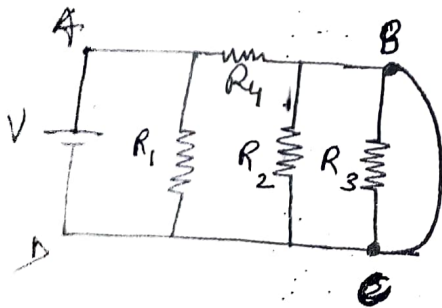- Not only R_3 is short circuited but both R_1 and R_2 are also shorted i.e. short across one branch means short across all branches.
- There is no current is shorted resistors. If there were three bulbs they will not glow.
- The shorted components are not damaged. For eg. if we had three bulbs, they would glow again when it is restored to normal conditions by removing the short circuit.




- In this fig., short circuit across R_3 may short out R_2 but not R_1 , since it is protected by R_4 .

OPEN CIRCUIT:

- Two points are said to be open circuited when there is no direct connection between them.
- Open: represents break in the continuity of the circuit.

Due to break: (I) resistance b/w two points is infinite.
 (II) No flow of current b/w two points.


OPEN IN A SERIES CIRCUIT

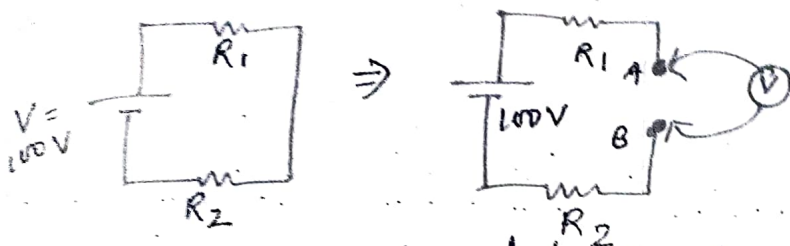

Effects produced due to open let:


- ① $\rightarrow$ Infinite resistance, circuit current = 0
No voltage drop across R_1 & R_2 .
- ② $\rightarrow$ Whole of the applied voltage (i.e. 100V) is felt across the 'open' i.e. across terminals A and B.

OPEN IN PARALLEL CIRCUIT

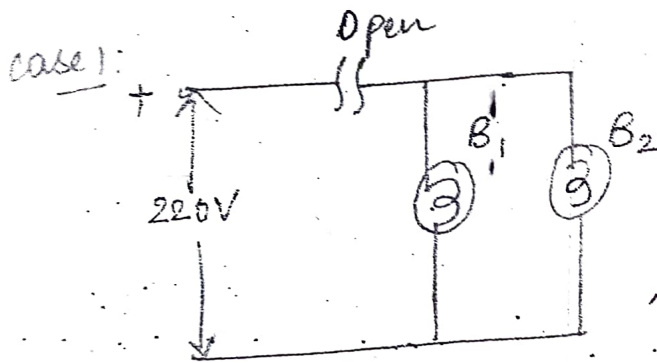

$\rightarrow$ An open in main line prevents flow of current to all branches.
Hence, neither of two bulb glows.
However, 220V (full applied voltage) is available across the open.

case 2:

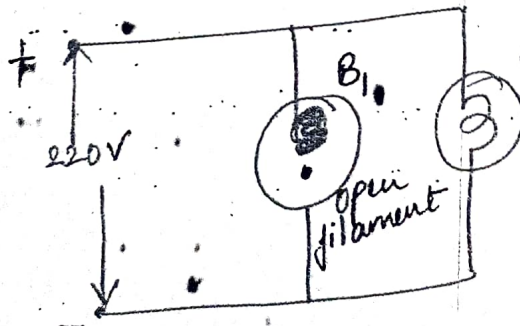

$\rightarrow$ open has occurred in branch circuits of B_1 .
No current in this branch, B_1 will not glow.
 $\rightarrow$ other bulb remains connected across supply, it would keep operating normally.

② KIRCHHOFF'S SECOND LAW OR VOLTAGE LAW


OR MESH LAW

"The algebraic sum of the products of currents and resistances in each of the conductors in any closed path in a network plus the algebraic sum of the emfs in that path is zero."

$$\sum IR + \sum \text{em.f} = 0$$

or

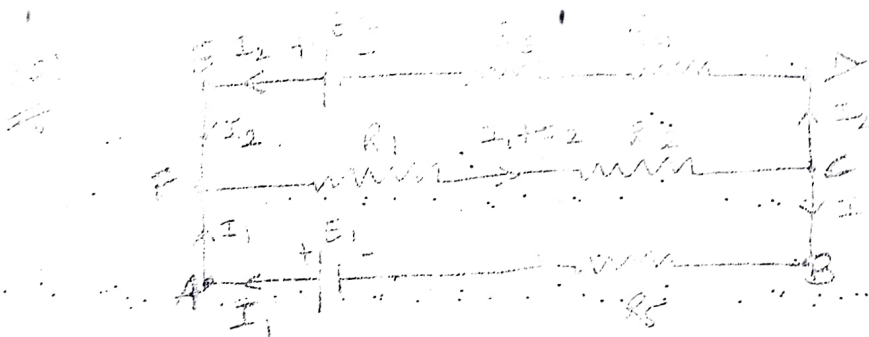Acc to this law, "In any closed circuit or mesh the algebraic sum of emfs acting in that circuit is equal to the algebraic sum of the products of the currents and resistances of each part of the circuit. i.e. $\sum \text{em.f} = \sum IR$ "



In mesh AFCBA,

Apply KVL

$$-E_1 + R_1(I_1 + I_2) + R_2(I_1 + I_2) + R_5 I_1 = 0 \quad (1^{st} \text{ eqn})$$

$$E_1 = I_1 R_5 + R_1(I_1 + I_2) + R_2(I_1 + I_2) \quad (2^{nd} \text{ eqn})$$

$$E_1 = I_1 R_5 + (R_1 + R_2)(I_1 + I_2)$$

In mesh FEDCF

$$R_4 I_2 + R_3 I_2 - E_2 + R_1(I_1 + I_2) + R_2(I_1 + I_2) = 0$$

$$-E_2 + (R_4 + R_3)I_2 + (R_1 + R_2)(I_1 + I_2) = 0 \quad (1^{st} \text{ eqn})$$

$$E_2 = (R_4 + R_3)I_2 + (R_1 + R_2)(I_1 + I_2) \quad (2^{nd} \text{ eqn})$$

KIRCHHOFF'S LAWS

These laws describe the relationships among circuit voltages and circuit currents.


These laws are very helpful in determining the
→ equivalent resistance of a complex network, &
→ the current flowing in the various branches of the network.

Gustav Robert Kirchhoff derived two basic laws:

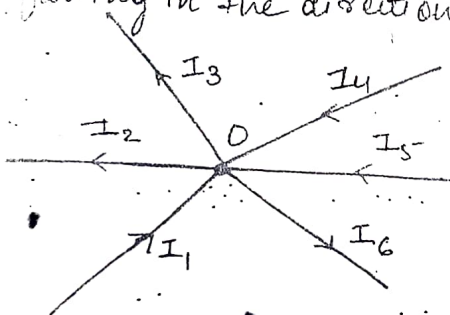(1) KIRCHHOFF'S FIRST LAW or CURRENT LAW (KCL) or Point Law

"According to this law in any network of wires carrying currents, the algebraic sum of all currents meeting at a point (or junction) 'is zero'."

Q. I_1, I_2, I_3, I_4, I_5 & I_6 are the current meeting at junction O, flowing in the directions of arrowheads marked on them.



$$I_1 - I_2 - I_3 + I_4 + I_5 - I_6 = 0$$

taking
incoming currents as +ve
& outgoing currents as -ve

or
"The sum of incoming currents towards any point is equal to the sum of outgoing currents away from that point."

$$I_1 + I_5 + I_4 = I_3 + I_2 + I_6$$

Incoming current = Outgoing current

in @ A F E D C B A

$$R_5 I_1 - E_1 + E_2 - R_3 I_2 - R_4 I_2 = 0$$

$$-E_1 + E_2 + R_5 I_1 - R_3 I_2 - R_4 I_2 = 0 \quad (1^{st} \text{ defn})$$

$$E_1 - E_2 = R_5 I_1 - (R_3 + R_4) I_2 \quad (2^{nd} \text{ defn})$$


SIGN CONVENTIONS

1st method : As discussed above.

- The resistive drops in a mesh due to current flowing in clockwise direction must be taken positive drops.
- The resistive drops in a mesh due to current flowing in counter-clockwise direction must be taken as -ve drops.
- Battery emf causing current to flow in clockwise direction in a mesh must be taken as positive emf.
- Battery emf causing current to flow in counter-clockwise direction in a mesh must be taken as negative emf.


2nd method :

→ Sign of Battery E.M.F.

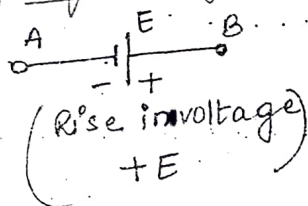

A rise in voltage should be given a +ve sign

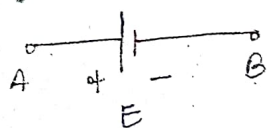i.e. if we go from -ve terminal of a battery to +ve terminal, there is a rise in potential.




A fall in voltage should be given a -ve sign.



i.e. if we go from +ve terminal to -ve terminal, there is a fall in voltage.

* It is important to note that the sign of the battery ^{emf} is independent of the direction of current although that branch.

→ Sign of IR drop:

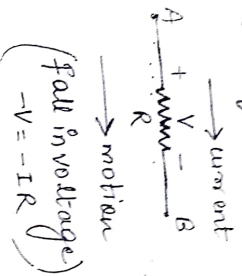

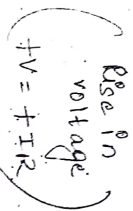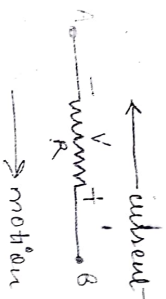If we go through a resistor in the same direction as the current, then there is a fall in potential because current flows from higher to a lower potential. Hence, this voltage fall should be taken as -ve.




If we go in a direction opposite to that of the current, the current flow is lower to higher we proceed.

So there is rise in voltage.

& it should be taken as +ve sig.

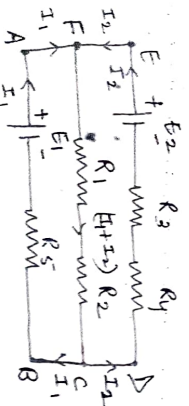Eg Consider the main circuit as discussed in previous example.



In mesh AFCBA

$$E_1 - R_1(I_1 + I_2) - R_2(I_1 + I_2) - I_1 R_4 = 0$$

$$E_1 = I_1 R_5 + (R_1 + R_2)(I_1 + I_2)$$

In mesh FEDCB


$$-E_2 + (R_2 + R_4)I_2 - R_5 I_1 + E_1 = 0$$

$$E_1 - E_2 = R_5 I_1 - (R_3 + R_4)I_2$$

$$E_2 = (R_1 + R_2)(I_1 + I_2) + (R_3 + R_4)I_2$$

QUESTIONS BASED ON KIRCHHOFF'S LAW

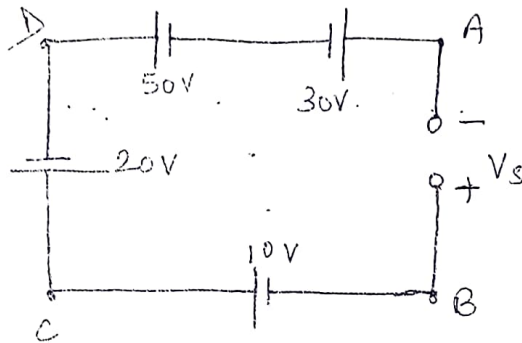Q.1 What is the voltage V_s across the open switch in the given ckt.



Apply KVL

$$+V_s + 30 - 50 - 20 + 10 = 0$$

$$V_s + 40 - 70 = 0$$

$$V_s - 30 = 0$$

$$V_s = 30V$$

(According to 1st method)


2nd method (sign convention)


$$-V_s - 30 + 50 + 20 - 10 = 0$$

$$V_s = 20 + 10$$

$$V_s = 30V$$

Q.2: Find the current I in the ckt.

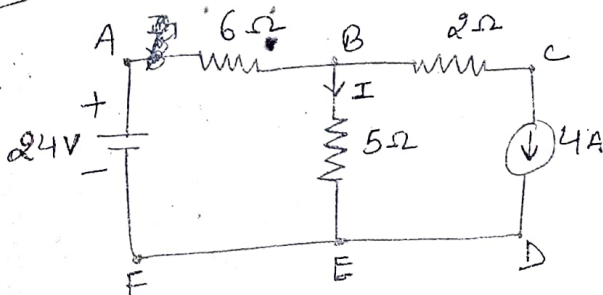

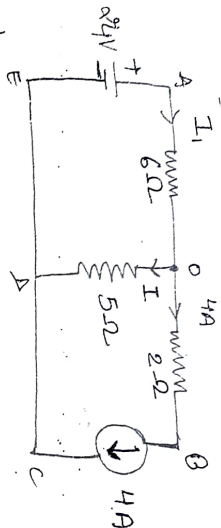

1st method

At node 0

By using KCL

$$I_1 = I + 4A$$

$$I = I_1 - 4$$

$$= \frac{24}{6} - 4$$

$$= 4 - 4$$

$$\boxed{I = 0}$$

2nd method

$$I_1 = I + 4$$

(Applying KCL)

Apply KVL, in mesh AODCA

$$-24 + 6I_1 + 5I = 0$$

$$-24 + 6(I + 4) + 5I = 0$$

$$-24 + 6I + 24 + 5I = 0$$

(Put the value $I_1 = I + 4$)


For applying KVL first we have to find current in each branch of given mesh

$$I = 0$$

$$\boxed{I = 0}$$

Q-3.

Obtain I_R in terms of I_S

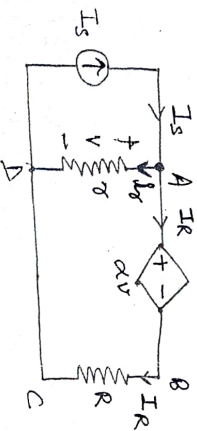

Apply KCL at node A

$$I_S = I_\alpha + I_R$$

Apply KVL in mesh ABCDA

$$+\alpha V + R I_R - V = 0$$

we know $V = r I_\alpha$

$$\alpha r I_\alpha + R I_R - r I_\alpha = 0$$

$$R I_R = r I_\alpha - \alpha r I_\alpha$$

$$= r (\gamma - \alpha \gamma)$$

$$R I_R = (I_S - I_R) (\gamma - \alpha \gamma)$$

$$R I_R = \gamma I_S - \alpha \gamma I_S - \gamma I_R + \alpha \gamma I_R$$

$$R I_R = (\gamma - \alpha \gamma) I_S + I_R (\alpha \gamma - \gamma)$$

$$I_R (R - \alpha \gamma + \gamma) = \gamma (1 - \alpha) I_S$$

$$I_R = \frac{\gamma (1 - \alpha) I_S}{R - \gamma (\alpha - 1)}$$

$$I_R = \frac{\gamma (1 - \alpha) I_S}{R + \gamma (1 - \alpha)}$$


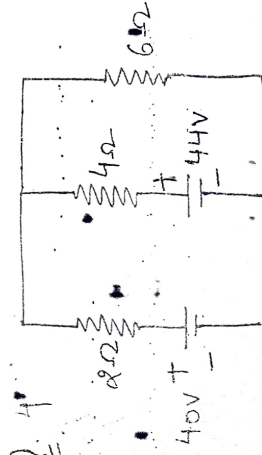


Fig. shows two batteries connected in parallel each represented by an emf along their internal resistances. A load resistance of 6Ω is connected across the ends of the batteries. Calculate current through each battery and load.

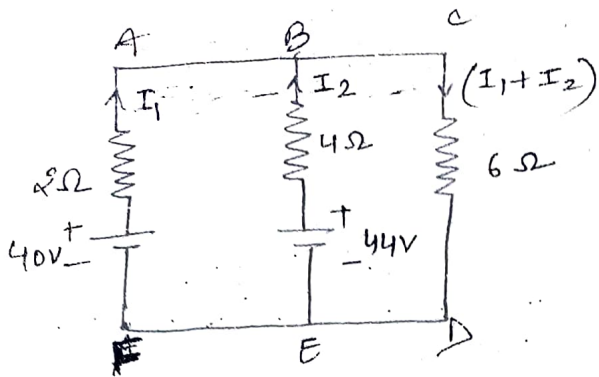

At node B Apply KCL

$$I_1 + I_2 = I_1 + I_2$$

$$\frac{40}{2} + \frac{44}{4} = I_1 + I_2$$

$$20 + 11$$

Apply KVL in mesh ABEFA

$$-40 + 2I_1 - 4I_2 + 44 = 0$$

$$2I_1 - 4I_2 + 4 = 0$$

$$I_1 - 2I_2 + 2 = 0$$

$$2I_2 - I_1 = 2 \quad \text{--- (1)}$$

Apply KVL in BCDEB

$$-44 + 4I_2 + 6(I_1 + I_2) = 0$$

$$-44 + 4I_2 + 6I_1 + 6I_2 = 0$$

$$6I_1 + 10I_2 = 44$$

$$3I_1 + 5I_2 = 22 \quad \text{--- (2)}$$

from eqⁿ (1)

$$I_1 = 2I_2 - 2 \quad \text{--- (3)}$$

Put I_1 in eqⁿ (2)

$$3(2I_2 - 2) + 5I_2 = 22$$

$$6I_2 - 6 + 5I_2 = 22$$

$$11I_2 = 28$$

$$I_2 = \frac{28}{11} \text{ A}$$

Put I_2 in eqⁿ (1)

$$2\left(\frac{28}{11}\right) - I_1 = 2$$


$$\frac{56}{11} - 2 = I_1$$

$$I_1 = \frac{56 - 22}{11} = \frac{34}{11}$$

$$I_1 = \frac{34}{11} \text{ A}$$

Current through load = $I_1 + I_2 = \frac{62}{11} \text{ A}$

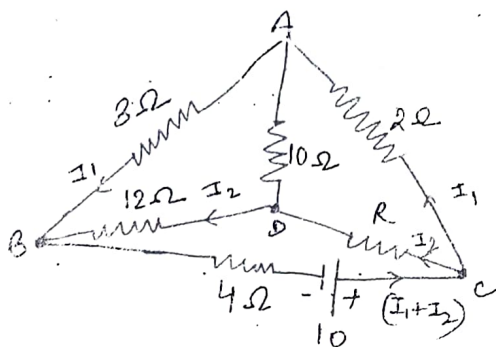6. Find the value of resistance R and current in the branch AD carries no current.



$$R = ?$$

$$I_R = I_2 = ?$$

In mesh ABDA,

$$3I_1 - 12I_2 = 0 \quad \text{--- (1)}$$

In mesh ADCA,

$$2I_1 - RI_2 = 0 \quad \text{--- (2)}$$

from eqn (1)

$$3I_1 = 12I_2$$

$$I_1 = 4I_2 \quad \text{--- (3)}$$

Put I_1 in eqn (2)

$$2(4I_2) - RI_2 = 0$$

$$8I_2 - RI_2 = 0$$

$$(8 - R)I_2 = 0$$

$$8 - R = 0$$

$$\boxed{R = 8\Omega}$$

Apply KVL in mesh

$$-10 + 4(I_1 + I_2) - R I_2 - 2I_1 = 0$$

$$10 = 4I_1 + 4I_2 - RI_2 - 2I_1$$

$$10 = 4I_1 + 16I_2 + 8I_2$$

$$10 = 4I_1 + 24I_2$$

$$5 = 2I_1 + 12I_2 \quad \text{--- (4)}$$

Put eqn (3) in (4)


$$5 = 2(4I_2) + 12I_2$$

$$5 = 8I_2 + 12I_2$$

$$5 = 20I_2$$

$$\boxed{I_2 = \frac{5}{20} = 0.25 \text{ A}}$$

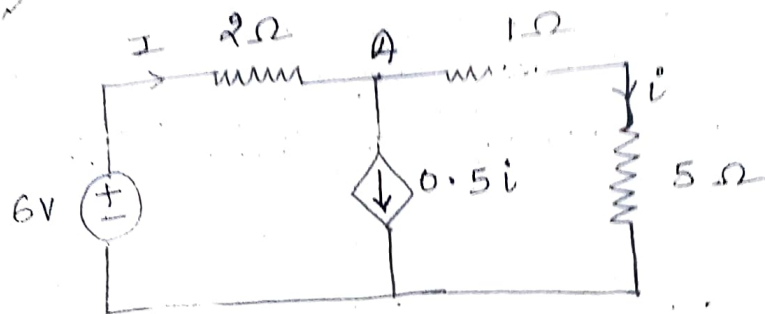Q7 Determine the current through 5Ω resistor.



Apply KCL at node A.

$$I = 0.5i + i$$

$$I = 1.5i \quad \text{--- (1)}$$

Apply KVL in outer loop,

$$-6 + 2I + i + 5i = 0$$

$$-6 + 2I + 6i = 0 \quad \text{--- (2)}$$

Put (1) in (2):


$$-6 + 2(1.5i) + 6i = 0$$

$$-6 + 3.0i + 6i = 0$$

$$6 = 9i$$

$$i = \frac{2}{3} \text{ A}$$

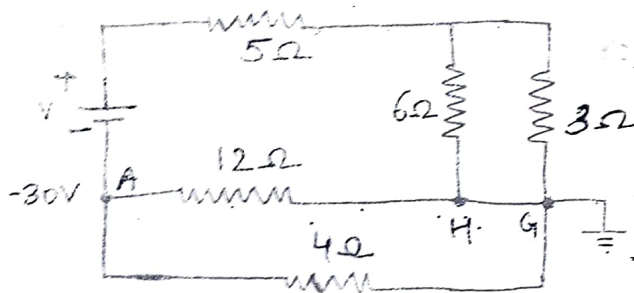Q5 In fig. the potential of point A = $-30V$. Using KCL & KVL find (a) value of V & (b) power dissipated by 5Ω resistance.



Sol potential at pt A = $-30V$
& at pt. G = $0V$.


p.d. across 12Ω resistor connected between H & G.
= $30V$

current flow through 12Ω resistor = $\frac{30}{12} = 2.5A$

& dirⁿ is $\leftarrow$ b/c current

higher potential to lower potential.

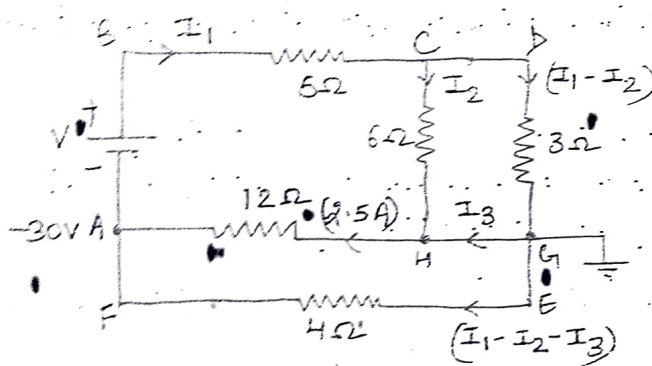Before applying KCL & KVL, first indicate current in each branch.



At node H, Apply KCL

$$I_2 + I_3 = 2.5 \quad \text{--- (1)}$$

Apply KVL in ABCHA

$$-V + 5I_1 + 6I_2 + 12(2.5) = 0$$

$$V = 5I_1 + 6I_2 + 30 \quad \text{--- (2)}$$

Apply KVL in CDGH

$$3(I_1 - I_2) - 6I_2 = 0$$

$$3I_1 - 3I_2 - 6I_2 = 0$$

$$3I_1 - 9I_2 = 0$$

$$I_1 - 3I_2 = 0 \quad \text{--- (3)}$$

Apply KVL in AMGEF

$$4(I_1 - I_2 - I_3) - 12(2.5) = 0$$

$$4I_1 - 4I_2 - 4I_3 = 30 \quad \text{--- (4)}$$

From (1)

$$I_3 = 2.5 - I_2$$

Put I_3 in eq (4)

$$4I_1 - 4I_2 - 4(2.5 - I_2) = 30$$

$$4I_1 - 4I_2 - 10.0 + 4I_2 = 30$$

$$4I_1 = 30 + 10$$

$$I_1 = \frac{40}{4} = 10 \text{ A}$$

$$\boxed{I_1 = 10 \text{ A}}$$

Put I_1 in eq (3)

$$10 - 3I_2 = 0$$

$$\boxed{I_2 = \frac{10}{3}}$$

Put I_1 & I_2 in eq (2)

$$\begin{aligned} V &= 5(10) + 6\left(\frac{10}{3}\right) + 30 \\ &= 50 + 20 + 30 \end{aligned}$$


Power dissipated by
5Ω resistance =

$$P = I_1^2 R$$

$$\boxed{P = 10 \times 10 \times 5 = 500 \text{ W}}$$

Applying Kirchhoff's current law, determine current I_2

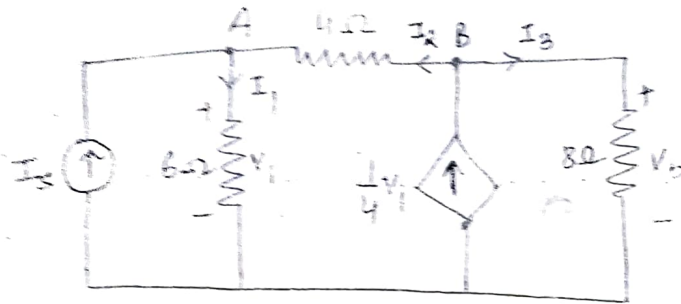in the electric circuit. Take $V_0 = 16V$



Soln

At node A, Apply KCL.

$$I_s + I_2 = I_1$$

$$I_s + \frac{V_0 - V_1}{4} = \frac{V_1}{6}$$

$$I_s + 4 - \frac{V_1}{4} = \frac{V_1}{6}$$

$$I_s + 4 = V_1 \left(\frac{1}{6} + \frac{1}{4} \right)$$

$$I_s + 4 = \frac{5V_1}{12} \quad \text{--- (1)}$$

At node B

$$\frac{1}{4}V_1 = I_2 + I_3$$

$$\frac{1}{4}V_1 = \frac{V_0 - V_1}{4} + \frac{V_0}{8}$$

$$\frac{V_1}{4} = 4 - \frac{V_1}{4} + 2$$

$$\frac{V_1}{4} + \frac{V_1}{4} = 6$$

$$\frac{2V_1}{4} = 6$$

$$V_1 = 6 \times \frac{4}{2}$$

$$\boxed{V_1 = 12V}$$



Put V_1 in eq (1)

$$I_s + 4 = \frac{5 \times 12}{12}$$

$$I_s = 5 - 4 = 1$$

$$\boxed{I_s = 1A}$$

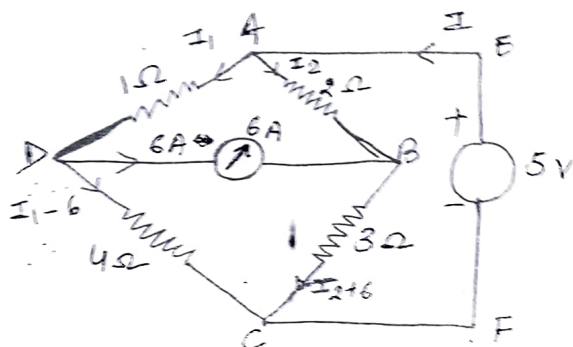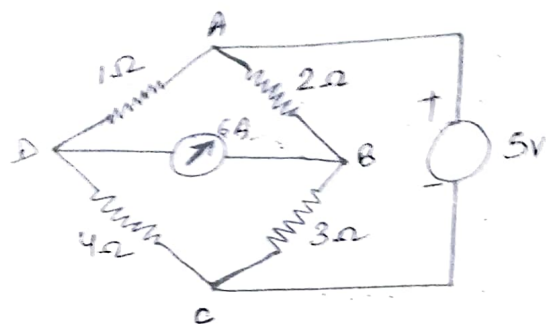Find the total power delivered to the circuit by the sources.



Apply KVL in AEFCBA,

$$-5 + 2I_2 + 3(I_2 + 6) = 0$$

$$2I_2 + 3I_2 + 18 - 5 = 0$$

$$5I_2 + 13 = 0$$

$$I_2 = -\frac{13}{5} \text{ A} = -2.6 \text{ A} \quad \text{--- (1)}$$

Apply KVL in ABDA,

$$2I_2 + 3(I_2 + 6) - 4(I_1 - 6) - I_1 = 0$$

$$2I_2 + 3I_2 + 18 - 4I_1 + 24 - I_1 = 0$$

$$5I_2 - 5I_1 + 42 = 0$$

$$5 \left[-\frac{13}{5} \right] - 5I_1 = -42$$


$$-13 + 42 = 5I_1$$

$$\frac{29}{5} = I_1 = 5.8 \text{ A} \quad \text{--- (2)}$$


Total power delivered by two sources =
Total power absorbed by the circuit =

$$\begin{aligned} & (I_2^2 \times 2) + (I_2 + 6)^2 \times 3 + \\ & + (I_1 - 6)^2 \times 4 + I_1^2 \times 1 \\ & = (-2.6)^2 \times 2 + (-2.6 + 6)^2 \times 3 \\ & + (5.8 - 6)^2 \times 4 + (5.8)^2 \times 1 \\ & = \underline{\underline{82 \text{ W}}} \end{aligned}$$

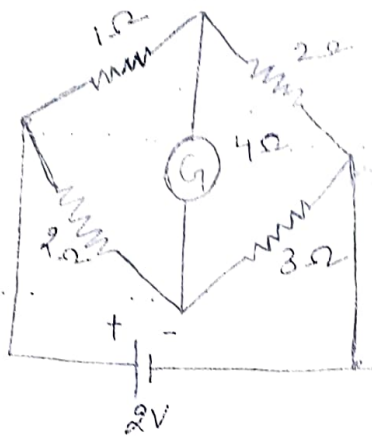Calculate the current through the galvanometer in the following bridge.



Soln

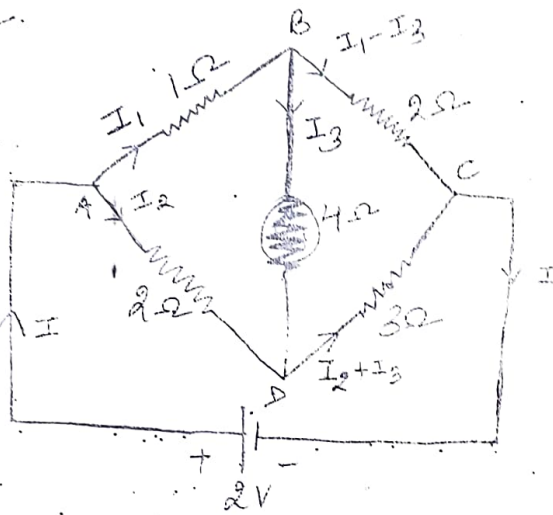

Apply KVL in mesh ABDA

$$I_1 + 4I_3 - 2I_2 = 0 \quad \text{--- (1)}$$

Apply KVL in mesh BCDB

$$2(I_1 - I_3) + 3(I_2 + I_3) - 4I_3 = 0$$

$$2I_1 - 2I_3 - 3I_2 + 3I_3 - 4I_3 = 0$$

$$2I_1 - 3I_2 - 9I_3 = 0 \quad \text{--- (2)}$$

In mesh ADCA

$$-2 + 2I_2 + 3(I_2 + I_3) = 0$$

$$-2 + 2I_2 + 3I_2 + 3I_3 = 0$$

$$-2 + 5I_2 + 3I_3 = 0$$

from (3)

$$-I_2 + 5I_2 + 3I_3 = 0$$

$$3I_3 = I_2 - 5I_2$$

$$I_3 = \left(\frac{I_2 - 5I_2}{3} \right)$$

Put I_3 in (1)

$$I_1 + 4I_3 - 2I_2 = 0$$

$$I_1 + 4 \left(\frac{I_2 - 5I_2}{3} \right) - 2I_2 = 0$$

$$I_1 + \frac{(8 - 20I_2)}{3} - 2I_2 = 0$$

$$3I_1 + 8 - 20I_2 - 6I_2 = 0$$

$$3I_1 + 8 - 26I_2 = 0$$

$$3I_1 - 26I_2 = -8 \quad \text{--- (4)}$$

$$3I_1 = 26I_2 - 8$$

$$I_1 = \frac{26I_2 - 8}{3} \quad \text{--- (5)}$$

Put I_1 & I_3 in eqn (2)

$$2 \left(\frac{26I_2 - 8}{3} \right) - 3I_2 - 9 \left(\frac{I_2 - 5I_2}{3} \right) = 0$$

$$\frac{52I_2 - 16}{3} - 3I_2 - \frac{(18 - 45I_2)}{3} = 0$$

$$52I_2 - 16 - 9I_2 - 18 + 45I_2 = 0$$

$$43I_2 + 45I_2 - 34 = 0$$

$$88I_2 = 34$$

$$I_2 = + \frac{34}{88} A = 17 A$$

$$= \frac{(26 \times 17) - 8}{3}$$

$$= \frac{26 \times 17 - 8 \times 1}{3 \times 1} = \frac{442 - 8}{3} = \frac{434}{3}$$

Put I_2 in (5)

$$I_1 = \frac{26 \left(\frac{17}{22} \right) - 8}{3}$$

$$= \frac{13 \cdot 17 - 8 \times 22}{22 \times 3}$$

$$= \frac{221 - 176}{66}$$

$$= \frac{45}{66} = \frac{15}{22} = 15A$$

Put I_2 in eqn of I_3

$$I_3 = \frac{I_2 - 5I_2}{3}$$


$$= \frac{88 - 85}{44 \times 3}$$

$$= \frac{3}{44 \times 3} = \frac{1}{44}$$

$$I_3 = \frac{1}{44}$$

$$\begin{array}{r} 13 \\ 11 \ 2 \\ \hline 91 \\ 13 \ 2 \\ \hline 126 \\ 52 \ 1 \\ \hline 178 \end{array}$$

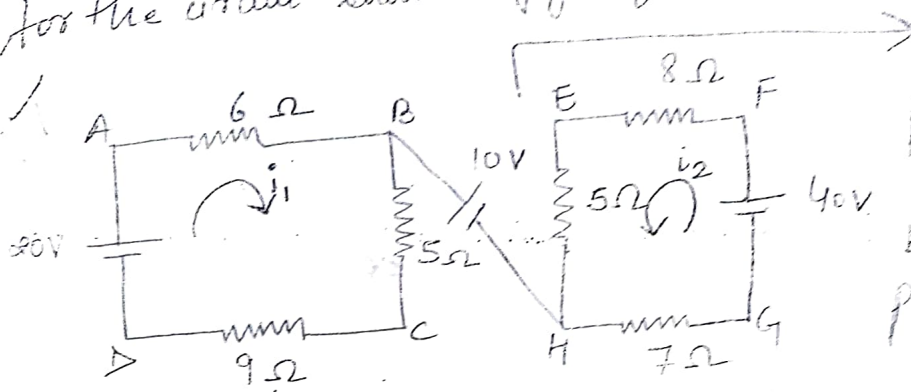Q.11 For the circuit shown in fig. find V_{CE} and V_{AG}



No path is there by 10V DC for closed path $\rightarrow$ wrong leave from point and we enter the same point 10V is just a potential difference between B & H

Let i_1 be the current flow in mesh ABCH.

$$i_1 = \frac{20}{6+5+9} = \frac{20}{20} = 1$$

$$i_1 = 1A$$

Let i_2 be the current flow in mesh EFGH.

$$i_2 = \frac{40}{5+7+8} = \frac{40}{20} = 2$$

$$i_2 = 2A$$

for V_{CE} , we can find out the value by taking the algebraic sum of the voltage drops met on the way from point C to E.

$$V_{CE} = (-5 \times 1) + 10 - (5 \times 2) = -5 + 10 - 10 = -5V$$


Blg, for V_{AG} , we proceed from A to G.

$$V_{AG} = (6 \times 1) + 10 + (7 \times 2) = 6 + 10 + 14 = 30V$$

$$V_{AG} = 30V$$

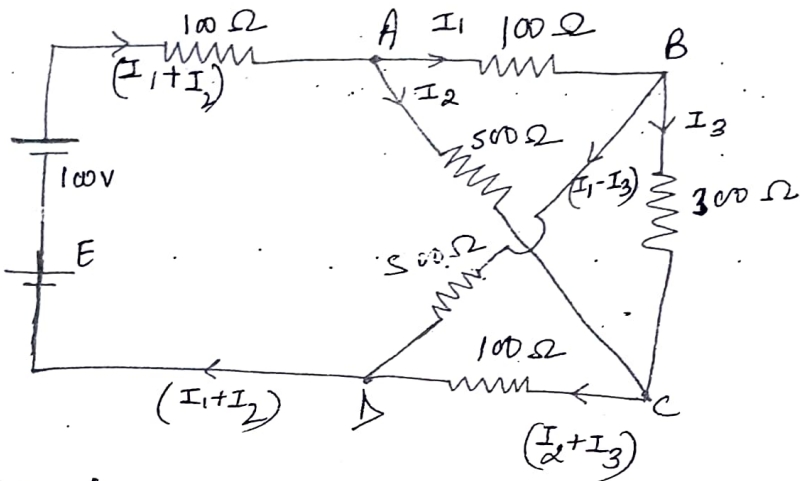Q. 12

Determine the current supplied by the bat in the circuit as shown in fig.



Apply KVL in mesh ABCA,

$$100I_1 + 300I_3 - 500I_2 = 0$$

$$100(I_1 + 3I_3 - 5I_2) = 0$$

$$I_1 + 3I_3 - 5I_2 = 0 \quad \text{--- (1)}$$

Apply KVL in mesh BCDB,

$$300I_3 + 100(I_2 + I_3) - 500(I_1 - I_3) = 0$$

$$300I_3 + 100I_2 + 100I_3 - 500I_1 + 500I_3 = 0$$

$$-500I_1 + 100I_2 + 900I_3 = 0$$

$$-5I_1 + I_2 + 9I_3 = 0 \quad \text{--- (2)}$$

$$5I_1 - I_2 - 9I_3 = 0 \quad \text{--- (2)}$$

Apply KVL in mesh ABDEA

$$100I_1 + 500(I_1 - I_3) - 100 + 100(I_1 + I_2) = 0$$

$$100I_1 + 500I_1 - 500I_3 - 100 + 100I_1 + 100I_2 = 0$$

$$700I_1 + 100I_2 - 500I_3 = 100$$

$$100(7I_1 + I_2 - 5I_3) = 100$$

consider 3 eqⁿs.

$$I_1 - 5I_2 + 3I_3 = 0 \quad \text{--- (1)}$$

$$5I_1 - I_2 - 9I_3 = 0 \quad \text{--- (2)}$$

$$7I_1 + I_2 - 5I_3 = 1 \quad \text{--- (3)}$$

Method 1

Solve by using Matrix Method (Cramer's Rule)

$$\begin{bmatrix} 1 & -5 & 3 \\ 5 & -1 & -9 \\ 7 & 1 & -5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$$

$$\begin{aligned} \Delta &= \begin{vmatrix} 1 & -5 & 3 \\ 5 & -1 & -9 \\ 7 & 1 & -5 \end{vmatrix} = 1(5 - (-9)) + 5(-25 + 63) + 3(5 + 7) \\ &= 14 + 5(38) + 3(12) \\ &= 14 + 190 + 36 \end{aligned}$$

$$\boxed{\Delta = 240}$$

$$\begin{aligned} \Delta_1 &= \begin{vmatrix} 0 & -5 & 3 \\ 0 & -1 & -9 \\ 1 & 1 & -5 \end{vmatrix} = 0 + 5(0 + 9) + 3(0 + 1) \\ &= 45 + 3 \end{aligned}$$

$$\boxed{\Delta_1 = 48}$$

$$\begin{aligned} \Delta_2 &= \begin{vmatrix} 1 & 0 & 3 \\ 5 & 0 & -9 \\ 7 & 1 & -5 \end{vmatrix} = 1(0 + 9) - 0 + 3(5) \\ &= 9 + 15 \end{aligned}$$

$$\boxed{\Delta_2 = 24}$$

$$A_3 = \begin{bmatrix} 1 & -5 & 0 \\ 5 & -1 & 0 \\ 7 & 1 & 1 \end{bmatrix}$$

$$= 1(-1) + 5(5-0) + 0$$

$$= -1 + 25$$

$$\boxed{A_3 = 24}$$

$$I_1 = \frac{A_1}{\Delta} = \frac{48}{240} = \frac{1}{5} \text{ A}$$

$$I_2 = \frac{A_2}{\Delta} = \frac{24}{240} = \frac{1}{10} \text{ A}$$

$$I_3 = \frac{A_3}{\Delta} = \frac{24}{240} = \frac{1}{10} \text{ A}$$

$$I = (I_1 + I_2) = \frac{1}{5} + \frac{1}{10} = \frac{2+1}{10} = \frac{3}{10} \text{ A}$$

Method 2's

Consider eqn ③

$$7I_1 + I_2 - 5I_3 = 1$$

Obtain I_3

$$7I_1 + I_2 - 1 = 5I_3$$

$$I_3 = \left(\frac{7I_1 + I_2 - 1}{5} \right)$$