
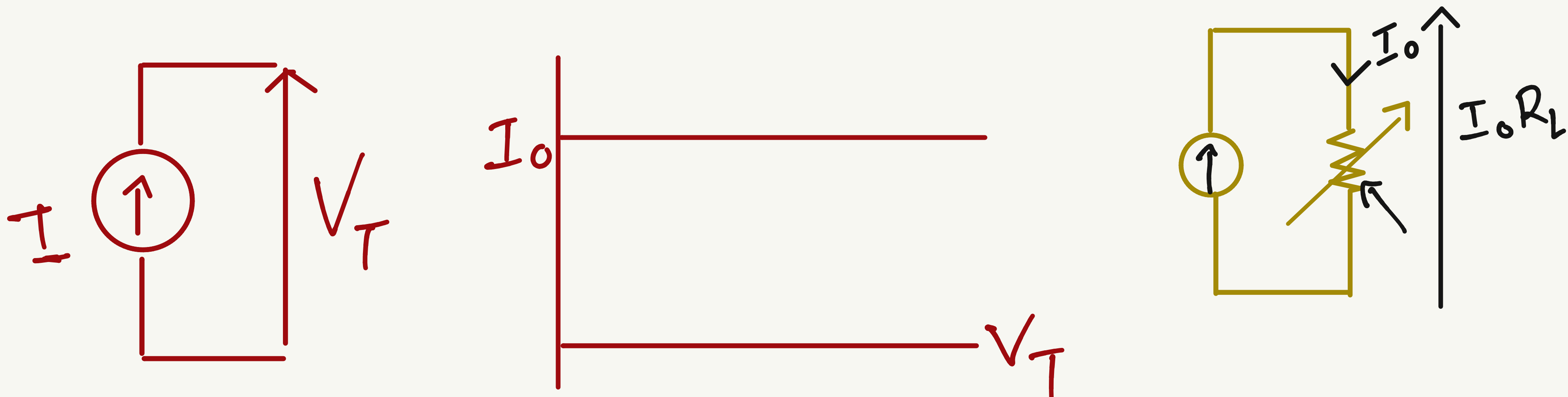


Ideal current source

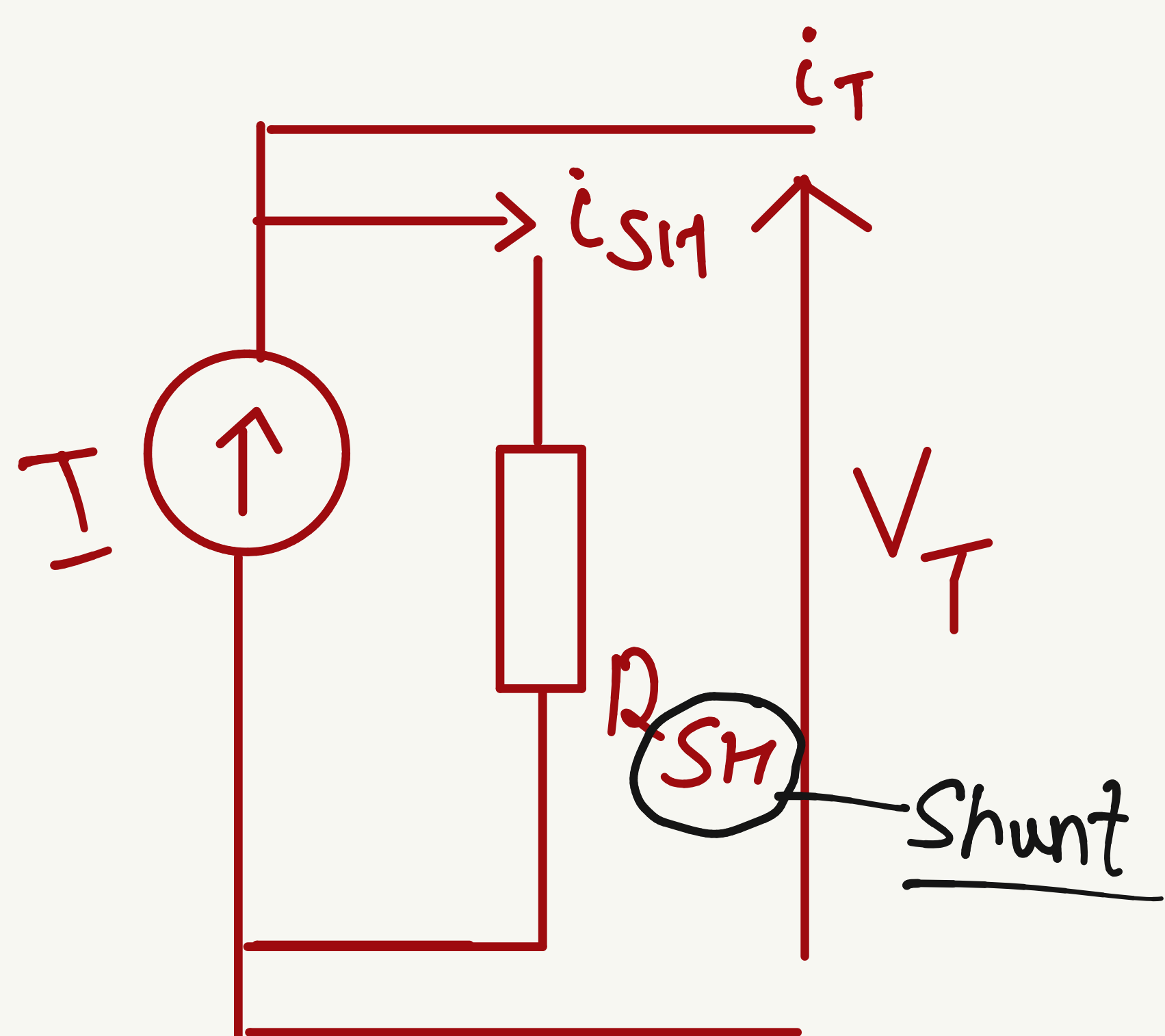


Practical current source



$$I = i_T + i_{SH}$$



$$I = i_T + \frac{V_T}{R_{SH}}$$

$$i_T = I - \frac{V_T}{R_{SH}}$$

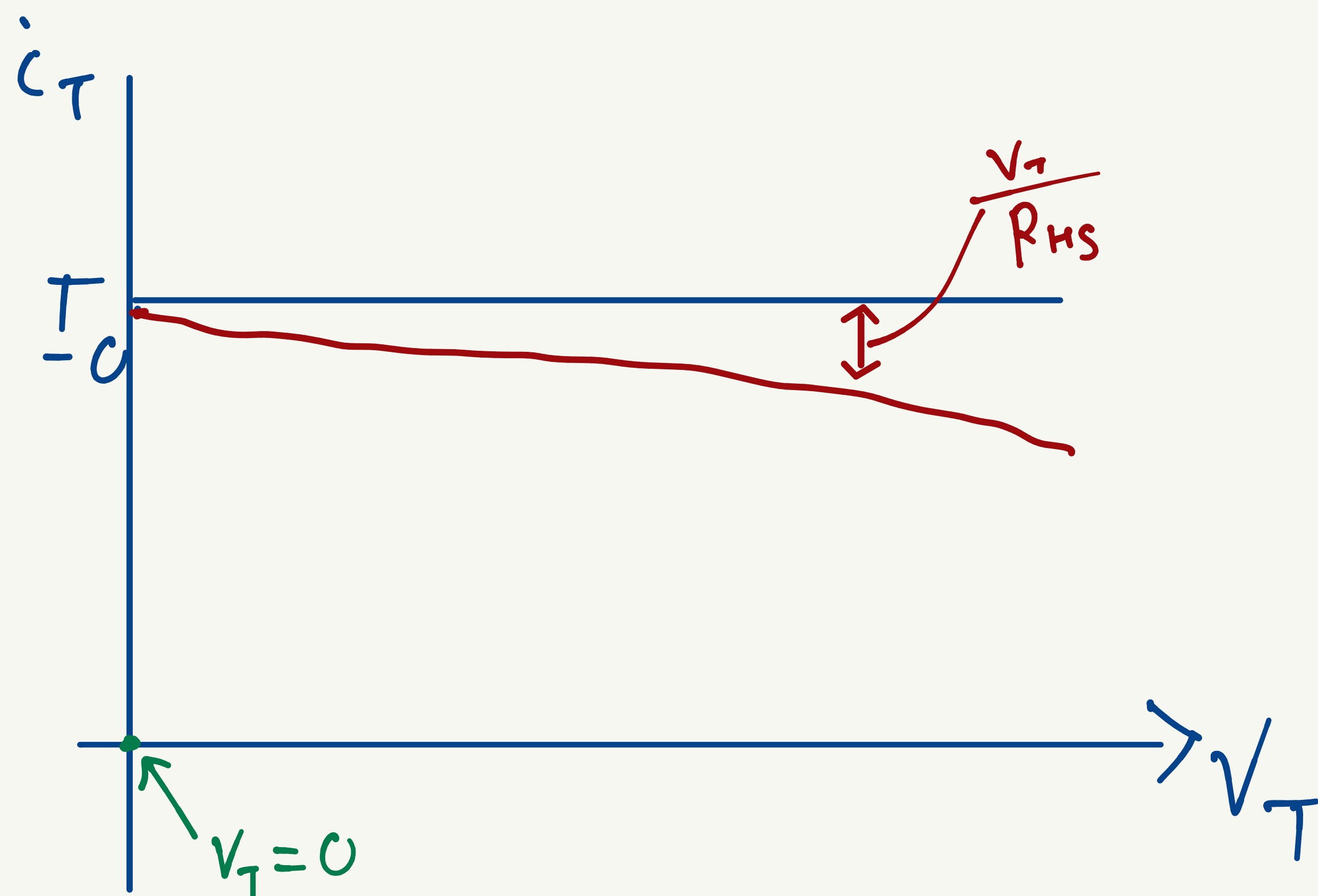

① Example

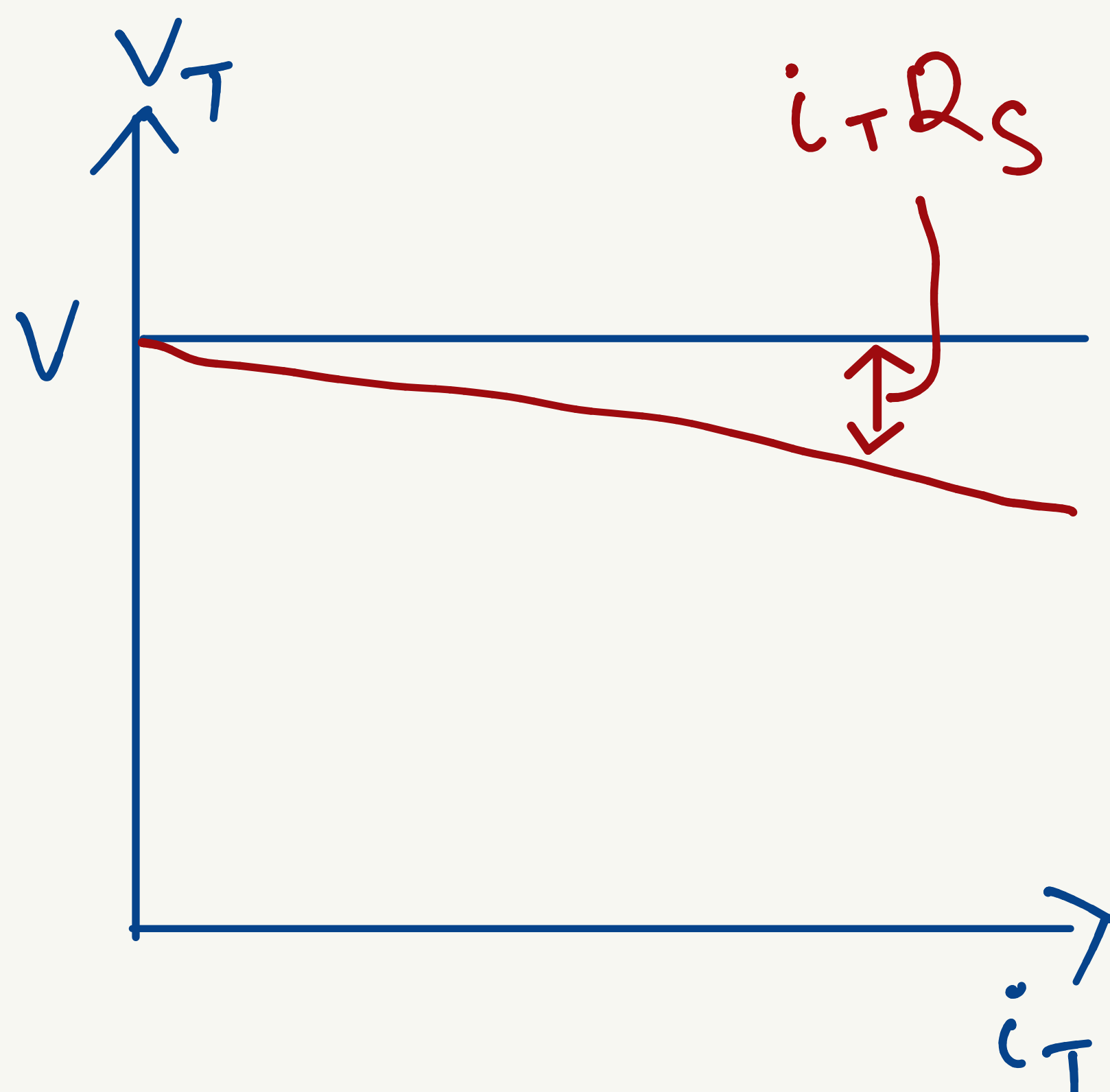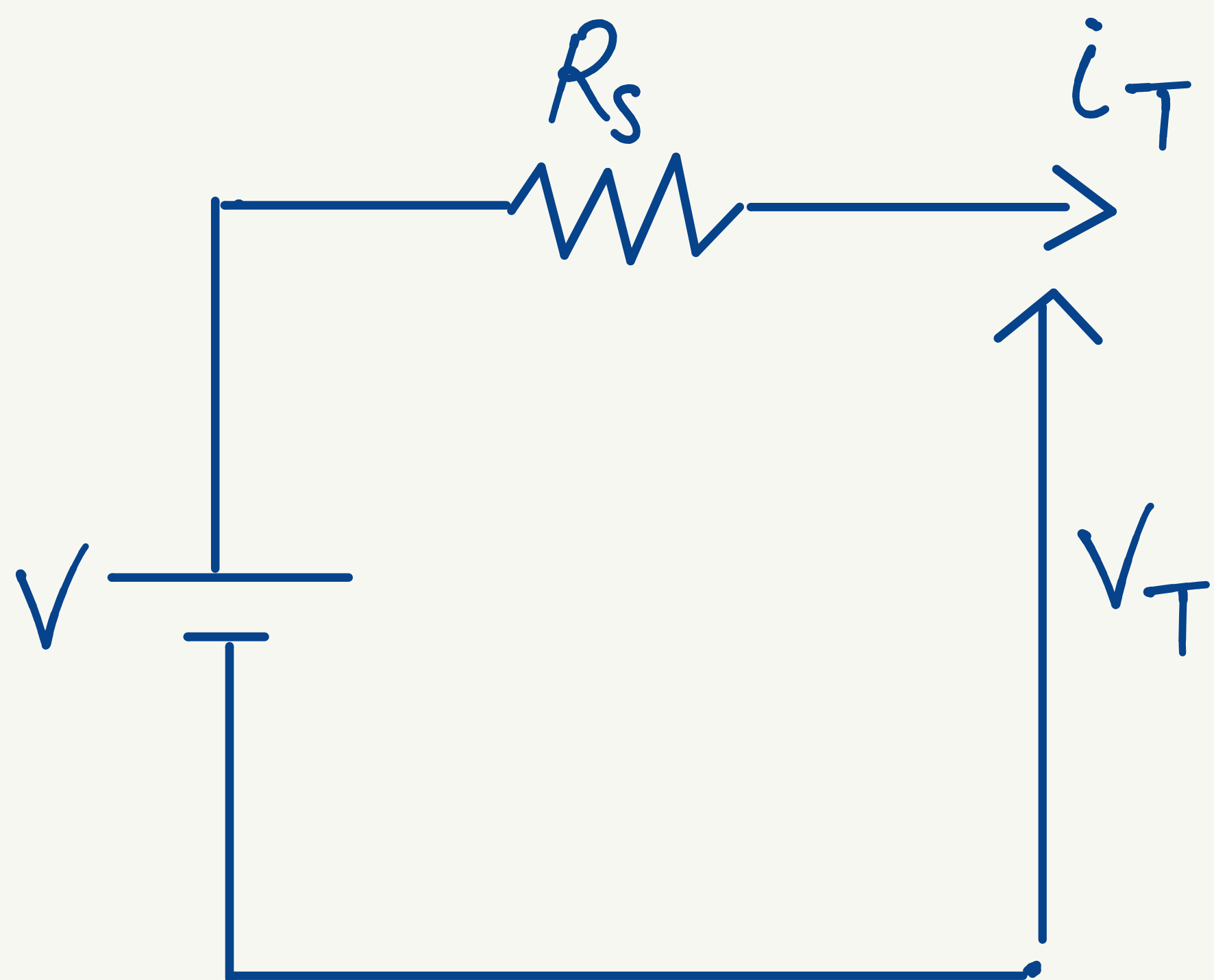Battery $\rightarrow$ voltage source.
(practical)



* Power supply (AC) $\rightarrow$ voltage source (practical)


* Solar source $\rightarrow$ practical current source.

which on $\rightarrow$ voltage source
 $\rightarrow$ current source

① No superconductor.

* Source Transformation

① Valid only for practical source.

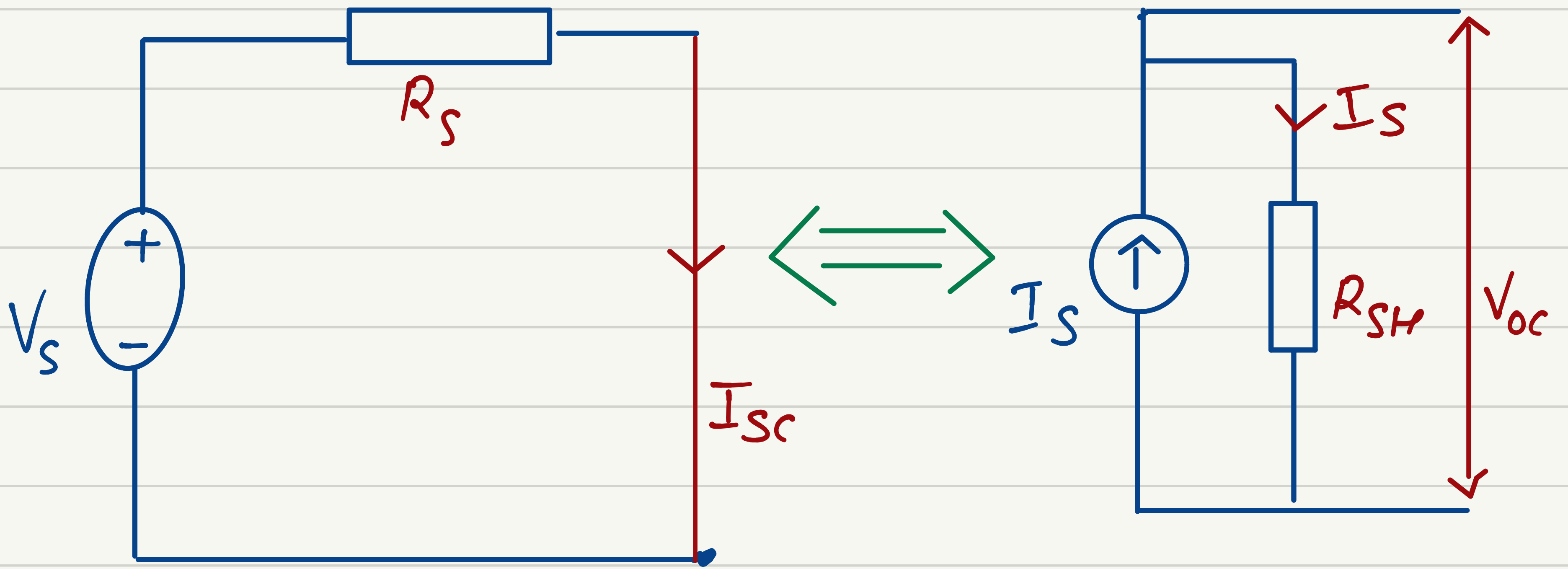


$$I_{sc} = \frac{V_s}{R_s} = I_s$$

&
 $R_s = R_{sh}$ (||)
 ↓
 parallel

$$V_{oc} = I_s R_{sh} = V_s$$

&
 $R_s = R_{sh}$ (series)


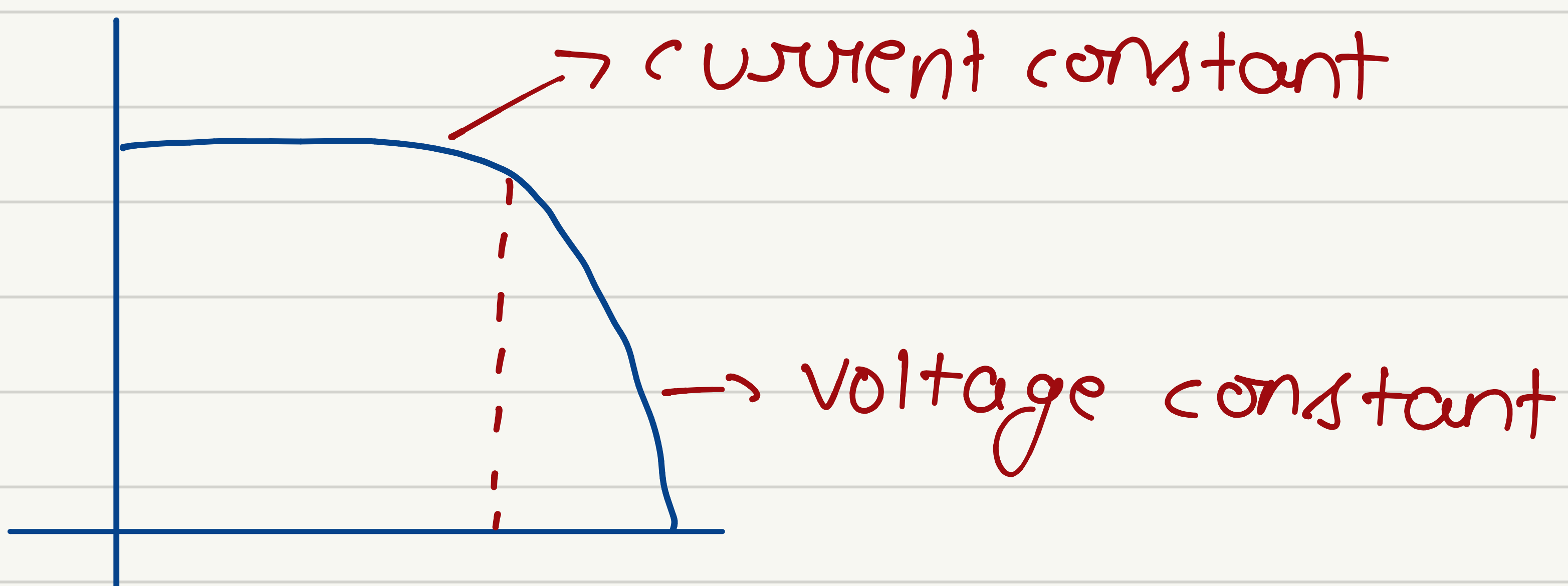


* Dependent sources (controlled sources)


① Voltage dependent voltage source

Voltage controlled voltage source

(VCVS)
VDVS

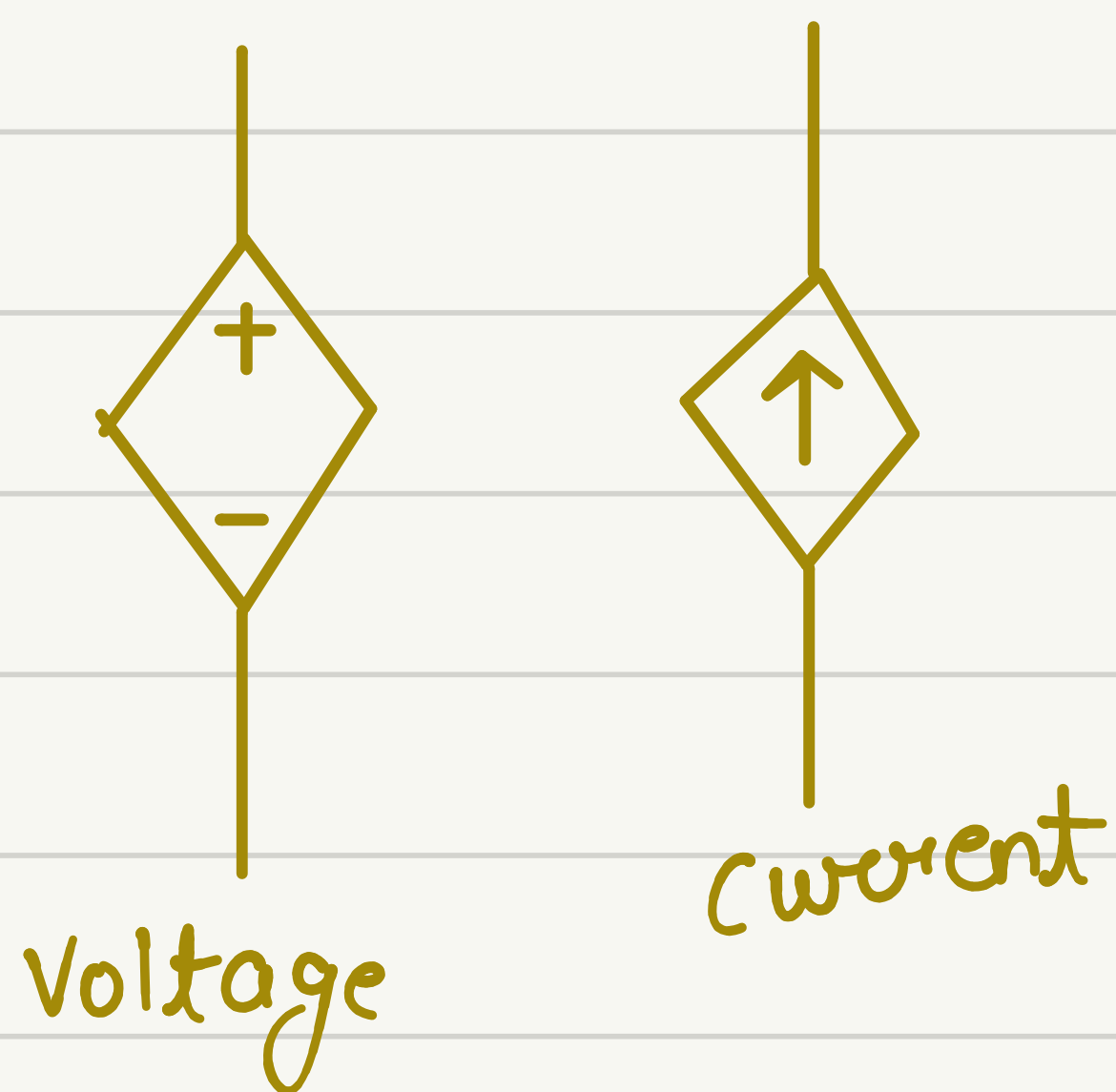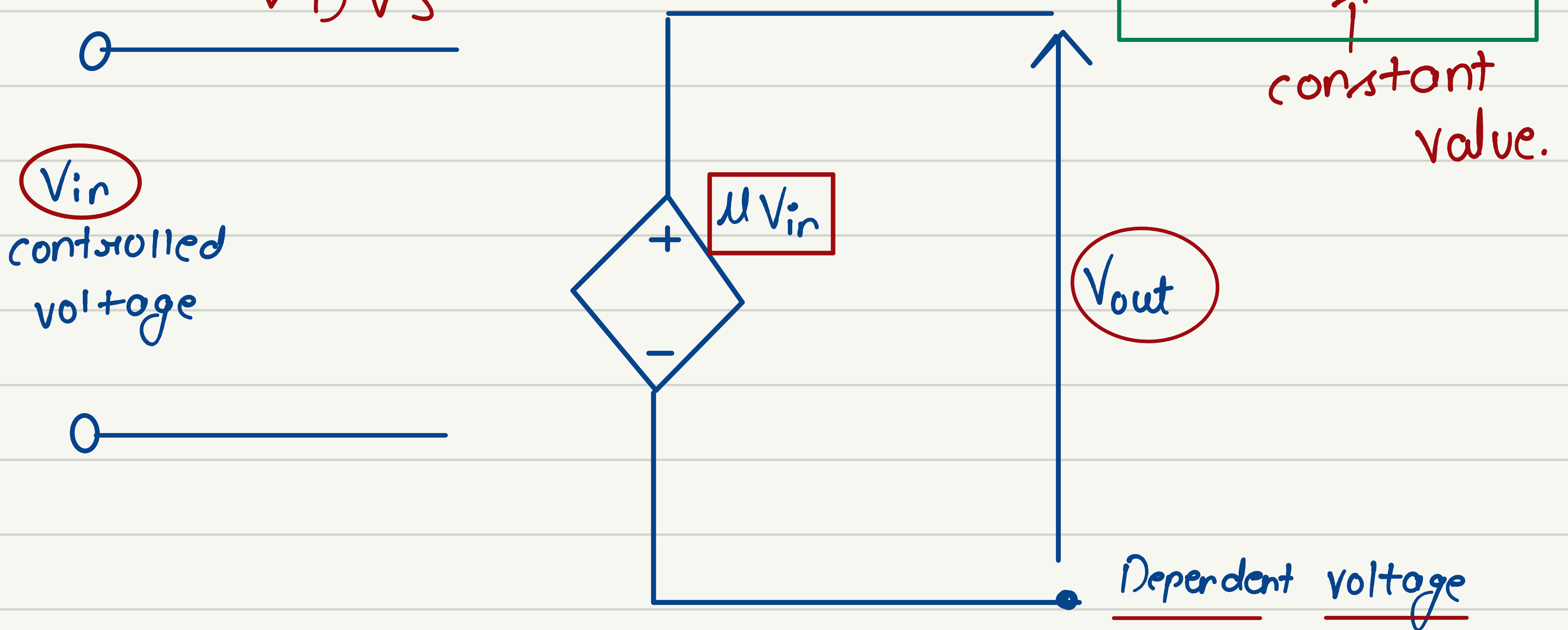


Transistor circuit

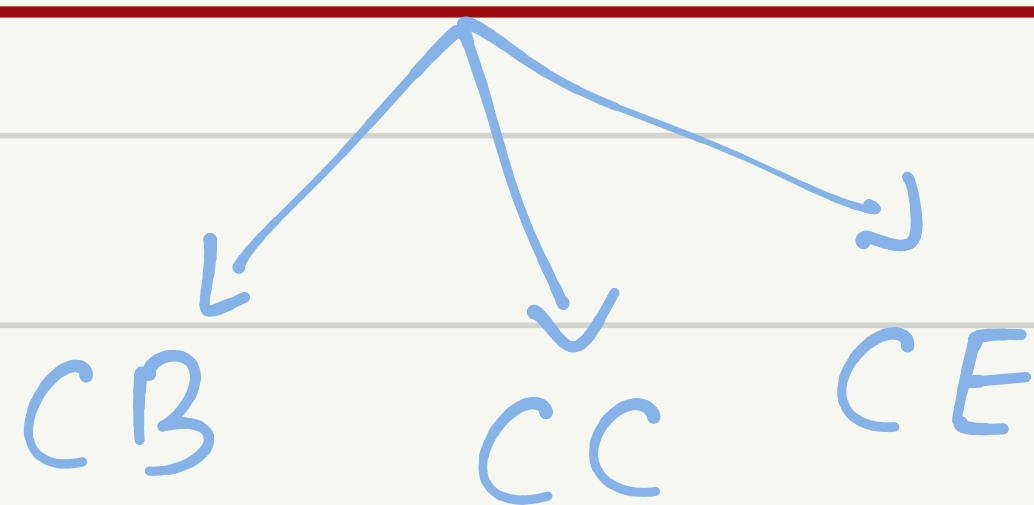


② CCVS


current controlled voltage source

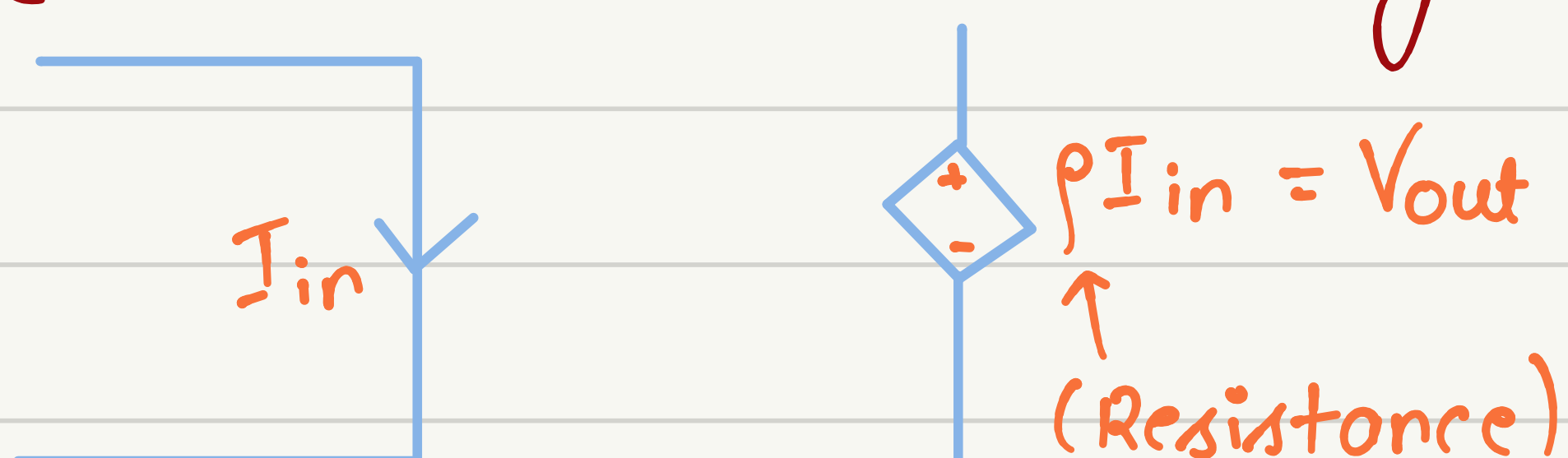



③ VCCS

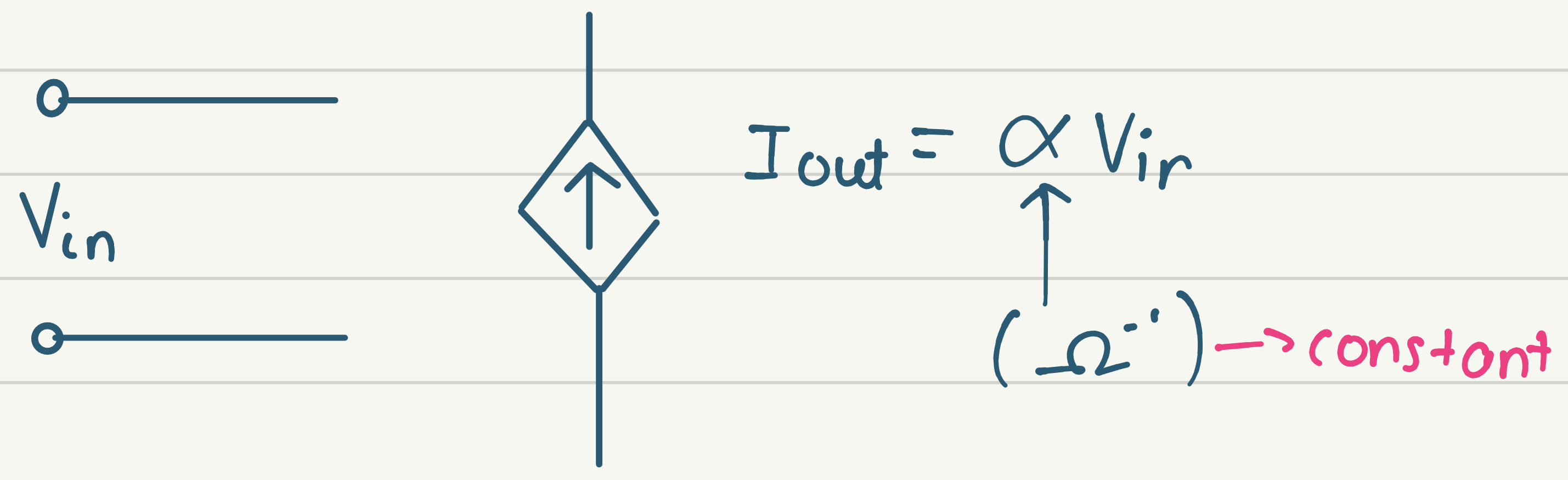


④ CCCS

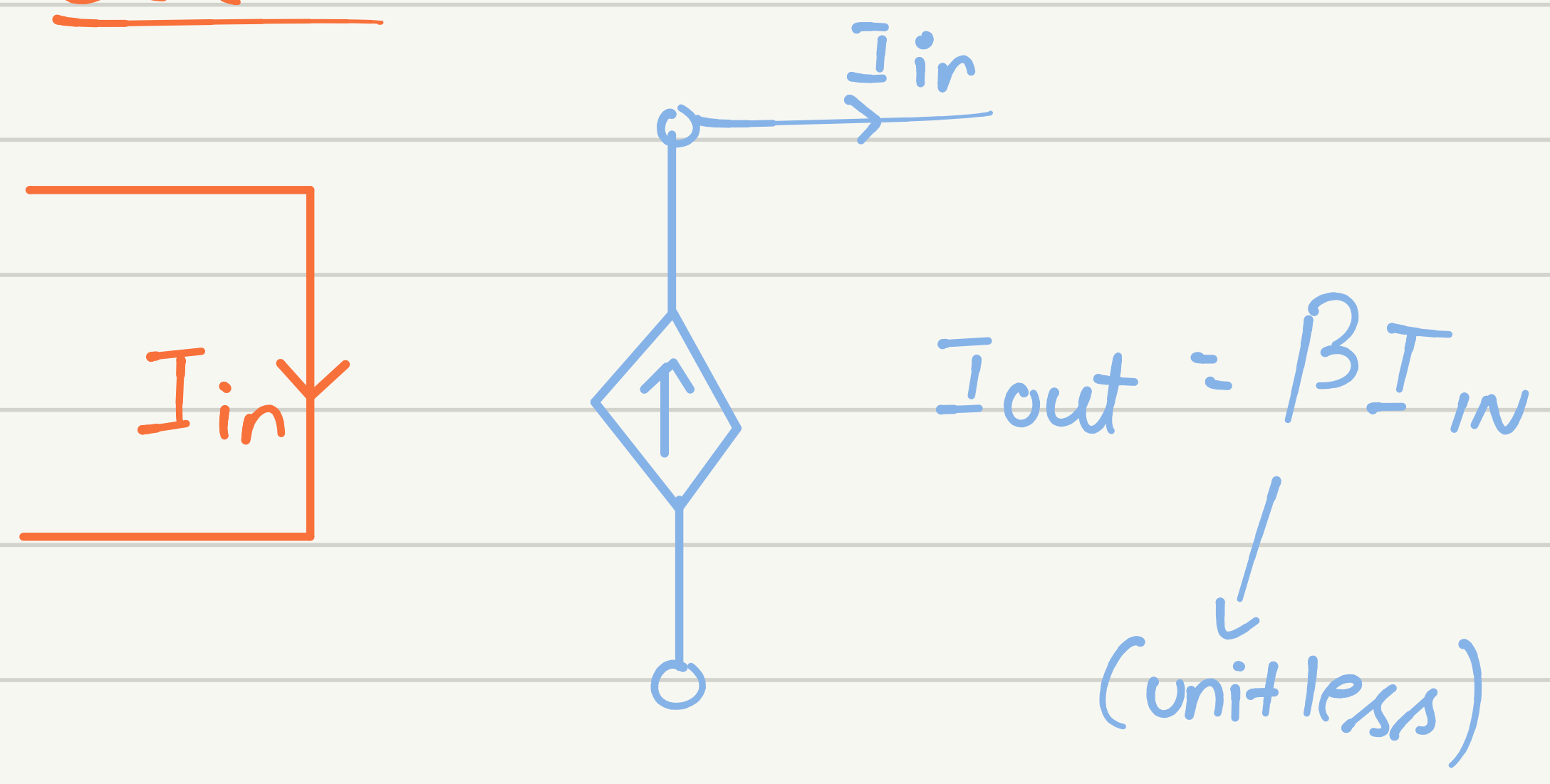

• Passive Elements

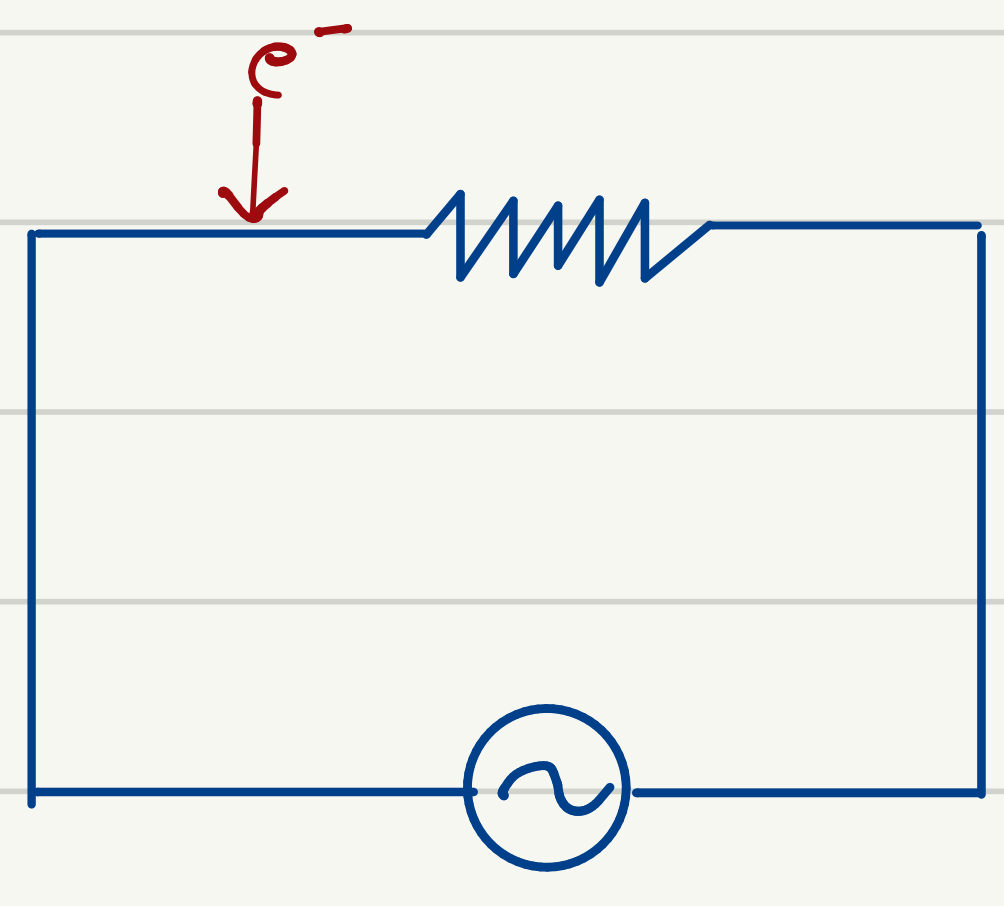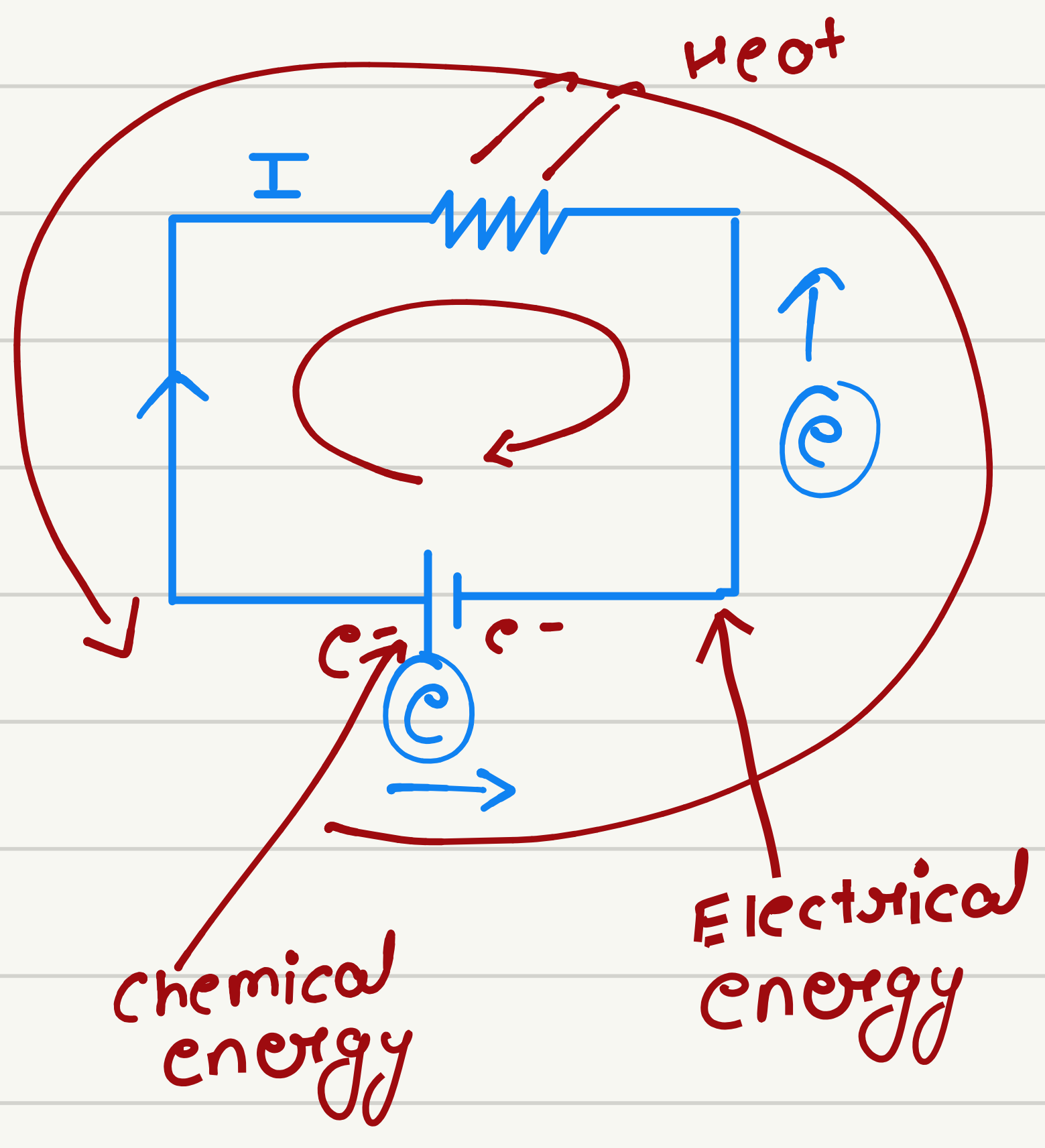

50 Hz
T = 20 ms

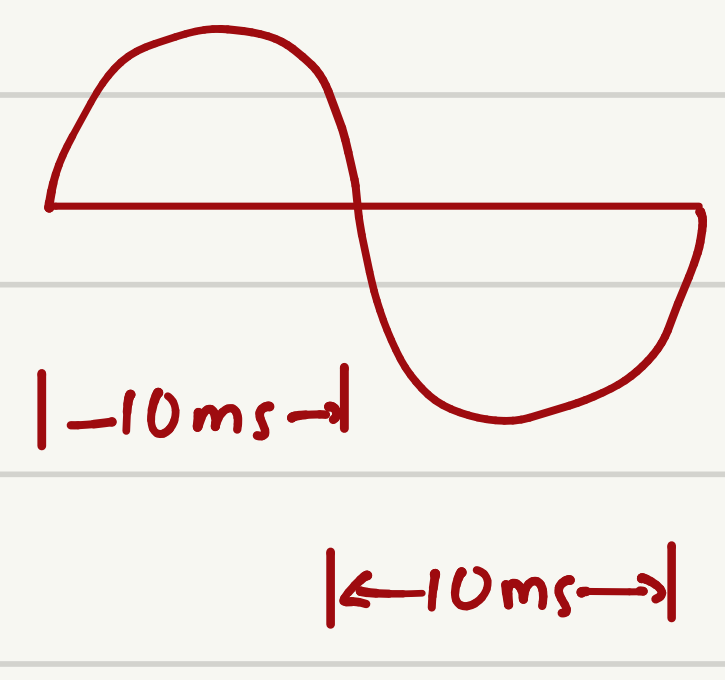


$$V = IR$$

Excitation $\rightarrow V$

Response $\rightarrow I \Rightarrow I = \frac{V}{R}$

Excitation $\rightarrow I$

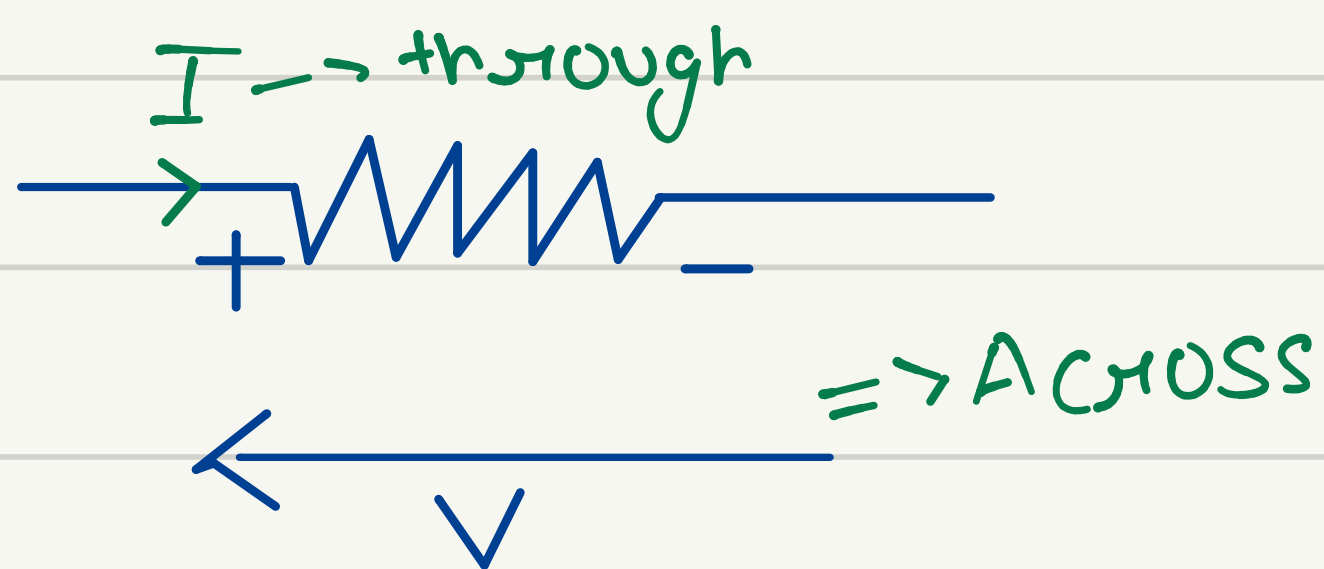Response $\rightarrow V \Rightarrow V = IR$




• L & C
memory

$\rightarrow$ initial condition is important

$$V_L = L \frac{di_L}{dt}$$

$$i_C = C \frac{dv_C}{dt}$$

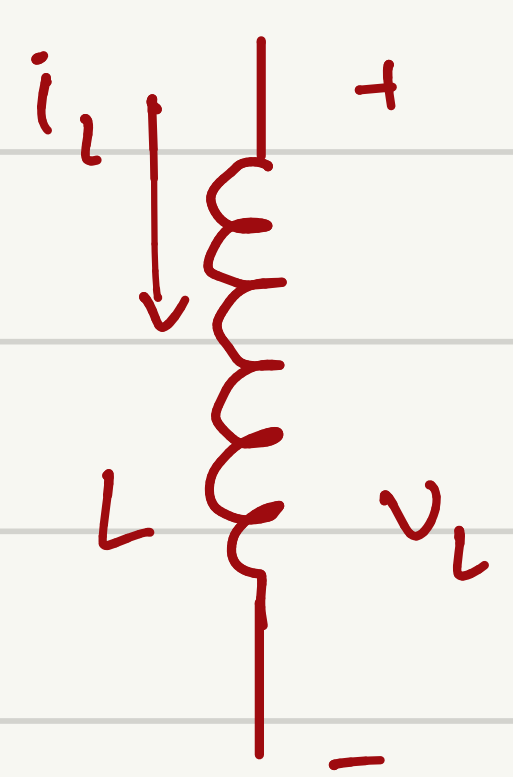* Ohm's law for induction (cause effect relationship)



i_L

v_L



L

$$V_L = L \frac{di_L}{dt}$$

$V = V_L(t)$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t V(t) dt$$
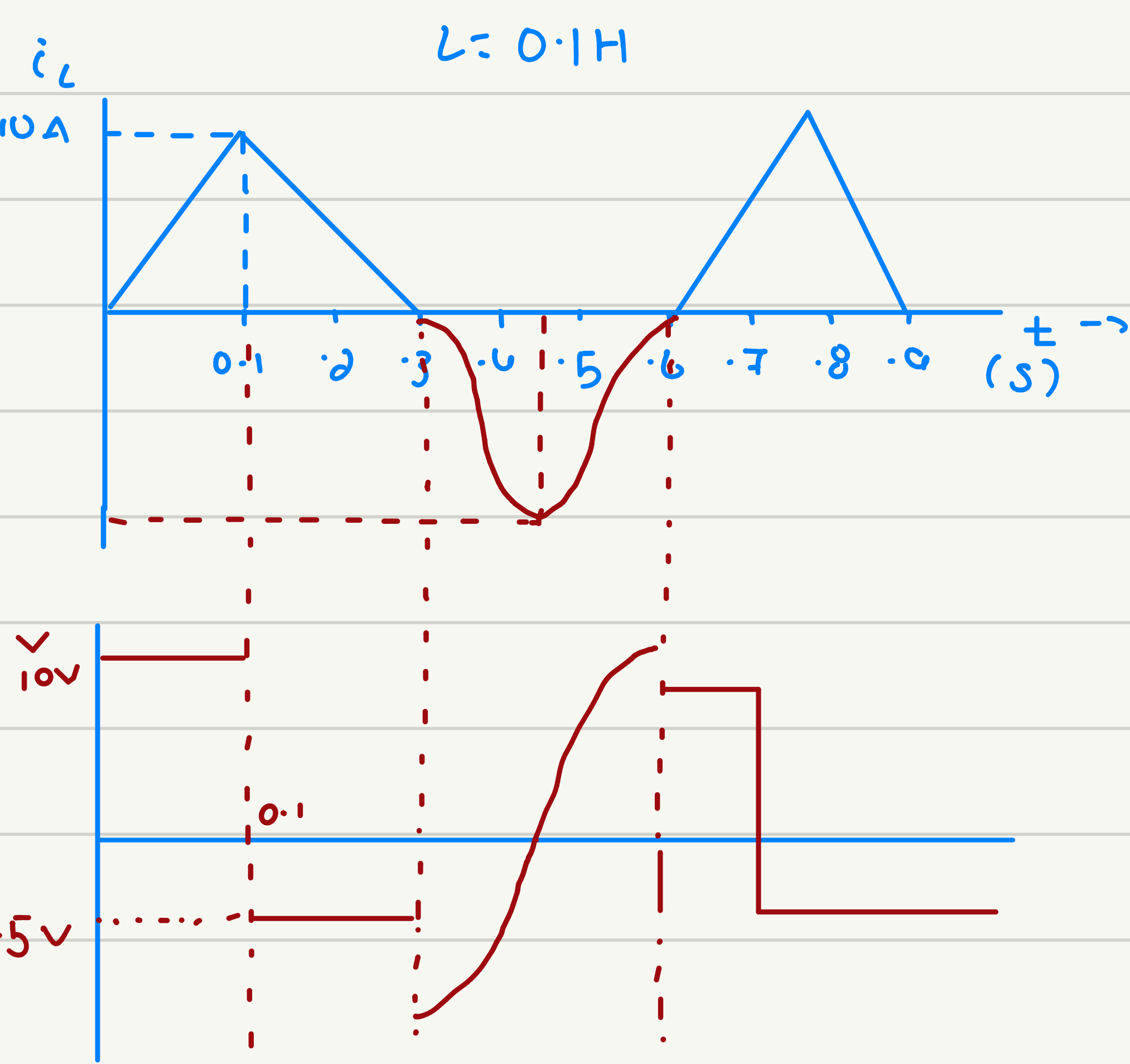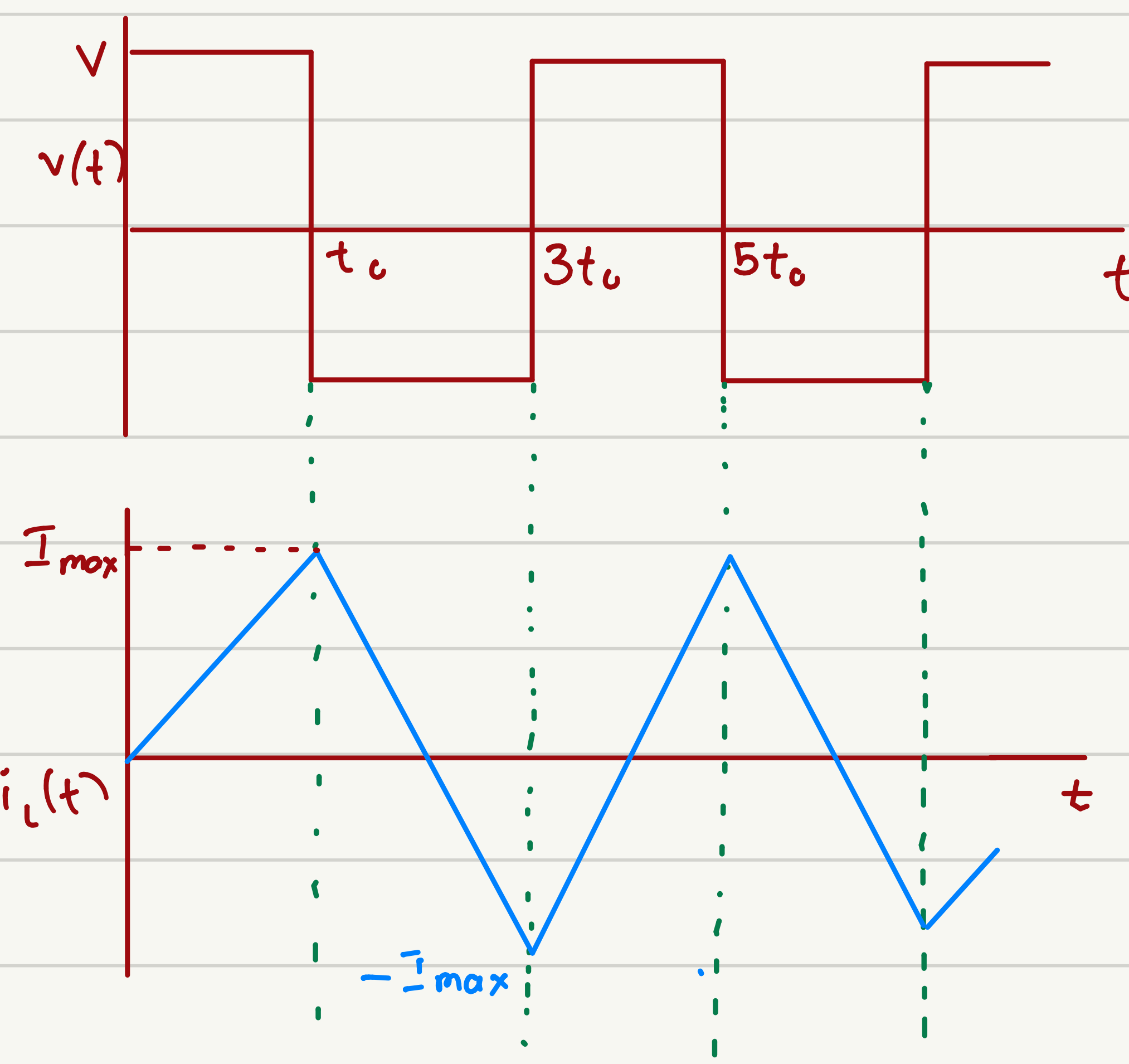
$$= \frac{1}{L} \int_{t_0}^t V(t) dt + i(t_0)$$




* Ohm's law for capacitor (cause effect relationship)

$$i_C = C \frac{dv_C}{dt}$$

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C dt$$

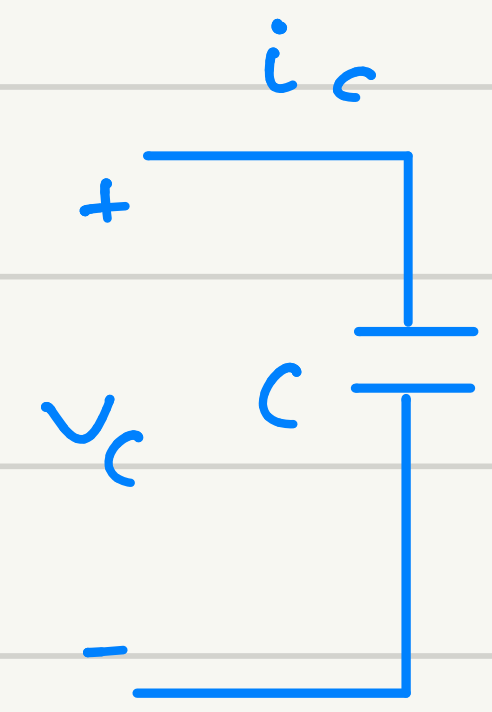
$$V_C(t) = \frac{1}{C} \int_{t_0}^t i_C dt + V_C(t_0)$$



i_C


v_C

C

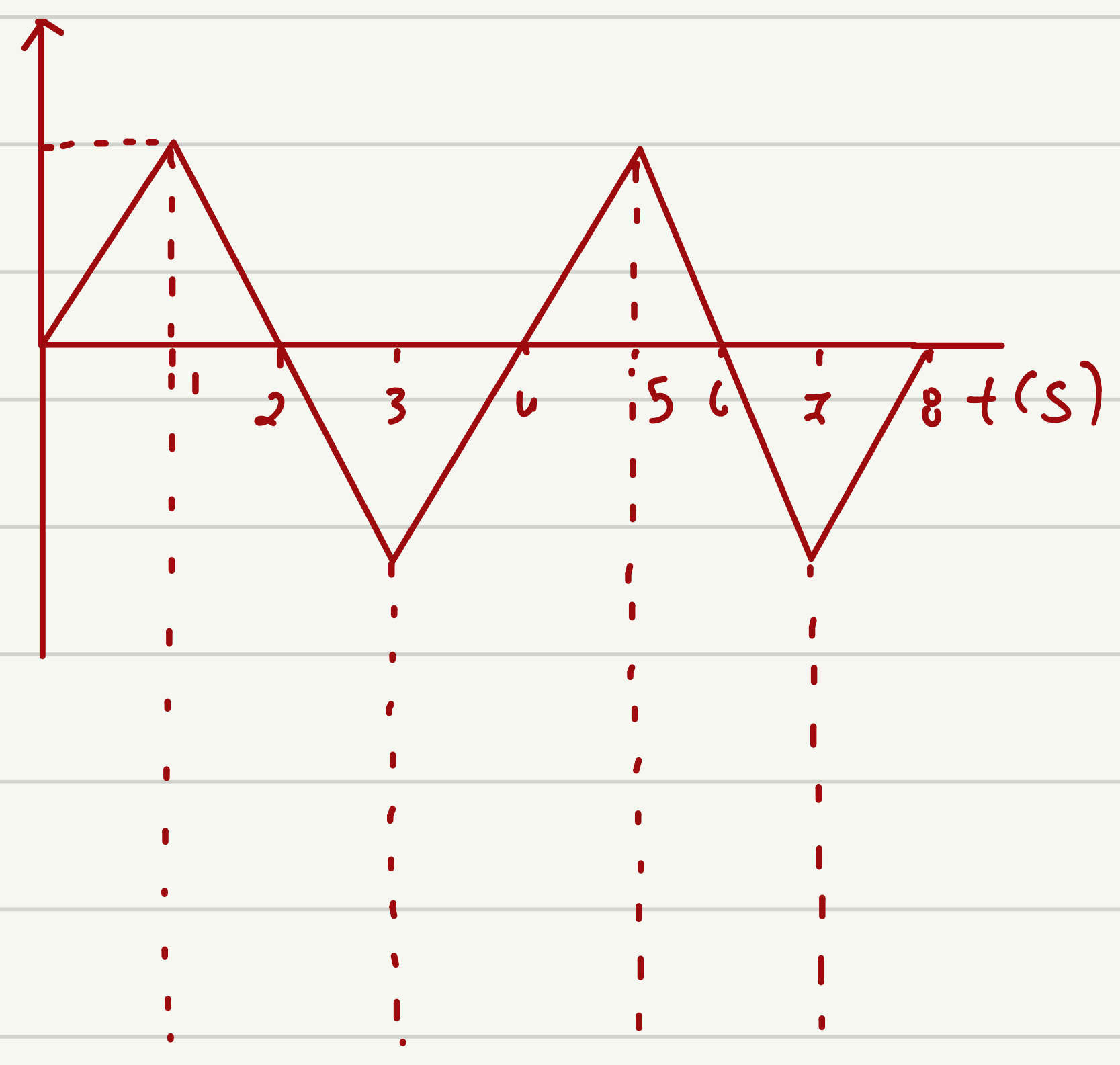

$V \rightarrow$ can change immediately
but i cannot.

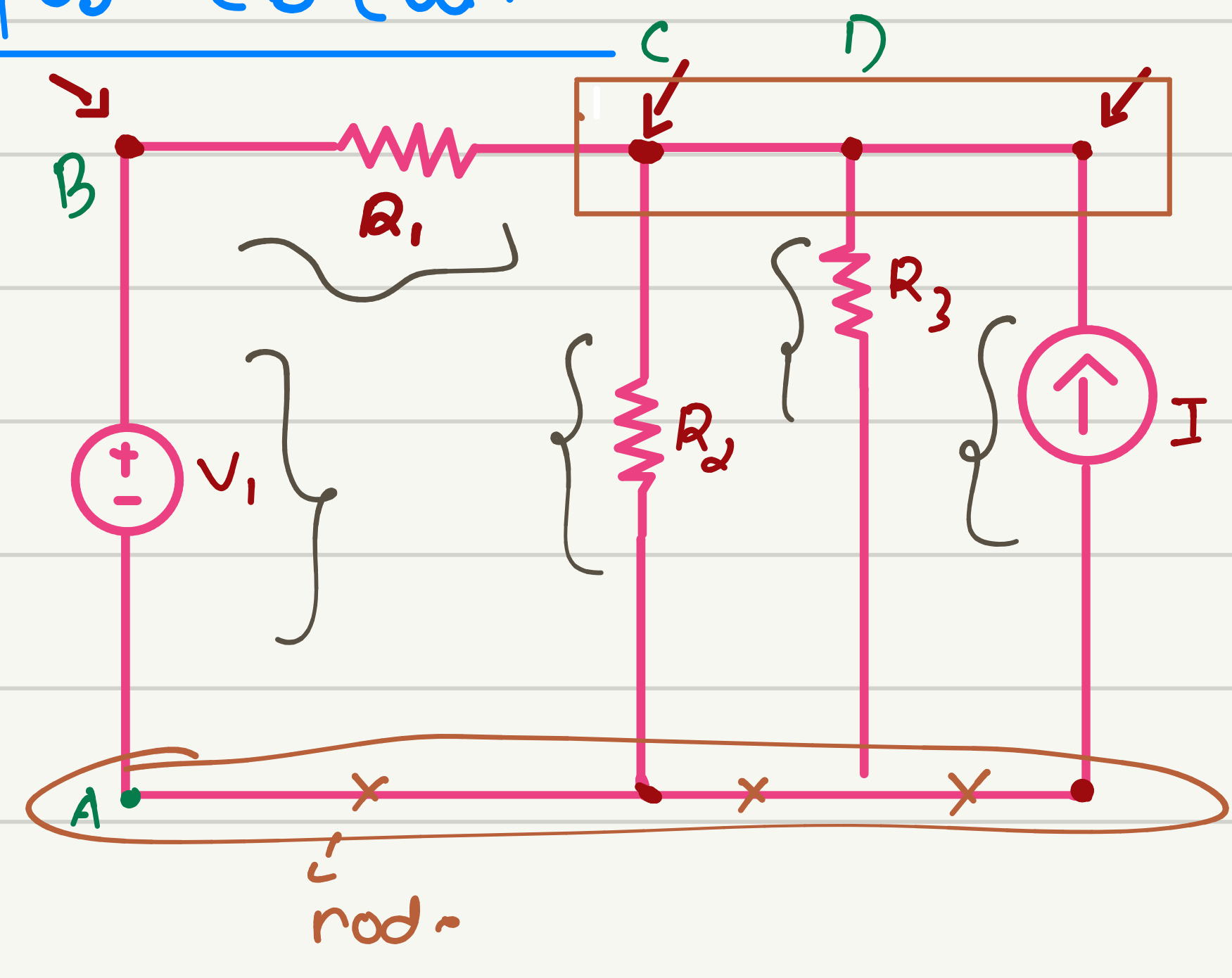* Few important terminologies for circuit



(1) Node $\rightarrow$ 3 node

(2) Branch $\rightarrow$ 5


(3) Loop $\rightarrow$ ABCDA

(4) Mesh $\rightarrow$ ABCA

Assign voltage to one node.

* KCL & KVL (review)

KCL (conservation charge)

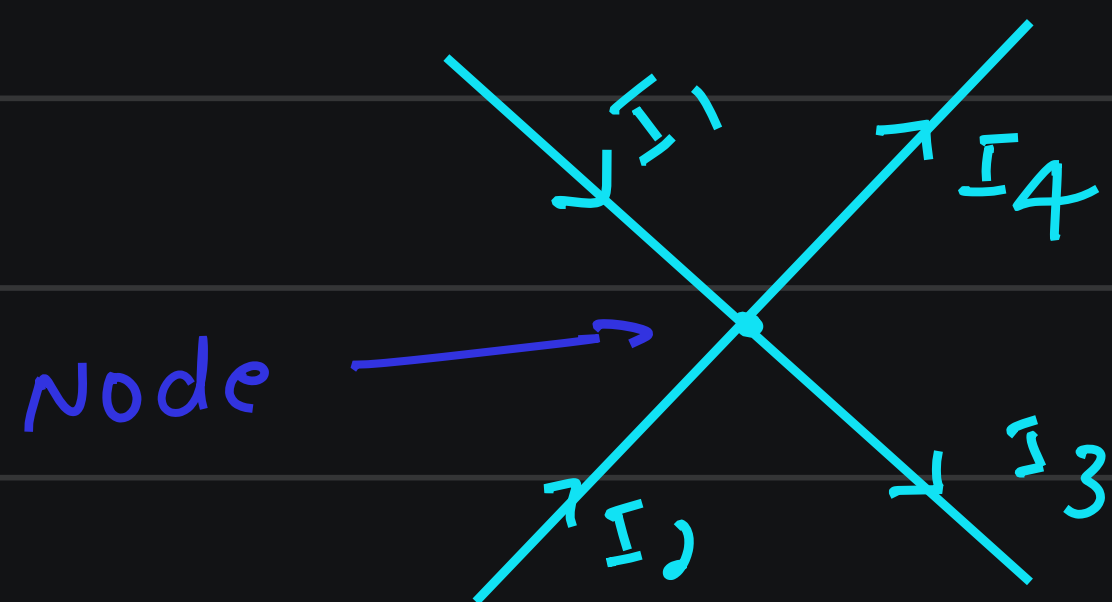


$$\sum I_i = 0$$

Entering current = Leaving current

$$-I_1 - I_2 + I_3 + I_4 = 0$$

Entering current
-ve

Leaving current
+ve.

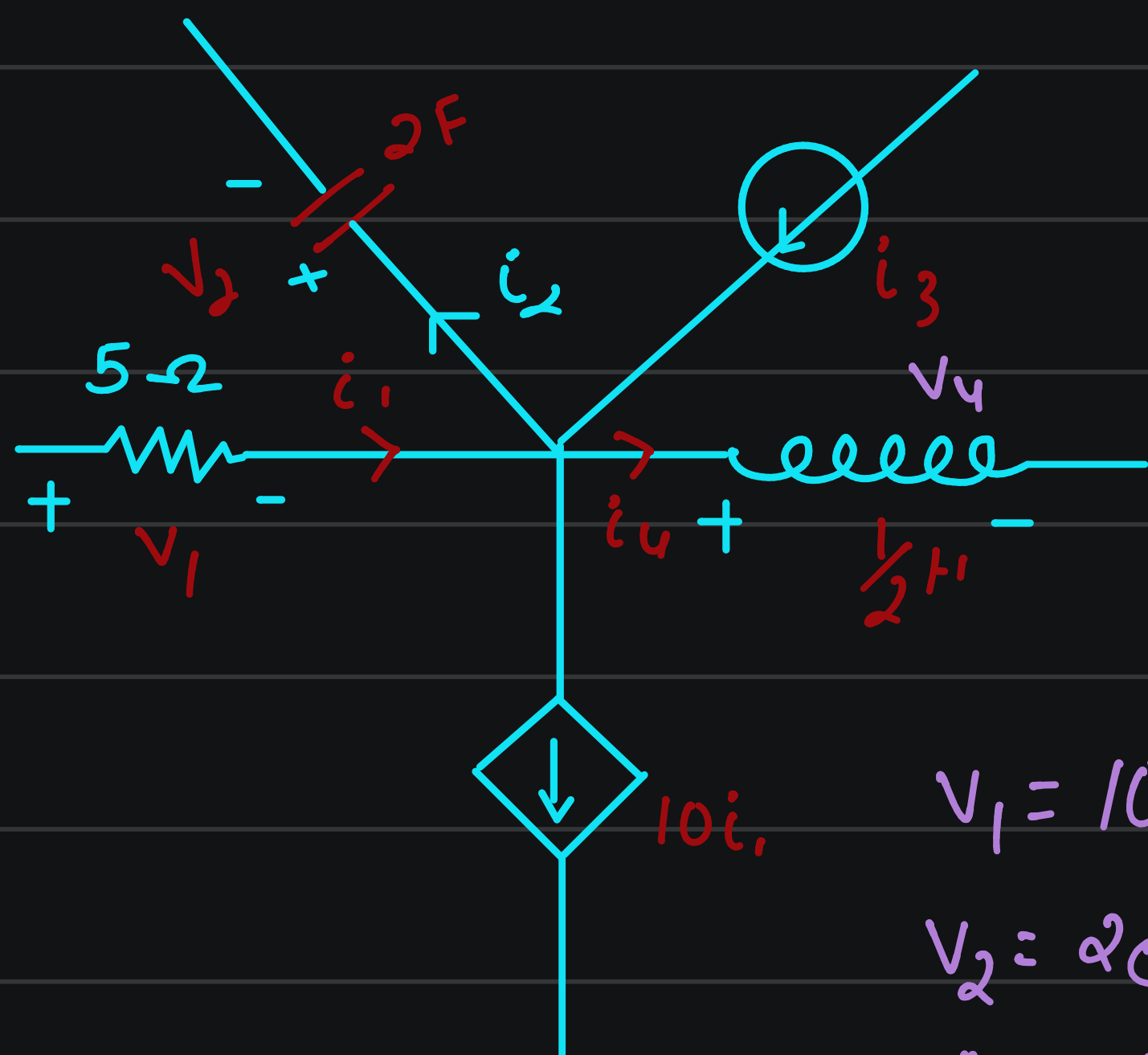

$$V_1 = 10e^{-2t} \text{ V}$$

$$V_2 = 2e^{-2t} \text{ V}$$

$$i_3 = 6e^{-2t} \text{ V}$$

Find V_u .

$$-i_1 + i_2 - i_3 + i_4 + 10i_1 = 0 \quad \text{--- (1)}$$

$$= \frac{10e^{-2t}}{5} + 2 \cdot (-2) 2e^{-2t} - 6e^{-2t}$$

$$+ i_4 + \frac{10 \times 10e^{-2t}}{5} = 0$$


$$= i_4 = -4e^{-2t}$$

$$V_u = L \frac{di}{dt} = 0.5 \times (-4) (-2) e^{-2t}$$

$$= 4e^{-2t} \text{ volts.}$$

KVL (conservation of energy)

$\rightarrow$ close path

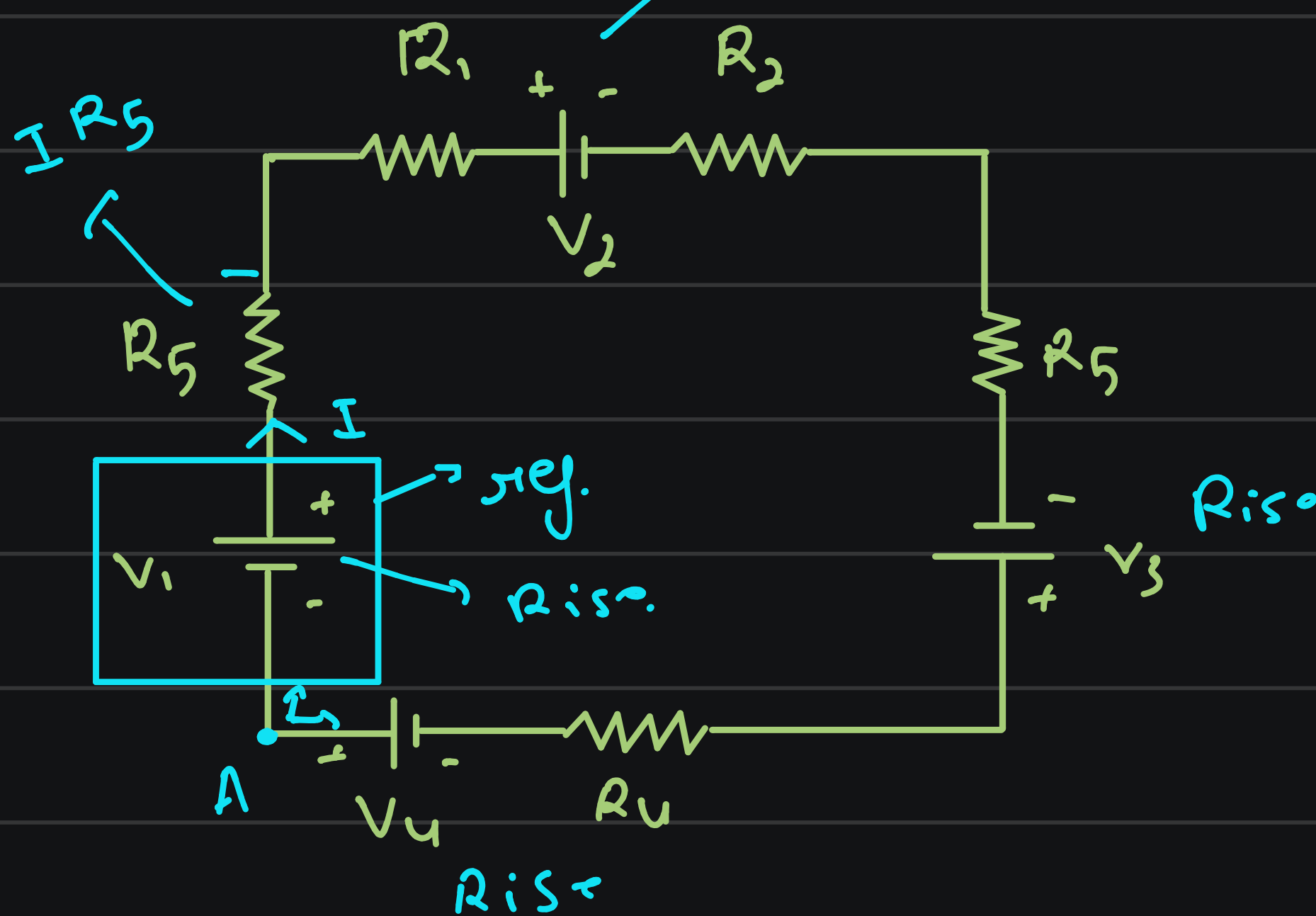


$$\sum V_i = 0$$

voltage $\rightarrow$ with ref.

$$\sum V_{\text{rise}} = \sum V_{\text{drop}}$$

$$\sum_{i=1}^n V_i = 0$$
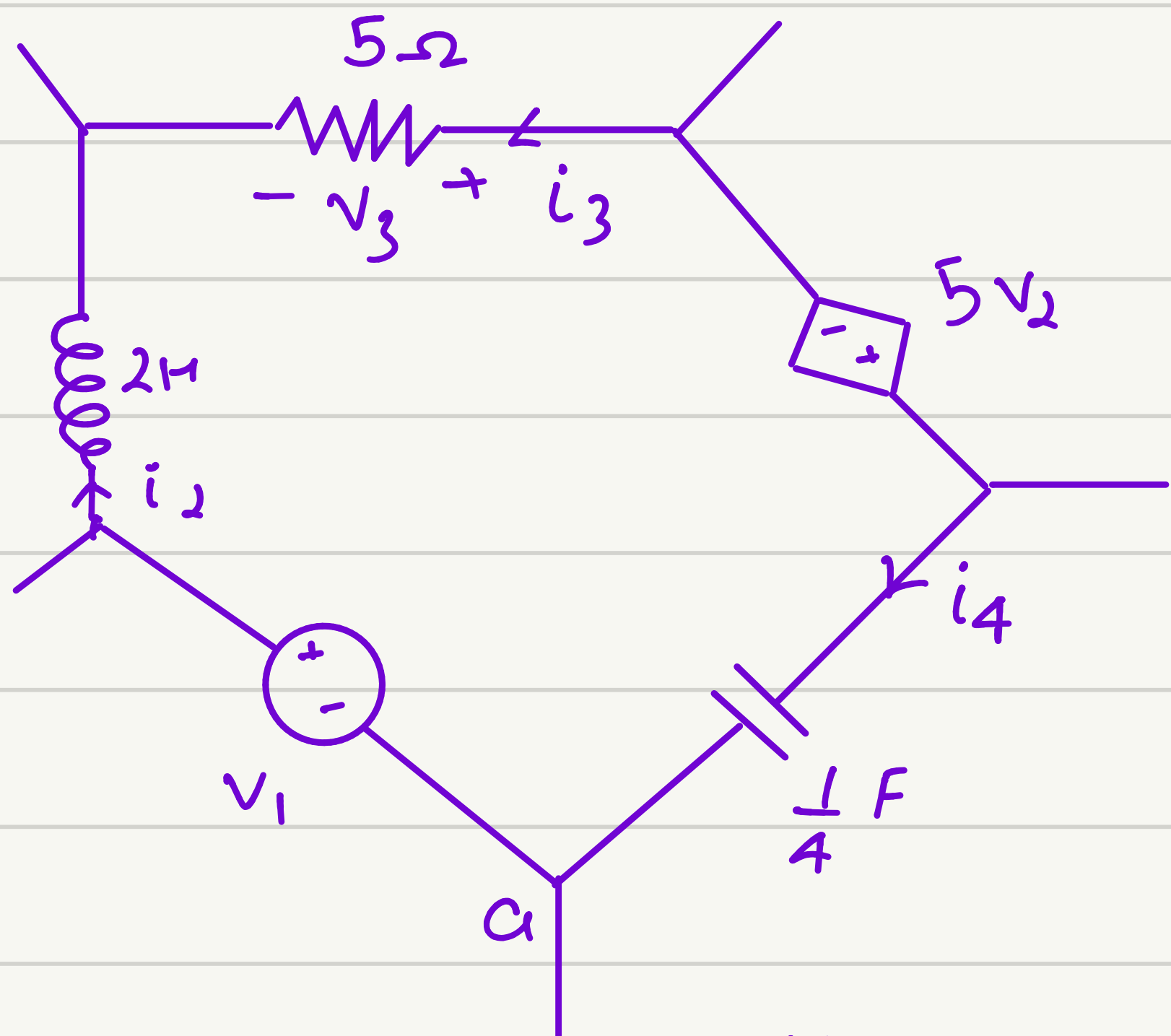
$$V_1 - IR_5 - IR_1 - V_2 - IR_2 - IR_3 + V_3 - IR_4 + V_4 = 0$$



$$V_1 = 12 \sin 2t$$

$$i_2 = 4 \sin 2t$$

$$i_3 = 2 \sin 2t - 4 \cos 2t$$

$$V_1 - V_2 + V_3 + 5V_2 - V_4 = 0$$

$$V_2 = 2 \frac{d}{dt} (4 \sin 2t) = 16 \cos 2t$$

$$V_3 = 5i_3 = 5(2 \sin 2t - 4 \cos 2t)$$


$$V_4 = V_1 - V_2 + V_3 + 5V_2$$

$$\begin{aligned} V_4 &= 12 \sin 2t - 16 \cos 2t + 10 \sin 2t \\ &\quad - 20 \cos 2t + 80 \cos 2t \\ &= 22 \sin 2t - 14 \cos 2t \end{aligned}$$

$$i_4 = 11 \cos 2t - 22 \sin 2t$$

Implementation / Application of KCL & KVL

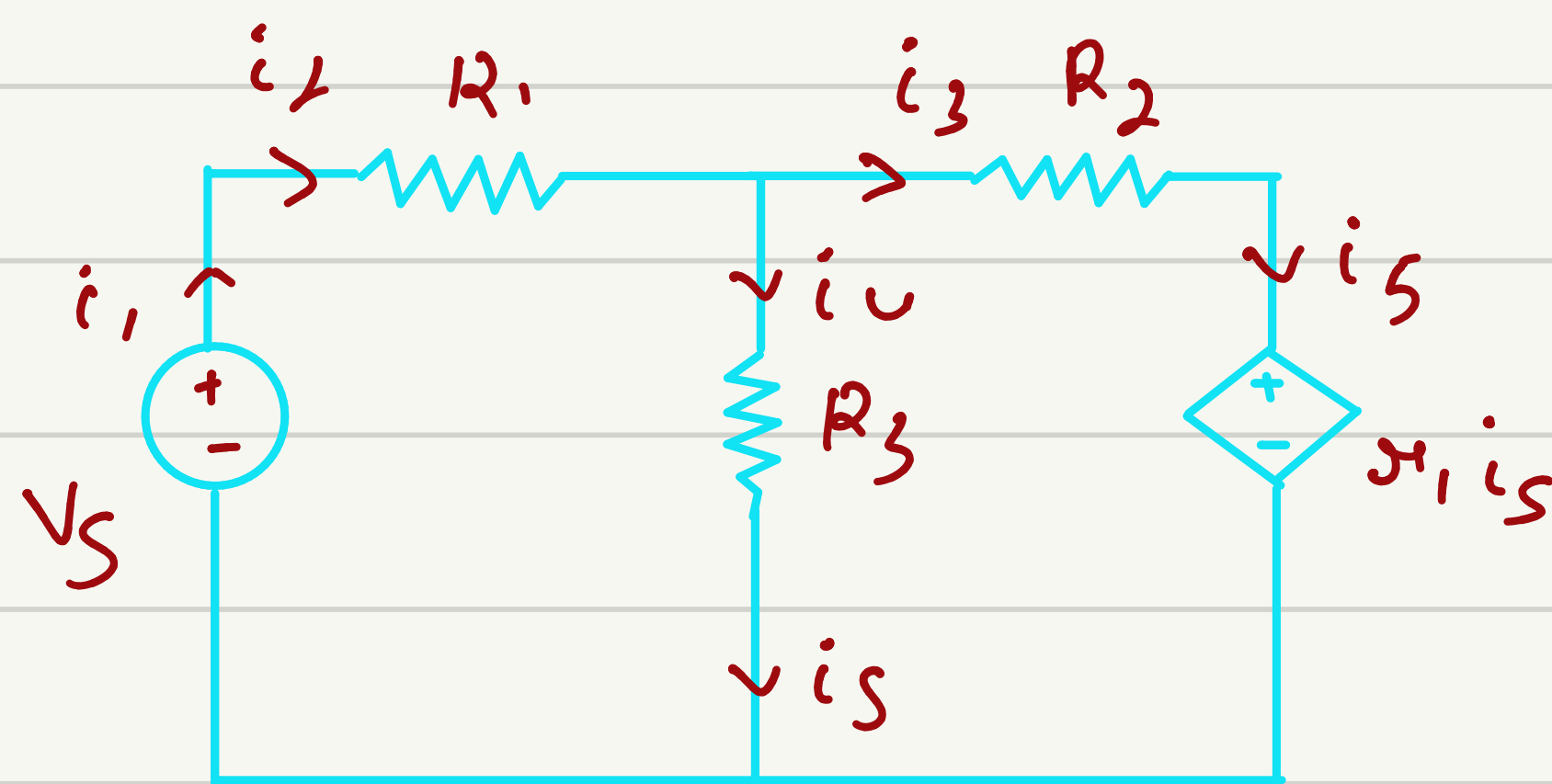1. Branch current method.
2. Mesh analysis (Loop analysis)
3. Nodal analysis
4. Supermesh analysis
5. Super node analysis.



$$-i_1 + i_2 = 0 \quad \text{--- (1)}$$

$$-i_2 + i_3 + i_4 = 0 \quad \text{--- (2)}$$


$$-i_3 + i_5 = 0 \quad \text{--- (3)}$$

$$-i_4 + i_1 - i_5 = 0 \quad \text{--- (4)}$$

$$i_4 = i_5 \quad \text{--- (5)}$$

→ Voltage across each branch

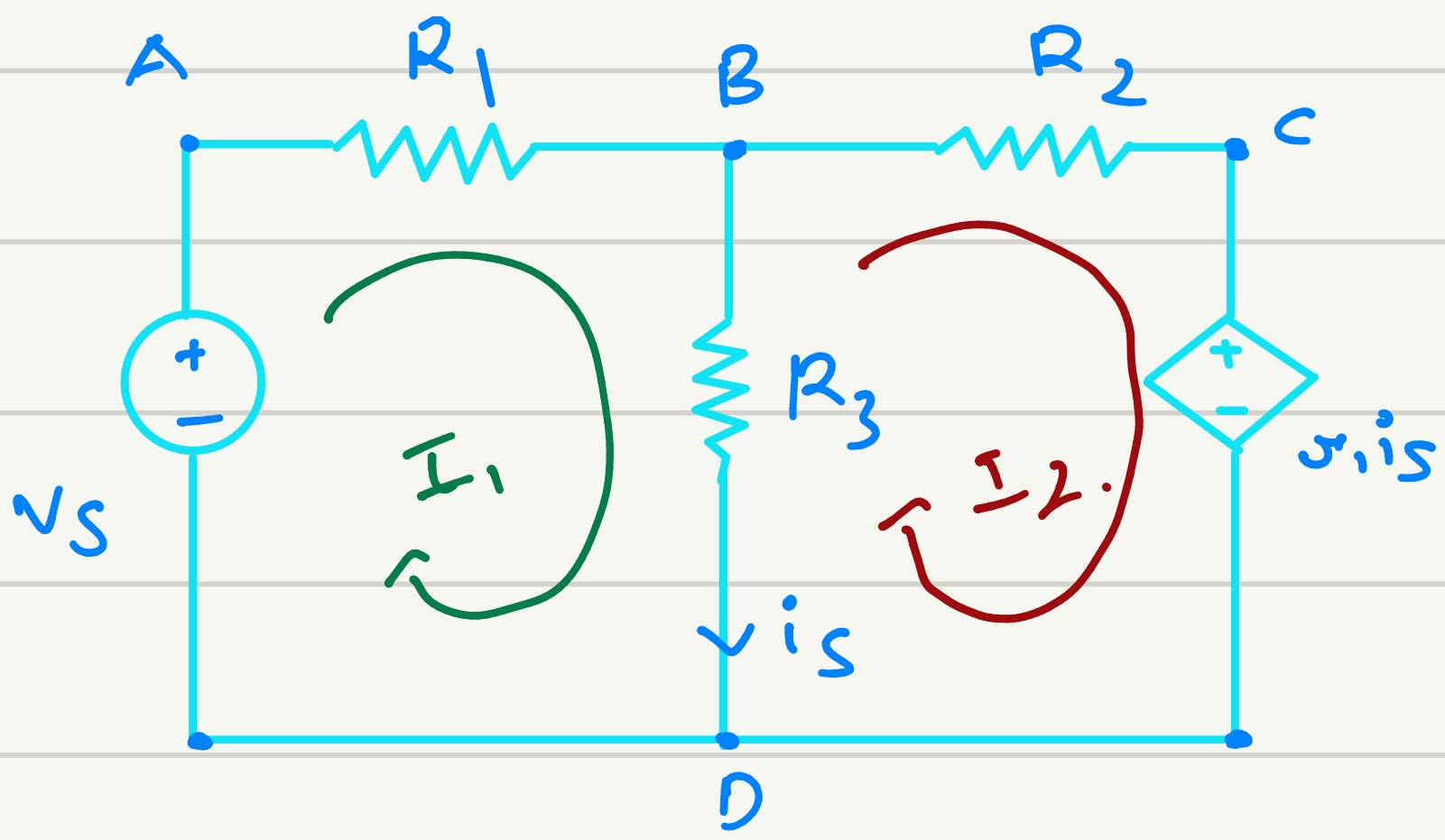→ Power $\begin{cases} \text{dissipated } (I^2 R) \\ \text{supply } \rightarrow V_1 \\ \text{Absorb } \rightarrow V_1 \end{cases}$



Mesh 1 $\Rightarrow$ A B C D
 Mesh 2 $\Rightarrow$ B C D B


KVL eg for Mesh ABCD

$$-I_1 R_1 - (I_1 - I_2) R_3 + V_S = 0 \quad (1)$$

KVL for Mesh BCDB

$$-I_2 R_2 - \mu_i i_S - (I_2 - I_1) R_3 = 0 \quad (2)$$

Casio fx 991 series calculator

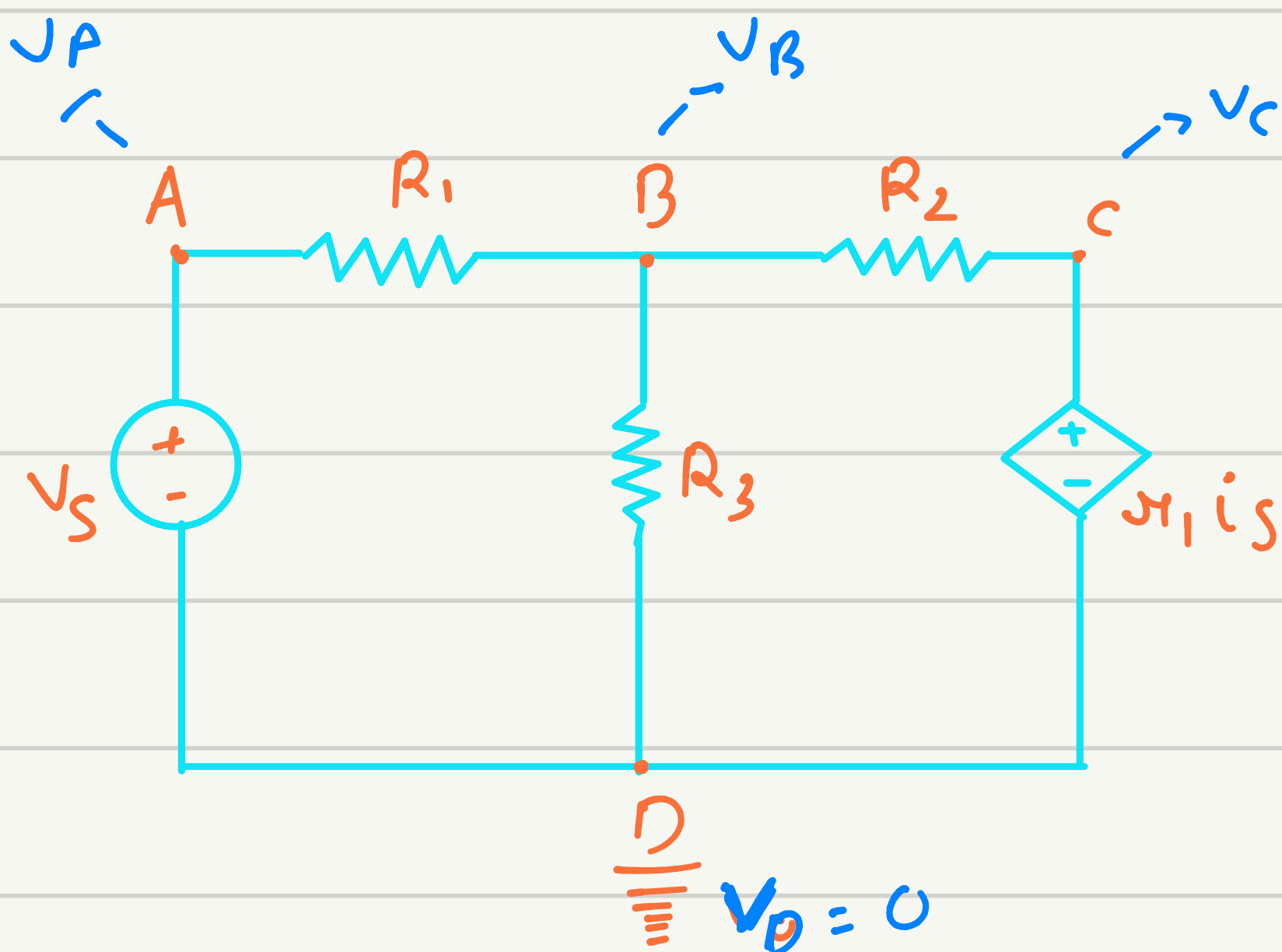

Step 1: Identify nodes
 A B C D

Step 2: Choose one node as Reference

$\rightarrow$ Max branch connected
 $\rightarrow$ The lower one in picture.

Step 3 - Assign voltage to ref nodes

$$0 \quad -25 \quad +25 \quad \dots$$

$\frac{1}{\dots} 0V$

Step 4: Write KCL for each non ref node

(1) for node A


$$\frac{V_S - V_B}{R_1} \quad \times \text{ not required}$$

(2) for node B

$$\frac{V_B - V_A}{R_1} + \frac{V_B - V_C}{R_2} + \frac{V_B}{R_3} = 0$$

(3) $\frac{V_C - V_B}{R_2} +$

Not required.

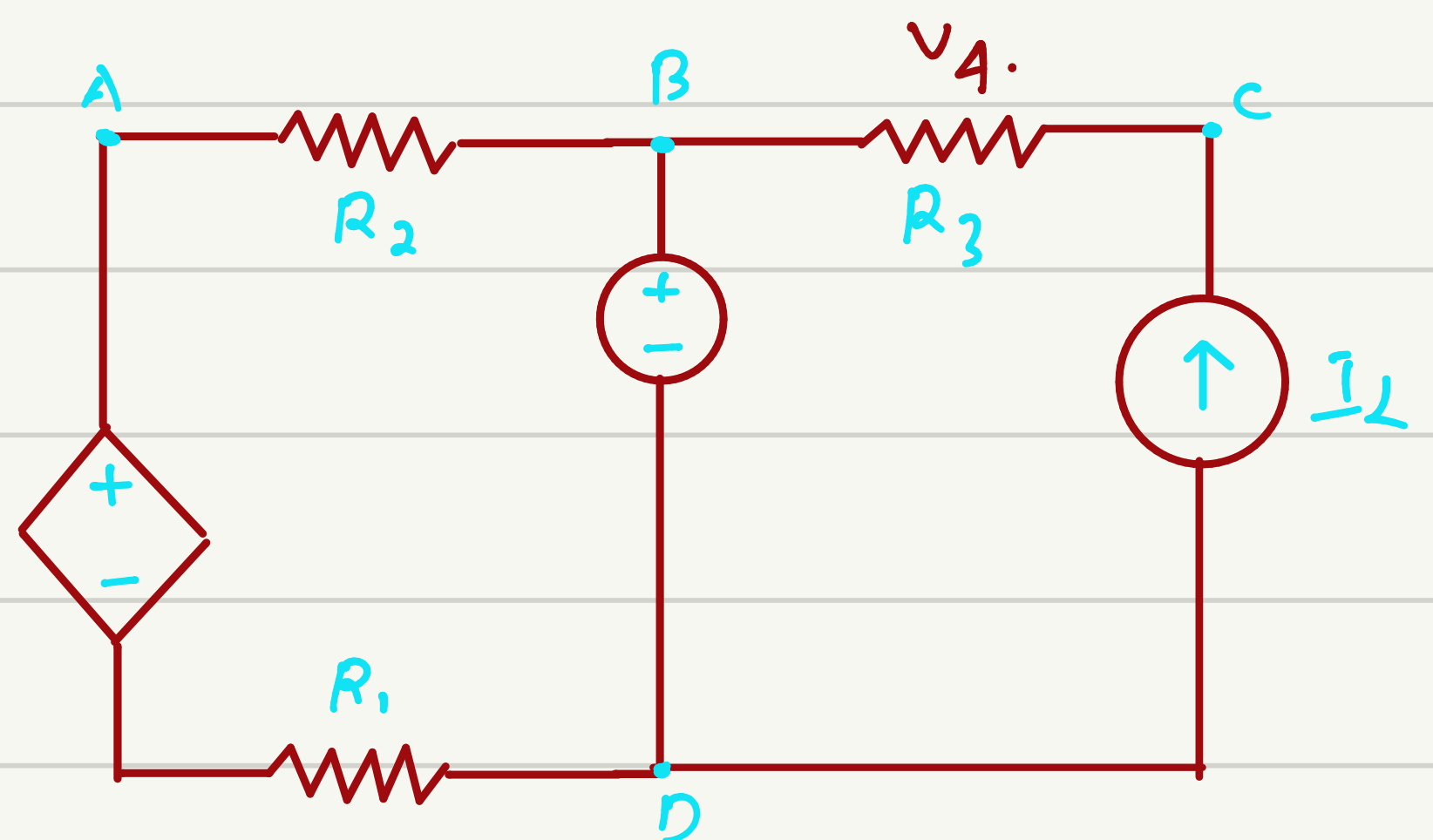

Calculate current, voltage & Power in each element of the circuit. with appropriate comment


Using branch current, nodal voltage analysis, mesh voltage. Try to compare.

$$\begin{aligned}
 R_1 &= 2\ \Omega \\
 R_2 &= 4\ \Omega \\
 R_3 &= 7\ \Omega \\
 V_0 &= 12\text{ V} \\
 I_0 &= 1\text{ A} \\
 \alpha &= 0.45
 \end{aligned}$$

Network Theorem

→ Partial solution of network

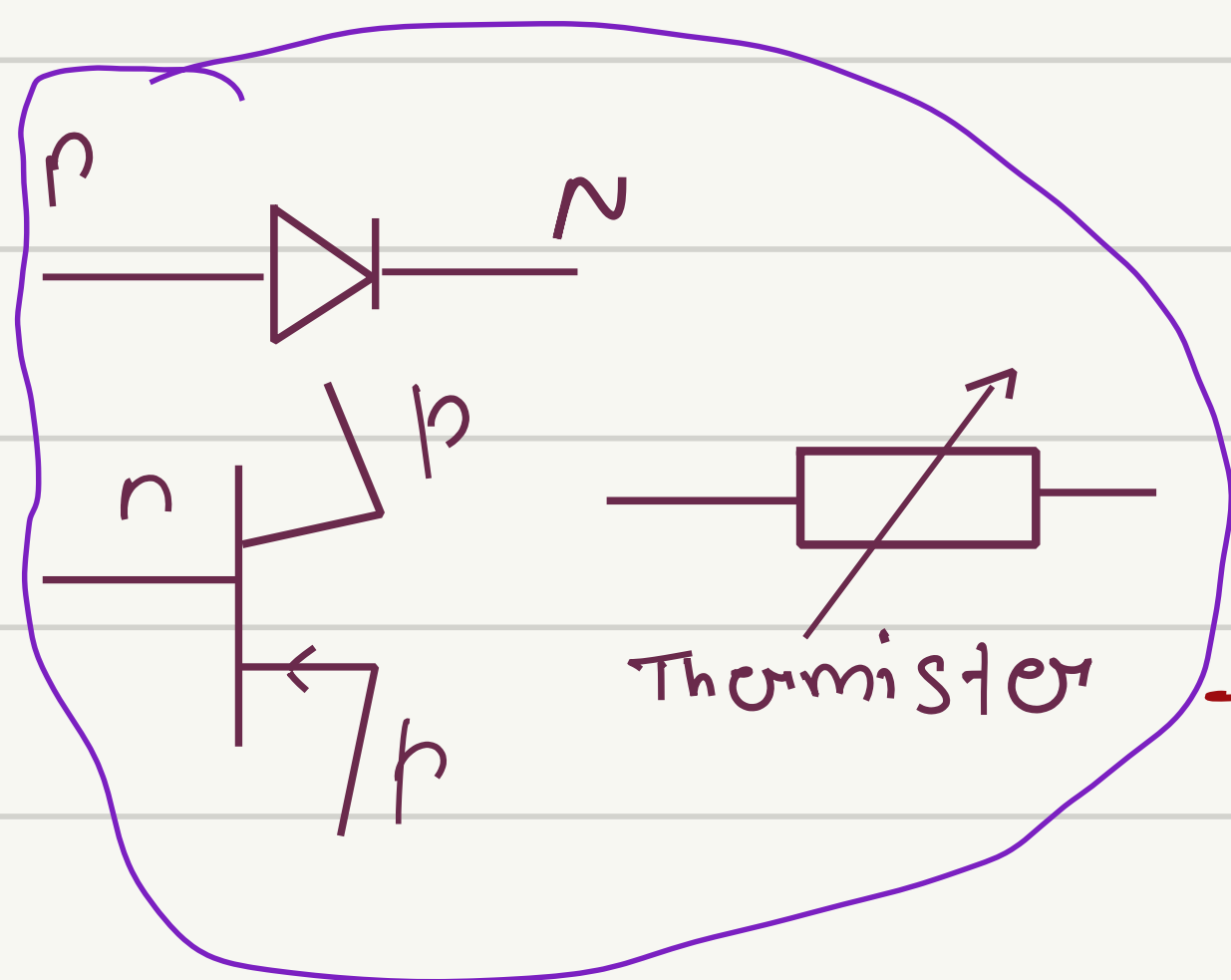- ① Super position theorem
- ② Thevenin's theorem
- ③ Norton's theorem
- ④ Maximum Power theorem
- ⑤ Tellegen's theorem




For linear network

$$V = iR$$


$$\frac{di}{dt}$$

$$\frac{dv}{dt}$$


→ Super position theorem

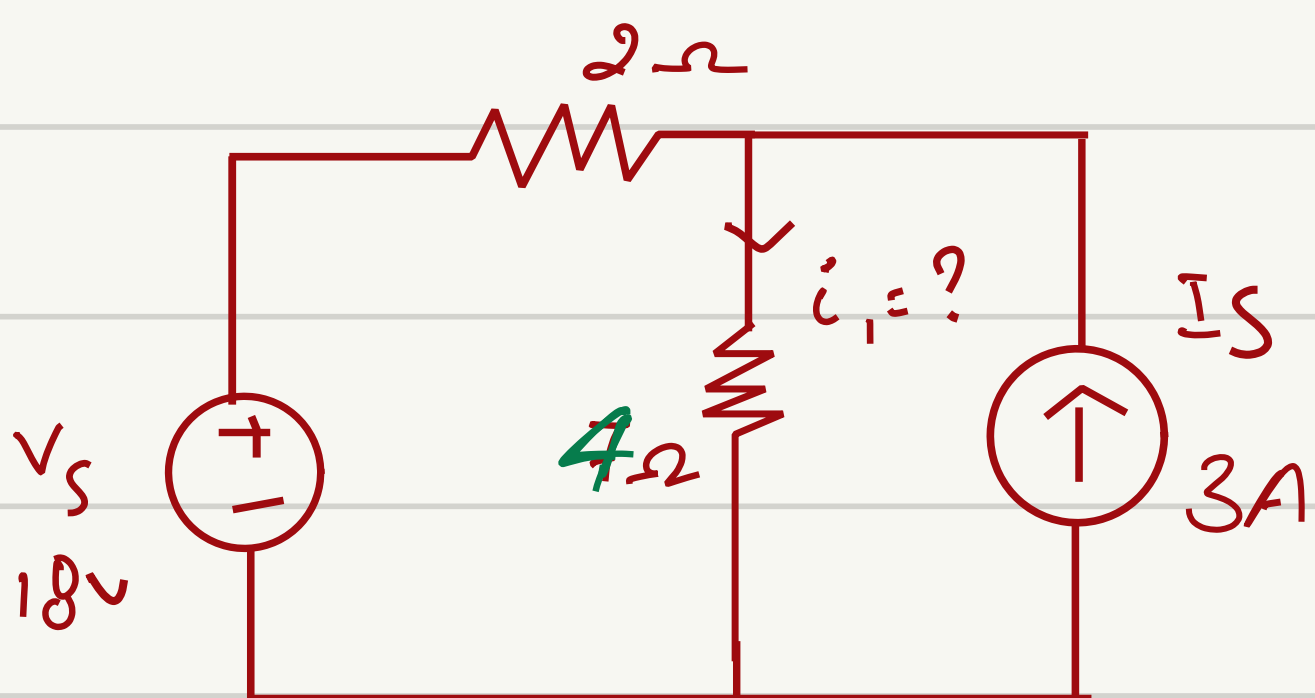

① When only 18V (V_S) is considered.

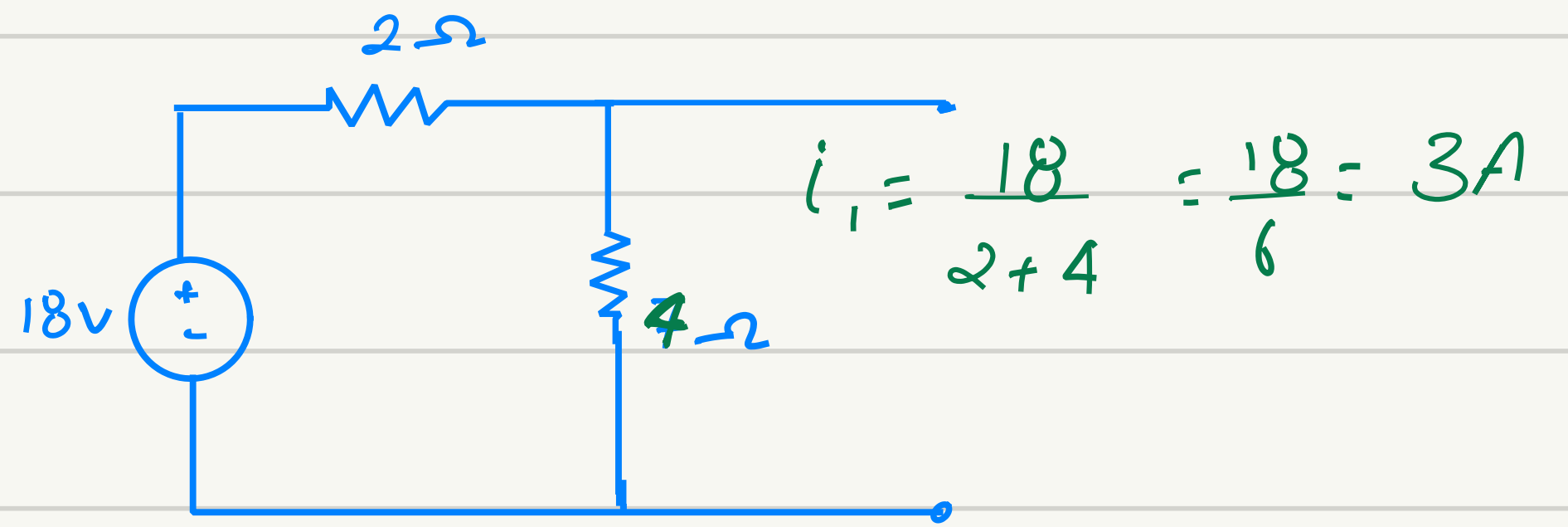


② When only 3A (I_S) is considered

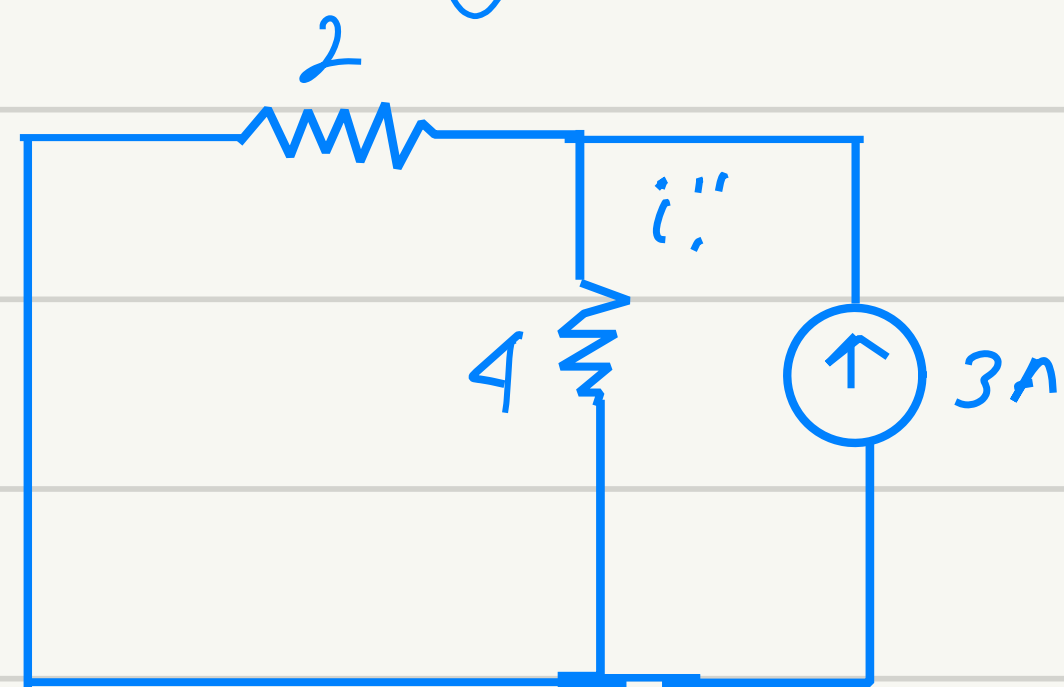


$$i_2 = \frac{3}{2+4} \times 2 = 1\text{ A}$$

Total current
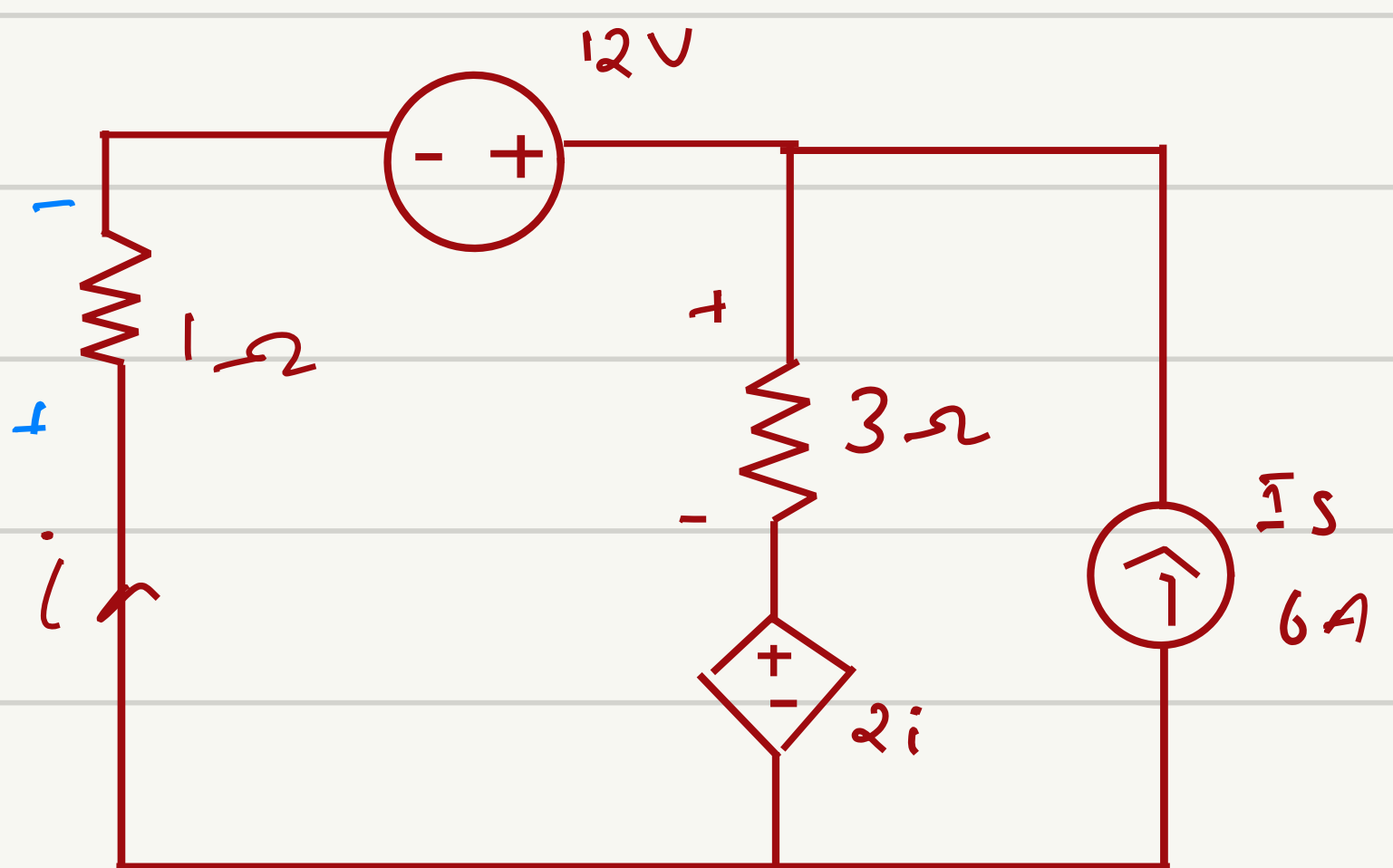
$$i_1 = i_1' + i_1'' = 3 + 1 = 4\text{ A}$$



Cose, keep V_S

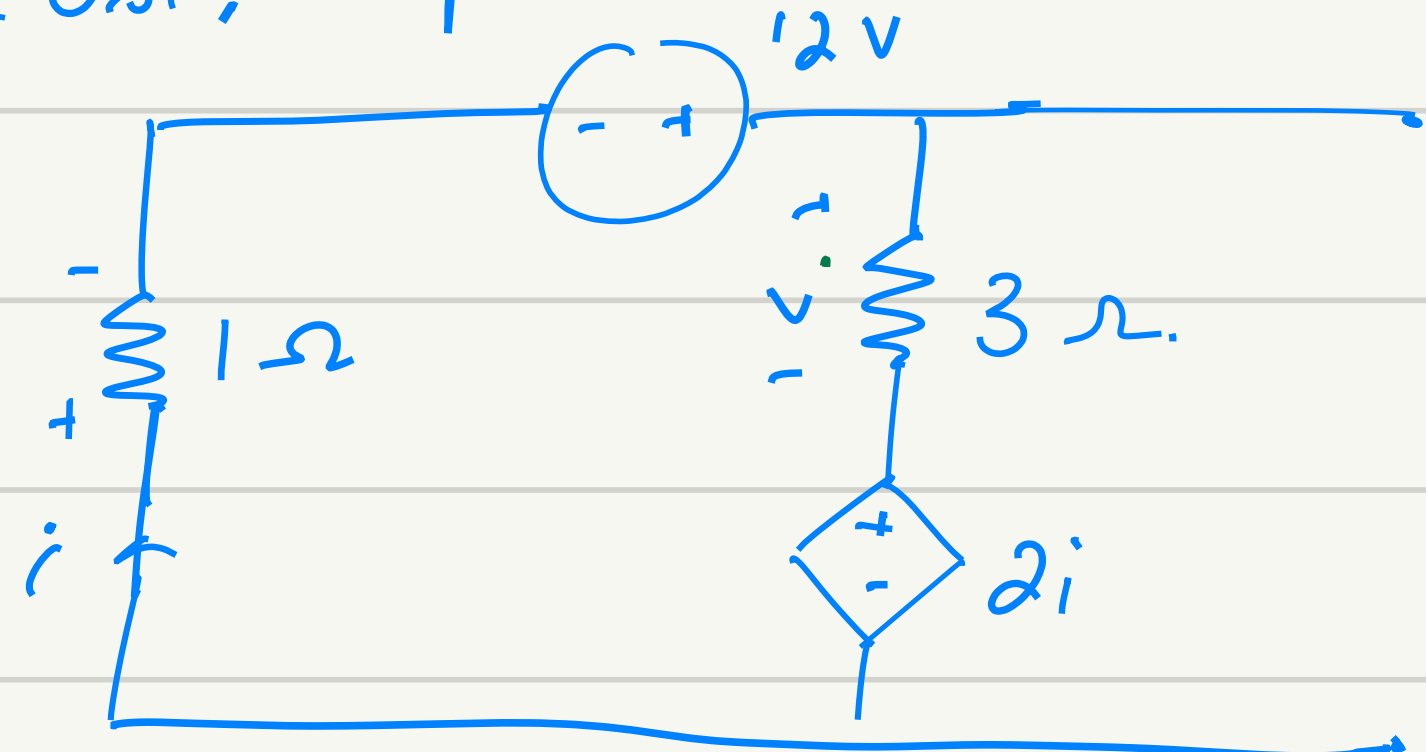


$$-i + 12 - 3i - 2i = 0$$

$$6i = 12$$

$$i = 2\text{ A}, \quad V' = 3 \times 2 = 6\text{ V}$$

→ Case 2. Keep I_s only

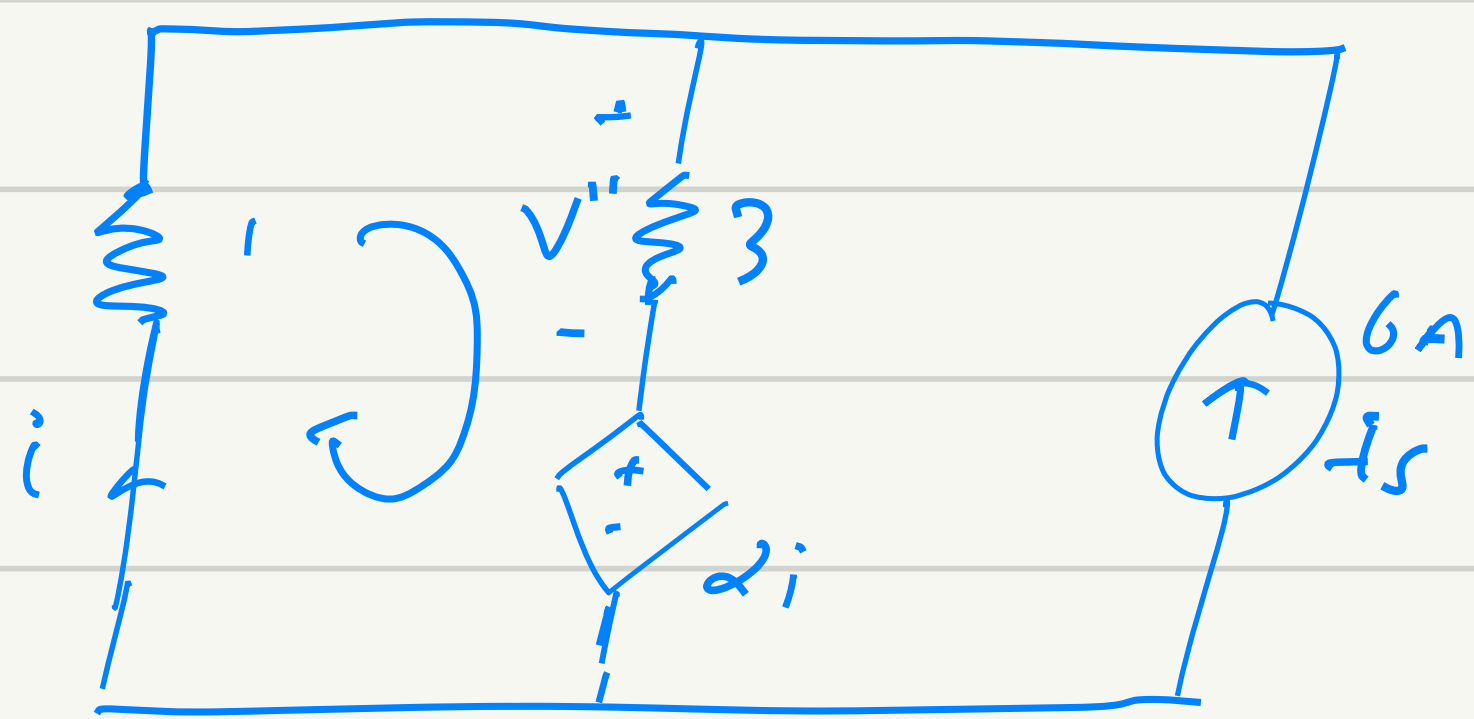


$$-i - 3(i+6) - 2i = 0$$

$$-i - 3i - 18 - 2i = 0$$

$$i = 3A$$

$$V = (-3+6) \times 3 = 9V$$

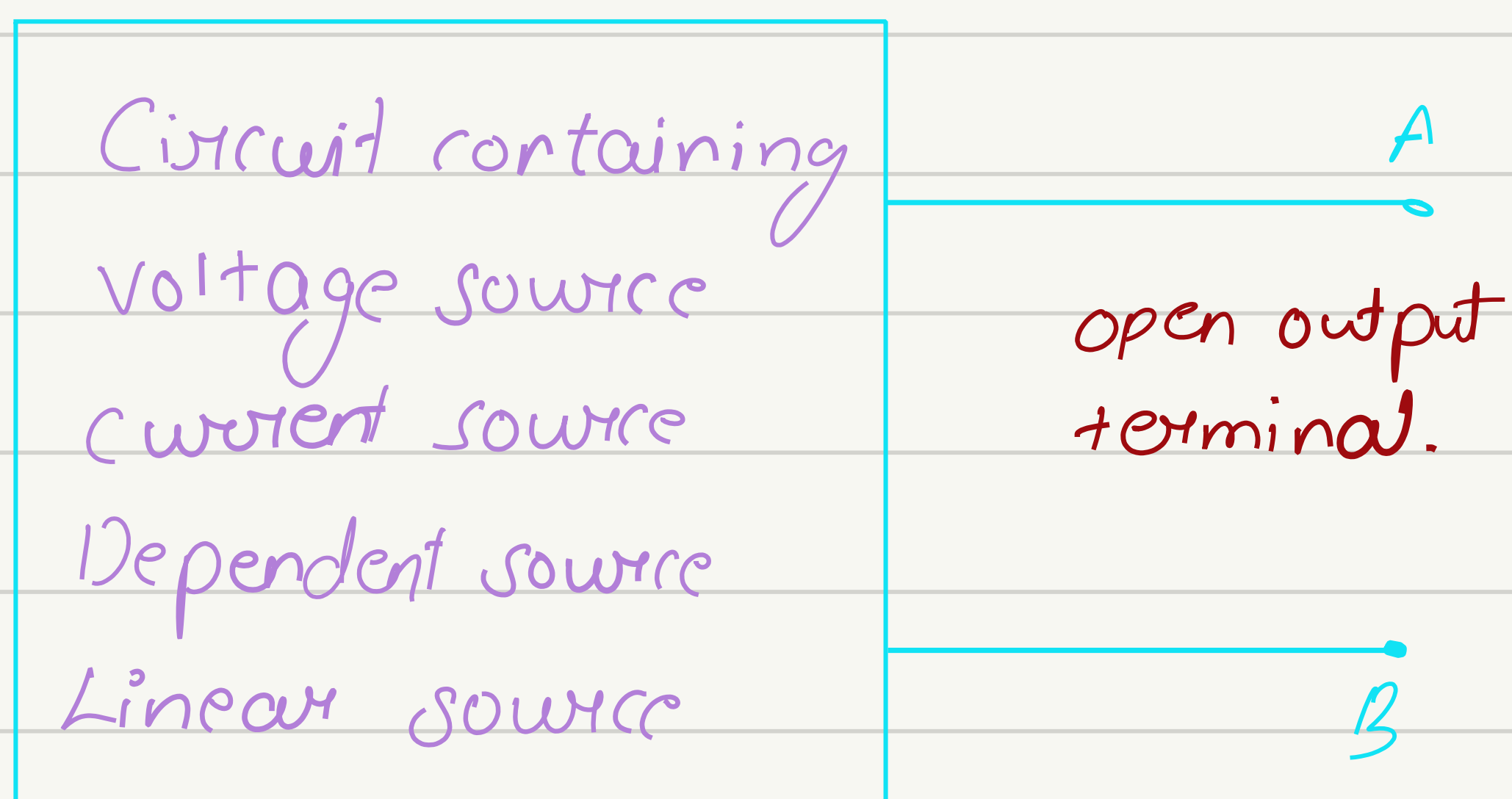


To determine V_{Th}

$$\text{Calculate } V_{oc} = V_A - V_B = V_{AB}$$

To determine R_{Th}


(1) When no dependent source

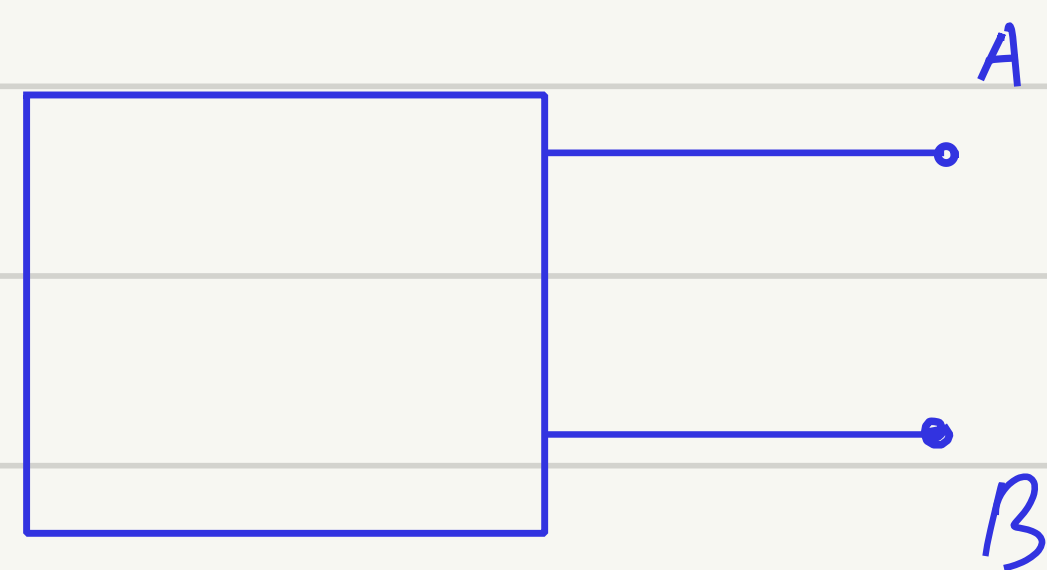


$V \rightarrow sc$

$I \rightarrow oc$


(2) Using test source

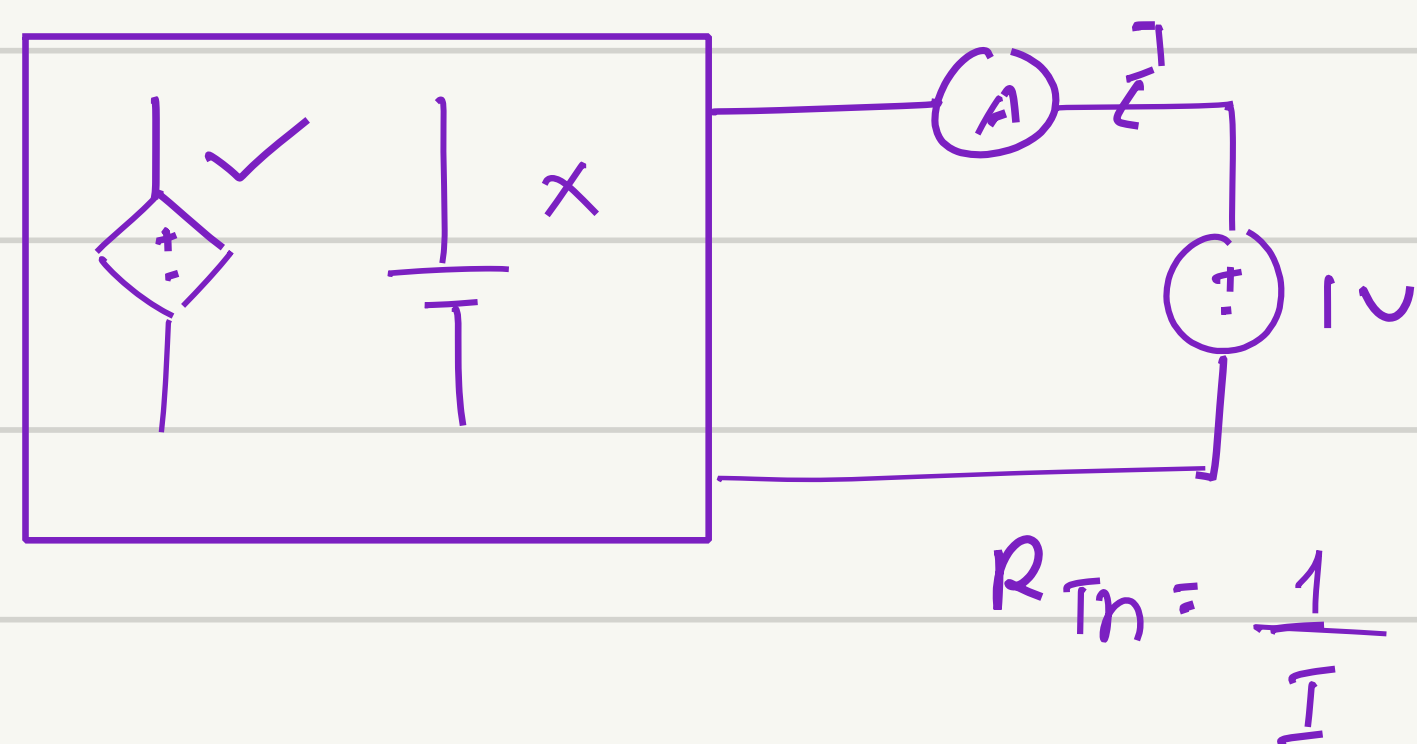

(3) By short circuit current

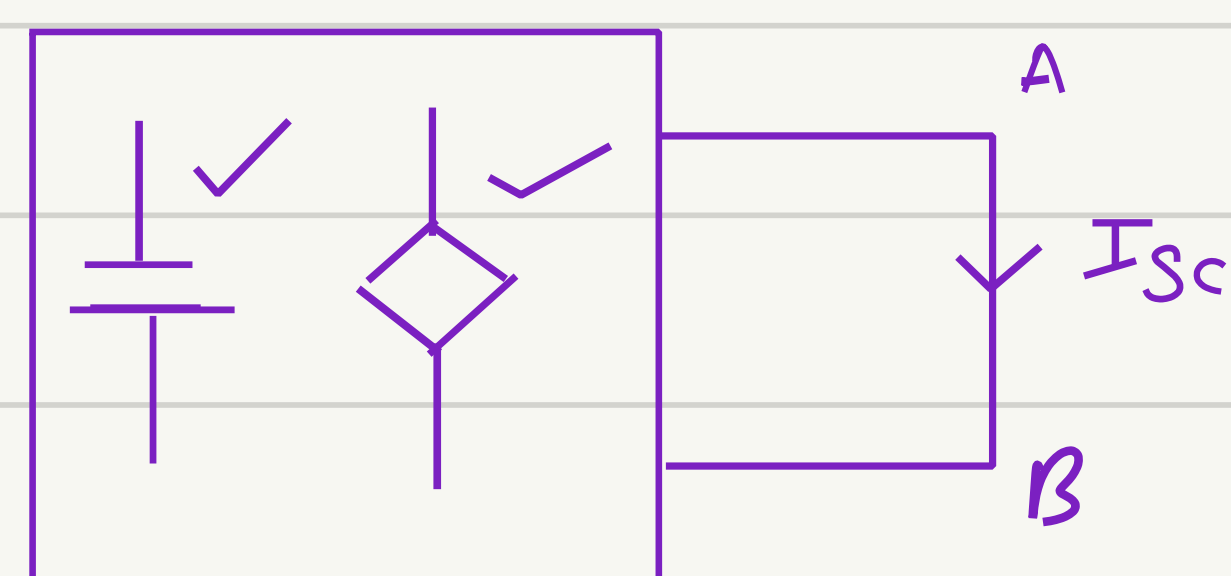

$$R_{Th} = \frac{V_{oc}}{I_{sc}}$$

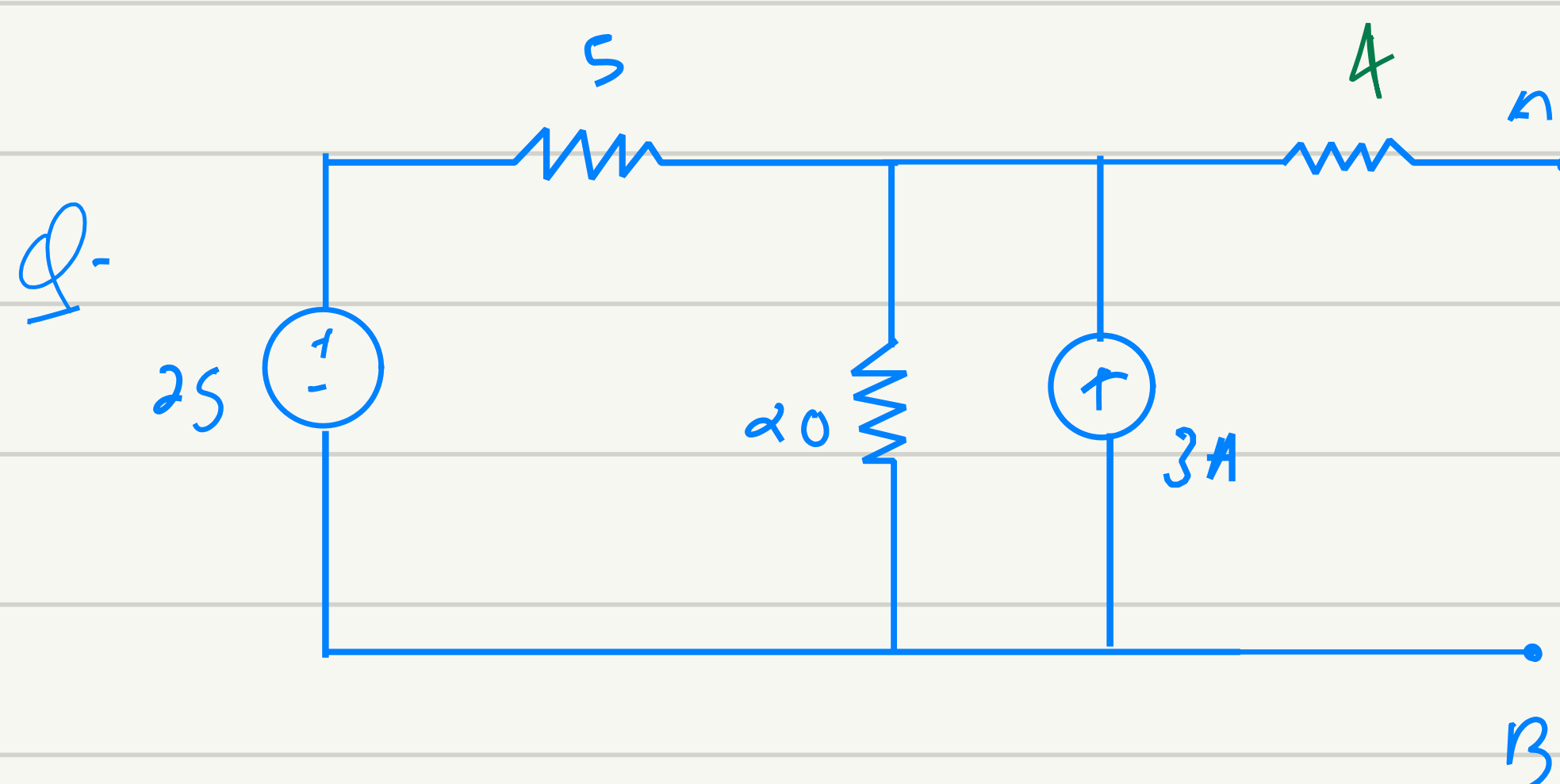


Find thevenin's Equivalent.


Solⁿ $V_{Th} = ? = V_{oc} = V_{AB} = V_{CB}$

$$\frac{V_c - 25}{5} + \frac{V_c}{20} - 3 = 0$$

$$V_c = 32V = V_{CB} = V_{AB} = V_{Th}$$

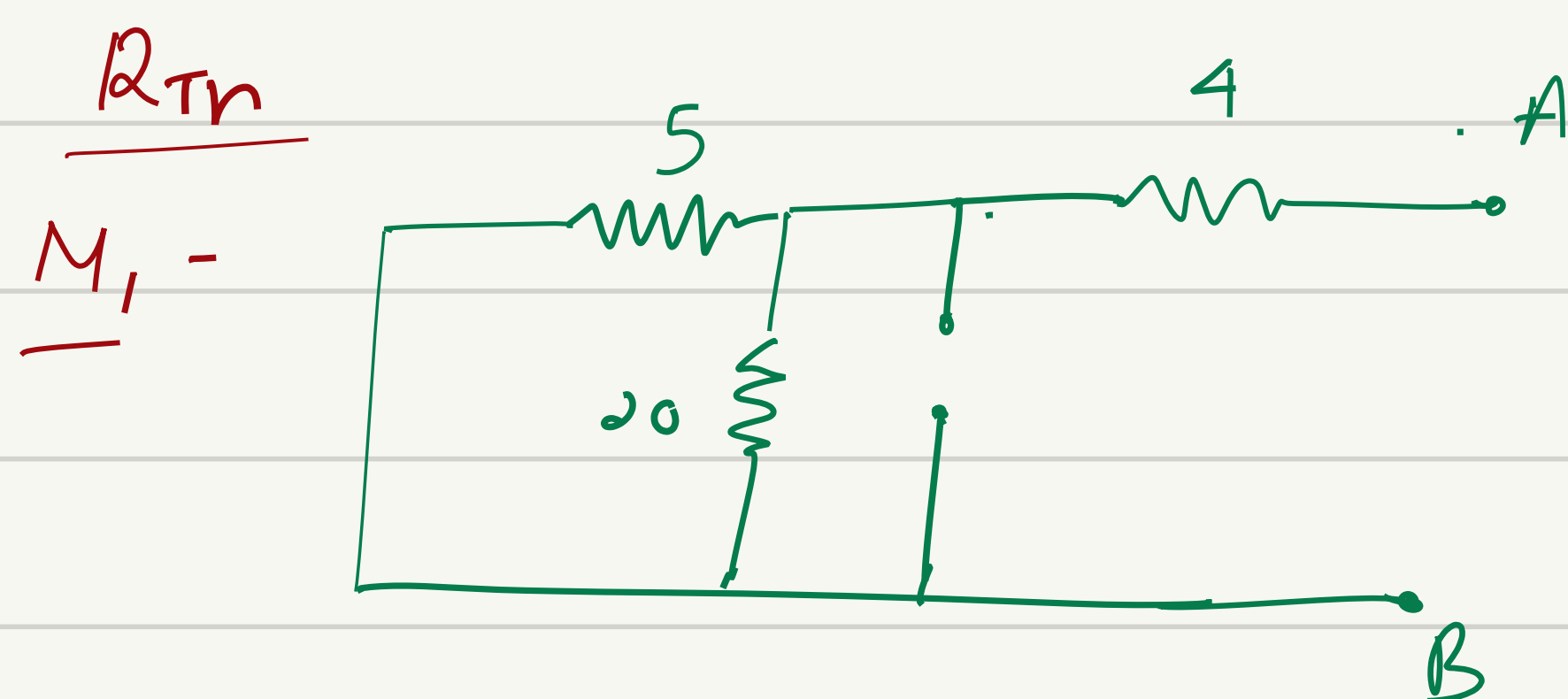

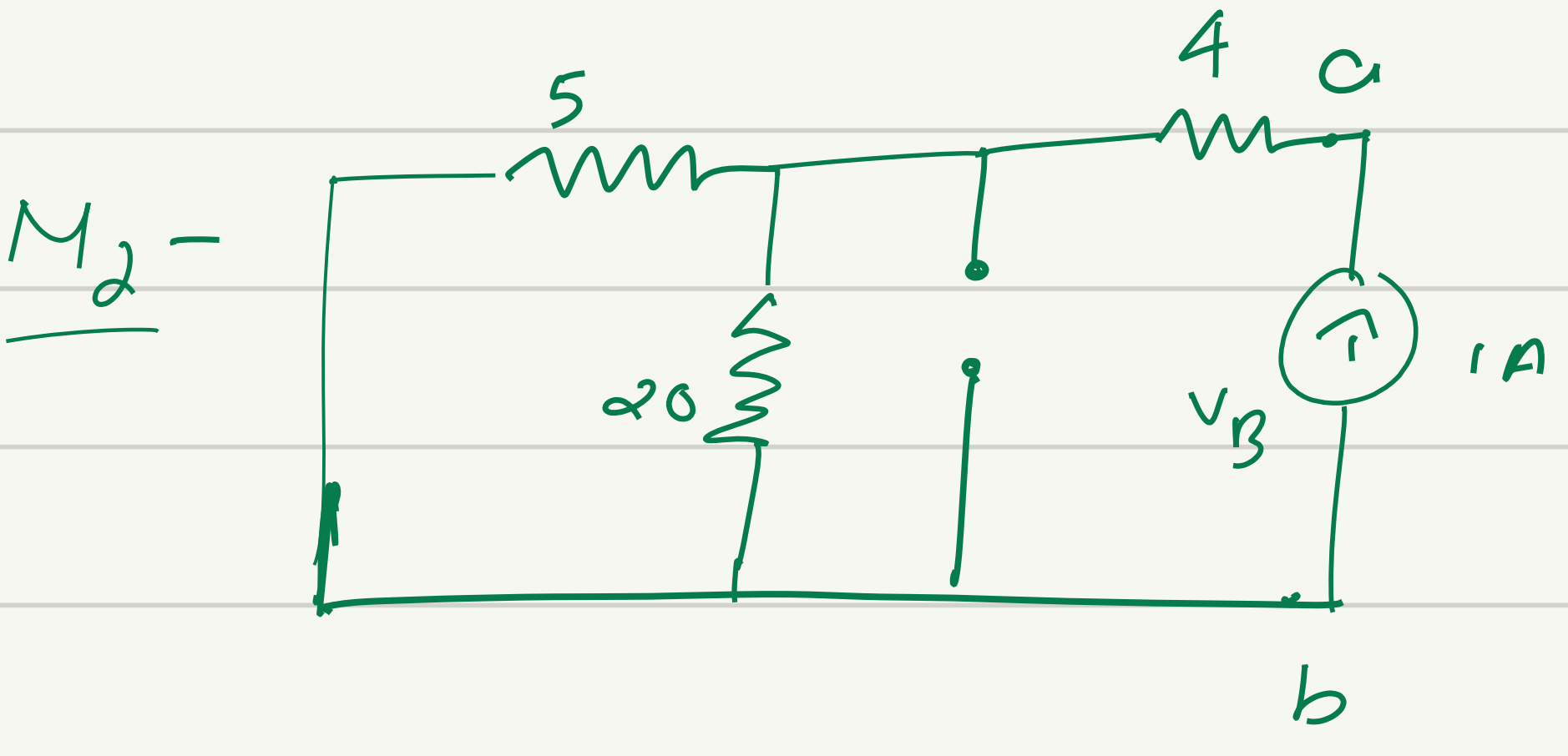
$$\frac{5 \times 20}{5 + 20} + 4 = 8 \Omega.$$



$$V_{AB} = 8V$$

$$R_{Th} = 8 = 8 \Omega.$$


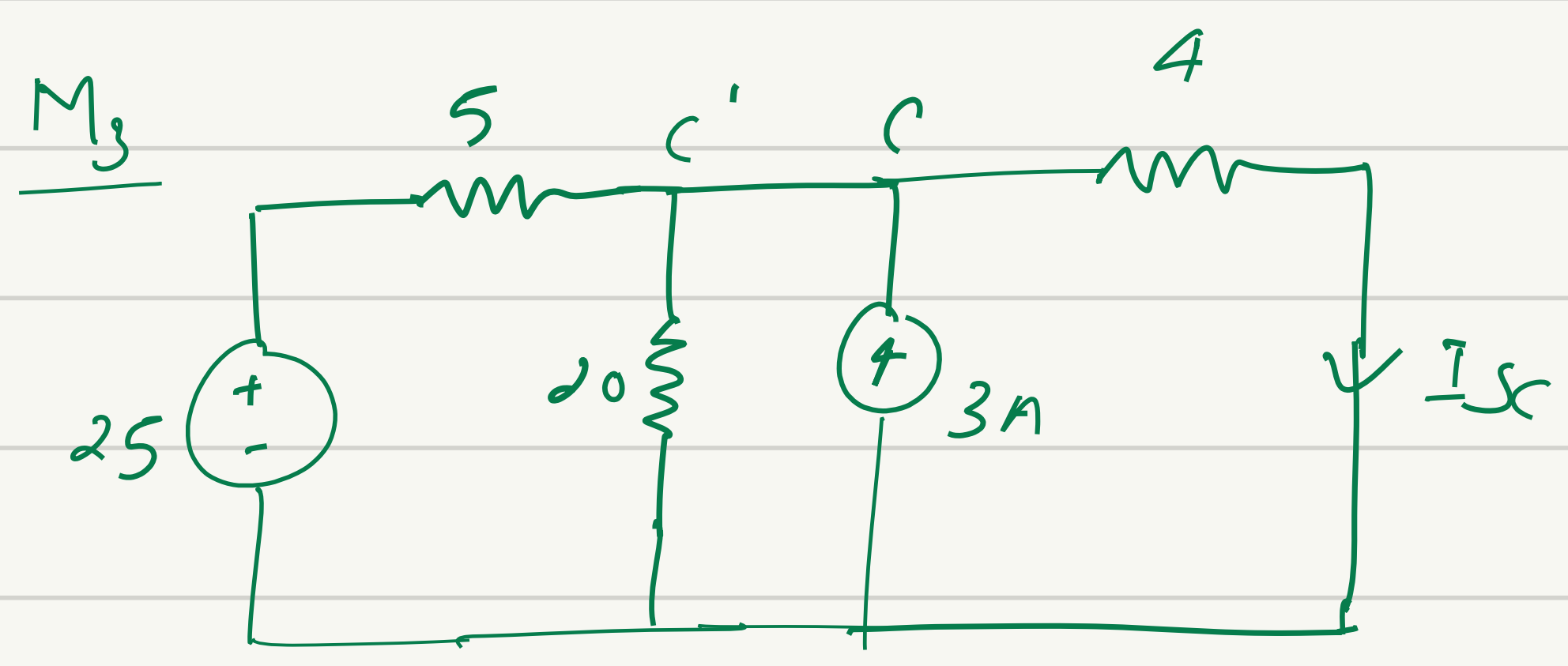


$$\frac{V_C - 25}{5} + \frac{V_C}{20} - 3 - I_{sc} = 0$$

$$\frac{V_C - 25}{5} + \frac{V_C}{20} - \frac{V_C}{4} - 3 = 0$$



$$I_{sc} = 4A.$$

Application of Thevenin's theorem

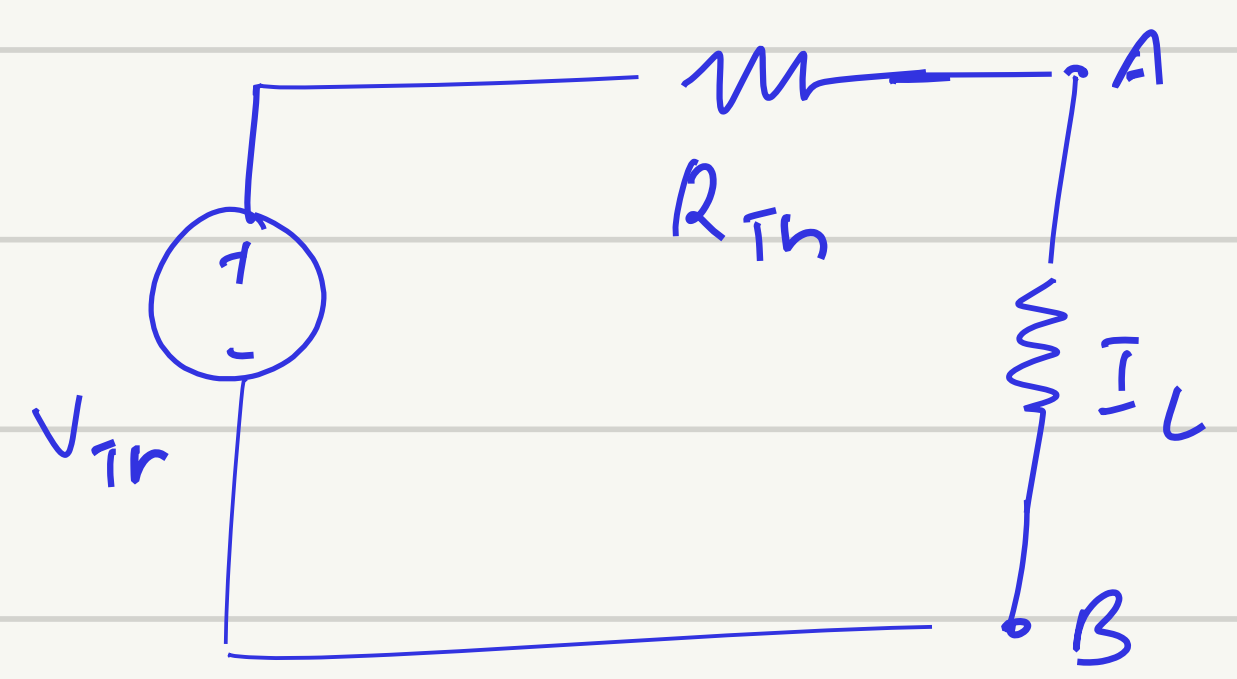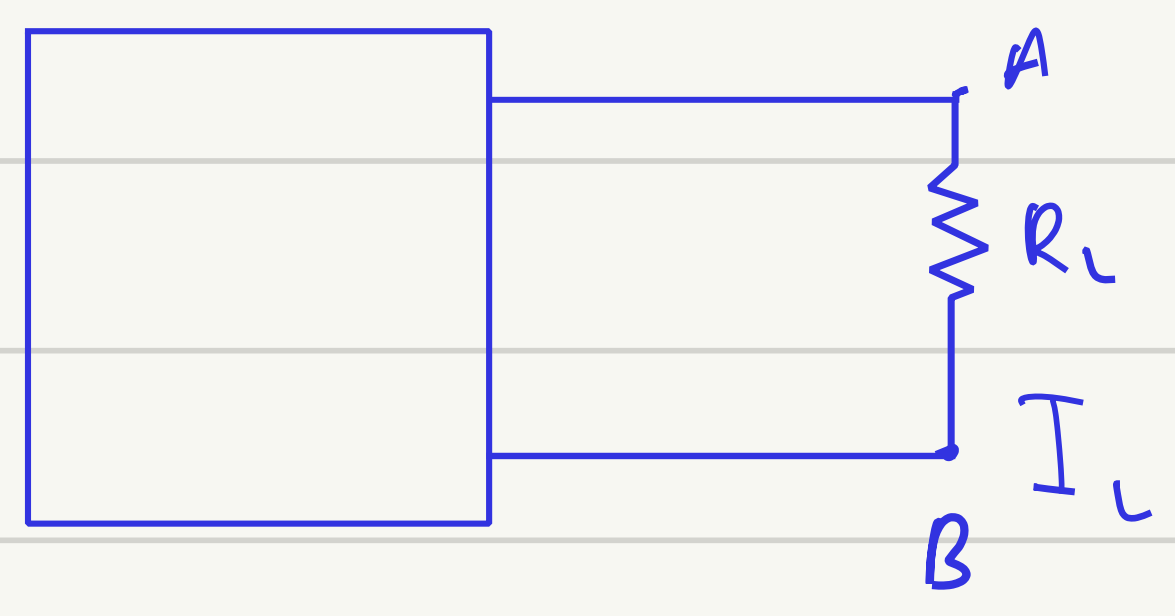

$$I_L = \frac{V_{Th}}{R_L + R_{Th}}$$

Norton Theorem

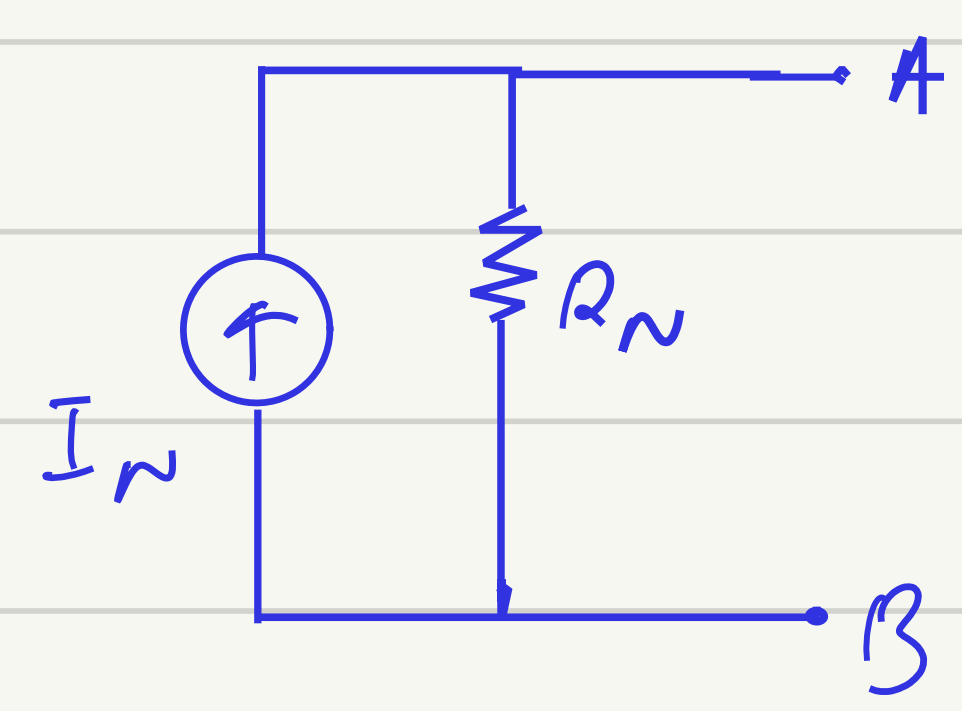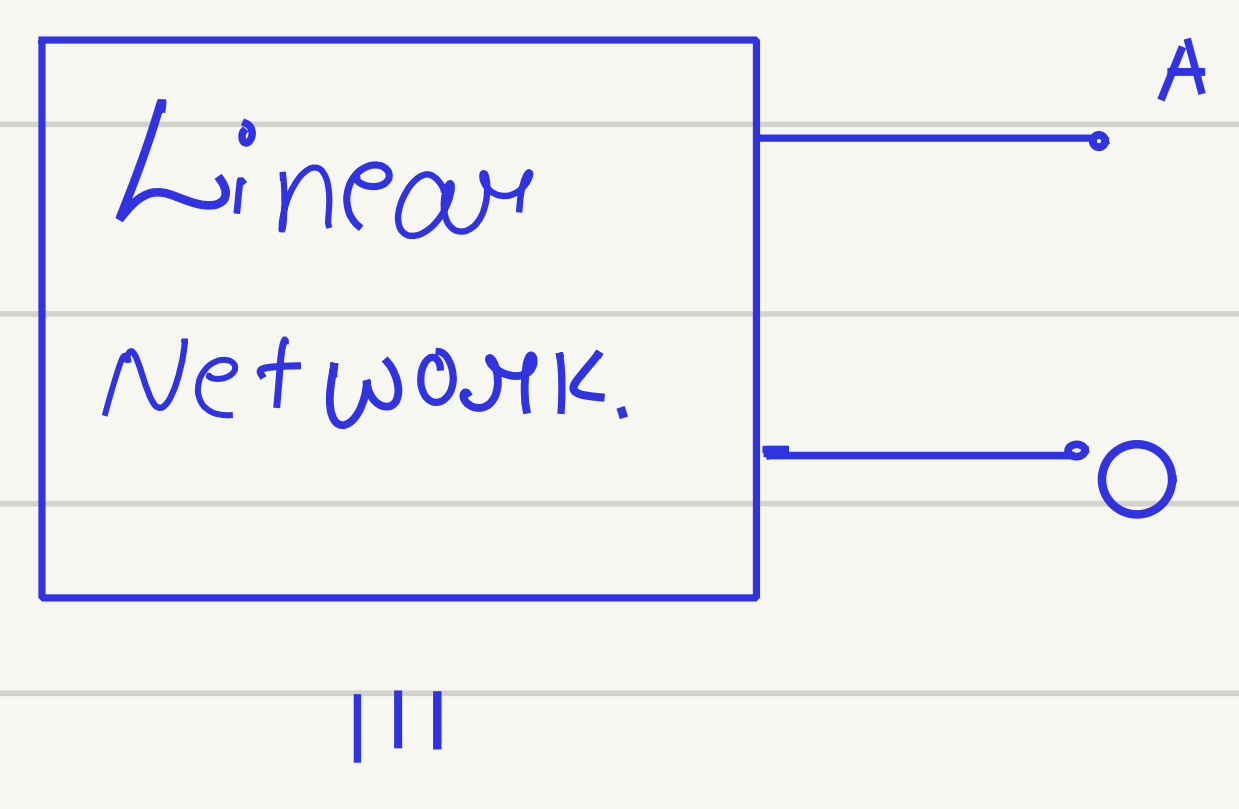


Norton equivalent circuit.

$$I_N = I_S = I_{AB}$$



$$R_N = R_{Th}$$

Source Transformation


Independent practical voltage source

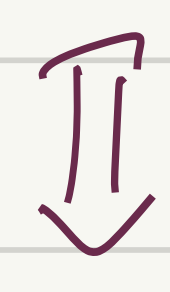

Independent practical current source

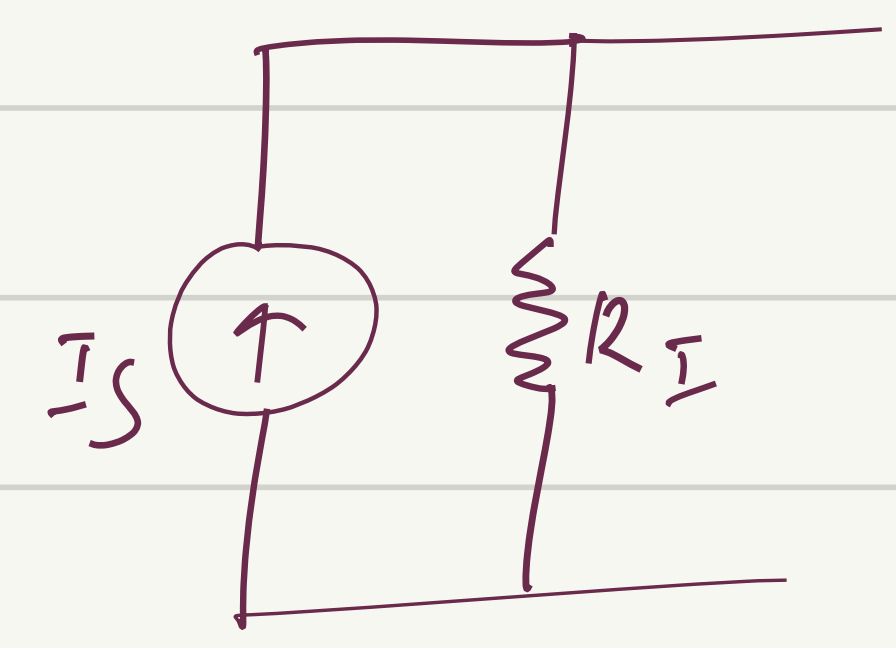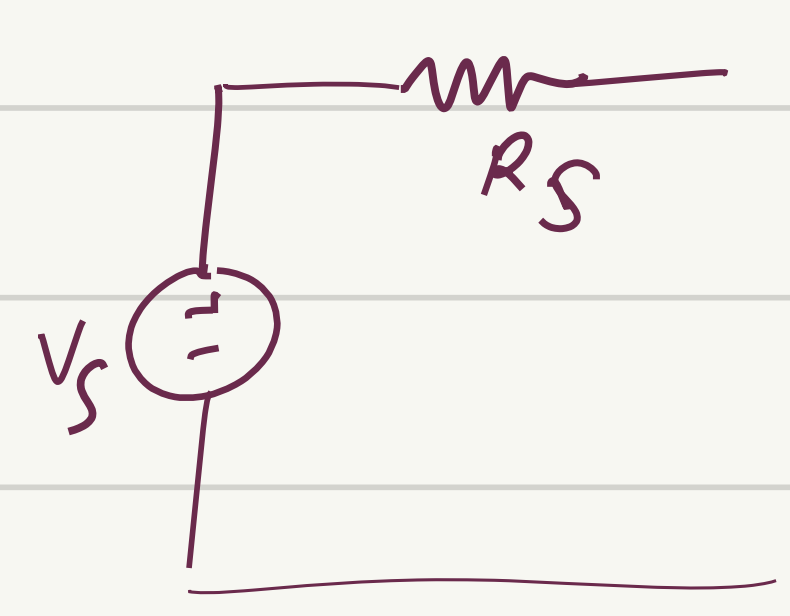

Maximum Power transfer theorem

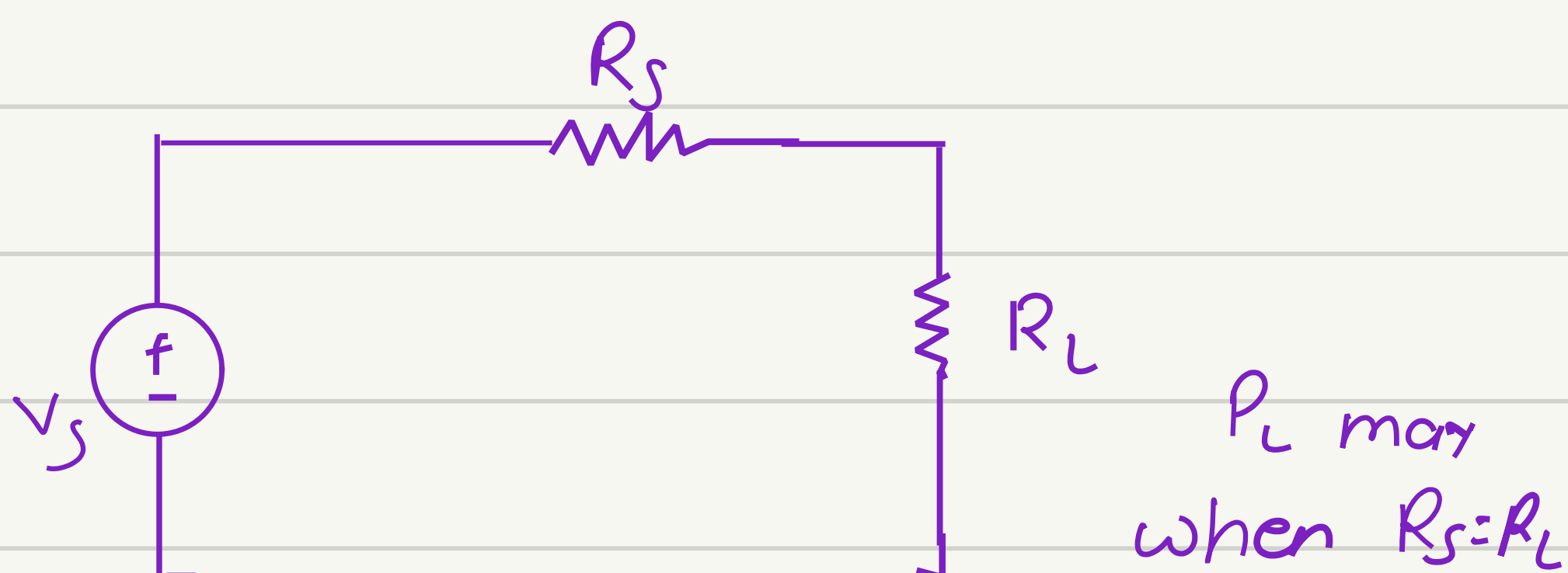

Tellegen's Theorem

$$\sum_{i=1}^n V_i I_i = 0$$








(Linear/non-linear network)

Unit-1 (Introduction)
DC circuit

Unit-2

Single Phase AC circuit.

Unit - 2 (Single Phase AC circuit)

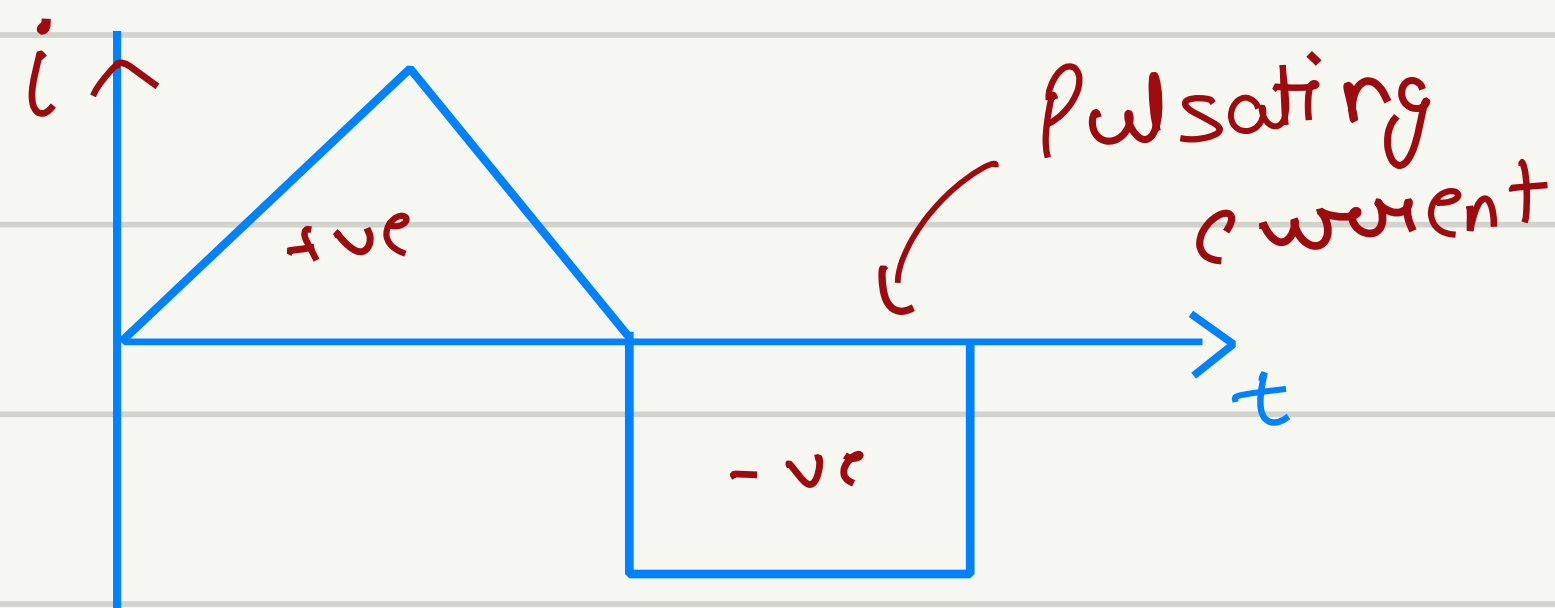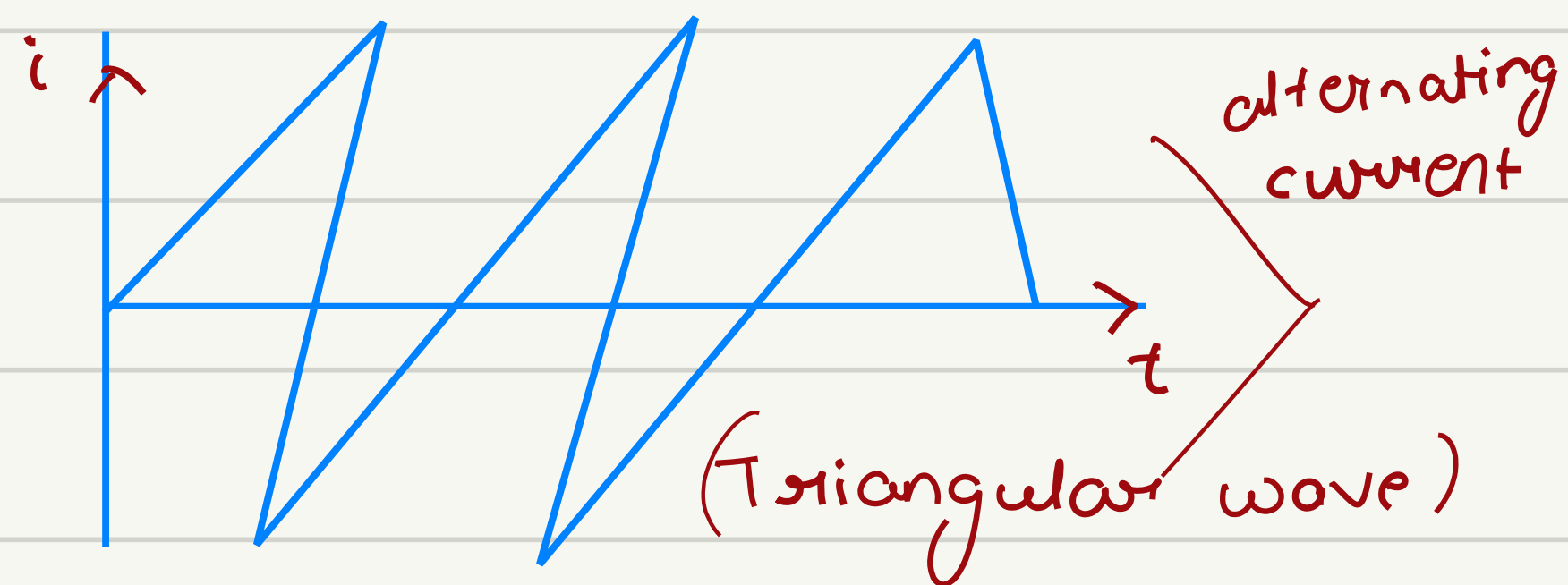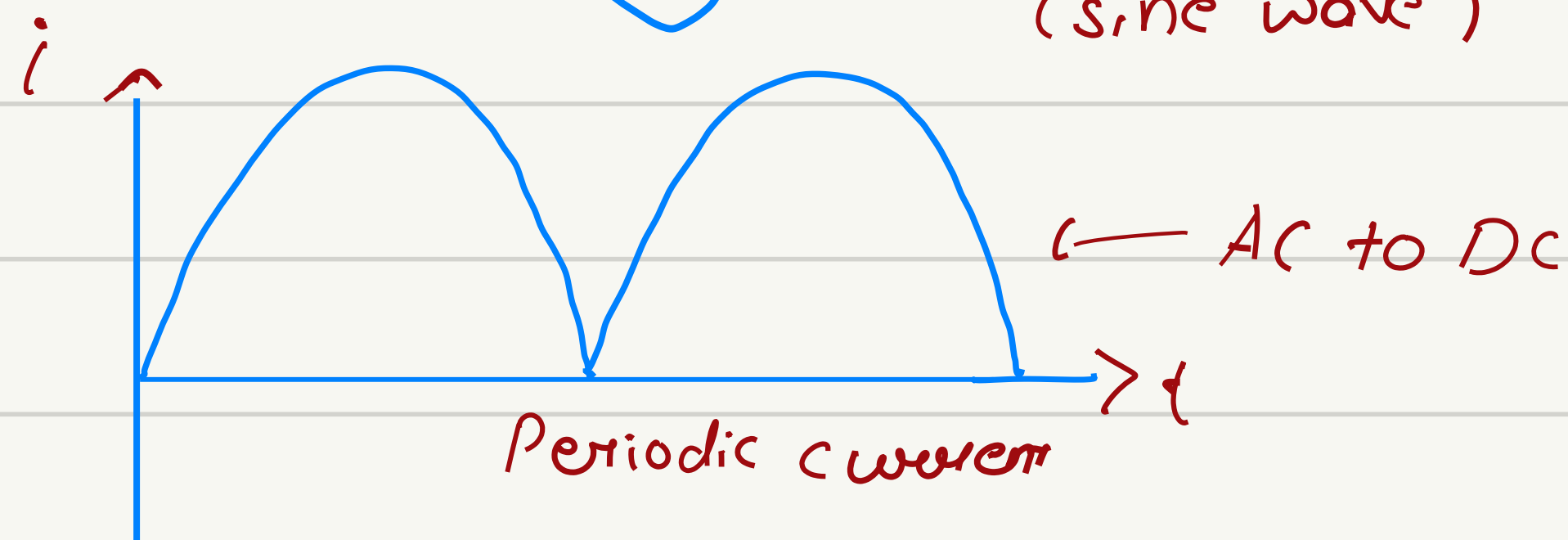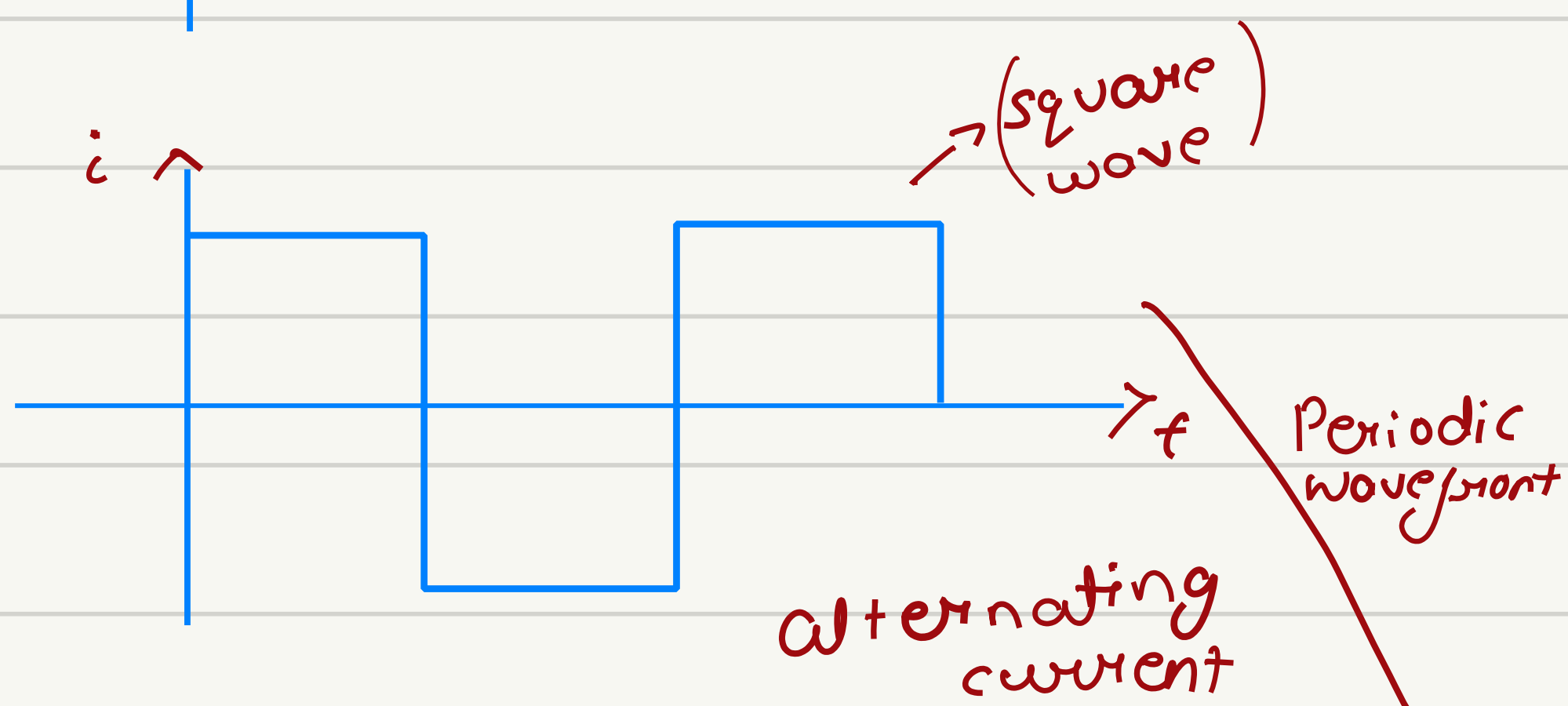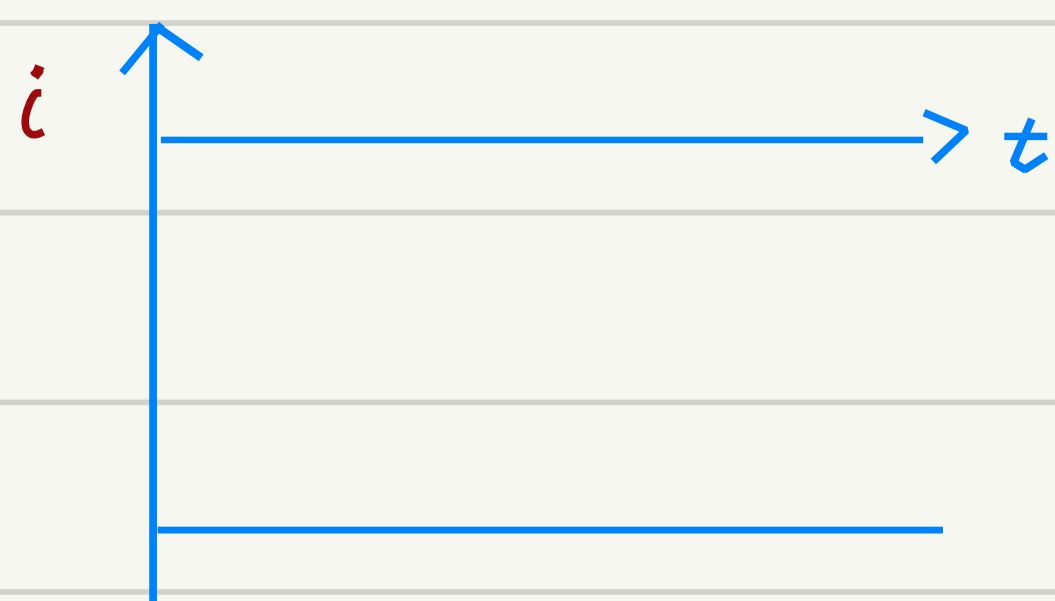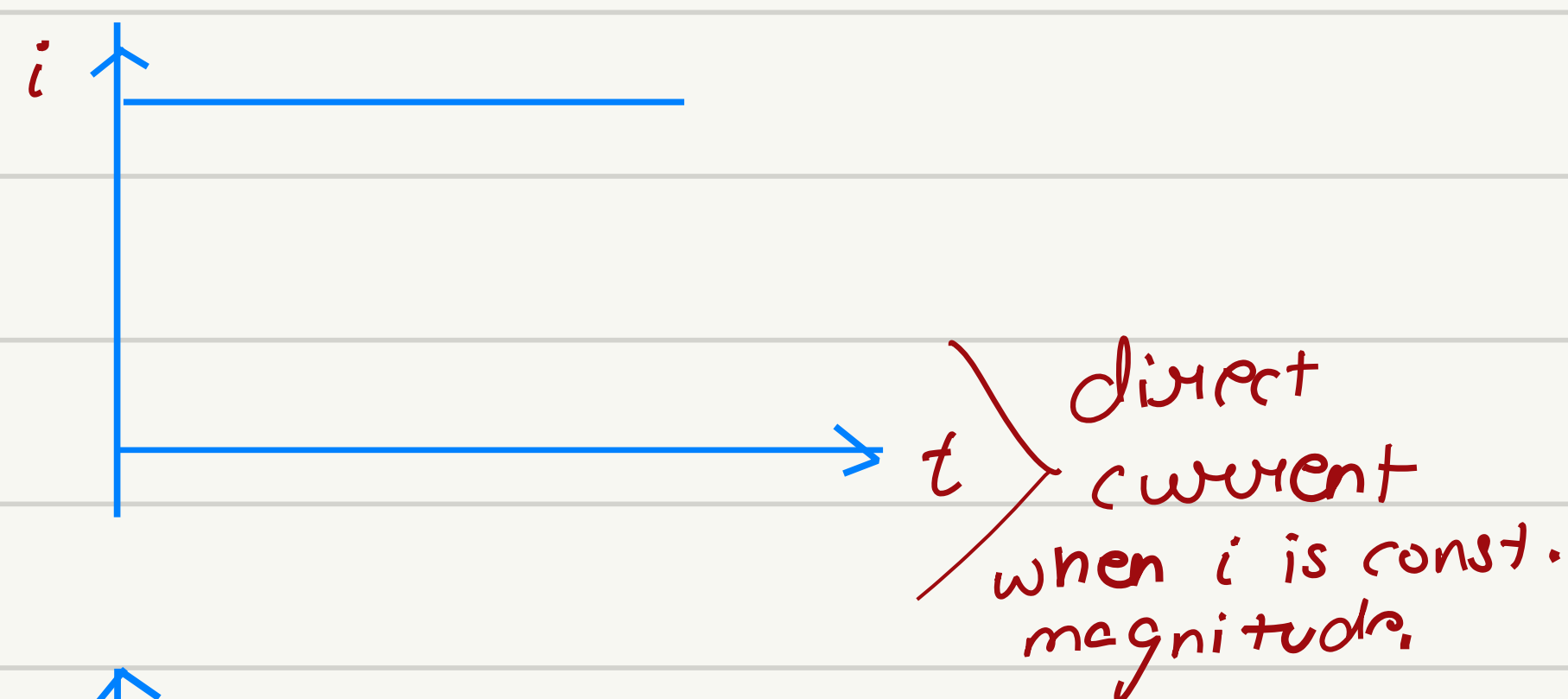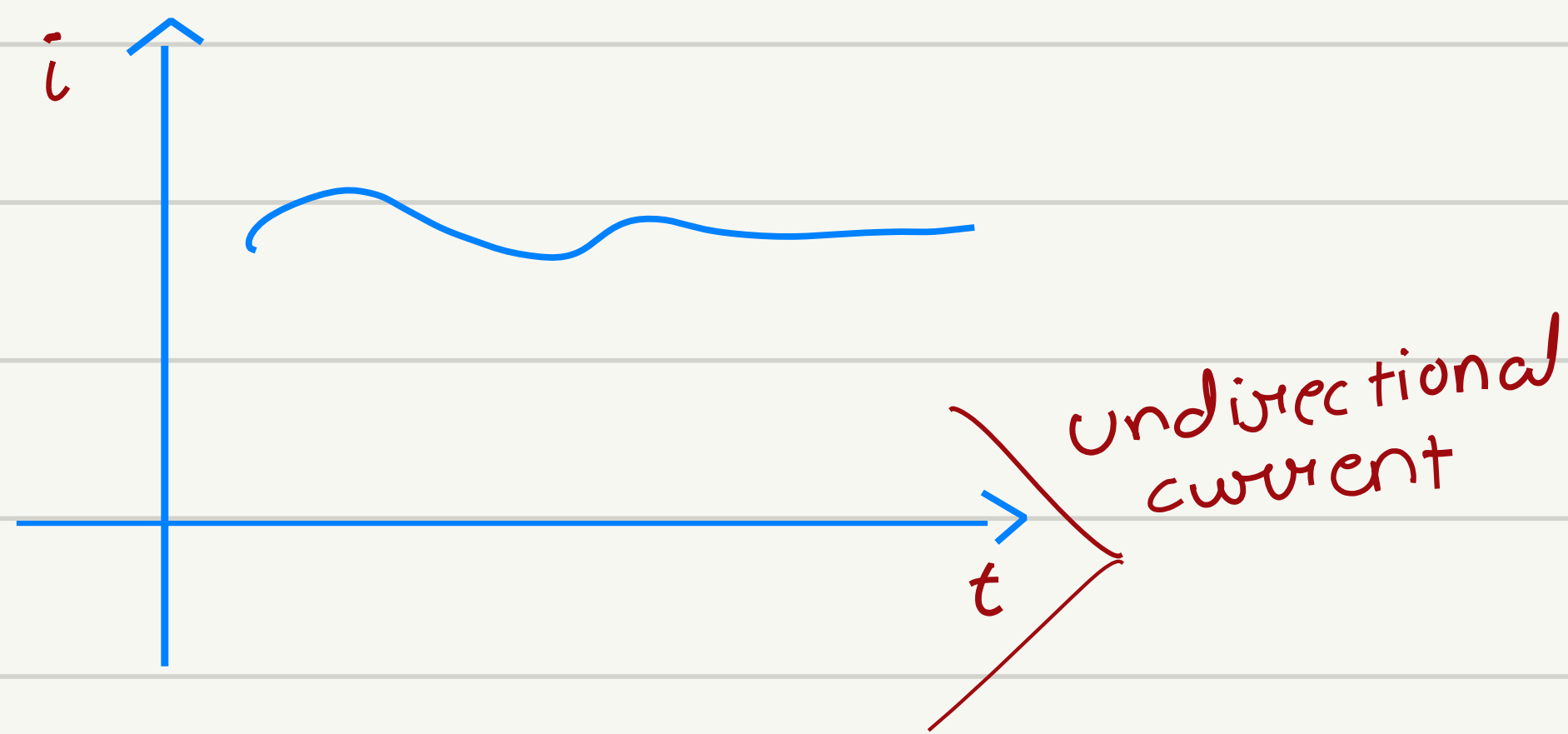

3000 RPM


1500 RPM

1000 RPM


600 RPM


Power Electronics


VSI

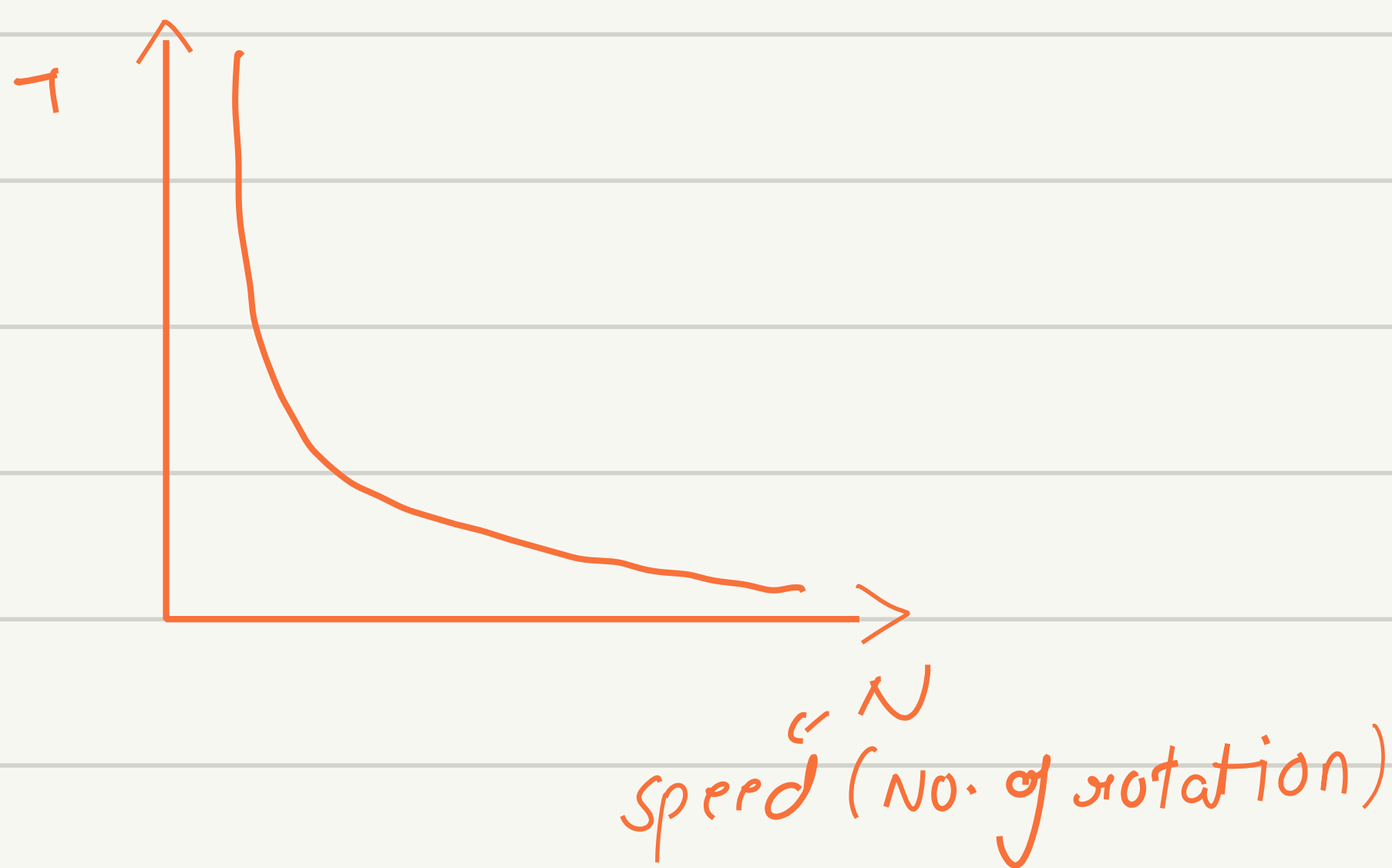





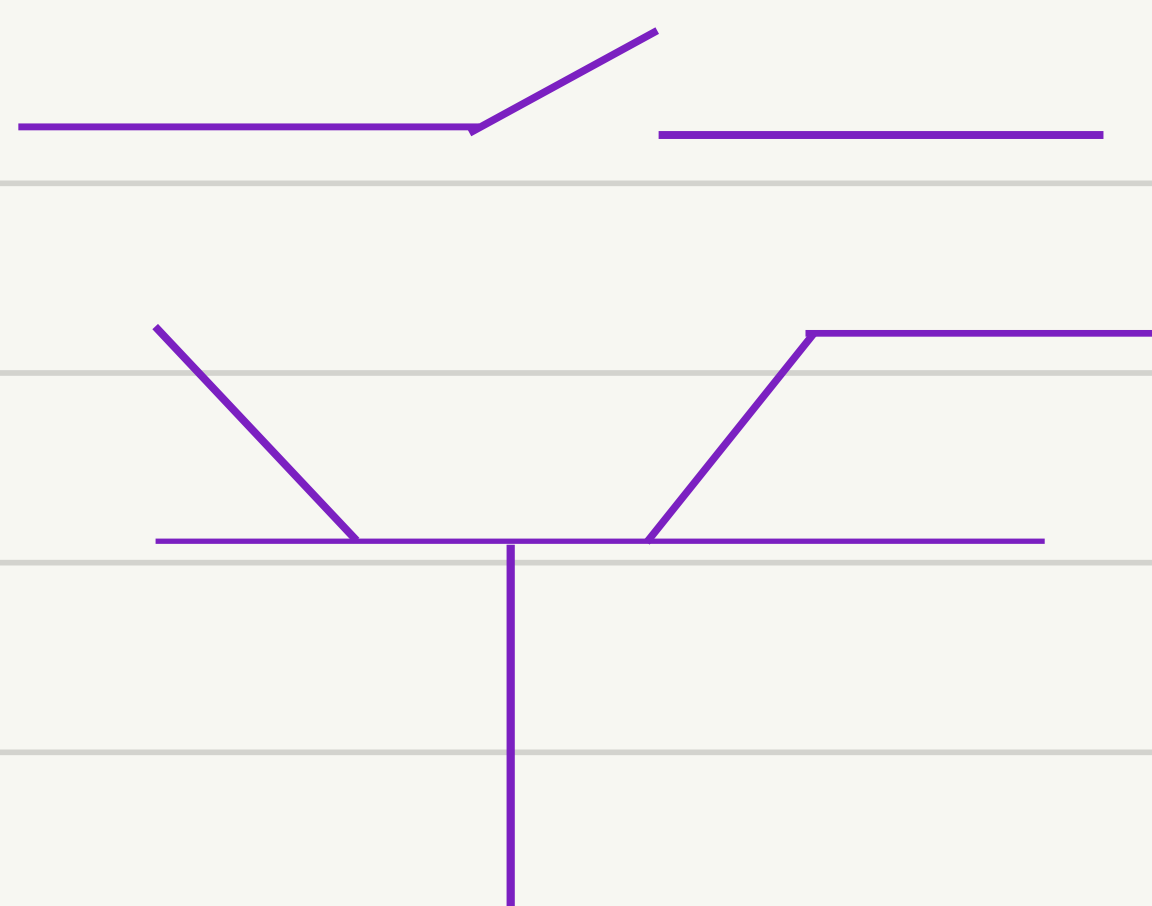
UPS (Uninterrupted power supply)
SMPS (Switch mode power supply)



 12V  DC to DC

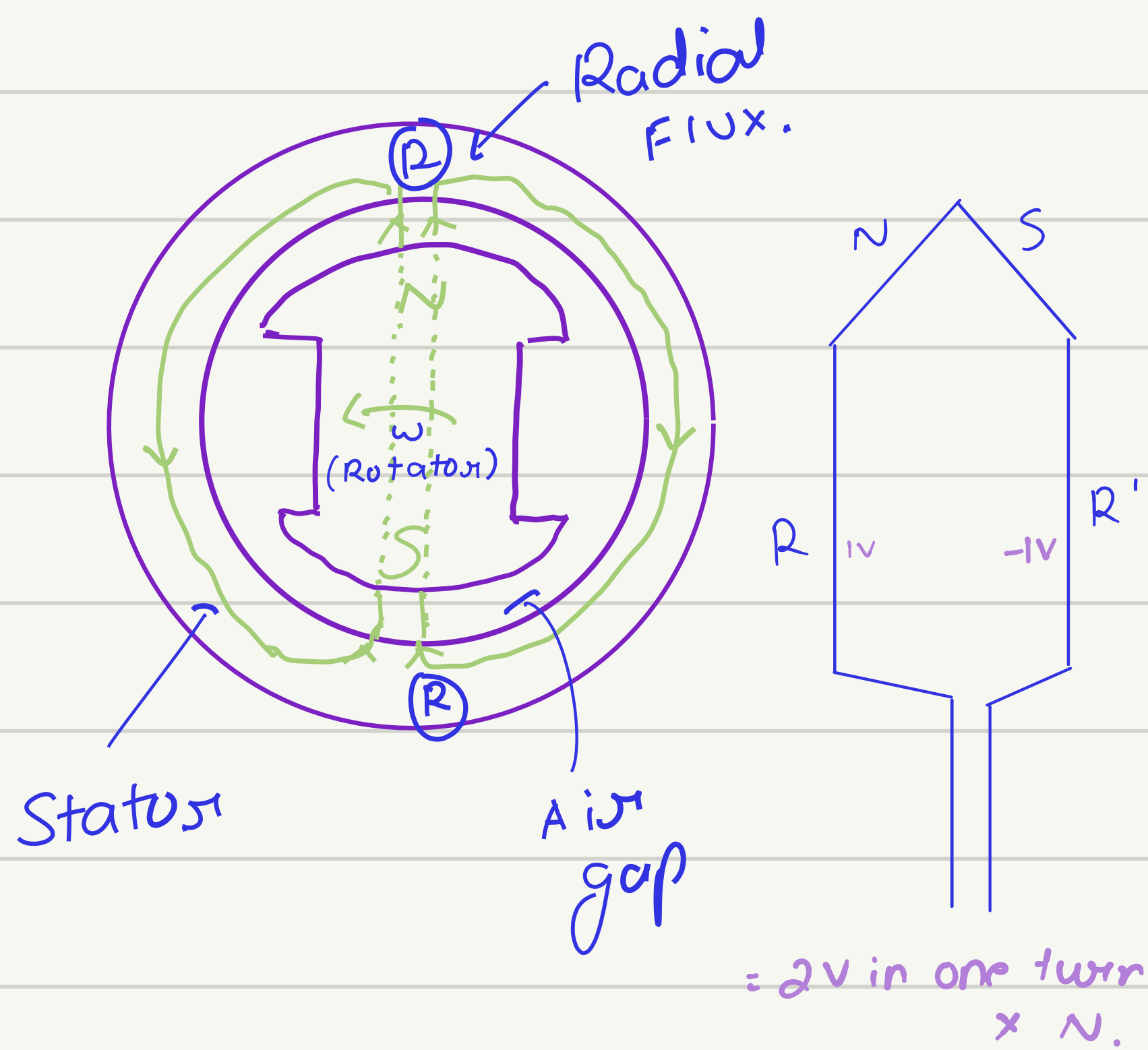

Average value

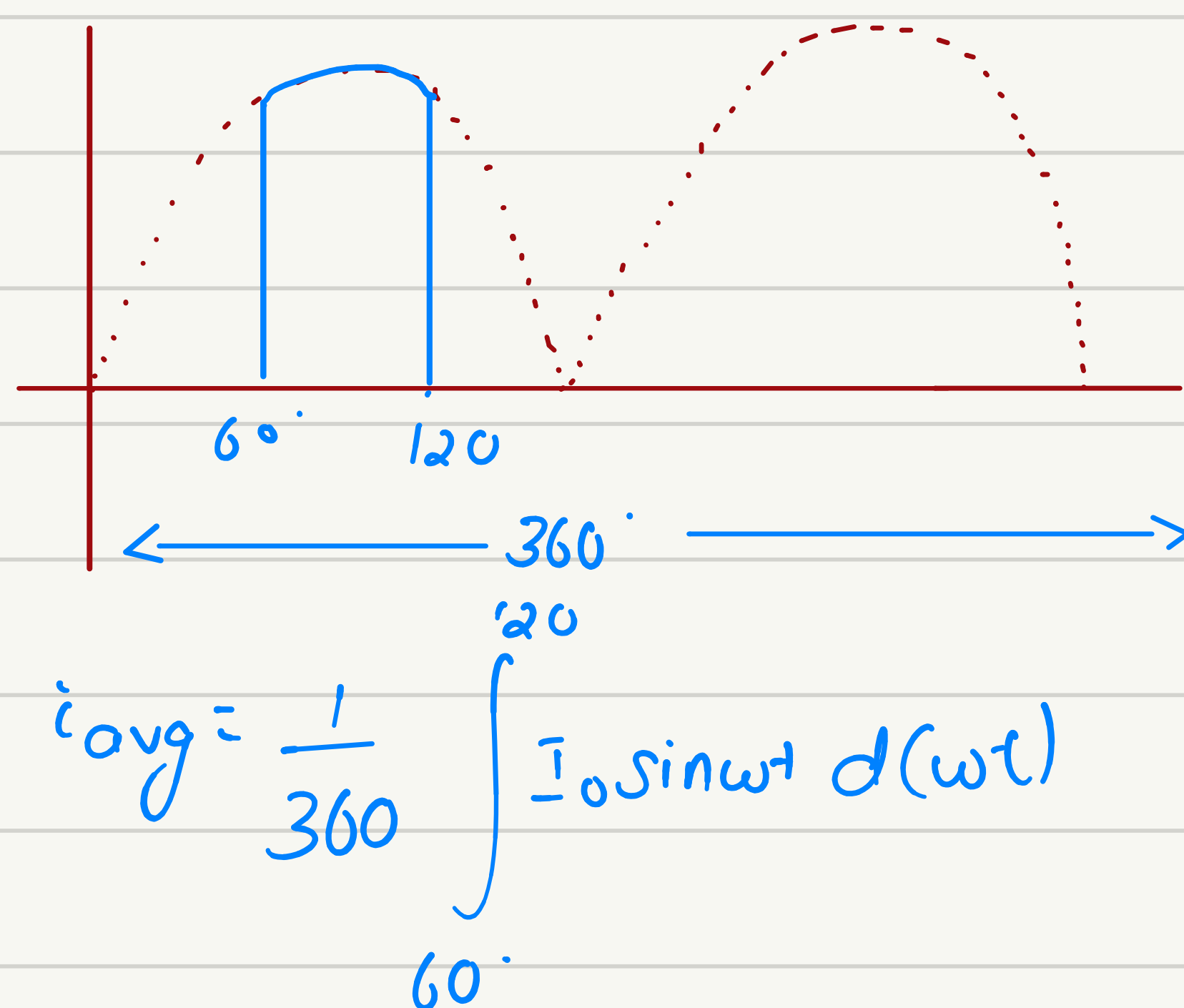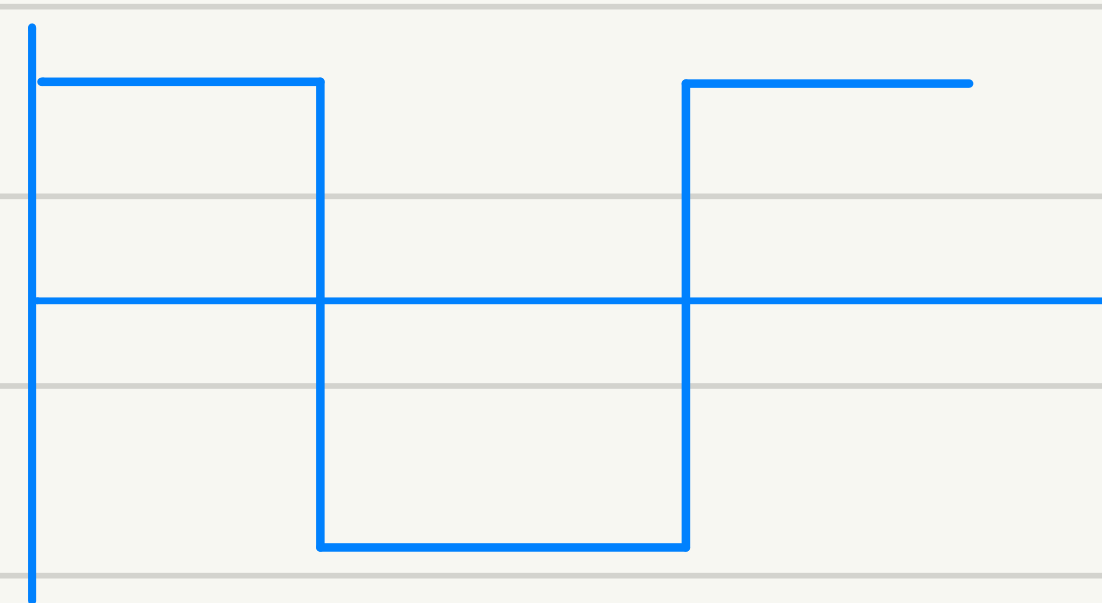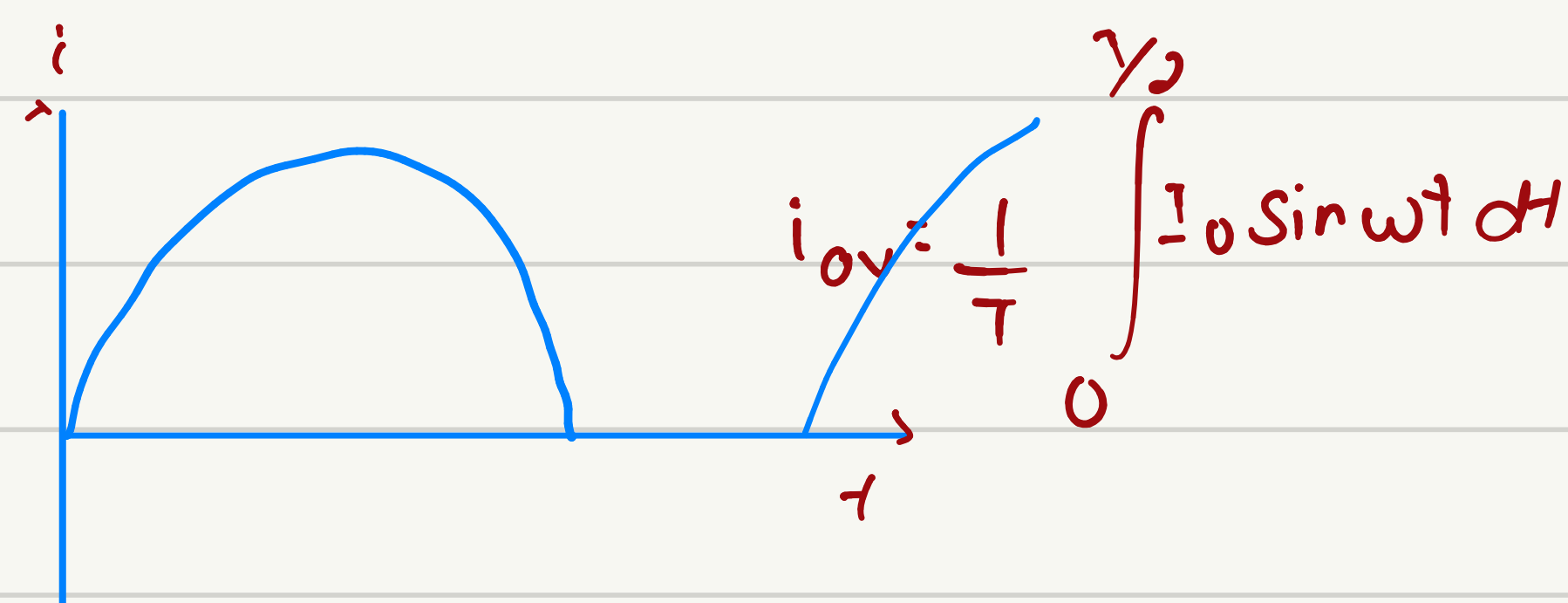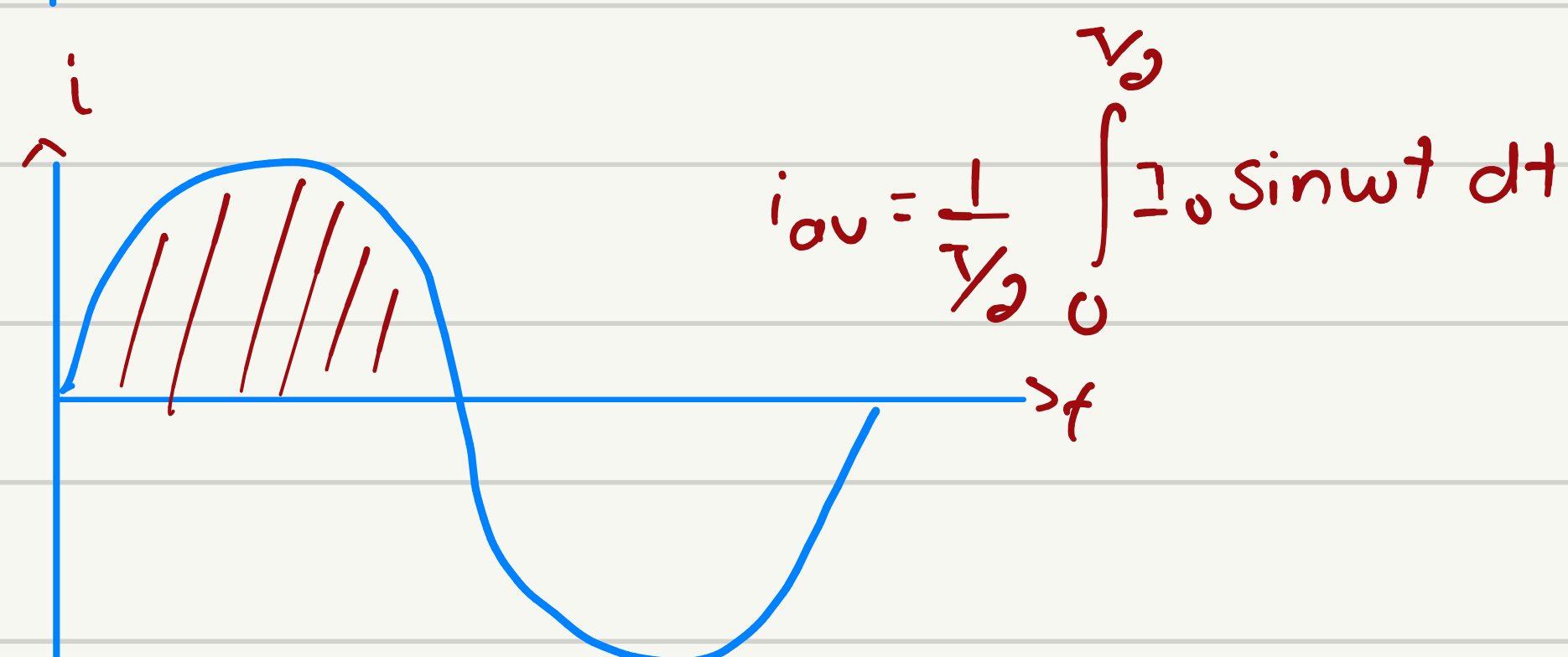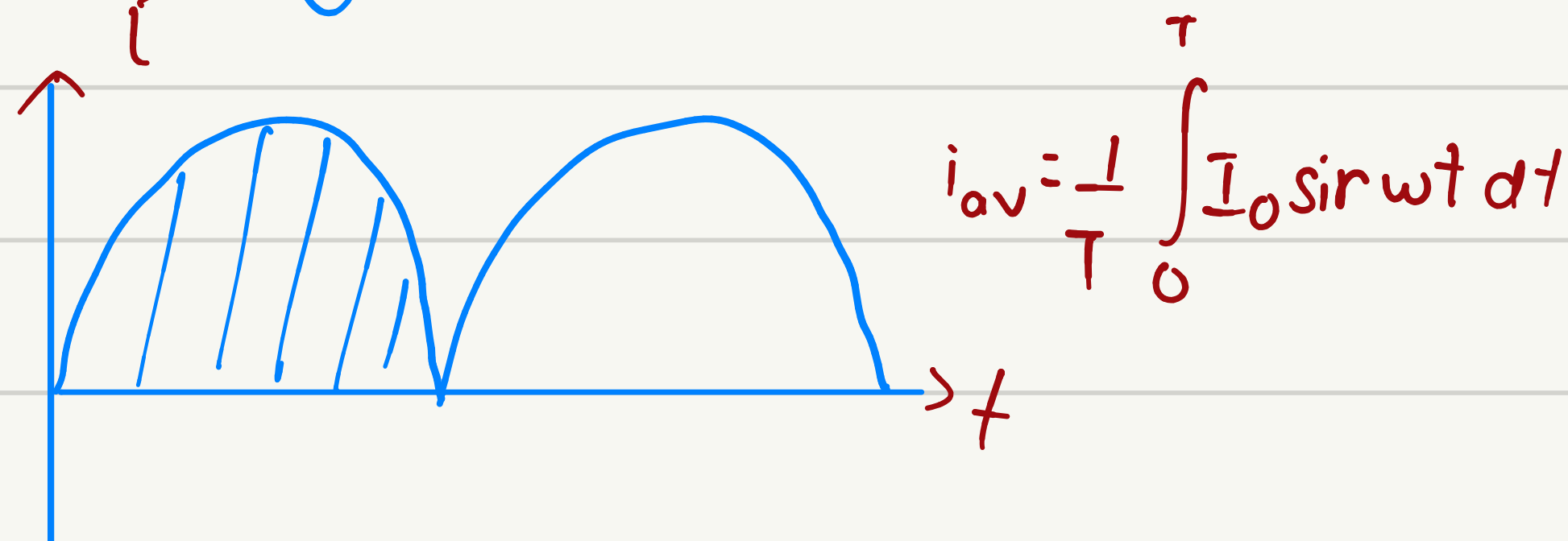

$l \rightarrow$ perpendicular

$\phi \rightarrow$ radial

$V \rightarrow$ tangential

$$\phi = \phi_m \cos(\omega t)$$

↓
De.


$\omega \rightarrow$ Radian/sec

$\theta_c \rightarrow$ Radian

$N \rightarrow$ no. of turns

$$\psi = N\phi$$
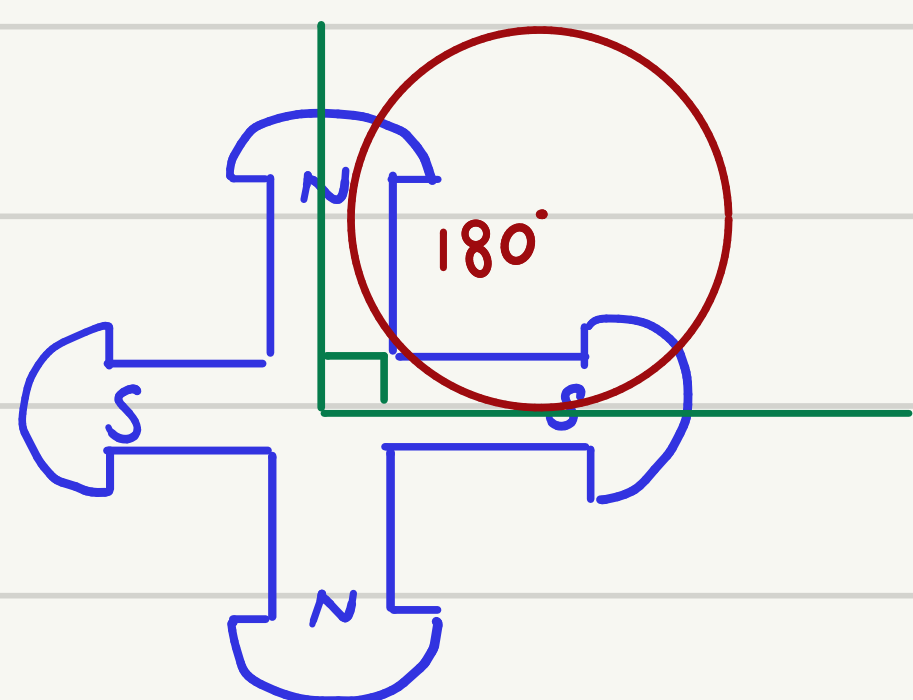
$$e = \frac{-d\psi}{dt} = N\omega \sin \omega t$$



$$\theta_c = \frac{P}{2} \theta_m$$

$$\omega_c = \frac{P}{2} \omega_m$$

$$\cancel{2\pi} f = \frac{P}{2} \cancel{2\pi} n$$

↓ ↓
Hz rps
 revolution

$$f = \frac{P}{2} n$$

$$f = \frac{P}{2} \frac{N}{60}$$

$$50 \text{ Hz} \leftarrow \boxed{f = \frac{PN}{120}} \leftarrow 3000 \text{ RPM}$$

↓
Min

$$N = 1500 \text{ RPM for } P = 4$$