

BE E Revision

Chapter - 1

→ Branch and Nodes → Two or more branches meet



Every circuit element constitute a branch

KCL:

Sum of current at node = 0

Incoming $I = +ve$
Outgoing $I = -ve$


KVL:

Sum of voltage rise / drop = 0

Voltage rise = $-ve$

Voltage drop = $+ve$

e.g.

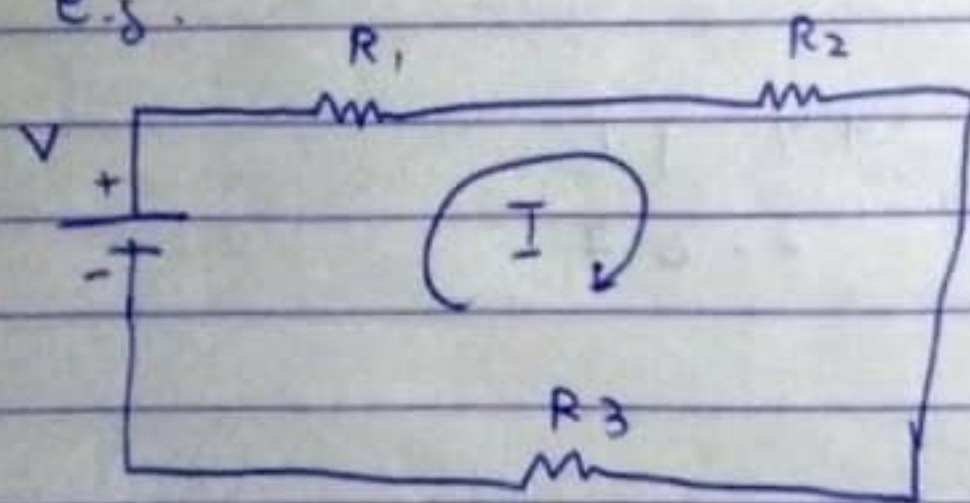

$$\Rightarrow -V + IR_1 + IR_2 + IR_3 = 0$$


$$\Rightarrow I(R_1 + R_2 + R_3) = V$$

→ If something is not defined then we can't apply them.


Mesh analysis: (Loop)

- 1) Identify total no. of loops and assign them loop current.
 - 2) Apply KVL
 - 3) Solve equations.
- Total no. of equations = $b - n + 1$
- $\xrightarrow{\text{No. of branches}}$
 $\xrightarrow{\text{No. of nodes}}$

Supermesh (Important) :

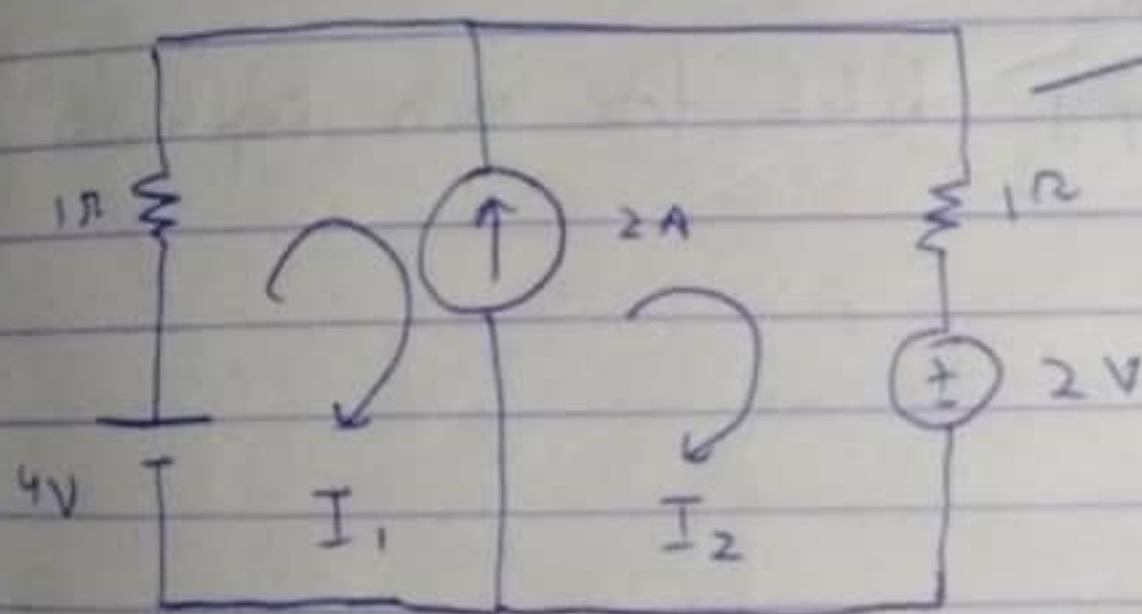

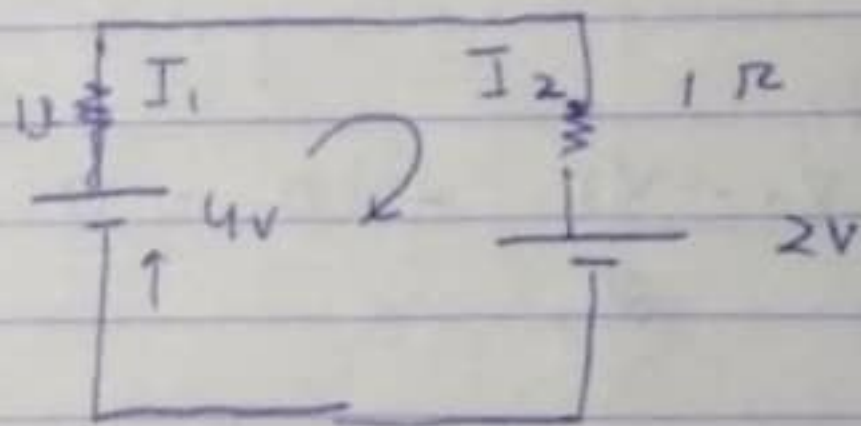This arrangement is super mesh.
(2A source b/w I_1 and I_2)
So, it is simplified as:



$$\Rightarrow -4 + I_1 + I_2 + 2 = 0$$

Also,

$$2 = I_2 - I_1 \quad (\rightarrow \text{ } I_1 \downarrow \text{ } 2A \text{ } \uparrow \text{ } I_2)$$

* Nodal analysis: $\rightarrow$ Identify total number of nodes (Only Principal)

$\rightarrow$ Take one node as reference node ($V = 0$)

$\rightarrow$ Assign voltage to remaining nodes $\rightarrow$ Apply KCL $\rightarrow$ Total eqn = $(N - 1)$


gm doing $\frac{V_1 - V_2}{R}$, V_1 is generally
 potential voltage

e.g. $\begin{matrix} V_1 \\ R \\ V_2 \end{matrix} \downarrow I \Rightarrow \frac{V_1 - V_2}{R}$

Also $\begin{matrix} V_1 & & V_2 \\ & + & - \\ & | & \\ & V & \end{matrix}$

$$V = V_1 - V_2$$

Super Node:

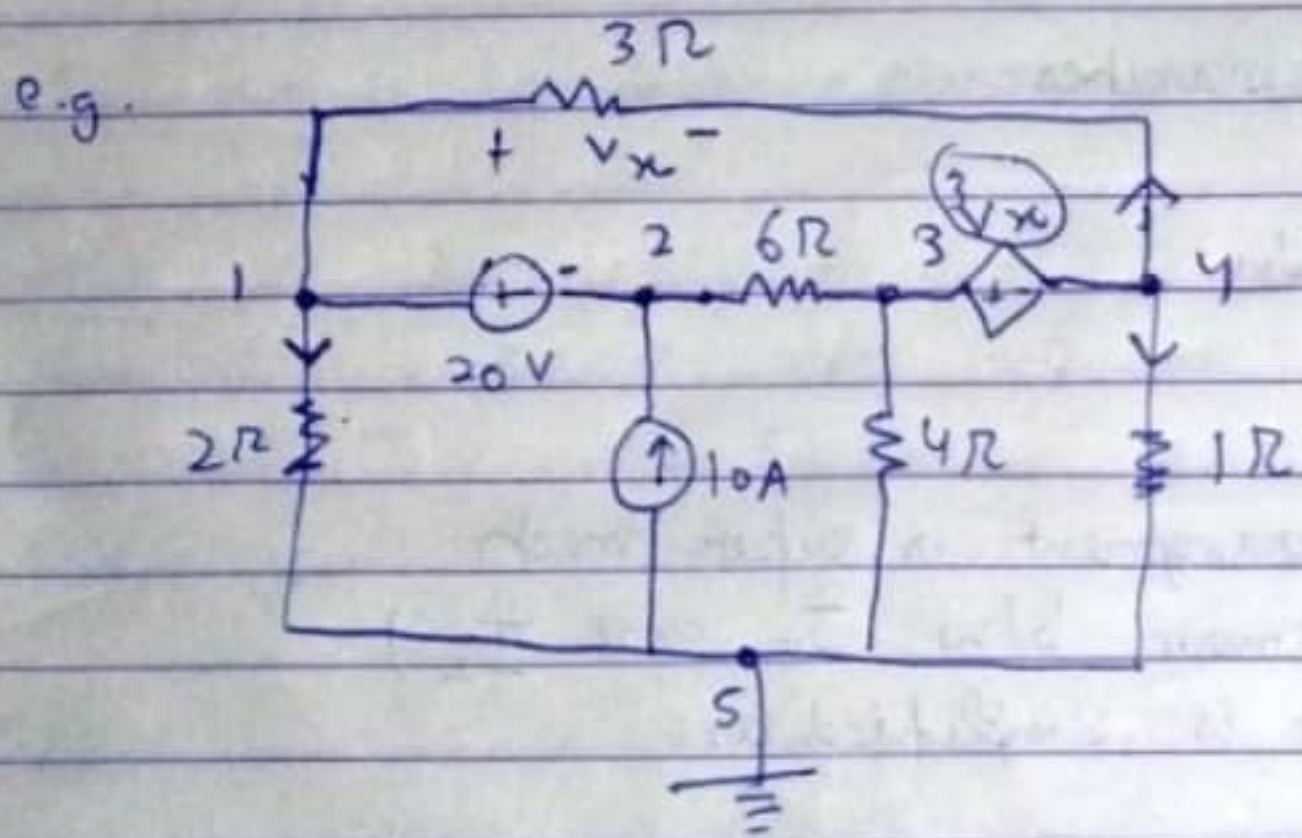

Total nodes = 5

1 and 2, 3 and 4 have ~~no~~ resistance in between so (1,2) and (3,4) constitute two supernodes

We will apply KCL for each supernode

For 1, 2 ~~node~~

$$\frac{V_1}{2} + \frac{V_1 - V_4}{3} + \frac{V_2 - V_3}{6} - 10 = 0$$

For 3, 4:

$$\frac{V_3 - V_2}{6} + \frac{V_3}{4} + V_4 + \frac{V_4 - V_1}{3} = 0$$


Also, $V_1 - V_2 = 20$

$V_3 - V_4 = 3V_x$

$V_1 - V_4 = V_x$

→ For finding equivalent resistance, identify the equivalent points and rearrange the circuit.

* Star Delta:

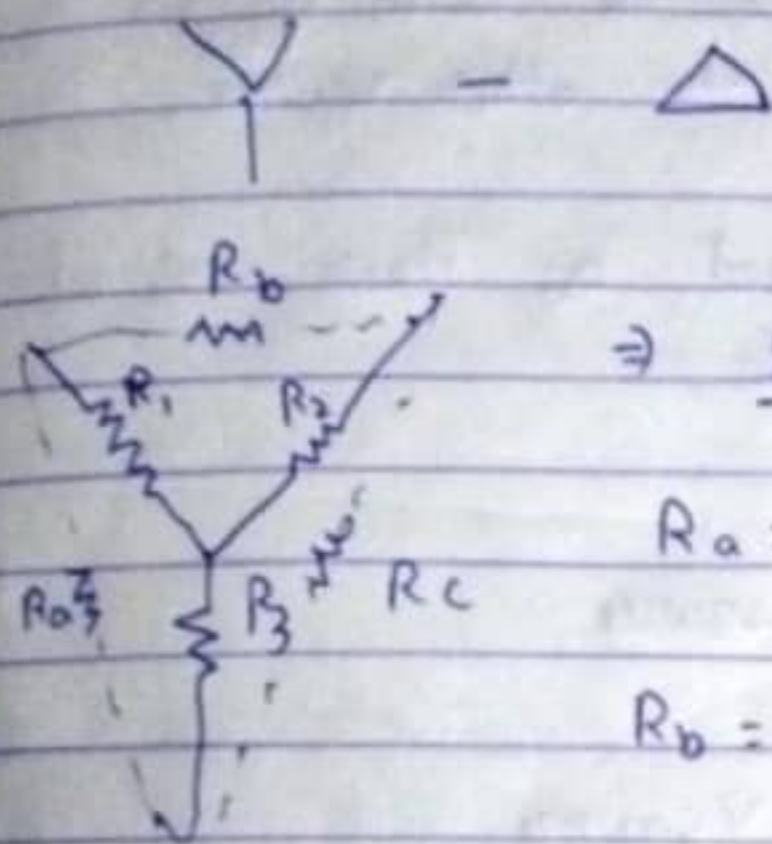


⇒ Star to Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

⇒ Delta to Star!

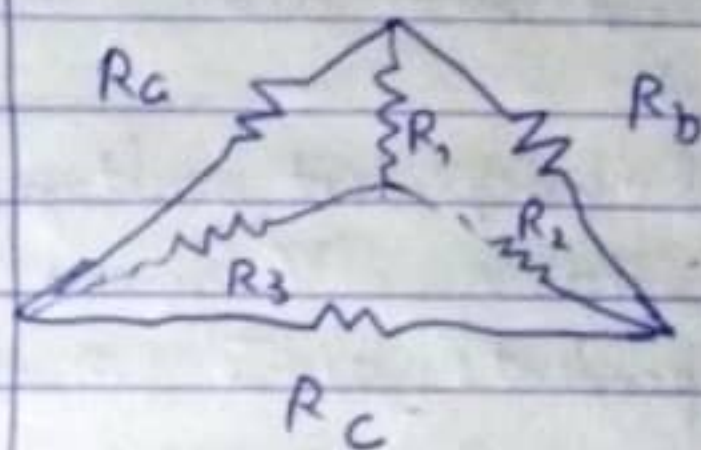

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$

* When resistors of equal values are transformed from Y-Δ

$$R_\Delta = 3R_Y$$

* When capacitors of equal — Y to Δ

$$C_\Delta = \frac{1}{3} C_Y$$

(In capacitors same transformation can be done by doing $\frac{1}{C}$ instead of R in both LHS and RHS)

S.C $\rightarrow$ Short Circuit, O.C $\rightarrow$ Open Circuit

* Superposition Theorem:

In a linear, bilateral network containing more than one independent / dependent voltage / current source, the response in any element is the sum of the responses obtained with one source acting at a time and the other source being deactivated.

- $\rightarrow$ All independent voltage / current source are replaced by their internal resistance. V Source $\rightarrow$ S.C, C Source $\rightarrow$ O.C
- $\rightarrow$ Dependent source $\Rightarrow$ No change



e.g

Q Find I using superposition theorem

More than one source


First consider 12V source

O.C $\rightarrow$ Current source

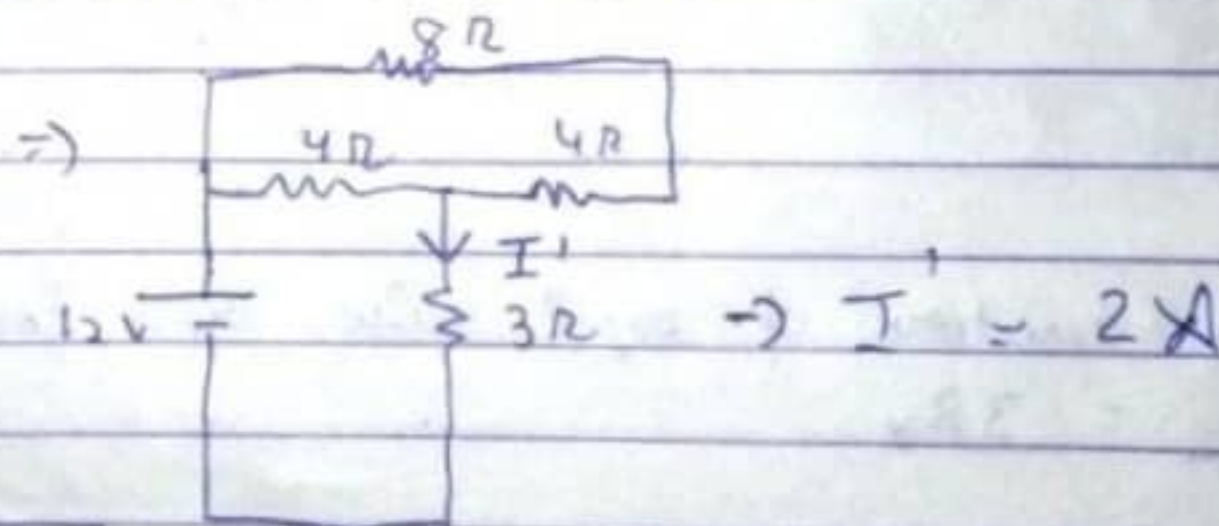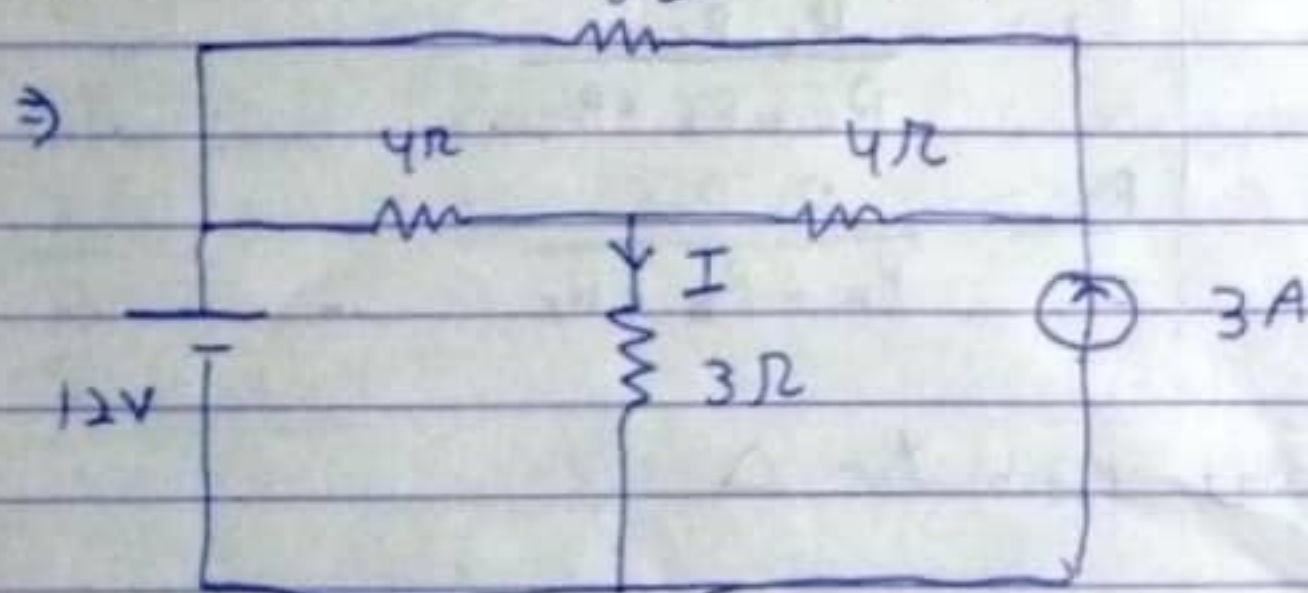

Now 3A source $\Rightarrow$

S.C $\rightarrow$ V.C

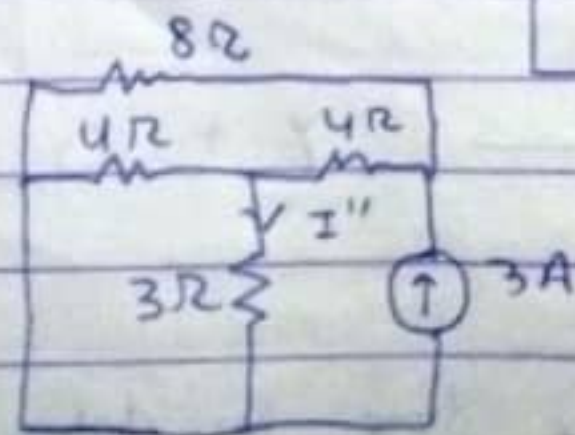


Apply KCV

$I'' = 1A$

So, $I = I' + I'' = 1A + 2A = 3A$ Ans.

Q Important Question

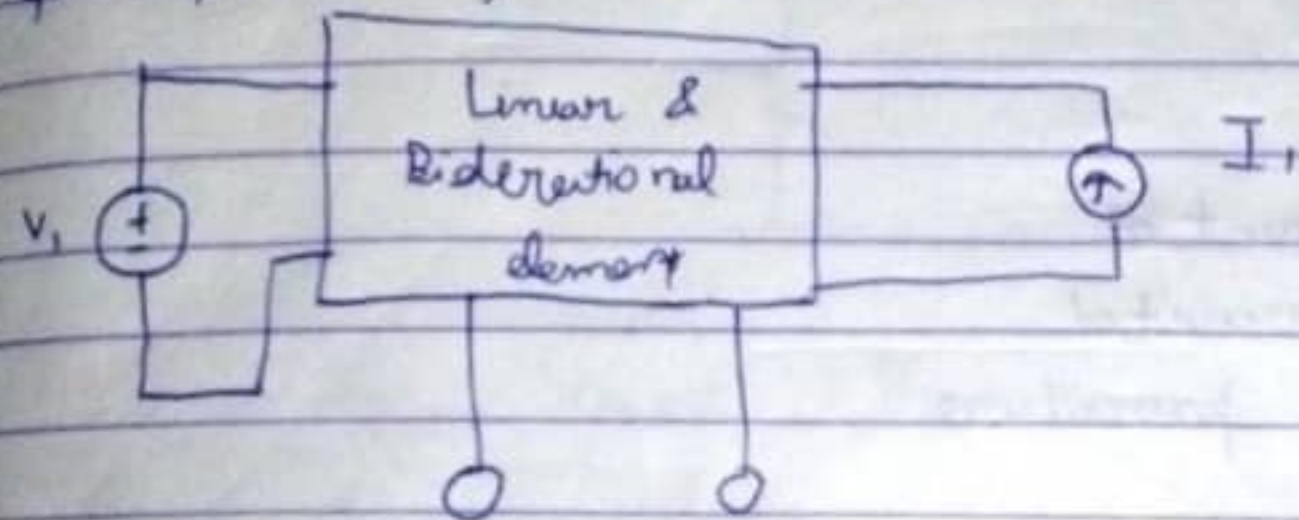

V_1	I_1	V_0
5V	0A	3V
0V	2A	6V

Find V_0 when $V_1 = 10V$
 $I_1 = 8A$


2) $V_0 = \alpha V_1 + \beta I_1$

$\Rightarrow 3 = \alpha \cdot 5 + \beta(0) \Rightarrow \alpha = \frac{3}{5}$


$6 = 2\beta \Rightarrow \beta = 3$

So, $V_0 = \frac{3}{5} \times 10 + 8 \times 3 = 6 + 24 = \underline{30V}$

* Theremin's theorem:

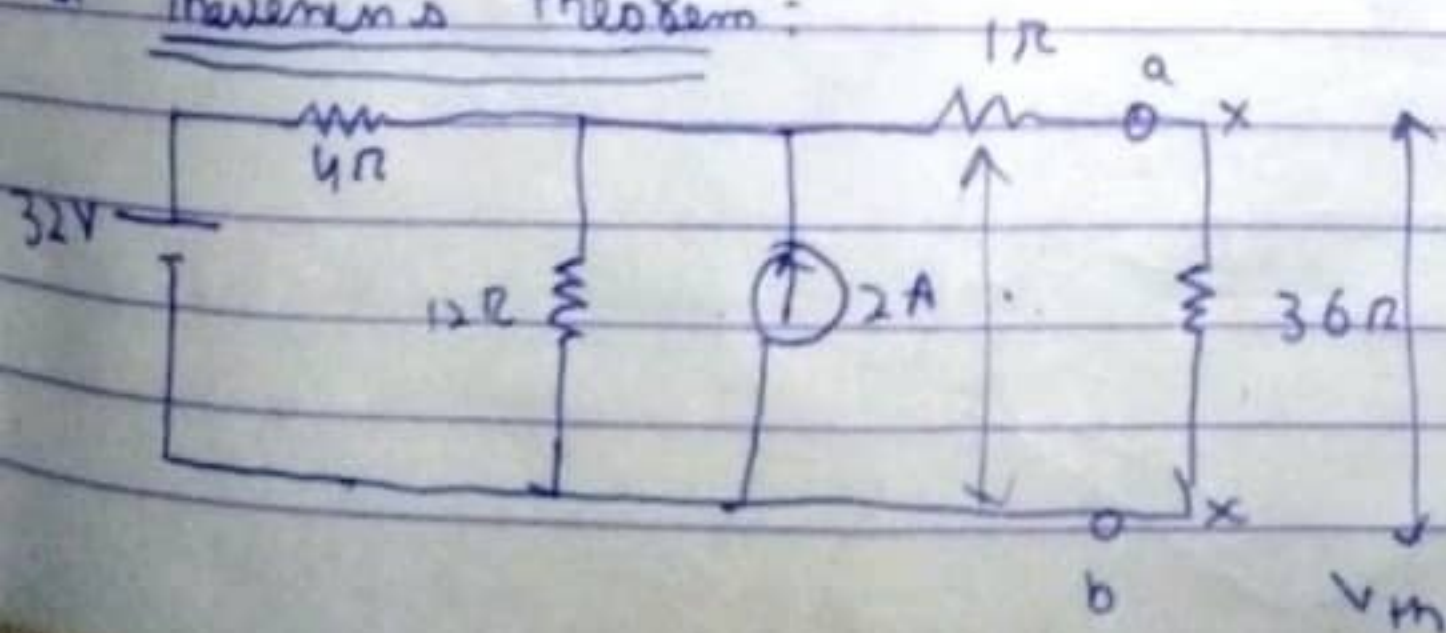

$\Rightarrow$ Thevenin Equivalent

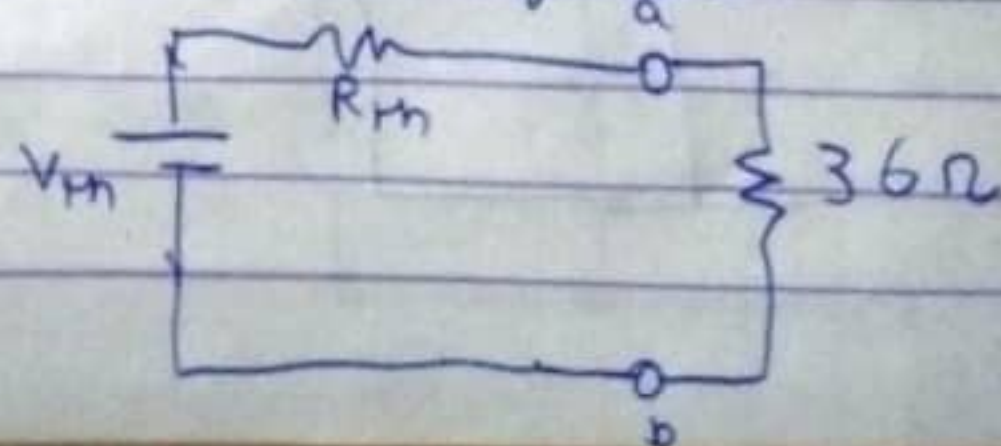

For V_{th}
Two terminal Open circuited, Voltage across the open circuited terminal is V_{th}

For R_{th}


- Terminal ab → Open
- Independent Vtg source = Short circuited
- " " Current " = Open circuited
- Dependent Vtg / I source ⇒ Diff. procedure


Dependent Sources:


Three ways:

- 1) Connect 1V source across the terminal
- 2) Connect 1A source
- 3) $R_{th} = \frac{V_{th}}{I_N}$

Norton Theorem:

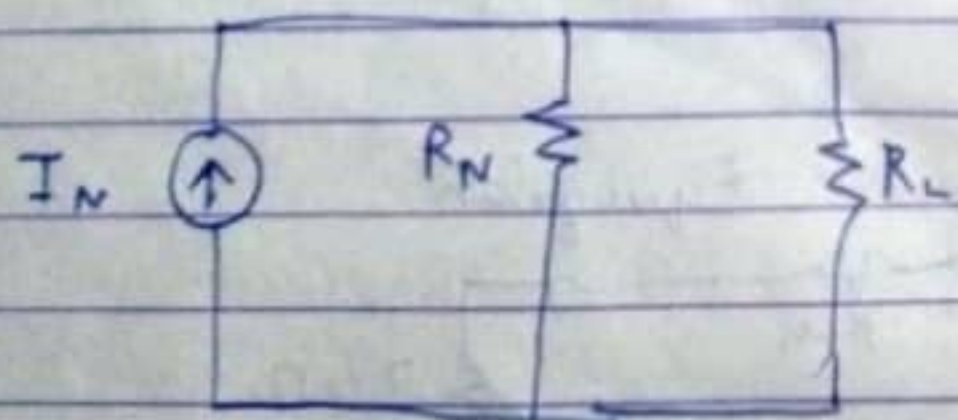

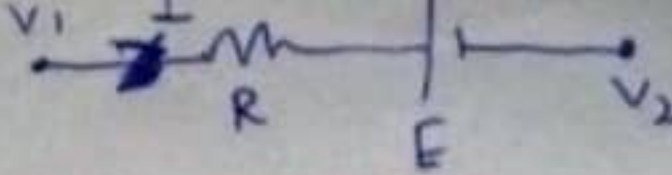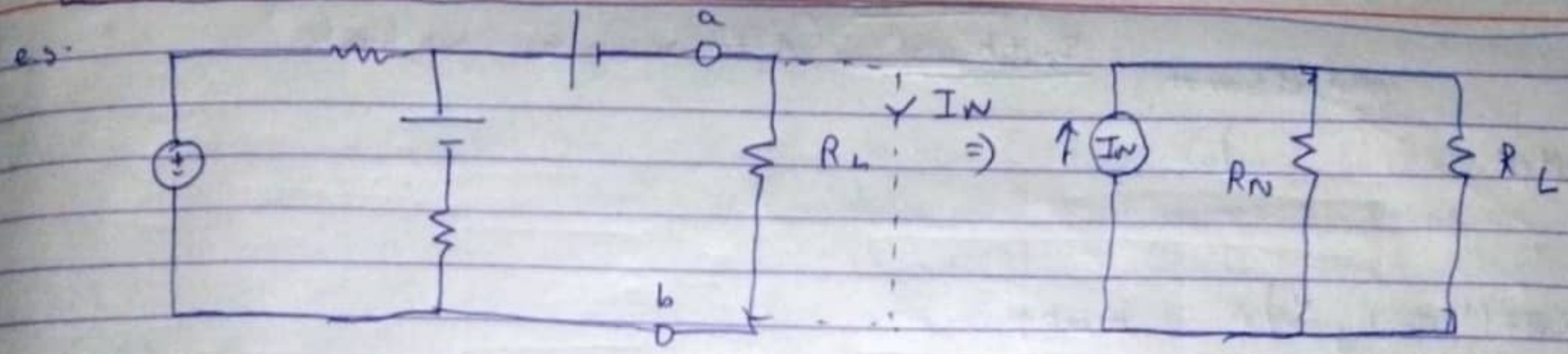
*  $\Rightarrow I = \frac{V_1 - V_2 + E}{R}$,, Reverse E polarity and it will be $-E$.




For I_N Short R_L
 For R_N :
 Short all voltage source

Maximum Power $\Rightarrow R_L = R_S$

Tellegm's $\sum P = 0$

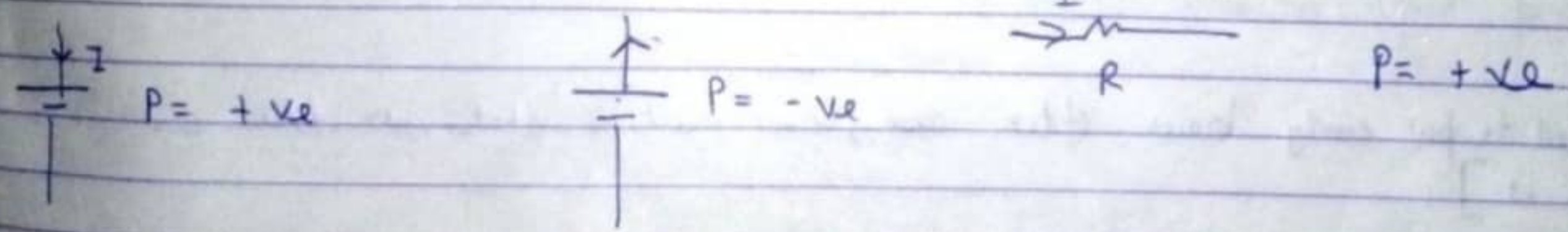

Source transformation:

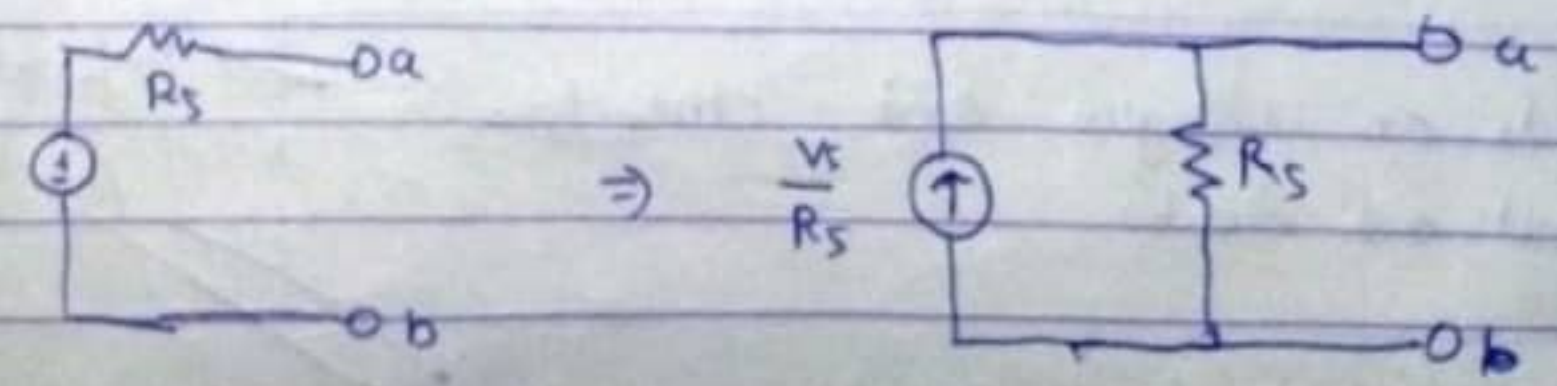

$$\omega = 2\pi f$$

$$f = \frac{1}{T}$$

x can be V or I whatever we need to calculate

$$x_{av} = \frac{1}{T} \int_0^T x_m \sin t \, dt$$

Values

R.M.S value:

The voltage / current at which the heat dissipated in an AC circuit is equal to the heat dissipated in a DC circuit (provided both have same resistance and operated for same time).

$$x_{r.m.s} = \sqrt{\frac{1}{T} \int_0^T (x_m \sin t)^2 \, dt}$$

$$\text{Form factor} = \frac{\text{R.m.s value}}{\text{Average value}}$$

$$\text{Peak or Amplitude or Crest factor} = \frac{\text{Max value}}{\text{R.M.S value}}$$

Peak is clearly the highest value reached

$$V(t) = V_m \sin(\omega t + \phi) \Leftrightarrow V_m \angle \phi \quad [\text{phasor}]$$

While doing mathematical operations on phasors ensure the following:-

- All the phasors must be a sine/cos form
- Same freq.
- Same sign of amplitude


Impedance :

$$Z = \frac{V}{I} = R + jX \quad \text{or} \quad |Z| \angle \theta$$

Z is not a phasor

X_L or X_C (j just means 90° angle)

$$|Z| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1}\left(\frac{X}{R}\right) \quad \begin{cases} R = |Z| \cos \theta \\ X = |Z| \sin \theta \end{cases}$$

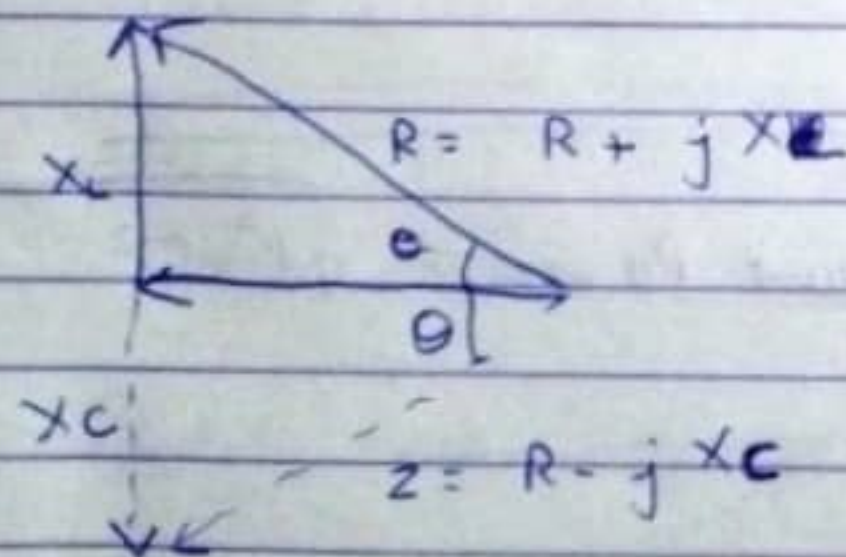

Impedance Δ

Admittance

$$Y = \frac{1}{Z} = \frac{I}{V}$$

$$G + jB = \frac{R}{R^2 + X^2} + j \frac{X}{R^2 + X^2}$$


Conductance Susceptance

$$X_L = j\omega L$$


$$X_C = \frac{1}{j\omega C}$$

$$P_{avg} = V_{rms} I_{rms}$$

* In inductor current lags by 90°

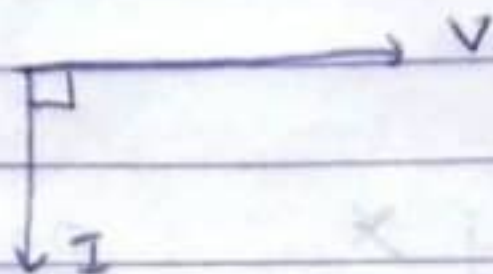

* In capacitor current leads by 90°

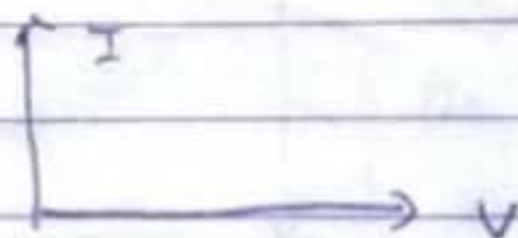

$$\text{Complex Power (S)} = V_{rms} I_{rms}^*$$

$$S = P + jQ$$

Complex Power (VA unit) Real (W-unit) Reactive (Var) (W-unit)

$$|S| \text{ is apparent Power} = \sqrt{P^2 + Q^2}$$


$$P = VI \cos \phi \quad Q = VI \sin \phi$$

$$S = P + jQ_L \text{ and } S = P - jQ_C$$

JATIN - 2K21/A12/03

$$P \downarrow$$
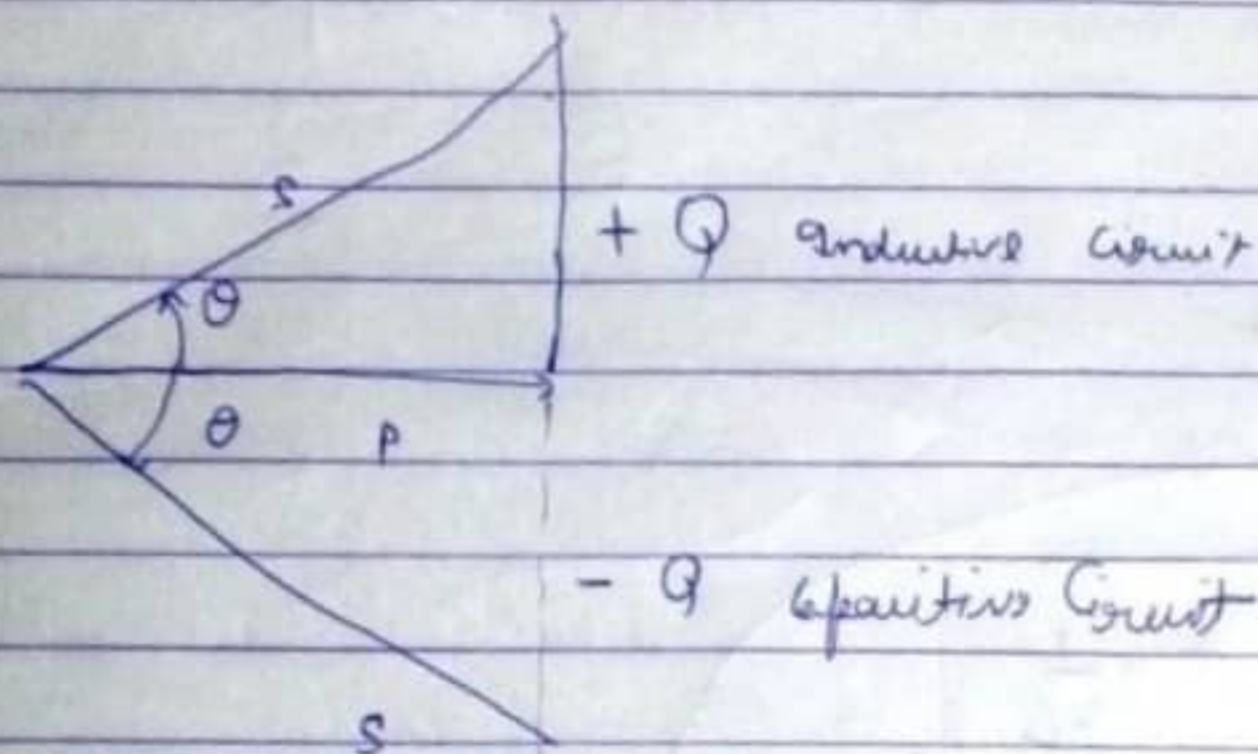
$$I_{r.m.s}^2 R \text{ and } Q = I_{r.m.s}^2 X$$



$$\cos \theta = \text{Power factor} = \frac{P}{S} = \cos (\theta_v - \theta_i)$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad f_0 = \frac{1}{2\pi \sqrt{LC}} \quad \rightarrow \text{Resonance}$$

Quality factor $Q_0 = \frac{\omega_0}{\Delta \omega}$

JATIN - 2K21/A12103

$$\text{Quality factor } Q_0 = \frac{W_0}{\Delta W} = \frac{\text{Max power energy stored}}{\text{Energy dissipated}} \quad \left. \vphantom{\frac{W_0}{\Delta W}} \right\} \text{ per cycle}$$

$$Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \left. \vphantom{\frac{1}{R} \sqrt{\frac{L}{C}}} \right\} \text{ Series circuit}$$

$$= \frac{R}{\sqrt{\frac{L}{C}}} \quad \rightarrow \text{Parallel}$$

$$\begin{aligned} \text{Lower Half Power freq: } & \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \\ \text{Upper } & \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \end{aligned}$$

Series

Just remember or try

$$\begin{aligned} W_1 = \text{lower} &= W_0 - \frac{1}{2} \Delta W \\ W_2 &= W_0 + \frac{1}{2} \Delta W \end{aligned}$$

Parallel RLC :

$$\frac{1}{R} \quad \frac{1}{\omega L} \quad \frac{1}{\omega C} \quad \frac{1}{2}$$

No jayega bas