

DC to DC Converters

Difference between 'Chopper' and 'Converter'

BUCK CHOPPER

$$V_o = \frac{t_{on}}{t_{on} + t_{off}}$$

V_s




S

$$t_{on} + t_{off}$$

V_s

XD

$$\Rightarrow V_o = \alpha V_s$$

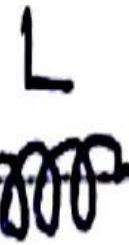

100007

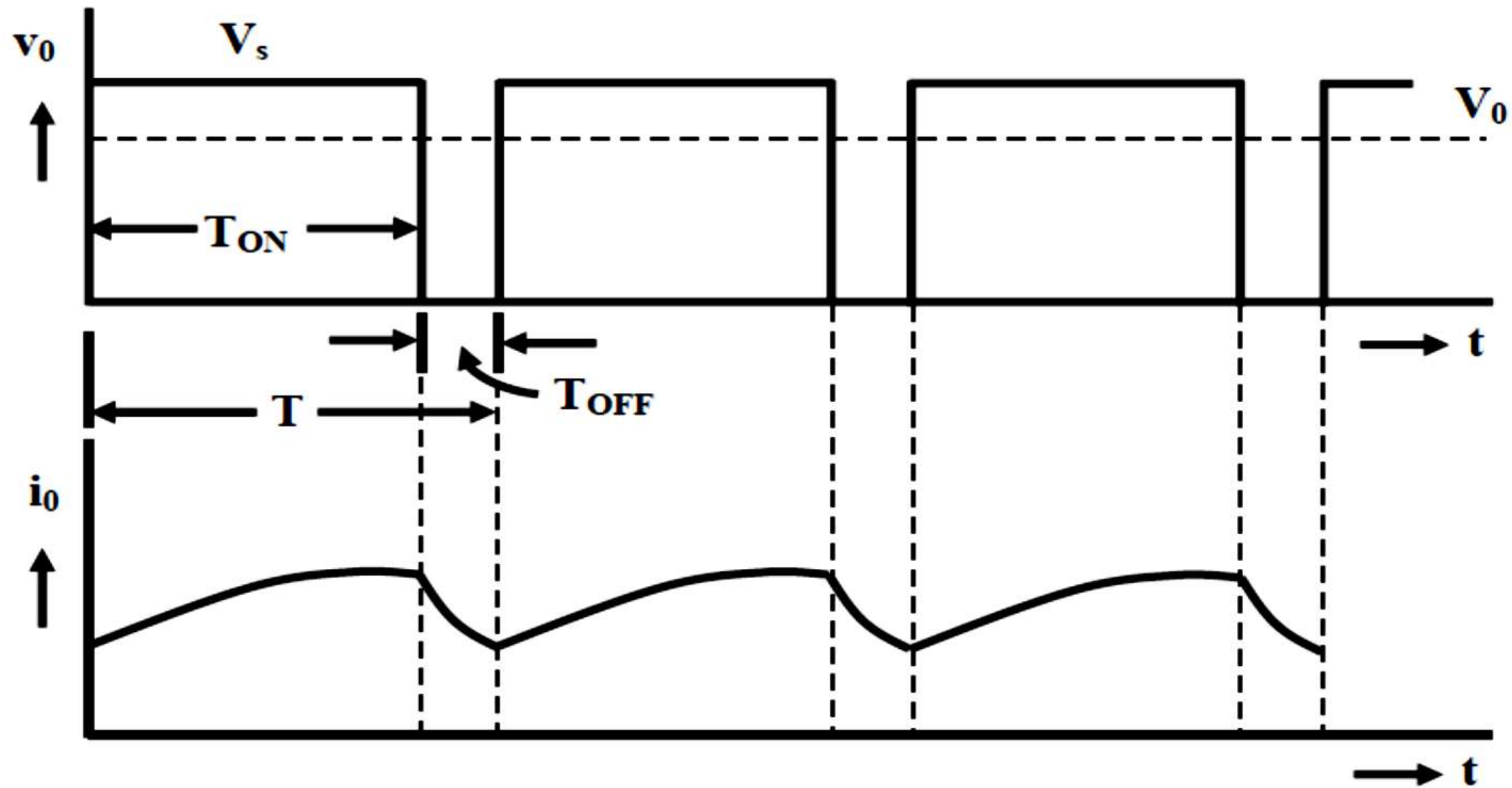


Fig. 17.1(b): Output voltage and current waveforms

BOOST CHOPPER

When 'S' is ON

$$V_L = V_S$$

When 'S' is OFF

$$V_S + V_L - V_o = 0$$

$$\Rightarrow V_L = V_o - V_S$$


$$V_S T_{on} = (V_o - V_S) T_{off}$$

$$\Rightarrow V_S T = V_o T_{off}$$

$$\Rightarrow \underline{V_o} = \frac{T}{T_{off}} V_S$$

$$\Rightarrow V_o = \frac{T}{T - T_{on}} V_S$$
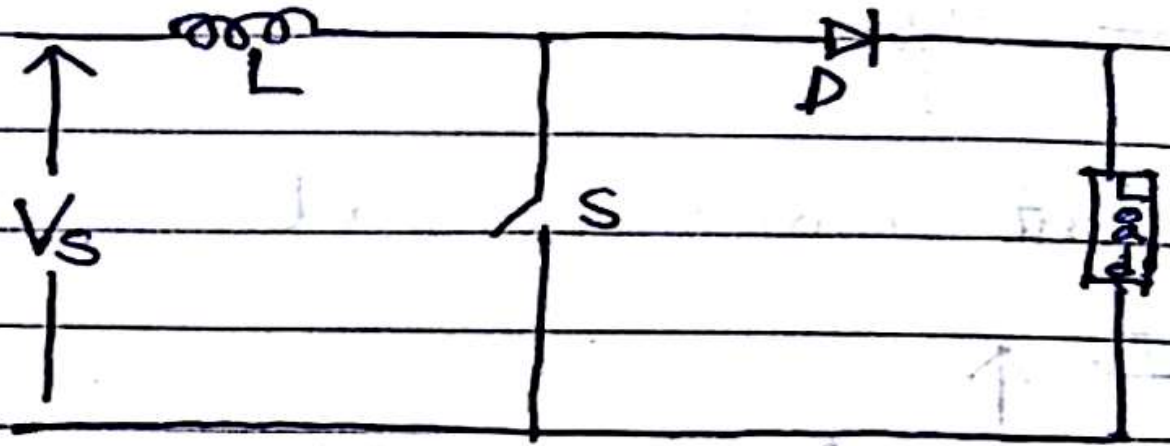
$$\Rightarrow V_o = \frac{1}{1 - \alpha} V_S$$



BUCK-BOOST CHOPPER

When 'S' is ON

$$V_L = V_s$$


When 'S' is OFF

$$V_L = -V_o$$


$$V_s T_{on} = -V_o T_{off}$$

$$\Rightarrow V_o = -V_s \frac{T_{on}}{T - T_{on}}$$


$$= -V_s \frac{\alpha}{1 - \alpha}$$

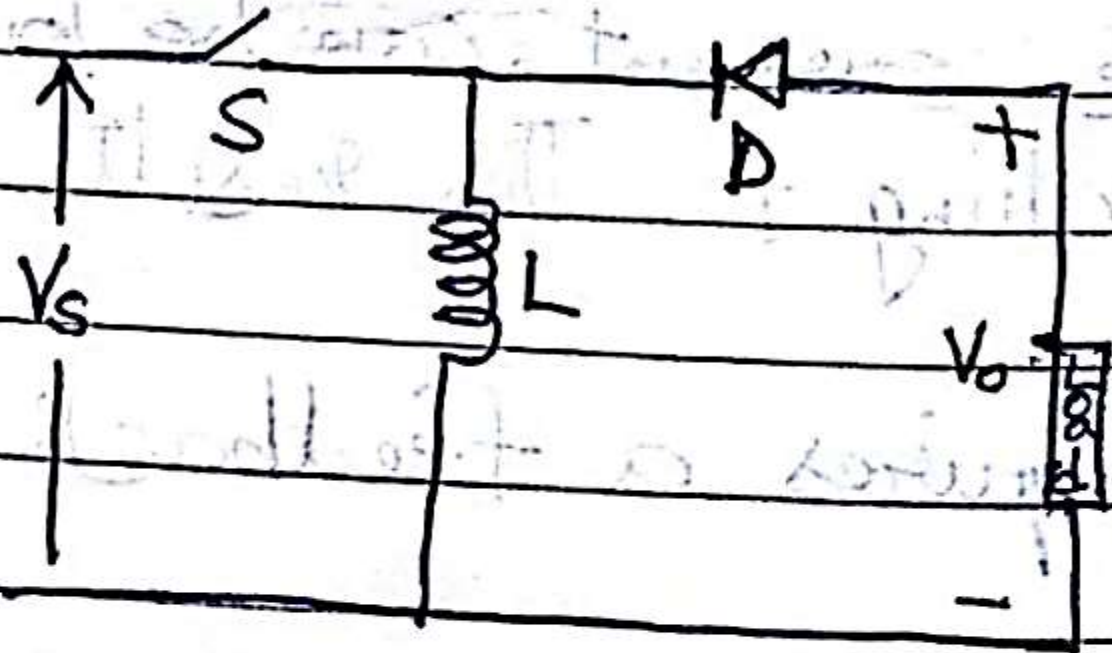

CUK CONVERTER

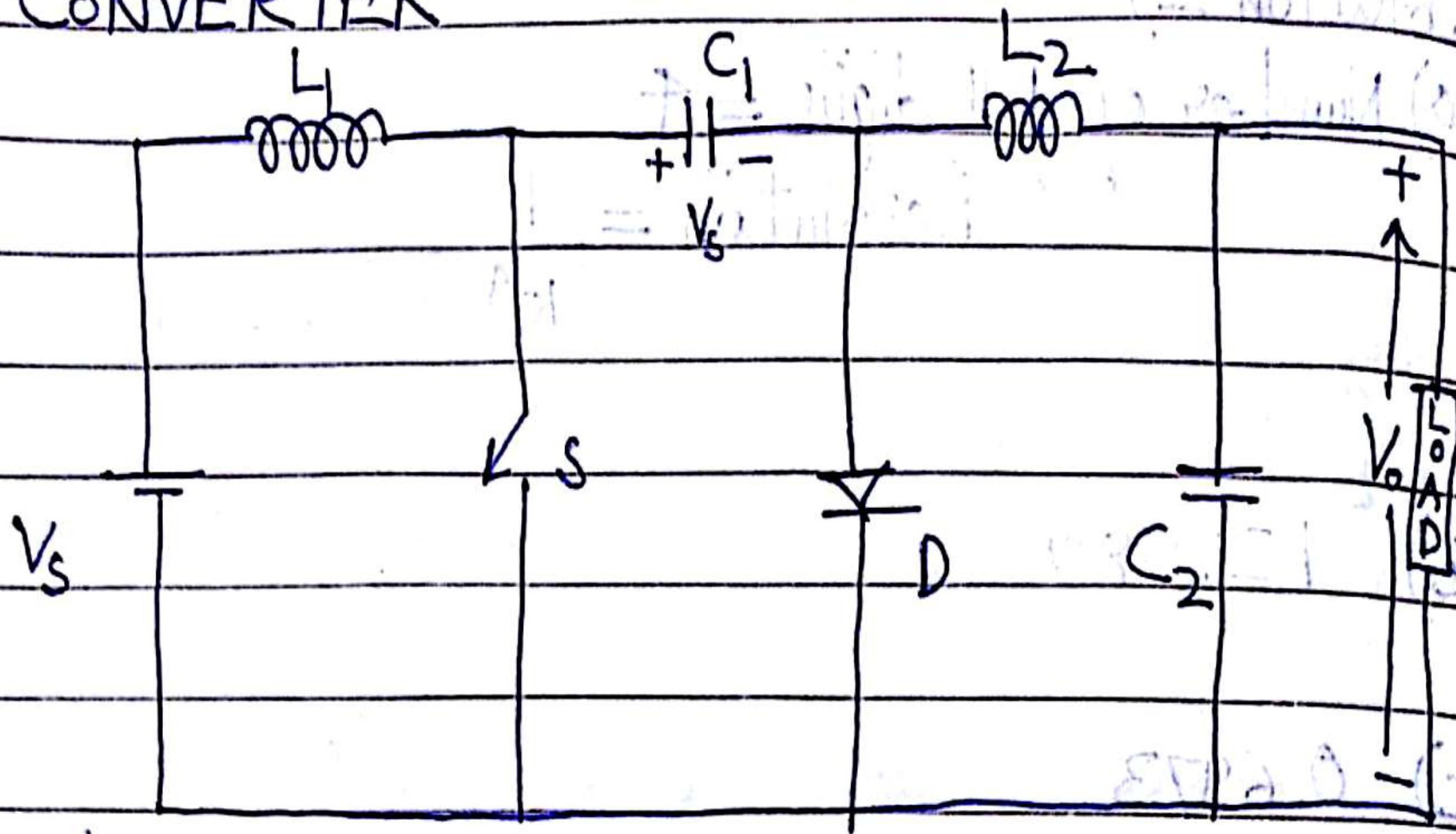


During ON

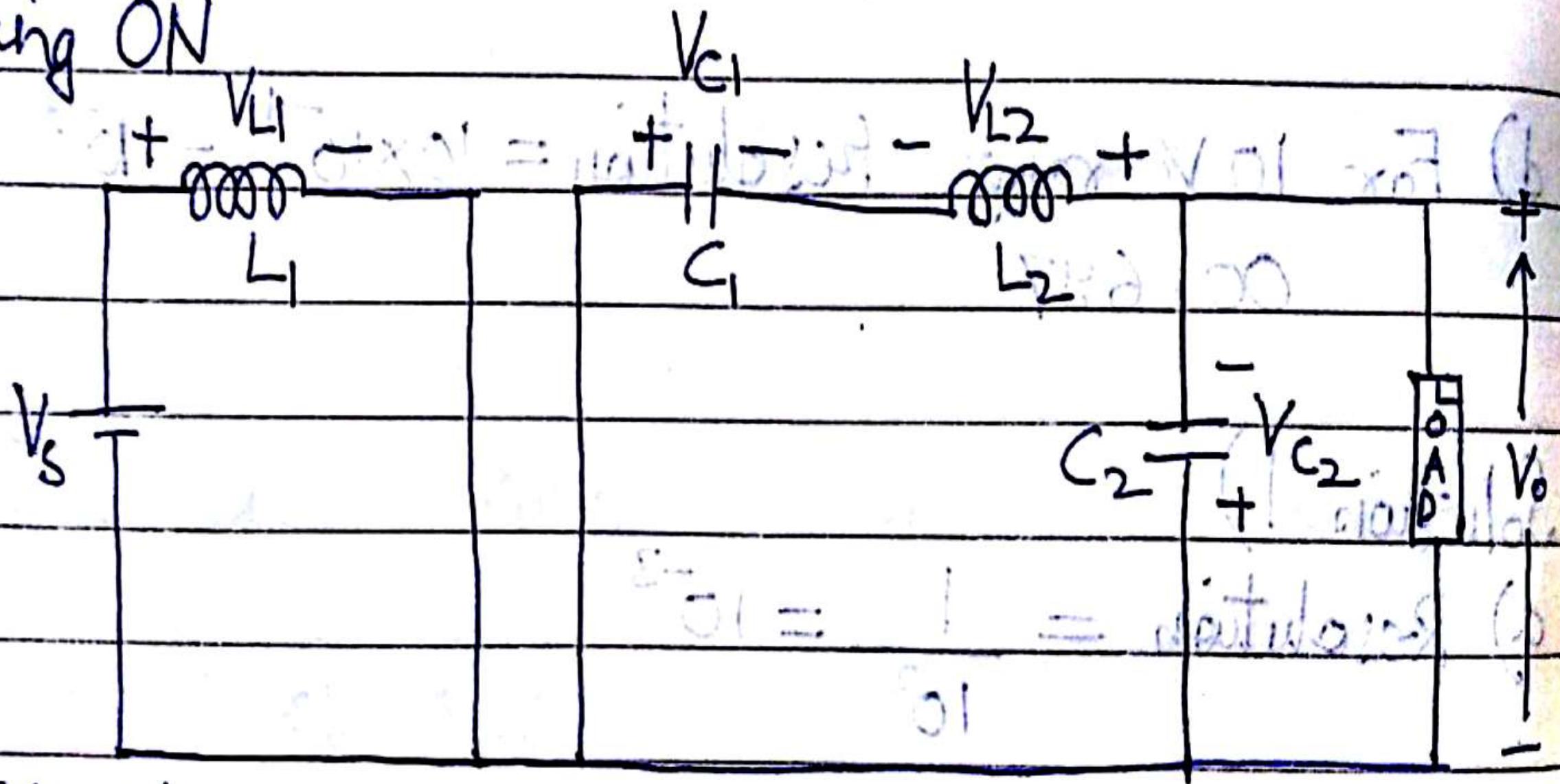

$$V_s = V_{L1}$$

$$V_{L2} = V_{C1} + V_o$$

During OFF

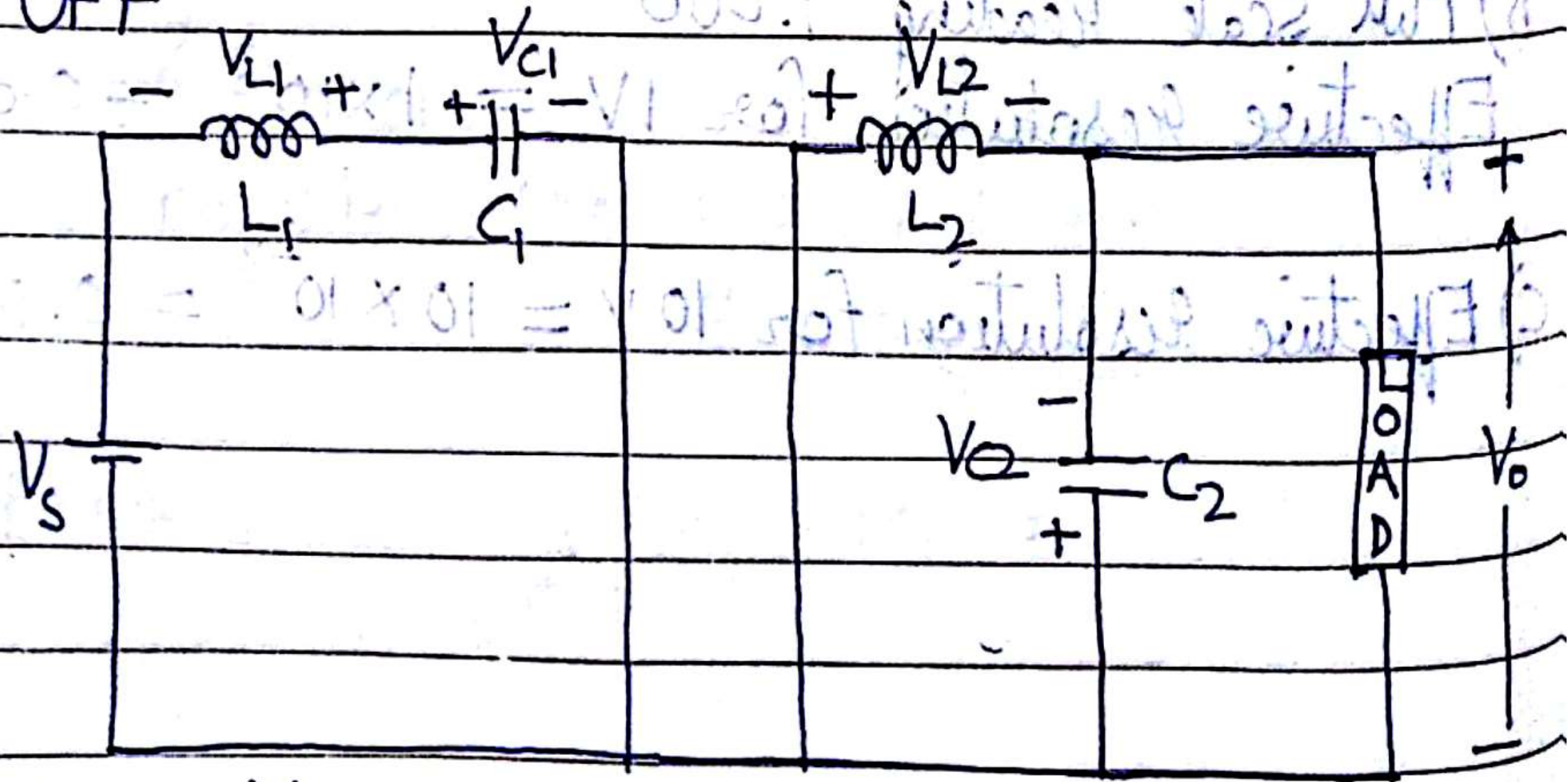

$$V_{L1} = V_{C1} - V_s$$

$$V_{L2} = -V_o$$

For L_1

$$V_s t_{on} = (V_{C1} - V_s) t_{off}$$

$$\Rightarrow V_s T = V_{C1} t_{off}$$

$$\Rightarrow V_{C1} = \frac{V_s T}{t_{off}}$$

$$\Rightarrow \frac{V_s T}{t_{off}} t_{on} + V_o T = 0$$

$$\Rightarrow V_s \frac{t_{on}}{t_{off}} + V_o = 0$$

$$\Rightarrow -V_s \frac{(t_{on})/T}{(T-t_{on})/T} = V_o$$

$$\Rightarrow V_o = -\left(\frac{D}{1-D}\right) V_s$$



For L_2

$$(V_{C1} + V_o) t_{on} = -V_o t_{off}$$



$$V_{C1} t_{on} + V_o T = 0$$

Quadrant based Classification



1) I Quad / Type A

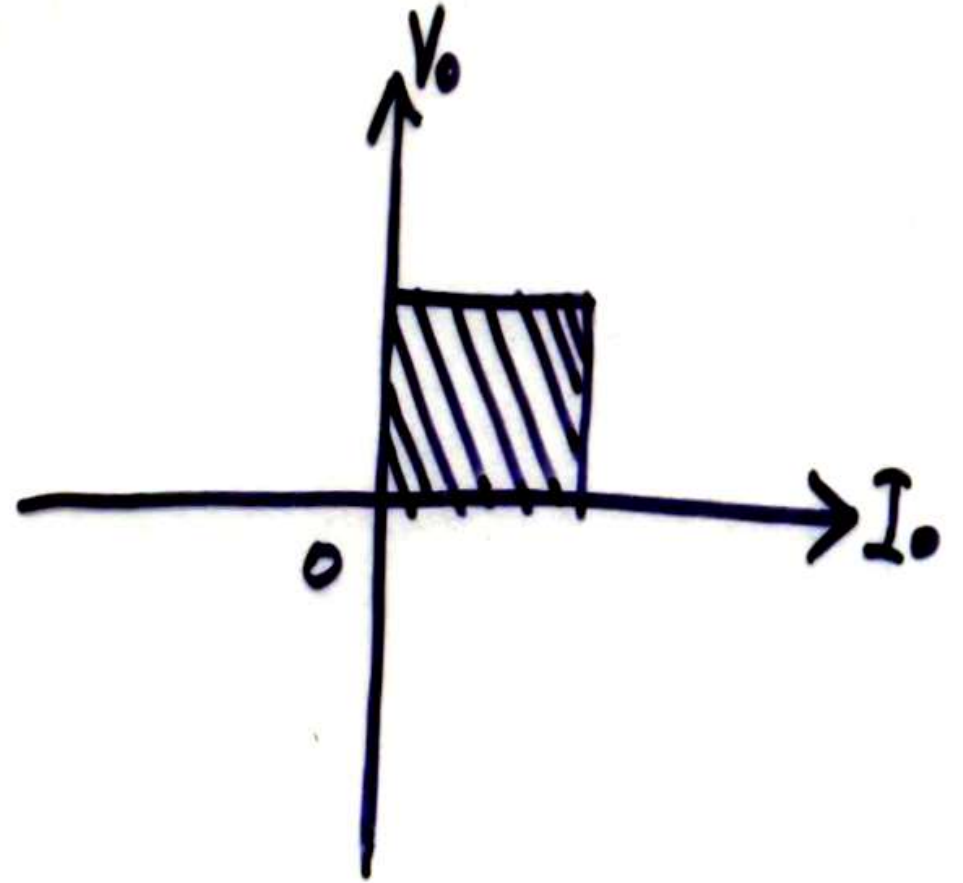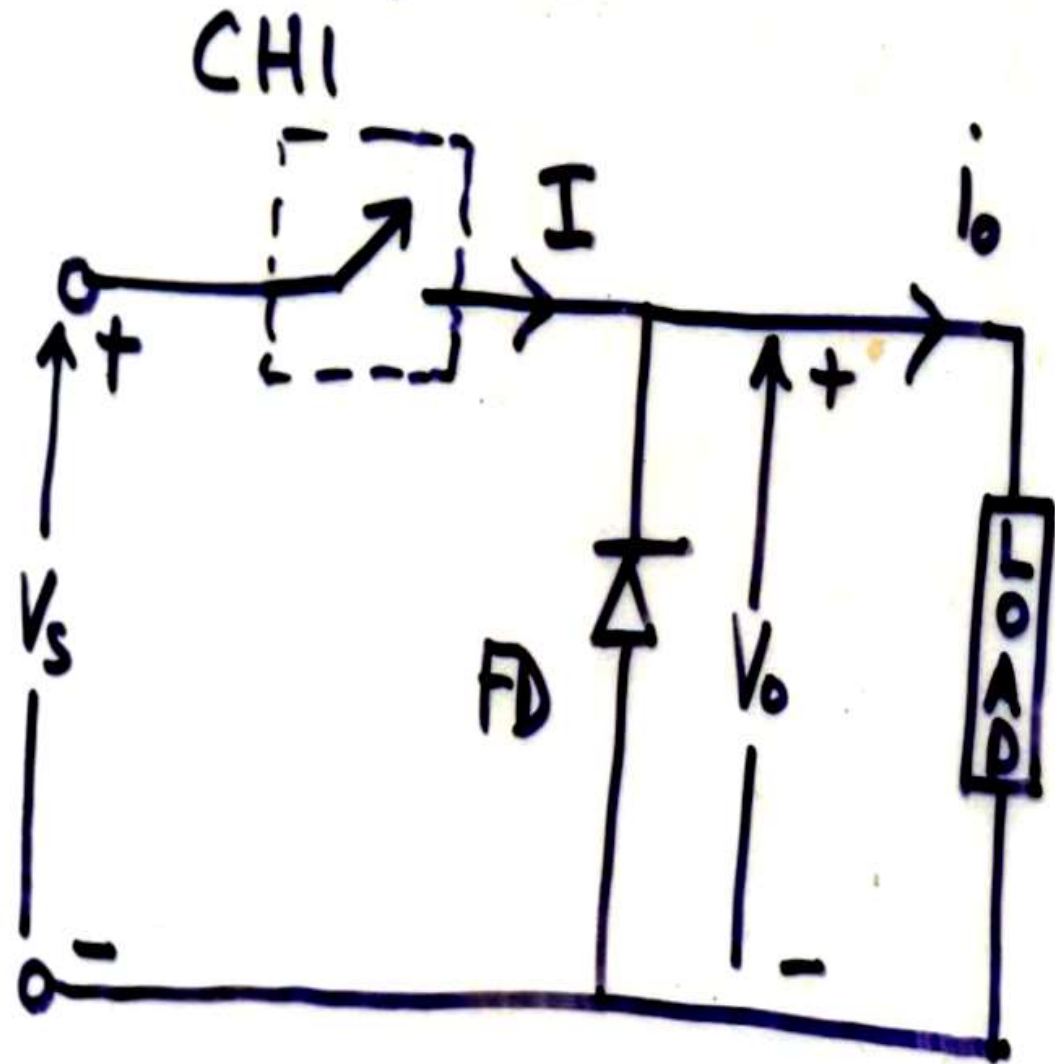



(2) II Quad/Type B

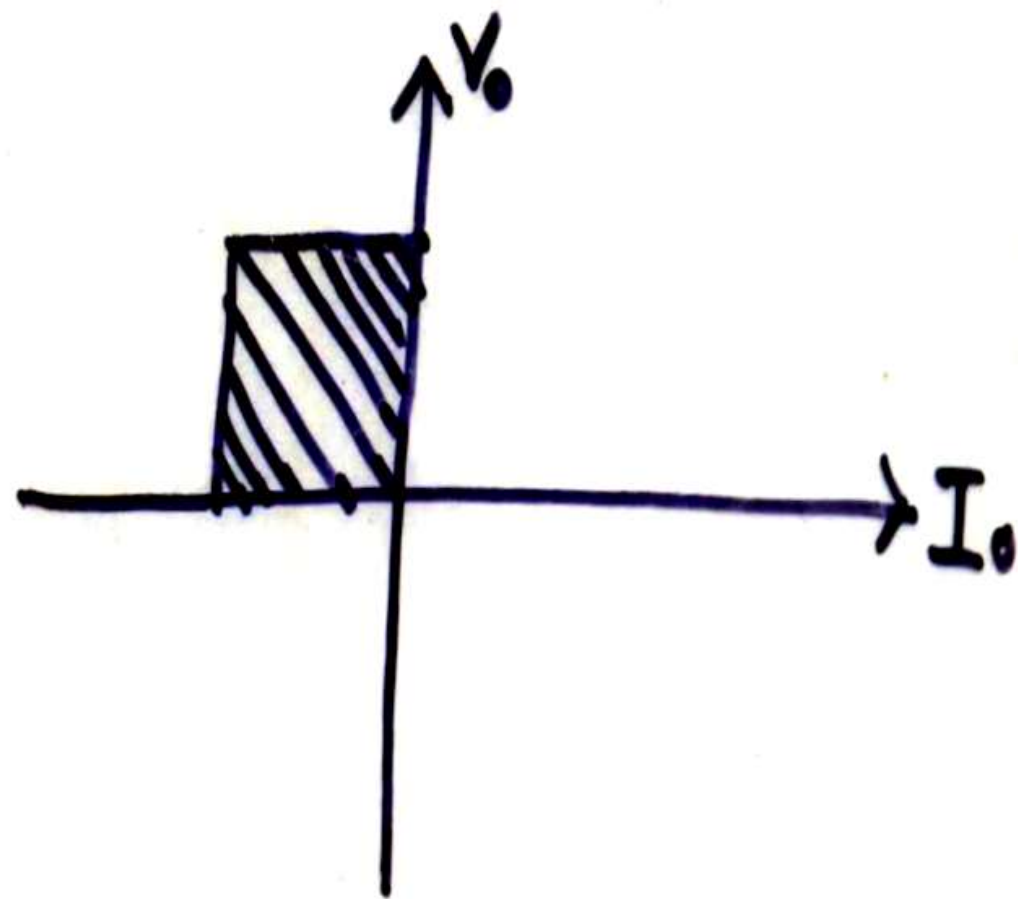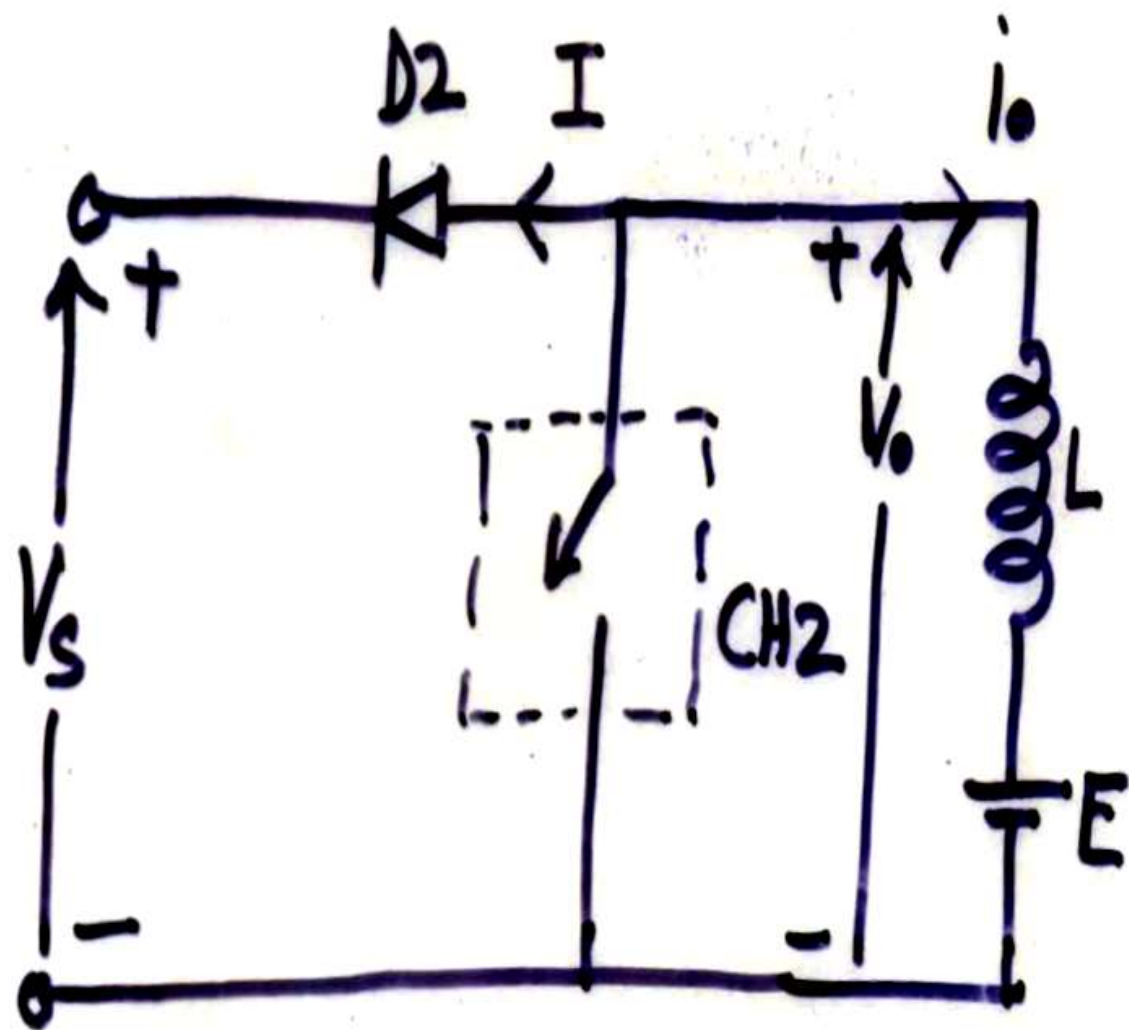


3) 2 Quad Type A/c

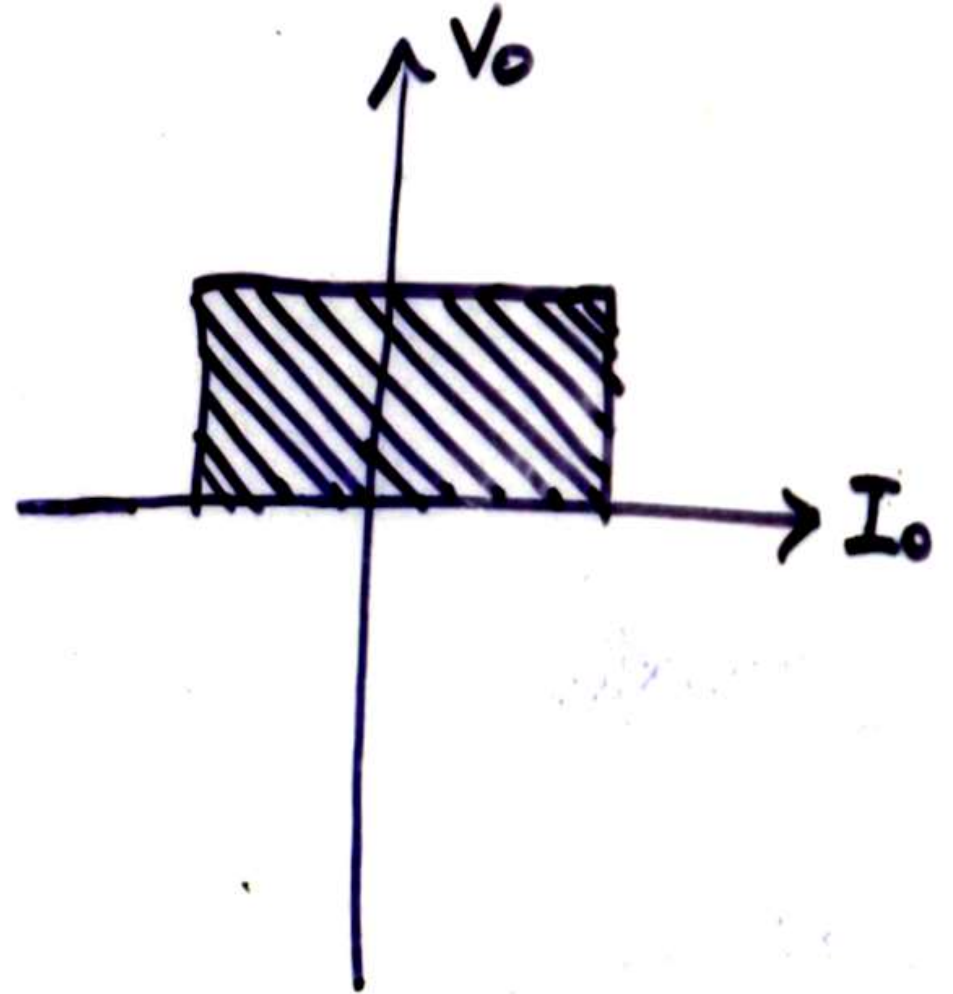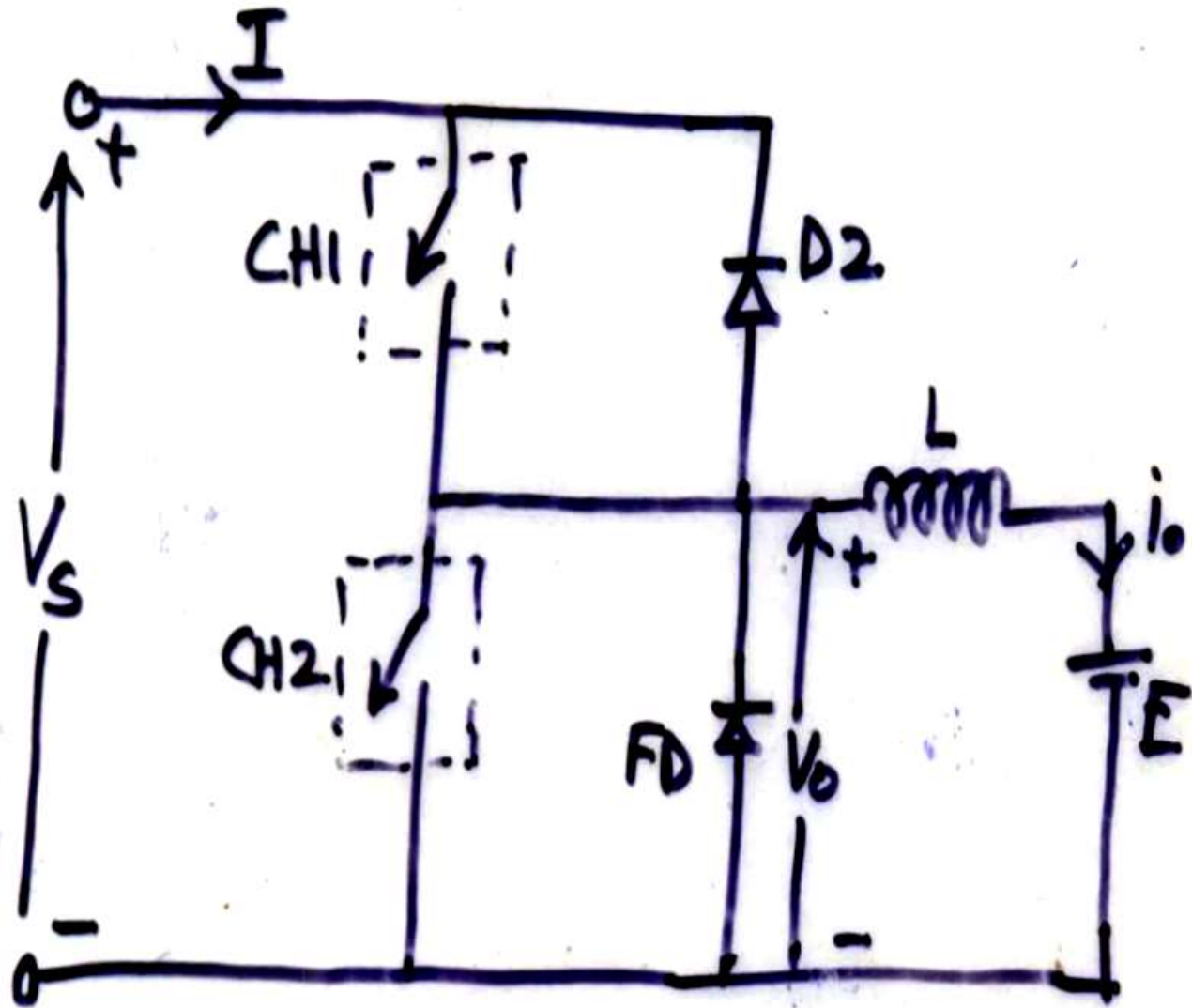

2 Quad Type B/D

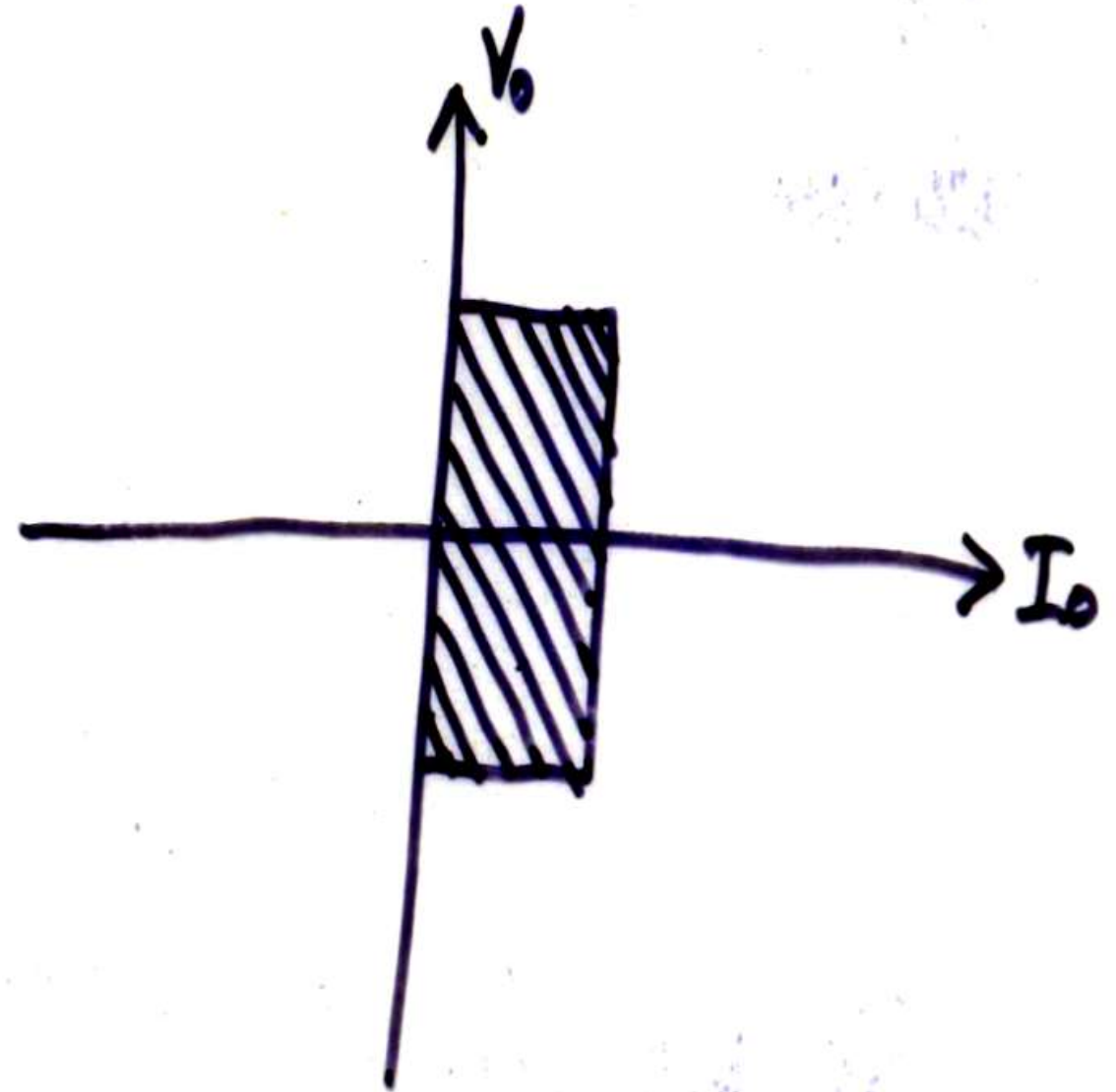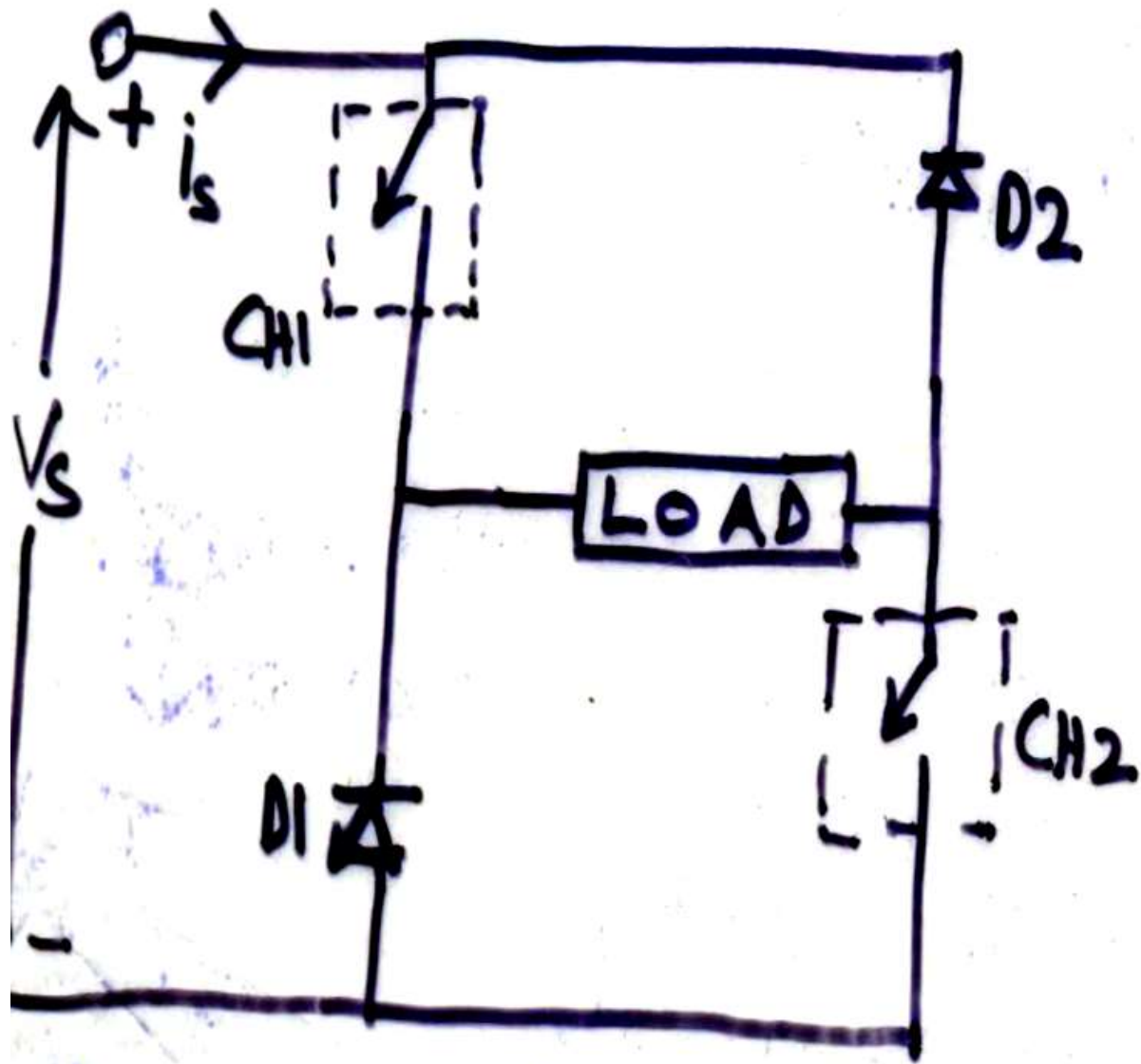

(5) 4 Quad Type E

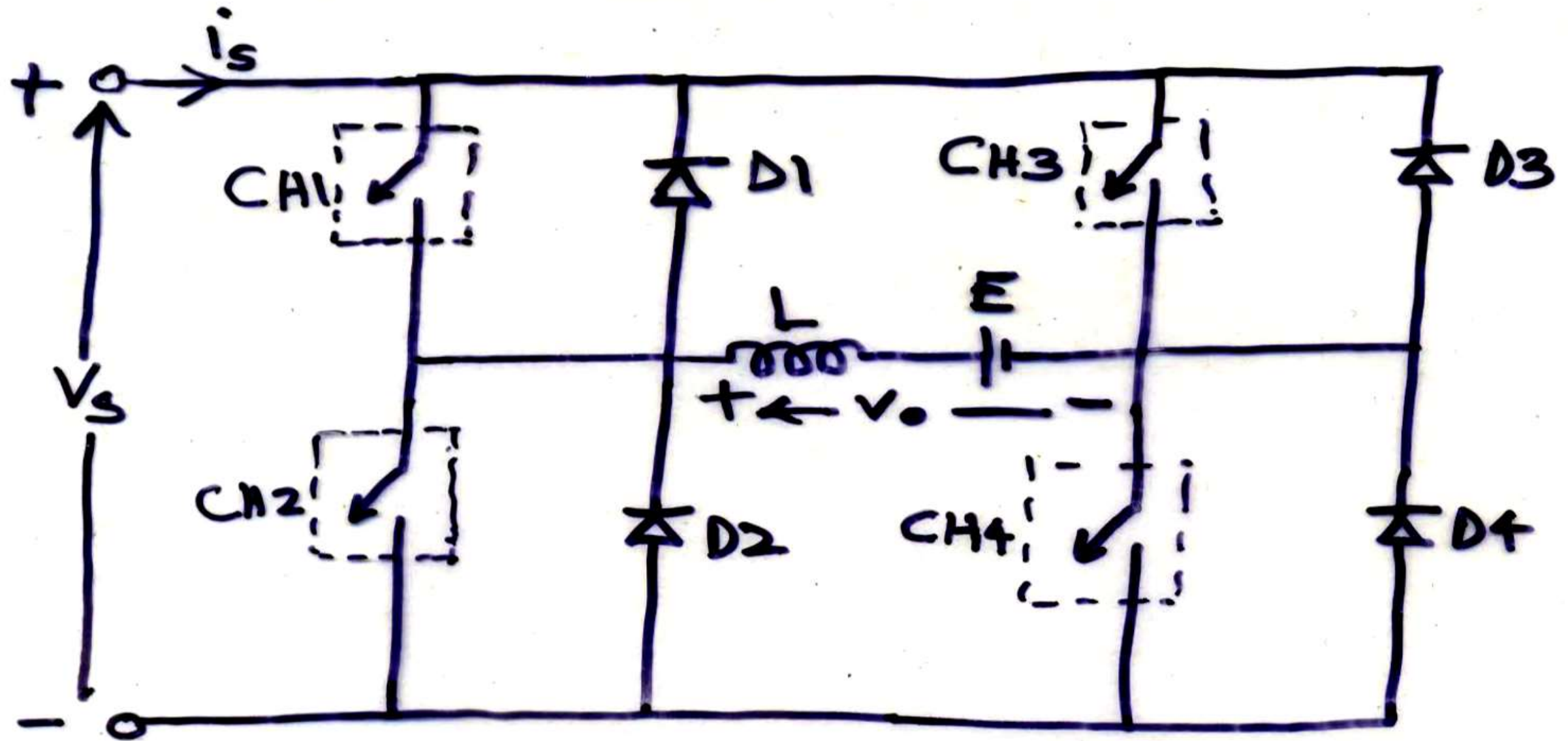

(5) 4 Quad Type E

